

---

# Ch 7. Finite State Machines

---

# Finite State Machines

- Sequential circuits
  - primitive sequential elements
  - combinational logic
- Models for representing sequential circuits
  - finite-state machines (Moore and Mealy)
- Basic sequential circuits revisited
  - shift registers
  - counters
- Design procedure
  - state diagrams
  - state transition table
  - next state functions

# Counters

- Sequential logic circuit that proceed through a well defined sequence of states
  - 3-bit binary up-counter
    - 000, 001, 010, 011, 100, 101, 110, 111; and return to 000
  - Decade counter
    - 0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000, 1001; and return to 0000 (binary-coded decimal)
  - Gray-code counter
    - Only a single bit of the counter changes at a time to avoid circuit hazard
    - 0000, 0001, 0011, 0010, 0110, 0111, 0101, 0100, 1100, 1101, 1111, 1110, 1010, 1011, 1001, 1000 and repeat

# Counters (cont'd)

- Ring counters
  - Shift registers can also be used as a kind of primitive counter
  - Uses minimal hardware for its implementation
  - Not efficient state encoding

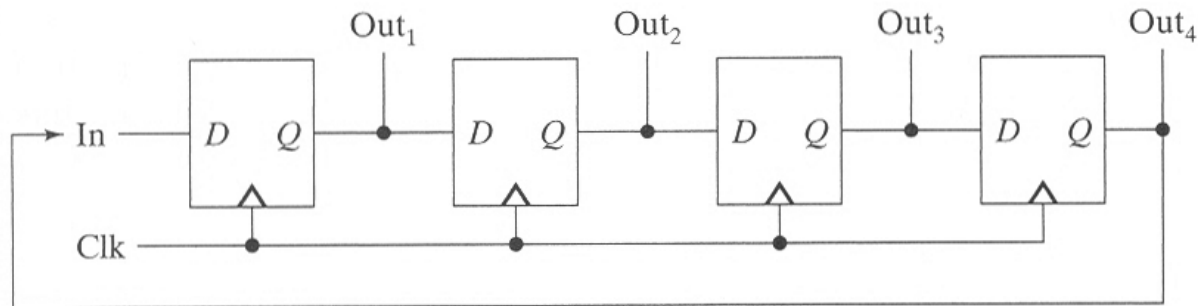


Figure 7.1 Four-bit simple ring counter.

# Counters (cont'd)

- Johnson counter (aka Mobius counter)
  - Requires only one inverter more than the basic ring counter
  - Can sequence through twice as many states

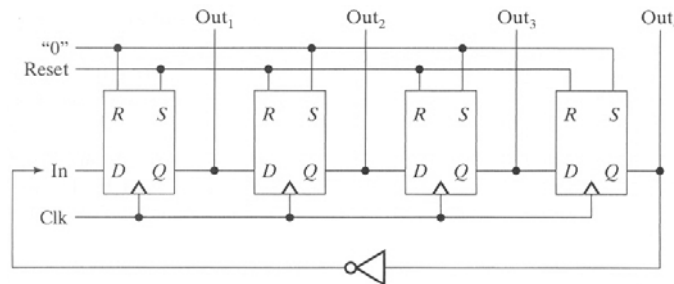


Figure 7.2 Four-bit Johnson counter.


 


Figure 7.3 Timing waveforms for 4-bit Johnson counter.
 
# Counter Design Procedure

- 3-bit binary up-counter
  - Describe state transition diagram and table



	Present State			Next State			
	C	B	A	C+	B+	A+	
0	0	0	0	0	0	1	1
1	0	0	1	0	1	0	2
2	0	1	0	0	1	1	3
3	0	1	1	1	0	0	4
4	1	0	0	1	0	1	5
5	1	0	1	1	1	0	6
6	1	1	0	1	1	1	7
7	1	1	1	0	0	0	0

Figure 7.4 State transition diagram and table for a 3-bit binary up-counter.

# Counter Design Procedure (cont'd)

- 3-bit binary up-counter
  - Design combinational logic through K-map methods



 


Figure 7.5 K-maps for up-counter flip-flops.

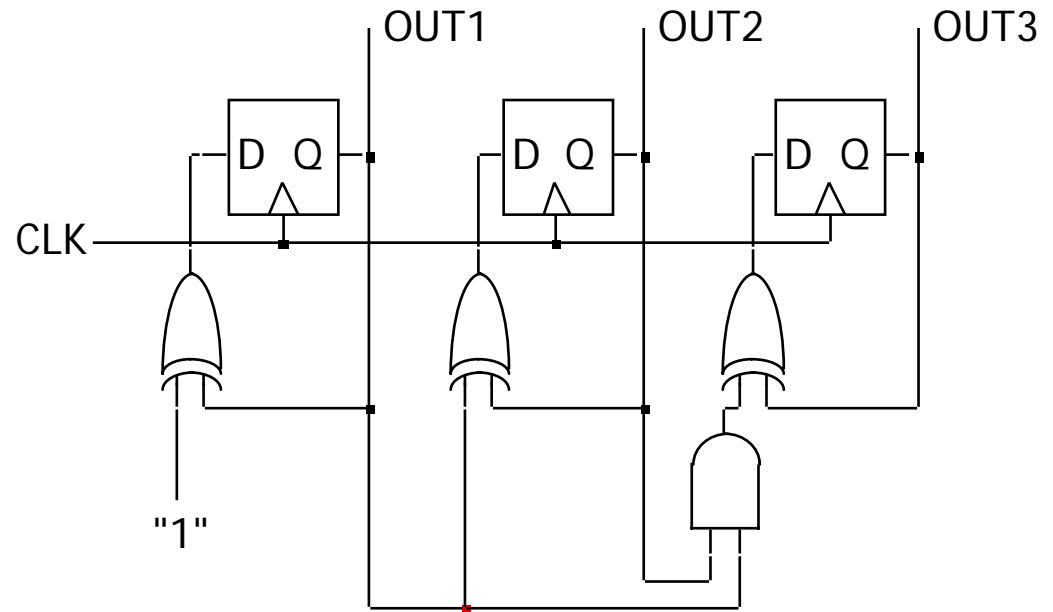
 
# More complex counter example

- Complex counter
  - repeats 5 states in sequence
  - not a binary number representation
- Step 1: derive the state transition diagram
  - count sequence: 000, 010, 011, 101, 110
- Step 2: derive the state transition table from the state transition diagram






Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	—	—	—
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	—	—	—
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	—	—	—

note the don't care conditions that arise from the unused state codes


   
# More complex counter example (cont'd)

- Step 3: K-maps for next state functions



$$C+ \leq A$$



$$B+ \leq B' + A'C'$$

$$A+ \leq BC'$$

Present State			Next State		
$C$	$B$	$A$	$C+$	$B+$	$A+$
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0
  
# Self-starting counters

- Start-up states
  - at power-up, counter may be in an unused or invalid state
  - designer must guarantee that it (eventually) enters a valid state
- Self-starting solution
  - design counter so that invalid states eventually transition to a valid state
  - may limit exploitation of don't cares



# Self-starting counters (cont'd)


- Re-deriving state transition table from don't care assignment

		C	
C+		0	0
	A	1	1
		B	

		C	
B+		1	1
	A	0	0
		B	


		C	
A+		0	1
	A	0	0
		B	

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

 

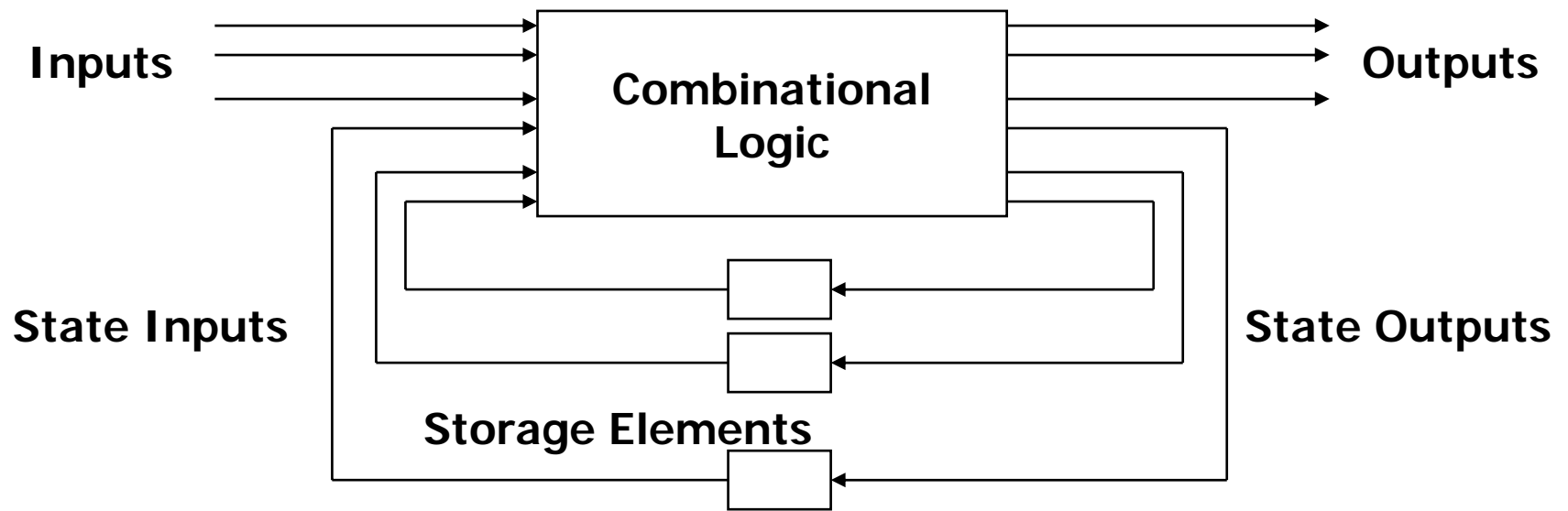
# Abstraction of state elements

- Divide circuit into combinational logic and state
- Localize the feedback loops and make it easy to break cycles
- Implementation of storage elements leads to various forms of sequential logic



 
# Finite state machine representations

- States: determined by possible values in sequential storage elements
- Transitions: change of state
- Clock: controls when state can change by controlling storage elements
  
- Sequential logic
  - sequences through a series of states
  - based on sequence of values on input signals
  - clock period defines elements of sequence


 
# Example finite state machine diagram



- Combination lock from introduction to course
  - 5 states
  - 5 self-transitions
  - 6 other transitions between states
  - 1 reset transition (from all states) to state S1



# Can any sequential system be represented with a state diagram?
  
## ■ Shift register

- input value shown on transition arcs
- output values shown within state node




# FSM design procedure

- Step 1. Understand the problem
  - Describe a finite state machine in an unambiguous manner
- Step 2. Obtain an abstract representation of the FSM
  - State diagram
- Step 3. Perform state minimization
  - Certain paths through the state machine can be eliminated
- Step 4. Perform state assignment
  - Counter: the state and the output are identical
  - General FSM: good state encoding often leads to a simpler implementation
- Step 5. Implement the finite state machine
  - Using Boolean equations or K-maps



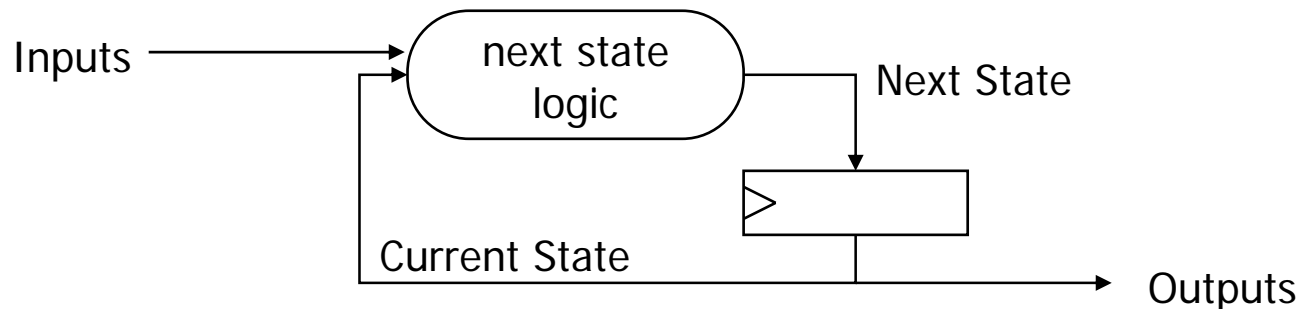
# Counter/shift-register model

- Values stored in registers (flip-flops) represent the state of the circuit
- Next state is function of current state and inputs
- **Outputs are the state**
- Combinational logic implements the function for next state




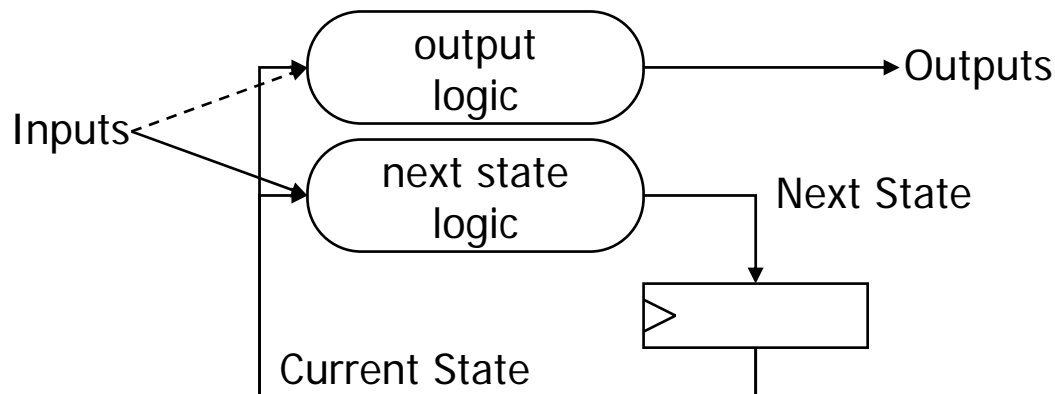
# General state machine model

- Values stored in registers represent the state of the circuit
- Next state is function of current state and inputs
- **Outputs are**
  - **function of current state and inputs (Mealy machine)**
  - **function of current state only (Moore machine)**
- Combinational logic implements the functions for next state and outputs


 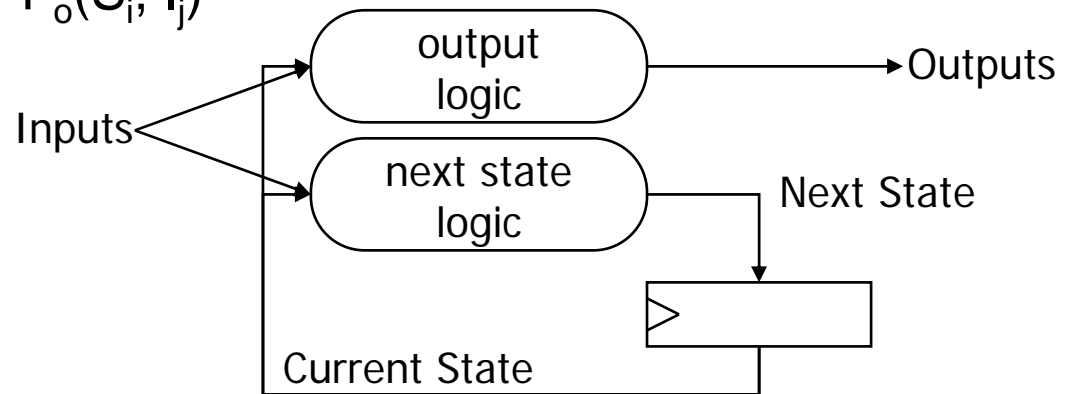
# State machine model (cont'd)

- States:  $S_1, S_2, \dots, S_k$
- Inputs:  $I_1, I_2, \dots, I_m$
- Outputs:  $O_1, O_2, \dots, O_n$
- Transition function:  $F_s(S_i, I_j)$
- Output function:  $F_o(S_i)$  or  $F_o(S_i, I_j)$




# Comparison of Mealy and Moore machines


- Mealy machines tend to have less states
  - different outputs on arcs ( $n^2$ ) rather than states ( $n$ )
- Moore machines are safer to use
  - outputs change at clock edge (always one cycle later)
  - in Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected – asynchronous feedback may occur if one isn't careful
- Mealy machines react faster to inputs
  - react in same cycle – don't need to wait for clock
  - in Moore machines, more logic may be necessary to decode state into outputs – more gate delays after clock edge

# Comparison of Mealy and Moore machines (cont'd)


## ■ Moore

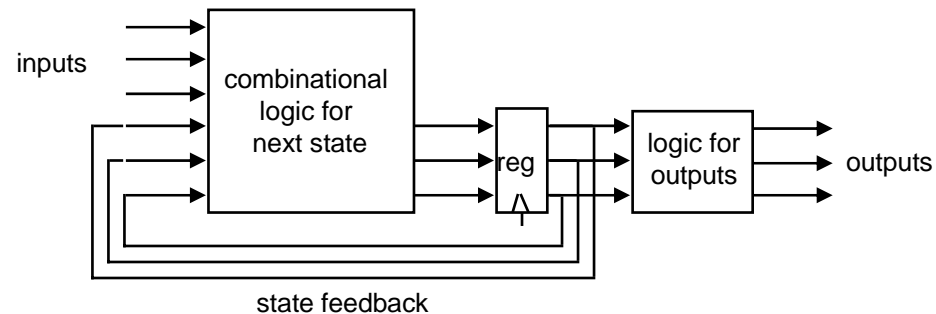

## ■ Mealy

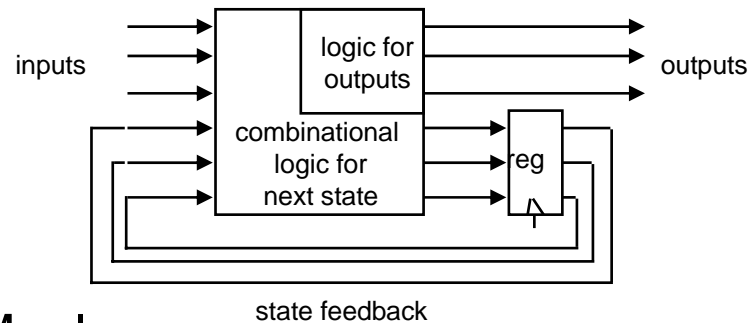


## ■ Synchronous Mealy

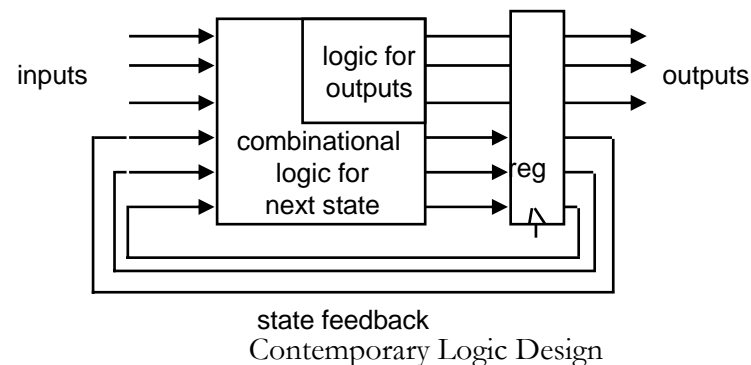
 
# Specifying outputs for a Moore machine


- Output is only function of state
  - specify in state bubble in state diagram
  - example: sequence detector for 01 or 10



reset	input	current state	next state	output
1	–	–	A	
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	1
 
# Specifying outputs for a Mealy machine


- Output is function of state and inputs
  - specify output on transition arc between states
  - example: sequence detector for 01 or 10



reset	input	current state	next state	output
1	–	–	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0
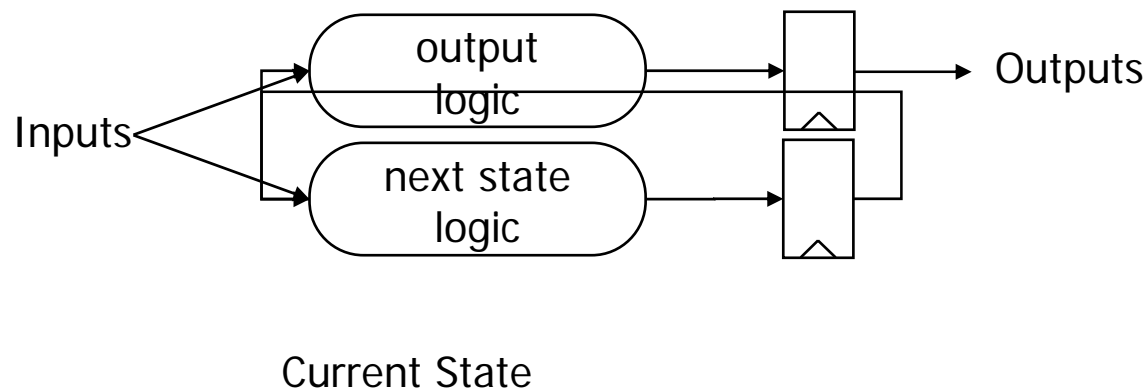
# Registered Mealy machine (really Moore)


- Synchronous (or registered) Mealy machine
  - registered state AND outputs
  - avoids 'glitchy' outputs
  - easy to implement in PLDs
- Moore machine with no output decoding
  - outputs computed on transition to next state rather than after entering
  - view outputs as expanded state vector





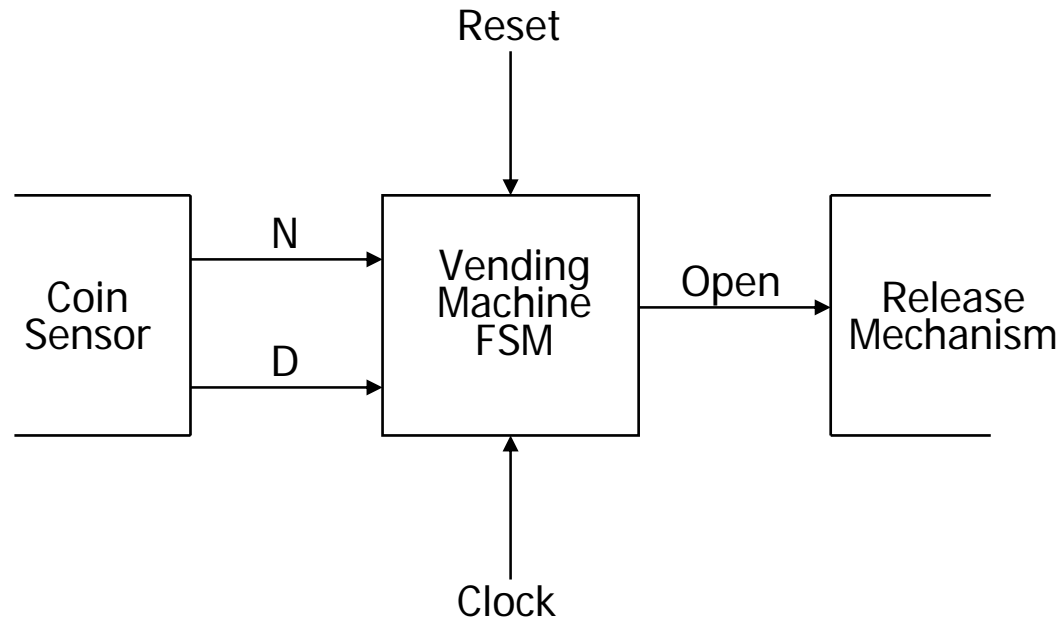
# Example: vending machine

- Release item after 15 cents are deposited
- Single coin slot for dimes, nickels
- No change



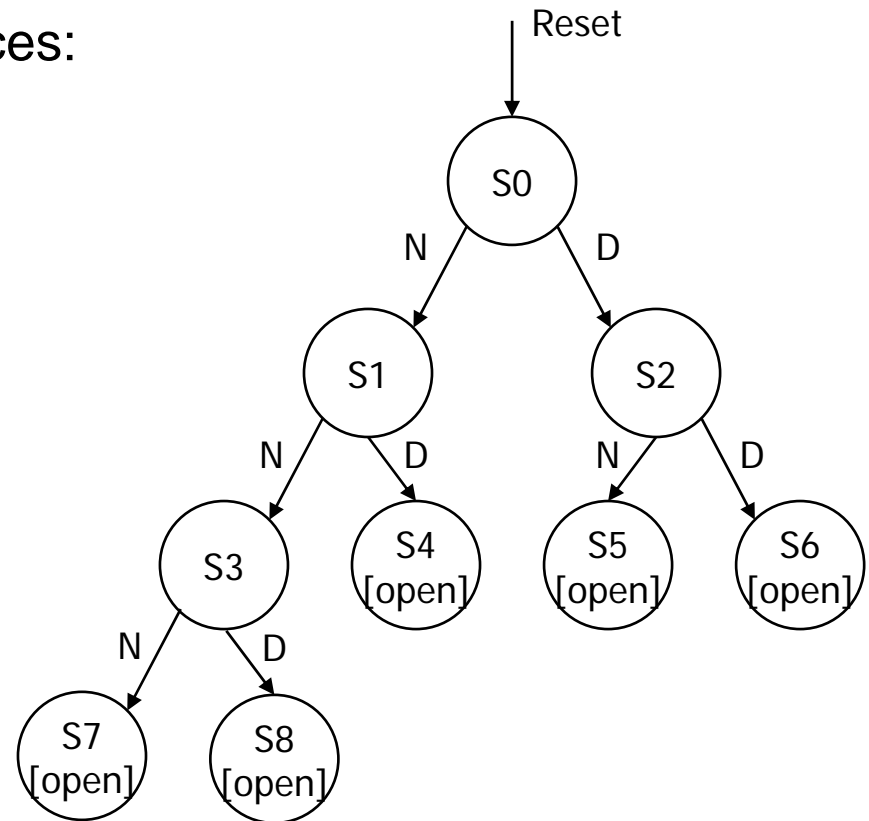
# Example: vending machine (cont'd)

- Suitable abstract representation
  - tabulate typical input sequences:
    - 3 nickels
    - nickel, dime
    - dime, nickel
    - two dimes
  - draw state diagram:
    - inputs: N, D, reset
    - output: open chute
  - assumptions:
    - assume N and D asserted for one cycle
    - each state has a self loop for  $N = D = 0$  (no coin)


 
# Example: vending machine (cont'd)

- Minimize number of states - reuse states whenever possible



present state	inputs		next state	output open
	D	N		
0¢	0	0	0¢	0
5¢	0	1	5¢	0
	1	0	10¢	0
	1	1	—	—
	0	0	5¢	0
10¢	0	1	10¢	0
	1	0	15¢	0
	1	1	—	—
	0	0	10¢	0
15¢	0	1	15¢	0
	1	0	15¢	0
	1	1	—	—
15¢	—	—	15¢	1

symbolic state table



# Example: vending machine (cont'd)

- Uniquely encode states

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	-	-	-
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	-	-	-
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
		1	1	-	-	-
1	1	-	-	1	1	1

# Example: Moore implementation

## ■ Mapping to logic

  

$$D0 = Q0' N + Q0 N' + Q1 N + Q1 D$$


$$D1 = Q1 + D + Q0 N$$

$$OPEN = Q1 Q0$$

# Equivalent Mealy and Moore state diagrams


- Moore machine

- outputs associated with state

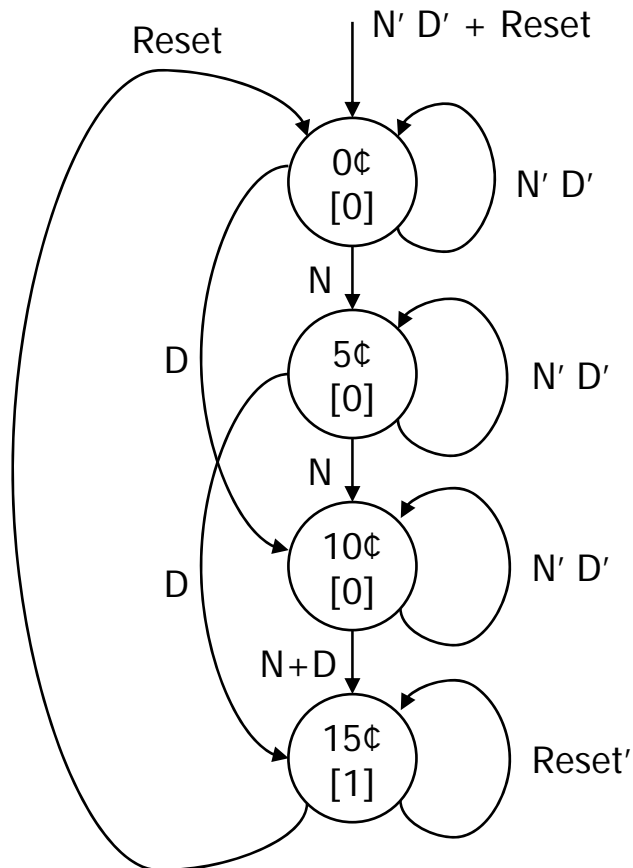


- Mealy machine

- outputs associated with transitions

 

# Example: Mealy implementation

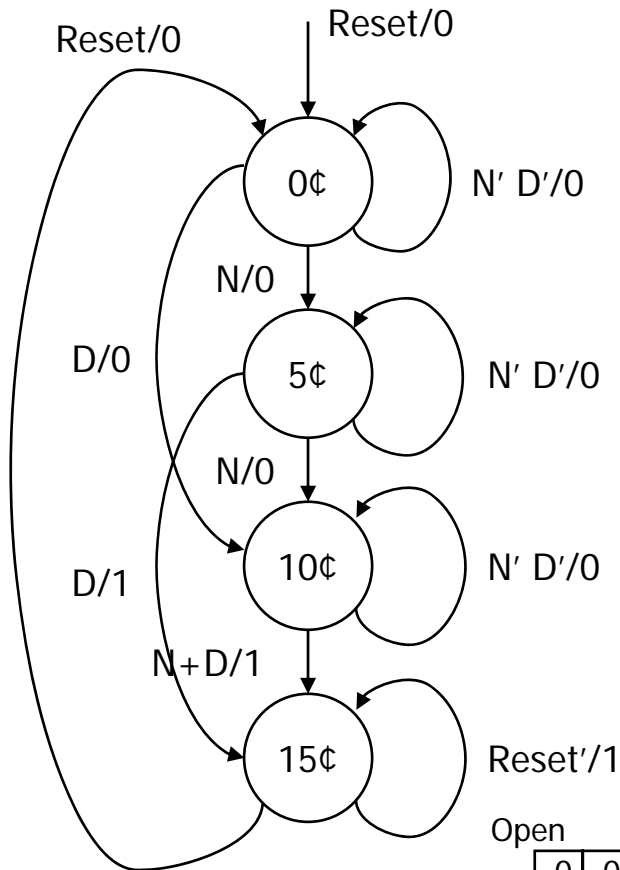

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	-	-	-
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	1
		1	1	-	-	-
1	0	0	0	1	0	0
		0	1	1	1	1
		1	0	1	1	1
		1	1	-	-	-
1	1	-	-	1	1	1

Open	Q1			
	0	0	1	0
D	0	0	1	0
	0	0	1	1
	X	X	1	X
	0	1	1	1

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$

$$OPEN = Q1Q0 + Q1N + Q1D + Q0D$$


# Example: Mealy implementation

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$

$$\text{OPEN} = Q1Q0 + Q1N + Q1D + Q0D$$


 
make sure OPEN is 0 when reset  
– by adding AND gate





 
 
# Vending machine: Moore to synch. Mealy

- OPEN = Q1Q0 creates a combinational delay after Q1 and Q0 change in Moore implementation
- This can be corrected by retiming, i.e., move flip-flops and logic through each other to improve delay
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$   
 $= Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$
- Implementation now looks like a synchronous Mealy machine
  - it is common for programmable devices to have FF at end of logic



  
# Vending machine: Mealy to synch. Mealy

- $OPEN.d = Q1Q0 + Q1N + Q1D + Q0D$
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$   
 $= Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$






Open.d		Q1		
		Q1	Q0	
D	0	0	1	0
	0	0	1	1
	1	0	1	1
	0	1	1	1

Open.d		Q1		
		Q1	Q0	
D	0	0	1	0
	0	0	1	1
	X	X	1	X
	0	1	1	1

 

  
 
# Mealy and Moore examples

- Recognize  $A, B = 0, 1$ 
  - Mealy or Moore?



 
 
# Mealy and Moore examples (cont'd)

- Recognize  $A, B = 1, 0$  then  $0, 1$ 
  - Mealy or Moore?


  
# Example: reduce-1-string-by-1

- Remove one 1 from every string of 1s on the input



# Finite state machines summary

- Models for representing sequential circuits
  - abstraction of sequential elements
  - finite state machines and their state diagrams
  - inputs/outputs
  - Mealy, Moore, and synchronous Mealy machines
- Finite state machine design procedure
  - deriving state diagram
  - deriving state transition table
  - determining next state and output functions
  - implementing combinational logic