

2007 Fall: Electronic Circuits 2

CHAPTER 10

Digital CMOS Logic Circuits

Deog-Kyoon Jeong

dkjeong@snu.ac.kr

School of Electrical Engineering
Seoul National University

Introduction

- ◆ In this chapter, we will be covering...
 - Digital Circuit Design
 - Design and Performance Analysis of the CMOS Inverter

10.1 Digital Circuit Design: An Overview

◆ Digital IC technologies and logic-circuit families

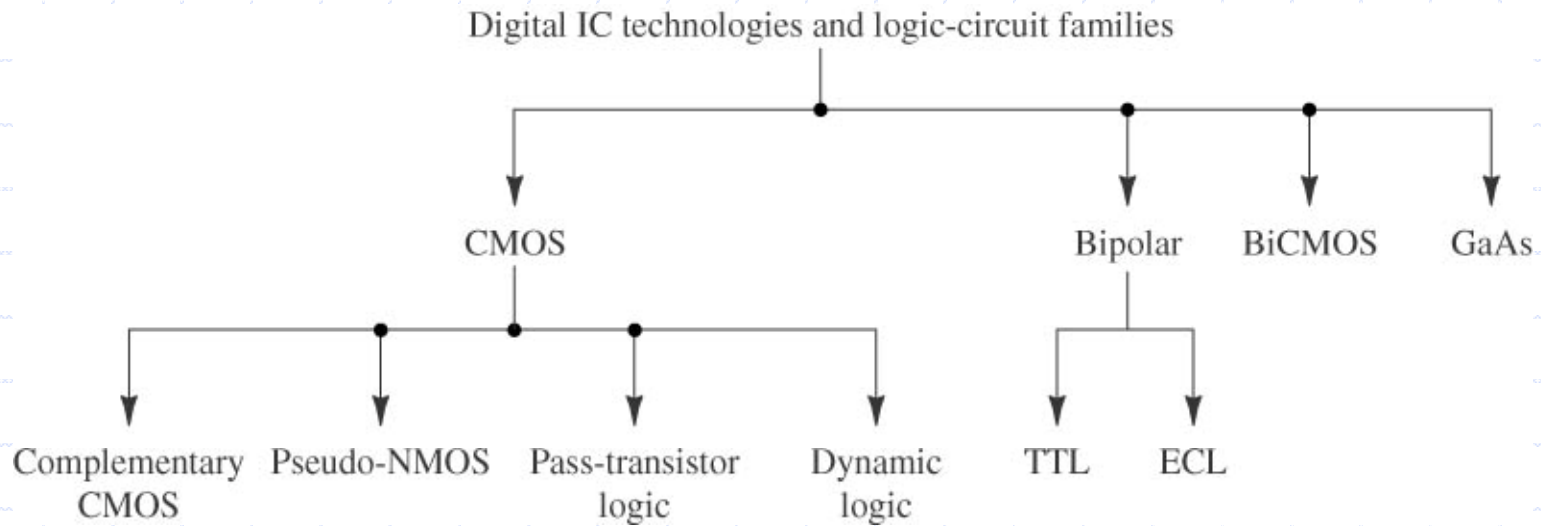


Figure 10.1 Digital IC technologies and logic-circuit families.

10.1 Digital Circuit Design: An Overview

- 10.1.1 Digital IC Technologies and Logic-Circuit Families

◆ Brief remarks of four technology

■ CMOS

- ◆ Low static power dissipation.
- ◆ High input impedance for temporary storage.
- ◆ Device scaling possible for higher level of integration.
- ◆ CMOS logic types: complementary MOS (CMOS), pseudo-NMOS, pass-transistor logic and dynamic CMOS logic.

■ Bipolar

- ◆ Transistor-transistor logic (TTL or Schottky TTL)
- ◆ Emitter-coupled logic (ECL): suitable for high speed operation

■ BiCMOS


■ GaAs

10.1 Digital Circuit Design: An Overview

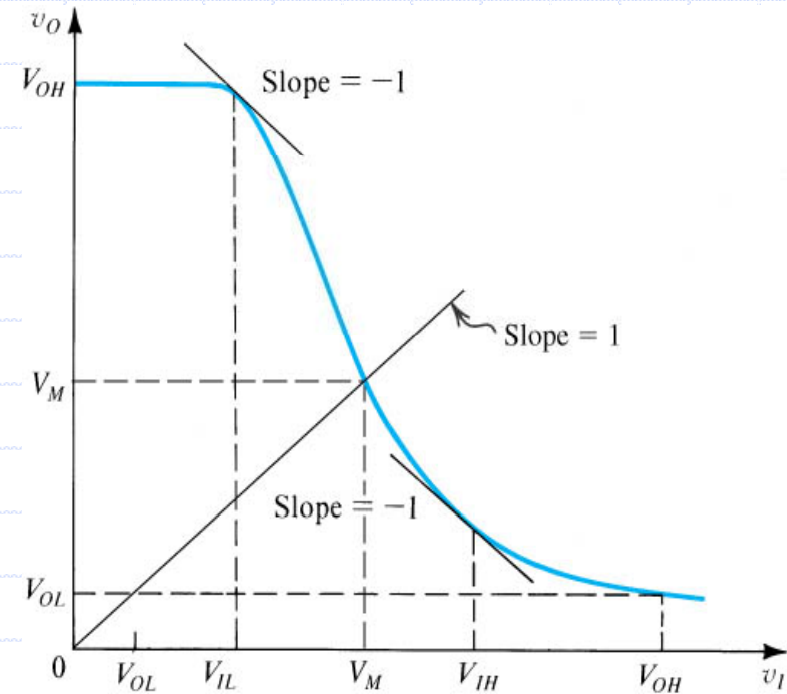- 10.1.2 Logic-Circuit Characterization

◆ Noise Margins

- V_{OH} : maximum output voltage
- V_{OL} : minimum output voltage
- V_{IH} , V_{IL} : the point at the slope of VTC = -1
- V_M : (logic) the point of threshold voltage at $v_O = v_I$
- $N_{MH} = V_{OH} - V_{IH}$
- $N_{ML} = V_{IL} - V_{OL}$




10.1 Digital Circuit Design: An Overview

 - 10.1.2 Logic-Circuit Characterization

◆ Propagation Delay

- t_{PHL} : high-to-low propagation delay
- t_{PLH} : low-to-high propagation delay
- t_p (propagation delay) = $(t_{PLH} + t_{PHL})/2$



10.1 Digital Circuit Design: An Overview

- 10.1.2 Logic-Circuit Characterization

◆ Power Dissipation

- Two types of power dissipation: static and dynamic
- Static power
 - ◆ The power that the gate dissipates in the absence of switching action
 - ◆ It results from the presence of a path in the gate circuit between the power supply and ground
- Dynamic power
 - ◆ Occurs when the gate is switched
 - ◆ An inverter operated from a power supply V_{DD} and driving a load capacitance C , dissipates dynamic power P_D

$$P_D = fCV_{DD}^2$$

(f is the frequency at which the inverter is being switched)

10.1 Digital Circuit Design: An Overview

- 10.1.2 Logic-Circuit Characterization

◆ Delay-Power Product

- Goal: High speed performance combined with low power dissipation.
- Figure-of-merit for comparing logic-circuit technologies is the delay-power product, defined as

$$DP = P_D t_p$$

10.1 Digital Circuit Design: An Overview

- 10.1.2 Logic-Circuit Characterization

◆ Silicon Area

- An obvious objective in the design of digital VLSI circuits is the minimization of silicon area per logic gate.

◆ Fan-In and Fan-Out

- The fan-in of a gate is the number of its inputs.
- A four-input NOR gate has a fan-in of 4.
- Fan-out is the maximum number of similar gates that a gate can drive while remaining within guaranteed specifications.

10.2 Design and Performance Analysis of the CMOS Inverter

- 10.2.1 Circuit Structure

- ◆ The CMOS logic inverter consists of a pair of complementary MOSFETs switched by the input voltage v_I

 


Figure 10.4 (a) The CMOS inverter and (b) its representation as a pair of switches operated in a complementary fashion.

10.2 Design and Performance Analysis of the CMOS Inverter

- 10.2.1 Circuit Structure

 


Figure 10.4 (a) The CMOS inverter and (b) its representation as a pair of switches operated in a complementary fashion.

- The source of each device is connected to its body, thus eliminating the body effect.
- Usually, the threshold voltages V_{in} V_{ip} are equal in magnitude.
- Each switch is modeled by a finite on resistance, which is the source-drain resistance of the respective transistor, evaluated near $|v_{DS}|=0$,

$$r_{DSN} = 1 / \left[k'_n \left(\frac{W}{L} \right)_n (V_{DD} - V_t) \right]$$

$$r_{DSP} = 1 / \left[k'_p \left(\frac{W}{L} \right)_p (V_{DD} - V_t) \right]$$

10.2 Design and Performance Analysis of the CMOS Inverter

- 10.2.2 Static Operation

- In the steady state, no direct-current path exists between V_{DD} and ground – the static-current and the static-power dissipation are both zero.
- The switching threshold V_{th}

$$V_{th} = \frac{V_{DD} - |V_{tp}| + \sqrt{k_n/k_p} V_{tn}}{1 + \sqrt{k_n/k_p}}$$

$$(k_n - k'_n (W/L)_n, k_p - k'_p (W/L)_p)$$

- For symmetry,

$$\left(\frac{W}{L}\right)_p = \frac{\mu_n}{\mu_p} \left(\frac{W}{L}\right)_n$$

 


Figure 10.5 The voltage transfer characteristic (VTC) of the CMOS inverter when Q_N and Q_P are matched.

10.2 Design and Performance Analysis of the CMOS Inverter

- 10.2.2 Static Operation

◆ Matching condition

- Symmetrical transfer characteristic

$$\left(\frac{W}{L}\right)_p = \frac{\mu_n}{\mu_p} \left(\frac{W}{L}\right)_n$$

- Equal driving capability for NMOS and PMOS
- Swing threshold is $V_{DD}/2$ in matched case.
- Noise margins in matched case:

$$NM_H = NM_L = \frac{3}{8} \left(V_{DD} + \frac{2}{3} V_t \right)$$

 


Figure 10.5 The voltage transfer characteristic (VTC) of the CMOS inverter when Q_N and Q_P are matched.


10.2 Design and Performance Analysis of the CMOS Inverter

- 10.2.3 Dynamic Operation

◆ Capacitance calculations

- The gate-drain overlap capacitance $\rightarrow 2C_{gd}$
(2 arises because of the Miller effect.)
- The drain-body capacitance $\rightarrow C_{db}$ (no miller effect)
- The input capacitance of second inverter $\rightarrow C_{g3} + C_{g4}$
 $= (W \cdot L)_3 C_{ox} + (W \cdot L)_4 C_{ox} + C_{gsov3} + C_{gdov3} + C_{gsov4} + C_{gdov4}$
- The wiring capacitance $\rightarrow C_w$
- The total value of load capacitance C is given by
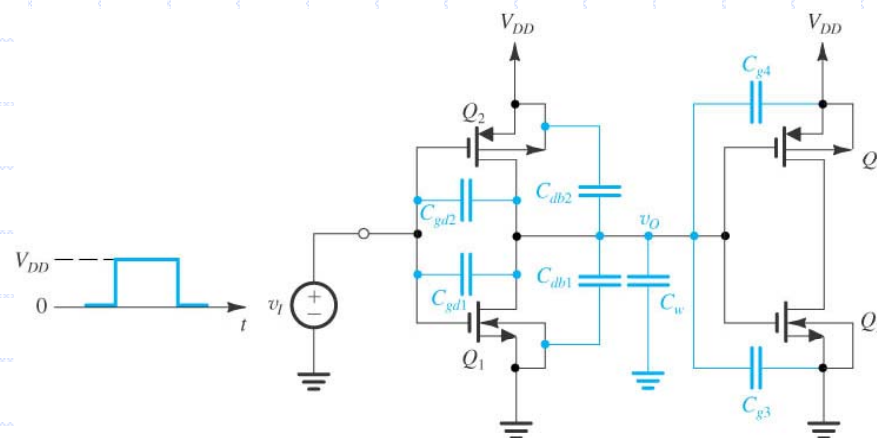
$$C = 2C_{gd1} + 2C_{gd2} + C_{db1} + C_{db2} + C_{g3} + C_{g4} + C_w$$



10.2 Design and Performance Analysis of the CMOS Inverter

- 10.2.3 Dynamic Operation

◆ Determining the propagation delays

- Computing an average value for the discharge current during the interval $t=0$ to $t=t_{PHL}$
- The average discharge current

$$i_{DN} |_{av} = \frac{1}{2} [i_{DN}(0) + i_{DN}(t_{PHL})] \text{ where,}$$

$$i_{DN}(0) = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_N (V_{DD} - V_t)^2$$

$$i_{DN}(t_{PHL}) = k'_n \left(\frac{W}{L} \right)_N \left[(V_{DD} - V_t) \frac{V_{DD}}{2} - \frac{1}{2} \left(\frac{V_{DD}}{2} \right)^2 \right]$$

- Assuming $V_t = 0.2V_{DD}$, t_{PHL} is

$$t_{PHL} = \frac{C\Delta V}{i_{DN} |_{av}} = \frac{CV_{DD}/2}{i_{DN} |_{av}} \approx \frac{1.7C}{k'_n \left(\frac{W}{L} \right)_N V_{DD}}$$

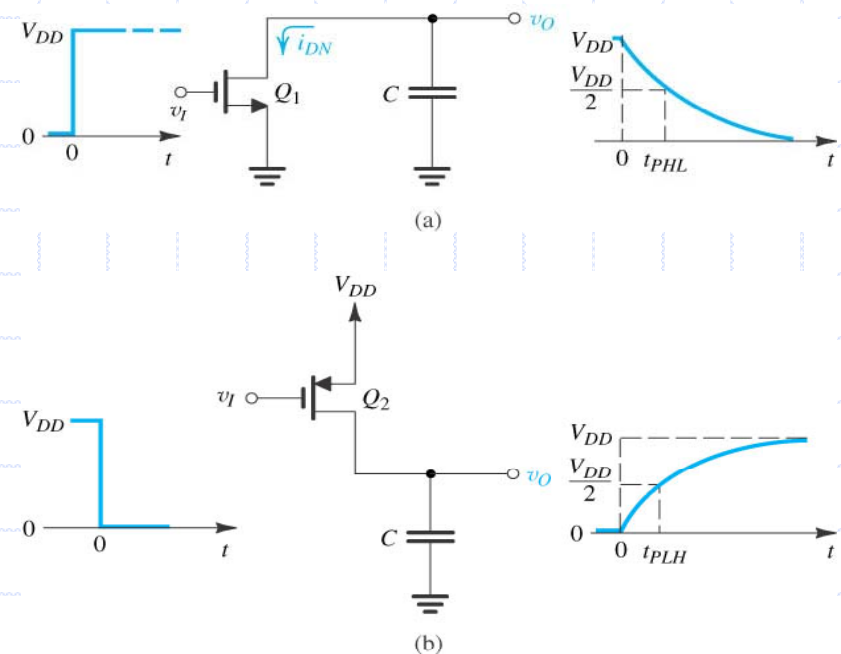


Figure 10.7 Equivalent circuits for determining the propagation delays (a) t_{PHL} and (b) t_{PLH} of the inverter.

10.2 Design and Performance Analysis of the CMOS Inverter

- 10.2.3 Dynamic Operation

- By analogy, t_{PLH} is

$$t_{PLH} = \frac{1.7C}{k'_p \left(\frac{W}{L}\right)_p V_{DD}}$$

- The propagation delay t_p can be found as the average of t_{PHL} and t_{PLH}

$$t_p = \frac{1}{2}(t_{PHL} + t_{PLH})$$

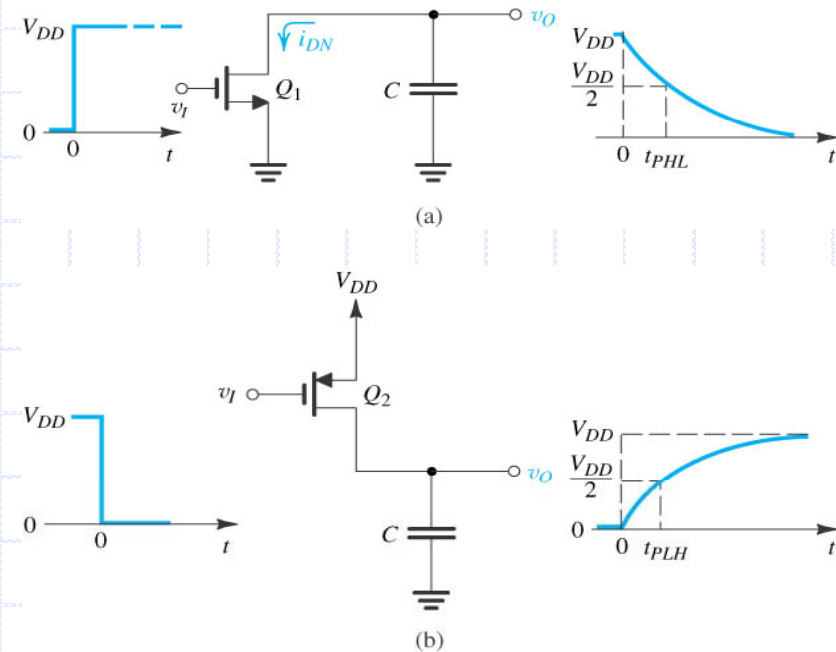


Figure 10.7 Equivalent circuits for determining the propagation delays (a) t_{PHL} and (b) t_{PLH} of the inverter.

10.2 Design and Performance Analysis of the CMOS Inverter

- 10.2.4 Dynamic Power Dissipation

- ◆ The dynamic power dissipated in the CMOS inverter is given by

$$P_D = fCV_{DD}^2$$

where f is the frequency at which the gate is switched.

10.2 Design and Performance Analysis of the CMOS Inverter

◆ Example 10.1

Consider a CMOS inverter fabricated in a 0.25- μm process for which $C_{\text{ox}} = 6 \text{ fF}/\mu\text{m}^2$, $\mu_n C_{\text{ox}} = 115 \text{ } \mu\text{A}/\text{V}^2$, $\mu_p C_{\text{ox}} = 30 \text{ } \mu\text{A}/\text{V}^2$, $V_{\text{tn}} = -V_{\text{tp}} = 0.4 \text{ V}$, and $V_{\text{DD}} = 2.5 \text{ V}$. The W/L ratio of Q_N is $0.375 \text{ } \mu\text{m}/0.25 \text{ } \mu\text{m}$, and that for Q_P is $1.125 \text{ } \mu\text{m}/0.25 \text{ } \mu\text{m}$. The gate-source and gate drain overlap capacitances are specified to be $0.3 \text{ fF}/\mu\text{m}$ of gate width. Further, the effective value of drain body capacitances are $C_{\text{dbn}} = 1 \text{ fF}$ and $C_{\text{dbp}} = 1 \text{ fF}$. The wiring capacitance $C_w = 0.2 \text{ fF}$. **Find t_{PHL} , t_{PLH} , and t_p .**

10.2 Design and Performance Analysis of the CMOS Inverter

◆ Example 10.1

■ Equivalent Capacitance

$$C_{gd1} = 0.3 \times W_n = 0.1125 \text{ fF}$$

$$C_{gd2} = 0.3 \times W_p = 0.3375 \text{ fF}$$

$$C_{db1} = 1 \text{ fF}$$

$$C_{db2} = 1 \text{ fF}$$

$$C_{g3} = 0.375 \times 0.25 \times 6 + 2 \times 0.3 \times 0.375 = 0.7875 \text{ fF}$$

$$C_{g4} = 1.125 \times 0.25 \times 6 + 2 \times 0.3 \times 1.125 = 2.3625 \text{ fF}$$

$$C_w = 0.2 \text{ fF}$$

■ Thus,

$$C = 2C_{gd1} + 2C_{gd2} + C_{db1} + C_{db2} + C_{g3} + C_{g4} + C_w = 6.25 \text{ fF}$$

10.2 Design and Performance Analysis of the CMOS Inverter

◆ Example 10.1

- Average discharge current

$$\begin{aligned}i_{DN}(0) &= \frac{1}{2} k'_n \left(\frac{W}{L} \right)_n (V_{DD} - V_t)^2 \\ &= 380 \mu\text{A}\end{aligned}$$

$$\begin{aligned}i_{DN}(t_{PHL}) &= k'_n \left(\frac{W}{L} \right)_n \left((V_{DD} - V_t) \frac{V_{DD}}{2} - \frac{1}{2} \left(\frac{V_{DD}}{2} \right)^2 \right) \\ &= 318 \mu\text{A}\end{aligned}$$

- Thus,

$$i_{DN|av} = \frac{i_{DN}(0) + i_{DN}(t_{PHL})}{2} = 349 \mu\text{A}$$

10.2 Design and Performance Analysis of the CMOS Inverter

◆ Example 10.1

- t_{PHL}

$$t_{PHL} = \frac{C(V_{DD}/2)}{i_{DN|av}} = 23.3 \text{ ps}$$

- t_{PLH} — since $W_p/W_n=3$ and $\mu_n/\mu_p=3.83$, the inverter is not perfectly matched. Therefore, we expect t_{PLH} to be greater than t_{PHL} by a factor of $3.83/3=1.3$, thus

$$t_{PLH} = 1.3 \times 23.3 = 30 \text{ ps}$$

- Thus,

$$t_p = \frac{t_{PHL} + t_{PLH}}{2} = 26.5 \text{ ps}$$