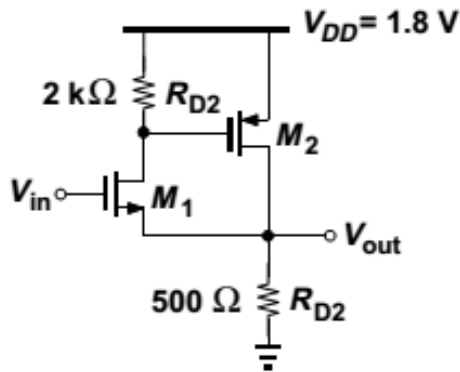


PSPICE Assignments #3

- Due: 2014/11/05(Wed) 3:30 PM
- Submit a hardcopy report.
- For any questions, send an e-mail to [jhlee88@isdl.snu.ac.kr](mailto:jhlee88@isdl.snu.ac.kr)

1. Solve the textbook problem 12.81. Use the provided spice library, "Midterm.lib". Assume  $\mu_n C_{ox} = 500 \mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 200 \mu\text{A}/\text{V}^2$ ,  $W = 20 \mu\text{m}$ ,  $L = 0.18 \mu\text{m}$ ,  $\lambda = 0$ ,  $V_{DD} = 3.3\text{V}$ ,  $V_{TN,n} = |V_{TN,p}| = 0.8\text{V}$ ,  $V_{in,offset} = 1.5\text{V}$ .

\* use  $V_{DD} = 3.3\text{V}$  for the Pspice simulation



- a) Setting the operation point ( $V_{in,offset} = 1.5\text{V}$ ) [3 point]
- b) Calculating the open-loop gain [3 point]
- c) Calculating the closed-loop gain and comparing it with the simulation result [4 point].

<End of PSPICE Assignments #3>