

## HW#5 - Selected solution

**8-18.** The standing-wave ratio on a lossless 300-( $\Omega$ ) transmission line terminated in an unknown load impedance is 2.0, and the nearest voltage minimum is at a distance  $0.3\lambda$  from the load. Determine (a) the reflection coefficient  $\Gamma$  of the load, and (b) the unknown load impedance  $Z_L$ .

a) From (8-91),  $|\Gamma| = \frac{s-1}{s+1} = \frac{1}{3}$ ,  $\Gamma = |\Gamma|e^{j\theta_r}$

From (7) on p.13 of the lecture note,

$$l_{\min} = \left( \frac{\theta_r}{\pi} + 1 \right) \frac{\lambda}{4} \longrightarrow \theta_r = l_{\min} \left( \frac{4\pi}{\lambda} \right) - \pi = 0.2\pi$$

$$\therefore \Gamma = |\Gamma|e^{j\theta_r} = \frac{1}{3}e^{j0.2\pi} = 0.27 + j0.196$$

b) From (8-88)

$$\begin{aligned} \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} &\longrightarrow Z_L(1 - \Gamma) = Z_0(1 + \Gamma) \\ &\longrightarrow Z_L = Z_0 \frac{1 + \Gamma}{1 - \Gamma} = 300 \frac{1.27 + j0.196}{0.73 - j0.196} = 466 + j206(\Omega) \end{aligned}$$

**8-24.** A dipole antenna having an input impedance of 73-( $\Omega$ ) is fed by a 200-(MHz) source through a 300-( $\Omega$ ) two-wire transmission line. Design a quarter-wave two-wire air line with a 2-(cm) spacing to match the antenna to the 300-( $\Omega$ ) line.

For a  $\frac{\lambda}{4}$  lossless air line,

$$(8-43): Z_0 = R_0 + jX_0 = R_0 = \sqrt{\frac{L}{C}} = \frac{1}{\pi} \sqrt{\frac{\mu_0}{\epsilon_0}} \cosh^{-1} \left( \frac{D}{2a} \right) \quad \textcircled{1}$$

$$(11) \text{ on p.17: } Z_0 = \sqrt{Z_1 Z_L} = \sqrt{73 \times 300} \approx 148(\Omega) \quad \textcircled{2}$$

$$\textcircled{2} = \textcircled{1} : 148 = \frac{120\pi}{\pi} \cosh^{-1}\left(\frac{2}{2a}\right)$$

$$\cosh^{-1}\left(\frac{1}{a}\right) \approx 1.233$$

$$a = \frac{1}{\cosh 1.233} \approx \frac{1}{1.861} \approx 0.54 \text{ cm}$$