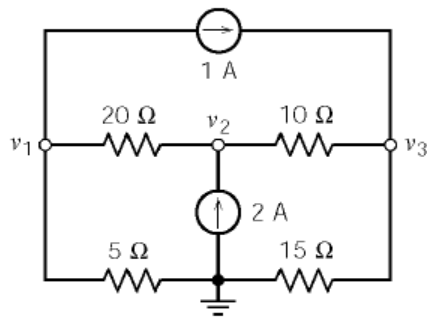


**P4.3-2**



KCL at node 1:

$$\frac{v_1 - v_2}{20} + \frac{v_1}{5} + 1 = 0 \Rightarrow 5v_1 - v_2 = -20$$

KCL at node 2:

$$\frac{v_1 - v_2}{20} + 2 = \frac{v_2 - v_3}{10} \Rightarrow -v_1 + 3v_2 - 2v_3 = 40$$


KCL at node 3:

$$\frac{v_2 - v_3}{10} + 1 = \frac{v_3}{15} \Rightarrow -3v_2 + 5v_3 = 30$$

Solving gives  $v_1 = 2$  V,  $v_2 = 30$  V and  $v_3 = 24$  V.

(checked using LNAP 8/13/02)

**P4.3-4**

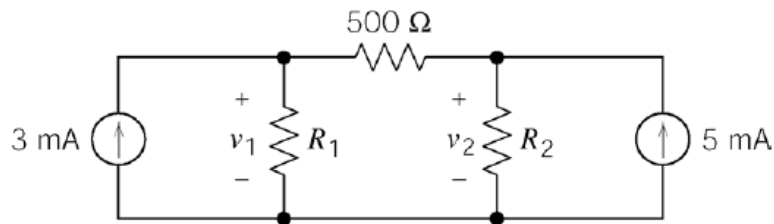

Node equations:

$$-.003 + \frac{v_1}{R_1} + \frac{v_1 - v_2}{500} = 0$$


$$-\frac{v_1 - v_2}{500} + \frac{v_2}{R_2} - .005 = 0$$

When  $v_1 = 1$  V,  $v_2 = 2$  V

$$-.003 + \frac{1}{R_1} + \frac{-1}{500} = 0 \Rightarrow R_1 = \frac{1}{.003 + \frac{1}{500}} = 200 \Omega$$

$$-\frac{-1}{500} + \frac{2}{R_2} - .005 = 0 \Rightarrow R_2 = \frac{2}{.005 - \frac{1}{500}} = 667 \Omega$$

**P4.4-4**

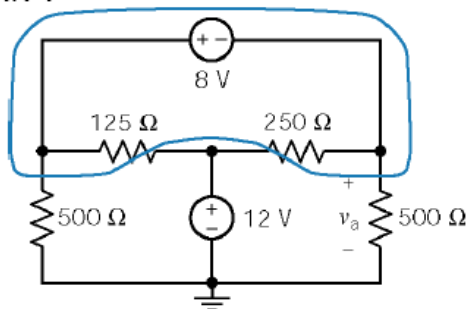

Apply KCL to the supernode:

$$\frac{v_a + 8}{500} + \frac{(v_a + 8) - 12}{125} + \frac{v_a - 12}{250} + \frac{v_a}{500} = 0$$


Solving yields

$$v_a = 4 \text{ V}$$

(checked using LNAP 8/13/02)

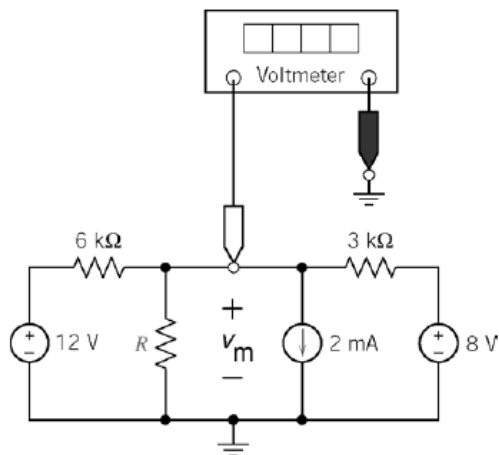**P4.4-6**

Label the voltage measured by the meter. Notice that this is a node voltage.



Write a node equation at the node at which the node voltage is measured.


$$-\left(\frac{12 - v_m}{6000}\right) + \frac{v_m}{R} + 0.002 + \frac{v_m - 8}{3000} = 0$$

That is

$$\left(3 + \frac{6000}{R}\right)v_m = 16 \Rightarrow R = \frac{6000}{\frac{16}{v_m} - 3}$$

- (a) The voltage measured by the meter will be 4 volts when  $R = 6 \text{ k}\Omega$ .
- (b) The voltage measured by the meter will be 2 volts when  $R = 1.2 \text{ k}\Omega$ .

**P4.5-1**

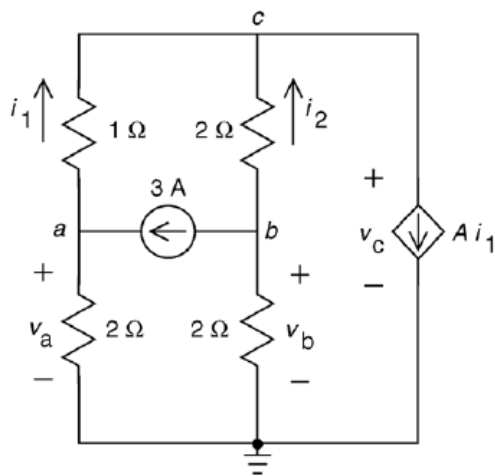

Express the resistor currents in terms of the node voltages:

$$i_1 = \frac{v_a - v_c}{1} = 8.667 - 10 = -1.333 \text{ A and}$$


$$i_2 = \frac{v_b - v_c}{2} = \frac{2 - 10}{2} = -4 \text{ A}$$

Apply KCL at node  $c$ :

$$\begin{aligned} i_1 + i_2 &= A i_1 \Rightarrow -1.333 + (-4) = A(-1.333) \\ \Rightarrow A &= \frac{-5.333}{-1.333} = 4 \end{aligned}$$

(checked using LNAP 8/13/02)

**P4.5-5**

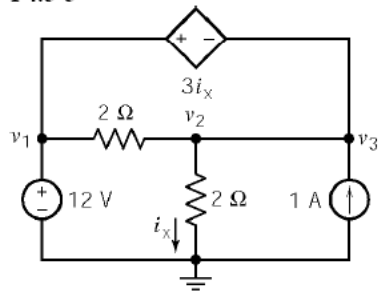

First, express the controlling current of the CCVS in terms of the node voltages:  $i_x = \frac{v_2}{2}$


Next, express the controlled voltage in terms of the node voltages:

$$12 - v_2 = 3i_x = 3 \frac{v_2}{2} \Rightarrow v_2 = \frac{24}{5} \text{ V}$$

so  $i_x = 12/5 \text{ A} = 2.4 \text{ A}$ .

(checked using ELab 9/5/02)

**P 4.6-1**

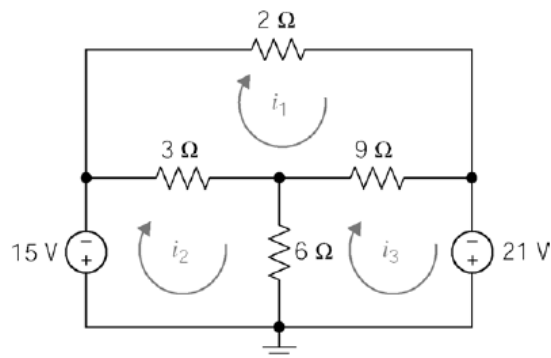

$$2i_1 + 9(i_1 - i_3) + 3(i_1 - i_2) = 0$$

$$15 - 3(i_1 - i_2) + 6(i_2 - i_3) = 0$$

$$-6(i_2 - i_3) - 9(i_1 - i_3) - 21 = 0$$

or

$$14i_1 - 3i_2 - 9i_3 = 0$$


$$-3i_1 + 9i_2 - 6i_3 = -15$$

$$-9i_1 - 6i_2 + 15i_3 = 21$$

so

$$i_1 = 3 \text{ A, } i_2 = 2 \text{ A and } i_3 = 4 \text{ A.}$$

**P4.6-4**

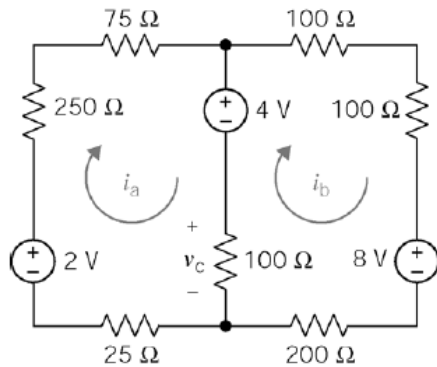

KVL loop 1:

$$25 i_a - 2 + 250 i_a + 75 i_a + 4 + 100 (i_a - i_b) = 0$$

$$450 i_a - 100 i_b = -2$$

KVL loop 2:

$$-100(i_a - i_b) - 4 + 100 i_b + 100 i_b + 8 + 200 i_b = 0$$

$$-100 i_a + 500 i_b = -4$$

$$\Rightarrow \underline{i_a = -6.5 \text{ mA}}, \underline{i_b = -9.3 \text{ mA}}$$

**P4.7-4**

Express the current source current in terms of the mesh currents:


$$i_b = i_a - 0.02$$

Apply KVL to the supermesh:

$$250 i_a + 100 (i_a - 0.02) + 9 = 0$$


$$\therefore i_a = -0.02 \text{ A} = -20 \text{ mA}$$
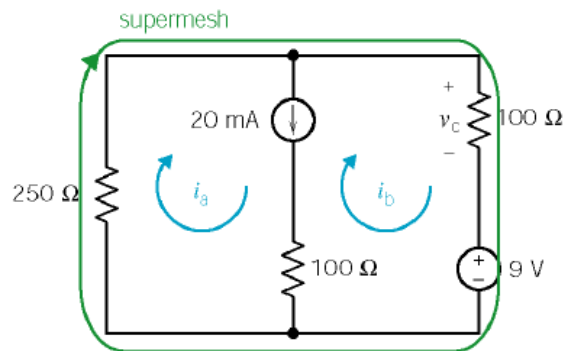
$$v_c = 100(i_a - 0.02) = \underline{-4 \text{ V}}$$



(checked using LNAP 8/14/02)

**P 4.7-9**

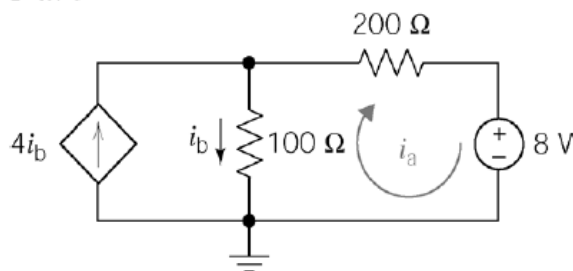


$$i_b = 4i_b - i_a \Rightarrow i_b = \frac{1}{3} i_a$$

$$-100 \left( \frac{1}{3} i_a \right) + 200 i_a + 8 = 0$$

$$\Rightarrow \underline{i_a = -0.048 \text{ A}}$$

(checked using LNAP 8/14/02)

P4.7-12

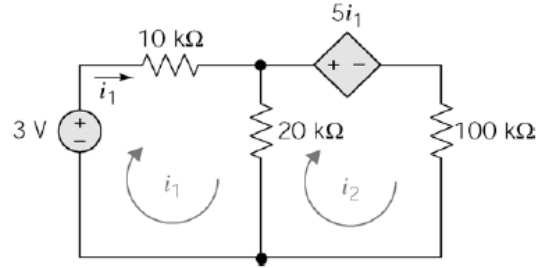

apply KVL to left mesh :  $-3 + 10 \times 10^3 i_1 + 20 \times 10^3 (i_1 - i_2) = 0 \Rightarrow 30 \times 10^3 i_1 - 20 \times 10^3 i_2 = 3$  (1)


apply KVL to right mesh :  $5 \times 10^3 i_1 + 100 \times 10^3 i_2 + 20 \times 10^3 (i_2 - i_1) = 0 \Rightarrow i_1 = 8i_2$  (2)

Solving (1) & (2) simultaneously  $\Rightarrow i_1 = \frac{6}{55} \text{ mA}, i_2 = \frac{3}{220} \text{ mA}$

$$\begin{aligned} \text{Power delivered to cathode} &= (5i_1)(i_2) + 100(i_2)^2 \\ &= 5\left(\frac{6}{55}\right)\left(\frac{3}{220}\right) + 100\left(\frac{3}{220}\right)^2 = 0.026 \text{ mW} \end{aligned}$$

$$\begin{aligned} \therefore \text{Energy in 24 hr.} &= Pt = (2.6 \times 10^{-5} \text{ W})(24 \text{ hr})(3600 \text{ s/hr}) \\ &= \underline{2.25 \text{ J}} \end{aligned}$$


P4.7-13

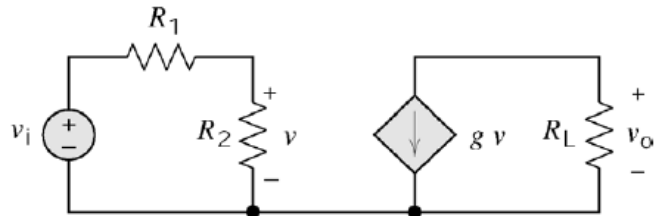

(a)  $v_o = -g R_L v$  and  $v = \frac{R_2}{R_1 + R_2} v_i \Rightarrow \frac{v_o}{v_i} = -g \frac{R_L R_2}{R_1 + R_2}$

(b)  $\therefore \frac{v_o}{v_i} = -g \frac{(5 \times 10^3)(10^3)}{1.1 \times 10^3} = -170 \Rightarrow \underline{g = 0.0374 \text{ S}}$

DP 4-2

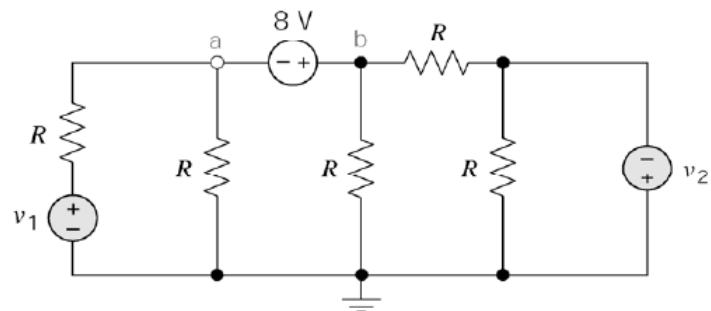

Express the voltage of the 8 V source in terms of its node voltages to get  $v_b - v_a = 8$ . Apply KCL to the supernode corresponding to the 8 V source:


$$\begin{aligned} \frac{v_a - v_1}{R} + \frac{v_a}{R} + \frac{v_b}{R} + \frac{v_b - (-v_2)}{R} &= 0 \Rightarrow 2v_a - v_1 + 2v_b + v_2 = 0 \\ &\Rightarrow 2v_a - v_1 + 2(v_a + 8) + v_2 = 0 \\ &\Rightarrow 4v_a - v_1 + v_2 + 16 = 0 \\ &\Rightarrow v_a = \frac{v_1 - v_2}{4} - 4 \end{aligned}$$

Next set  $v_a = 0$  to get

$$0 = \frac{v_1 - v_2}{4} - 4 \Rightarrow v_1 - v_2 = 16 \text{ V}$$

For example,  $v_1 = 18 \text{ V}$  and  $v_2 = 2 \text{ V}$ .

**DP 4-4**

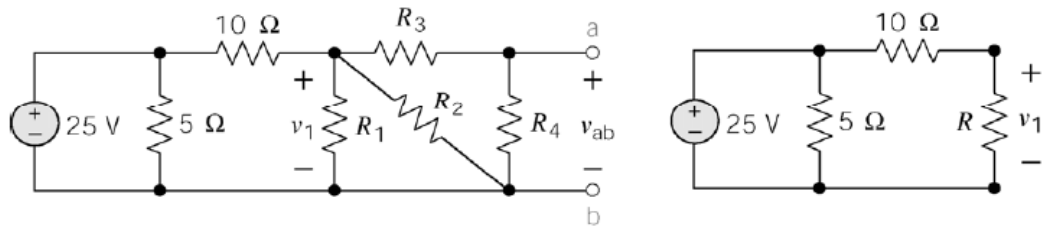

Equivalent resistance:  $R = R_1 \parallel R_2 \parallel (R_3 + R_4)$

Voltage division in the equivalent circuit:  $v_1 = \frac{R}{10 + R}(25)$

We require  $v_{ab} = 10$  V. Apply the voltage division principle in the left circuit to get:

$$10 = \frac{R_4}{R_3 + R_4} v_1 = \frac{R_4}{R_3 + R_4} \times \frac{(R_1 \parallel R_2 \parallel (R_3 + R_4))}{10 + (R_1 \parallel R_2 \parallel (R_3 + R_4))} \times 25$$

This equation does not have a unique solution. Here's one solution:

choose  $R_1 = R_2 = 25 \Omega$  and  $R_3 + R_4 = 20 \Omega$

$$\text{then } 10 = \frac{R_4}{20} \times \frac{(12.5 \parallel 20)}{10 + (12.5 \parallel 20)} \times 25 \Rightarrow \underline{R_4 = 18.4 \Omega}$$

$$\text{and } R_3 + R_4 = 20 \Rightarrow \underline{R_3 = 1.6 \Omega}$$