
Chapter 10

Sinusoidal Steady-State Analysis

Seoul National University

Department of Electrical and Computer Engineering

Prof. SungJune Kim

Sinusoidal Sources

- Sinusoidal function

$$v(t) = A \sin(\omega t) \text{ V}$$

- Sinusoid is periodic function having period of T.

$$v(t + T) = v(t)$$

- Frequency f and angular frequency ω is defined as below

$$f = \frac{1}{T} \text{ [Hz]} \quad \omega = 2\pi f = \frac{2\pi}{T} \text{ [rad/s]}$$

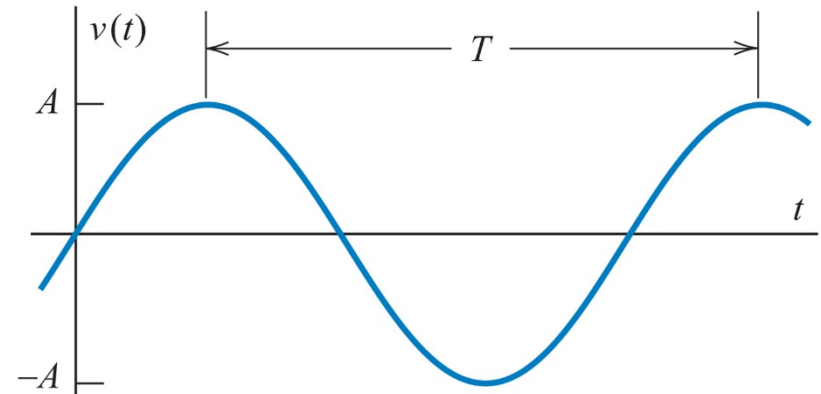


FIGURE 10.2-1



What is Phase?

- Consider the effect of replacing t by $t + t_a$ where t_a is some arbitrary time.

- We have

$$v(t + t_a) = A \sin(\omega(t + t_a)) = A \sin(\omega t + \omega t_a) = A \sin(\omega t + \theta) \quad V$$

where

$$\theta = \omega t_a = \frac{2\pi}{T} t_a = 2\pi \frac{t_a}{T} \quad [\mathbf{rad}]$$

θ is called the **phase angle** of the sinusoid $A \sin(\omega t + \theta)$.

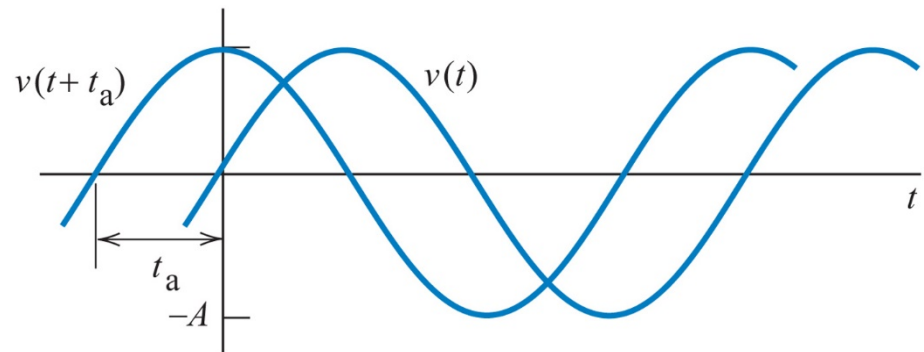


FIGURE 10.2-3



Example 10.2-1 Phase Shift and Delay

- Consider the sinusoids

$$v_1(t) = 10 \cos(200t + 45^\circ) \text{ V and } v_2(t) = 8 \sin(200t + 15^\circ) \text{ V}$$

Determine the time by which $v_2(t)$ is advanced or delayed with respect to $v_1(t)$.



Solution (1/2)

$v_1(t)$ and $v_2(t)$ have the same frequency but different amplitudes

Therefore, period of both sinusoids are given by

$$200 = \frac{2\pi}{T} \Rightarrow T = \frac{\pi}{100} = 0.0314159 = 31.4159 \text{ ms}$$

To compare the phase angle of $v_1(t)$ and $v_2(t)$, represent $v_2(t)$ as

$$v_2(t) = 8 \sin(200t + 15^\circ) = 8 \cos(200t - 75^\circ) \text{ V}$$

Then difference of phase angles of $v_1(t)$ and $v_2(t)$ is given by

$$\theta_2 - \theta_1 = -75^\circ - 45^\circ = -120^\circ = -\frac{2\pi}{3} [\text{rad}]$$

The minus sign indicates a delay rather than an advance. Convert this angle to time.

$$\theta_2 - \theta_1 = 2\pi \frac{t_d}{T} \Rightarrow t_d = \frac{(\theta_2 - \theta_1)T}{2\pi} = -10.47 \text{ ms}$$

Finally, $v_2(t)$ is delayed by about 10.5 ms with respect to $v_1(t)$



Solution (2/2)

Also MATLAB plot shows.


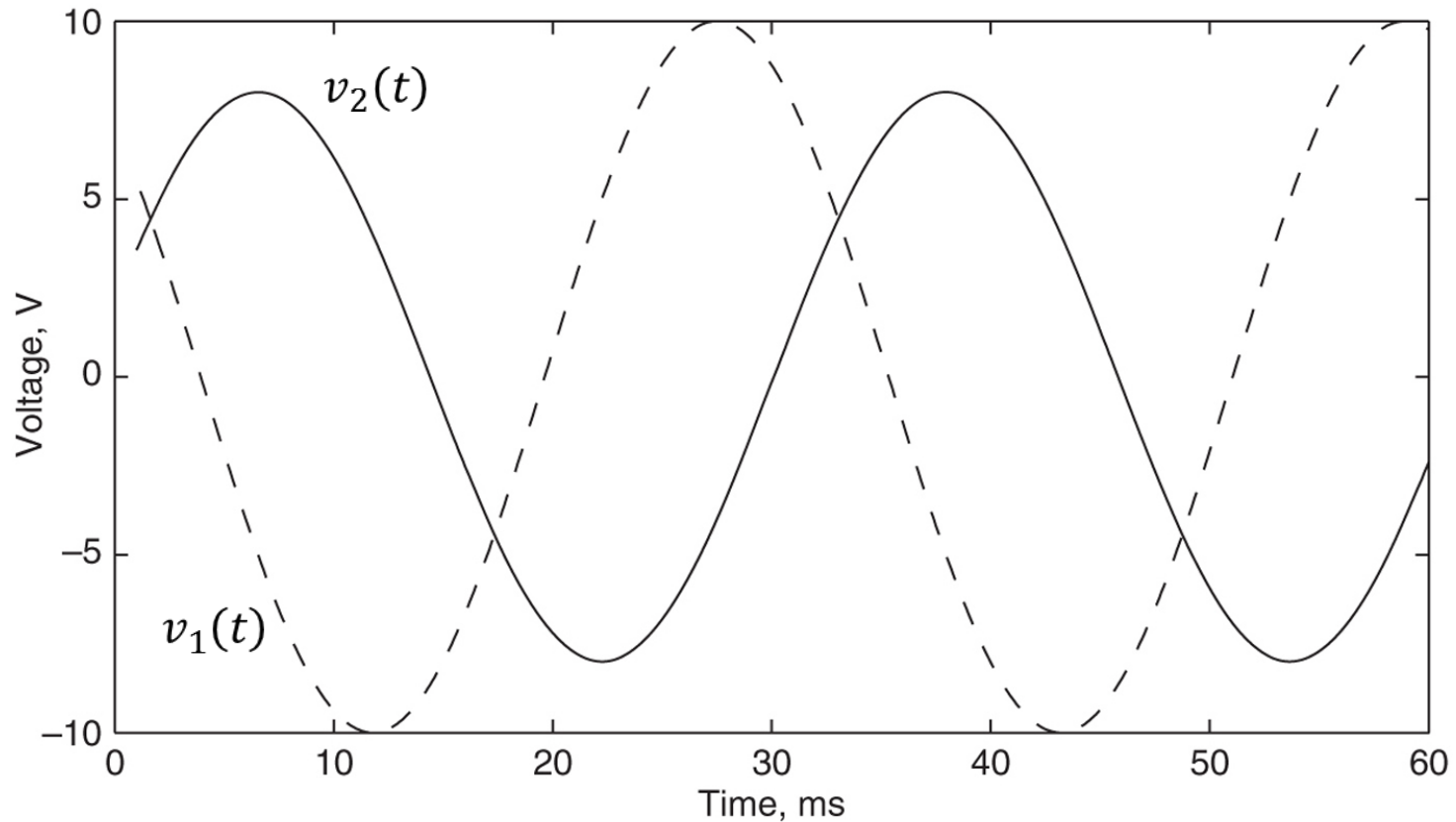


FIGURE 10.2-4

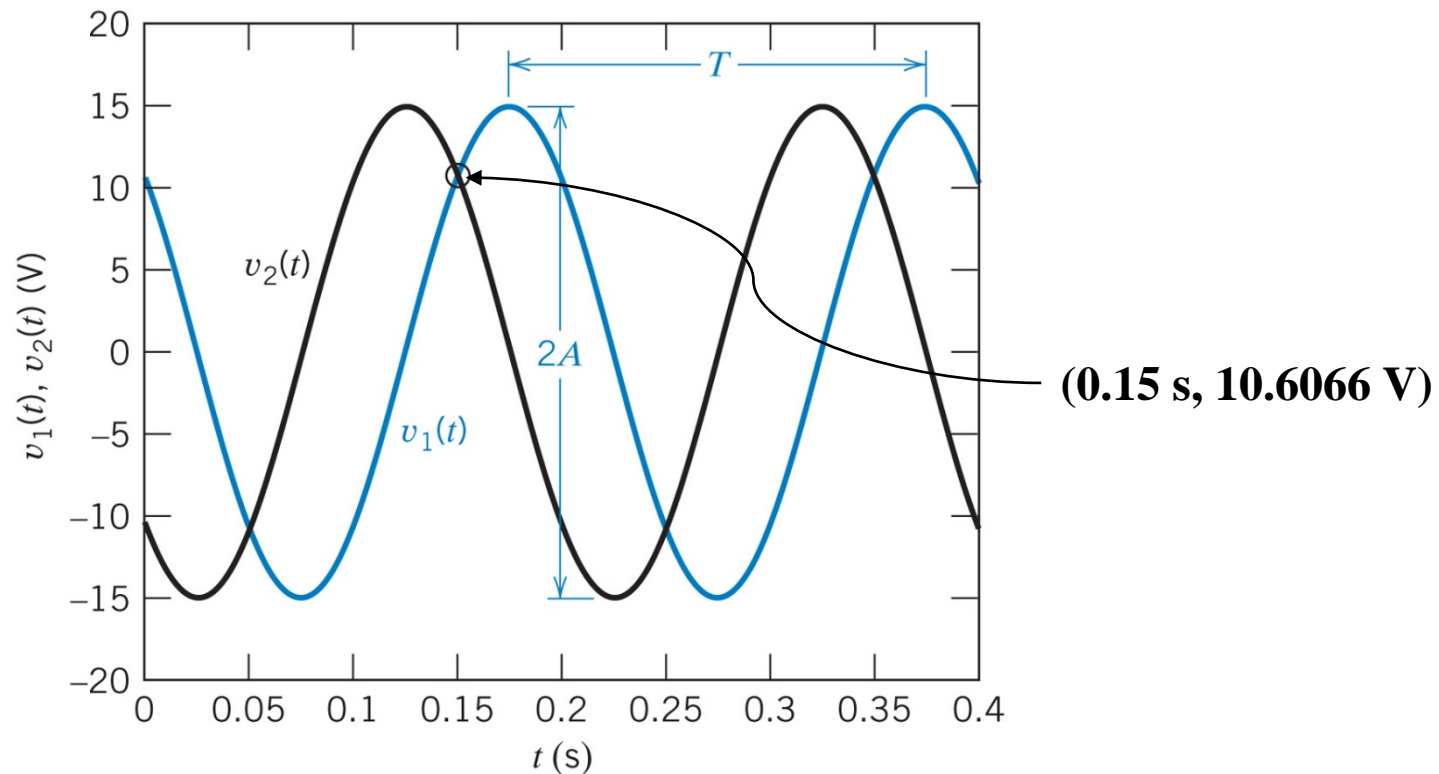

Example 10.2-2 Graphical and Analytic Representation of Sinusoids

- Determine the analytic representations of the sinusoidal voltages $v_1(t)$ and $v_2(t)$ shown in Figure 10.2-5



Solution

$v_1(t)$ and $v_2(t)$ have the same amplitude and period :

$$2A = 30 \Rightarrow A = 15 \text{ V and } T = 0.2 \text{ s} \Rightarrow \omega = \frac{2\pi}{0.2} = 10\pi \text{ rad/s}$$

Because $v_1(t_1)$ and $v_2(t_1) = 10.6066 \text{ V}$ at $t_1 = 0.15 \text{ s}$, and $v_1(t)$ is increasing, phase angle θ_1 is calculated as

$$\theta_1 = -\cos^{-1}\left(\frac{v_1(t_1)}{A}\right) - \omega t_1 = -5.498 \text{ rad} = -315^\circ = 45^\circ$$

Then $v_1(t)$ is represented as

$$v_1(t) = 15 \cos(10\pi t + 45^\circ) \text{ V}$$

Because $v_2(t)$ is decreasing at time t_1 , the phase angle θ_2 of $v_2(t)$ is calculated as

$$\theta_2 = \cos^{-1}\left(\frac{v_2(t_1)}{A}\right) - \omega t_1 = -3.927 \text{ rad} = -225^\circ = 135^\circ$$

Then $v_2(t)$ is represented as

$$v_2(t) = 15 \cos(10\pi t + 135^\circ) \text{ V}$$



Another Representation : Phasor

- Characteristics of sinusoids with same period are determined by the **amplitude** and **phase angle**.
- A phasor is a complex number that is used to represent the **amplitude** and **phase angle** of a sinusoid. The relationship between the sinusoid and the phasor is described by

$$A \cos(\omega t + \theta) \quad \leftrightarrow \quad A \angle \theta$$



Exponential Form of Phasor

- Exponential form of phasor

$$A\angle\theta = Ae^{j(\omega t + \theta)}$$

- From Euler's formular,

$$Ae^{j(\omega t + \theta)} = A \cos(\omega t + \theta) + j A \sin(\omega t + \theta)$$



Example 10.3-1 Phasor and Sinusoids

- Determine the phasors corresponding to the sinusoids

$$i_1(t) = 120 \cos(400t + 60^\circ) \text{ mA} \text{ and } i_2(t) = 100 \sin(400t - 75^\circ) \text{ mA}$$



Solution

Using the relationship between the sinusoid and the phasor, we have

$$\mathbf{I}_1(\omega) = 120\angle 60^\circ \text{ mA}$$

For i_2 , we have to express this using the cosine instead of sine

$$i_2(t) = 100 \sin(400t - 75^\circ) = 100 \cos(400t - 165^\circ) \text{ mA}$$


Then, we have

$$\mathbf{I}_2(\omega) = 100\angle -165^\circ \text{ mA}$$




Polar and Rectangular Forms of Phasor

- Since phasor is a complex number, **it indicates a point on complex plane** as we can see in figure 10.3-1.
- Figure 10.3-1 (a) and (b) are showing same phasor in polar and rectangular forms respectively.
- From figure 10.3-1 (a), we have
$$A = |\mathbf{V}| \text{ and } \theta = \angle \mathbf{V}$$
- And comparing this with (b), we have
$$a = \text{Re}\{\mathbf{V}\} \text{ and } b = \text{Im}\{\mathbf{V}\}$$

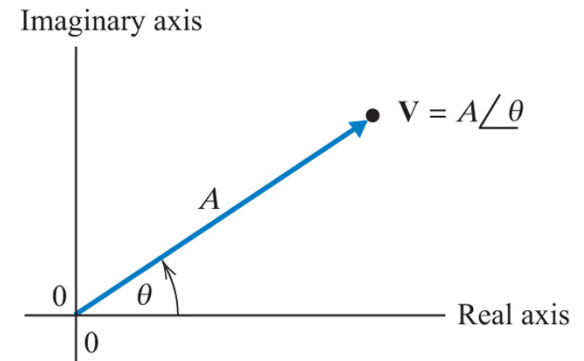

(a)

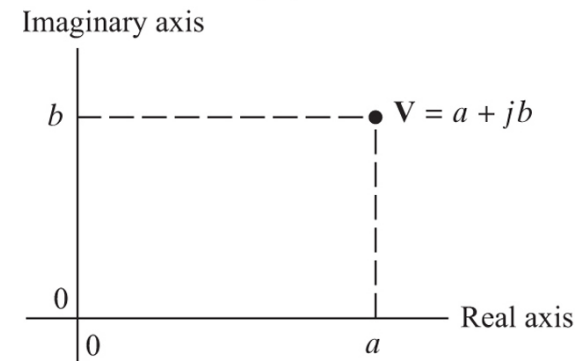

(b)

FIGURE 10.3-1



How to Convert Form?


- Since polar and rectangular forms indicate same point,

$$\mathbf{V} = A\angle\theta = a + jb$$


- From figure 10.3-1, we can find

$$a = A \cos(\theta), \quad b = A \sin(\theta), \quad A = \sqrt{a^2 + b^2}$$
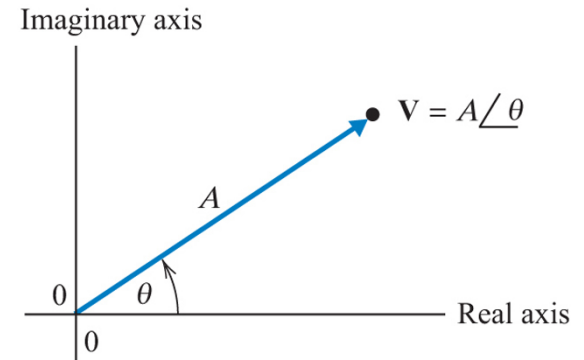
$$\theta = \begin{cases} \tan^{-1}\left(\frac{b}{a}\right) & a > 0 \\ 180^\circ - \tan^{-1}\left(\frac{b}{-a}\right) & a < 0 \end{cases}$$



(a)

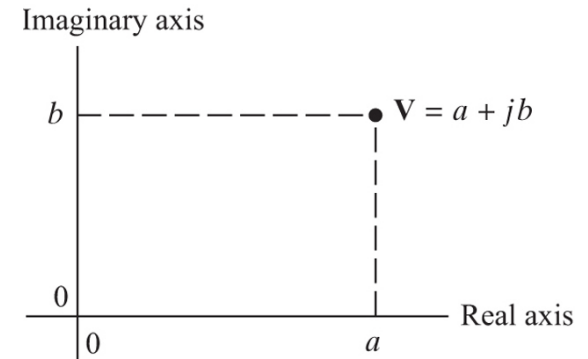

(b)

FIGURE 10.3-1



Example 10.3-2 Rectangular and Polar Forms of Phasors

- Consider the phasors

$$\mathbf{V}_1 = 4.25\angle 115^\circ \text{ and } \mathbf{V}_2 = -4 + j3$$



Solution

Using conversion equation

$$\mathbf{V}_1 = \text{Re}\{\mathbf{V}_1\} + j\text{Im}\{\mathbf{V}_1\} = 4.25 \cos(115^\circ) + j4.25 \sin(115^\circ) = -1.796 + j3.852$$

$$|\mathbf{V}_2| = |-4 + j3| = \sqrt{(-4)^2 + 3^2} = 5 \quad \angle \mathbf{V}_2 = 180^\circ - \tan^{-1}\left(\frac{3}{-(-4)}\right) = 143^\circ$$

Therefore,

$$\mathbf{V}_1 = -1.796 + j3.852 \quad \text{and} \quad \mathbf{V}_2 = 5\angle 143^\circ$$



Arithmetic Operations

- Let's consider doing arithmetic with two arbitrary phasors, \mathbf{V}_1 and \mathbf{V}_2 , each represented in both rectangular and polar forms.

$$\mathbf{V}_1 = a + jb = E \angle \theta \text{ and } \mathbf{V}_2 = c + jd = F \angle \phi$$

- Then, phasors are **added and subtracted** using the **rectangular forms** of the phasors

$$\mathbf{V}_1 + \mathbf{V}_2 = (a + jb) + (c + jd) = (a + c) + j(b + d)$$

$$\mathbf{V}_1 - \mathbf{V}_2 = (a + jb) - (c + jd) = (a - c) + j(b - d)$$

- On the other hands, phasors are **multiplied and divided** using the **polar forms** of the phasors

$$\mathbf{V}_1 \cdot \mathbf{V}_2 = (E \angle \theta) (F \angle \phi) = EF \angle (\theta + \phi) \text{ and } \frac{\mathbf{V}_1}{\mathbf{V}_2} = \frac{A \angle \theta}{B \angle \phi} = \frac{A}{B} \angle (\theta - \phi)$$

- And, the conjugate form of the phasor \mathbf{V}_1 is denoted as \mathbf{V}_1^* and defined as

$$\begin{aligned} \mathbf{V}_1^* &= (a + jb)^* = a - jb \\ &= (E \angle \theta)^* = E \angle -\theta \end{aligned}$$



Example 10.3-3 Arithmetic Using Phasors

- Consider the phasors

$$\mathbf{V}_1 = -1.796 + j3.852 = 4.25\angle 115^\circ \text{ and } \mathbf{V}_2 = -4 + j3 = 5\angle 143^\circ$$



Solution

Using rectangular forms of \mathbf{V}_1 and \mathbf{V}_2 ,

$$\mathbf{V}_1 - \mathbf{V}_2 = (-1.796 + j3.852) + (-4 + j3) = -5.796 + j6.852$$

Then, with polar forms,

$$\begin{aligned}\mathbf{V}_1 \cdot \mathbf{V}_2 &= (4.25 \angle 115^\circ)(5 \angle 143^\circ) = (4.25)(5) \angle (115^\circ + 143^\circ) \\ &= 21.25 \angle 258^\circ = 21.25 \angle -102^\circ\end{aligned}$$

$$\frac{\mathbf{V}_1}{\mathbf{V}_2} = \frac{4.25 \angle 115^\circ}{5 \angle 143^\circ} = \frac{4.25}{5} \angle (115^\circ - 143^\circ) = 0.85 \angle -28^\circ$$



Euler's Formula

- As we learned at engineering mathematics,

$$\cos \varphi + j \sin \varphi = e^{j\varphi}$$

Consequently, $A \angle \varphi = A \cos \varphi + j A \sin \varphi = Ae^{j\varphi}$

- $Ae^{j\varphi}$ is called the **exponential form** of a phasor.
The conversion between the polar and exponential forms is immediate.

- Next, consider

$$A e^{j(\omega t + \theta)} = A \cos (\omega t + \theta) + j A \sin(\omega t + \theta)$$

Taking the real part of both sides gives,

$$A \cos (\omega t + \theta) = \operatorname{Re}\{A e^{j(\omega t + \theta)}\} = \operatorname{Re}\{A e^{j\theta} e^{j\omega t}\}$$



Kirchhoff's Law for AC Circuits

- Then, consider a sinusoid and corresponding phasor,

$$v(t) = A \cos(\omega t + \theta) \quad \text{and} \quad \mathbf{V}(\omega) = A \angle \theta = A e^{j\theta}$$

Therefore, $v(t) = \text{Re}\{ \mathbf{V}(\omega) e^{j\omega t} \}$

- Then consider a KVL from an ac circuit, for example,

$$0 = \sum_i v_i(t) = \sum_i \text{Re}\{ \mathbf{V}_i(\omega) e^{j\omega t} \} = \text{Re}\left\{ e^{j\omega t} \sum_i \mathbf{V}_i(\omega) \right\}$$

- This is required to be true for all values of time t . Let $t = 0$ and $\pi/2$.

$$0 = \text{Re}\left\{ \sum_i \mathbf{V}_i(\omega) \right\} \quad \text{and} \quad 0 = \text{Re}\left\{ -j \sum_i \mathbf{V}_i(\omega) \right\} = \text{Im}\left\{ \sum_i \mathbf{V}_i(\omega) \right\}$$

- Therefore,

$$0 = \sum_i \mathbf{V}_i(\omega)$$



Example 10.3-4 Kirchhoff's Laws for AC Circuits

- The input to the circuit shown in Figure 10.3-3 is the voltage source voltage,

$$v_s(t) = 25\cos(100t + 15^\circ) \text{ V}$$

$$v_C(t) = 25\cos(100t - 22^\circ) \text{ V}$$

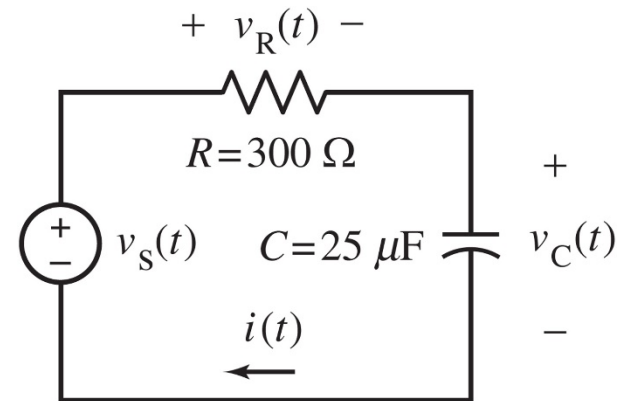


FIGURE 10.3-3



Solution

Apply KVL,

$$v_R(t) = v_s(t) - v_C(t) = 25 \cos(100t + 15^\circ) - 20 \cos(100t - 22^\circ)$$

Writing this equation using phasor, we have

$$\begin{aligned} \mathbf{V}_R(\omega) &= \mathbf{V}_s(\omega) - \mathbf{V}_C(\omega) = 25\angle 15^\circ - 20\angle -22^\circ \\ &= (24.15 + j6.47) - (18.54 - j7.49) \\ &= 5.61 + j13.96 \\ &= 15\angle 68.1^\circ \text{ V} \end{aligned}$$

$$\mathbf{V}_R(\omega) = 15\angle 68.1^\circ \text{ V} \leftrightarrow v_R(t) = 15 \cos(100t + 68.1^\circ) \text{ V}$$

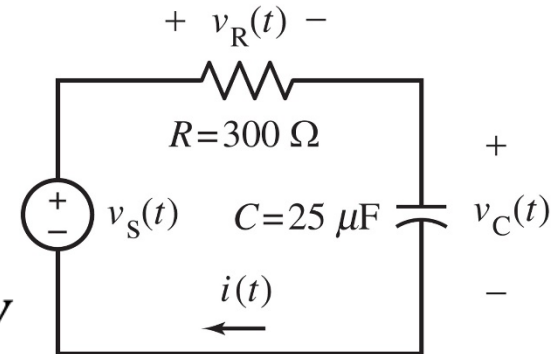


FIGURE 10.3-3



What is Impedance?

- Figure 10.4-1 (a) represents **time domain** and (b) represents **frequency domain**
- Figure 10.4-1(a) shows an element of an ac circuit. We can write

$$v(t) = V_m \cos(\omega t + \theta) \quad \text{and} \quad i(t) = I_m \cos(\omega t + \varphi)$$

The corresponding phasors are

$$\mathbf{V}(\omega) = V_m \angle \theta \quad \text{and} \quad \mathbf{I}(\omega) = I_m \angle \varphi$$

- Then, the impedance is denoted as $\mathbf{Z}(\omega)$ so

$$\mathbf{Z}(\omega) = \frac{\mathbf{V}(\omega)}{\mathbf{I}(\omega)} = \frac{V_m \angle \theta}{I_m \angle \varphi} = \frac{V_m}{I_m} \angle (\theta - \varphi) \quad [\Omega]$$

- **Ohm's law for ac circuits** satisfy

$$\mathbf{V}(\omega) = \mathbf{Z}(\omega)\mathbf{I}(\omega)$$

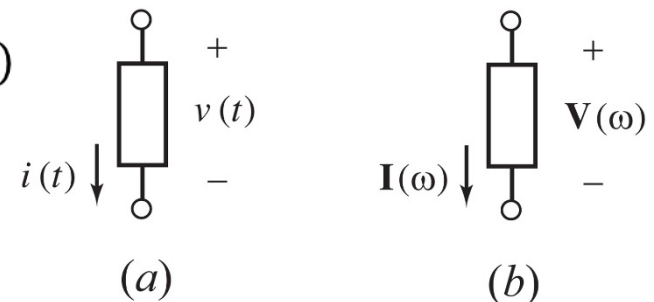


FIGURE 10.4-1



cf) Admittance

- For dc circuits, we used inverse of the resistance as the conductance of an element.
- Of course, there is the ac version of the conductance, which is called **admittance**.

- Consider same element with previous slide
 $v(t) = V_m \cos(\omega t + \theta)$ and $i(t) = I_m \cos(\omega t + \varphi)$
The corresponding phasors are

$$\mathbf{V}(\omega) = V_m \angle \theta \quad \text{and} \quad \mathbf{I}(\omega) = I_m \angle \varphi$$

- Then, the admittance is denoted as $\mathbf{Y}(\omega)$ so

$$\mathbf{Y}(\omega) = \frac{\mathbf{I}(\omega)}{\mathbf{V}(\omega)} = \frac{I_m \angle \varphi}{V_m \angle \theta} = \frac{I_m}{V_m} \angle (\varphi - \theta) \text{ [S]}$$

- Obviously, the admittance is **inversion of the impedance**

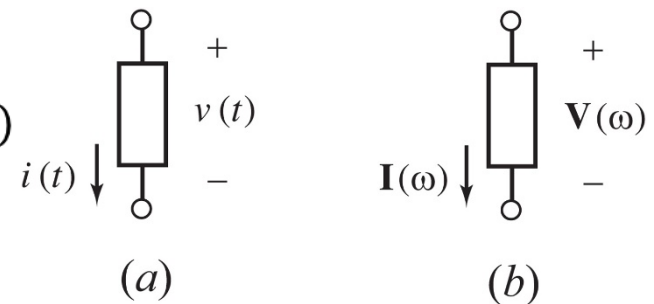


FIGURE 10.4-1

$$\mathbf{Y}(\omega) = \frac{1}{\mathbf{Z}(\omega)}$$



Impedance of Capacitor

- Figure 10.4-2 shows an capacitor of an ac circuit. For $v_c(t) = A\cos(\omega t + \theta)$, as we studied at chapter 7,

$$i_c(t) = C \frac{d}{dt} v_c(t) = -\omega CA \sin(\omega t + \theta) = \omega CA \cos(\omega t + \theta + 90^\circ)$$

The corresponding phasors are

$$\mathbf{V}_c(\omega) = A\angle\theta \text{ and } \mathbf{I}_c(\omega) = \omega CA\angle(\theta + 90^\circ) = (\omega C\angle 90^\circ)(A\angle\theta) = j\omega CA\angle\theta$$

Therefore,

$$\mathbf{Z}_c(\omega) = \frac{\mathbf{V}_c(\omega)}{\mathbf{I}_c(\omega)} = \frac{A\angle\theta}{j\omega CA\angle\theta} = \frac{1}{j\omega C}$$

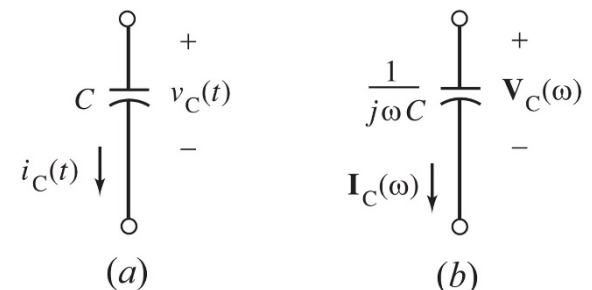


FIGURE 10.4-2



Impedance of Inductor

- Figure 10.4-3 shows an inductor of an ac circuit. For $i_L(t) = A\cos(\omega t + \theta)$, as we studied at chapter 7,

$$v_L(t) = L \frac{d}{dt} i_L(t) = -\omega LA \sin(\omega t + \theta) = \omega LA \cos(\omega t + \theta + 90^\circ)$$

The corresponding phasors are

$$\mathbf{I}_L(\omega) = A\angle\theta \text{ and } \mathbf{V}_L(\omega) = \omega LA\angle(\theta + 90^\circ) = (\omega L\angle 90^\circ)(A\angle\theta) = j\omega LA\angle\theta$$

Therefore,

$$\mathbf{Z}_L(\omega) = \frac{\mathbf{V}_L(\omega)}{\mathbf{I}_L(\omega)} = \frac{j\omega LA\angle\theta}{A\angle\theta} = j\omega L$$

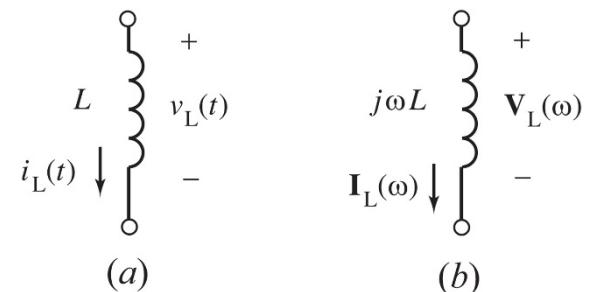


FIGURE 10.4-3



Impedance of Elements

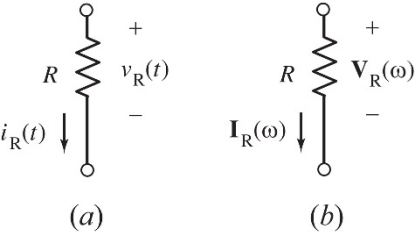
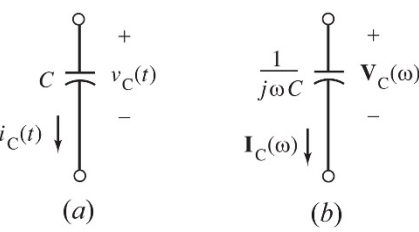
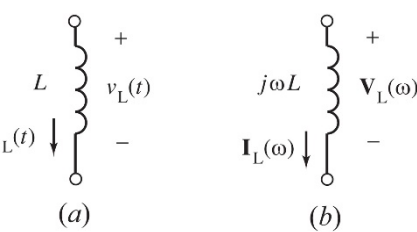
Element	Resistor	Capacitor	Inductor
Impedance [Ω]	 <p>FIGURE 10.4-4</p>	 <p>FIGURE 10.4-2</p>	 <p>FIGURE 10.4-3</p>
	R	$\frac{1}{j\omega C}$	$j\omega L$

CHART 10.4-1



Example 10.4-1 Impedances

- The input to the ac circuit shown in Figure 10.4-5 is the source voltage

$$v_s(t) = 12\cos(1000t + 15^\circ) \text{ V}$$

Determine (a) the impedances of the capacitor, inductor, and resistance and
(b) the current $i(t)$

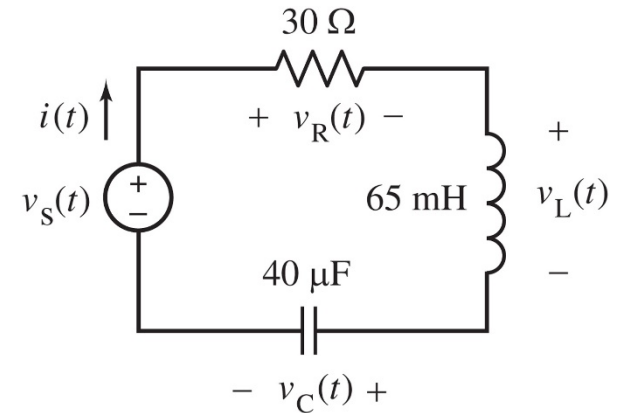


FIGURE 10.4-5



Solution

(a) input frequency is $\omega = 1000 \text{ rad/s}$. From the chart 10.4-1, impedances of each elements are

$$\mathbf{Z}_R(\omega) = 30 \Omega, \mathbf{Z}_L(\omega) = j\omega L = j65 \Omega, \text{ and } \mathbf{Z}_C(\omega) = \frac{1}{j\omega C} = -j25 \Omega$$

(b) applying KVL using phasor,

$$\begin{aligned}\mathbf{V}_s(\omega) &= \mathbf{V}_R(\omega) + \mathbf{V}_L(\omega) + \mathbf{V}_C(\omega) = \mathbf{I}(\omega) \cdot \mathbf{Z}_R(\omega) + \mathbf{I}(\omega) \cdot \mathbf{Z}_L(\omega) + \mathbf{I}(\omega) \cdot \mathbf{Z}_C(\omega) \\ &= \mathbf{I}(\omega) \cdot \{\mathbf{Z}_R(\omega) + \mathbf{Z}_L(\omega) + \mathbf{Z}_C(\omega)\}\end{aligned}$$

$$12\angle 15^\circ = \mathbf{I}(\omega) \cdot \{30\angle 0^\circ + 65\angle 90^\circ + 25\angle -90^\circ\}$$

$$= \mathbf{I}(\omega) \cdot 50\angle 53.13^\circ$$

$$\mathbf{I}(\omega) = \frac{12\angle 15^\circ}{50\angle 53.13^\circ} = 0.24\angle -38.13^\circ$$

$$i(t) = 0.24\cos(1000t - 38.13^\circ)$$

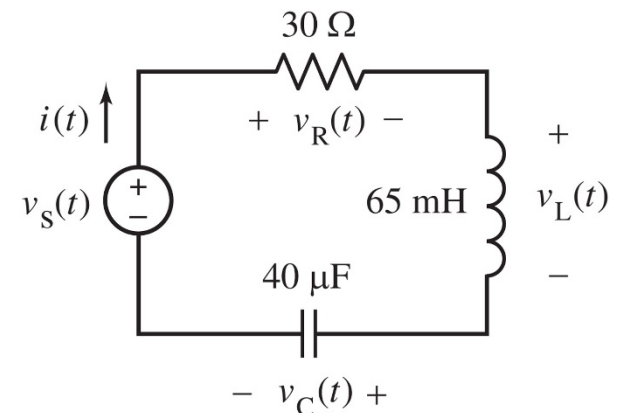


FIGURE 10.4-5



Example 10.4-2 AC Circuits in the Frequency Domain

- The input to the ac circuit shown in Figure 10.4-7 is the source voltage

$$v_s(t) = 48 \cos(500t + 75^\circ) \text{ V}$$

Determine the voltage $v(t)$.

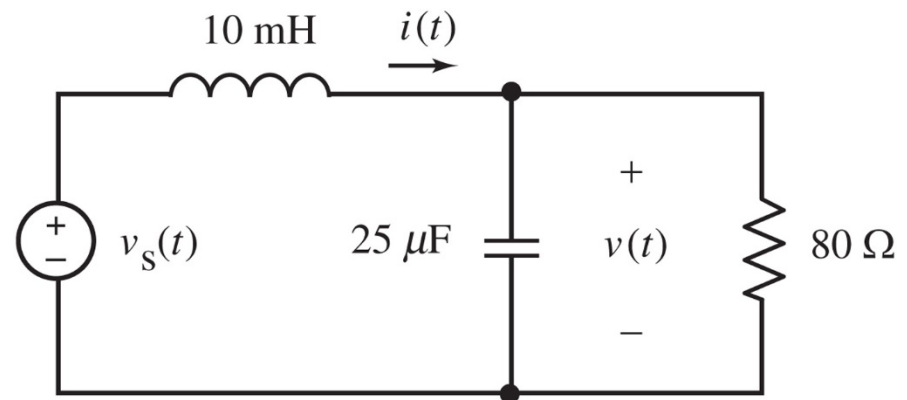


FIGURE 10.4-7



Solution (1/2)

The input frequency is $\omega = 500 \text{ rad/s}$. From the chart 10.4-1, impedances of each elements are

$$\mathbf{Z}_R(\omega) = 80 \Omega, \mathbf{Z}_L(\omega) = j\omega L = j5 \Omega, \text{ and } \mathbf{Z}_C(\omega) = \frac{1}{j\omega C} = -j80 \Omega$$

Figure 10.4-8 represents same circuit in frequency domain. By applying Ohm's law to each of the impedances,

$$\mathbf{V}_L(\omega) = \mathbf{I}(\omega) \cdot 5\angle 90^\circ \text{ and } \mathbf{V}(\omega) = \mathbf{I}_C(\omega) \cdot 80\angle -90^\circ = \mathbf{I}_R(\omega) \cdot 80\angle 0^\circ$$

By applying KCL at node a, we have

$$\begin{aligned} \mathbf{I}(\omega) &= \mathbf{I}_C(\omega) + \mathbf{I}_R(\omega) \\ \Rightarrow \frac{48\angle 75^\circ - \mathbf{V}(\omega)}{5\angle 90^\circ} &= \frac{\mathbf{V}(\omega)}{80\angle -90^\circ} + \frac{\mathbf{V}(\omega)}{80\angle 0^\circ} \end{aligned}$$

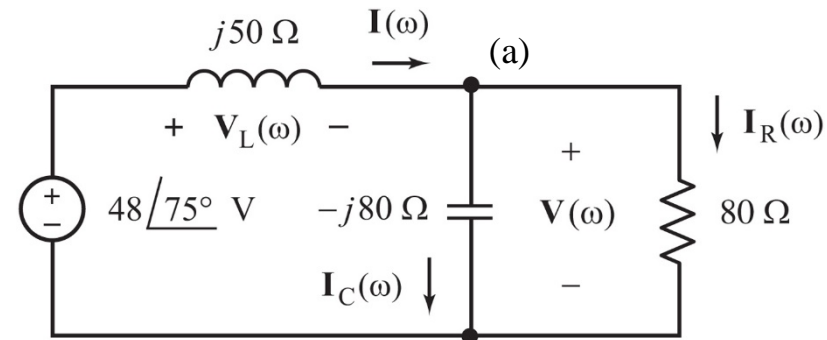


FIGURE 10.4-8



Solution (2/2)

From the equation, we have

$$\frac{48\angle 75^\circ}{5\angle 90^\circ} = \mathbf{V}(\omega) \left\{ \frac{1}{5\angle 90^\circ} + \frac{1}{80\angle -90^\circ} + \frac{1}{80\angle 0^\circ} \right\}$$

$$\Rightarrow 9.6\angle 15^\circ = \mathbf{V}(\omega) \left\{ \frac{1}{j5} + \frac{1}{-j80} + \frac{1}{80} \right\} = \mathbf{V}(\omega) \cdot \frac{-16j + j + 1}{80} = \frac{1 - j15}{80} \cdot \mathbf{V}(\omega)$$

$$\Rightarrow \mathbf{V}(\omega) = 80 \cdot \frac{9.6\angle 15^\circ}{1 - j15} = 51.1\angle 101.2^\circ$$

Therefore,

$$v(t) = 51.1 \cos(500t + 101.2^\circ) \text{ V}$$

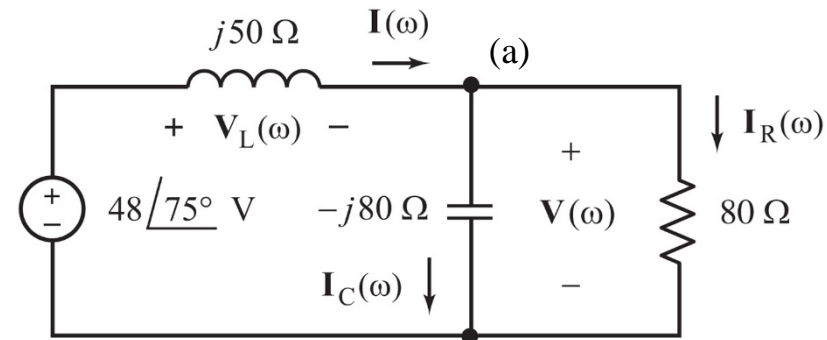


FIGURE 10.4-8



Example 10.4-3 AC Circuits Containing a Dependent Source

- The input to the ac circuit shown in Figure 10.4-10 is the source voltage

$$v_s(t) = 12 \cos(1000t + 45^\circ) \text{ V}$$

Determine the voltage $v_o(t)$.

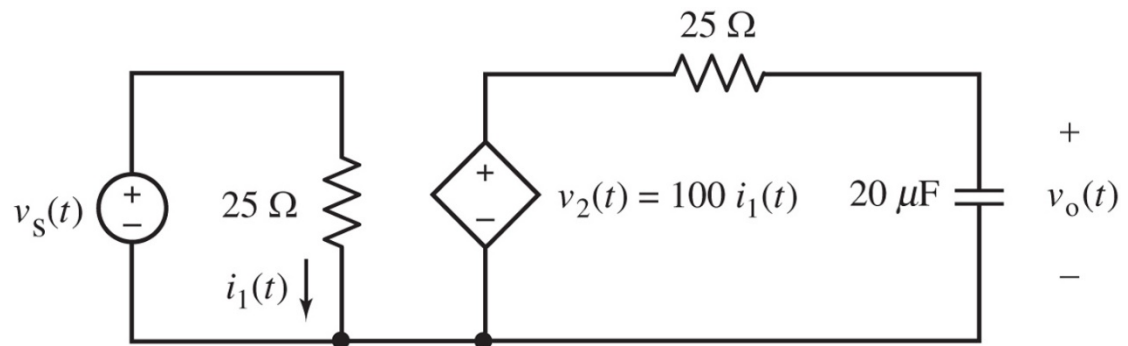


FIGURE 10.4-10



Solution

The input frequency is $\omega = 1000 \text{ rad/s}$. Impedance of the capacitor is,

$$\mathbf{Z}_C(\omega) = \frac{1}{j\omega C} = -j50 \Omega$$

Figure 10.4-11 represents same circuit in frequency domain. By applying Ohm's law to each of the impedances, we can find $\mathbf{V}_2(\omega)$ from $\mathbf{I}_1(\omega)$.

$$\mathbf{V}_2(\omega) = 100\mathbf{I}_1(\omega) = 100 \cdot \frac{12\angle 45^\circ}{25} = 48\angle 45^\circ$$

By applying KVL at right mesh, we have

$$\begin{aligned} \mathbf{V}_2(\omega) - 25\mathbf{I}_2(\omega) &= \mathbf{V}_o(\omega) & \Rightarrow 48\angle 45^\circ - 25 \frac{\mathbf{V}_o(\omega)}{50\angle -90^\circ} &= \mathbf{V}_o(\omega) \\ \Rightarrow 48\angle 45^\circ &= (1 + j0.5)\mathbf{V}_o(\omega) & \Rightarrow \mathbf{V}_o(\omega) &= 42.9\angle 18.4^\circ \end{aligned}$$

Therefore,

$$v(t) = 42.9 \cos(1000t + 18.4^\circ) \text{ V}$$

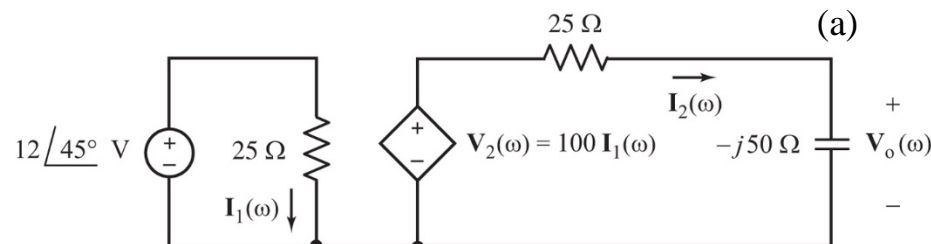


FIGURE 10.4-11



Series Impedances

- Figure 10.5-1 shows two series elements connected to “Circuit A”.

We have $\mathbf{I} = \mathbf{I}_1 = \mathbf{I}_2$ and $\mathbf{V} = \mathbf{V}_1 + \mathbf{V}_2 = \mathbf{Z}_1 \mathbf{I}_1 + \mathbf{Z}_2 \mathbf{I}_2 = (\mathbf{Z}_1 + \mathbf{Z}_2) \mathbf{I}$.

- Therefore, $\mathbf{Z}_{eq} = \mathbf{Z}_1 + \mathbf{Z}_2$
- This generalizes to the case of n series impedances

$$\mathbf{Z}_{eq} = \mathbf{Z}_1 + \mathbf{Z}_2 + \cdots + \mathbf{Z}_n$$

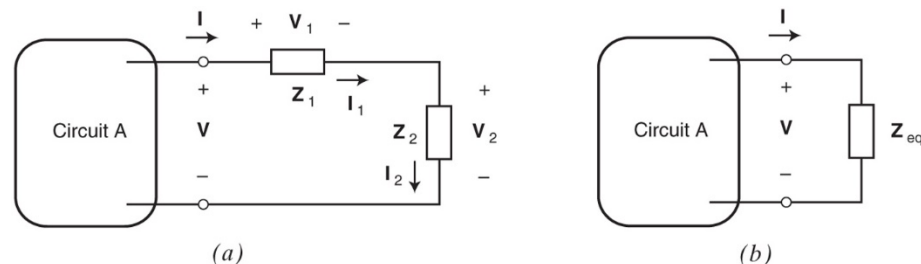


FIGURE 10.5-1



Parallel Impedances

- Figure 10.5-2 shows two parallel elements connected to “Circuit A”.

We have $\mathbf{V} = \mathbf{V}_1 = \mathbf{V}_2$ and $\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2 = \frac{\mathbf{V}_1}{\mathbf{Z}_1} + \frac{\mathbf{V}_2}{\mathbf{Z}_2} = \left(\frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} \right) \mathbf{I}$.

- Therefore,
$$\mathbf{Z}_{eq} = \frac{1}{\frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2}}$$

- This generalizes to the case of n series impedances

$$\mathbf{Z}_{eq} = \frac{1}{\frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \dots + \frac{1}{\mathbf{Z}_n}}$$

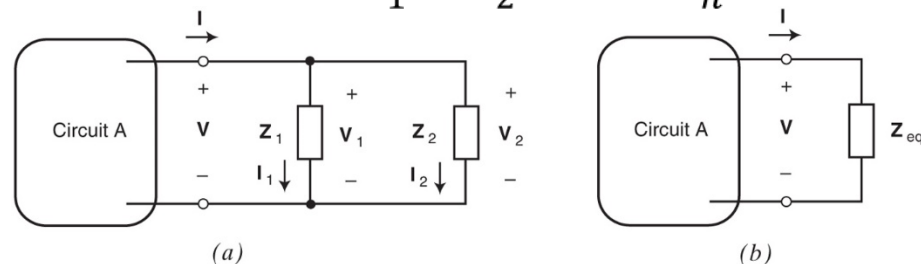


FIGURE 10.5-2



Example 10.5-1 Analysis of AC Circuits Using Impedances

- Determine the steady state current $i(t)$ in the RLC circuit shown in Figure 10.5-3a, using phasors and impedances.

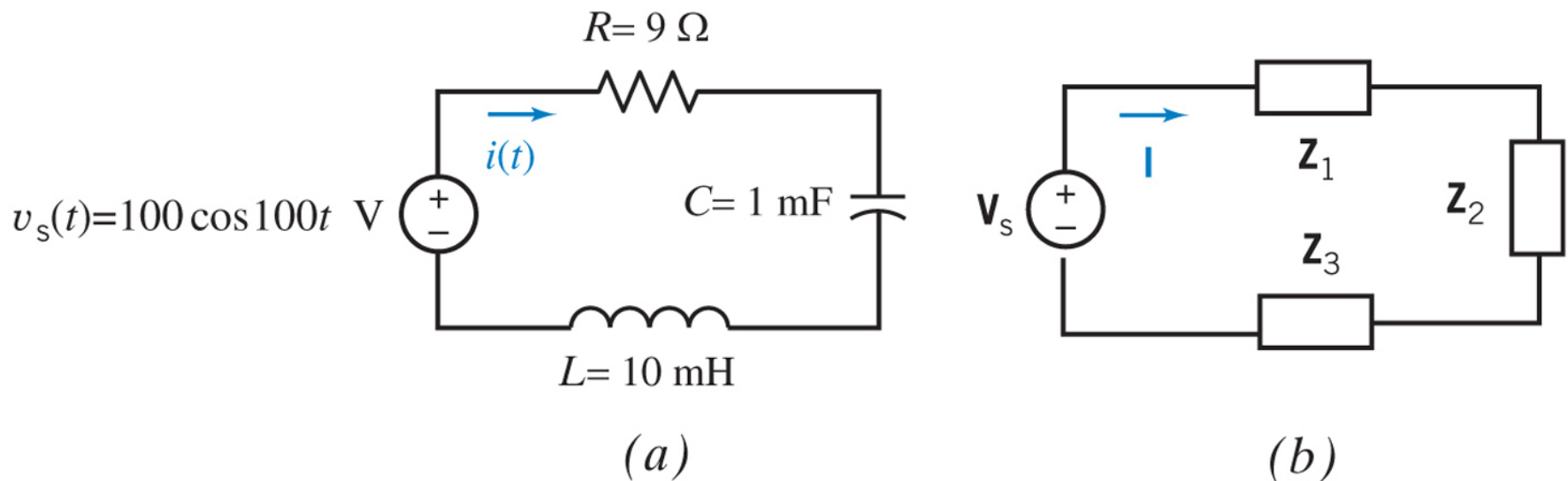


FIGURE 10.5-3



Solution

The input frequency is $\omega = 100 \text{ rad/s}$. Let's represent the circuit in using phasors and impedances as shown in (b)

$$\mathbf{Z}_1(\omega) = 9 \Omega, \mathbf{Z}_2(\omega) = \frac{1}{j\omega C} = -j10 \Omega, \text{ and } \mathbf{Z}_3(\omega) = j\omega L = j1 \Omega$$


The input phasor is $\mathbf{V}_s = 100\angle 0^\circ$

Using KVL,

$$\begin{aligned} \mathbf{V}_s &= \mathbf{I} \cdot (\mathbf{Z}_1(\omega) + \mathbf{Z}_2(\omega) + \mathbf{Z}_3(\omega)) \\ \Rightarrow \mathbf{I} &= \frac{\mathbf{V}_s}{\mathbf{Z}_1(\omega) + \mathbf{Z}_2(\omega) + \mathbf{Z}_3(\omega)} \\ &= \frac{100\angle 0^\circ}{9 - j10 + j1} = \frac{100\angle 0^\circ}{9\sqrt{2}\angle -45^\circ} \\ &= 7.86\angle 45^\circ \text{ A} \end{aligned}$$

Therefore,
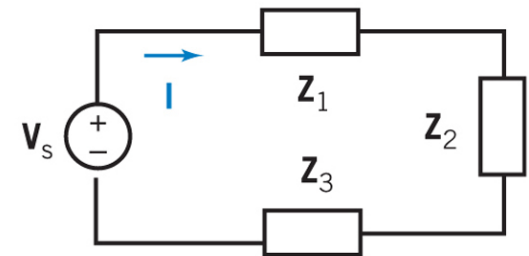
$$i(t) = 7.86 \cos(100t + 45^\circ) \text{ A}$$



(b)

FIGURE 10.5-3(b)



Example 10.5-2 Voltage Division Using Impedances

- Consider the circuit shown in Figure 10.5-4a. The input to the circuit is the voltage of the voltage source,

$$v_s(t) = 7.28 \cos(4t + 77^\circ) \text{ V}$$

The output is the voltage across the inductor $v_o(t)$. Determine the steady-state output voltage $v_o(t)$.

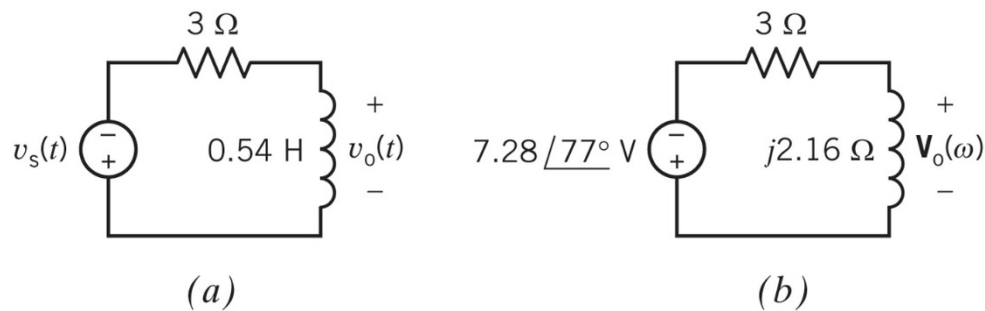


FIGURE 10.5-4



Solution

The input and output are sinusoids of the same frequency. After the circuit has reached steady state, voltage divider is also satisfied at ac circuit.

$$\mathbf{V}_s = 7.28\angle 77^\circ, \quad \omega = 4$$

$$\mathbf{V}_o(\omega) = \frac{\mathbf{Z}_L}{\mathbf{Z}_R + \mathbf{Z}_L} \mathbf{V}_s = \frac{2.16\angle 90^\circ}{3\angle 0^\circ + 2.16\angle 90^\circ} (-7.28\angle 77^\circ) = 4.25\angle 131.25^\circ$$

Therefore,

$$v_o(t) = 4.25 \cos(4t + 131.25^\circ) \text{ V}$$

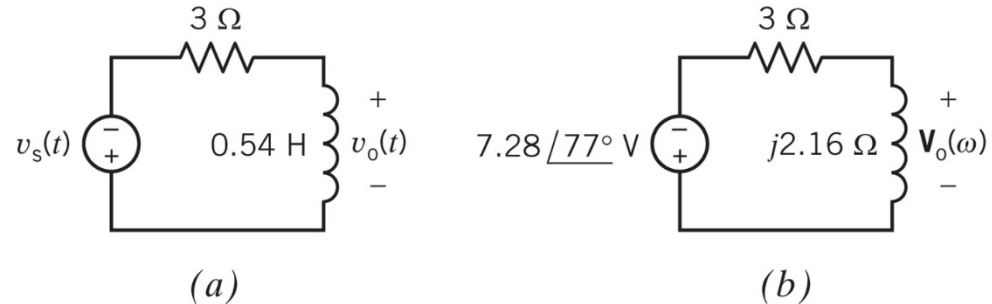


FIGURE 10.5-4



Example 10.5-3 AC Circuit Analysis

- Consider the circuit shown in Figure 10.5-5a. The input to the circuit is the voltage of the voltage source,

$$v_s(t) = 7.68 \cos(2t + 47^\circ) \text{ V}$$

The output is the voltage across the resistor,

$$v_o(t) = 1.59 \cos(2t + 125^\circ) \text{ V}$$

Determine capacitance C of the capacitor.

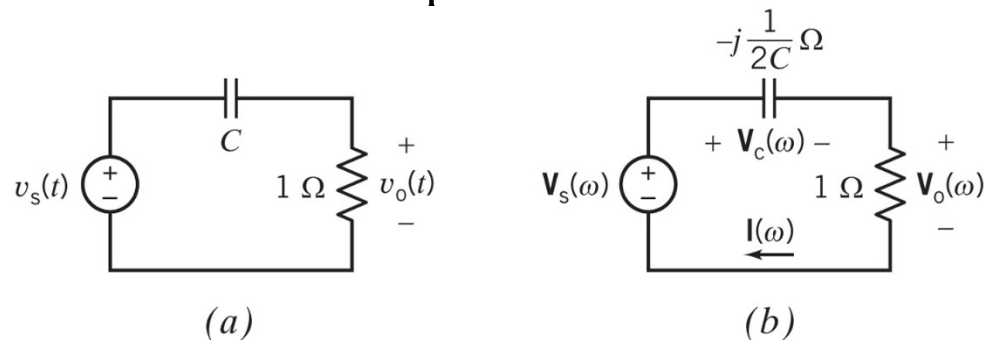


FIGURE 10.5-5



Solution

The input and output are sinusoids of the same frequency. After the circuit has reached steady state, voltage divider is also satisfied at ac circuit.

$$\mathbf{V}_s = 7.68\angle 47^\circ, \mathbf{V}_o = 1.59\angle 125^\circ, \omega = 2$$

$$\mathbf{V}_o = \frac{\mathbf{Z}_R}{\mathbf{Z}_R + \mathbf{Z}_C} \mathbf{V}_s \Rightarrow \mathbf{Z}_C = \frac{\mathbf{V}_s}{\mathbf{V}_o} \mathbf{Z}_R - \mathbf{Z}_R = \left(\frac{\mathbf{V}_s}{\mathbf{V}_o} - 1 \right) \mathbf{Z}_R$$

$$\mathbf{Z}_C = \left(\frac{7.68\angle 47^\circ}{1.59\angle 125^\circ} - 1 \right) 1\angle 0^\circ = 4.27\angle -90^\circ = \frac{1}{j2C} = \left(\frac{1}{C} \angle 0^\circ \right) (0.5\angle -90^\circ)$$

Therefore,

$$C = 0.106 \text{ F}$$



Example 10.5-4 AC Circuit Analysis

- Consider the circuit shown in Figure 10.5-6a. The input to the circuit is the voltage of the voltage source $v_s(t)$, and the output is the voltage across the $4\text{-}\Omega$ resistor, $v_o(t)$. When the input is $v_s(t) = 8.93 \cos(2t + 54^\circ) \text{ V}$, the corresponding output is $v_o(t) = 3.83 \cos(2t + 83^\circ) \text{ V}$. Determine the voltage across the $9\text{-}\Omega$ resistor $v_a(t)$ and the value of the capacitance C of the capacitor.

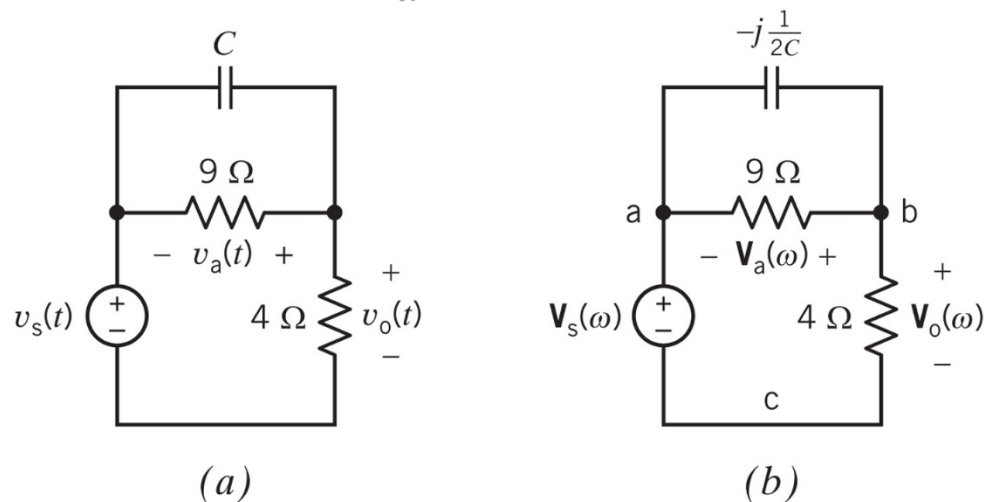


FIGURE 10.5-6



Solution (1/2)

The input and output are sinusoids of the same frequency. After the circuit has reached steady state, voltage divider is also satisfied at ac circuit.

$$\mathbf{V}_s(\omega) = 8.93\angle 54^\circ, \mathbf{V}_o(\omega) = 3.83\angle 83^\circ, \omega = 2$$

$$\begin{aligned}\mathbf{V}_a(\omega) &= \mathbf{V}_o(\omega) - \mathbf{V}_s(\omega) = 3.83\angle 83^\circ - 8.93\angle 54^\circ = (0.47 + j3.80) - (5.25 + j7.22) \\ &= -4.78 - j3.42 = 5.88\angle 216^\circ\end{aligned}$$

Therefore, the voltage across the 9- Ω resistor $v_a(t)$ is given

$$v_a(t) = 5.88 \cos(2t + 216^\circ) \text{ V}$$

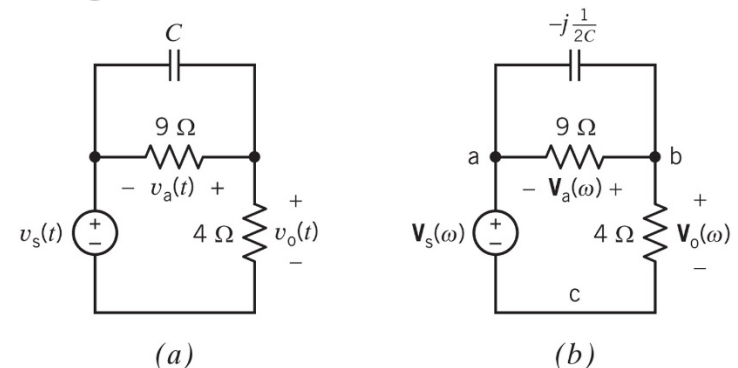


FIGURE 10.5-6



Solution (2/2)

Then, applying KCL at node b, we have

$$\mathbf{I}_{9-\Omega} + \mathbf{I}_C = \mathbf{I}_{4-\Omega} \Rightarrow \frac{-\mathbf{V}_a(\omega)}{\mathbf{Z}_{9-\Omega}} + \frac{-\mathbf{V}_a(\omega)}{\mathbf{Z}_C} = \frac{\mathbf{V}_o(\omega)}{\mathbf{Z}_{4-\Omega}} \Rightarrow -\mathbf{V}_a(\omega) \left\{ \frac{1}{\mathbf{Z}_{9-\Omega}} + \frac{1}{\mathbf{Z}_C} \right\} = \frac{\mathbf{V}_o(\omega)}{\mathbf{Z}_{4-\Omega}}$$

$$-5.88 \angle 216^\circ \left\{ \frac{1}{9 \angle 0^\circ} + \frac{1}{-j \frac{1}{2C}} \right\} = 5.88 \angle 36^\circ \left(\frac{1}{9} + j2C \right) = \frac{3.83 \angle 83^\circ}{4 \angle 0^\circ}$$

$$\Rightarrow \frac{1}{9} + 2Cj = \frac{0.958 \angle 83^\circ}{5.88 \angle 36^\circ} = 0.163 \angle 47^\circ$$

$$\Rightarrow C = \frac{0.163 \angle 47^\circ - \frac{1}{9}}{2j} = 0.06 \text{ F}$$



Example 10.5-5 Equivalent Impedance

- Determine the equivalent impedance of circuit shown in Figure 10.5-7a at the frequency $\omega = 1000 \text{ rad/s}$.

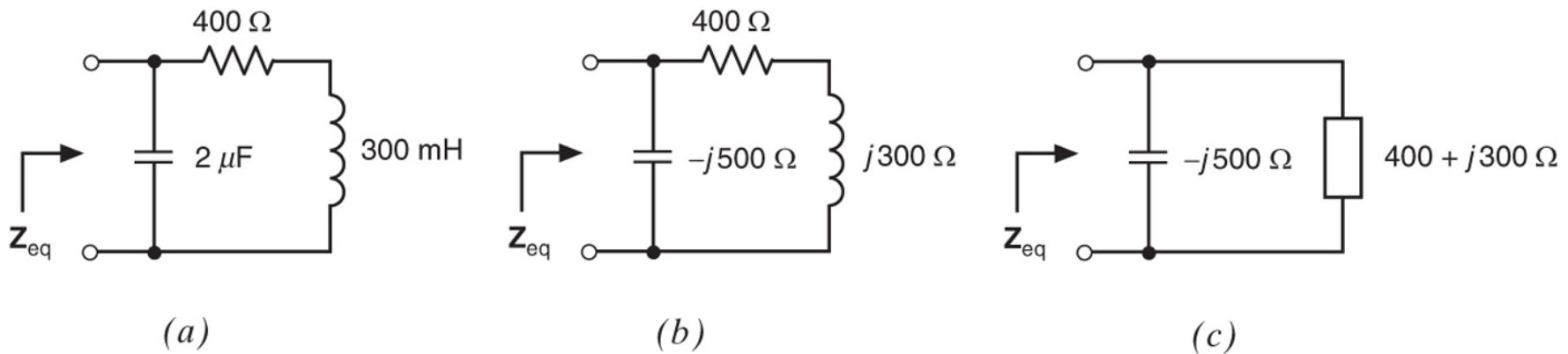


FIGURE 10.5-7



Solution

Represent the circuit in the frequency domain shown in Figure 10.5-7(b). Then replace series impedance by an equivalent impedance, we have the circuit shown in Figure 10.5-7(c). Then find the equivalent impedance of parallel impedances.

$$\mathbf{Z}_{eq} = \mathbf{Z}_C \parallel (\mathbf{Z}_R + \mathbf{Z}_L) = \frac{\mathbf{Z}_C(\mathbf{Z}_R + \mathbf{Z}_L)}{\mathbf{Z}_C + (\mathbf{Z}_R + \mathbf{Z}_L)}$$

Since $\omega = 1000 \text{ rad/s}$,

$$\mathbf{Z}_R = 400 \ \Omega, \mathbf{Z}_L = j\omega L = j300 \ \Omega, \text{ and } \mathbf{Z}_C = \frac{1}{j\omega C} = -j500 \ \Omega$$


Therefore,

$$\mathbf{Z}_{eq} = \frac{-j500(400 + j300)}{-j500 + (400 + j300)} = 559.0 \angle -26.5^\circ \Omega$$



Mesh and Node Equations

- Ohm's and Kirchhoff's laws can be used to an ac circuits as well as dc circuits.
- Therefore, mesh and node equations are available with ac circuits as following convention

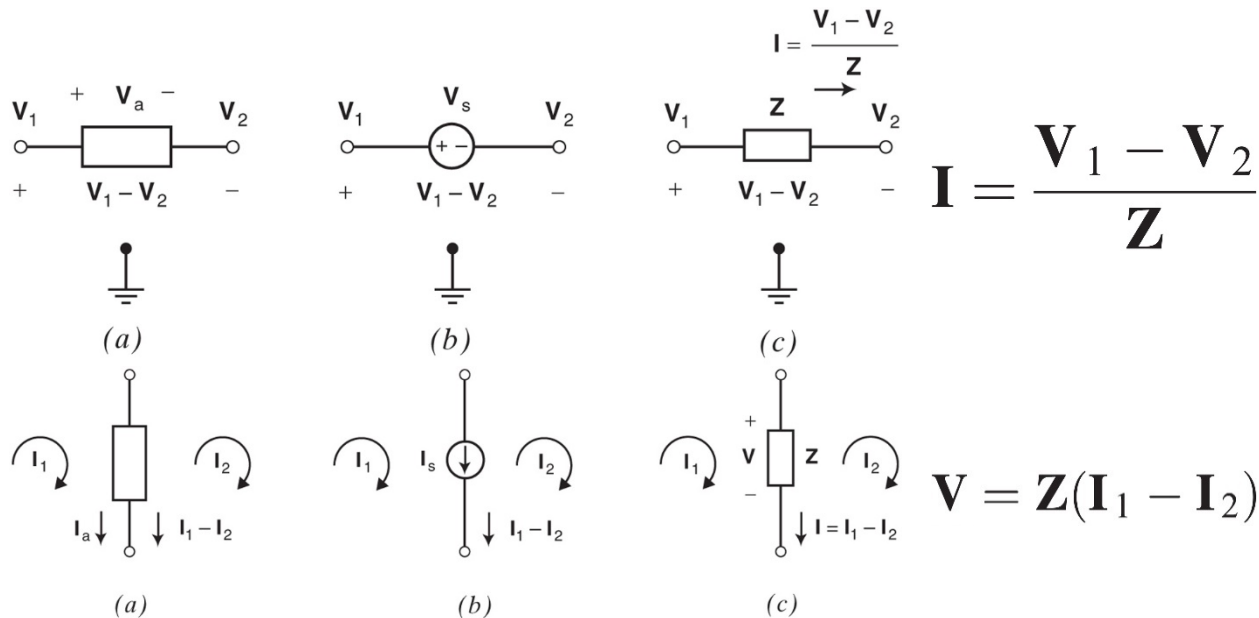

Example 10.6-2 Mesh Equations for AC Circuits

- Determine the mesh currents for the circuit below.

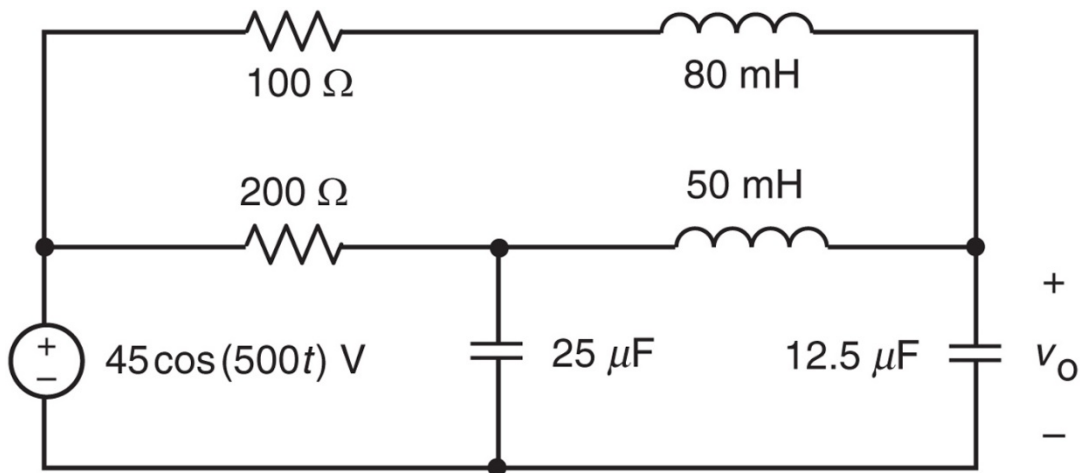


FIGURE 10.6-7



Solution

- Represent the circuit in frequency domain.

$$\mathbf{Z}_C = \frac{1}{j\omega C} \quad \mathbf{Z}_L = j\omega L$$



- Apply KVL to each mesh.

$$\begin{aligned} 100I_1 + j40I_1 - j25(I_2 - I_1) &= 0 \\ 200(I_2 - I_1) - j80(I_2 - I_3) - 45\angle 0 &= 0 \\ -j25(I_2 - I_1) - j160I_3 + j80(I_1 - I_3) &= 0 \end{aligned}$$

$$I_1 = 0.374\angle 115 \text{ [A]}$$

$$I_2 = 0.575\angle 25 \text{ [A]}$$

$$I_3 = 0.171\angle 28 \text{ [A]}$$

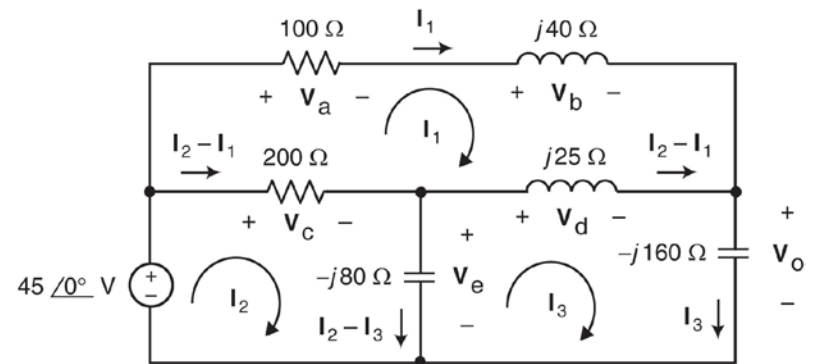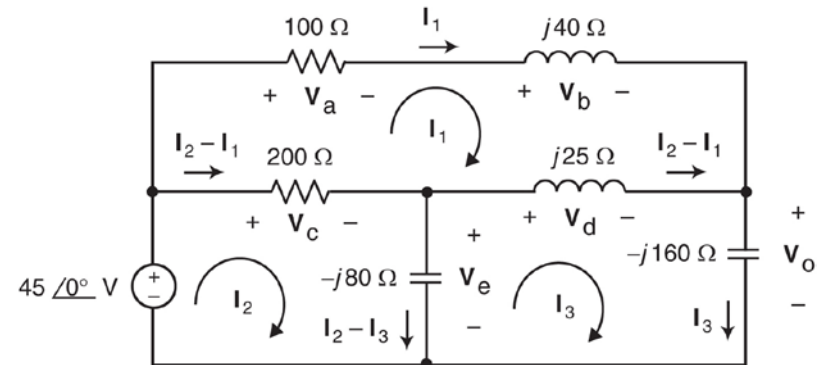

Example 10.6-3 Node Equations for AC Circuits with a Supernode

- The input to the ac circuit shown in Figure 10.6-10 is the voltage source voltage

$$v_s(t) = 10 \cos(10t) \text{ V}$$

The output is the current $i(t)$ in resistor R_1 . Determine $i(t)$.

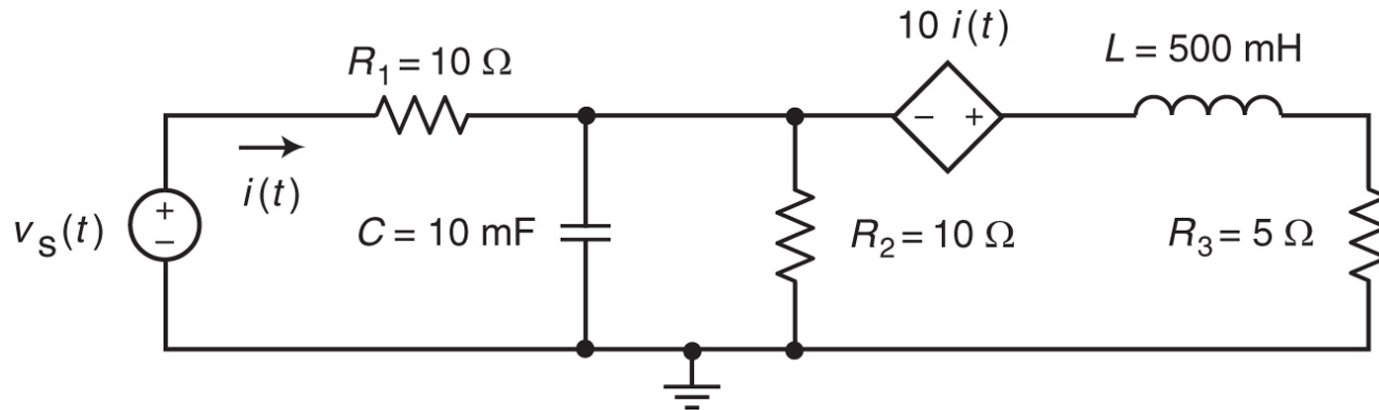


FIGURE 10.6-10



Solution (1/3)

First, we will represent the circuit in the frequency domain using phasors and impedances. The impedances of the capacitor and inductor are

$$\mathbf{Z}_C = -j \frac{1}{10(0.010)} = -j10 \ \Omega \text{ and } \mathbf{Z}_L = j10(0.5) = j5 \ \Omega$$

The frequency domain representation of the circuit is shown in Figure 10.6-11

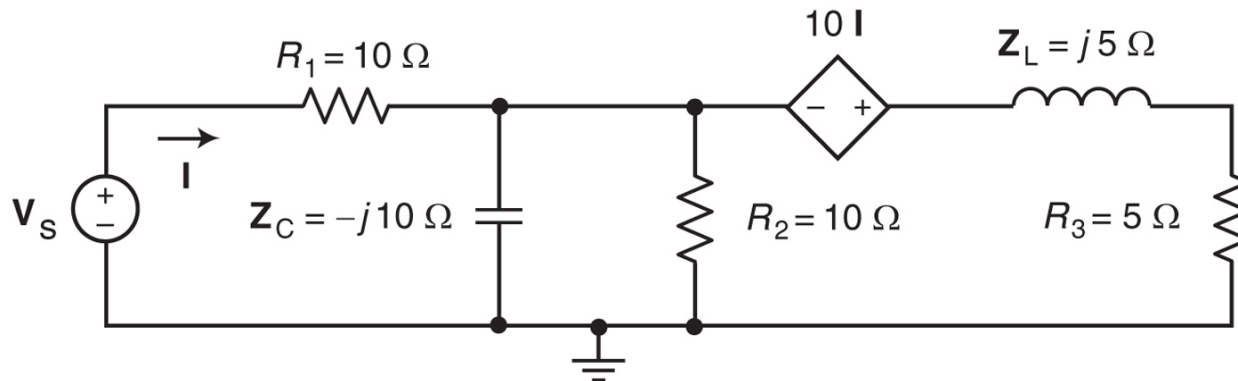


FIGURE 10.6-11



Solution (2/3)

We can analyze this circuit by node equations. To simplify this process, replace parallel and series impedances by equivalent impedances as shown in Figure 10.6-12.

$$\mathbf{Z}_C = -j \frac{1}{10(0.010)} = -j10 \text{ } \Omega \text{ and } \mathbf{Z}_L = j10(0.5) = j5 \text{ } \Omega$$

The frequency domain representation of the circuit is shown in Figure 10.6-11

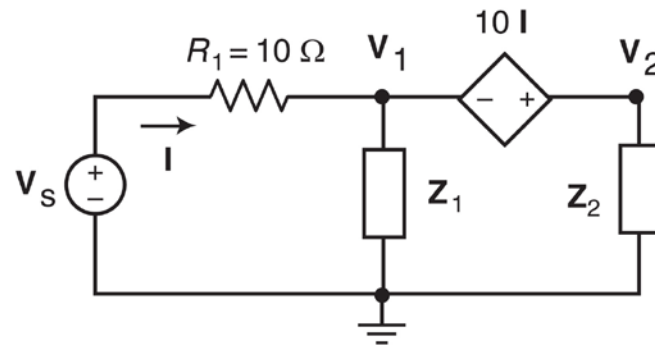


FIGURE 10.6-12

$$\mathbf{Z}_1 = 10 || (-j10) = \frac{-j100}{10-j10} = 5 - j5 \text{ } \Omega \text{ and } \mathbf{Z}_2 = 5 + j5 \text{ } \Omega$$



Solution (3/3)

Next, consider the dependent source in Figure 10.6-12. We can find \mathbf{I} and also express the dependent source voltage as

$$\mathbf{I} = \frac{\mathbf{V}_s - \mathbf{V}_1}{R_1} \quad \text{and} \quad 10\mathbf{I} = \mathbf{V}_2 - \mathbf{V}_1$$

Apply KCL to supernode containing dependent source identified in Figure 10.6-12 to get

$$\mathbf{I} = \frac{\mathbf{V}_1}{\mathbf{Z}_1} + \frac{\mathbf{V}_2}{\mathbf{Z}_2} = \frac{\mathbf{V}_1}{\mathbf{Z}_1} + \frac{\mathbf{V}_1 + 10\mathbf{I}}{\mathbf{Z}_2} \Rightarrow (\mathbf{Z}_1 + \mathbf{Z}_2)\mathbf{V}_1 + \mathbf{Z}_1(10 - \mathbf{Z}_2)\mathbf{I} = 0$$

Organizing Eqs. Into matrix form, we get

$$\begin{bmatrix} 1 & R_1 \\ \mathbf{Z}_1 + \mathbf{Z}_2 & \mathbf{Z}_1(10 - \mathbf{Z}_2) \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I} \end{bmatrix} = \begin{bmatrix} \mathbf{V}_s \\ 0 \end{bmatrix}$$

Solving these equations, perhaps using MATLAB, gives

$$\mathbf{V}_1 = 4.4721 \angle 63.4^\circ \text{ V}, \quad \text{and} \quad \mathbf{I} = 0.89443 \angle -26.6^\circ \text{ A}$$

In the time domain, the output current is

$$i(t) = 0.89443 \cos(10t - 26.6^\circ) \text{ A}$$



Example 10.6-4 AC Circuits Containing OP Amps

- The input to the ac circuit shown in figure below is the voltage source voltage

$$V_s(t) = 125 \cos(500t + 15) \text{ [mV]}$$

Determine the output voltage $v_o(t)$.

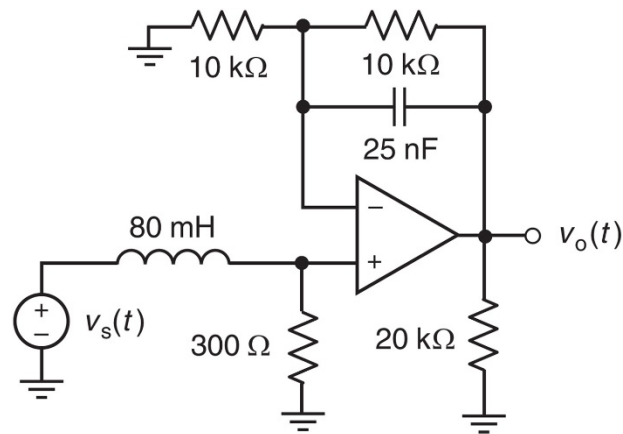


FIGURE 10.6-13




Solution

- Represent the circuit in frequency domain.

$$\mathbf{Z}_C = \frac{1}{j\omega\mathbf{C}} \quad \mathbf{Z}_L = j\omega\mathbf{L}$$

- Apply KCL at the each node of OP amp

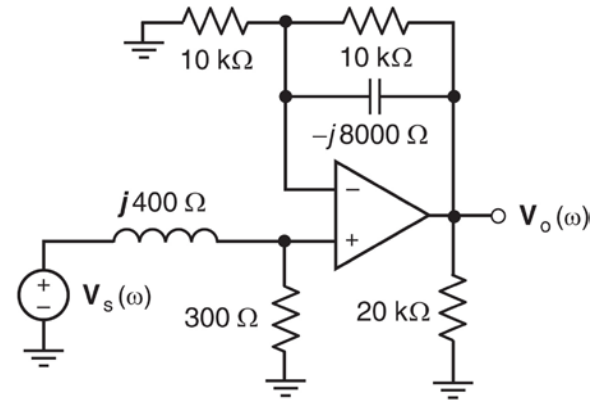

$$\frac{\mathbf{V}_s - \mathbf{V}_a}{j400} = \frac{\mathbf{V}_a}{300} + 0 \rightarrow \mathbf{V}_s = \mathbf{V}_a \left(1 + \frac{j400}{300} \right) \rightarrow \mathbf{V}_a = \frac{300}{300 + j400} \mathbf{V}_s \dots (1)$$

$$\frac{\mathbf{V}_a - \mathbf{V}_o}{10000} + \frac{\mathbf{V}_a}{10000} + \frac{\mathbf{V}_a - \mathbf{V}_o}{-j8000} = 0 \dots (2)$$

- Equation (2) gives

$$\begin{aligned} \mathbf{V}_o &= \left(\frac{16 + j10}{8 + j10} \right) \mathbf{V}_a = \left(\frac{16 + j10}{8 + j10} \right) \left(\frac{300}{300 + j400} \right) \mathbf{V}_s = (0.884 \angle -72.5^\circ) \mathbf{V}_s \\ &= (0.884 \angle -72.5^\circ)(125 \angle 15^\circ) = 111 \angle -57.5^\circ \end{aligned}$$

$$v_o(t) = 111 \cos(500t - 57.5^\circ) [mV]$$




Thévenin and Norton Equivalent Circuit

- Thévenin and Norton equivalent circuits of an ac circuit can be determined by the open-circuit voltage V_{OC} , the short-circuit current I_{SC} , and the Thévenin impedance Z_t .

They are related by the equation

$$V_{oc} = Z_t I_{sc}$$

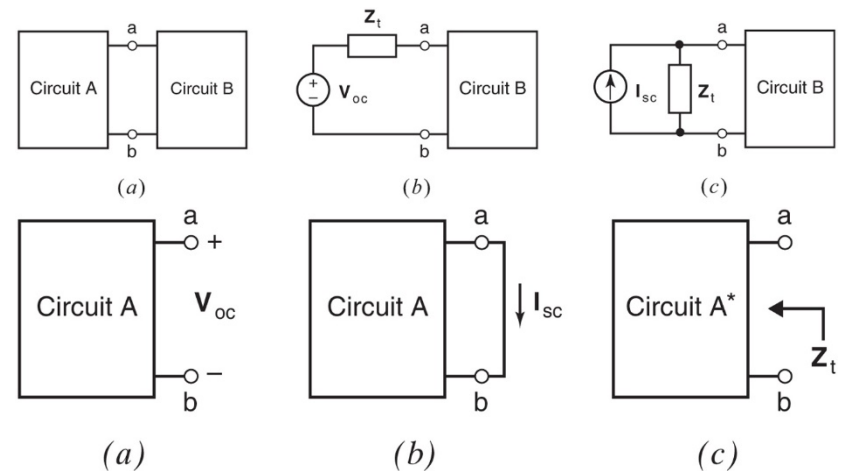

Example 10.7-1 Thévenin Equivalent Circuit

- Find the Thévenin equivalent circuit of the ac circuit in Figure shown in Figure 10.7-3.

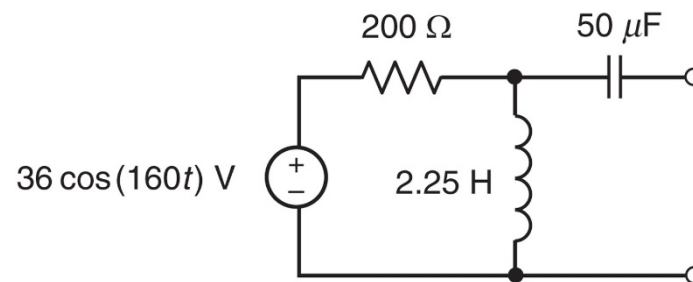


FIGURE 10.7-3



Solution (1/3)

Begin by representing the circuit from Figure 10.7-3 in the frequency domain, using phasors and impedances. As shown in Figure 10.7-4.

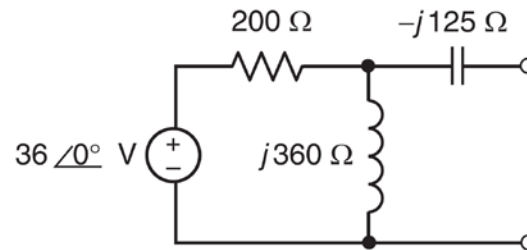


FIGURE 10.7-4

Next, we determine the open-circuit voltage and the Thévenin impedance using circuits shown in Figure 10.7-5.

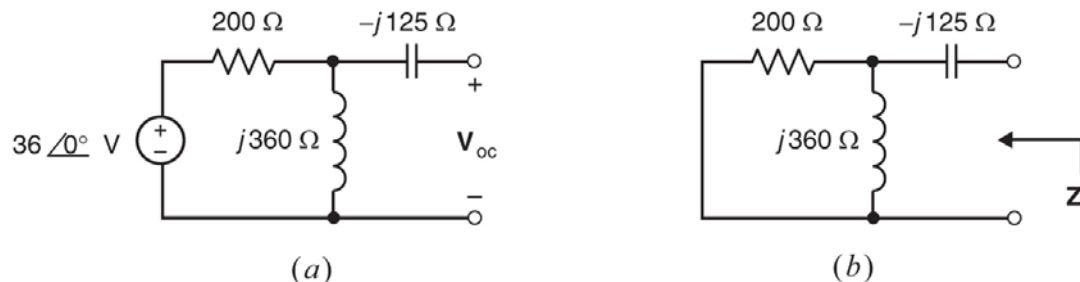


FIGURE 10.7-5



Solution (1/3)

For the open-circuit voltage, using voltage division, we calculate

$$\mathbf{V}_{oc} = \frac{j360}{200 + j360} 36\angle 0^\circ = 31.470\angle 29.1^\circ \text{ V}$$

Next, the Thévenin impedance is determined using circuit shown in Figure 10.7-5 b. Then we calculate

$$\mathbf{Z}_t = -j125 + \frac{200(j360)}{200 + j360} = 152.83 - j40.094 = 158\angle -14.7^\circ \Omega$$

Therefore, the Thévenin equivalent circuit is as below

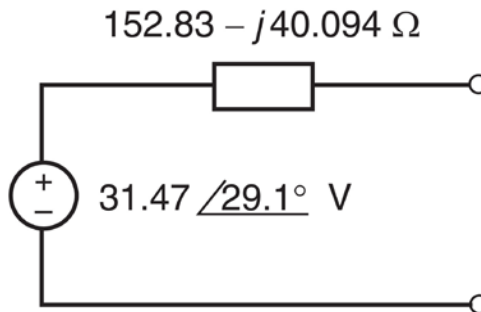



FIGURE 10.7-6




Source Transformation

- Thévenin and Norton equivalent circuits of an ac circuit can be transformed to each other like those of an dc circuit.

$$V_{oc} = Z_t I_{sc}$$

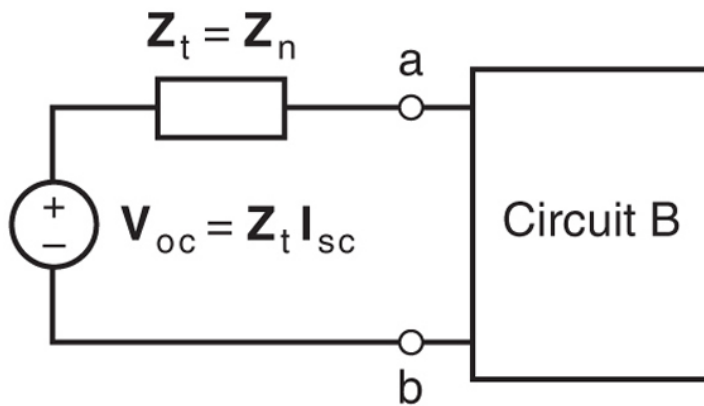

(a)

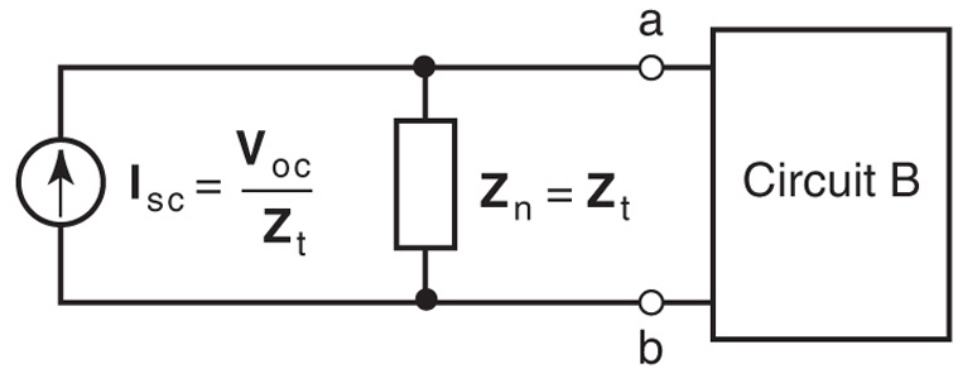

(b)

FIGURE 10.7-11



Example 10.7-3 Source Transformation

- Use source transformation and equivalent impedance to find the Thévenin and equivalent circuit of an ac circuit shown in Figure 10.7-3


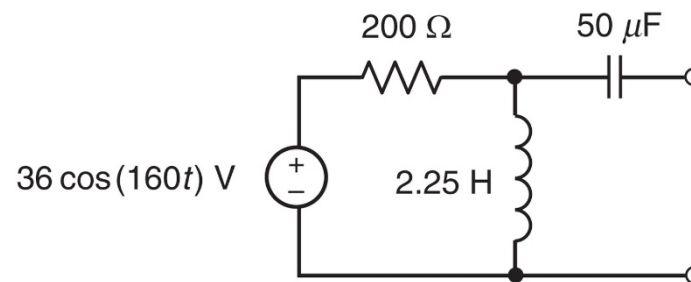


FIGURE 10.7-3

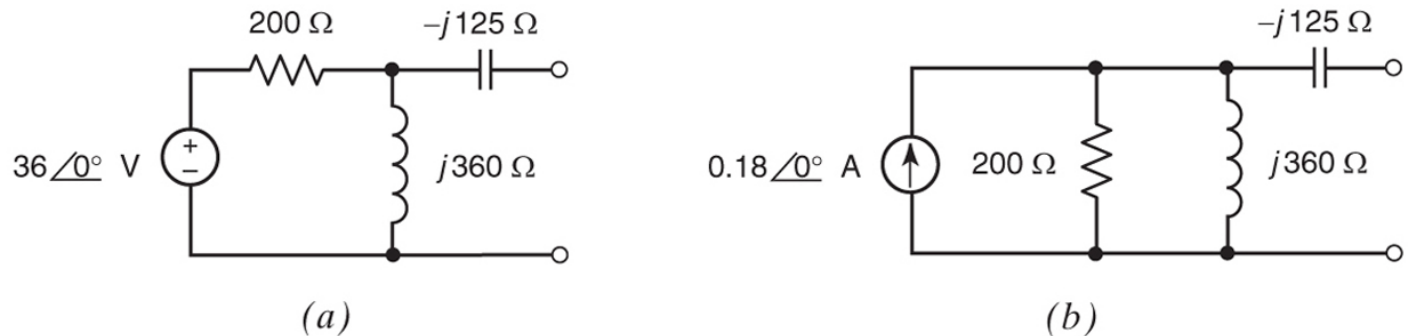

Solution (1/3)

Figure 10.7-12 illustrates the process. Figure 10.7-12a identifies a series combination of a voltage source and impedance. A source transformation replaces this series combination with a parallel combination of a current source and impedance in Figure 10.7-12b.




Then we calculate the equivalent impedance of $200\text{-}\Omega$ resistor and $j360\text{-}\Omega$ inductor to obtain Figure 10.7-12c


$$200 \parallel j360 = \frac{(200)(j360)}{200 + j360} = \frac{72000 \angle 90^\circ}{411.8 \angle 60.9^\circ} = 174.8 \angle 29.1^\circ$$



Solution (2/3)

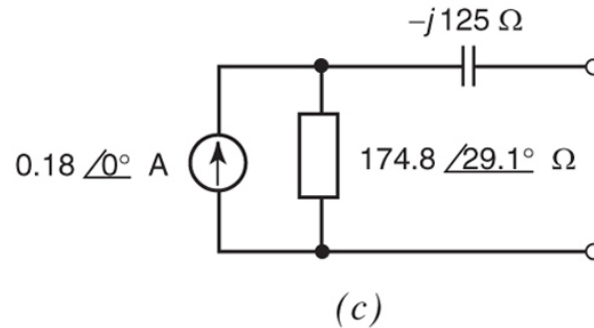

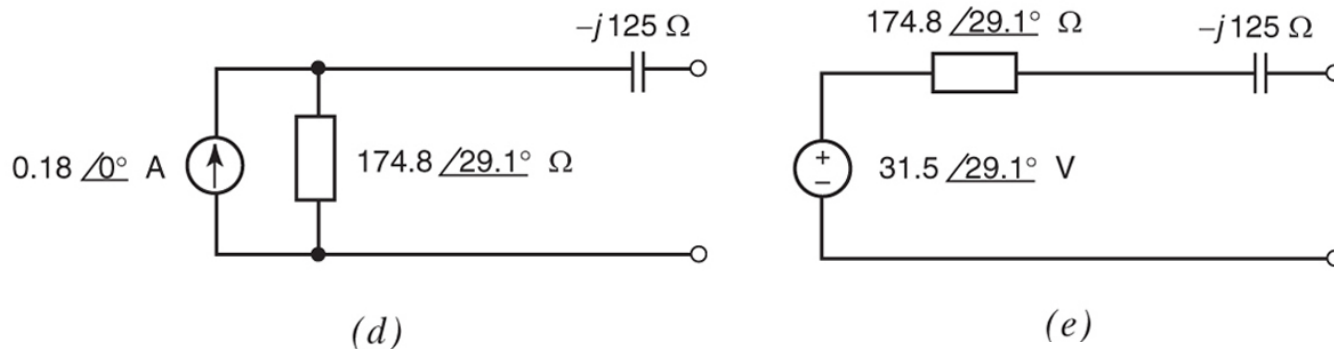Then, Figure 10.7-12 c and d shows a source transformation replacing the parallel combination with a series combination of a voltage source and impedance in Figure 10.7-12d




Solution (3/3)

Then we calculate the equivalent impedance of $174.8\angle 29.1^\circ\text{-}\Omega$ impedance and $-j125\text{-}\Omega$ inductor to obtain Figure 10.7-12f

$$174.8\angle 29.1^\circ - j125 = 152.83 + j84.907 - j125 = 152.83 - j40.094$$

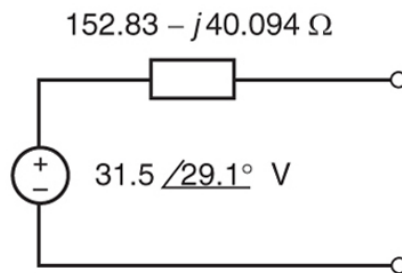Then, Figure 10.7-12 f shows the Thévenin equivalent circuit of Figure 10.7-3.



(f)



Superposition

- Also, the superposition is available with ac circuits **with linear elements**.
- As we did with dc circuits, when we set all but one input to zero, the other inputs become 0-V voltage sources(short circuits) and 0-A current sources(open circuits)



Example 10.8-1 Surperposition

- Determine the voltage $v_o(t)$ across the $8\text{-}\Omega$ resistor in the circuit shown in Figure 10.8-1.

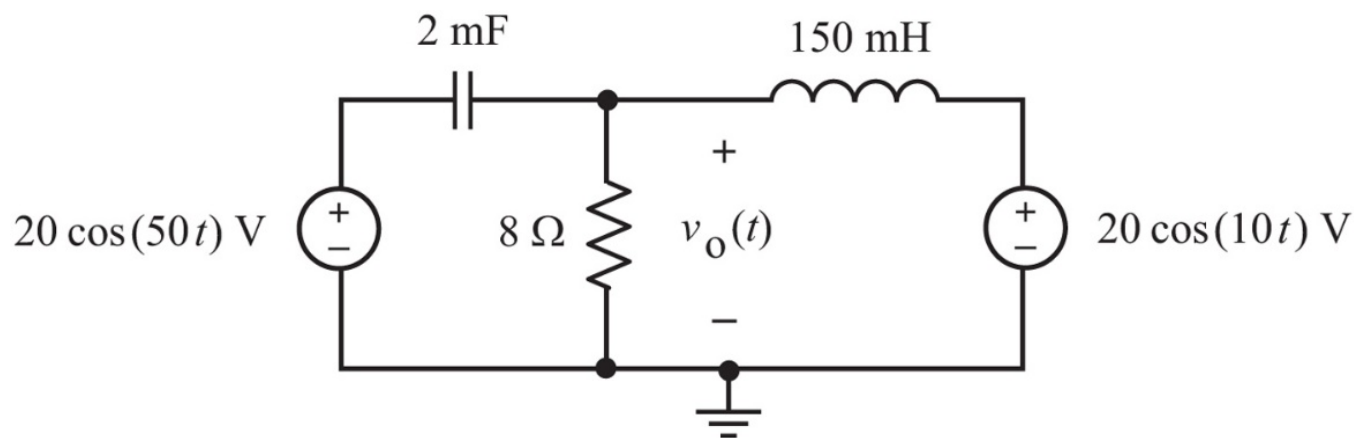


FIGURE 10.8-1



Solution (1/3)

The voltage $v_o(t)$ is caused by two sinusoidal sources, one having a frequency of 50 rad/s and the other having a frequency of 10 rad/s. Let $v_{o1}(t)$ be the part of $v_o(t)$ caused by 50 rad/s source acting alone, and let $v_{o2}(t)$ be the part of $v_o(t)$ by 10 rad/s source acting alone. Figure 10.8-2 shows each circuits used to calculate $v_{o1}(t)$ and $v_{o2}(t)$.

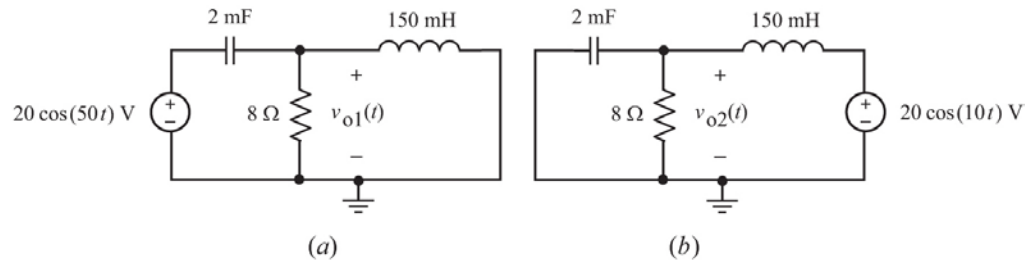


FIGURE 10.8-2

Then the frequency domain representations are shown in Figure 10.8-3.

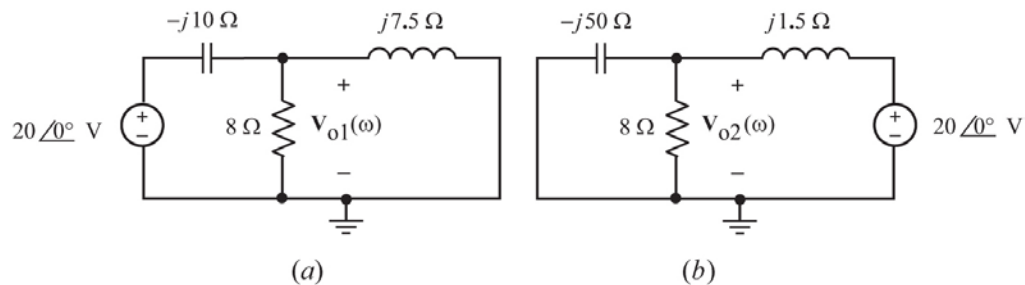


FIGURE 10.8-3



Solution (2/3)

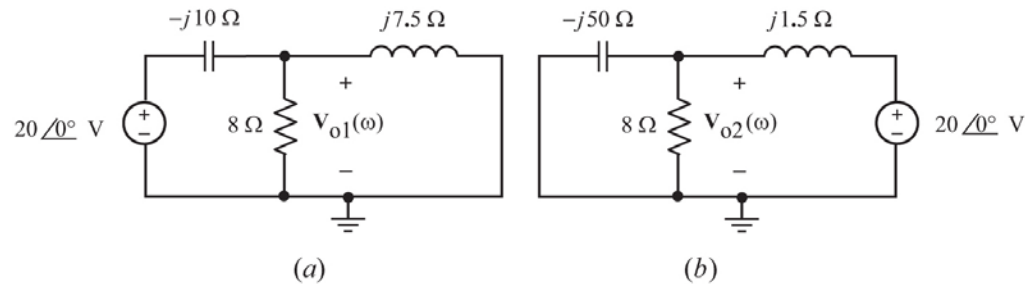


FIGURE 10.8-3

Using equivalent impedance and voltage division in Figure 10.8-3a, we calculate

$$\mathbf{V}_{o1} = \frac{\frac{8(j7.5)}{8 + j7.5}}{-j10 + \frac{8(j7.5)}{8 + j7.5}} (20\angle 0^\circ) = 15.46\angle 104.9^\circ$$

Similarly in Figure 10.8-3b, we calculate

$$\mathbf{V}_{o2} = \frac{\frac{8(-j50)}{8 - j50}}{j1.5 + \frac{8(-j50)}{8 - j50}} (20\angle 0^\circ) = 20.24\angle -10.94^\circ$$

The corresponding sinusoids are

$$v_{o1}(t) = 15.46 \cos(50t + 104.9^\circ) \text{ and } v_{o2}(t) = 20.24 \cos(10t - 10.94^\circ)$$



Solution (3/3)

The response to both sources working together is equal to the sum of the responses to the two sources working separately, therefore

$$v_o(t) = v_{o1}(t) + v_{o2}(t) = 15.46 \cos(50t + 104.9^\circ) + 20.24 \cos(10t - 10.94^\circ)$$

The output voltage $v_o(t)$ is plotted in Figure 10.8-4. As expected, it is not sinusoid.

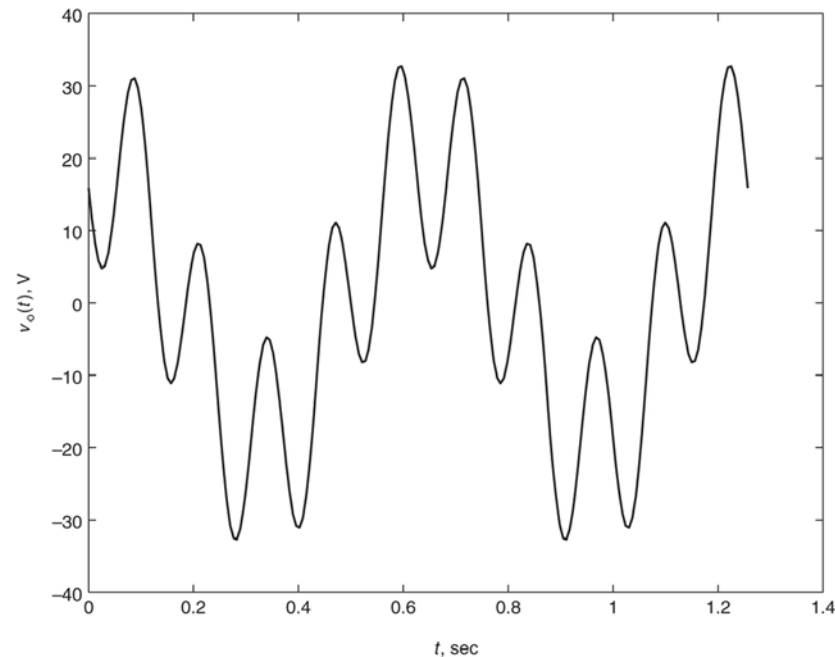


FIGURE 10.8-4



Phase Diagram

- A **phasor diagram** is a **graphical representation** of phasors and their relationship on complex plane.
- Consider a circuit represented in the time and frequency domain in Figure 10.9-1. The input is the current of the current source, $i(t)$.

Then phasor voltages across the impedances in Figure 10.9-1(b) are given by

$$\mathbf{V}_R = R(I_m \angle 0^\circ), \mathbf{V}_L = j\omega L(I_m \angle 0^\circ) = \omega L I_m \angle 90^\circ, \text{ and } \mathbf{V}_C = \frac{1}{j\omega C} (I_m \angle 0^\circ) = \frac{I_m}{\omega C} \angle -90^\circ$$

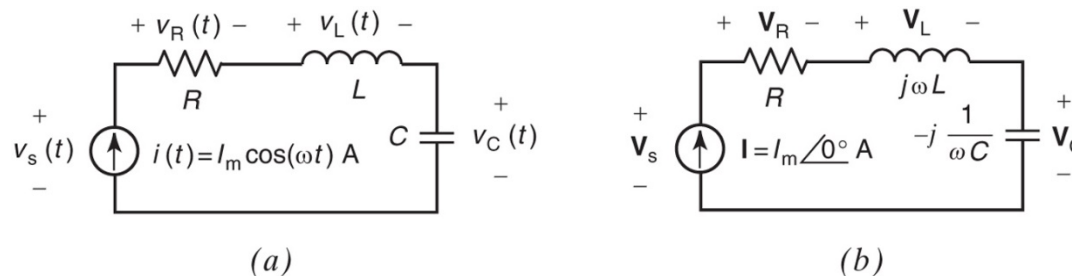


FIGURE 10.9-1



Phase Diagram (cont'd)

- Then the voltage across the input current source \mathbf{V}_s is given by,

$$\begin{aligned}\mathbf{V}_s &= \mathbf{V}_R + \mathbf{V}_L + \mathbf{V}_C = RI_m\angle 0^\circ + \omega LI_m\angle 90^\circ + \frac{I_m}{\omega C}\angle -90^\circ \\ &= I_m\angle 0^\circ \left(R + j\omega L - j\frac{1}{\omega C} \right) = RI_m + j \left(\omega L - \frac{1}{\omega C} \right) I_m\end{aligned}$$

This phasor is shown in complex plane in Figure 10.9-2(c)

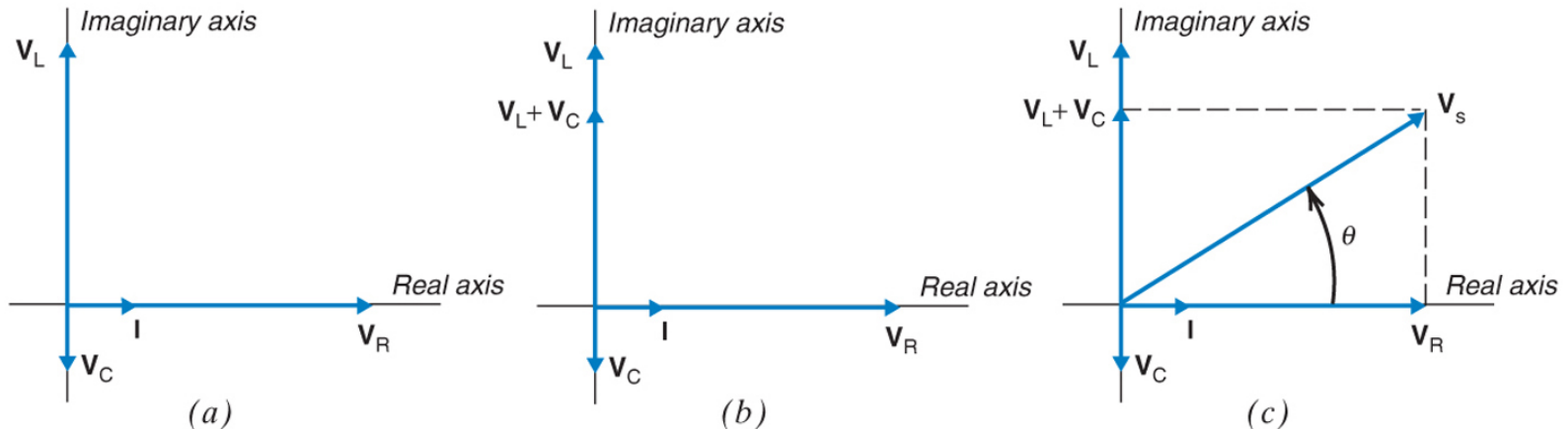


FIGURE 10.9-2



Example 10.9-1 Phasor Diagrams

- Consider the circuit shown in Figure 10.9-1a when $R = 80 \Omega$, $L = 8 \text{ H}$, $C = 5 \text{ mF}$ and

$$i(t) = 0.25 \cos(10t) \text{ A}$$

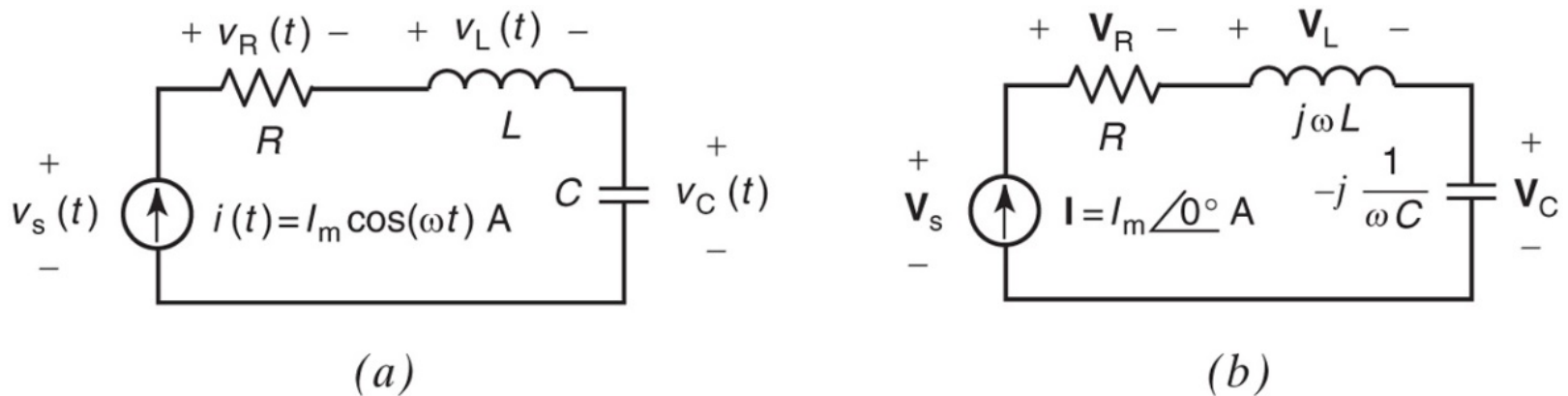


FIGURE 10.9-1



Solution

Noticing that $\omega = 10 \text{ rad/s}$, we calculate

$$j\omega L = j80 \Omega \text{ and } -j\frac{1}{\omega C} = -j\frac{1}{0.05} = -j20 \Omega$$

The phasor voltages across the impedances in Figure 10.9-1b are

$$\mathbf{V}_R = 80(0.25\angle 0^\circ) = 20\angle 0^\circ \text{ V}, \mathbf{V}_L = j80(0.25\angle 0^\circ) = 20\angle 90^\circ \text{ V},$$
$$\text{and } \mathbf{V}_C = -j20(0.25\angle 0^\circ) = 5\angle -90^\circ \text{ V}$$

These phasors are drawn in the complex plane in Figure 10.9-2a.

The phasor $\mathbf{V}_L + \mathbf{V}_C$ shown in the complex plane in Figure 10.9-2b is given by

$$\mathbf{V}_L + \mathbf{V}_C = j20 - j5 = 15\angle 90^\circ \text{ V}$$

Using KVL gives

$$\mathbf{V}_S = \mathbf{V}_R + (\mathbf{V}_L + \mathbf{V}_C) = 20 + j15 = 25\angle 36.9^\circ \text{ V}$$

This phasor is shown in the complex plane in Figure 10.9-2c

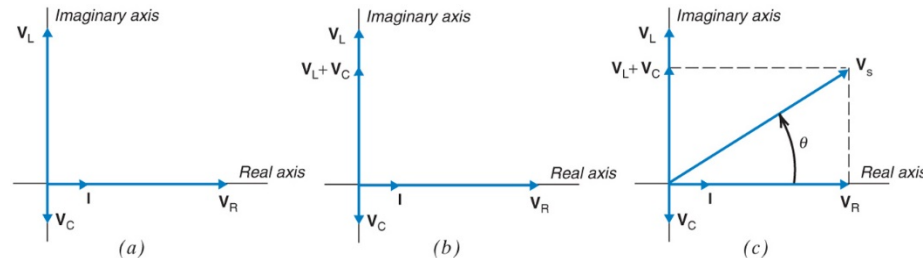


FIGURE 10.9-2



OP-Amps in AC Circuits

- Figure 10.10-1 shows two frequently used op-amp circuits.

The ratio of output-to-input voltage V_o/V_s for inverting amplifier (a) is determined by

$$\frac{V_o}{V_s} = -\frac{Z_2}{Z_1}$$

Then for noninverting amplifier (b) is determined by

$$\frac{V_o}{V_s} = \frac{Z_1 + Z_2}{Z_1}$$

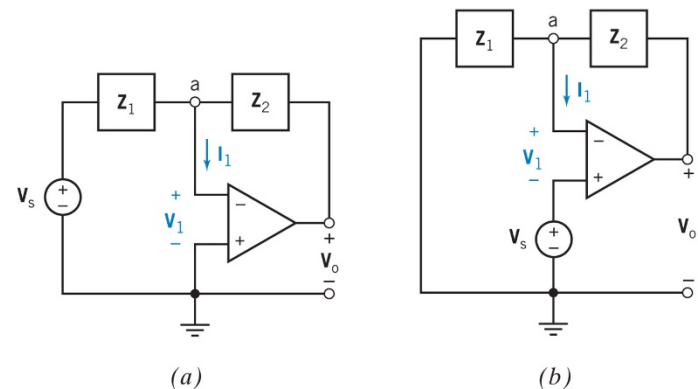


FIGURE 10.10-1



Example 10.10-1 AC Amplifiers

- Find the ratio V_o/V_s for the circuit of Figure 10.10-2 when $R_1 = 1\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $C_1 = 0\text{ F}$, and $C_2 = 0.1\text{ }\mu\text{F}$ for $\omega = 1000\text{ rad/s}$.

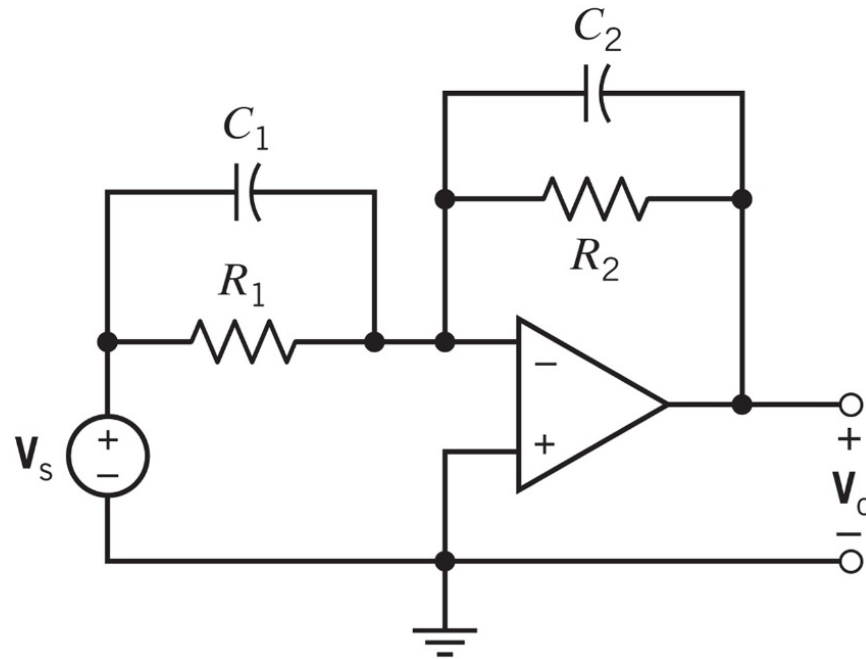


FIGURE 10.10-2



Solution

The circuit of Figure 10.10-2 is an example of the inverting amplifier shown in Figure 10.10-1a. Using equation 10.10-3 and 10.10-6, we obtain

$$\frac{V_o}{V_s} = -\frac{Z_1}{Z_2} = -\frac{\frac{R_2}{1 + j\omega C_2 R_2}}{\frac{R_1}{1 + j\omega C_1 R_1}} = -\frac{R_2(1 + j\omega C_1 R_1)}{R_1(1 + j\omega C_2 R_2)}$$

Using the given values of R_1 , R_2 , C_1 , and C_2 gives

$$\frac{V_o}{V_s} = -\frac{10^4(1 + j10^3(0))10^3}{10^3(1 + j10^3(0.1 \times 10^{-6})10^4)} = -\frac{10}{1 + j} = 7.07 \angle 135^\circ$$



How to Find Complete Response?

-
- To find the complete response of circuits with sinusoidal inputs that are subject to abrupt changes,
 1. Represent the circuit by a differential equations.
 2. Find the general solution. This is the natural response $v_n(t)$.
 3. Find a particular solution. This is the forced response $v_f(t)$.
 4. Represent the response of the circuit as $v(t) = v_n(t) + v_f(t)$.
 5. Use the initial conditions to evaluate the unknown constants.



Example 10.11-1 Complete Response

- Determine $v(t)$, the voltage across the capacitor in Figure 10.11-1, both before and after the switch closes.

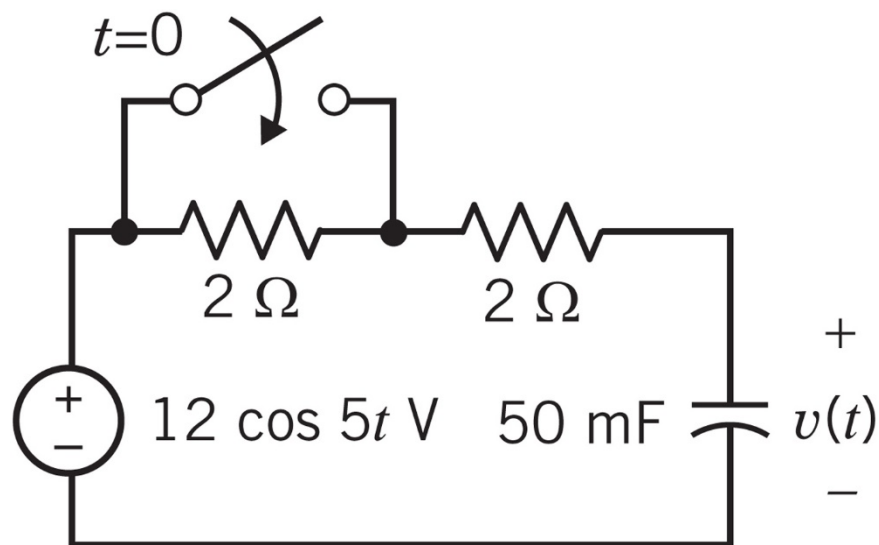



FIGURE 10.11-1



Solution (1/5)

Step 1: For $t < 0$, the switch is open and the circuit is at steady state.

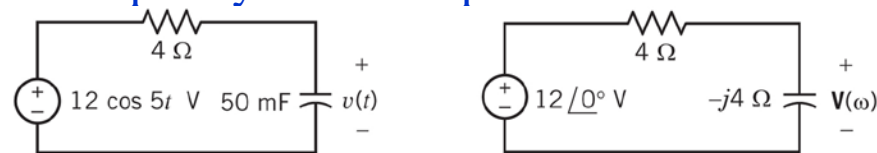Since the open switch acts like an open circuit, we can represent the circuit with Figure 10.11-2a and its frequency domain representation b.



(a) FIGURE 10.11-2 (b)

Using voltage division in the frequency domain gives

$$V(\omega) = \left(\frac{-j4}{4 - j4} \right) (12 \angle 0^\circ) = \frac{48 \angle -90^\circ}{5.66 \angle -45^\circ} = 8.485 \angle -45^\circ V$$

In the time domain,

$$v(t) = 8.485 \cos(5t - 45^\circ) V$$

Therefore immediately before the switch closes, the capacitor voltage is

$$v(0^-) = \lim_{t \rightarrow 0^-} v(t) = 8.485 \cos(-45^\circ) = 6 V$$

$$v(0^-) = v(0^+) = 6 V$$



Solution (2/5)

Step 2: For $t > 0$, the switch is closed.

Eventually, the circuit will reach a new steady state. Since the closed switch acts like an short circuit, we can represent the circuit with Figure 10.11-3a and its frequency domain representation b.

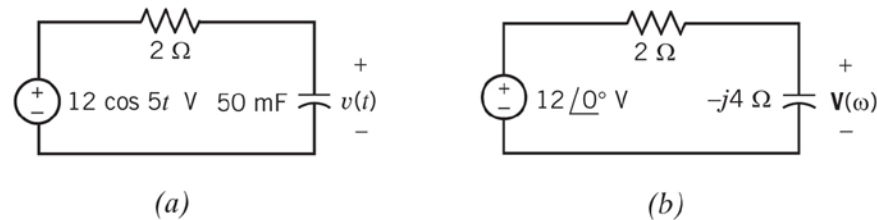


FIGURE 10.11-3

Using voltage division in the frequency domain gives

$$V(\omega) = \left(\frac{-j4}{2 - j4} \right) (12 \angle 0^\circ) = \frac{48 \angle -90^\circ}{4.47 \angle -63.4^\circ} = 10.74 \angle -26.6^\circ V$$

In the time domain,

$$v(t) = 10.74 \cos(5t - 26.6^\circ) V$$



Solution (3/5)

Step 3: For immediately after $t = 0$, the switch is closed but the circuit is not at steady state. We must find the complete response of a first-order circuit.

In Figure 10.11-3a, capacitor is connected to a series voltage source and resistor, that is, a Thévenin equivalent circuit. We can identify R_t and v_{oc} as shown in Figure 10.11-4.

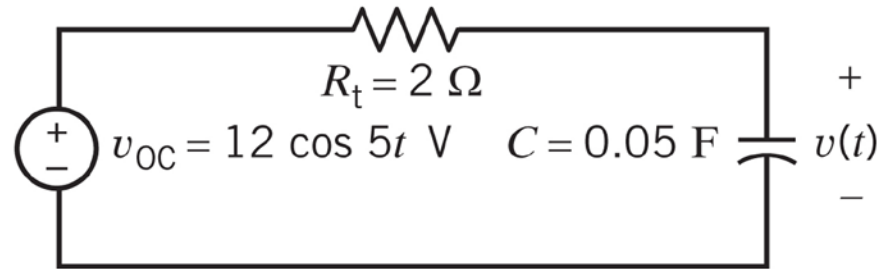


FIGURE 10.11-4

Consequently, the time constant of the circuit is

$$\tau = R_t v_{oc} = 2 \times 0.05 = 0.1 \text{ s}$$

Then the natural response of the circuit is

$$v_n(t) = K e^{-\frac{1}{\tau}t} = K e^{-10t} \text{ V}$$



Solution (4/5)

The steady state response for $t > 0$ can be used as the forced response, so

$$v_f(t) = 10.74 \cos(5t - 26.6^\circ) \text{ V}$$

The complete response is

$$v(t) = v_n(t) + v_f(t) = Ke^{-10t} + 10.74 \cos(5t - 26.6^\circ) \text{ V}$$

We can find the constant, K , using the initial capacitor voltage, $v(0+)$:

$$v(0+) = 6 = Ke^{-0} + 10.74 \cos(-26.6^\circ) = K + 9.6, \text{ thus, } K = -3.6$$

Then,

$$v(t) = -3.6e^{-10t} + 10.74 \cos(5t - 26.6^\circ) \text{ V}$$



Solution (5/5)

Step 4: Summarize the results.

The capacitor voltage, $v(t)$ is,

$$v(t) = \begin{cases} 8.485 \cos(5t - 45^\circ) \text{ V}, & \text{for } t \leq 0 \\ -3.6e^{-10t} + 10.74 \cos(5t - 26.6^\circ) \text{ V}, & \text{for } t \geq 0 \end{cases}$$

And Figure 10.11-5 shows the capacitor voltage as a function of time:

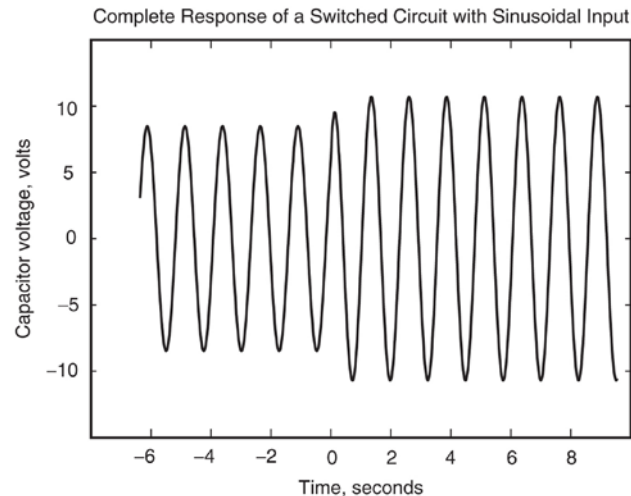


FIGURE 10.11-5



Example 10.11-2 Responses of Various Types of Circuits

- The input to the ac circuit shown in figure below is the voltage source voltage. The output of each circuit is the current $i(t)$. Determine the output of each of the circuit.


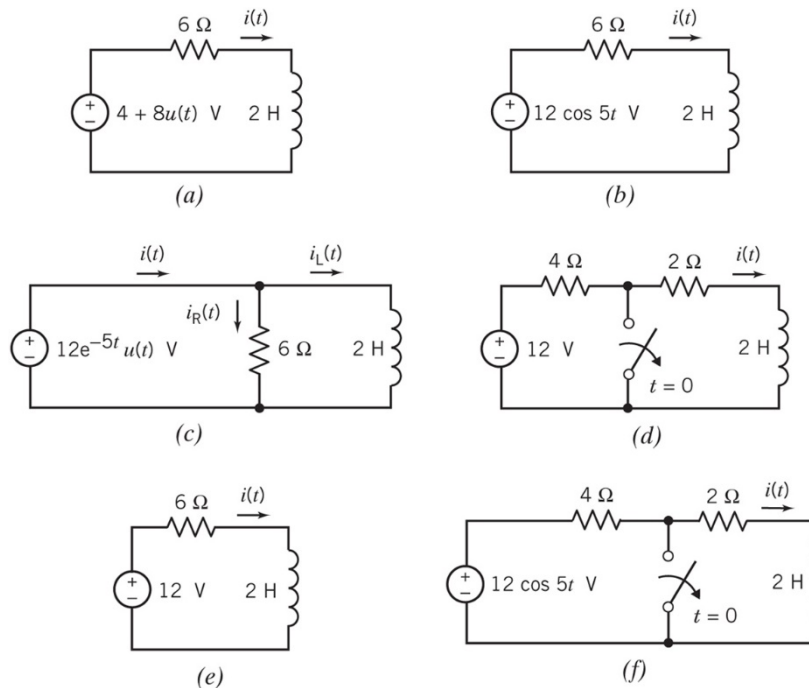


FIGURE 10.11-6

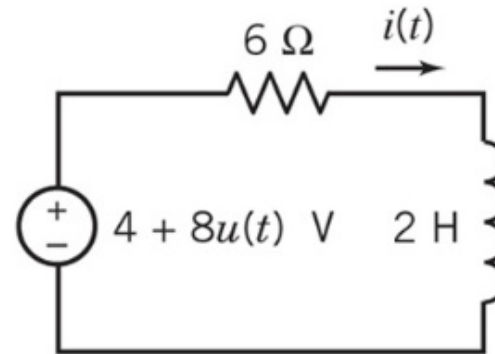


Solution (1/7)

■ (a)



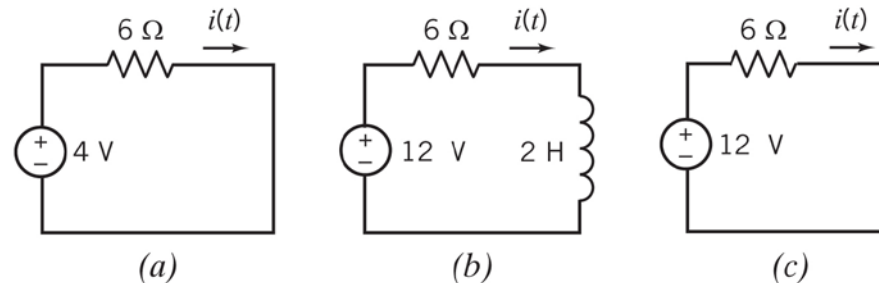- Draw the circuit when $t < 0$, $t \geq 0$ before steady state, $t > 0$ after steady state



- Initial condition at $t=0$

$$i(0+) = i(0-) = \frac{4}{6} [A]$$

- Find the Thevenin equivalent circuit for figure (b)

$$R_t = 6 [\Omega], V_{OC} = 12 [V] \rightarrow i_{SC} = 2 [A], \tau = \frac{1}{3} [s]$$


- Determine current

$$i(t) = i_{SC} + (i(0+) - i_{SC})e^{-t/\tau} = 2 - 1.33e^{-3t} [A]$$




Solution (2/7)

■ (b)

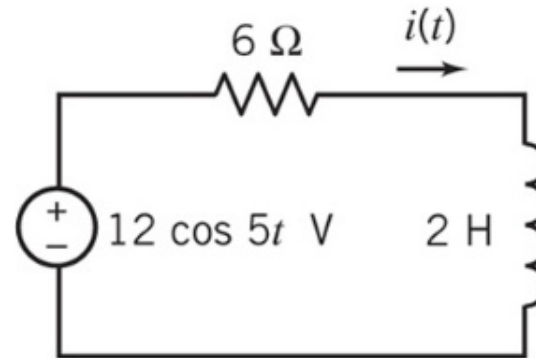

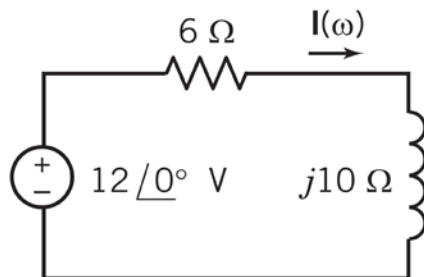- There is no switch and input does not change abruptly, so we expect the circuit is at steady state
- Using Ohm's law,




$$\mathbf{I}(\omega) = \frac{12 \angle 0}{6 + j10} = 1.03 \angle -59 \text{ [A]}$$

$$i(t) = 1.03 \cos(5t - 59) \text{ [A]}$$



Solution (3/7)

■ (c)

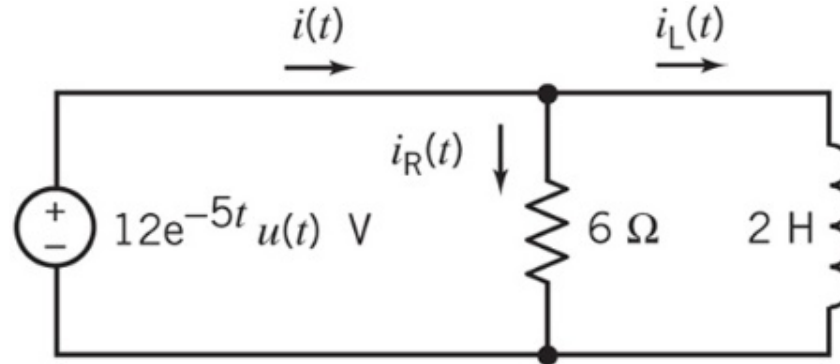

□ Apply KCL

$$i_R(t) = \frac{12e^{-5t}}{6}, \quad i_L(t) = \frac{1}{L} \int_0^t v(t) dt + i_L(0) = 1.2 + i_L(0) - 1.2e^{-5t}$$


$$i(t) = i_R(t) + i_L(t)$$

$$i(t) = 1.2 + 0.8e^{-5t} \text{ [A]}$$




Solution (4/7)

■ (d)

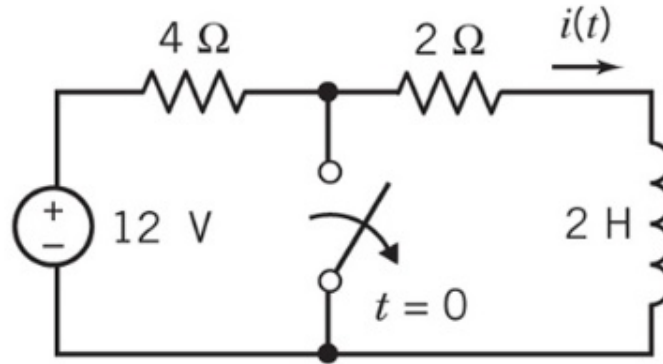

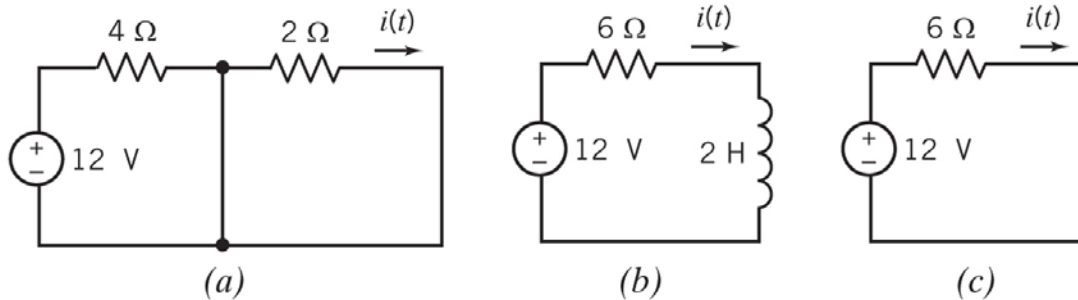□ Draw the circuit when $t < 0$, $t \geq 0$ before steady state, $t > 0$ after steady state



□ Initial condition at $t=0$

$$i(0+) = i(0-) = 0 \text{ [A]}$$

□ Find the Thevenin equivalent circuit for figure (b)

$$R_t = 6 \text{ } [\Omega], V_{OC} = 12 \text{ [V]} \rightarrow i_{SC} = 2 \text{ [A]}, \tau = \frac{1}{3} \text{ [s]}$$


□ Determine current

$$i(t) = i_{SC} + (i(0+) - i_{SC})e^{-t/\tau} = 2 - 2e^{-3t} \text{ [A]}$$



Solution (5/7)

■ (e)

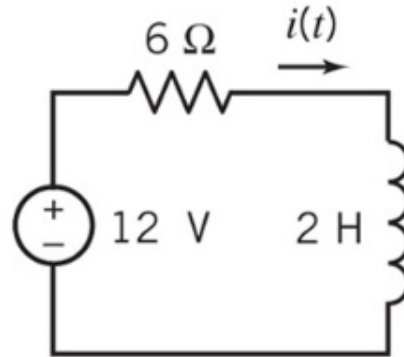

- There is no switch and input does not change abruptly, so we expect the circuit is at steady state.
- Find the Thevenin equivalent circuit for figure (e)

$$R_t = 6 [\Omega], V_{OC} = 12 [V] \rightarrow i_{SC} = 2[A], \tau = \frac{1}{3} [s]$$


- The output current is given as

$$i(t) = 2 [A]$$



Solution (6/7)

■ (f)

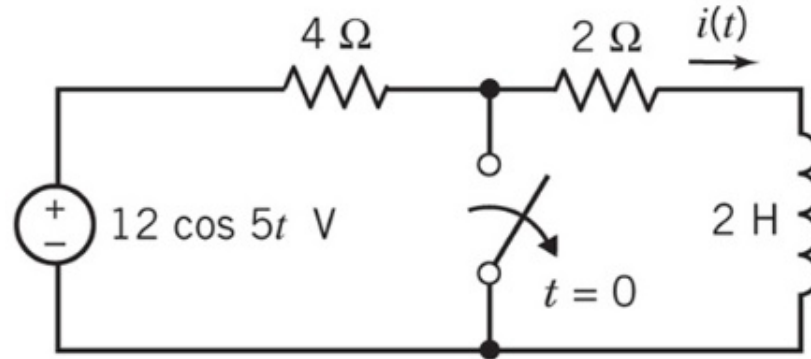

□ Applying KVL for $t > 0$ gives

$$2i(t) + 2 \frac{d}{dt}i(t) = 0$$

□ Initial condition at $t=0$

$$i(0+) = i(0-) = 0 [A]$$

□ The Thévenin equivalent resistance for $t > 0$ and time constant is given,

$$R_t = 6 [\Omega], \tau = \frac{L}{R_t} = \frac{1}{3}$$

□ Then the natural response of the circuit is

$$i_n(t) = K e^{-3t} [A]$$



Solution (7/7)

- From figure 10.11-10, we can find the steady-state response as the forced response from representation in frequency

$$\mathbf{I}(\omega) = \frac{12}{6 + j10} = 1.03 \angle -59^\circ \text{ [A]}$$

$$i_f(t) = 1.03 \cos(5t - 59^\circ)$$

- Then,

$$\begin{aligned} i(t) &= i_n(t) + i_f(t) \\ &= K e^{-3t} + 1.03 \cos(5t - 59^\circ) \text{ [A]} \end{aligned}$$

- At $t=0$,

$$\begin{aligned} i(0) &= K + 1.03 \cos(-59^\circ) \\ &= K + 0.53 = i(0+) = 0 \end{aligned}$$

- Finally,

$$i(t) = -0.53 e^{-3t} + 1.03 \cos(5t - 59^\circ) \text{ [A]}$$

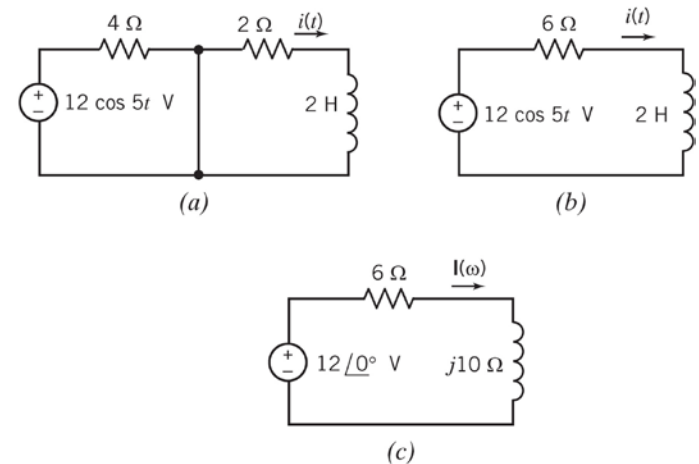


FIGURE 10.11-10

