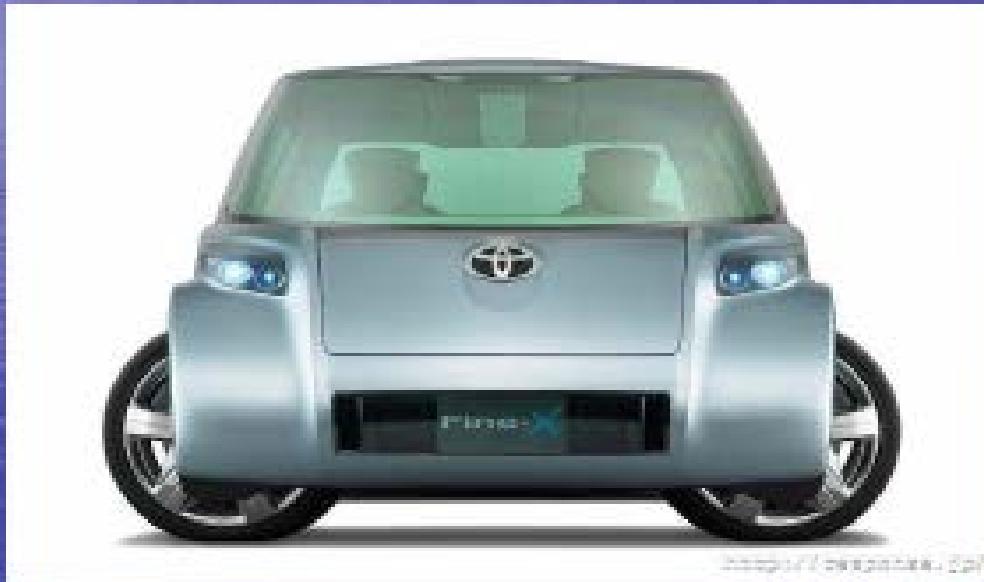


Lecture 6-1

Electrical Systems I

Development of Integrated Vehicle Control System of “Fine-X” Which Realized Freeer Movement.



Mitsuhisa Shida, Akira Matsui, Masayoshi Hoshino
Integrated System Engineering Div.
Toyota Motor Corporation.



TOYOTA Freer Movement Control System




- 4Wheel independent drive
- 4wheel independent steering
- 4wheel independent braking
- By 'wheel-in-motor'




TOYOTA Freer Movement Control System

Integrated vehicle control

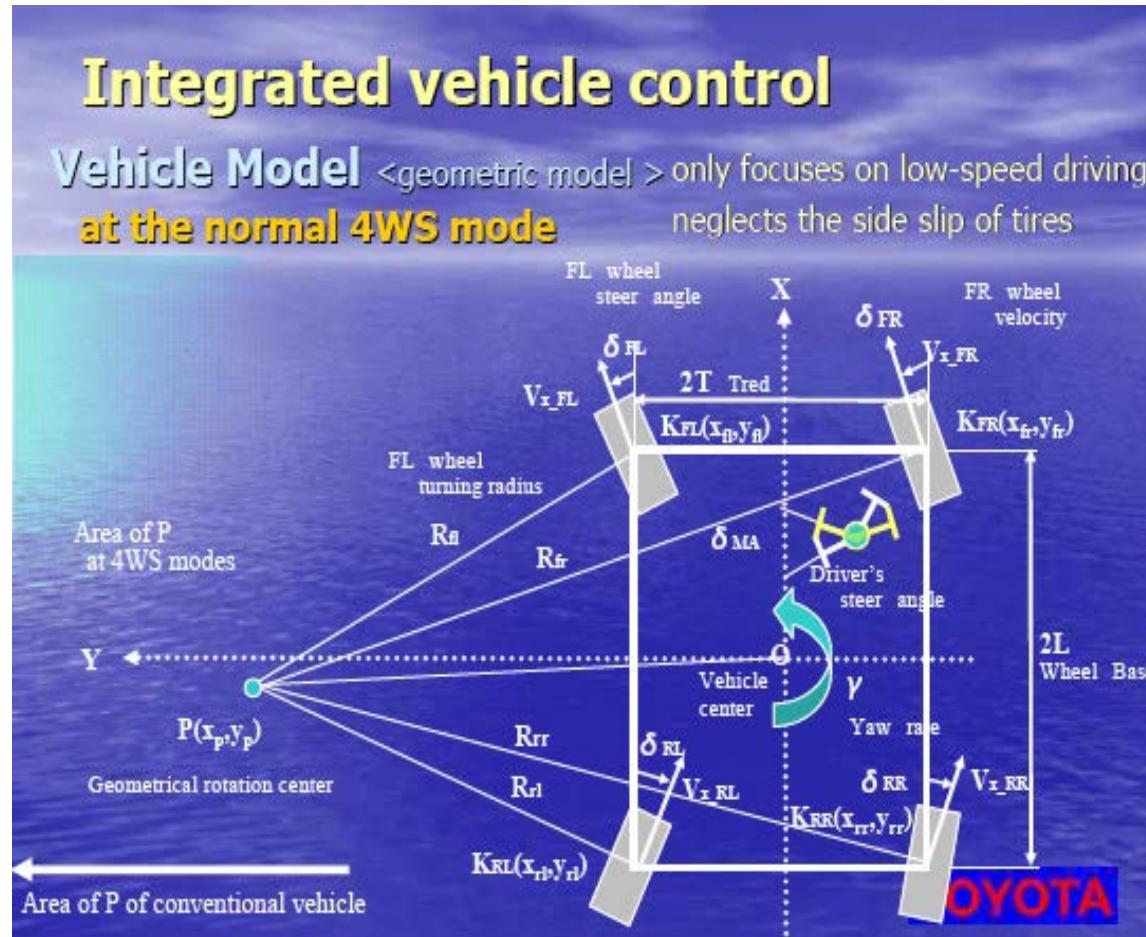
Vehicle Model <geometric model> only focuses on low-speed driving at the normal 4WS mode
neglects the side slip of tires





TOYOTA Freer Movement Control System

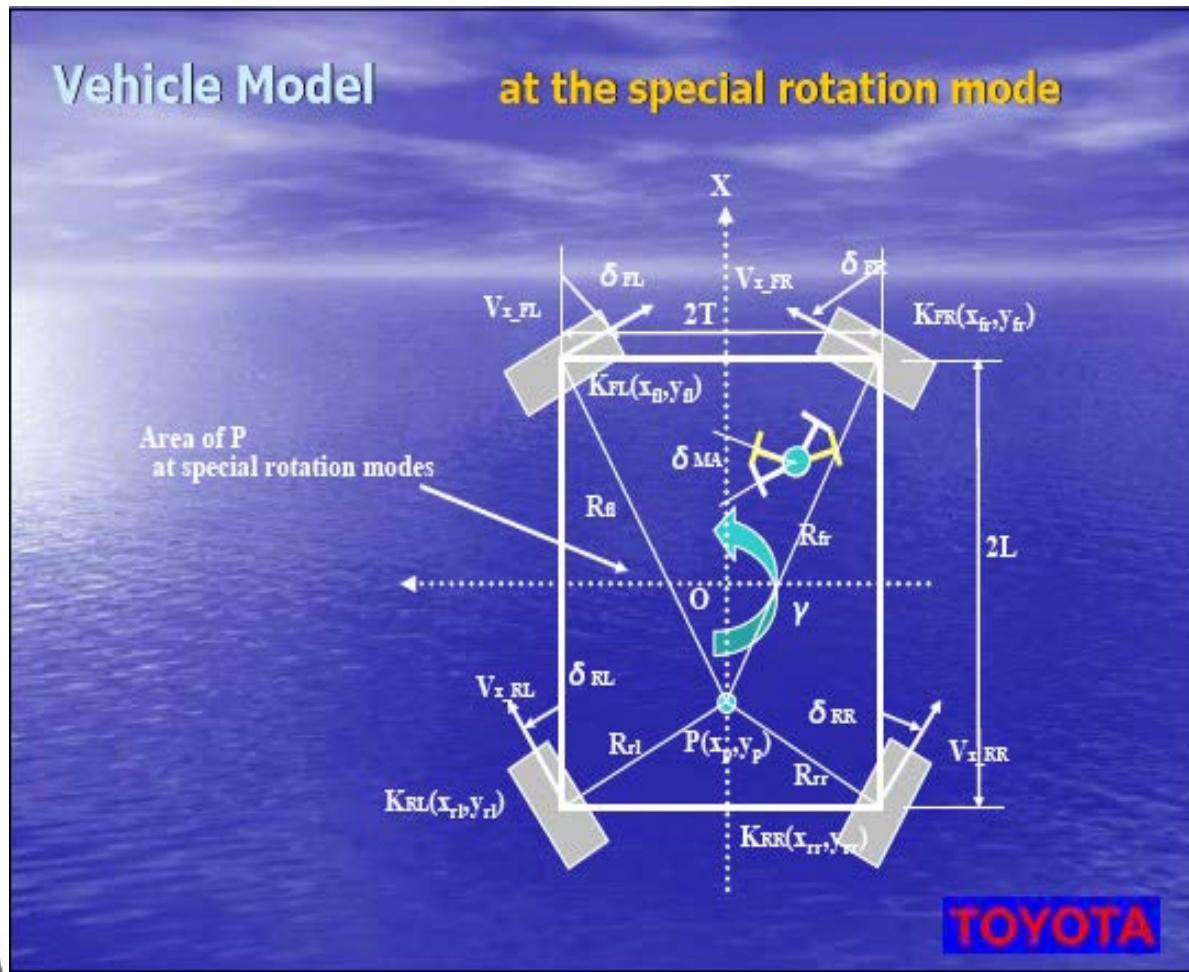


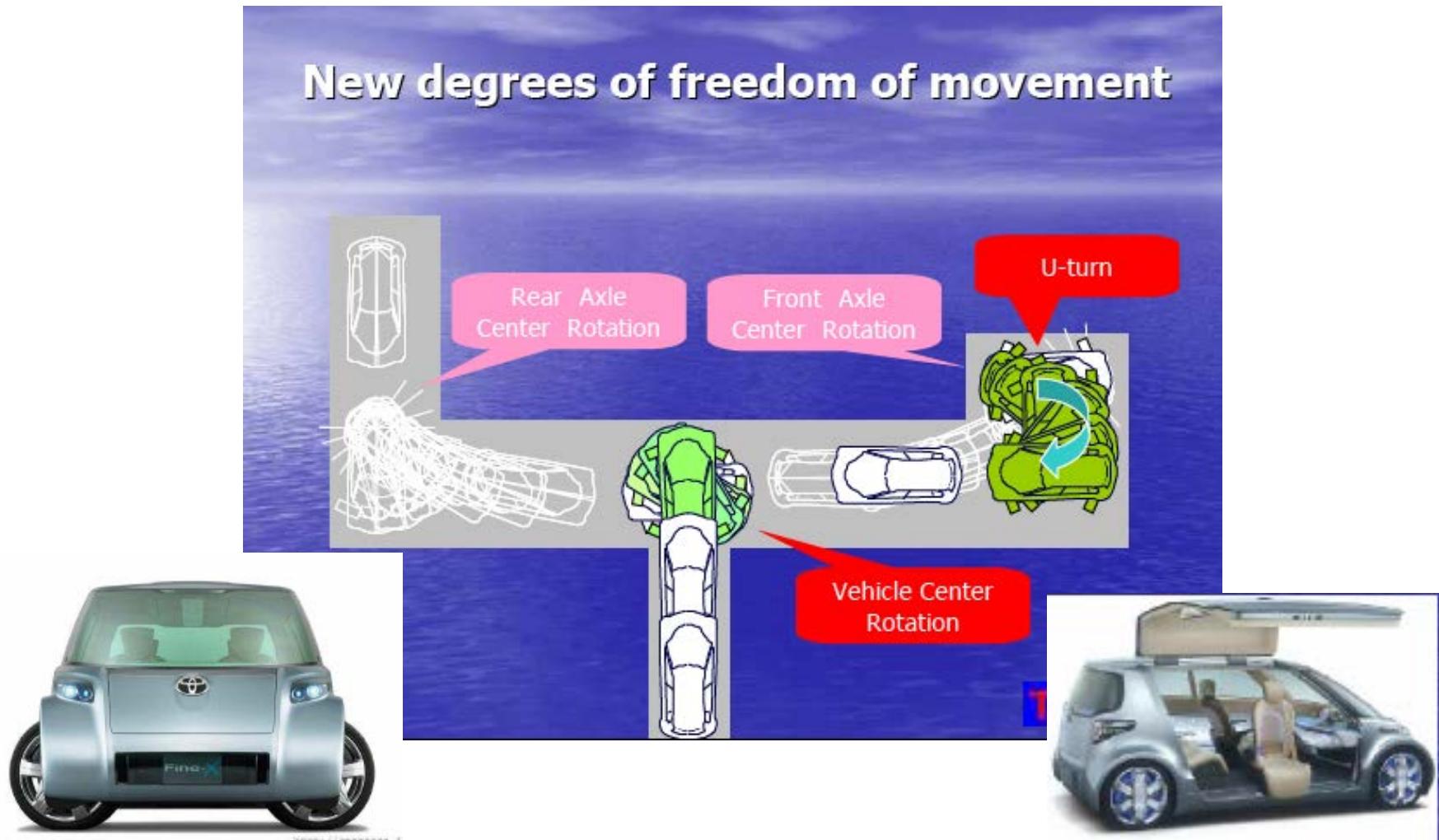
TOYOTA Freer Movement Control System for Auto-Parking



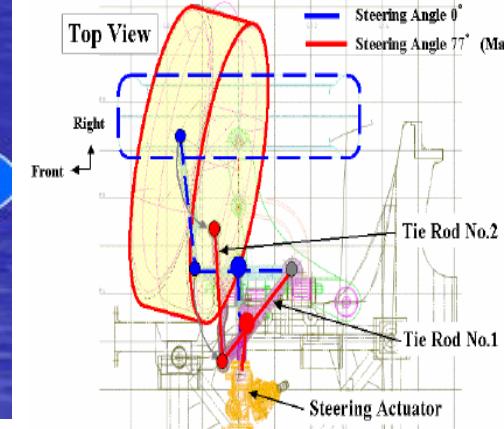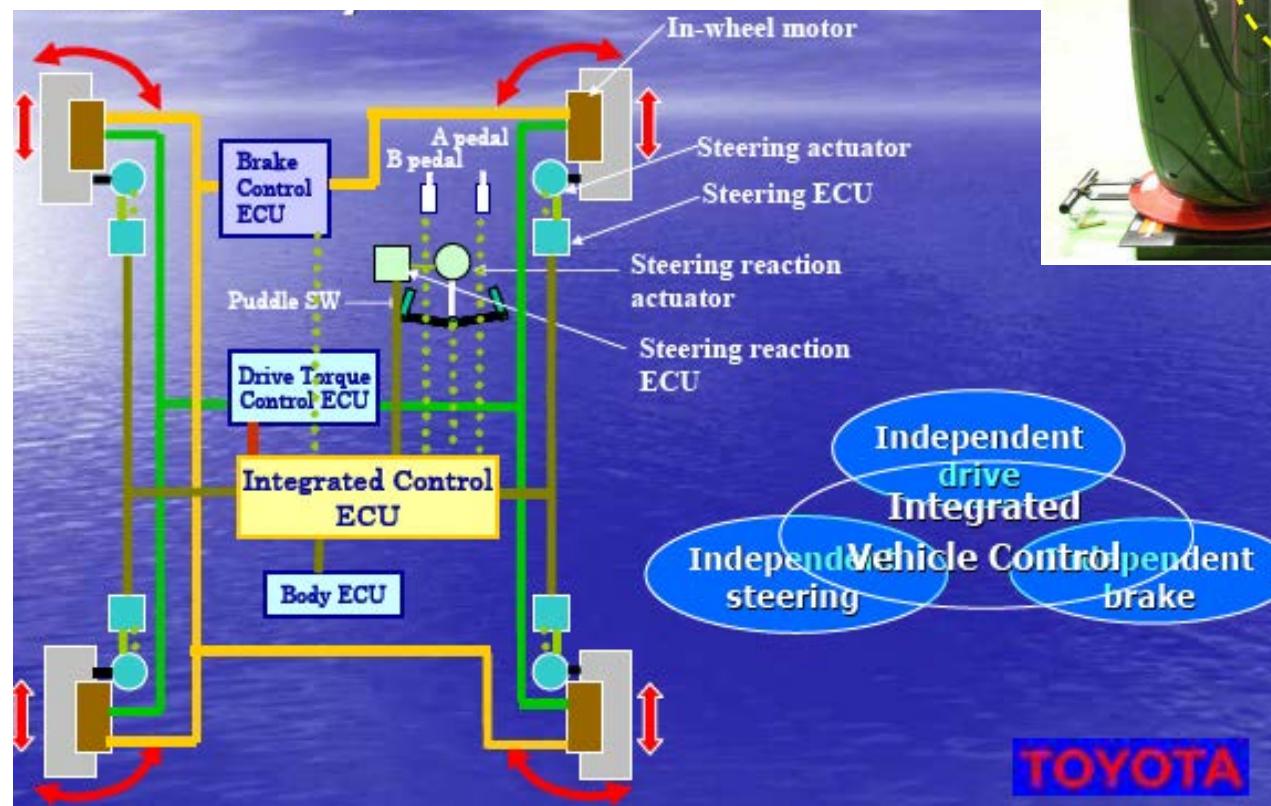TOYOTA Freer Movement Control System for Auto-Parking



6WD6WS Vehicle

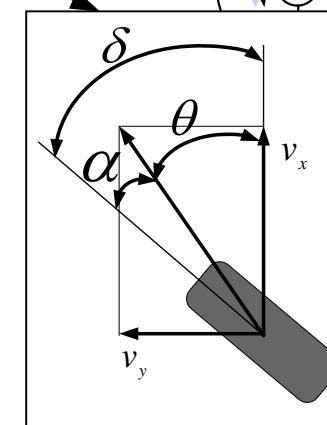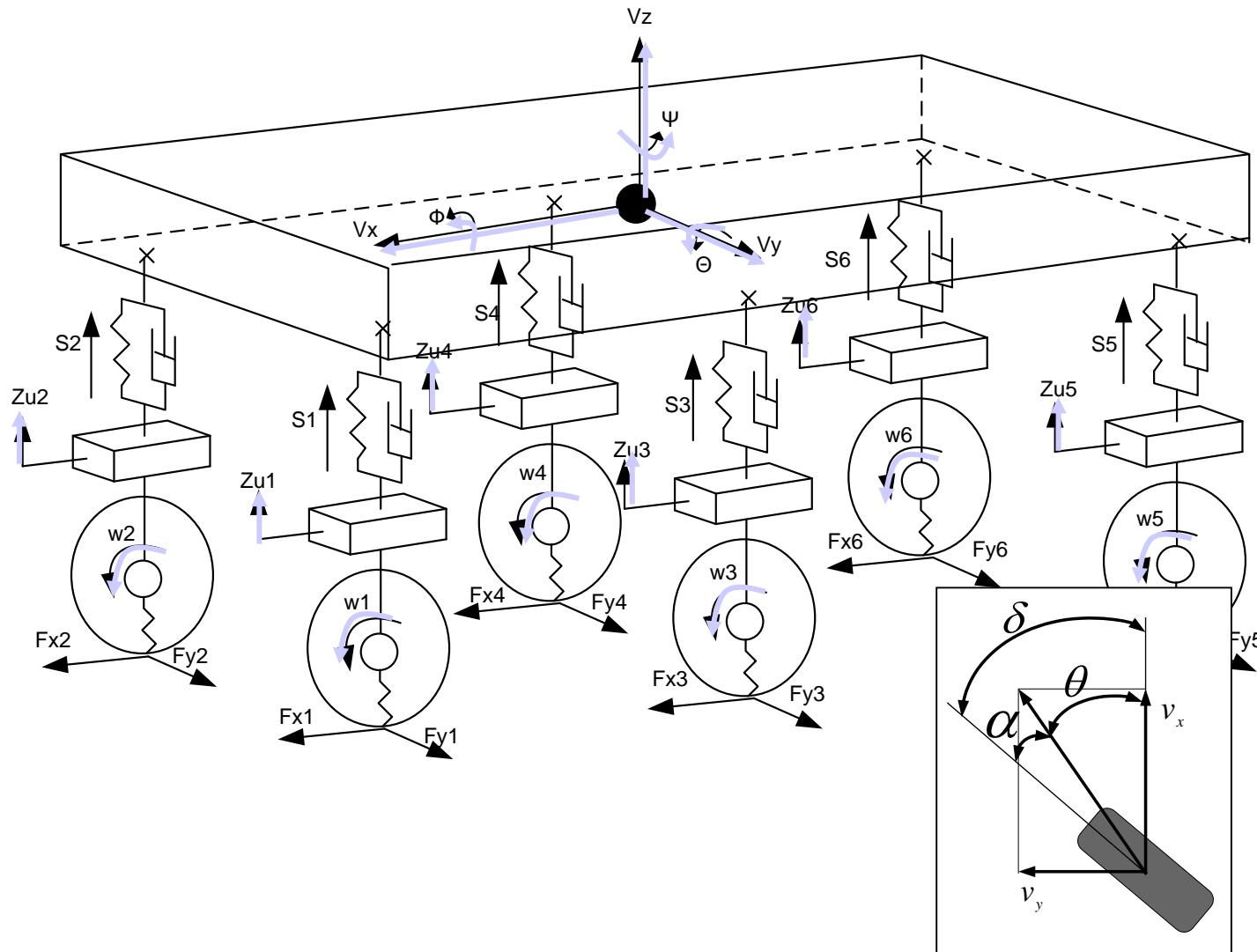


$$u = \begin{bmatrix} \Delta\delta_f \\ \delta_r \end{bmatrix}$$

$$\delta_m = X_1\beta + X_2r$$

BLDC Wheel-in-Motor of 6WD6WS Vehicle



Configuration of 6WD6WS Vehicle

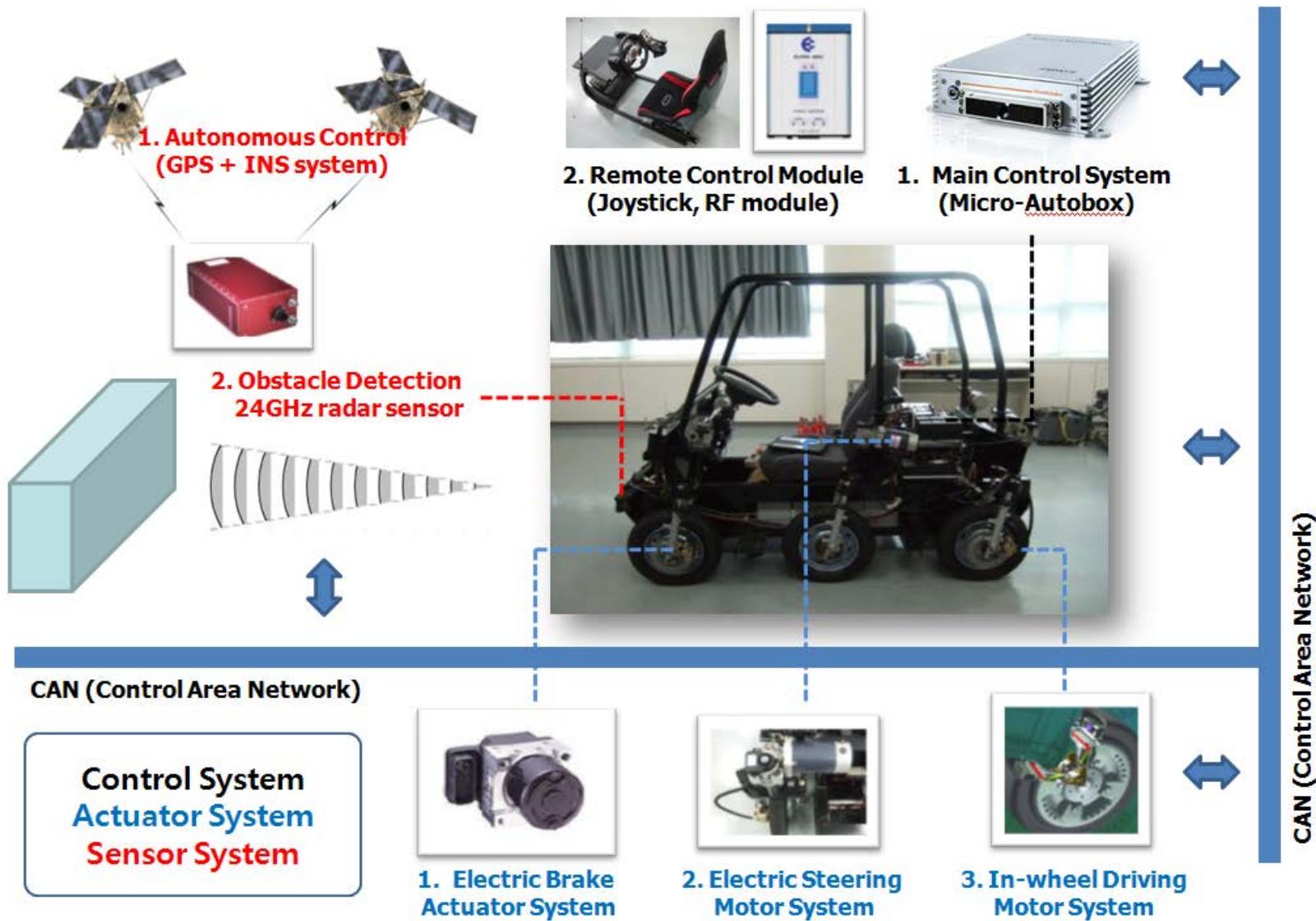

Sectional View of BLDC Motor



Video of 6WD/6WS Vehicle equipped with Wheel-in Motor

Parallel & Circular Turning



평행_제자리선회.wmv

Remote Control



Remote_general_recent.avi

Autonomous Driving




Autonomous_path_tracking.avi

Hybrid and Electrical Vehicles

● Advantages

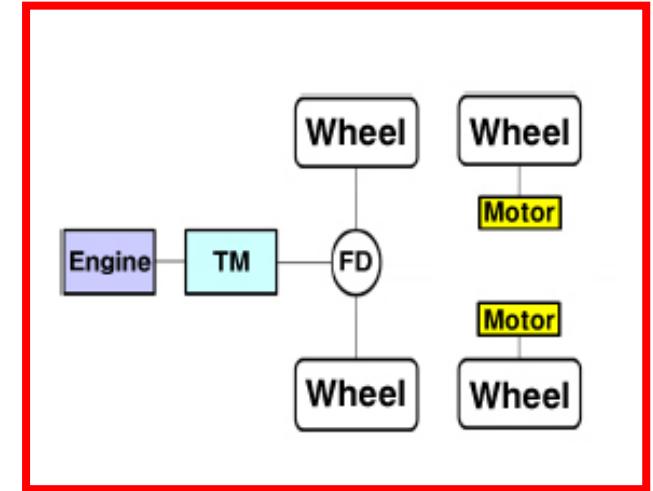- Minimized both costs and technical issues
- Even weight distribution
- Simplest packaging
- Improved vehicle chassis control



● Targets

- To maintain or improve on Euro 4 emissions
- To achieve a 30% overall reduction in CO₂ tail pipe emissions of the baseline vehicle operating with the same fuel, over the NEDC cycle as per EC/98/69 and EC/70/220 for vehicles less than 3500kg.
- Equivalent fuel economy $\geq 60\text{mpg}=25.4\text{kpl}$ (50% improvement in mpg on baseline vehicle)

Hybrid and Electrical Vehicles

Skoda Fabia (Compact SUV)




Hybrid 4WD Vehicle Configuration

Developed by MIRA (Skoda Fabia)

35 KW / 250 Nm Peak Torque

1400 cc 100 HP ICE

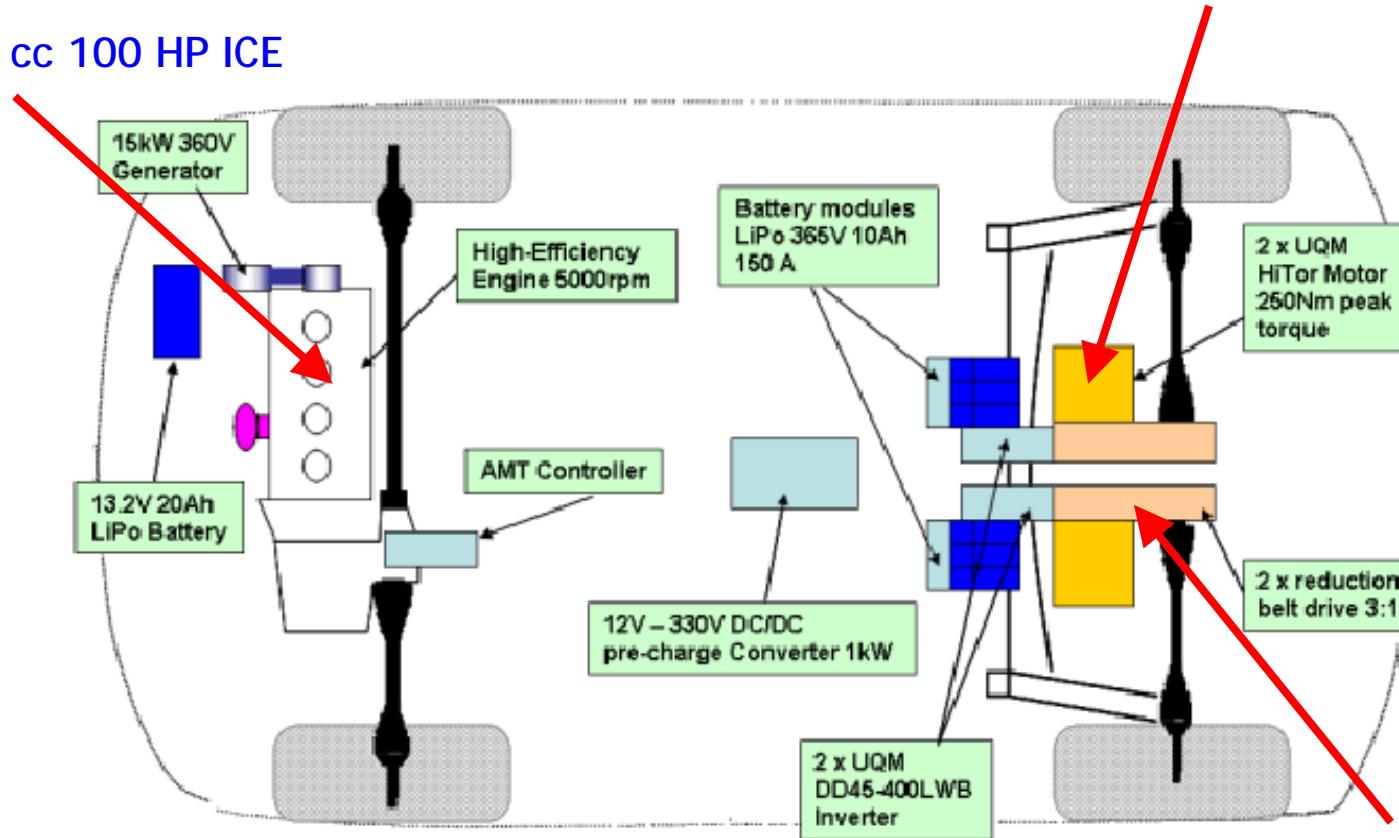


A total weight of around 150kg:
motors = 2x45kg, inverters=2x15kg, structure=30kg

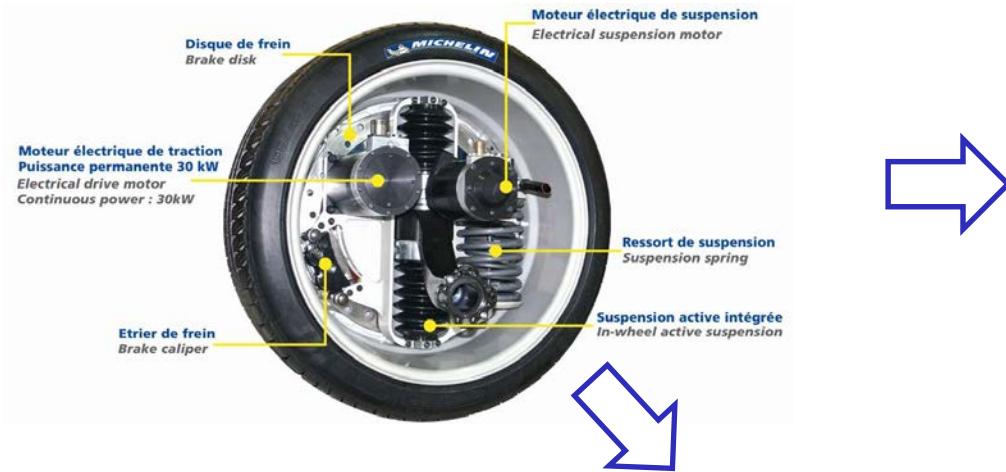3:1 reduction belt drive
→ Peak torque = 750 Nm

4 WD In-wheel Electric Vehicle


Michelin Active Wheel with in-wheel motor, suspension and brake system



Electric vehicle equipped with Front two in-wheel motors




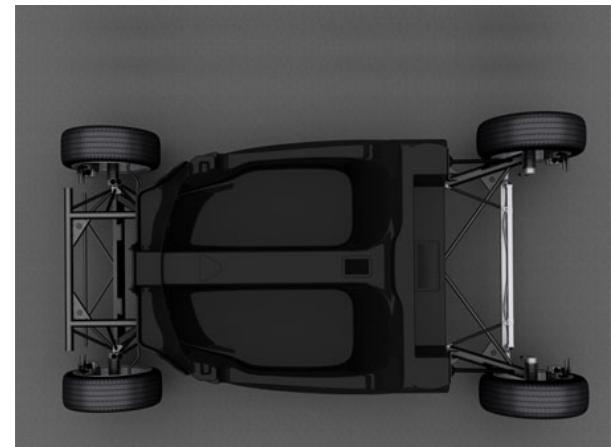Electric vehicle equipped with four in-wheel motors




4 WD Electric Vehicle Combinations


- Front/rear Two In-line Motors

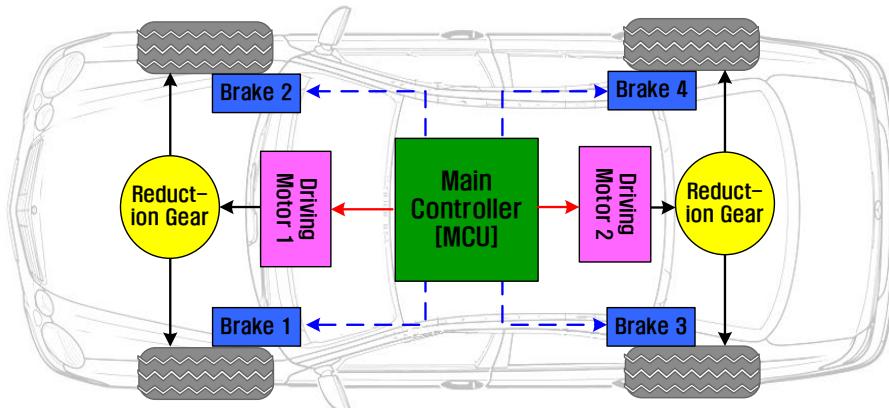

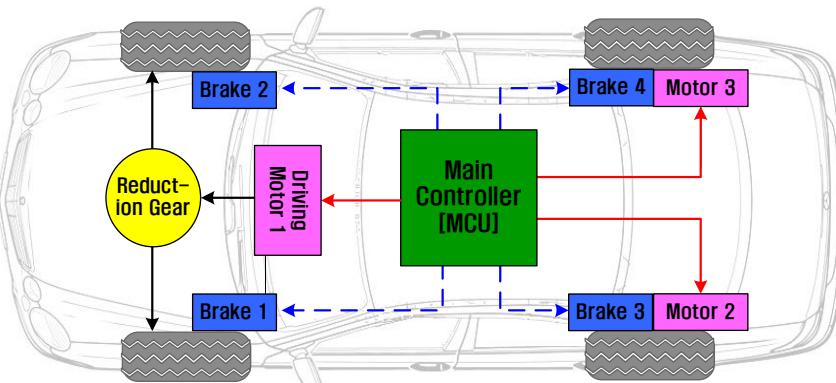
- Front In-line Motor/Rear In-wheel motors



- Four In-wheel Motors

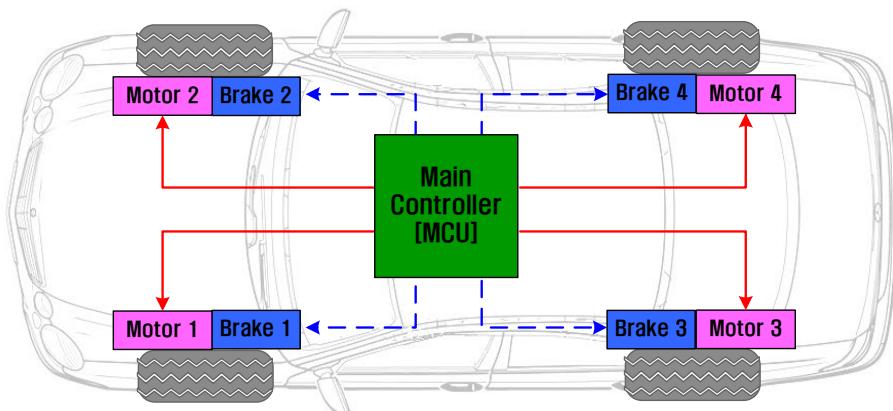

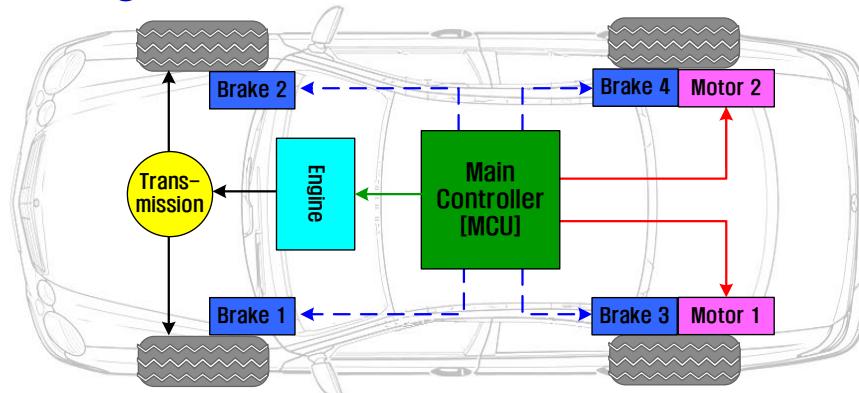- Front Engine Drive/Rear Two In-wheel Motors



6WD Skid Steering Vehicle

Crusher




Crusher highlights.wmv

APD



**Autonomous Platform Demonstrator
(APD) Overview.wmv**

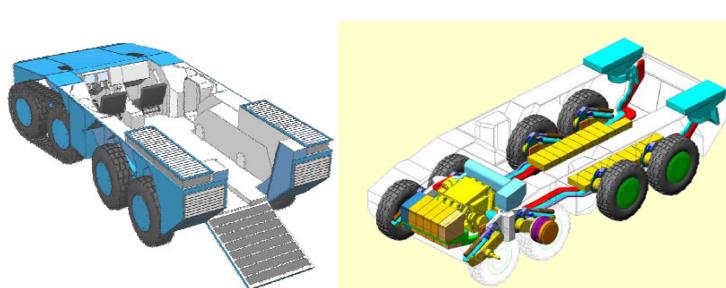8WD/4WS Vehicle Equipped with 8 In-wheel Motor AHED



AHED_8x8_vehicle_vedio.wmv

Basic Elements

- **Active Elements:** OP Amp etc.
(Has transistors/amplifiers that require active source of power to work)
- **Passive Elements:** Inductor, Resistor, Capacitor etc.
(Simply respond to an applied voltage or current.)

- **Current :** the rate of flow of charge
- **Charge :** (electric charge) the integral of current with respect to time [C]

$$i = \frac{dq}{dt} \quad [\text{ampere}] = \frac{[\text{coulomb}]}{[\text{sec}]}$$

- **Voltage :** electromotive force needed to produce a flow of current in a wire [V]
Change in energy as the charge is passed through a component.
[V] = [J/C]

- **Power:** product of voltage and current

$$[W] = [J/\text{Sec}]$$

Basic Elements - Resistance


- Resistance : the change in voltage required to make a unit change in current.

Analogous to → Damping Element

$$R = \frac{\text{Change in voltage}}{\text{Change in current}} = \frac{[V]}{[A]} = [\text{Ohm}(\Omega)]$$

- Resistor
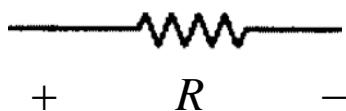
$$V_R = R \cdot i_R \quad R = \frac{V_R}{i_R}$$



Basic Elements - Capacitance

- Capacitance: the change in the quantity of electric charge required to make a unit change in voltage.

Analogous to → Spring Element (Stores Potential Energy)


$$C = \frac{[\text{Coulomb}]}{[V]} = [\text{Farad} (F)]$$

- Capacitor: two conductor separated by non-conducting medium.

$$i = dq/dt, \quad e_c = q/C \rightarrow i = C \frac{de_c}{dt}, \quad de_c = \frac{1}{C} i dt$$

$$\therefore e_c(t) = \frac{1}{C} \int_0^t i dt + e_c(0)$$
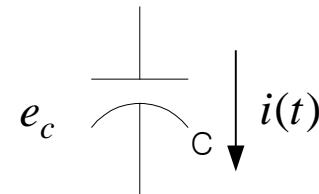
$$I(s) = CsV(s), \quad V(s) = \frac{1}{Cs} I(s)$$



Basic Elements - Inductance


- Inductance: An electromotive force induced in a circuit, if the circuit lies in a time-varying magnetic field.

Analogous to → Inertia Element (Stores Kinetic Energy)

$$L = \frac{[V]}{[A/\text{sec}]} = [\text{Henry (H)}]$$


• Inductor: $e_L = L \frac{di_L}{dt}$ $V(s) = LsI(s)$
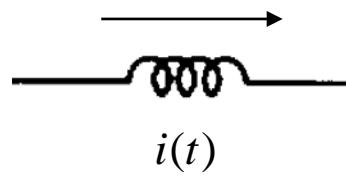
$$\therefore i_L(t) = \frac{1}{L} \int_0^t e_L dt + i_L(0)$$
 $I(s) = \frac{1}{Ls} V(s)$



Series & Parallel Resistance


- Series Resistance

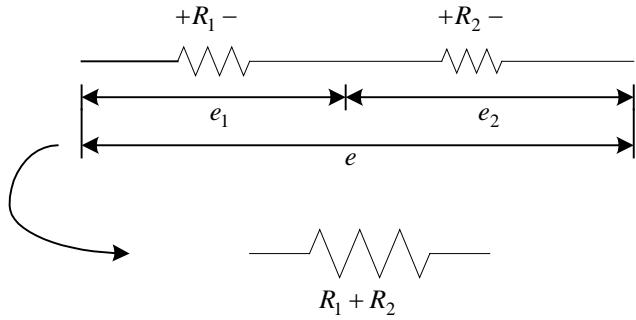

$$e_1 = iR_1, \quad e_2 = iR_2$$

$$e = e_1 + e_2 = i(R_1 + R_2)$$

- Parallel Resistance

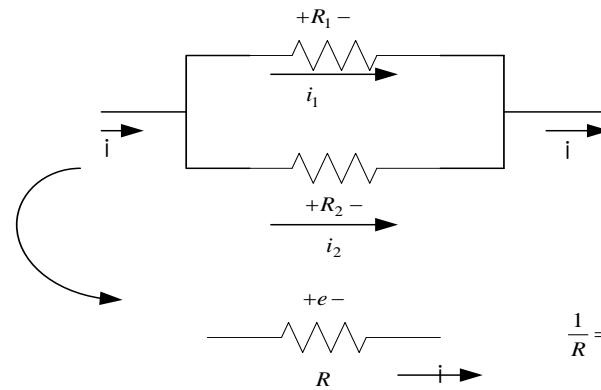

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$-e_1 + e_2 = 0 \Rightarrow e_1 = e_2$$

$$i = i_1 + i_2 = \frac{e_1}{R_1} + \frac{e_2}{R_2} = e\left(\frac{1}{R_1} + \frac{1}{R_2}\right) = \frac{e}{R}$$

Series/Parallel Capacitance?


Kirchhoff's laws

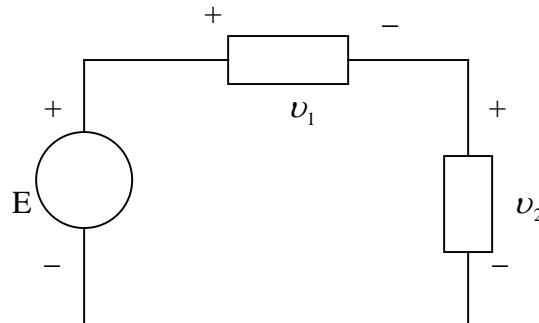1. The algebraic sum of the potential difference around a closed path equals zero.



$$-v_1 - v_2 + E = 0$$

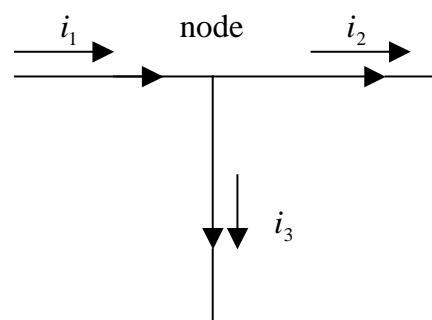2. The algebraic sum of the currents entering (or leaving) a node is equal to zero.




$$i_1 - i_2 - i_3 = 0$$

Current in = Current out

$$\rightarrow i_1 = i_2 + i_3$$

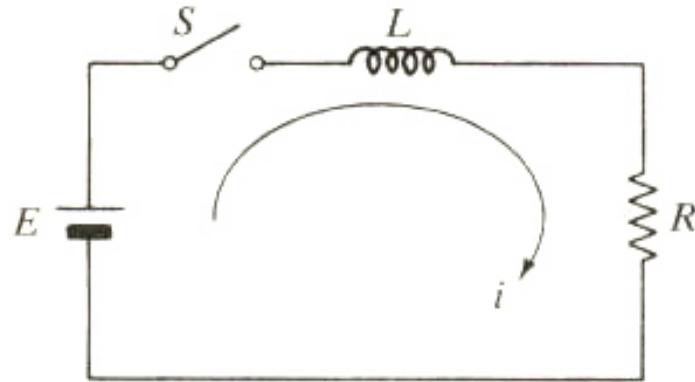Mathematical Modeling of Electrical Systems



The switch S is closed at $t=0$

$$E - L \frac{di}{dt} - Ri = 0 \quad \text{or} \quad L \frac{di}{dt} + Ri = E$$


At the instant that switch S is closed,
the current $i(0) = 0$

Laplace Transformation : $L[sI(s) - i(0)] + RI(s) = \frac{E}{s}$

$$i(0) = 0 \rightarrow (Ls + R)I(s) = \frac{E}{s}$$


$$I(s) = \frac{E}{s(Ls + R)} = \frac{E}{R} \left[\frac{1}{s} - \frac{1}{s + (R/L)} \right]$$
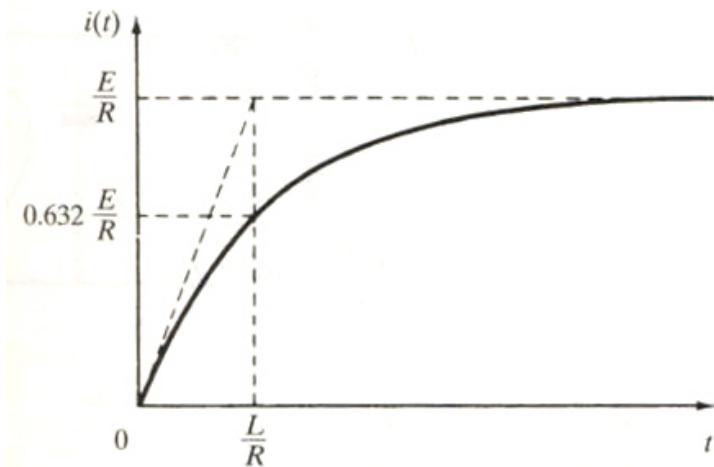
$$\therefore i(t) = \frac{E}{R} \left[1 - e^{-(R/L)t} \right]$$



Examples of Circuit Analysis

ex) R-L-C Circuit

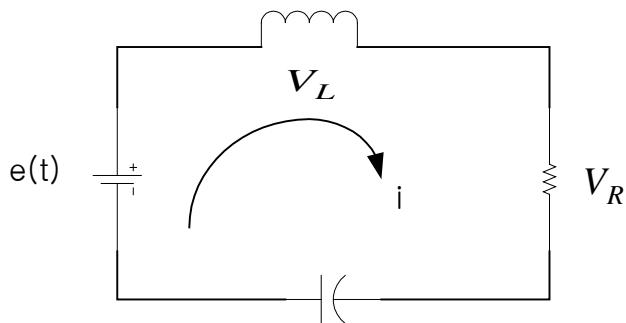

$$V_o(s) = \frac{1}{Cs} I(s)$$

$$V_o(s) = \frac{\frac{1}{Cs}}{(Ls + R + \frac{1}{Cs})} E(s) = \frac{1}{(LCs^2 + RCs + 1)} E(s)$$

$$-V_L - V_R - V_C + e(t) = 0$$

$$V_L = L \frac{di}{dt}, \quad V_R = iR, \quad V_c = \frac{1}{C} \int i dt + V_C(t)$$

$$\frac{dV_c}{dt} = \frac{1}{C} i$$

$$L \frac{di}{dt} + Ri = e(t) - V_C(t)$$


Laplace Transform,

$$(Ls + R + \frac{1}{Cs}) I(s) = E(s)$$

$$\frac{I(s)}{E(s)} = \frac{1}{(Ls + R + \frac{1}{Cs})}$$

Step Response?

Complex Impedance

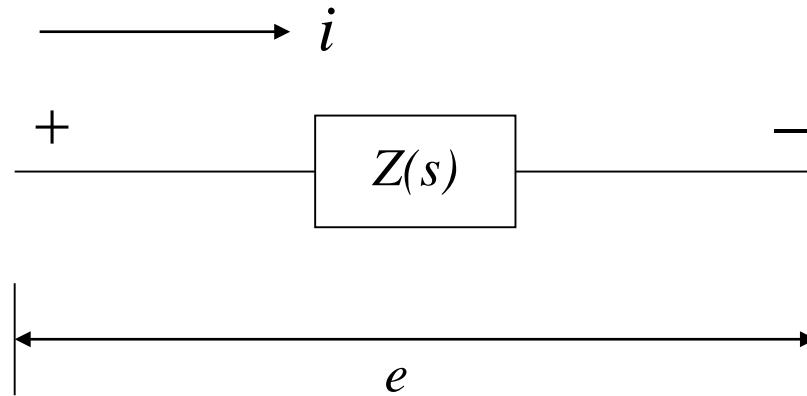


$$I(s) = \frac{E(s)}{Z(s)}$$

$$E(s) = Z(s)I(s)$$

$Z(s)$: complex impedance

Complex Impedance

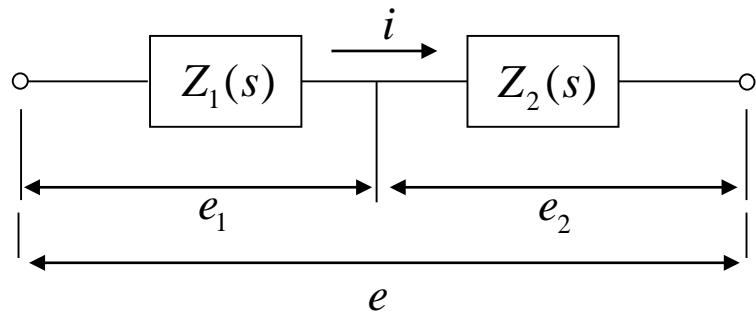The complex impedance $Z(s)$ of a two-terminal circuit is : the ratio of $E(s)$ to $I(s)$



$$Z(s) = \frac{E(s)}{I(s)}, \quad E(s) = Z(s)I(s)$$

$$E_1(s) = Z_1(s)I(s), \quad E_2(s) = Z_2(s)I(s)$$


$$E(s) = E_1(s) + E_2(s)$$

Direct derivation of transfer function,
without writing differential equations first.

$$\begin{aligned} &= Z_1(s)I(s) + Z_2(s)I(s) \\ &= (Z_1(s) + Z_2(s))I(s) \end{aligned}$$

Complex Impedance


Resistance :

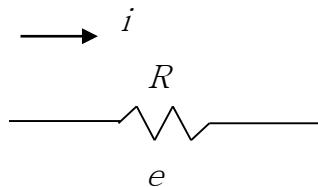

$$e = Ri, \quad E(s) = RI(s)$$

$$Z(s) = R$$

Capacitance :

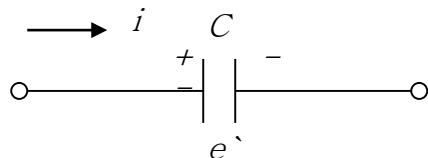


$$\frac{de}{dt} = \frac{1}{C}i$$

$$sE(s) = \frac{1}{C}I(s) \rightarrow E(s) = \frac{1}{Cs}I(s)$$


$$\therefore Z(s) = \frac{1}{Cs}$$




Inductance :

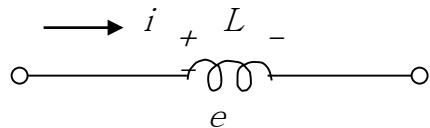

$$e = L \frac{di}{dt}, \quad E(s) = Ls I(s)$$

$$\therefore Z(s) = Ls$$

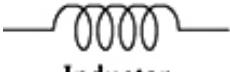
Component	Voltage-current	Current-voltage	Voltage-charge	Impedance $Z(s) = V(s)/I(s)$	Admittance $Y(s) = I(s)/V(s)$
 Capacitor	$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$	$i(t) = C \frac{dv(t)}{dt}$	$v(t) = \frac{1}{C} q(t)$	$\frac{1}{Cs}$	Cs
 Resistor	$v(t) = Ri(t)$	$i(t) = \frac{1}{R} v(t)$	$v(t) = R \frac{dq(t)}{dt}$	R	$\frac{1}{R} = G$
 Inductor	$v(t) = L \frac{di(t)}{dt}$	$i(t) = \frac{1}{L} \int_0^t v(\tau) d\tau$	$v(t) = L \frac{d^2q(t)}{dt^2}$	Ls	$\frac{1}{Ls}$

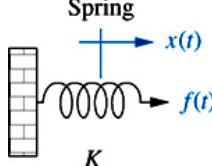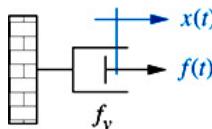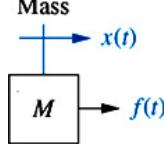Component	Force-velocity	Force-displacement	Impedance $Z_M(s) = F(s)/X(s)$
 Spring K	$f(t) = K \int_0^t v(\tau) d\tau$	$f(t) = Kx(t)$	K
 Viscous damper f_v	$f(t) = f_v v(t)$	$f(t) = f_v \frac{dx(t)}{dt}$	$f_v s$
 Mass M	$f(t) = M \frac{dv(t)}{dt}$	$f(t) = M \frac{d^2x(t)}{dt^2}$	Ms^2

Examples of Complex Impedance

Series Impedances


ex1)

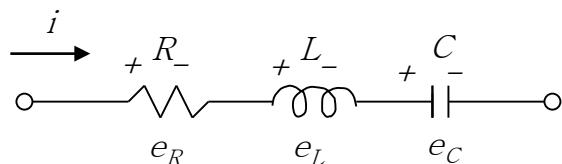

$$e_R = iR, \quad e_L = L \frac{di}{dt}, \quad \frac{de_C}{dt} = \frac{1}{C} i$$

$$e = e_R + e_L + e_C$$
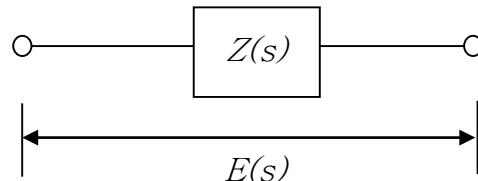
$$\begin{aligned} E(s) &= E_R(s) + E_L(s) + E_C(s) \\ &= RI(s) + LsI(s) + \frac{1}{Cs} I(s) \\ &= \left(R + Ls + \frac{1}{Cs} \right) I(s) \end{aligned}$$




$$\therefore Z(s) = R + Ls + \frac{1}{Cs} = Z_R(s) + Z_L(s) + Z_C(s)$$

Examples of Complex Impedance

Parallel Impedances

ex2)

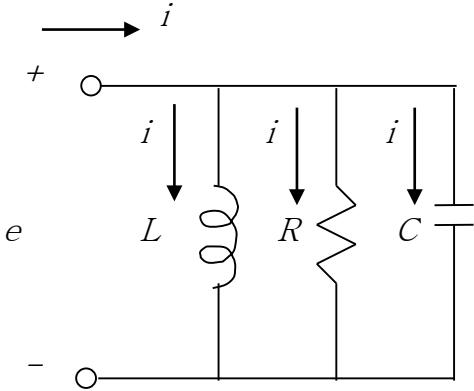


$$i = i_L + i_R + i_C \quad E(s) = Z(s)I(s)$$

$$I(s) = I_L(s) + I_R(s) + I_C(s)$$

$$= \frac{E(s)}{Z_L(s)} + \frac{E(s)}{Z_R(s)} + \frac{E(s)}{Z_C(s)}$$

$$= \left(\frac{1}{Z_L(s)} + \frac{1}{Z_R(s)} + \frac{1}{Z_C(s)} \right) E(s)$$


$$= \frac{1}{Z(s)} E(s)$$

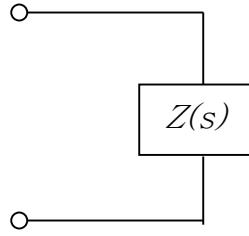

$$\therefore Z(s) = \frac{1}{\frac{1}{Z_R(s)} + \frac{1}{Z_L(s)} + \frac{1}{Z_C(s)}} = \frac{1}{\frac{1}{Ls} + \frac{1}{R} + Cs}$$

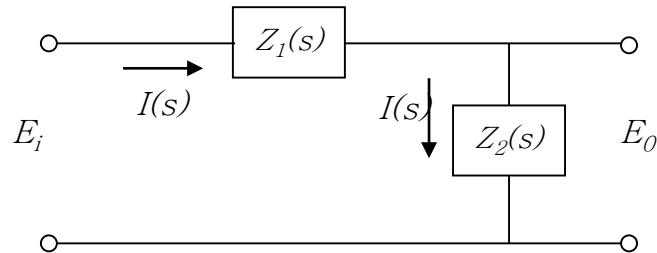Examples of Complex Impedance


Deriving transfer functions of Electrical circuits by the use of complex impedances.



$$E_i(s) = Z_1(s)I(s) + Z_2(s)I(s), \quad E_o(s) = Z_2(s)I(s)$$

$$\frac{E_o(s)}{E_i(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$

ex)

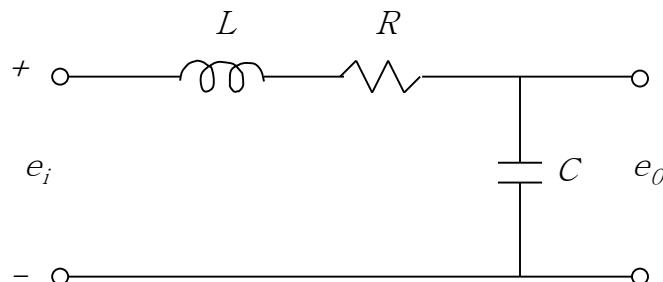


$$\frac{E_o(s)}{E_i(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$

$$Z_1(s) = Ls + R, \quad Z_2(s) = \frac{1}{Cs}$$


$$\frac{E_o(s)}{E_i(s)} = \frac{\frac{1}{Cs}}{Ls + R + \frac{1}{Cs}} = \frac{1}{Ls^2 + Rs + \frac{1}{C}}$$

Transfer Functions of Cascaded Elements


Consider two RC circuits

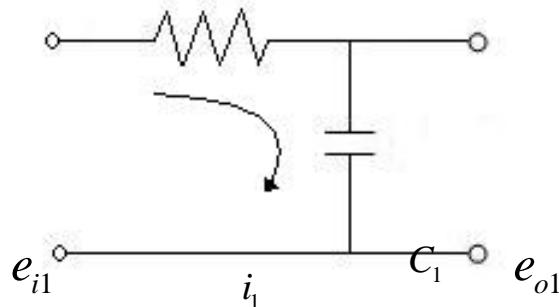
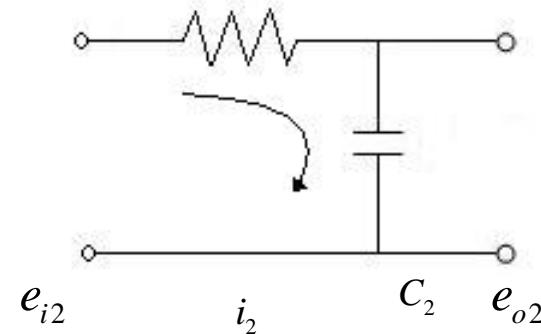
$$\frac{E_{o1}(s)}{E_{i1}(s)} = \frac{1}{R_1 C_1 s + 1} = G_1(s)$$



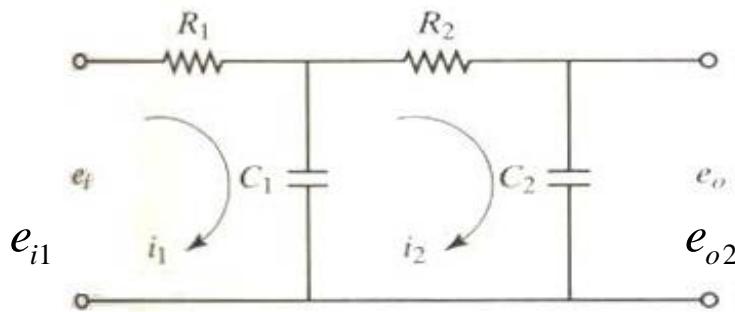
$$\frac{E_{o2}(s)}{E_{i2}(s)} = \frac{1}{R_2 C_2 s + 1} = G_2(s)$$



$$\frac{E_{o2}(s)}{E_{i1}(s)} = ?$$

Transfer Functions of Cascaded Elements

Loading Effect

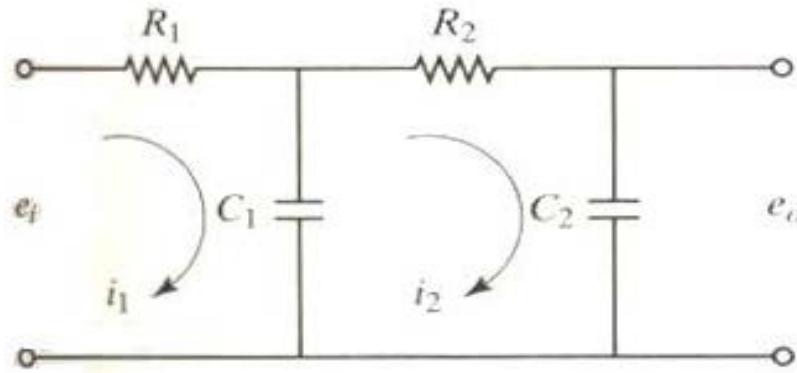


$$E_i(s) = \frac{1}{C_1 s} [I_1(s) - I_2(s)] + R_1 I_1(s), \quad \frac{1}{C_1 s} [I_2(s) - I_1(s)] + R_2 I_2(s) + \frac{1}{C_2 s} I_2(s) = 0, \quad E_o(s) = \frac{1}{C_2 s} I_2(s)$$

$$T.F : \frac{E_o(s)}{E_i(s)} = \frac{1}{(R_1 C_1 s + 1)(R_2 C_2 s + 1) + R_1 C_2 s} \neq \frac{1}{(R_1 C_1 s + 1)(R_2 C_2 s + 1)}$$

$$\therefore \frac{E_o(s)}{E_i(s)} \neq \frac{E_{o1}(s)}{E_{i1}(s)} \cdot \frac{E_{o2}(s)}{E_{i2}(s)} \quad \longrightarrow \text{Loading effect}$$

Transfer Functions of Cascade Elements

Input Impedance, Output Impedance

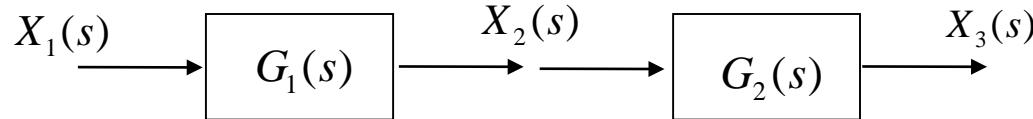


$$G(s) = \frac{X_3(s)}{X_1(s)} = \frac{X_2(s)}{X_1(s)} \cdot \frac{X_3(s)}{X_2(s)} = G_1(s)G_2(s)$$

If the "input Impedance" of the second element is infinite, the output of the first element is not affected by connecting it to the second element.

Then, $G(s) = G_1(s)G_2(s)$

Transfer Functions of Cascade Elements

Isolating Amplifier

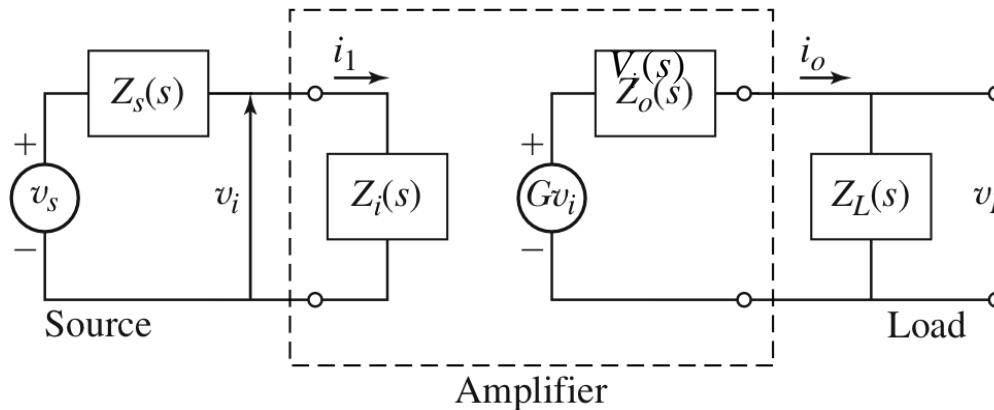

This amplifier circuit has to

1. Not affect the behavior of the source circuit.
2. Not be affected by the loading circuit.


$$V_i(s) = \frac{Z_i(s)}{Z_i(s) + Z_s(s)} V_s(s) \approx V_s(s)$$

This isolating amplifier circuit has to have

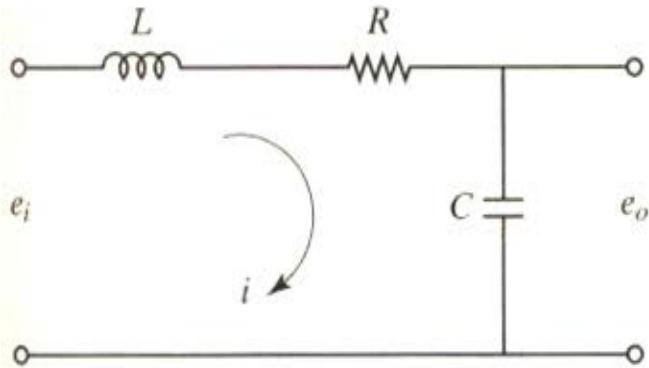1. a very high input impedance,
2. very low output impedance

$$V_L(s) = Z_L(s) I_o(s) = \frac{Z_L(s)}{Z_o(s) + Z_L(s)} G V_o(s) \approx G V_o(s)$$

State-Space Mathematical Modeling of Electrical Systems



By Kirchhoff's voltage law

$$L \frac{di}{dt} + Ri + v_c = e_i, \quad \frac{dv_c}{dt} = \frac{1}{C} i, \quad e_o = v_c$$

Assume, initial condition is 0,

$$LI(s) + RI(s) + V_c(s) = E_i(s), \quad V_c(s) = \frac{1}{Cs} I(s)$$

$$T.F : \frac{E_o(s)}{E_i(s)} = \frac{1}{LCs^2 + RCs + 1}$$

State-Space Mathematical Modeling of Electrical Systems

Differential equation : $\ddot{e}_o + \frac{R}{L}\dot{e}_o + \frac{1}{LC}e_o = \frac{1}{LC}e_i$

State variable : $x_1 = e_o, \quad x_2 = \dot{e}_o$

Input and output : $u = e_i, \quad y = e_o = x_1$

State-space equation :

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{LC} \end{bmatrix} u, \quad y = [1 \ 0] \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

End of lecture 6–1