

2007 Fall: Electronic Circuits 2

CHAPTER 8

Feedback

Deog-Kyoon Jeong

dkjeong@snu.ac.kr

School of Electrical Engineering
Seoul National University

Introduction

- ◆ In this chapter, we will be covering...
- Negative Feedback
- The General Feedback Structure
- The Four Basic Feedback Topologies
- Feedback in relation with Stability
- Feedback in relation with Frequency Response

Introduction


- ◆ Two types of Feedback
 - Positive (Regenerative) Feedback
 - Negative (Degenerative) Feedback

- ◆ This chapter will focus on Negative Feedback

Introduction – Negative FB

- ◆ Negative Feedback – Trades off **gain** for other desired properties, such as…
 - ◆ Desensitized gain
 - ◆ Reduced non-linear distortion
 - ◆ Reduced effect of noise
 - ◆ Controlled input and output impedance
 - ◆ Extended bandwidth
- These trade-offs take place under the influence of a numeric factor called ‘amount of feedback’.


1. The General Feedback Structure

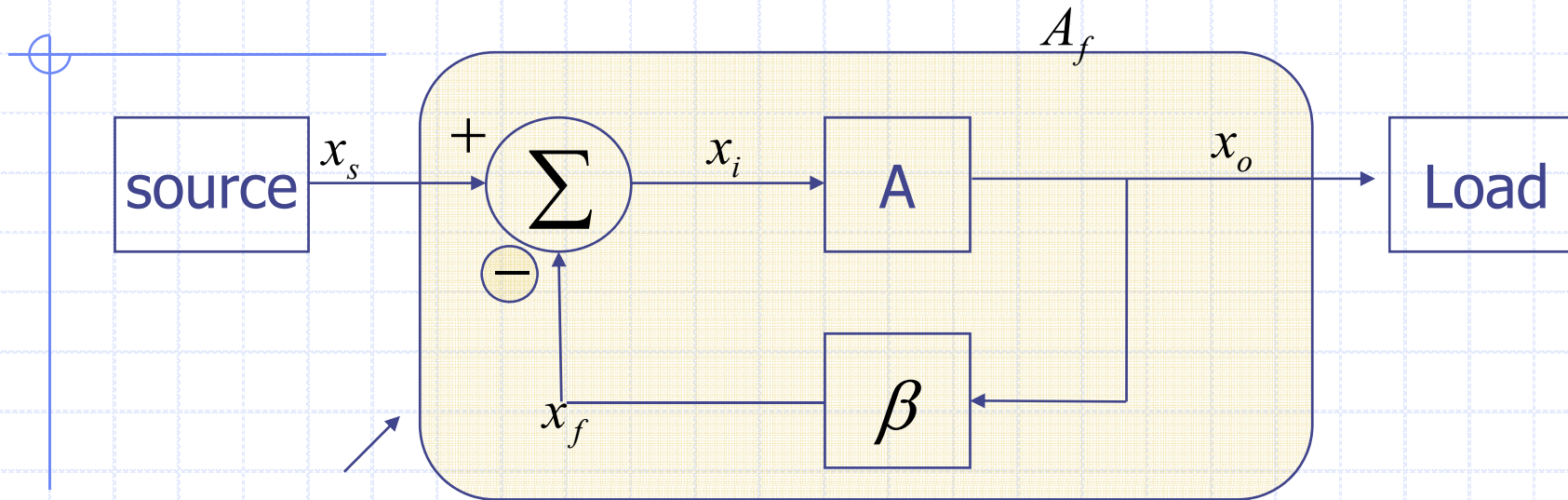

This is a signal-flow diagram of the general negative feedback structure.

$$\left[\begin{array}{l} x_o = A \cdot x_i \\ x_f = \beta \cdot x_o \\ x_i = x_s - x_f \end{array} \right] \longrightarrow \left[\begin{array}{l} x_o = A \cdot x_i \\ = A \cdot (x_s - x_f) \\ = A \cdot (x_s - \beta \cdot x_o) \\ A_f \equiv \frac{x_o}{x_s} = \frac{A}{1 + A \cdot \beta} \end{array} \right]$$

1. The General Feedback Structure

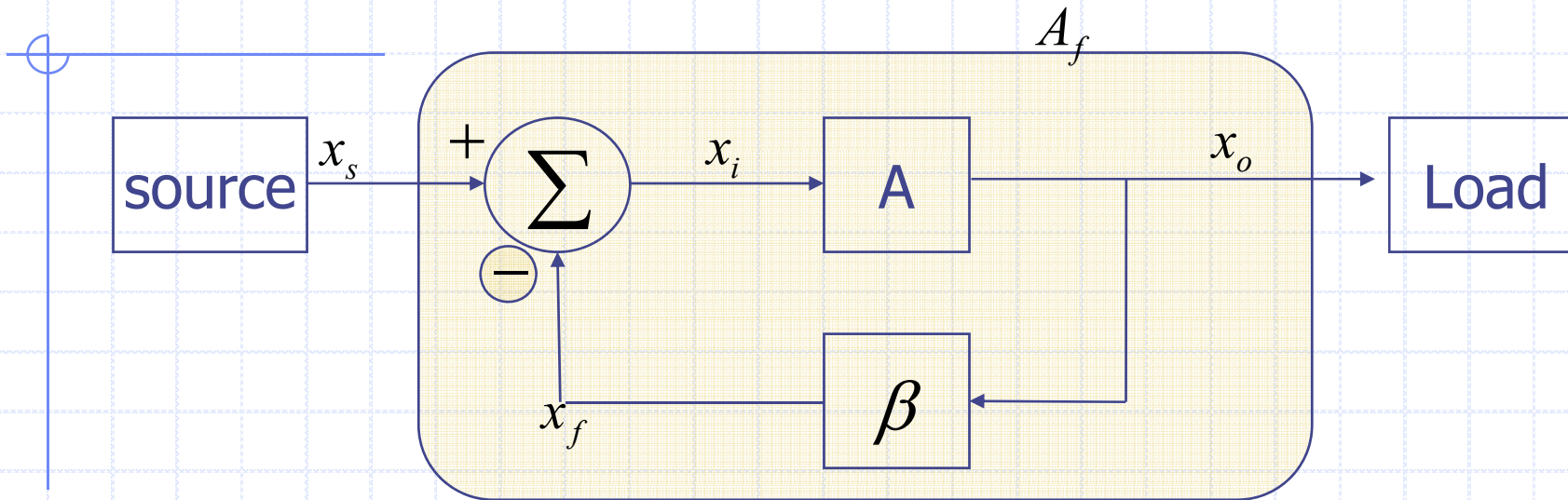

A : open loop gain

β : feedback factor

$A \cdot \beta \Rightarrow$ loop gain

$1 + A \cdot \beta \Rightarrow$ amount of feedback

A_f : closed loop gain

$$A_f \equiv \frac{x_o}{x_s} = \frac{A}{1 + A \cdot \beta}$$

$$A_f = \frac{1}{\beta} \text{ as } A \rightarrow \infty$$

Note that A and β are in fact transfer functions.

2. Some Properties of Negative Feedback

- ◆ As mentioned in the introduction, negative FB trades off gain for some other desired properties.
- ◆ It will become apparent explicitly in this section.

2. Some Properties of Negative Feedback

◆ Gain Desensitivity

$$A_f = \frac{A}{1 + A\beta} \longrightarrow \frac{dA_f}{dA} = \frac{(1 + A\beta) - A\beta}{(1 + A\beta)^2} = \frac{1}{(1 + A\beta)^2}$$
$$= \frac{1}{1 + A\beta} \cdot \frac{A}{1 + A\beta} \cdot \frac{1}{A}$$

$$\longrightarrow \boxed{\frac{dA_f}{A_f} = \frac{1}{1 + A\beta} \cdot \frac{dA}{A}}$$

The percentage change in A_f is smaller than the percentage change in A by the amount of feedback ($\equiv 1 + A\beta$).

2. Some Properties of Negative Feedback

◆ Bandwidth Extension

Consider an amplifier with a single pole, then

$$\text{open-loop TF: } A(s) = \frac{A_M}{1 + s/\omega_H}$$


$$A_f(s) = \frac{A(s)}{1 + A(s)\beta} \longrightarrow A_f(s) = \frac{\frac{A_M}{1 + s/\omega_H}}{1 + \frac{A_M}{1 + s/\omega_H} \cdot \beta} = \frac{A_f}{1 + s/((1 + A_M\beta)\omega_H)}$$

$$\therefore \omega_{Hf} = \omega_H (1 + A_M\beta)$$

The upper 3-dB frequency is increased by a factor equal to the amount of feedback ($\equiv 1 + A\beta$), where A_M denotes the midband gain and ω_H is the upper 3-dB frequency. However, the gain-bandwidth product remains constant.

2. Some Properties of Negative Feedback

◆ Noise Reduction

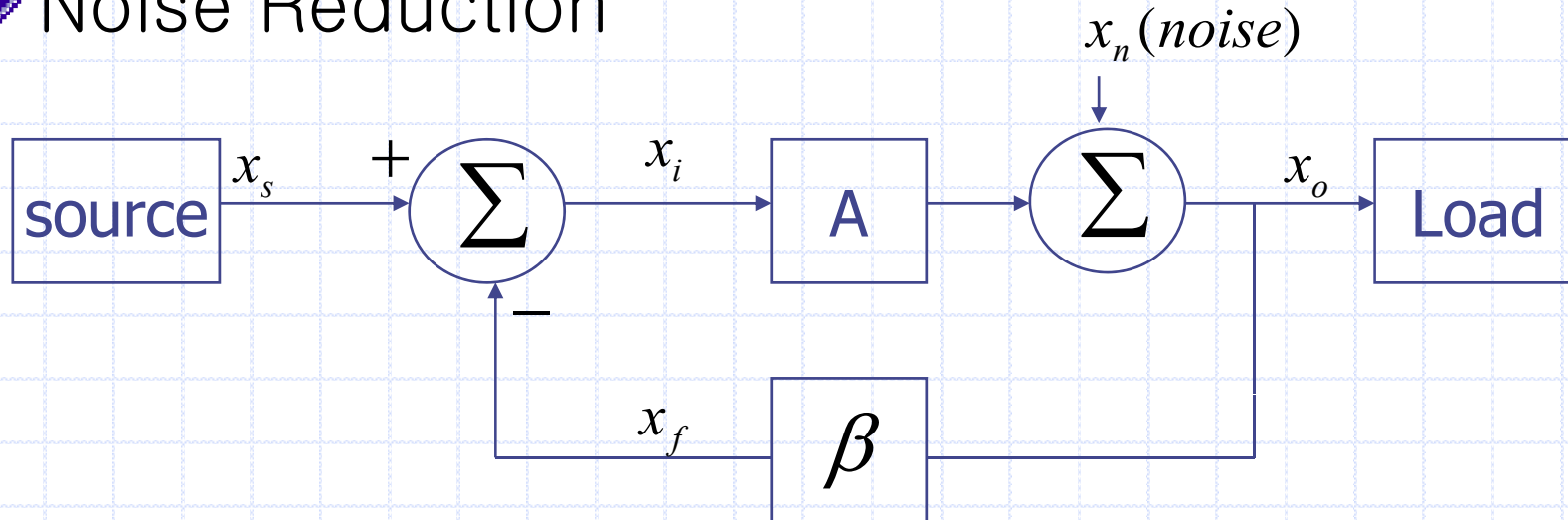

$$\left[\begin{array}{l} x_o = A \cdot x_i + x_n \\ x_f = \beta \cdot x_o \\ x_i = x_s - x_f \end{array} \right]$$

→


$$\begin{aligned} x_o &= A \cdot (x_s - x_f) + x_n \\ &= A \cdot x_s - A \cdot \beta \cdot x_o + x_n \\ \therefore x_o &= \frac{A \cdot x_s}{1 + A\beta} + \frac{x_n}{1 + A\beta} = A_f \cdot x_s + \frac{x_n}{1 + A\beta} \end{aligned}$$

The magnitude of noise seen at the output is reduced by the amount of feedback.

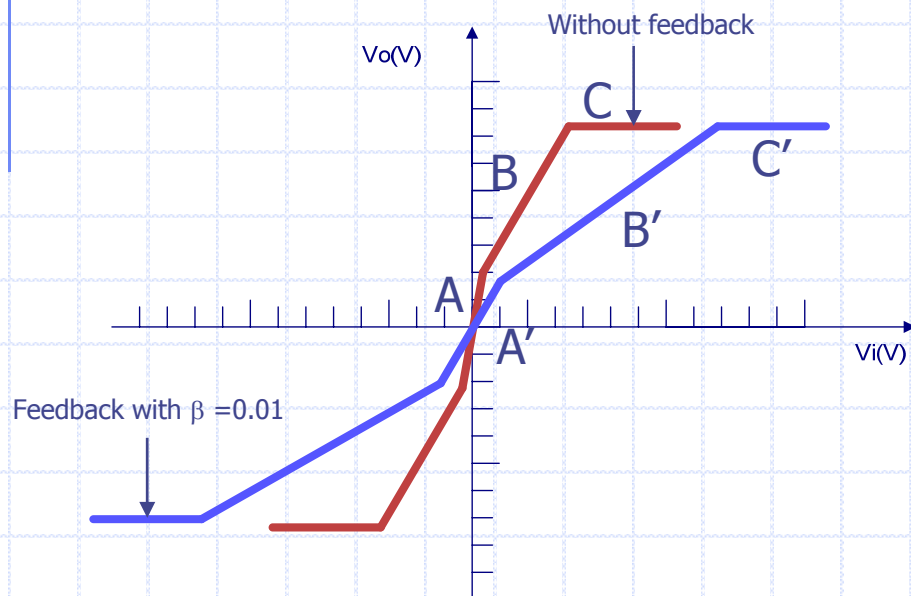2. Some Properties of Negative Feedback

◆ Reduction in Nonlinear Distortion

Consider an amplifier with the gain of 1000 in region A, 100 in region B, and 0 in region C.



Under feedback,
by $A_f = \frac{A}{1 + A\beta}$ ($\beta = 0.01$)

Gain in region A' is 90.9

Gain in region B' is 50

Gain in region C' is 0

The amplifier transfer characteristic is considerably **linearized**.

3. The Four Basic Feedback Topologies

◆ There are four basic feedback topologies, namely,

- Series–Shunt
- Shunt–Series
- Series–Series
- Shunt–Shunt


◆ Each has an aptitude on four different kinds of amplifiers discussed in Chapter 1. Correct application of feedback topology **idealizes** the amplifier's **input/output impedance**.

3. The Four Basic Feedback Topologies


- ◆ The term ‘shunt’ is an another expression for ‘parallel’.
- ◆ Why are the names like that?
 - ◆ The word before the dash describes how the feedback signal is ‘mixed’ into the input.
 - ◆ The word after the dash describes how the feedback signal is ‘sampled’ from the output.
 - ◆ Voltage is mixed in series and sampled in parallel.
 - ◆ Current is mixed in parallel and sampled in series.
 - ◆ Ex) Series–shunt mixes in series and samples in parallel. So both input and output has to be a voltage.

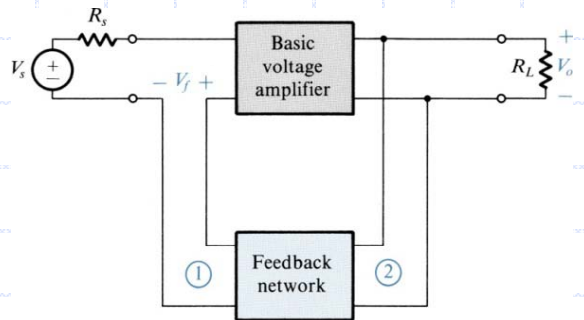3. The Four Basic Feedback Topologies


◆ Four kinds of amplifier paired with its most effective feedback topology.




(a) Voltage Amp.(series-shunt)

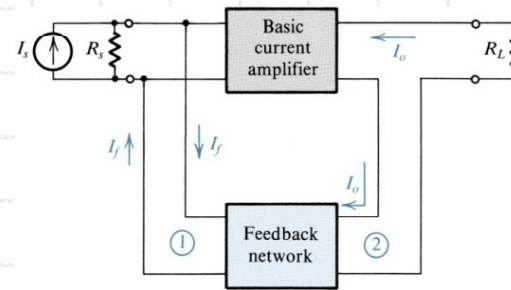

(b) Current Amp.(shunt-series)

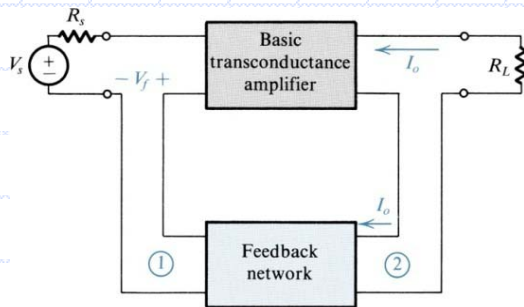

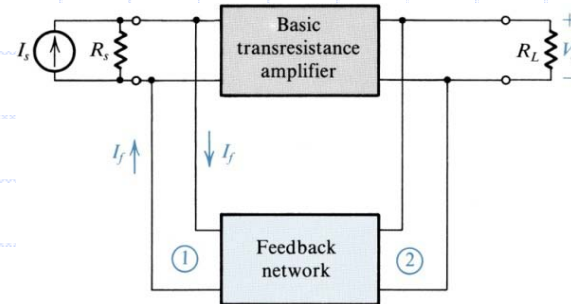
(c) Transconductance Amp.
(series-series)



(d) Transresistance Amp.
(shunt-shunt)

Appendix B – Two Port Network Parameters

◆ Review of Two Port Network

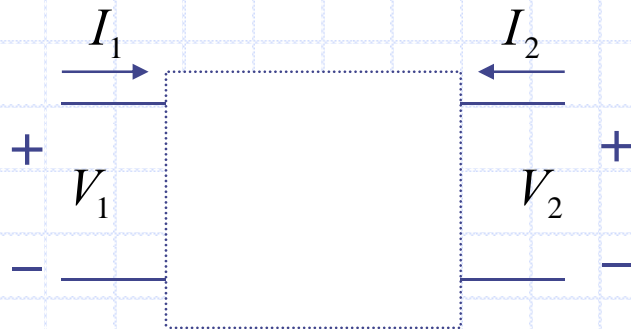

1) h param.(series-shunt)

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

2) z param.(series-series)

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

3) y param.(shunt-shunt)

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

4) g param.(shunt-series)

$$I_1 = g_{11}V_1 + g_{12}I_2$$






$$V_2 = g_{21}V_1 + g_{22}I_2$$

Appendix B – Two Port Network Parameters

1) h param.(series-shunt) – I_1 and V_2 are the stimuli

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

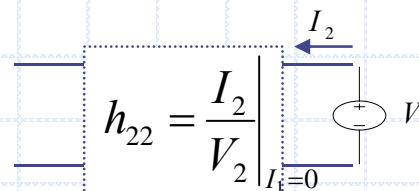
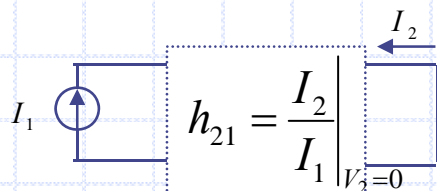
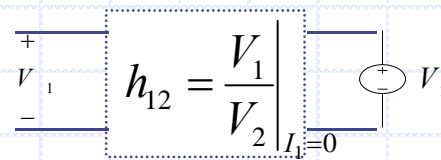
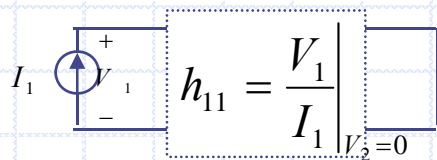
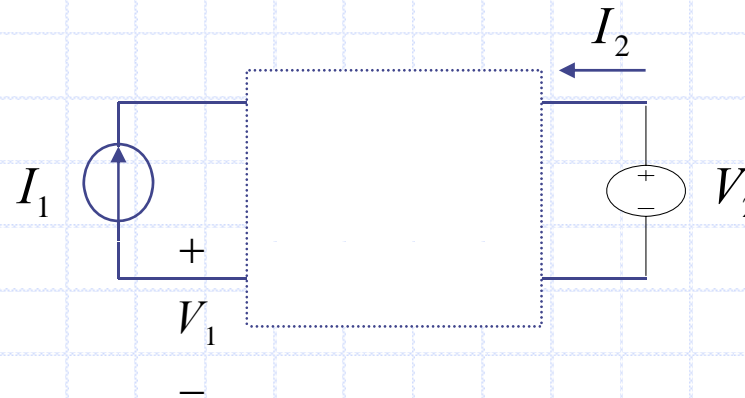


Appendix B – Two Port Network Parameters

2) z param.(series-series) – I_1 and I_2 are the stimuli

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

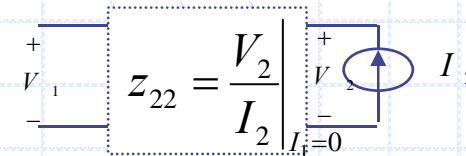
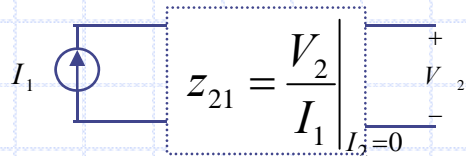
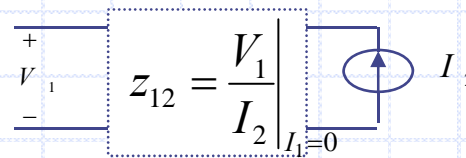
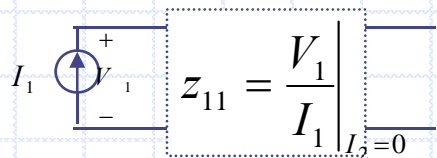
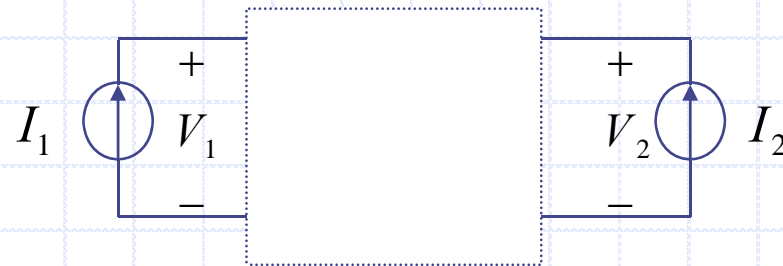


Appendix B – Two Port Network Parameters

3) y param.(shunt-shunt) – V_1 and V_2 are the stimuli

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

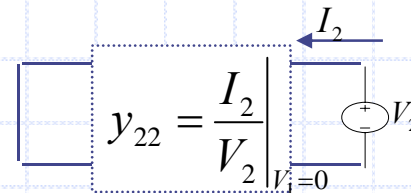
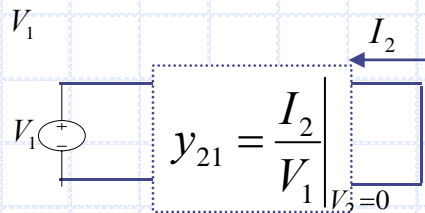
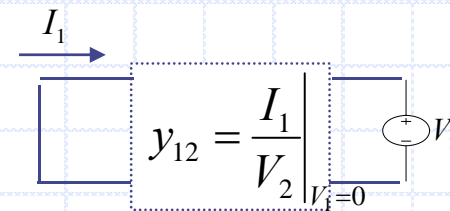
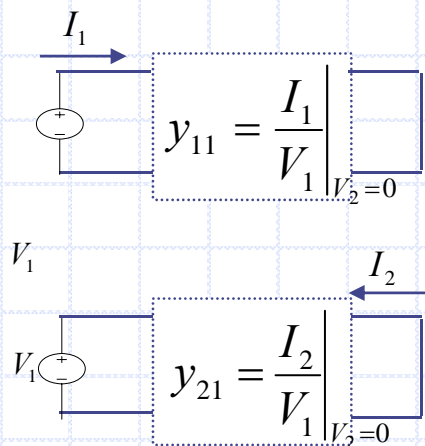
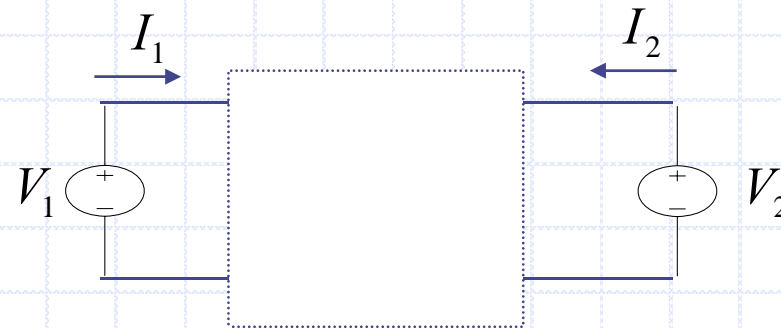


Appendix B – Two Port Network Parameters

4) g param.(shunt-series) – V_1 and I_2 are the stimuli

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$

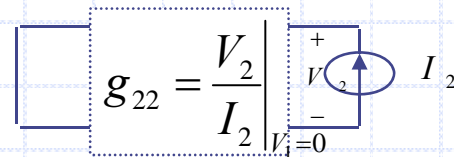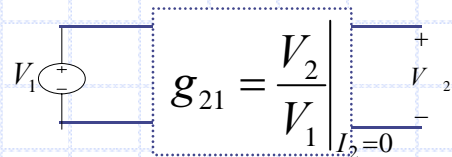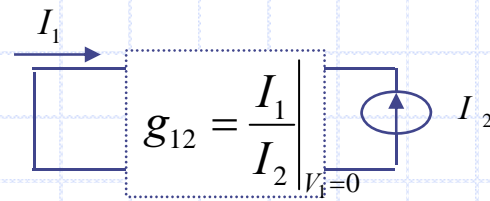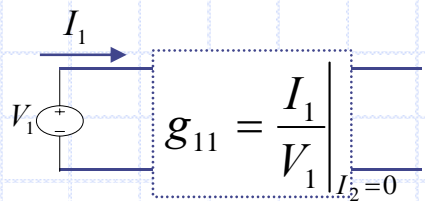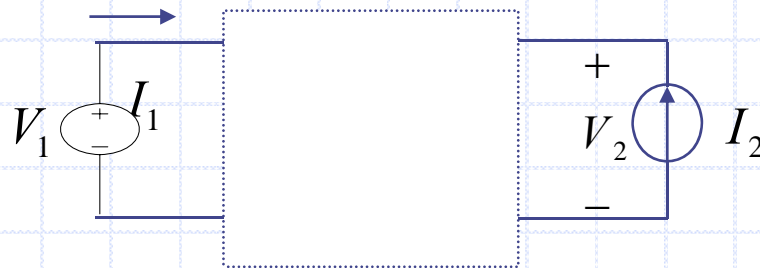

4. The Series-Shunt Feedback Amplifier


◆ Series-Shunt (voltage amp)

=> Input is mixed in voltage(series), and output is sampled in voltage(shunt).

- Whenever **voltage is mixed**, the input impedance is **increased** by the amount of feedback.
- Whenever **voltage is sampled**, the output impedance is **reduced** by the amount of feedback.

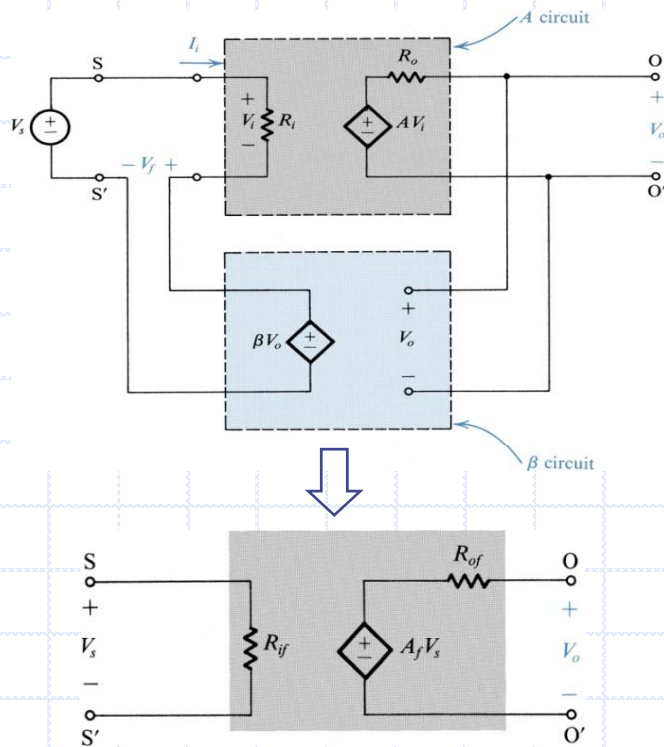4. The Series-Shunt Feedback Amplifier

◆ Ideal Situation (w/o load and source res.)



$$A_f \equiv \frac{V_o}{V_s} = \frac{A}{1 + A\beta}$$


$$R_{if} \equiv \frac{V_s}{I_i} = \frac{V_s}{V_i / R_i} = R_i \frac{V_s}{V_i} = R_i \frac{V_i + A\beta V_i}{V_i}$$

$$R_{if} = R_i(1 + A\beta)$$

$$Z_{if} = Z_i(1 + A(s)\beta(s))$$

4. The Series-Shunt Feedback Amplifier

◆ Ideal Situation(Cont'd)

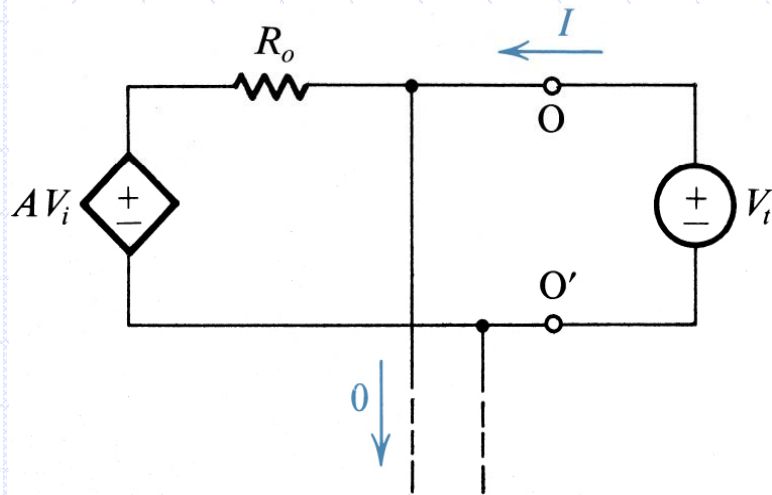

To find R_{of} , Set $V_S=0$, apply test voltage V_t

$$R_{of} \equiv \frac{V_t}{I}$$

$$I = \frac{V_t - AV_i}{R_o}$$

$$V_i = -V_f = -\beta V_o = -\beta V_t$$


$$I = \frac{V_t + A\beta V_t}{R_o}$$

$$R_{of} = \frac{R_o}{1 + A\beta}$$


$$Z_{of} = \frac{Z_i(s)}{1 + A(s)\beta(s)}$$

4. The Series-Shunt Feedback Amplifier


◆ Practical Situation

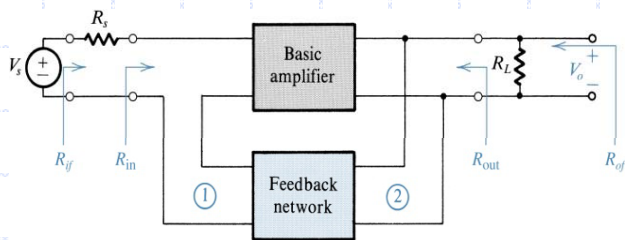

(a) Practical series-shunt amp.

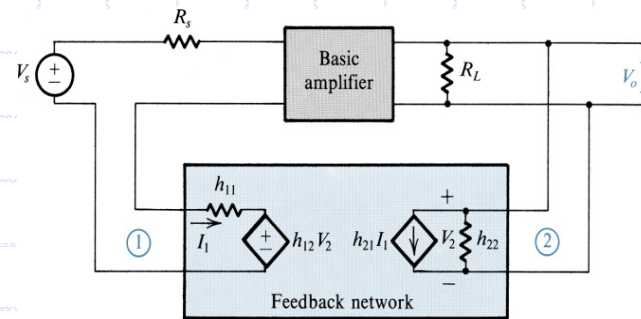

(b) Represented by h parameters

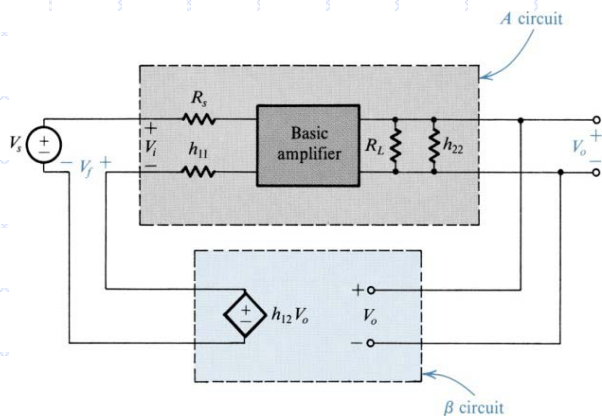


(c) Neglecting h_{21} (similar to ideal case)

$$\beta = h_{21} \equiv \frac{V_1}{V_2} \Big|_{I_1=0}$$

4. The Series-Shunt Feedback Amplifier

Summary

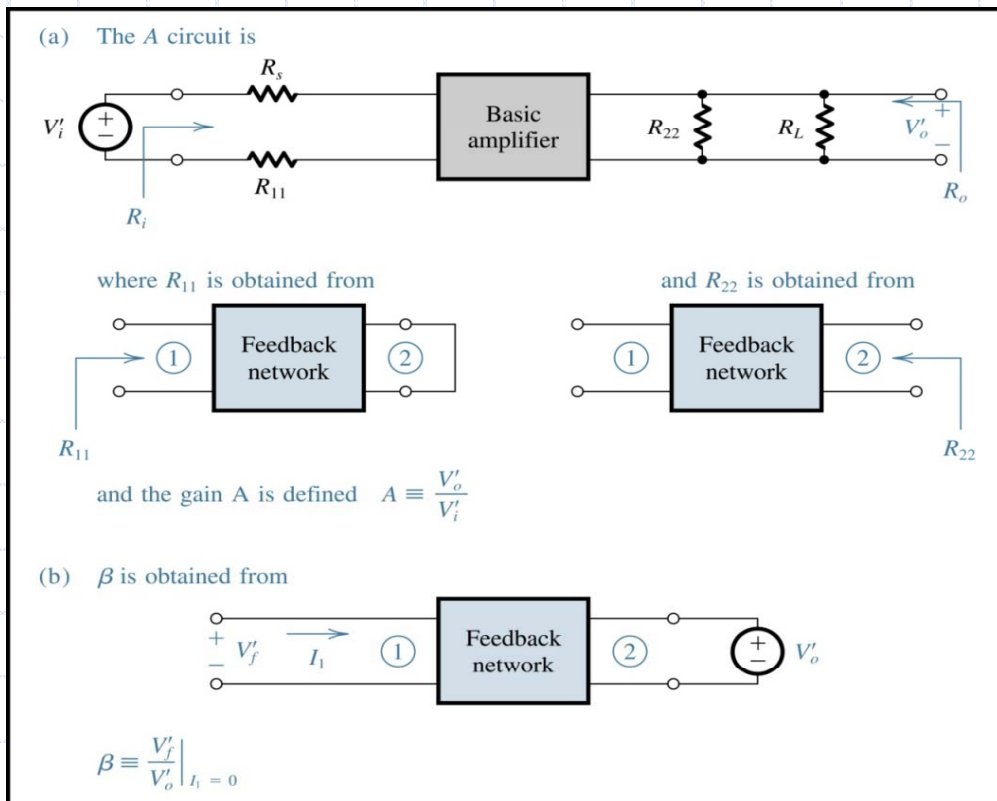

$$R_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$R_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

$$R_{in} = R_{if} - R_s$$


$$R_{out} = 1 / \left(\frac{1}{R_{of}} - \frac{1}{R_L} \right)$$

(in Fig. 8.10(a))

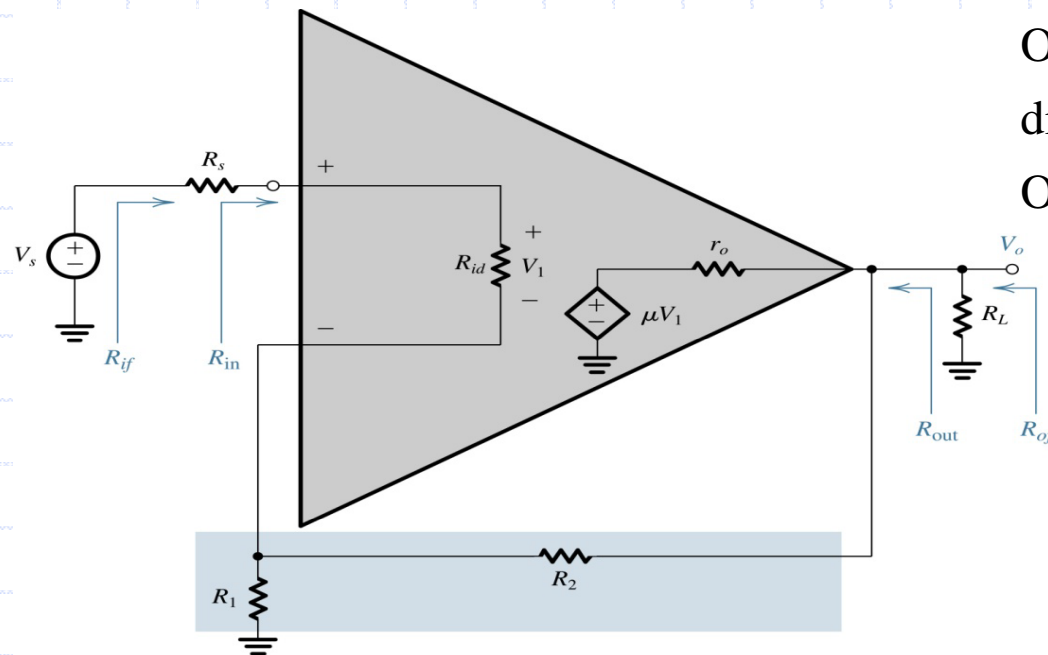4. The Series-Shunt Feedback Amplifier

◆ Example 8.1

Q : find the expressions for A , β , V_o / V_s , R_{in} and R_{out} .



Open loop gain : $\mu = 10^4$

diff. input resistance : $R_{id} = 100 \text{ k}\Omega$

Output resistance : $r_o = 1 \text{ k}\Omega$

$$R_1 = 1 \text{ k}\Omega$$


$$R_2 = 1 \text{ M}\Omega$$

$$R_s = 10 \text{ k}\Omega$$

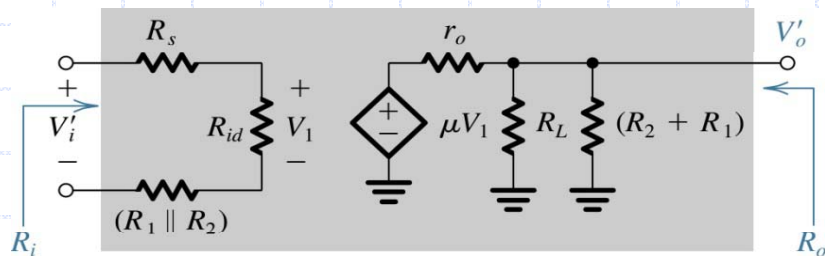4. The Series-Shunt Feedback Amplifier


◆ Example 8.1 (Cont'd)

It sample voltage and mixes voltage, so series-shunt...



$$A \equiv \frac{V_o'}{V_i} = \mu \frac{R_L \parallel (R_1 + R_2)}{[R_L \parallel (R_1 + R_2)] + r_o} \cdot \frac{R_{id}}{R_{id} + R_s + (R_1 \parallel R_2)}$$

$$\approx 6000(V/V)$$


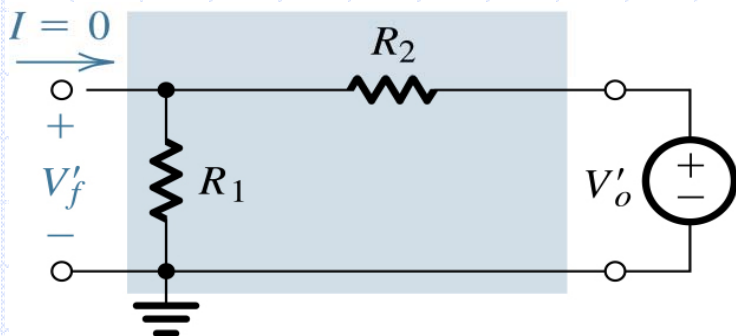


$$\beta \equiv \frac{V_f'}{V_o'} = \frac{R_1}{R_1 + R_2} \approx 10^{-3}(V/V)$$

$$A_f \equiv \frac{V_o}{V_s} = \frac{A}{1 + A\beta} \approx 857(V/V)$$

4. The Series-Shunt Feedback Amplifier

◆ Example 8.1 (Cont'd)

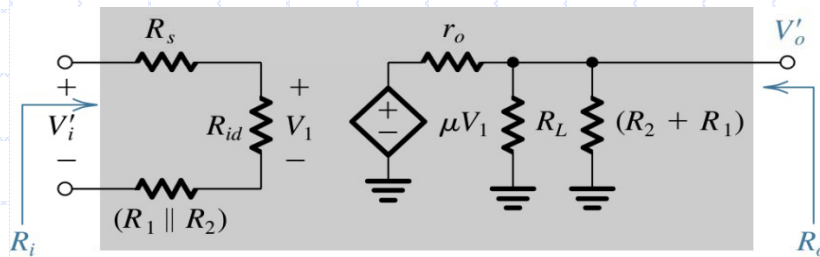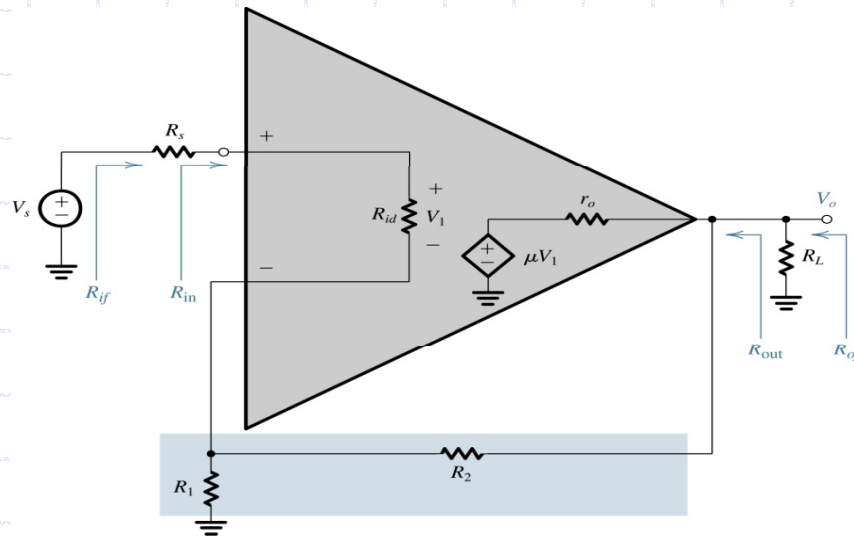

$$R_{if} = R_i(1 + A\beta)$$

$$R_i = R_s + R_{id} + (R_1 // R_2) \approx 111 \text{ k}\Omega$$

$$R_{if} = 111 \times 7 = 777 \text{ k}\Omega$$

$$R_{in} = R_{if} - R_s \approx 739 \text{ k}\Omega$$

$$R_{of} = \frac{R_o}{1 + A\beta}$$

$$R_o = r_o // R_L // (R_2 + R_1) \approx 667 \Omega$$

$$R_{of} = \frac{667}{7} \approx 95.3 \Omega$$


$$R_{out} = 1 / \left(\frac{1}{R_{of}} - \frac{1}{R_L} \right) \approx 100 \Omega$$

5. The Series-Series Feedback Amplifier

- ◆ Series-Series (transconductance amp.)
=> Input is mixed in voltage(series), and output is sampled in current(series).
 - Whenever **voltage is mixed**, the input impedance is **increased** by the amount of feedback.
 - Whenever **current is sampled**, the output impedance is **increased** by the amount of feedback.

5. The Series-Series Feedback Amplifier


◆ Ideal Situation

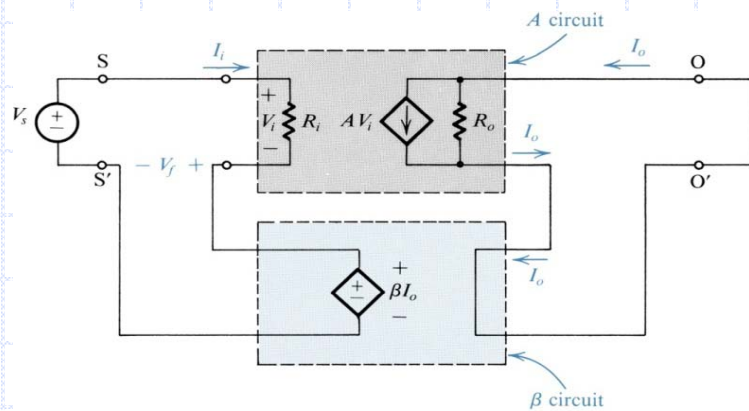

As shown previously,

$$A_f \equiv \frac{V_o}{V_s} = \frac{A}{1 + A\beta}$$


$$R_{if} = R_i(1 + A\beta)$$

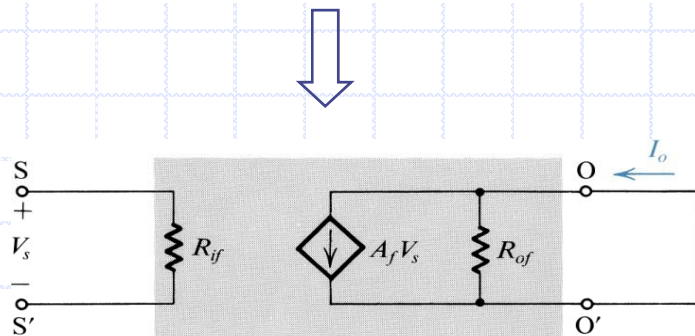

$$Z_{if} = Z_i(1 + A(s)\beta(s))$$

5. The Series-Series Feedback Amplifier

◆ Ideal Situation(Cont'd)

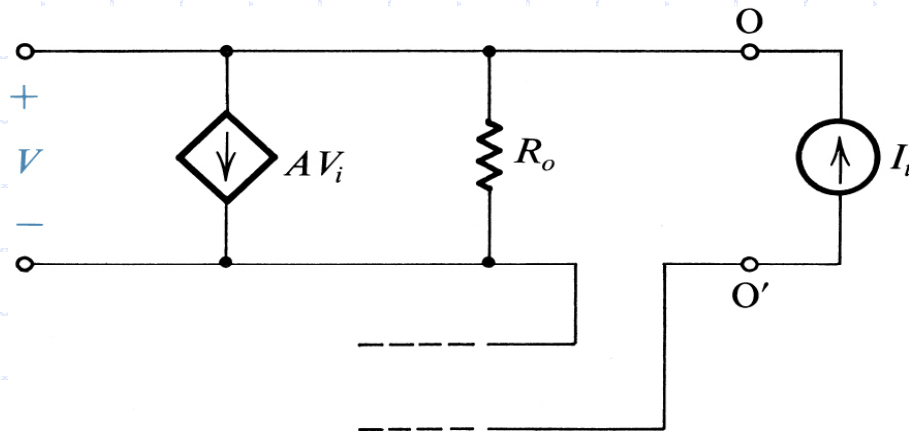

$$R_{of} \equiv \frac{V_t}{I_t}$$

$$V_i = -V_f = -\beta I_o = -\beta I_t$$

$$V = (I_t - AV_i)R_o = (I_t + A\beta I_t)R_o$$


$$R_{of} = (1 + A\beta)R_o$$

To find R_{of} , Set $V_S=0$, apply test current V_t


$$Z_{of} = Z_o (1 + A(s)\beta(s))$$

5. The Series-Series Feedback Amplifier


◆ Practical Situation

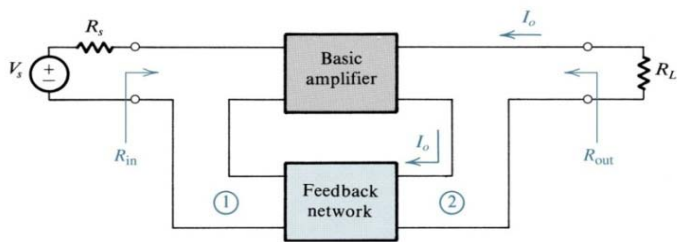

(a) Practical series-series amp.

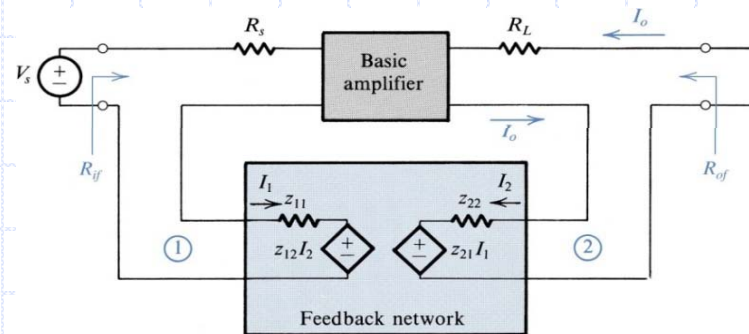

(b) Represented by z parameters

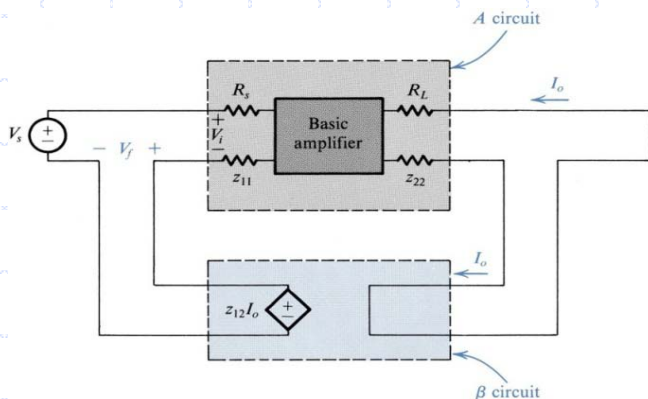


(c) Neglecting z_{21} (similar to ideal case)

$$\beta = z_{21} \equiv \frac{V_1}{I_2} \Big|_{I_1=0}$$

5. The Series-Series Feedback Amplifier

Summary

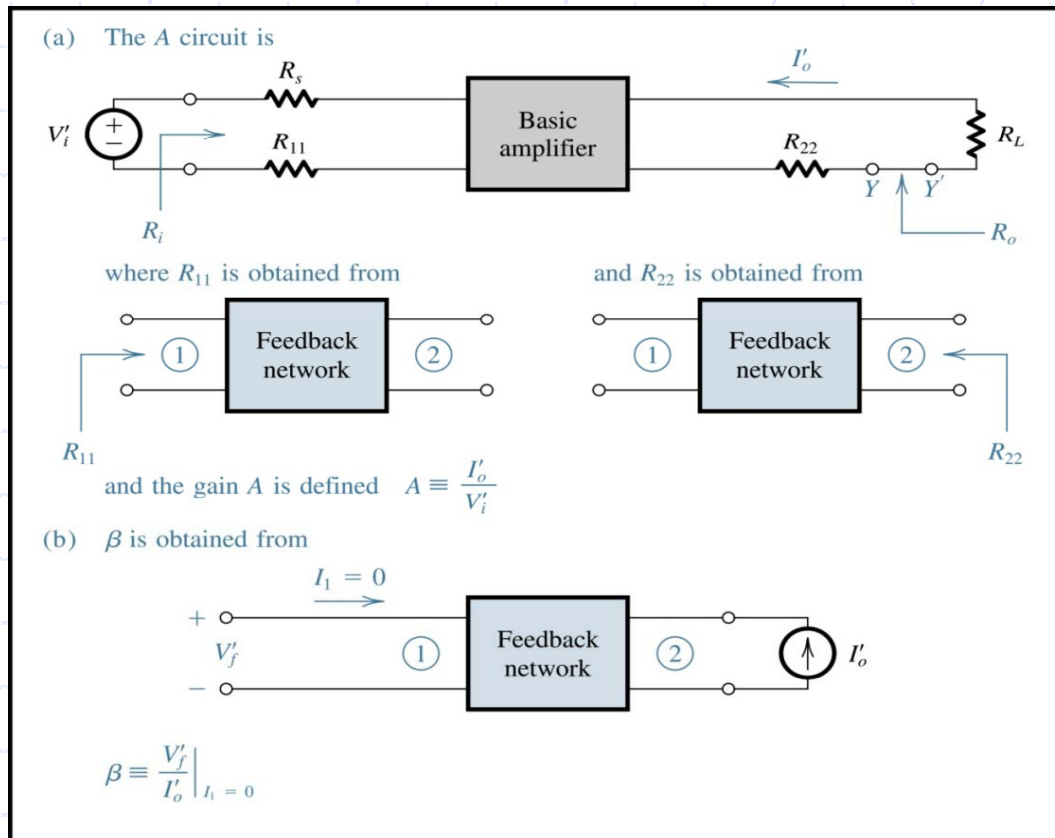

$$R_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$R_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

$$R_{in} = R_{if} - R_s$$


$$R_{out} = R_{of} - R_L$$

(in Fig. 8.15(b))

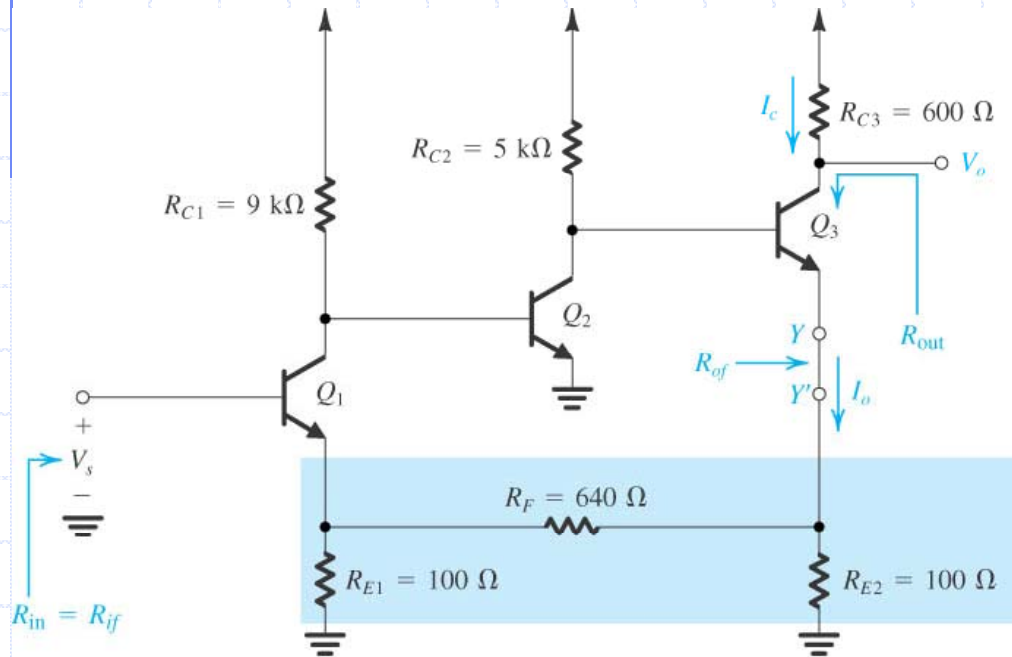5. The Series-Series Feedback Amplifier

◆ Example 8.2

Q : find the expressions for A , β , A_f , V_o / V_s , R_{in} , R_{of} , and R_{out} .



(a)

$$I_{C1} = 0.6\text{ mA}$$

$$I_{C2} = 1\text{ mA}$$


$$I_{C3} = 4\text{ mA}$$

$$h_{fe} = 100$$

$$\text{assume } r_o = \infty$$

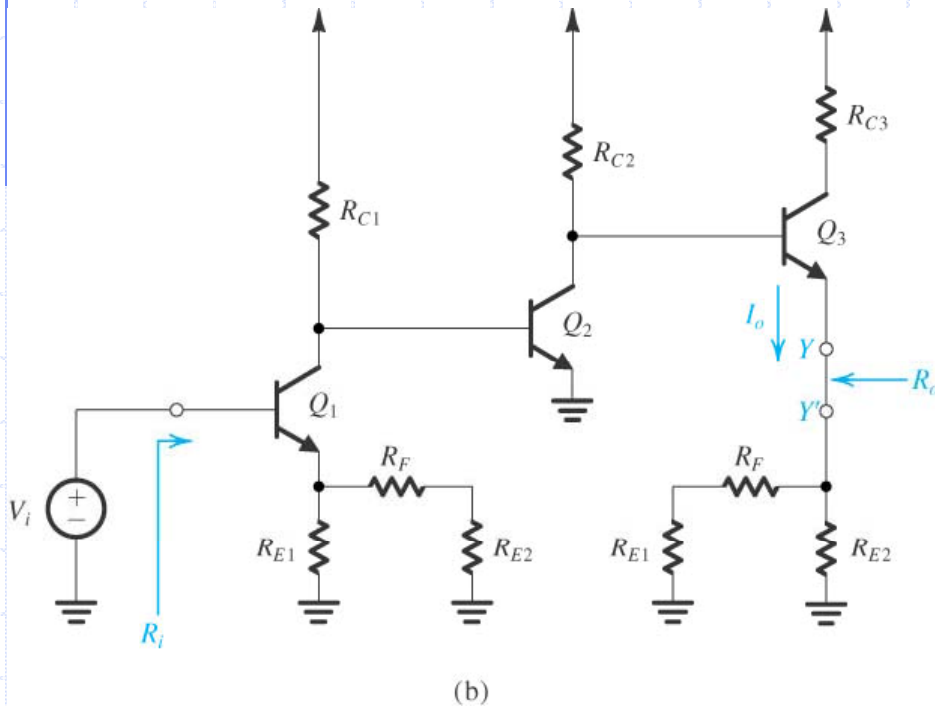5. The Series-Series Feedback Amplifier

◆ Example 8.2(Cont'd)
It samples current and mixes voltage, so series-series...



$$\frac{V_{c1}}{V_i} = \frac{-\alpha_1(R_{C1} // r_{\pi 2})}{r_{e1} + [R_{E1} // (R_F + R_{E2})]} \approx -14.92 (V/V)$$

$$\frac{V_{c2}}{V_{c1}} = -g_{m2} \{ R_{C2} // (h_{fe} + 1)[r_{e3} + (R_{E2} // (R_F + R_{E1}))] \} \approx -131.2 (V/V)$$


$$\frac{I_o}{V_{c2}} = \frac{I_{e3}}{V_{b3}} = \frac{1}{r_{e3} + (R_{E2} // (R_F + R_{E1}))} \approx 10.6 (mA/V)$$

$$A = \frac{I_o}{V_i} = \frac{V_{c1}}{V_i} \cdot \frac{V_{c2}}{V_{c1}} \cdot \frac{I_o}{V_{c2}} \approx 20.7 (A/V)$$

$$\beta = \frac{V_f}{I_o} = \frac{R_{E2}}{R_{E2} + R_F + R_{E1}} \times R_{E1} \approx 11.9 (\Omega)$$

5. The Series-Series Feedback Amplifier

◆ Example 8.2(Cont'd)

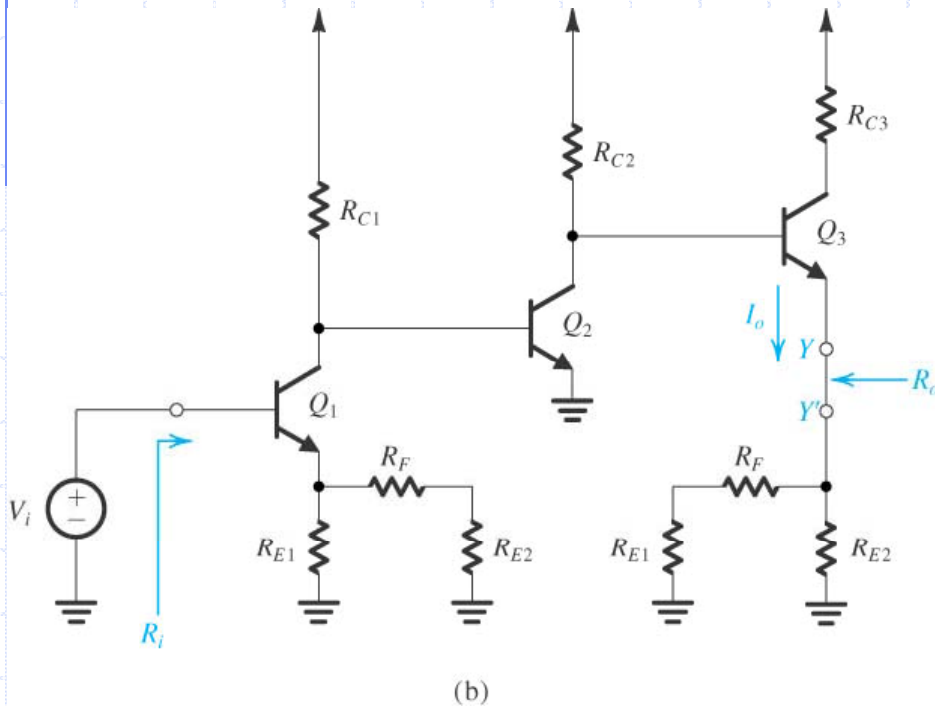

$$A_f = \frac{I_o}{V_s} = \frac{A}{1 + A\beta}$$

$$\approx 83.7 (mA/V)$$

$$\frac{V_o}{V_s} = \frac{I_c R_{C3}}{V_s} \cong \frac{-I_o R_{C3}}{V_s} = -A_f R_{C3}$$

$$\approx -50.2 (V/V)$$

$$R_{if} = R_i (1 + A\beta)$$

$$= (h_{fe} + 1) [r_{e1} + (R_{E1} // (R_F + R_{E2}))] (1 + A\beta)$$

$$\approx 13.65 \times (1 + 20.5 \times 11.9) = 3.34 (M\Omega)$$

$$R_{of} = R_o (1 + A\beta)$$

$$= \left\{ [R_{E2} // (R_F + R_{E1})] + r_{e3} + \frac{R_{C2}}{h_{fe} + 1} \right\} (1 + A\beta)$$

$$\approx 143.9 \times (1 + 20.5 \times 11.9) = 35.6 (k\Omega)$$

if $r_o = 25 k\Omega$

$$R_{out} = r_o + (1 + g_{m3} r_o) (R_{of} // r_{\pi 3})$$


$$\approx 2.5 (M\Omega)$$

6.1 The Shunt-Shunt Feedback Amplifier

- ◆ Shunt–Shunt (transresistance amp)
=> Input is mixed in current(shunt), and output is sampled in voltage(shunt).
 - Whenever **current is mixed**, the input impedance is **reduced** by the amount of feedback.
 - Whenever **voltage is sampled**, the output impedance is **reduced** by the amount of feedback.

6.1 The Shunt-Shunt Feedback Amplifier

◆ Ideal Situation

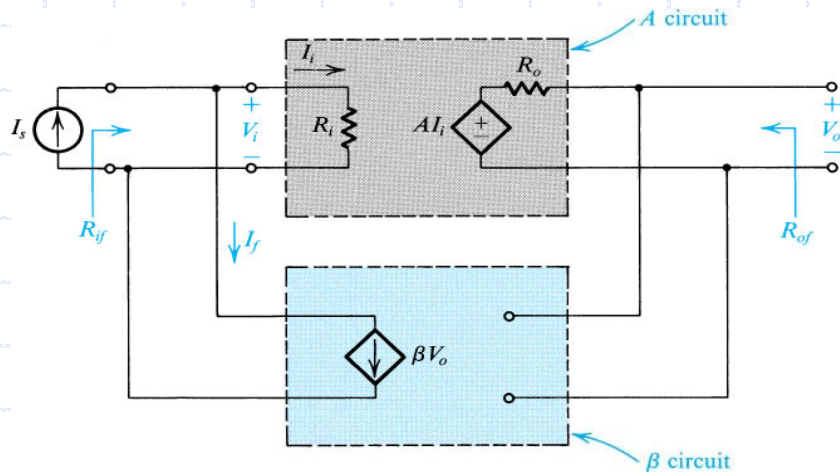


$$Z_{if} = \frac{Z_i(s)}{1 + A(s)\beta(s)}$$

$$Z_{of} = \frac{Z_o(s)}{1 + A(s)\beta(s)}$$

6.1 The Shunt-Shunt Feedback Amplifier

Summary

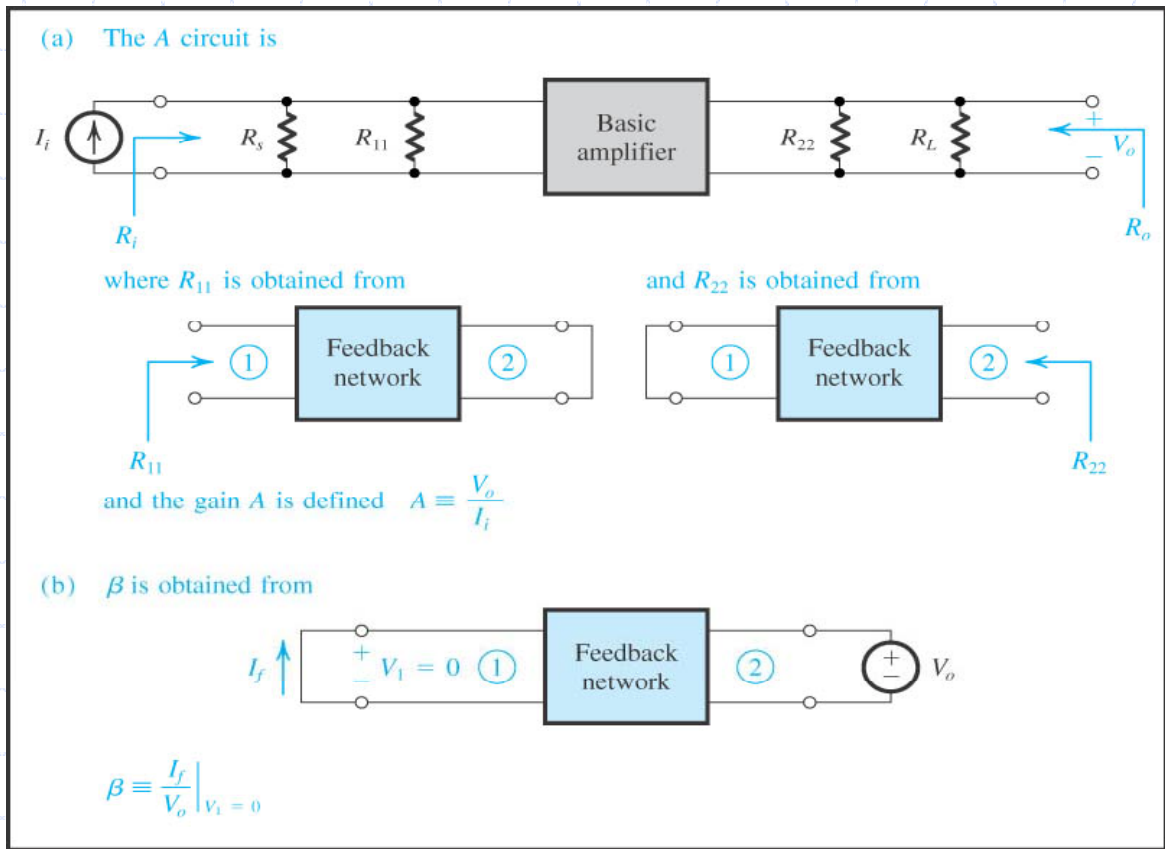



$$R_{in} = 1 / \left(\frac{1}{R_{if}} - \frac{1}{R_s} \right)$$

$$R_{out} = 1 / \left(\frac{1}{R_{of}} - \frac{1}{R_L} \right)$$

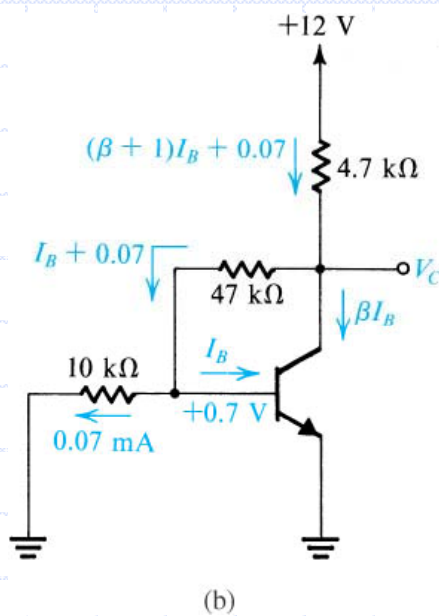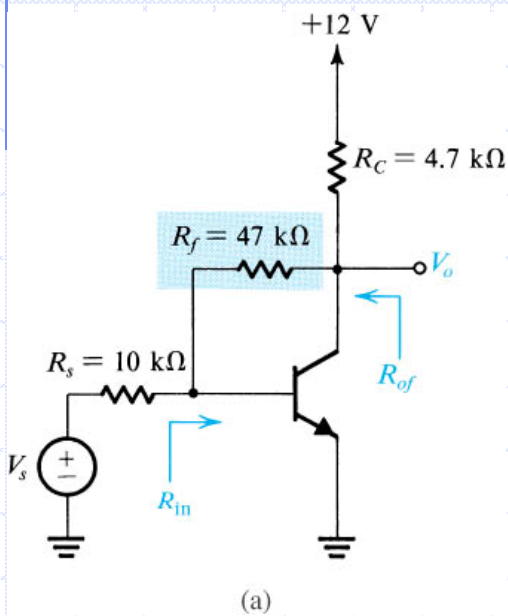6.1 The Shunt-Shunt Feedback Amplifier

◆ Example 8.3

Q : Determine $V_o / V_s, R_{in}, R_{of}.$ ($\beta = 100$)



$$V_C = 0.7 + (I_B + 0.07)47 = 3.99 + 47 I_B$$

$$\frac{12 - V_C}{4.7} = (\beta + 1)I_B + 0.07$$

$$I_B \approx 0.015 \text{ (mA)}$$




$$I_C \approx 1.5 \text{ (mA)}$$

$$V_C \approx 4.7 \text{ (V)}$$

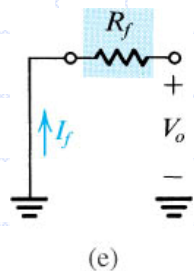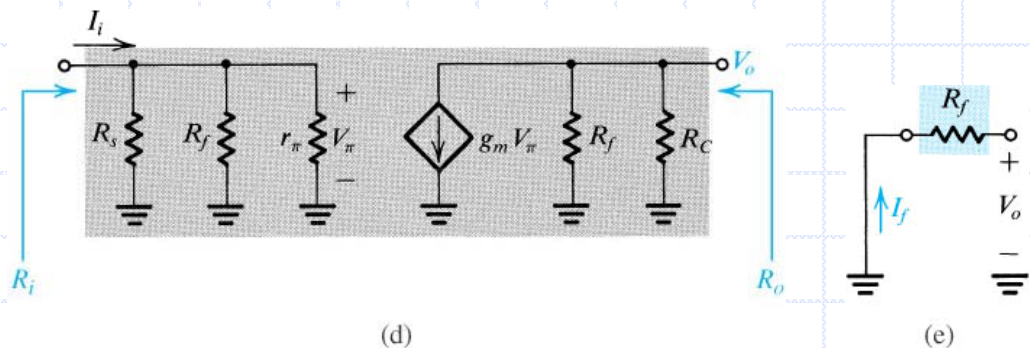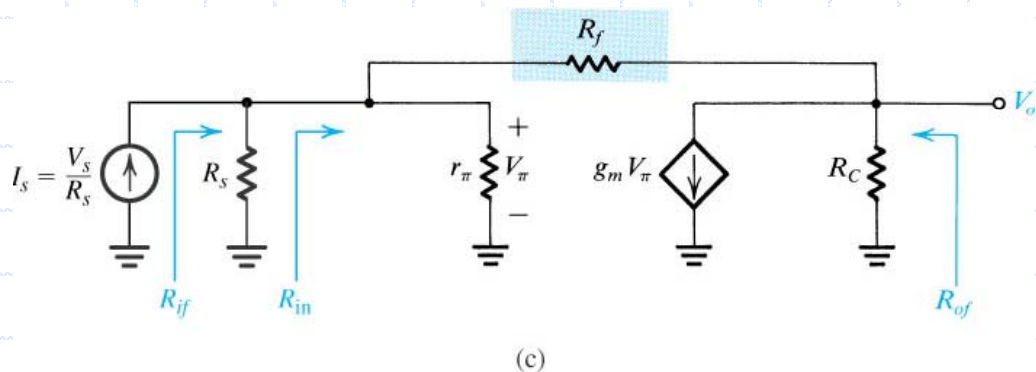6.1 The Shunt-Shunt Feedback Amplifier

◆ Example 8.3(Cont'd)

It samples voltage and mixes current, so shunt-shunt...



$$V_{\pi} = I_i (R_s \parallel R_f \parallel r_{\pi})$$

$$V_o = -g_m V_{\pi} (R_f \parallel R_C)$$



$$A = \frac{V_o}{I_i} = -g_m (R_f \parallel R_C) (R_s \parallel R_f \parallel r_{\pi})$$

$$= -358.7 (k\Omega)$$


$$\beta = \frac{I_f}{V_o} = -\frac{1}{R_f} = -\frac{1}{47 (k\Omega)}$$

$$A_f = \frac{V_o}{I_s} = \frac{A}{1 + A\beta}$$


$$= -41.6 (k\Omega)$$

6.1 The Shunt-Shunt Feedback Amplifier

◆ Example 8.3(Cont'd)

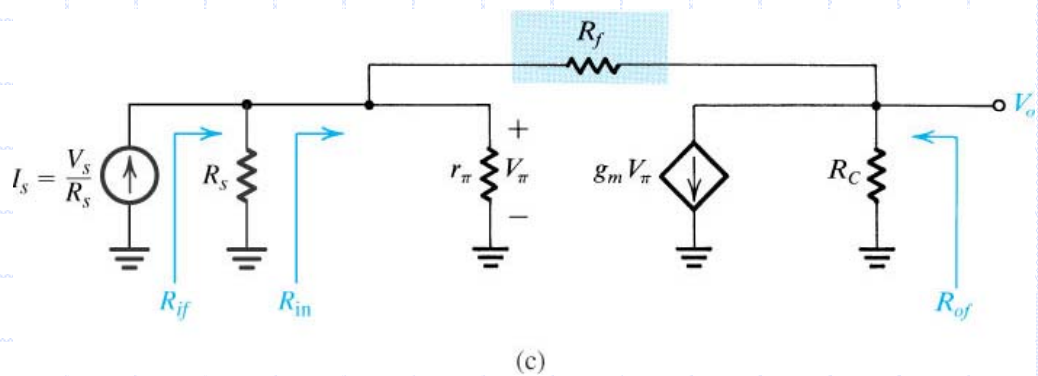
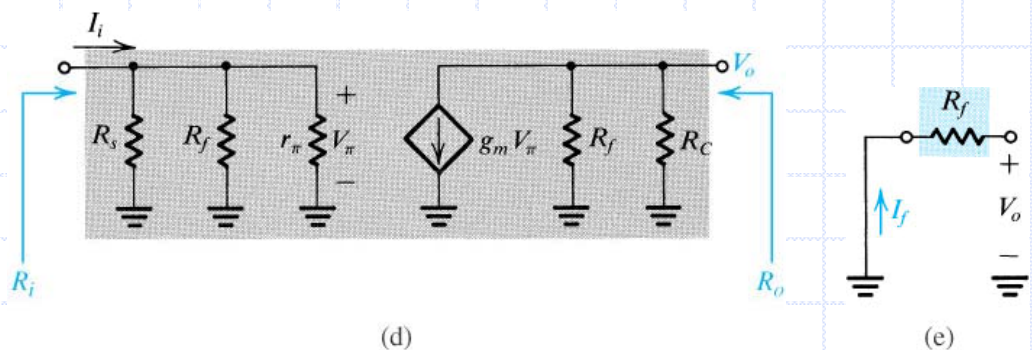
$$\frac{V_o}{V_s} = \frac{V_o}{I_s R_s} = \frac{A_f}{R_s} = -4.16 (V/V)$$




$$R_{if} = \frac{R_i}{1 + A\beta} = \frac{R_s // R_f // r_{\pi}}{1 + A\beta} = 162.2 (\Omega)$$

$$R_{of} = \frac{R_o}{1 + A\beta} = \frac{R_C // R_f}{1 + A\beta} = 495 (\Omega)$$

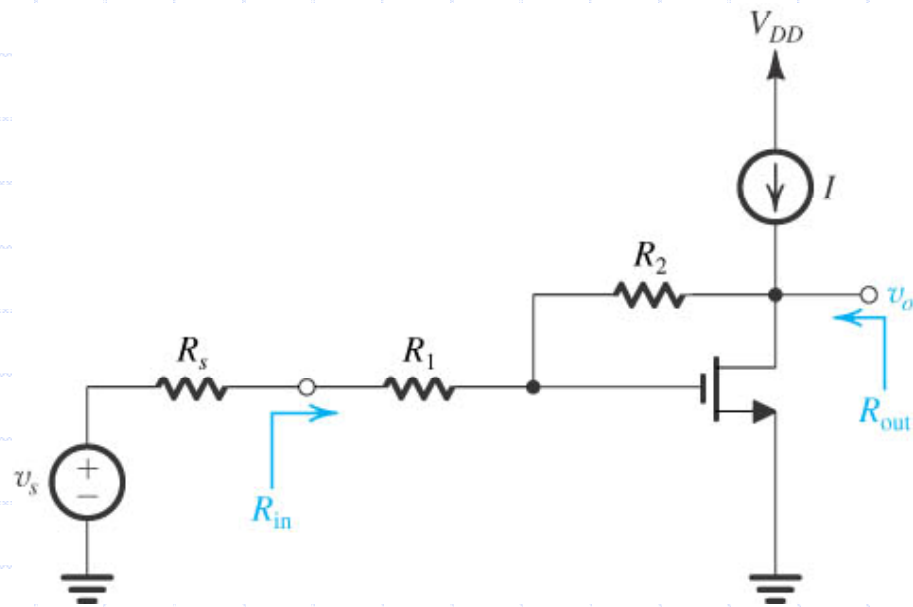6.1 The Shunt-Shunt Feedback Amplifier

◆ Problem 8.42(p.866)

Q : Identify the type of feedback used and find V_o/V_s , R_{in} , and R_{out} .



Given

$$I = 1(mA)$$

$$V_{GS} = 0.8(V)$$

$$V_t = 0.6(V)$$

$$V_A = 30(V)$$

$$R_S = 10(k\Omega)$$


$$R_1 = 10(M\Omega)$$

$$R_2 = 4.7(M\Omega)$$

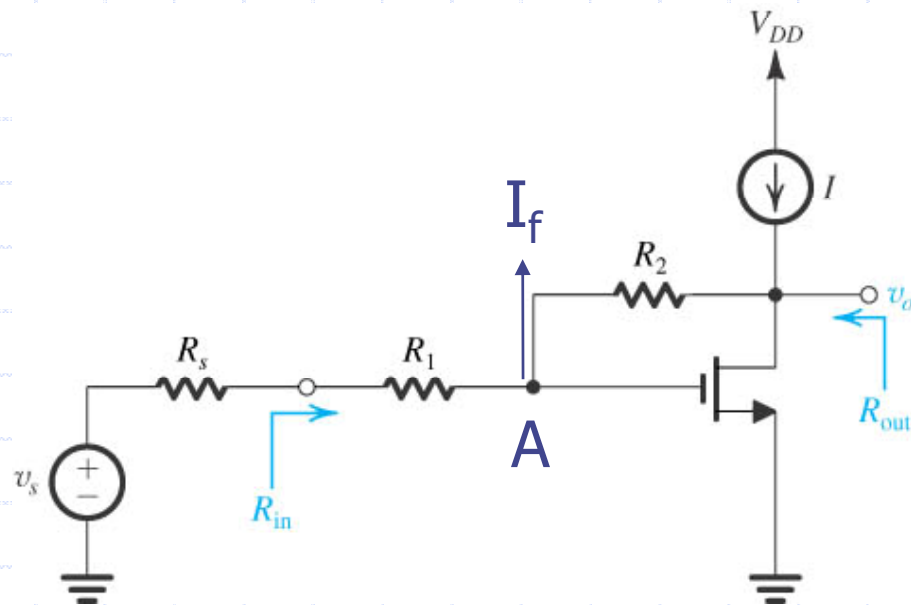6.1 The Shunt-Shunt Feedback Amplifier

◆ Problem 8.42(p.866) (Cont'd)

Voltage is sampled, and current is mixed.
So shunt-shunt feedback amplifier.



$$\begin{aligned}
 A &= \frac{V_o}{I_s} = \frac{V_A}{I_s} \frac{V_o}{V_A} \\
 &= -[(R_s + R_1) \parallel R_2](R_2 \parallel r_o) g_m \\
 &= -2.4 \times 10^7 (V / A)
 \end{aligned}$$


$$\beta = \frac{I_f}{V_o} = -\frac{1}{R_f} = -2.1 \times 10^{-7} (A / V)$$

$$A_f = \frac{A}{1 + A\beta} = -3.9 \times 10^3 (V / A)$$

$$\frac{V_o}{V_s} = \frac{A_f}{R_s + R_1} = -3.89 (V / V)$$

6.1 The Shunt-Shunt Feedback Amplifier

◆ Problem 8.42(p.866) (Cont'd)

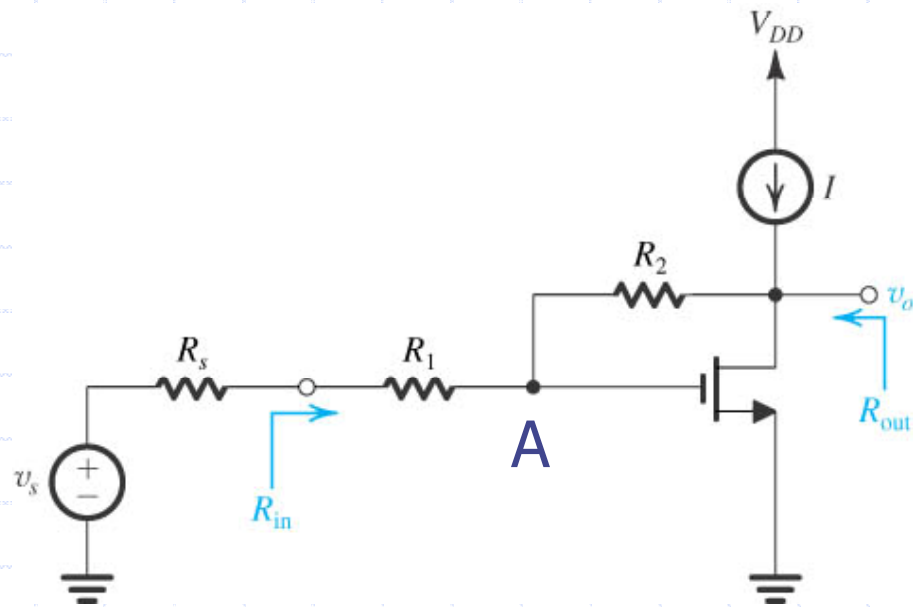

$$R_{in} = R_{if} - R_s = \frac{(R_s + R_1) // R_2}{1 + A\beta} - R_s$$

$$= 126 \text{ (k}\Omega\text{)}$$

$$R_{out} = R_{of} = \frac{r_o // R_2}{1 + A\beta}$$

$$= 4.86 \text{ (k}\Omega\text{)}$$

6.2 The Shunt-Series Feedback Amplifier


◆ Shunt-Series (current amp)

=> Input is mixed in current (shunt), and output is sampled in current (series).

- Whenever **current is mixed**, the input impedance is **reduced** by the amount of feedback.
- Whenever **current is sampled**, the output impedance is **increased** by the amount of feedback.

6.2 The Shunt-Series Feedback Amplifier

◆ Ideal Situation

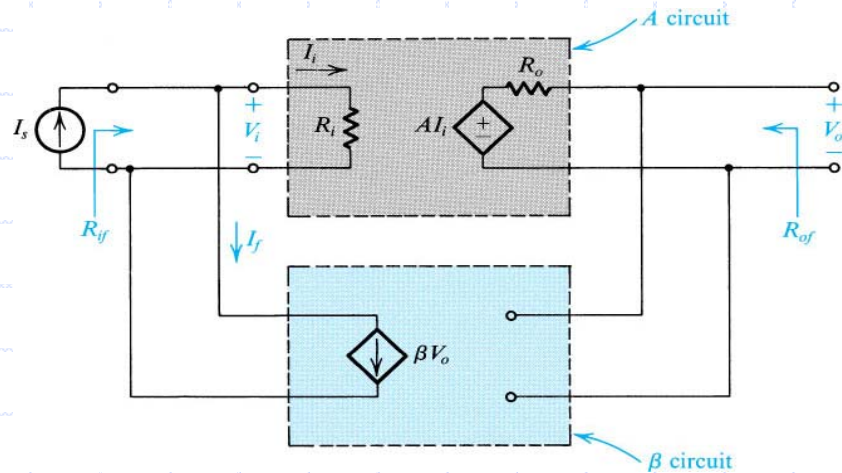


$$Z_{if} = \frac{Z_i(s)}{1 + A(s)\beta(s)}$$

$$Z_{of} = Z_o(1 + A(s)\beta(s))$$

6.2 The Shunt-Series Feedback Amplifier

Summary

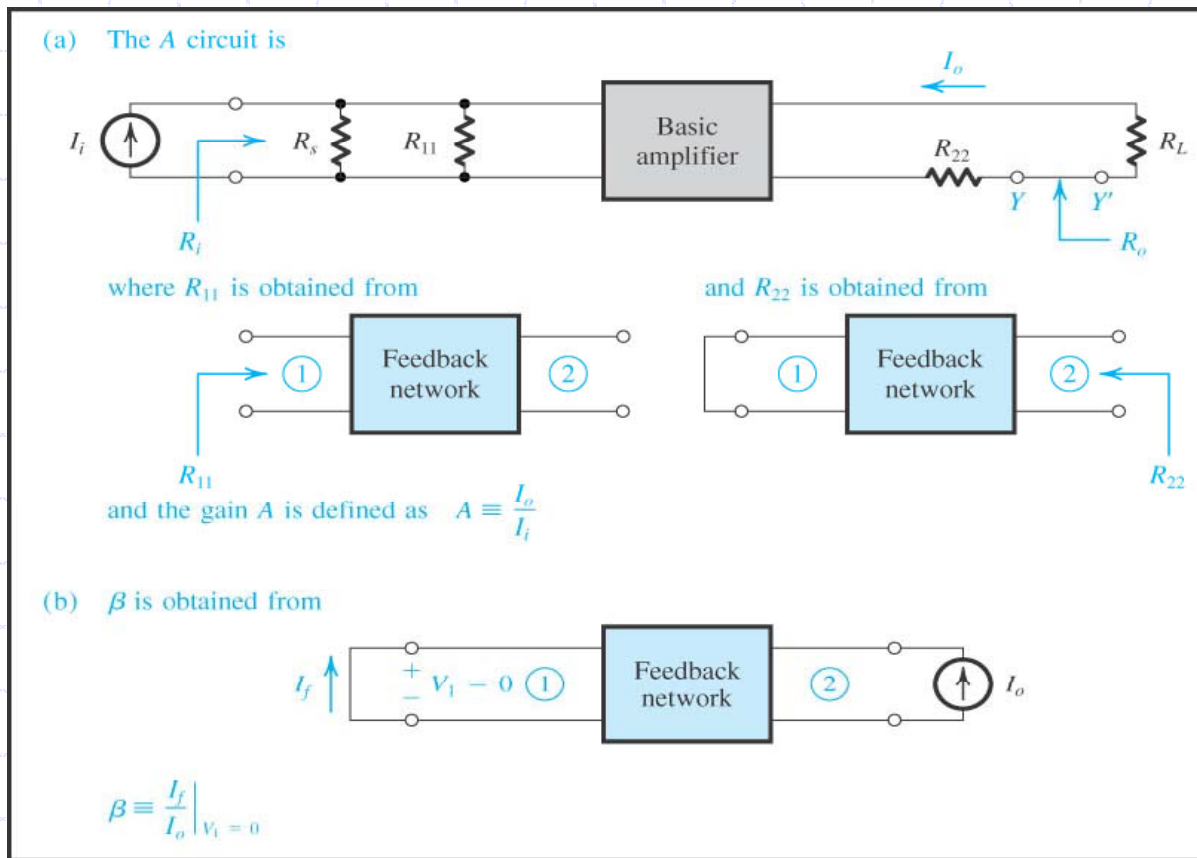


$$R_{in} = 1 / \left(\frac{1}{R_{if}} - \frac{1}{R_s} \right)$$

$$R_{out} = R_{of} - R_L$$

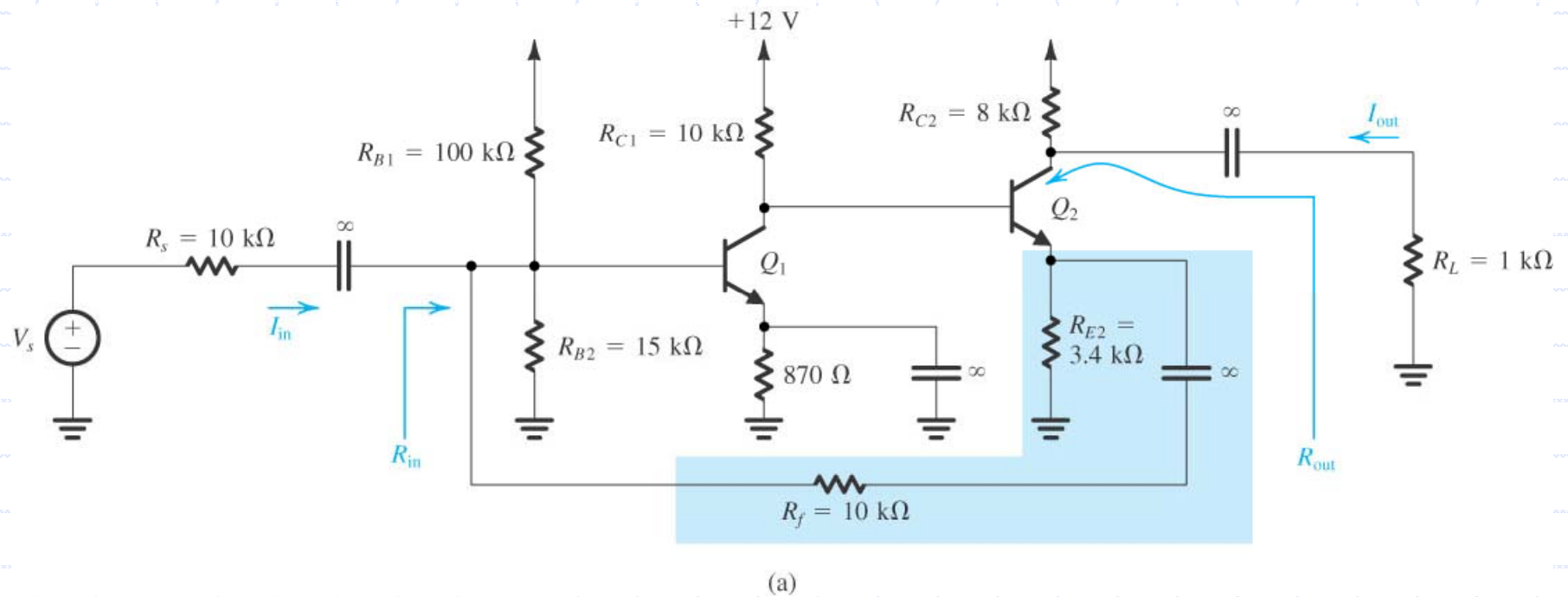6.2 The Shunt-Series Feedback Amplifier

◆ Example 8.4


Q : Find out I_{out}/I_{in} , R_{in} , and R_{out} . ($\beta = 100$, $V_A = 75(V)$)



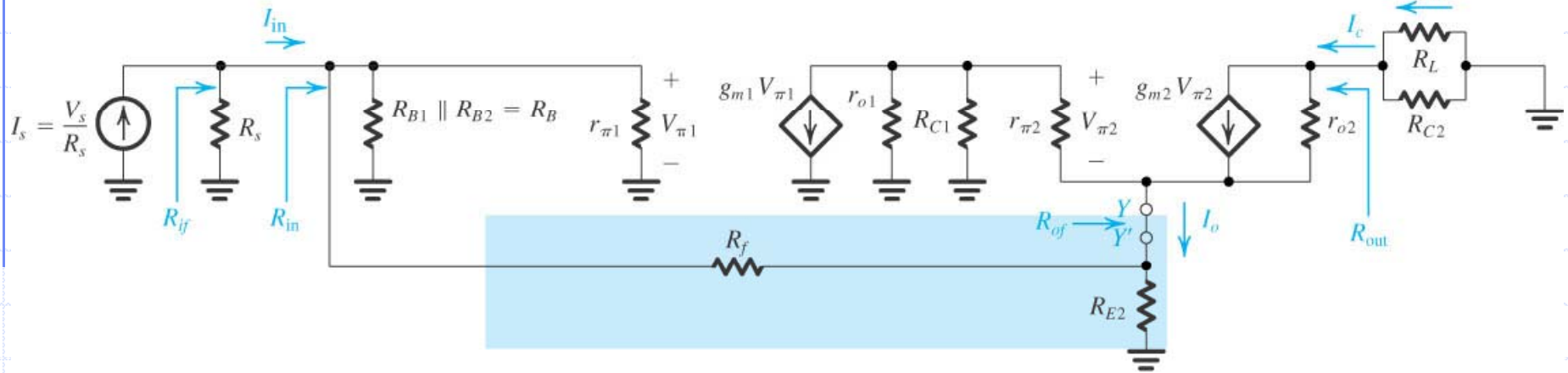6.2 The Shunt-Series Feedback Amplifier

◆ Example 8.4(Cont'd)

It samples current and mixes current, so shunt-series...



(b)

$$V_{B1} \approx 12 \times [15 / (100 + 15)] = 1.57 (V)$$

$$V_{E1} \approx 1.57 - 0.7 = 0.87 (V)$$

$$I_{E1} \approx 0.87 / 0.87 = 1 (mA)$$

$$V_{C1} \approx 12 - 10 \times 1 = 2 (V)$$




$$V_{E2} \approx 2 - 0.7 = 1.3 (V)$$

$$I_{E2} \approx 1.3 / 3.4 = 0.4 (mA)$$

$$V_{C2} \approx 12 - 0.4 \times 8 = 8.8 (V)$$

6.2 The Shunt-Series Feedback Amplifier

Example 8.4(Cont'd)

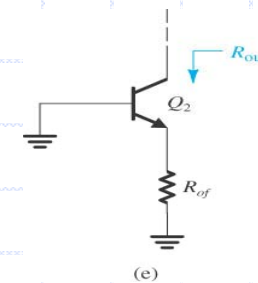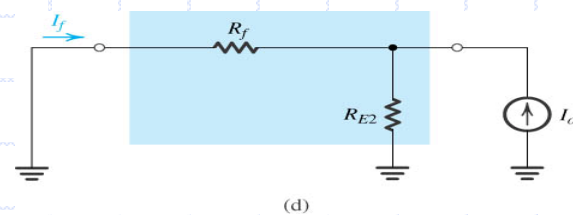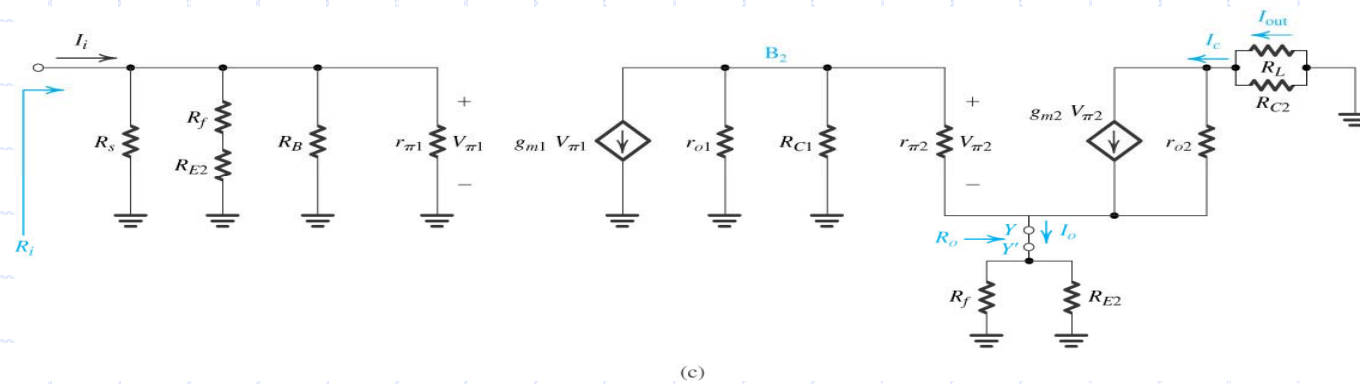

$$V_{\pi 1} = I_i [R_s \parallel (R_{E2} + R_f) \parallel R_B \parallel r_{\pi 1}]$$

$$V_{b2} = -g_{m1} V_{\pi 1} \{r_{o1} \parallel R_{C1} \parallel [r_{\pi 2} + (\beta + 1)(R_{E2} \parallel R_f)]\} \quad A = \frac{I_o}{I_i} \approx -201.45 (A / A)$$

$$I_o = \frac{V_{b2}}{r_{e2} + (R_{E2} \parallel R_f)}$$

$$\beta = \frac{I_f}{I_o} = -\frac{R_{E2}}{R_{E2} + R_f} = -0.254$$

6.2 The Shunt-Series Feedback Amplifier

◆ Example 8.4(Cont'd)

$$1 + A\beta = 52.1$$

$$R_i = R_s \parallel (R_{E2} + R_f) \parallel R_B \parallel r_{\pi 1}$$

$$= 1.535 \text{ (k}\Omega\text{)}$$

$$R_{if} = \frac{R_i}{1 + A\beta} = 29.5 \text{ (}\Omega\text{)}$$

$$R_{in} = \frac{1}{1/R_{if} - 1/R_s} = 29.5 \text{ (}\Omega\text{)}$$

$$R_o = (R_{E2} \parallel R_f) + r_{e2} + \frac{R_{C1} \parallel r_{o1}}{\beta + 1}$$

$$= 2.69 \text{ (k}\Omega\text{)}$$

$$R_{of} = R_o (1 + A\beta) = 140.1 \text{ (k}\Omega\text{)}$$

$$R_{out} = r_{o2} [1 + g_{m2} (r_{\pi 2} \parallel R_{of})]$$

$$= 18.1 \text{ (M}\Omega\text{)}$$


$$A_f = \frac{I_o}{I_s} = \frac{A}{1 + A\beta} = -3.87 \text{ (A / A)}$$

$$\frac{I_{out}}{I_{in}} \approx \frac{I_{out}}{I_s} = \frac{R_{C2}}{R_L + R_{C2}} \frac{I_c}{I_s} \approx \frac{R_{C2}}{R_L + R_{C2}} \frac{I_o}{I_s} = -3.44 \text{ (A / A)}$$

6.2 The Shunt-Series Feedback Amplifier

◆ Exercise


Q : Identify the type of feedback used.

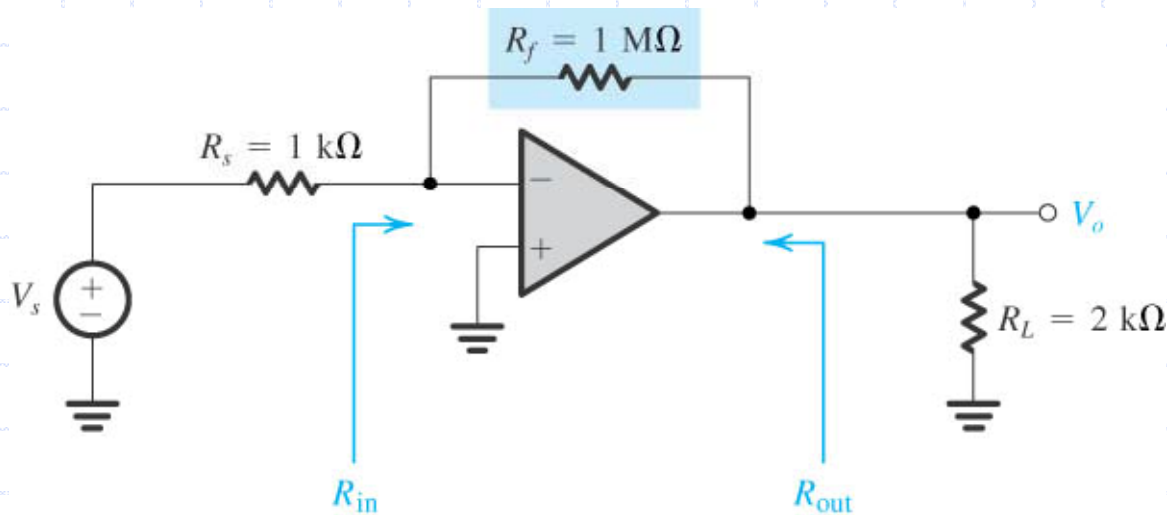

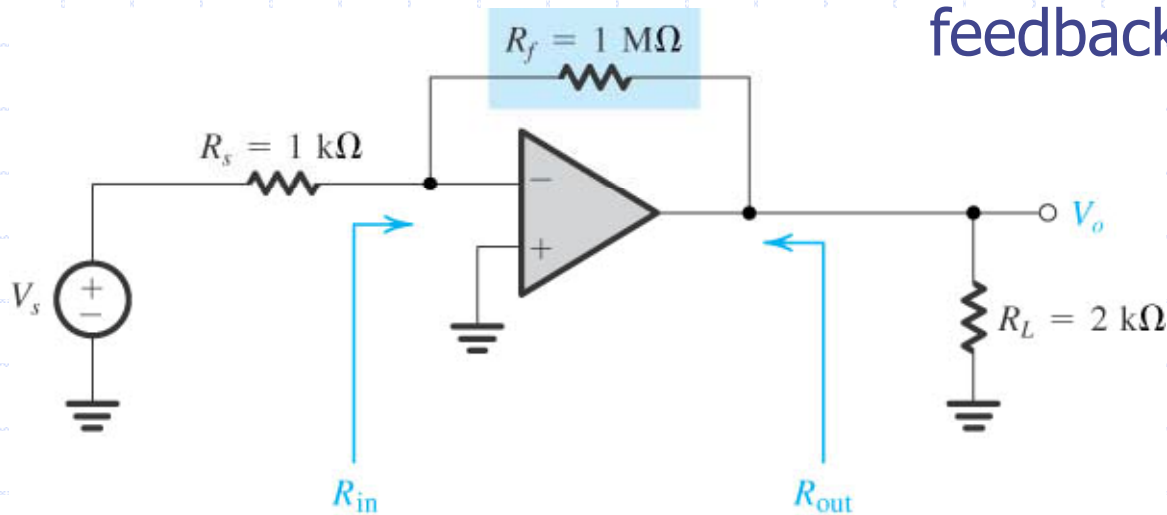6.2 The Shunt-Series Feedback Amplifier

◆ Exercise (Cont'd)


Voltage is sampled and current is mixed, so shunt-shunt feedback amplifier.



7. Determining The Loop Gain


Alternative Approaches

$L(s) = A(s)\beta(s) = \text{loop transmission}$

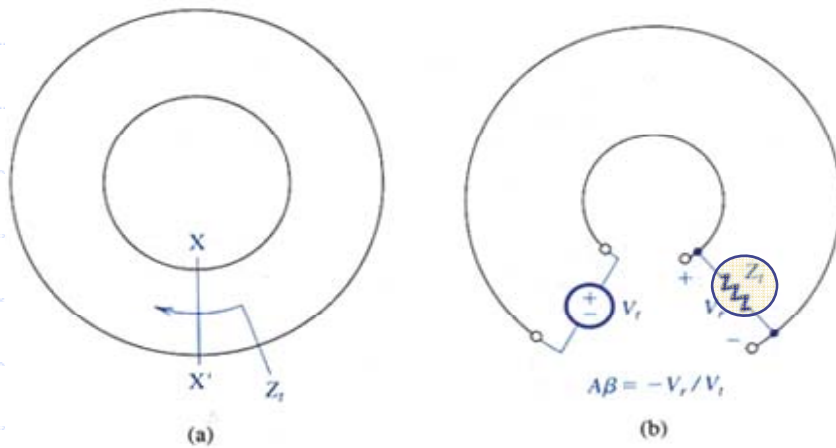

Approach 1.

$$A\beta = -\frac{V_r}{V_t}$$

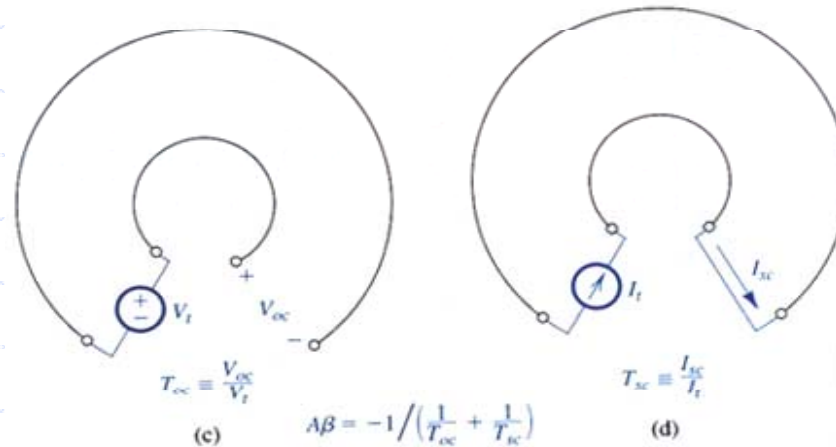

Approach 2.


$$A\beta = \frac{-1}{\frac{1}{T_{oc}} + \frac{1}{T_{sc}}}$$

(Rosenstark, 1986)

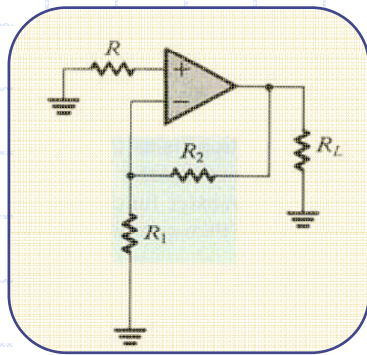
7. Determining The Loop Gain

◆ Example – Approach 1.


Q. Determine the loop gain of the following circuit.



(a)

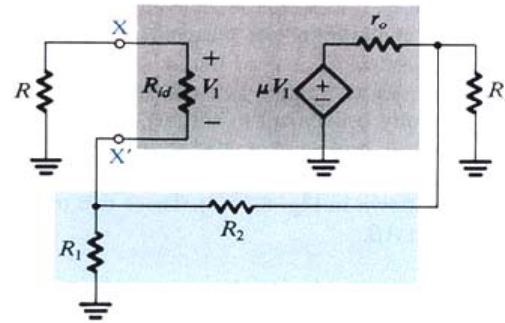

(b)

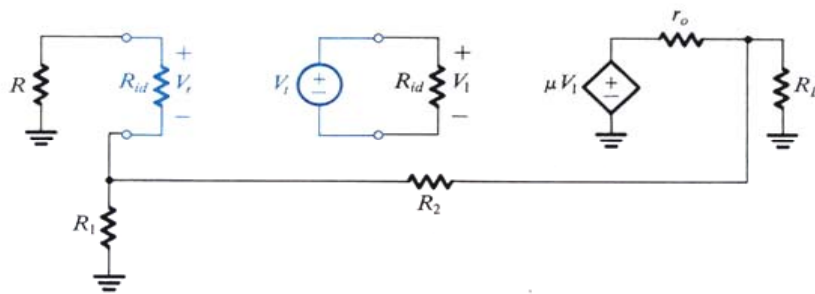

(c)

$$A\beta_1 = -\frac{R_{id}}{R_{id} + R} \cdot \mu$$

$$\cdot \frac{R_L \parallel [R_2 + R_1 \parallel (R_{id} + R)]}{r_o + R_L \parallel [R_2 + R_1 \parallel (R_{id} + R)]}$$


$$\cdot \frac{R_1 \parallel (R_{id} + R)}{R_2 + (R_1 \parallel (R_{id} + R))}$$

$$\approx -\frac{R_1}{R_1 + R_2} \cdot \mu$$

when $R_{id} \gg (R_1, R_2)$, $r_o \approx 0$

7. Determining The Loop Gain

◆ Example – Approach 2.

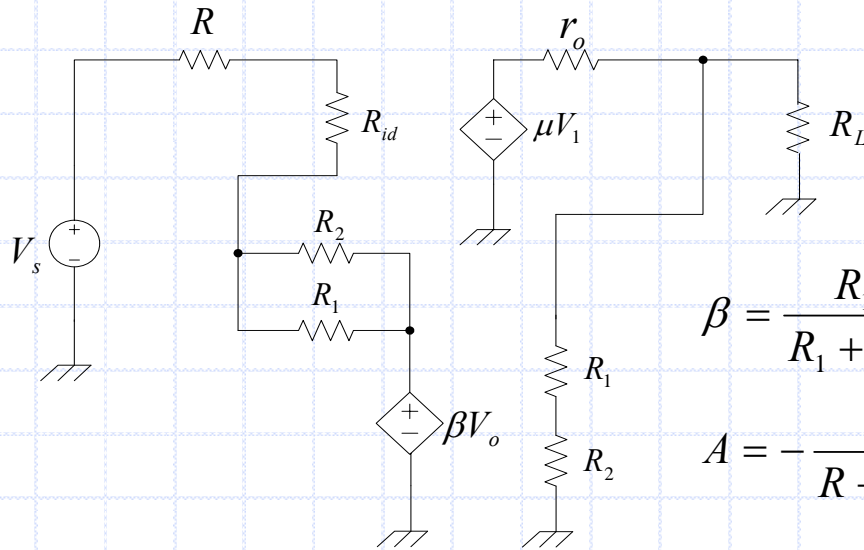

$$\beta = \frac{R_1}{R_1 + R_2}$$

$$A = -\frac{R_{id}}{R + R_{id} + (R_1 \parallel R_2)} \cdot \mu \cdot \frac{R_L \parallel (R_1 + R_2)}{r_o + R_L \parallel (R_1 + R_2)}$$

$$A\beta_2 = -\frac{R_{id}}{R + R_{id} + (R_1 \parallel R_2)} \cdot \mu \cdot \frac{R_L \parallel (R_1 + R_2)}{r_o + R_L \parallel (R_1 + R_2)} \cdot \frac{R_1}{R_1 + R_2}$$

$$\approx -\frac{\mu}{R_1 + R_2}$$

when $R_{id} \gg (R_1, R_2)$, $r_o \approx 0$

7. Determining The Loop Gain

◆ Comparison of the two results

$$A\beta_1 = \frac{R_{id}}{R_{id} + R} \cdot \mu \cdot \frac{R_L \parallel [R_2 + R_1 \parallel (R_{id} + R)]}{r_o + R_L \parallel (R_2 + R_1 \parallel (R_{id} + R))} \cdot \frac{R_L \parallel (R_{id} + R)}{R_2 + R_1 \parallel (R_{id} + R)}$$


$$A\beta_2 = -\frac{R_{id}}{R + R_{id} + (R_1 \parallel R_2)} \cdot \mu \cdot \frac{R_L \parallel (R_1 + R_2)}{r_o + R_L \parallel (R_1 + R_2)} \cdot \frac{R_1}{R_1 + R_2}$$

When $R_{id} \gg (R_1, R_2)$, $r_o \approx 0$, both values come to

$$A\beta_1 \cong A\beta_2 \cong -\frac{\mu}{R_1 + R_2}$$

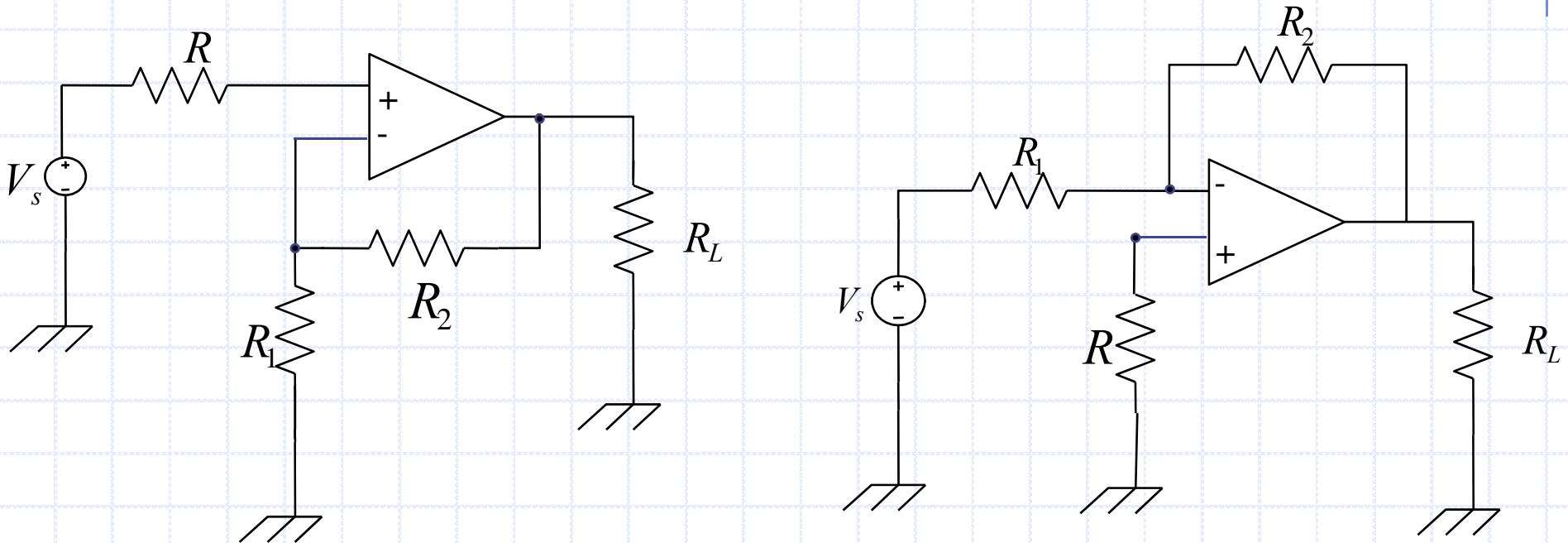
7. Determining The Loop Gain

◆ Loop Equivalent with Different Op-Amp Circuits




7. Determining The Loop Gain

Example – Approach 3. Shunt–Shunt FB

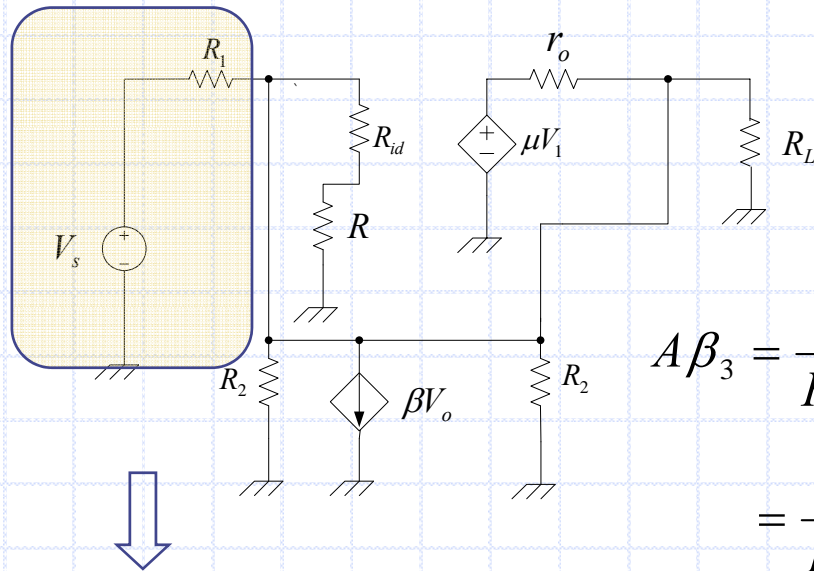

$$A\beta_3 = \frac{R_{id}}{R + R_{id}} \cdot \frac{1}{R_1 \parallel R_2 \parallel (R_{id} + R)} \cdot \mu \cdot \frac{R_L \parallel R_2}{r_o + (R_L + R_2)} \cdot \frac{1}{R_2}$$
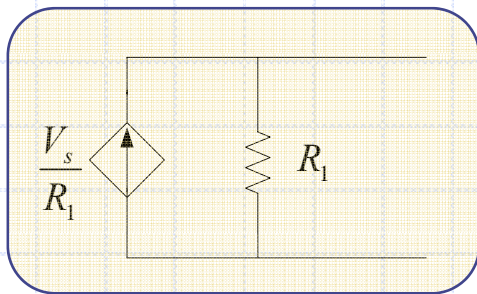
$$= \frac{R_{id}}{R + R_{id}} \cdot \frac{R_1 \parallel R_2}{R_2} \cdot \mu = \frac{R_{id}}{R + R_{id}} \cdot \frac{R_1}{R_1 + R_2} \cdot \mu$$



As $r_o \approx 0, R_{id} \approx \infty,$


$$A\beta_3 \approx -\frac{R_1}{R_1 + R_2} \cdot \mu$$

8. Stability Problem

- ◆ Feedback systems do not always have a tendency to stabilize.
- ◆ Under some conditions, the system will diverge and oscillate.

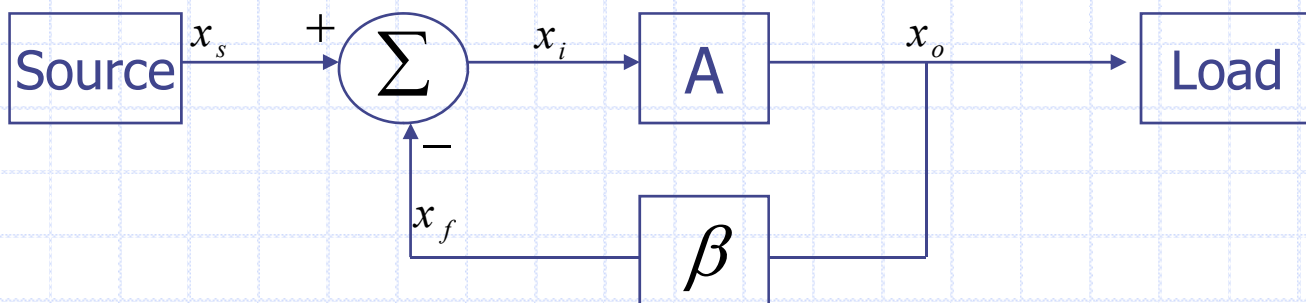8. Stability Problem

◆ In an iterative process inside the loop...



x_s	1		
x_i	1	$1 - A\beta$	$1 - A\beta(1 - A\beta)$
x_o	A	$A(1 - A\beta)$	$A(1 - A\beta(1 - A\beta))$
x_f	$A\beta$	$A\beta(1 - A\beta)$	$A\beta(1 - A\beta(1 - A\beta))$

$$\begin{aligned}
 x_o(\infty) &= A[1 - A\beta(1 - A\beta(1 - A\beta \dots)) \\
 &= A[1 - A\beta + (A\beta)^2 - (A\beta)^3 \dots] \\
 &= A \cdot \frac{1 - (-A\beta)^\infty}{1 + A\beta}
 \end{aligned}$$

8. Stability Problem


◆ Conditions for stability under negative FB.

- The system is stable IFF $x_0(\infty)$ converges.

All events occur simultaneously => stable

what if there is a delay in the loop => unstable
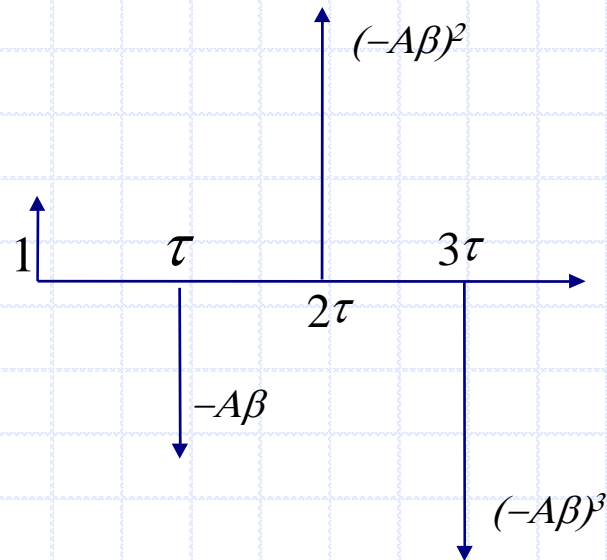
$$A(j\omega) = \frac{A(j\omega)}{1 + A(j\omega)\beta(j\omega)}$$



[unstable]

$$L(j\omega) = A(j\omega)\beta(j\omega) = |A(j\omega)\beta(j\omega)| e^{j\Phi(\omega)}$$

if $A(j\omega)\beta(j\omega) \leq -1$ => oscillation

when $\angle A(j\omega)\beta(j\omega) = -180^\circ$,
 $|A(j\omega)\beta(j\omega)| > 1$ => oscillation

Magnitude of oscillation will grow until some nonlinearity eventually makes $|A\beta|=1$.

8. Stability Problem

◆ Problem 8.63(p.869)

Q. Find the value of k above which the closed-loop amplifier becomes unstable.

Given \longrightarrow $A(s) = \frac{1000}{1 + \frac{s}{10^4}}$ $\beta(s) = \frac{k}{(1 + \frac{s}{10^4})^2}$

8. Stability Problem

◆ Problem 8.63(p.869) (Cont'd)

$$\text{Ang}(A(s)\beta(s)) = -180^\circ = -3 \tan^{-1} \frac{\omega_{180}}{10^4} \implies \omega_{180} = \sqrt{3} \times 10^4 (\text{rad} / \text{s})$$

If $|A\beta|_{\omega=\omega_{180}} < 1$ the system is stable.


$$\implies \frac{10^3}{\sqrt{1+(\sqrt{3})^2}} \cdot \frac{k}{1+(\sqrt{3})^2} < 1$$

$$\implies k < 0.008$$

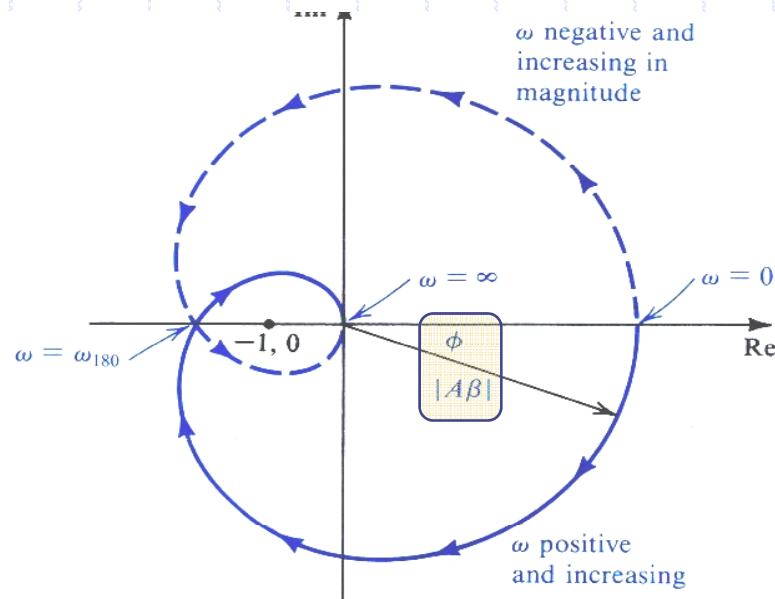8. Stability Problem

◆ Nyquist plot example

$$A(s)\beta(s) = \frac{A_o}{(1 + s / \omega_1)(1 + s / \omega_2)(1 + s / \omega_3)}$$



Because the magnitude of the loop gain is an even function and the phase is an odd function, the nyquist plot for negative frequency is a mirror image of nyquist plot of the positive frequency.

If the nyquist plot intersects the real axis on the left of $(-1, 0)$, then the system is unstable.
-> The plot encircles the point $(-1, 0)$, thus the system is unstable.

9. Effect of Feedback on The Amplifier Poles

◆ Stability and pole location

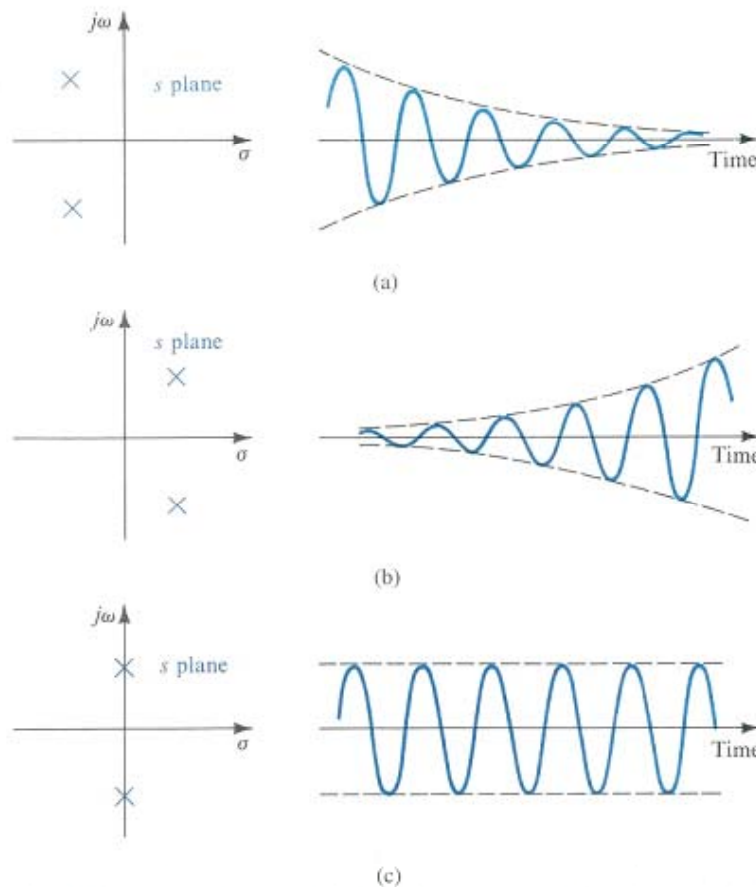


Fig. 8.29 Relationship between pole location and transient response.

$$v(t) = e^{\sigma t} (e^{j\omega_n t} + e^{-j\omega_n t})$$

$$= 2e^{\sigma t} \cos \omega_n t$$

$$\begin{cases} \sigma \geq 0 : \text{unstable} \\ \sigma < 0 : \text{stable} \end{cases}$$

Poles of FB system

$$V_o(s) = H(s)V_i(s)$$



$$H(s) = \frac{A(s)}{1 + A(s)\beta(s)}$$

Characteristic equation

$$1 + A(s)\beta(s) = 0$$

9. Effect of Feedback on The Amplifier Poles

◆ Amplifier with one pole

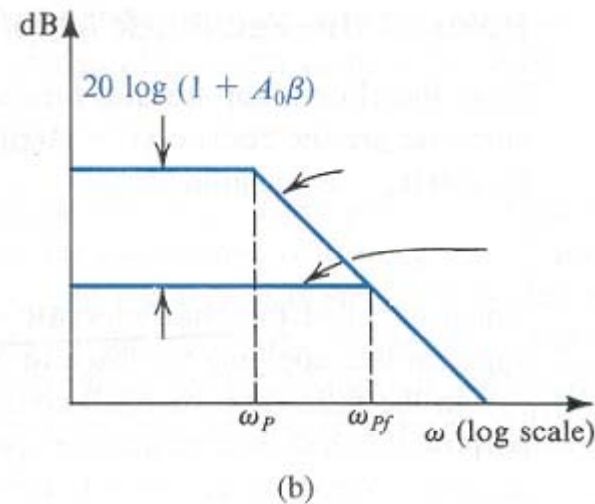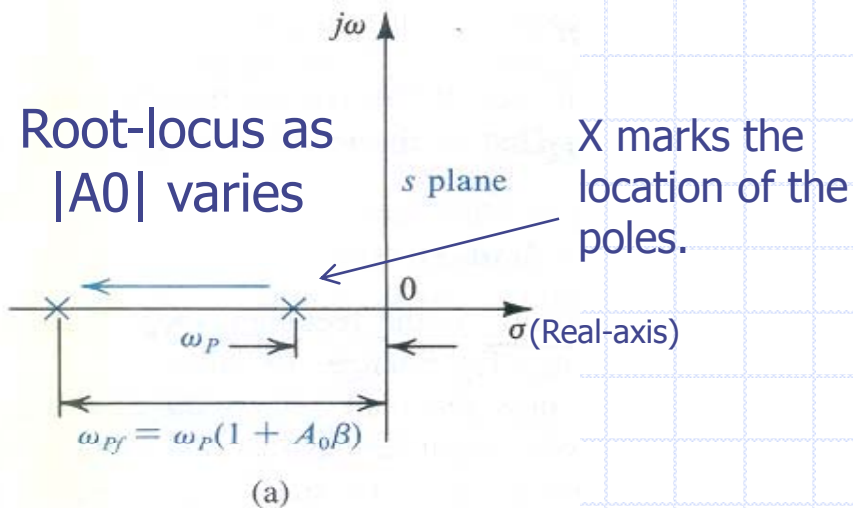

$$A(s) = \frac{A_0}{1 + s/\omega_p}$$

Characteristic Eq.



$$1 + A(s) \cdot \beta = 1 + \frac{\beta A_0}{1 + s/\omega_p} = 0$$

$$\beta A_0 + 1 + s/\omega_p = 0$$

Solve this to find where the pole is.

9. Effect of Feedback on The Amplifier Poles

◆ Amplifier with two poles

$$\begin{aligned}
 A_f(s) &= \frac{A(s)}{1 + A(s) \cdot \beta(s)} \\
 &= \frac{A_0 / (1 + s/\omega_{p1})(1 + s/\omega_{p2})}{1 + \beta A_0 / (1 + s/\omega_{p1})(1 + s/\omega_{p2})} \\
 &= \frac{A_0 \omega_{p1} \omega_{p2}}{s^2 + s(\omega_{p1} + \omega_{p2}) + (1 + A_0 \beta) \omega_{p1} \omega_{p2}}
 \end{aligned}$$

$$|A_f(j\omega)| = \frac{A_0 \omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + \left(\frac{\omega \omega_0}{Q}\right)^2}}$$

$$\frac{A_0 \omega_0^2}{s^2 + s \cdot \frac{\omega_0}{Q} + \omega_0^2}$$

$$s^2 + s \frac{\omega_0}{Q} + \omega_0^2 = 0$$


ω_0 : pole frequency , Q : pole Q factor

$$\omega_0 = \sqrt{(1 + A_0 \beta) \omega_{p1} \omega_{p2}} \quad Q = \frac{\sqrt{(1 + A_0 \beta) \omega_{p1} \omega_{p2}}}{\omega_{p1} + \omega_{p2}}$$

■ Characteristic equation

- ◆ **Peaking starts** to show in frequency domain at $Q > 0.707$.
- ◆ **Ringing starts** to show in time domain at $Q > 0.5$.

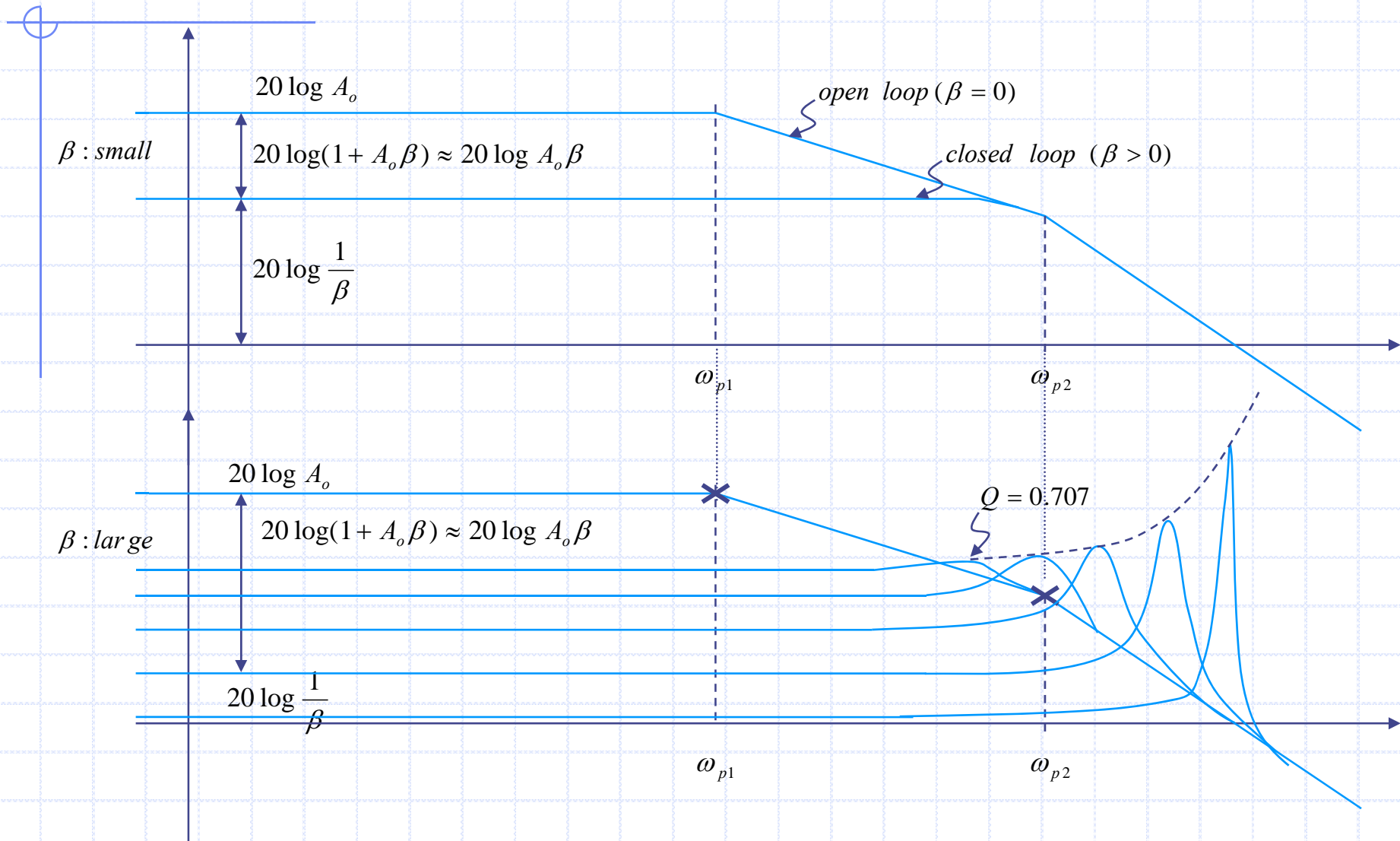9. Effect of Feedback on The Amplifier Poles



9. Effect of Feedback on The Amplifier Poles


◆ Amplifier with more poles or zeros

- ◆ Too complex for hand analysis
- ◆ Use CAD tool + Intuition

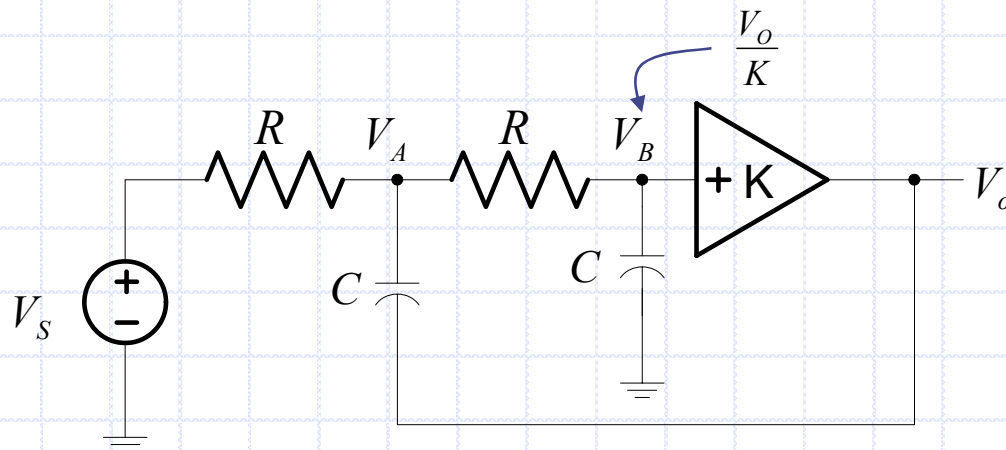9. Effect of Feedback on The Amplifier Poles

◆ Example 8.5

Q: find k for maximally flat frequency response.



KCL @ V_A ;

$$\frac{V_A - V_S}{R} + sC(V_A - V_O) + \frac{V_A - V_B}{R} = 0$$

KCL @ V_B ;

$$V_B = \frac{V_O}{K} = V_A \cdot \frac{\frac{1}{sC}}{R + \frac{1}{sC}} + sC \Rightarrow V_A = \frac{V_O}{K} \cdot (1 + sCR)$$


$$\left(\frac{1}{R} + sC + \frac{1}{R}\right)V_A - \frac{V_S}{R} - sCV_O - \frac{V_O}{R \cdot K} = 0$$

$$\left(\frac{2}{R} + sC\right) \cdot \frac{V_O}{K} \cdot (1 + sCR) - sCV_O - \frac{V_O}{R \cdot K} = \frac{V_S}{R}$$

$$\left[\left(\frac{2}{R} + sC\right) \cdot \frac{1}{K} \cdot (1 + sCR) - sC - \frac{1}{R \cdot K}\right] V_O = \frac{V_S}{R}$$

9. Effect of Feedback on The Amplifier Poles

◆ Example 8.5 (Cont'd)

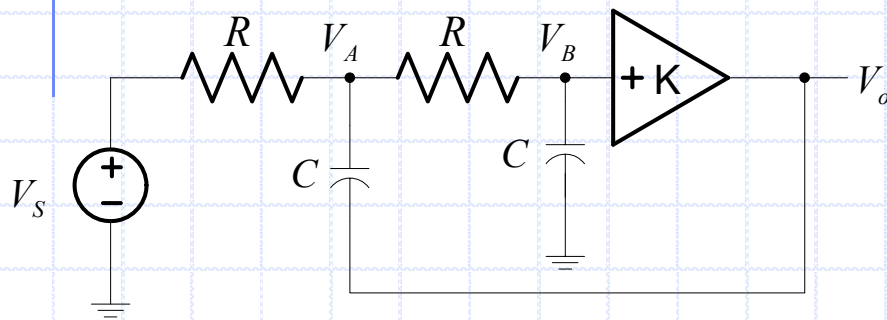

$$\begin{aligned} \frac{V_o}{V_s} &= \frac{\frac{1}{R}}{\left(\frac{2}{R} + sC\right) \cdot \frac{1}{K} \cdot (1 + sCR) - sC - \frac{1}{R \cdot K}} \\ &= \frac{\frac{1}{R}}{\frac{RC}{K} \cdot C \cdot s^2 + \left[\left(\frac{1}{K} \cdot \frac{2}{R} \cdot C + \frac{C}{K}\right) - C\right] s + \frac{1}{K} \cdot \frac{2}{R} - \frac{1}{R \cdot K}} \\ &= \frac{\frac{1}{R}}{\frac{RC^2}{K} \cdot s^2 + \left(\frac{3}{K} - 1\right) C \cdot s + \frac{1}{KR}} \\ &= \frac{K}{R^2 C^2} \cdot \frac{1}{s^2 + \frac{1}{RC} \cdot (3 - K) \cdot s + \frac{1}{R^2 C^2}} \end{aligned}$$

9. Effect of Feedback on The Amplifier Poles

◆ Example 8.5 (Cont'd)

$$\frac{V_o}{V_s} = \frac{K \cdot \omega_o^2}{s^2 + \frac{\omega_o}{Q} \cdot s + \omega_o^2} \quad Q = \frac{1}{3-K}, \quad \omega_o^2 = \frac{1}{R^2 C^2}$$

$$Q = \frac{1}{\sqrt{2}} \text{ 일 때 maximally flat - no peaking !!}$$


$$\therefore \frac{1}{3-K} = \frac{1}{\sqrt{2}}$$

$$3-K = \sqrt{2}$$

$$K = 3 - \sqrt{2} = 1.586$$

10. Stability Study Using Bode Plots

◆ Bode Plot

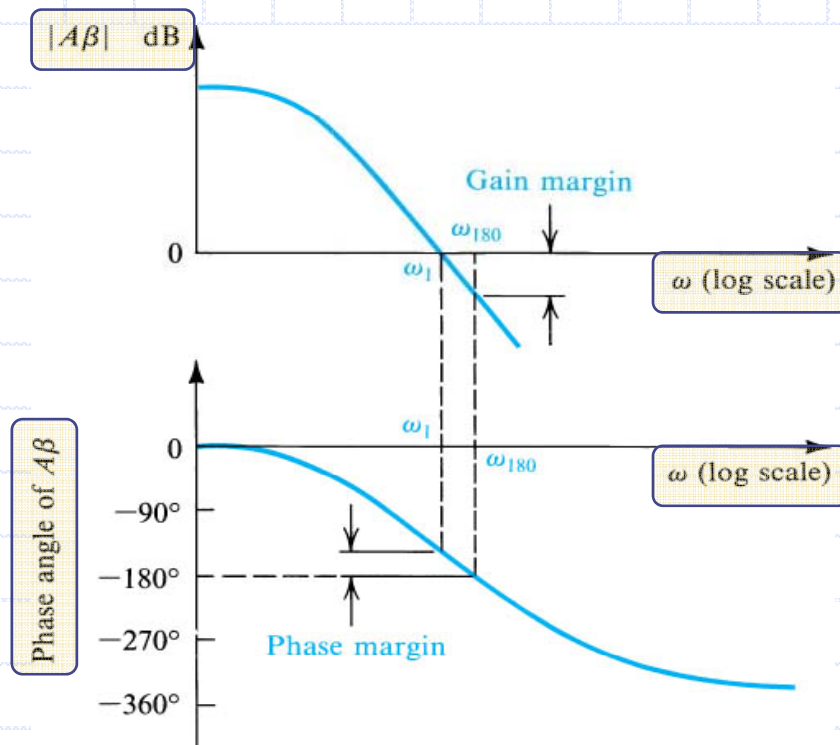


Every pole contributes to magnitude change of 20dB decrease per decade beyond its location.

Every pole contributes to phase change of 90° decrease through two consecutive decades where it is nested at the center.

10. Stability Study Using Bode Plots

◆ Gain margin and phase margin

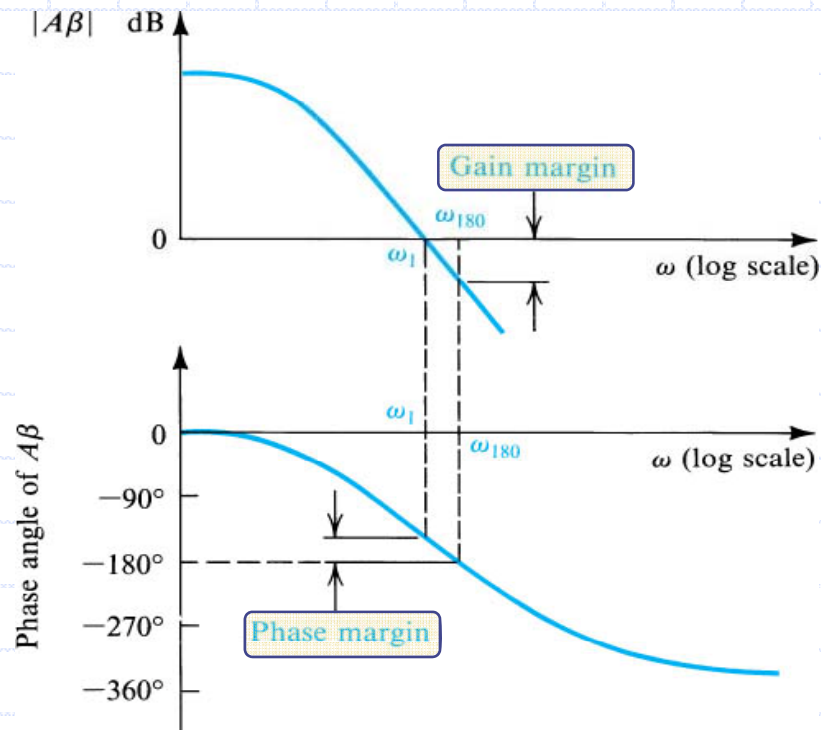

Gain margin is the difference between the value of $|A\beta|$ at ω_{180} and unity(0dB).

Phase margin is the difference between the phase angle from the point where gain crosses unity(0dB) to 180° .

10. Stability Study Using Bode Plots

◆ Conditions for Stability

- Stable = Phase margin is greater than 0.
- However, system with phase margin close to 0 suffers from severe **peaking** in its **closed loop-gain**. (freq. domain)
- Typically, system with phase margin above 45° is well accepted to be stable.

10. Stability Study Using Bode Plots

◆ Phase margin of 45°

$$\text{loopgain} = A(j\omega_1)\beta = 1 \times e^{-j\theta} \quad \leftarrow \text{Loop gain is unity at } \omega_1.$$

(Where $\theta = 180^\circ - \text{phase margin}$)

$$A_f(j\omega_1) = \frac{A(j\omega_1)}{1 + A(j\omega_1)\beta} \rightarrow |A_f(j\omega_1)| = \frac{\frac{1}{\beta}}{|1 + e^{-j\theta}|}$$

$$= \frac{\frac{1}{\beta} e^{-j\theta}}{1 + e^{-j\theta}}$$

If the phase margin is 45°
 $\rightarrow \theta = 135^\circ$

$$|A_f(j\omega_1)| = 1.3 \frac{1}{\beta}$$

Closed loop gain peaks by 30% at ω_1 from the low frequency gain of $1/\beta$.
 Peaking would reach ∞ as phase margin approaches 0°.

10. Stability Study Using Bode Plots

◆ Alternative approach for Investigating Stability


- It would be very tiresome to find the best value for β by numerical iteration.
- There is an alternative method to graphically estimate the value of β by using,

$$20\log|A(j\omega)| - 20\log\frac{1}{\beta} = 20\log|A\beta| = \text{loop gain in dB}$$

→
See next

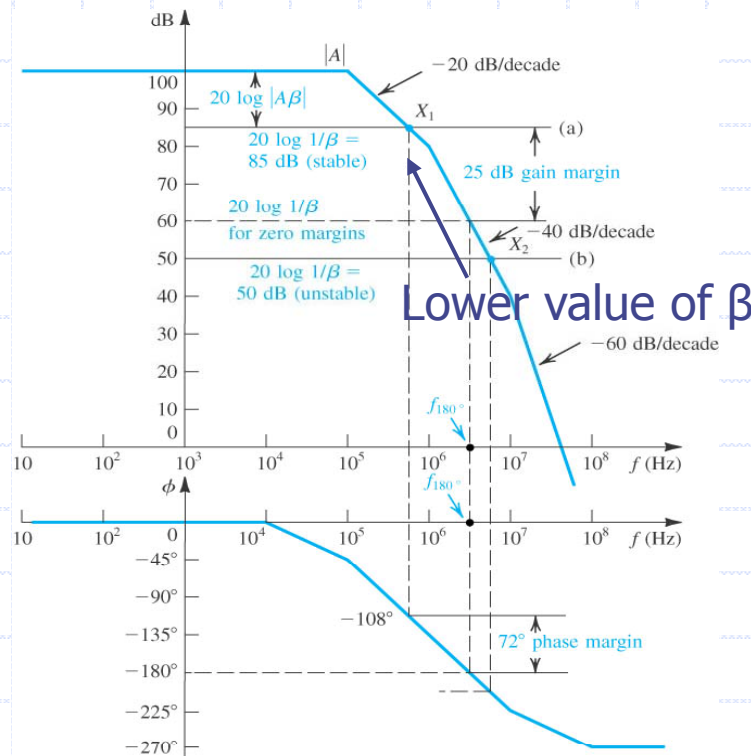10. Stability Study Using Bode Plots

◆ Q: System has poles at 10^5 Hz, 10^6 Hz, and 10^7 Hz. Find β that yields phase margin of 72° ?




1. Draw $20 \log |A(j\omega)|$
2. Draw the phase graph
3. Draw a line for $20 \log 1/\beta$ so as it intersects $20 \log |A(j\omega)|$ at the frequency that gives the needed phase margin.

The area enclosed by $20 \log |A(j\omega)|$ and $20 \log 1/\beta$ redrawn with $20 \log 1/\beta$ line as f-axis becomes the graph of the loop gain ($20 \log |A(j\omega)\beta|$).

10. Stability Study Using Bode Plots

◆ Q: (Cont'd)

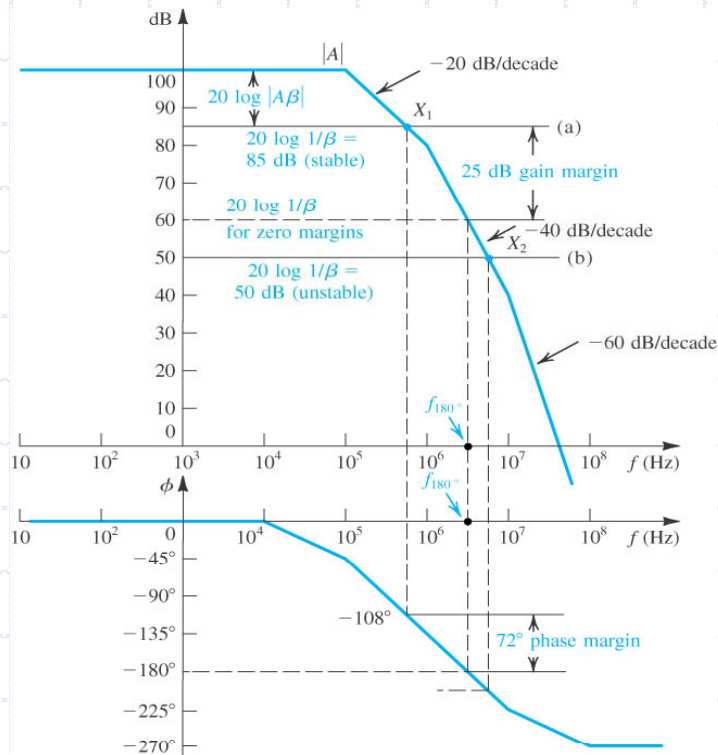

$$A = \frac{10^5}{(1 + j \frac{f}{10^5})(1 + j \frac{f}{10^6})(1 + j \frac{f}{10^7})}$$

$$\phi = -[\tan^{-1}(\frac{f}{10^5}) + \tan^{-1}(\frac{f}{10^6}) + \tan^{-1}(\frac{f}{10^7})]$$

$$f_{180} \doteq 3.2 \times 10^6 \text{ Hz}$$


$$(f_{180} \doteq 3.34 \times 10^6 \text{ Hz with more iteration})$$

$$f_{108} \doteq 5.6 \times 10^5 \text{ Hz} \rightarrow |A(j\omega_{108})| = 85 \text{ dB}$$

$$\beta = 5.623 \times 10^{-5}$$

10. Stability Study Using Bode Plots

◆ Rule of thumb for stability

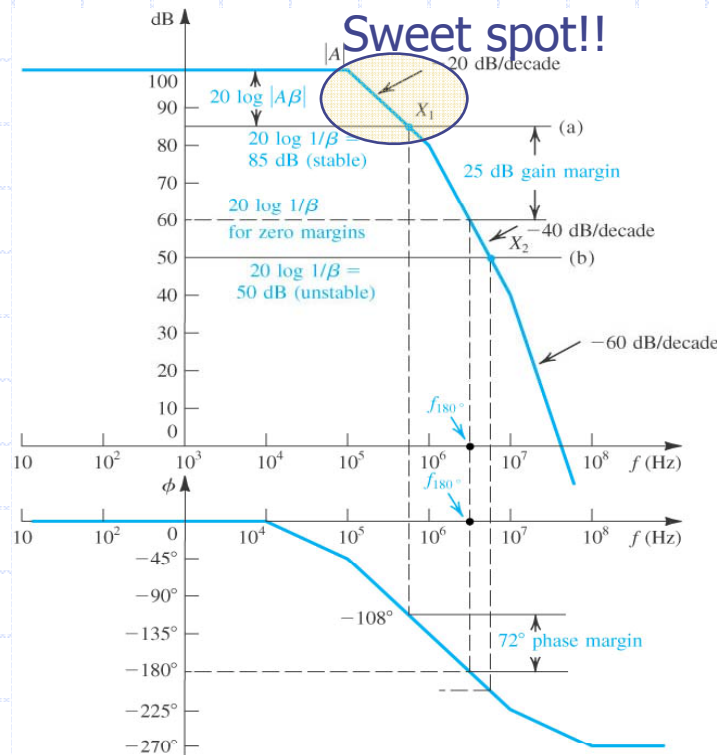

To guarantee stability,
the $20 \log 1/\beta$ should intersect the $20 \log |A|$ on its -20 dB/dec segment.
(then the phase margin $> 45^\circ$)


More generally, if β is a function of frequency...

The difference of slopes (= rate of closure) at the intersection of $20 \log 1/\beta(j\omega)$ and $20 \log |A(j\omega)|$ should not exceed 20 dB/dec .

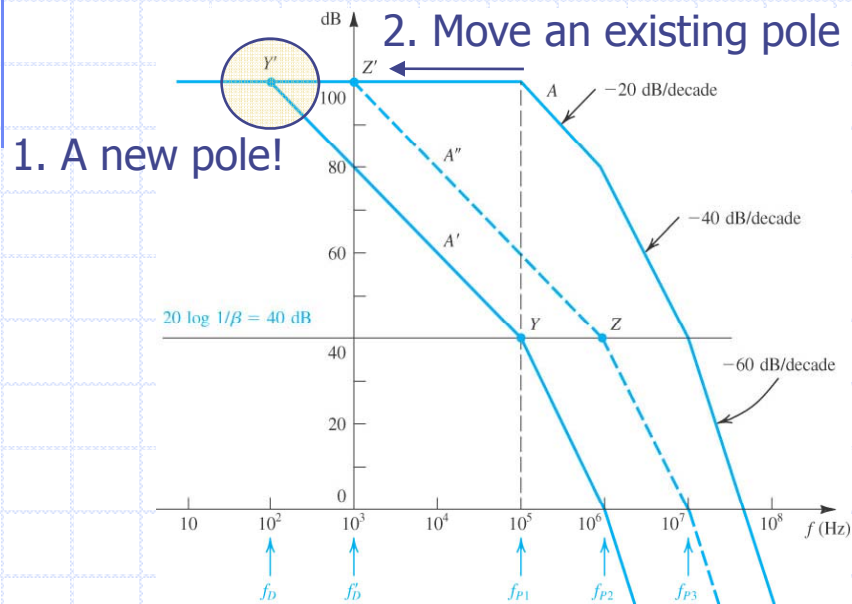11. Frequency Compensation

◆ Theory

- A system can be made stable by introducing a new pole or moving the location of its existing pole.



1. Place a new pole so as to guarantee that the slope difference of $20 \log |A(j\omega)|$ and $20 \log 1/\beta$ does not exceed 20 dB/dec.

OR

2. Move an existing pole the same way as 1. (preferred)


↓

STABLE

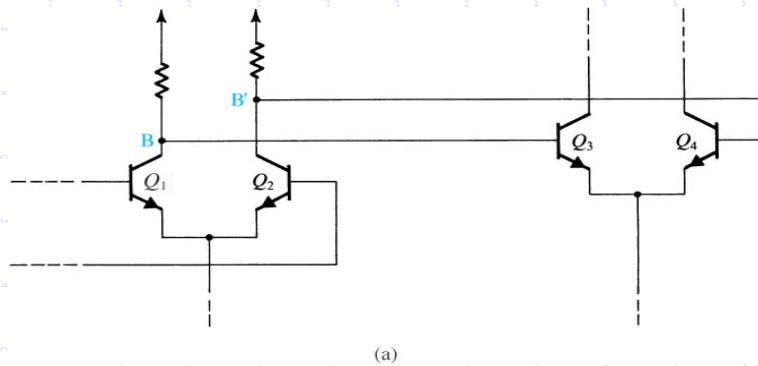11. Frequency Compensation



◆ Implementation

- Assume that the first pole f_{p1} is introduced at the interface between the two stages.



(a)'s small signal equivalent circuit can be simplified to the circuit shown in (b).

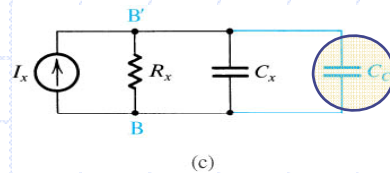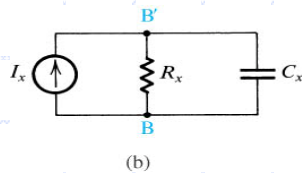By adding C_c we are capable of moving the location of f_{p1} to a lower frequency.



$$f_{P1} = \frac{1}{2\pi C_x R_x}$$


$$f_D' = \frac{1}{2\pi (C_x + C_c) R_x}$$

However, the required value of C_c is usually large and C_c has an secondary effect on poles other than f_{p1} .

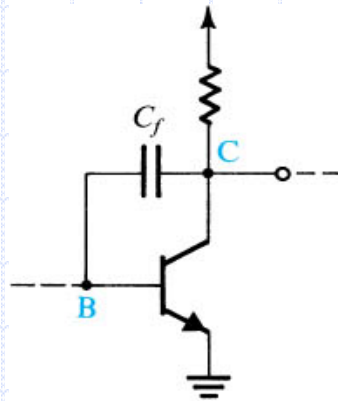
11. Frequency Compensation

◆ Miller compensation and pole splitting

- A miller effect is used in ICs to minimize $C_c(C_f)$.



(a)

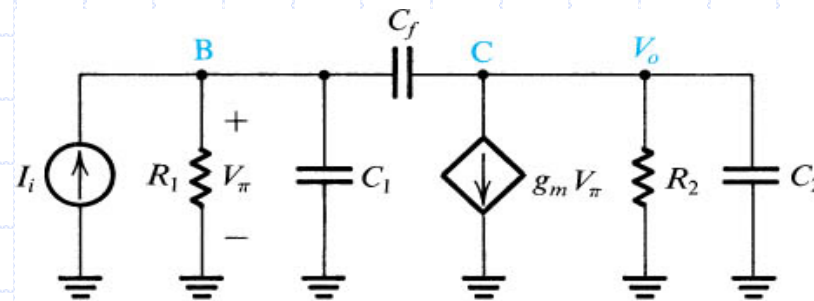

(b)

- Assume that C_1 includes the Miller component due to C_μ , C_2 includes the input capacitance of the subsequent stage.

11. Frequency Compensation

◆ Miller comp. & pole splitting (Cont'd)

- Pole locations **without** C_f

$$f_{P1} = \frac{1}{2\pi C_1 R_1}, \quad f_{P2} = \frac{1}{2\pi C_2 R_2}$$

- Pole locations **with** C_f

$$\frac{V_o}{I_i} = \frac{(sC_f - g_m)R_1R_2}{1 + s[C_1R_1 + C_2R_2 + C_f(g_mR_1R_2 + R_1 + R_2)] + s^2[C_1C_2 + C_f(C_1 + C_2)]R_1R_2}$$

$$D(s) = \left(1 + \frac{s}{\omega_{P1}'}\right)\left(1 + \frac{s}{\omega_{P2}'}\right) = 1 + s\left(\frac{1}{\omega_{P1}'} + \frac{1}{\omega_{P2}'}\right) + \frac{s^2}{\omega_{P1}'\omega_{P2}'}$$

$$\cong 1 + \frac{s}{\omega_{P1}'} + \frac{s^2}{\omega_{P1}'\omega_{P2}'} \quad (\omega_{P1}' \ll \omega_{P2}')$$

The zero is usually at a much higher frequency, so we will neglect its effect.

$$\omega_{P1}' = \frac{1}{C_1R_1 + C_2R_2 + C_f(g_mR_1R_2 + R_1 + R_2)} \cong \frac{1}{g_mR_2C_fR_1} \quad \omega_{P2}' \cong \frac{g_mC_f}{C_1 + C_2 + C_f(C_1 + C_2)}$$

11. Frequency Compensation

◆ Miller comp.& pole splitting(Cont'd)

$$\omega_{P1}' = \frac{1}{C_1 R_1 + C_2 R_2 + C_f (g_m R_1 R_2 + R_1 + R_2)} \cong \frac{1}{\boxed{g_m R_2 C_f} R_1} \quad \omega_{P2}' \cong \frac{g_m C_f}{C_1 + C_2 + C_f (C_1 + C_2)}$$

Miller effect

As $C_f \uparrow$, $\omega'_{p1} \downarrow$ and $\omega'_{p2} \uparrow$: Pole Splitting


This method not only reduces the size of the needed compensation capacitance with miller effect, but also sends the second pole to a higher frequency.
-> Wider bandwidth.

Two goods in one package!!

11. Frequency Compensation

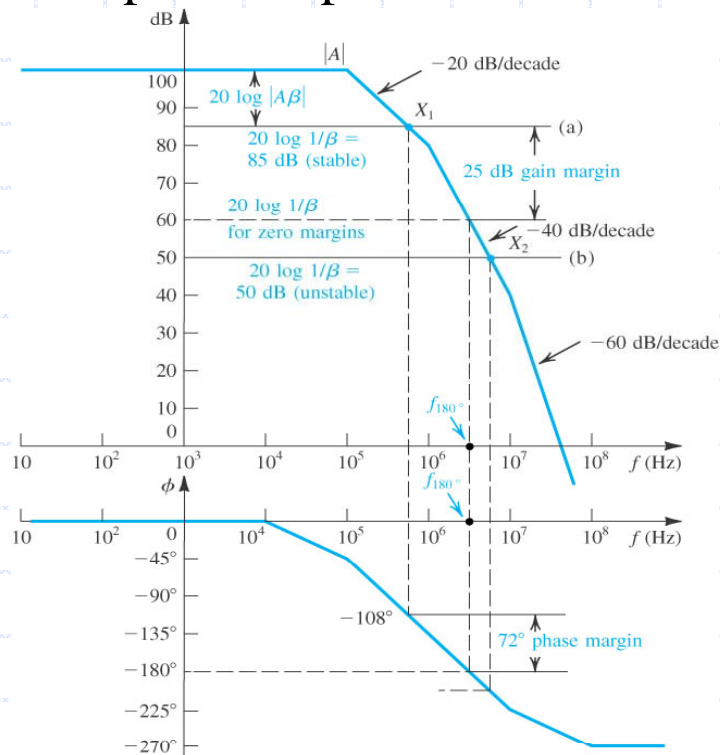
Example 8.6

Q : Find the value of C_f needed to make the amplifier with following open - loop characteri stic stable for $\beta \leq 1$.



(Solve for two cases :

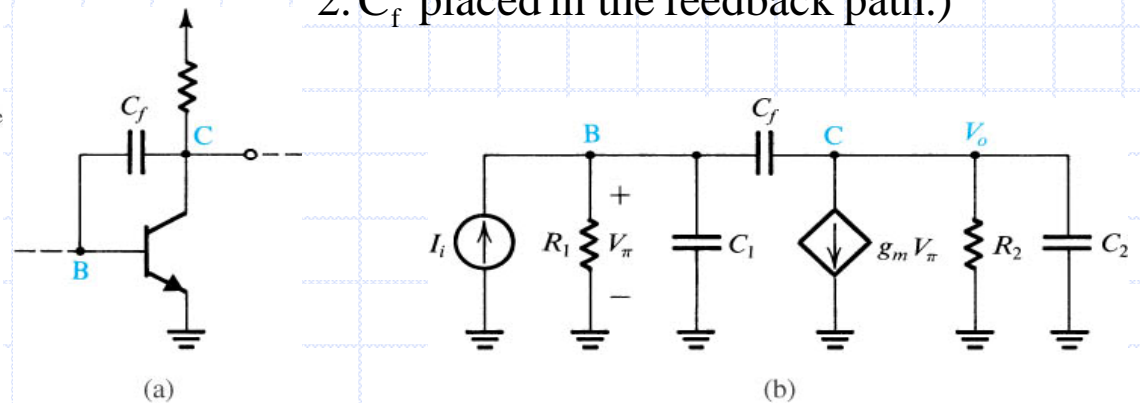
1. C_f placed between node B and ground.
2. C_f placed in the feedback path.)



Given $C_1 = 100\text{pF}$, $C_2 = 5\text{pF}$, and $g_m = 40\text{mA/V}$.

11. Frequency Compensation

◆ Example 8.6(Cont'd) – case 1.

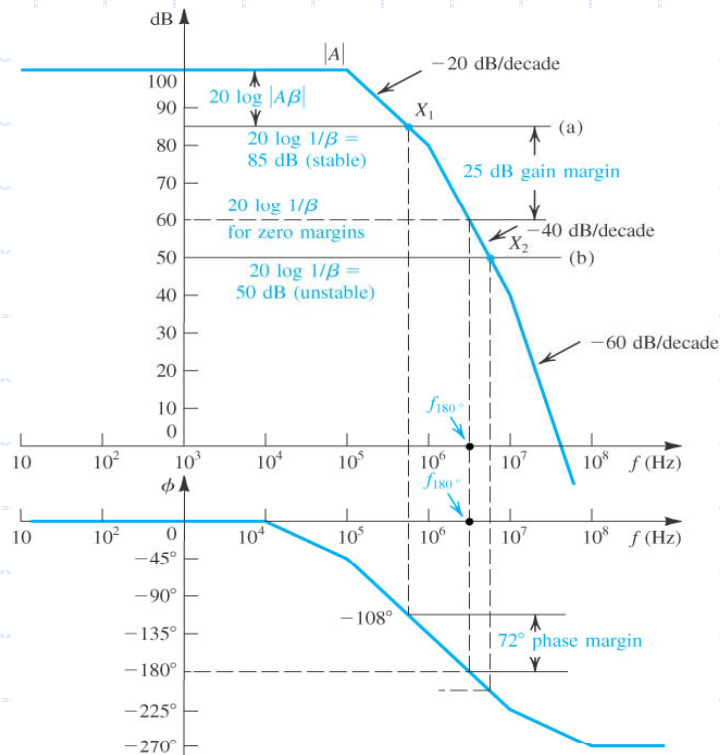

$$f_p = \frac{1}{2\pi C_1 R_1} \implies R_1 = \frac{1}{2\pi C_1 f_{p1}} = \frac{10^5}{2\pi} (\Omega)$$


$$R_2 = \frac{1}{2\pi C_2 f_{p2}} = \frac{10^5}{\pi} (\Omega)$$

C_f moves f_{p1} . To make the amplifier stable, the first pole must be moved so that the $20 \log |A(s)|$ intersects 0dB at $f_{p2}(=1\text{MHz})$.

$$f_{p1}' = \boxed{10\text{Hz}} = \frac{1}{2\pi(C_1 + C_f)R_1} \implies \boxed{C_f \approx 1\mu\text{F}}$$

11. Frequency Compensation

◆ Example 8.6(Cont'd) – case 2.

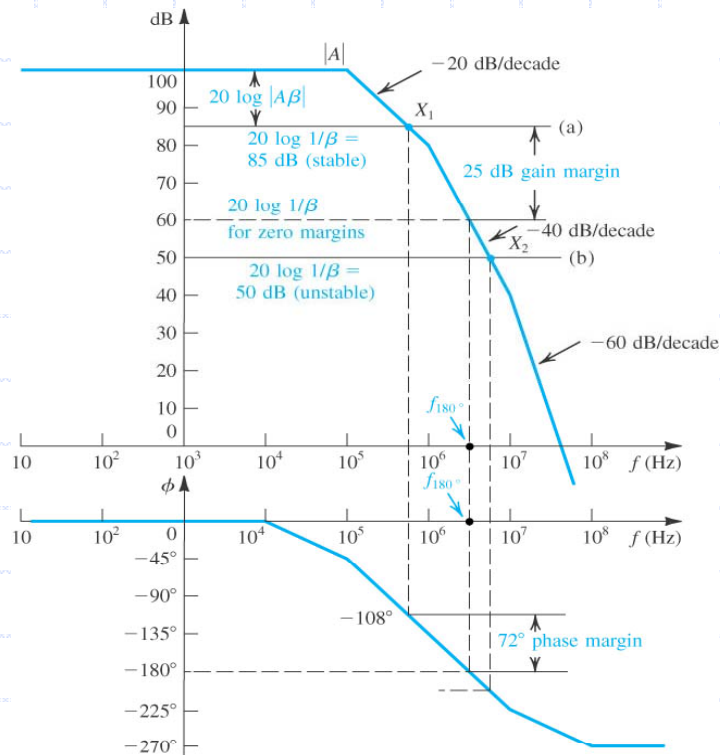

$$f_{P1}' \cong \frac{1}{2\pi g_m R_2 C_f R_1}$$

$$f_{P2}' \cong \frac{g_m C_f}{2\pi(C_1 + C_2 + C_f(C_1 + C_2))}$$

Assume $C_f \gg C_2$. Then,

$$f_{P2}' \cong \frac{g_m}{2\pi(C_1 + C_2)} = 60.6 \text{ MHz}$$

f_{P2}' is higher than f_{P3} , so the second pole of the system will be f_{P3} (=10MHz). Thus,

$$f_{P1}' \cong \boxed{100 \text{ Hz}} = \frac{1}{2\pi g_m R_2 C_f R_1} \implies \boxed{C_f = 78.5 \text{ pF}}$$



Smaller C_f & higher f_{P1}'