

Ch 9. Sequential Logic Technologies

Overview


- Basic Sequential Logic Components
- FSM Design with Counters
- FSM Design with Programmable Logic
- FSM Design with More Sophisticated Programmable Logic
- Case Study: Traffic Light Controller

Sequential logic implementation

- Implementation
 - ❑ discrete logic gates and flip-flops
 - ❑ ROMs or PALs/PLAs
 - ❑ CPLDs or FPGAs
- Design procedure
 - ❑ state diagram
 - ❑ state transition table
 - ❑ state assignment
 - ❑ next state and output functions

Median filter FSM

 - Remove single 0s between two 1s (output = PS3)



I	PS1	PS2	PS3	NS1	NS2	NS3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	X	X	X
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	0
1	1	0	1	X	X	X
1	1	1	0	1	1	1
1	1	1	1	1	1	1

Median filter FSM (cont'd)

- Realized using the standard procedure and individual FFs and gates

I	PS1	PS2	PS3	NS1	NS2	NS3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	X	X	X
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	0
1	1	0	1	X	X	X
1	1	1	0	1	1	1
1	1	1	1	1	1	1

NS1 = Reset' (I)



NS2 = Reset' (PS1 + PS2 I)

NS3 = Reset' PS2

O = PS3


Median filter FSM (cont'd)

  - But it looks like a shift register if you look at it right



Median filter FSM (cont'd)

 
- An alternate implementation with S/R FFs



- The set input (S) does the median filter function by making the next state 111 whenever the input is 1 and PS2 is 1 (1 input to state x1x)


Implementation using PALs

 - Programmable logic building block for sequential logic
 - macro-cell: FF + logic
 - D-FF
 - Two-level logic capability like PAL (e.g., 8 product terms)





Using a Shift Register

- 4-bit string (0110, 1010) recognizer

 

Using a Shift Register

 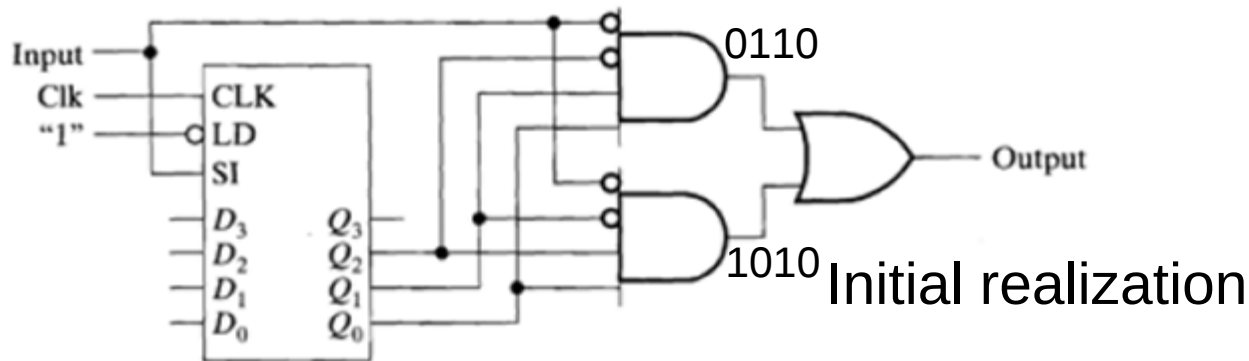


FSM Design with Counters

- Synchronous counters: CLR, LD, CNT

- Four kinds of transition for each state:

 - ❑ To State 0 (CLR)
- ❑ To next state in sequence (CNT)
- ❑ To arbitrary next state (LD)
- ❑ Loop in current state



- Careful state assignment is needed to reflect basic sequencing of the counter

BCD to Excess 3 Serial Converter


■ Conversion Process

Bits are presented in bit serial fashion
starting with the least significant bit

Single input X, single output Z

BCD	Excess 3 Code
0000	0011
0001	0100
0010	0101
0011	0110
0100	0111
0101	1000
0110	1001
0111	1010
1000	1011
1001	1100

 BCD to Excess 3 Serial Converter (Cont'd)



State Diagram

Present State		Next State		Output	
		X=0	X=1	X=0	X=1
S0	000 (0)	S1	S2	1	0
S1	001 (1)	S3	S4	1	0
S2	100 (4)	S4	S4	0	1
S3	010 (2)	S5	S5	0	1
S4	101 (5)	S5	S6	1	0
S5	011 (3)	S0	S0	0	1
S6	110 (6)	S0	--	1	--

State Transition Table

Note the sequential nature of the state assignment


Serial Converter: Transition Table

Inputs/Current State				Next State			Outputs						
X	Q2	Q1	Q0	Q2+	Q1+	Q0+	Z	$\overline{\text{CLR}}$	$\overline{\text{LD}}$	EN	C	B	A
0	0	0	0	0	0	1	1	1	1	1	X	X	X
0	0	0	1	0	1	0	1	1	1	1	X	X	X
0	0	1	0	0	1	1	0	1	1	1	X	X	X
0	0	1	1	0	0	0	0	0	X	X	X	X	X
0	1	0	0	1	0	1	0	1	1	1	X	X	X
0	1	0	1	0	1	1	1	1	0	X	0	1	1
0	1	1	0	0	0	0	1	0	X	X	X	X	X
0	1	1	1	X	X	X	X	X	X	X	X	X	X
1	0	0	0	1	0	0	0	1	0	X	1	0	0
1	0	0	1	1	0	1	0	1	0	X	1	0	1
1	0	1	0	0	1	1	1	1	1	1	X	X	X
1	0	1	1	0	0	0	1	0	X	X	X	X	X
1	1	0	0	1	0	1	1	1	1	1	X	X	X
1	1	0	1	1	1	0	0	1	1	1	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X	X	X

CLR signal dominates LD which dominates Count

Serial Converter (Cont'd)

 
- Counter-based implementation of code converter




Synchronous Output Register

When the state diagram has fewer out-of-sequence jumps, a counter based implementation can be very effective

Rom-Based Design

 

 ■ Block Diagram for Synchronous Mealy Machine




■ ROM-based Realization

- Inputs & Current State form the address
- ROM data bits form the Outputs & Next State

Rom-Based Design (Cont'd)

ROM ADDRESS				ROM Outputs			
X	Q2	Q1	Q0	Z	D2	D1	D0
0	0	0	0	1	0	0	1
0	0	0	1	1	0	1	1
0	0	1	0	0	1	0	0
0	0	1	1	0	1	0	1
0	1	0	0	1	1	0	1
0	1	0	1	0	0	0	0
0	1	1	0	1	0	0	0
0	1	1	1	X	X	X	X
1	0	0	0	0	0	1	0
1	0	0	1	0	1	0	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	0	1	1	0
1	1	0	1	1	0	0	0
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

 

Excess-3 synchronous Mealy ROM-based implementation

PLA-Based Design

- State assignment with NOVA

S0 = 000

S1 = 001


S2 = 011

S3 = 110

S4 = 100

S5 = 111

S6 = 101

 

PLA-Based Design (Cont'd)

```
.i 4
.o 4
.ilb x q2 q1 q0
.ob d2 d1 d0 z
.p 16
0 000 001 1
1 000 011 0
0 001 110 1
1 001 100 0
0 011 100 0
1 011 100 1
0 110 111 0
1 110 111 1
0 100 111 1
1 100 101 0
0 111 000 0
1 111 000 1
0 101 000 1
1 101 --- -
0 010 --- -
1 010 --- -
.e
```

```
.i 4
.o 4
.ilb x q2 q1 q0
.ob d2 d1 d0 z
.p 9
0001 0100
10-0 0100
01-0 0100
1-1- 0001
-0-1 1000
0-0- 0001
-1-0 1000
--10 0100
--0 0010
.e
```


$$Q2^+ = Q2'Q0 + Q2Q0'$$

$$Q1^+ = X'Q2'Q1'Q0 + XQ2'Q0' + X'Q2Q0' + Q1Q0'$$

$$Q0^+ = Q0'$$

$$Z = XQ1 + X'Q1'$$

9 product term
implementation

 



Espresso Inputs Espresso Outputs

PAL-Based Design (Cont'd)


- PAL10H8: 10 inputs, 8 outputs, 2 product terms per OR gate

$$\begin{aligned} Q2+ &= Q2'Q0 + Q2Q0' \\ Q1+ &= X'Q2'Q1'Q0 + XQ2'Q0' + X'Q2Q0' + Q1Q0' \\ Q0+ &= Q0' \\ Z &= XQ1 + X'Q1' \end{aligned}$$
  
$$\begin{aligned} Q1+ &= Q11+Q12 \\ Q11 &= X'Q2'Q1'Q0 + XQ2'Q0' \\ Q12 &= X'Q2Q0' + Q1Q0' \end{aligned}$$



Alternative PAL Architectures

 

$$D2' = Q2Q0 + Q2'Q0'$$

$$D1' = X'Q2'Q1'Q0' + XQ2 + XQ0 + Q2Q0 + Q1Q0$$

$$D0' = Q0$$


$$Z' = XQ1' + X'Q1$$

Vending machine example (Moore PLD mapping)

D0 = reset'(Q0'N + Q0N' + Q1N + Q1D)


D1 = reset'(Q1 + D + Q0N)

OPEN = Q1Q0

 

Vending machine (synch. Mealy PLD mapping)

 
$$\text{OPEN} = \text{reset}'(\text{Q1Q0N}' + \text{Q1N} + \text{Q1D} + \text{Q0}'\text{ND} + \text{Q0N}'\text{D})$$



22V10 PAL


- Combinational logic elements (SoP)
- Sequential logic elements (D-FFs)
- Up to 10 outputs
- Up to 10 FFs
- Up to 22 inputs

Functional Logic Diagram for PALC22V10D

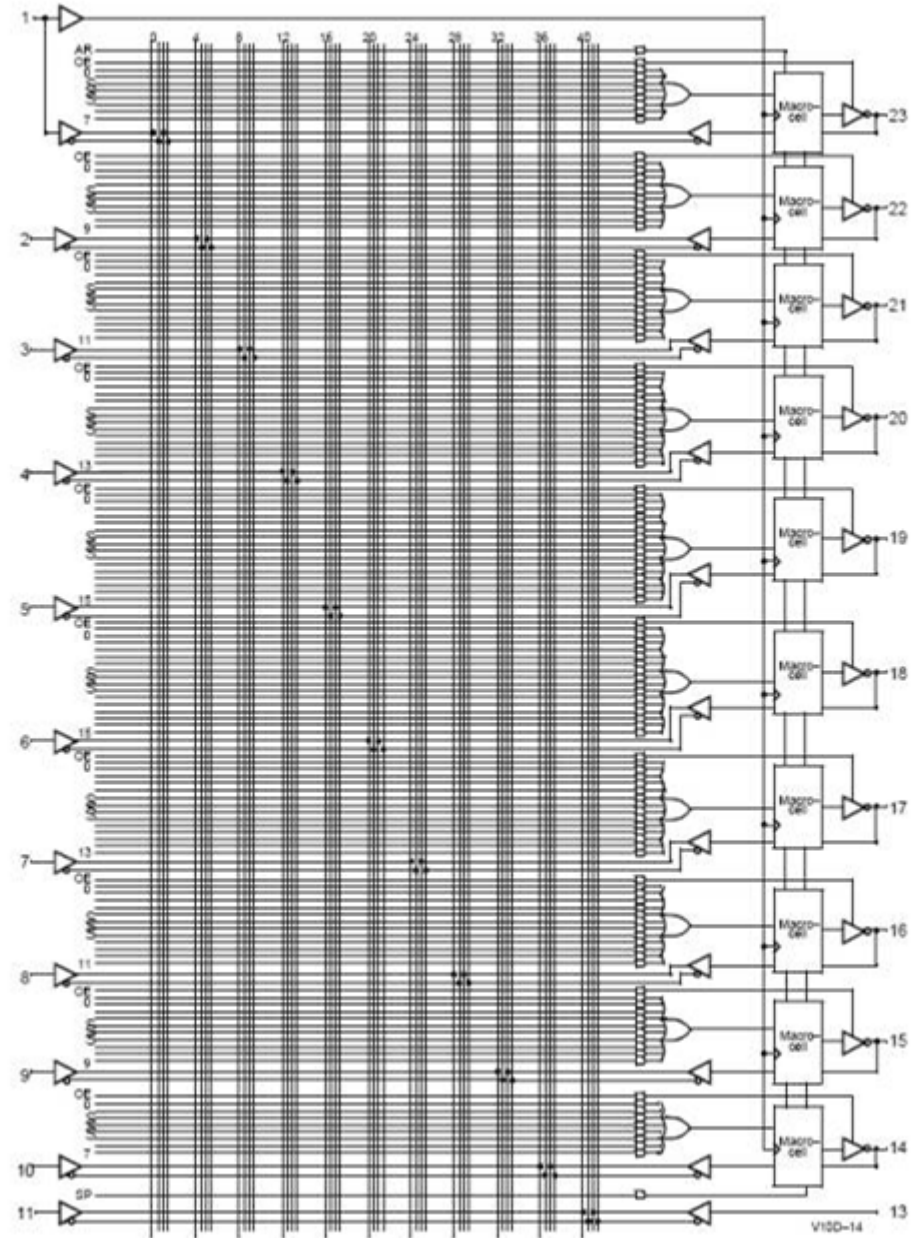

22V10 PAL Macro Cell

 - Sequential logic element + output/input selection



FPGA (Field Programmable Gate Array)

- Array of programmable logic-blocks with programmable interconnects
- Actel Programmable Gate Array
 - Multiplexer-based logic blocks
 - Anti-fuse technology for interconnects
- Xilinx Logic Cell Array
 - SRAM-based logic blocks and interconnects

FPGA (Cont'd)


■ Actel Programmable Gate Arrays

Rows of programmable
logic building blocks


+

rows of interconnect

Anti-fuse Technology:
Program Once

 

 
Use Anti-fuses to build
up long wiring runs from
short segments



FFs constructed from discrete cross coupled gates


FPGA (Cont'd)

Actel Logic Module

 

**Basic Module is a
Modified 4:1 Multiplexer**

 
**Example:
Implementation of $\overline{S}$ - $\overline{R}$ Latch**



FPGA (Cont'd)

■ Xilinx Logic Cell Arrays

 - ❑ CMOS Static RAM Technology: programmable on the fly!
- ❑ All personality elements connected into serial shift register
- ❑ Shift in string of 1's and 0's on power up
- ❑ General Chip Architecture:
 - Logic Blocks (CLBs)
 - IO Blocks (IOBs)
 - Wiring Channels



FPGA (Cont'd)

IO block

Inputs:

- Tri-state enable
- bit to output
- input, output clocks

Outputs:


- input bit

Internal FFs for input & output paths

Fast/Slow outputs


- 5 ns vs. 30 ns rise

Pull-up used with unused IOBs

 

FPGA (Cont'd)

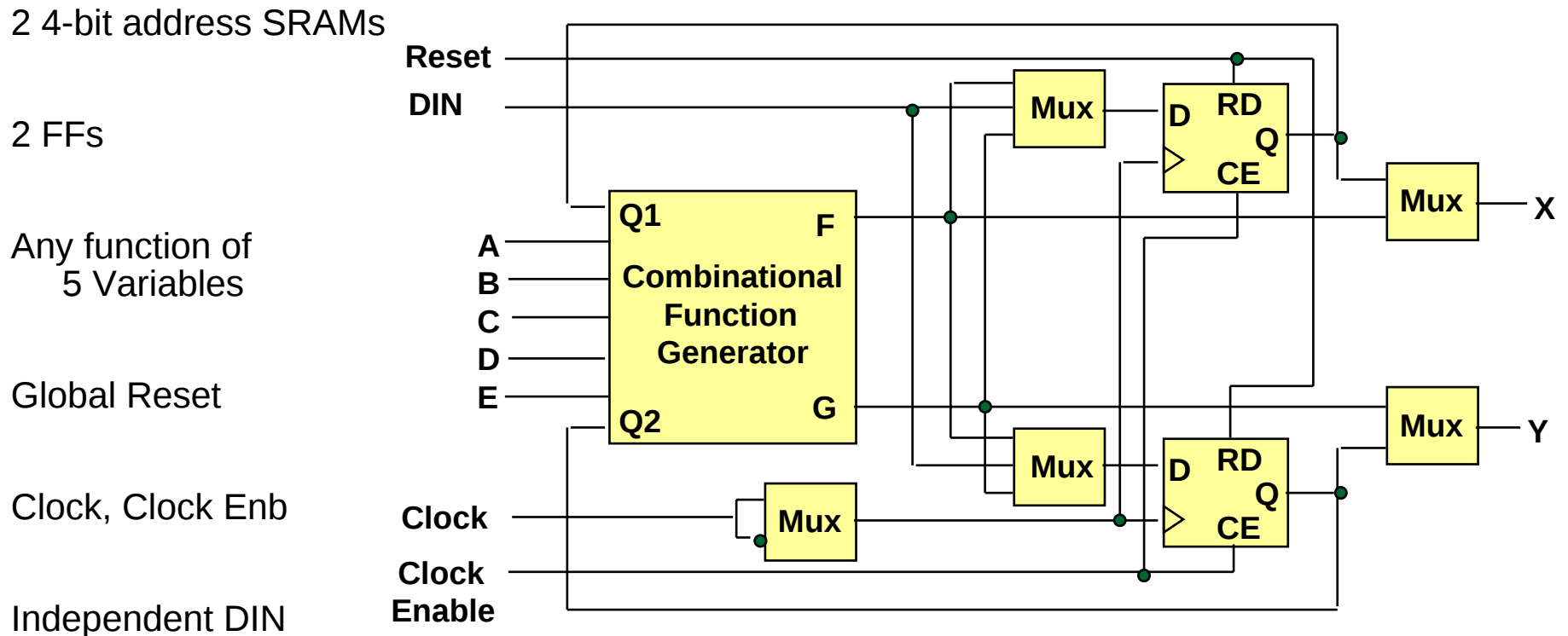
- ❑ Xilinx LCA Architecture
 - Configurable Logic Block (CLB)




FPGA (Cont'd)

- ❑ n-input Majority Circuit
 - Assert 1 whenever $n/2$ or greater inputs are 1
- ❑ n-input Parity Functions
 - 5 input = 1 CLB, 2 Levels of CLBs yield up to 25 inputs!


5-input Majority Circuit

 

7-input Majority Circuit

 


9 Input Parity Logic

 


FPGA (Cont'd)

4-bit Binary Adder

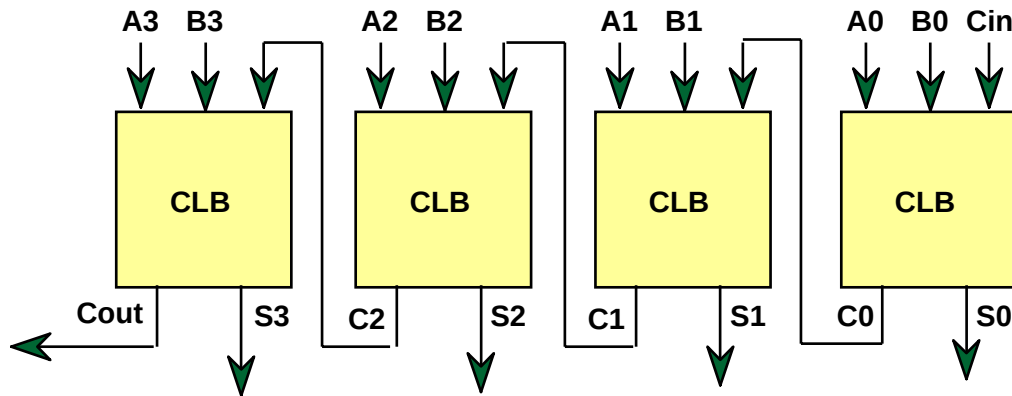

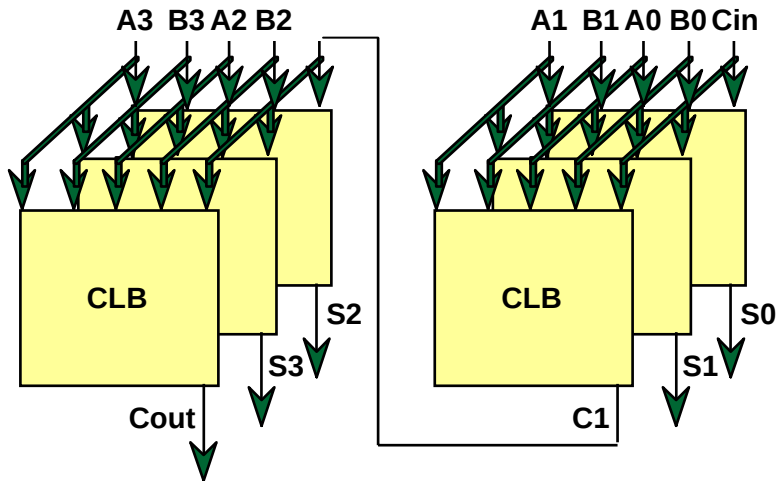
Full Adder, 4 CLB delays to final carry out



2 x Two-bit Adders (3 CLBs each) yields 2 CLBs to final carry out

FPGA (Cont'd)

 - ❑ Interconnect
 - Direct Connections
 - Global Long Line
 - Horizontal/Vertical Long Lines
 - Long Lines
 - Switching Matrix
 - Connections



FPGA (Cont'd)

■ Xilinx Application Example (BCD to Excess 3 FSM)

$$Q2+ = Q2' Q0 + Q2 Q0'$$

$$Q1+ = X' Q2' Q1' Q0 + X' Q2' Q0' + X Q2' Q0 + Q1' Q0$$

$$Q0+ = Q0'$$


$$Z = X Q1 + X' Q1'$$

- ❑ Synchronous Mealy Machine
- ❑ No function has more than 4 variables + 4 FFs implies 2 CLBs
- ❑ Global Reset to be used
- ❑ Place $Q2+$, $Q0+$ in one CLB and $Q1$, Z in second CLB
--> maximize use of direct & general purpose interconnections

FPGA (Cont'd)


Implementing the BCD to Excess 3 FSM
 
$$\begin{aligned} Q2+ &= Q2' Q0 + Q2 Q0' \\ Q1+ &= X' Q2' Q1' Q0 + X' Q2' Q0' \\ &\quad + X Q2' Q0 + Q1' Q0 \\ Q0+ &= Q0' \\ Z &= X Q1 + X' Q1' \end{aligned}$$



Case Study: Traffic Light Controller

- A busy highway is intersected by a little used farmroad
- Detectors C sense the presence of cars waiting on the farmroad
 - ❑ with no car on farmroad, light remain green in highway direction
 - ❑ if vehicle on farmroad, highway lights go from Green to Yellow to Red, allowing the farmroad lights to become green
 - ❑ these stay green only as long as a farmroad car is detected but never longer than a set interval
 - ❑ when these are met, farm lights transition from Green to Yellow to Red, allowing highway to return to green
 - ❑ even if farmroad vehicles are waiting, highway gets at least a set interval as green
- Assume you have an interval timer that generates:
 - ❑ a short time pulse (TS) and
 - ❑ a long time pulse (TL),
 - ❑ in response to a set (ST) signal.
 - ❑ TS is to be used for timing yellow lights and TL for green lights

 


Traffic Light Controller (cont'd)


- Decomposition into primitive subsystems
 - Controller FSM: next state/output functions, state register
 - Short time/long time interval counter
 - Car Sensor
 - Output Decoders and Traffic Lights

Traffic Light Controller (cont'd)

 
- Block diagram of complete traffic light system



Traffic Light Controller (cont'd)

 


Car Detector

 

Interval Timer

Light Decoders

 

Traffic Light Controller (cont'd)

■ Tabulation of inputs and outputs

inputs	description	outputs	description
reset	place FSM in initial state	HG, HY, HR	assert green/yellow/red highway lights
C	detect vehicle on the farm road	FG, FY, FR	assert green/yellow/red highway lights
TS	short time interval expired	ST	start timing a short or long interval
TL	long time interval expired		

■ Tabulation of unique states – some light configurations imply others

state	description
HG	highway green (farm road red)
HY	highway yellow (farm road red)
FG	farm road green (highway red)
FY	farm road yellow (highway red)

Traffic Light Controller (cont'd)

■ Next State/Output Logic

State Assignment: HG=00, HY=10, FG=01, FY=11

$$P1 = CTLQ1' + TS'Q1Q0' + C'Q1'Q0 + TS'Q1Q0$$

$$P0 = TSQ1Q0' + Q1'Q0 + TS'Q1Q0$$

$$ST = CTLQ1' + C'Q1'Q0 + TSQ1Q0' + TSQ1Q0$$

$$H1 = TSQ1Q0 + Q1'Q0 + TS'Q1Q0$$

$$H0 = TS'Q1Q0' + TSQ1Q0'$$

$$F1 = Q0'$$

$$F0 = TS'Q1Q0 + TSQ1Q0$$

■ PAL/PLA Implementation


- ❑ 5 inputs, 7 outputs, 8 product terms
- ❑ PAL 22V10 – 12 inputs, 10 prog. IOs, 8 to 16 prod terms per OR

■ ROM Implementation

- ❑ 32 word by 8-bit ROM (256 bits)
- ❑ Reset may double ROM size

Traffic Light Controller (cont'd)

 
- Next State Logic
 - ❑ Counter-based Implementation
 - ❑ $HG=00$, $HY=01$, $FG=10$, $FY=11$



Traffic Light Controller (cont'd)

- Next State Logic

 - ❑ Counter-based Implementation
- ❑ Dispense with direct output functions for the traffic lights



Sequential logic implementation summary

- Models for representing sequential circuits
 - finite state machines and their state diagrams
 - Mealy, Moore, and synchronous Mealy machines
- Finite state machine design procedure
 - deriving state diagram
 - deriving state transition table
 - assigning codes to states
 - determining next state and output functions
 - implementing combinational logic
- Implementation technologies
 - random logic with FFs
 - PAL/PLA/ROM with FFs
 - CPLD/FPGA