

Electromagnetics

<Chap. 9> Transmission Lines

Section 9.3 ~ 9.4

(1st of week 10)

Jaesang Lee

Dept. of Electrical and Computer Engineering

Seoul National University

(email: jsanglee@snu.ac.kr)

Chap. 9 | Contents for 1st class of week 10

Review of last class

- Equivalent circuit model: Lossy transmission lines

Sec 3. General Transmission-Line Equations


- General equations
- Special cases
- TR-line circuit parameters

Chap. 9 | Lossy TR lines: Equivalent circuit model (1/3)

• Attenuation in the parallel-plate transmission lines caused by...

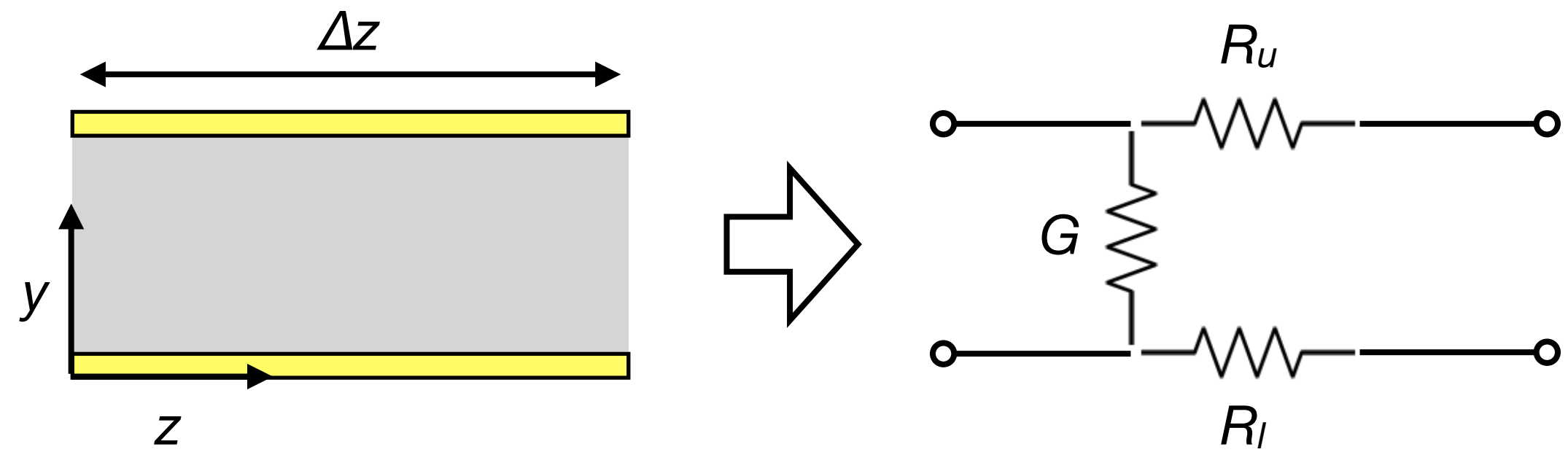- (1) Lossy dielectric ($\sigma \neq 0$)
- (2) Imperfectly conducting walls ($\sigma_c \neq \infty$)

$$\alpha = \alpha_d + \alpha_c = \frac{\sigma}{2} \eta + \frac{1}{d} \sqrt{\frac{\pi f \epsilon}{\sigma_c}}$$




<Circuit representation>

• Conductance (G) between two conductors per unit length

$$G = C \frac{\sigma}{\epsilon} \quad (\text{from right})$$

$$= \epsilon \frac{w}{d} \cdot \frac{\sigma}{\epsilon} = \sigma \frac{w}{d} \quad (\text{S/m})$$

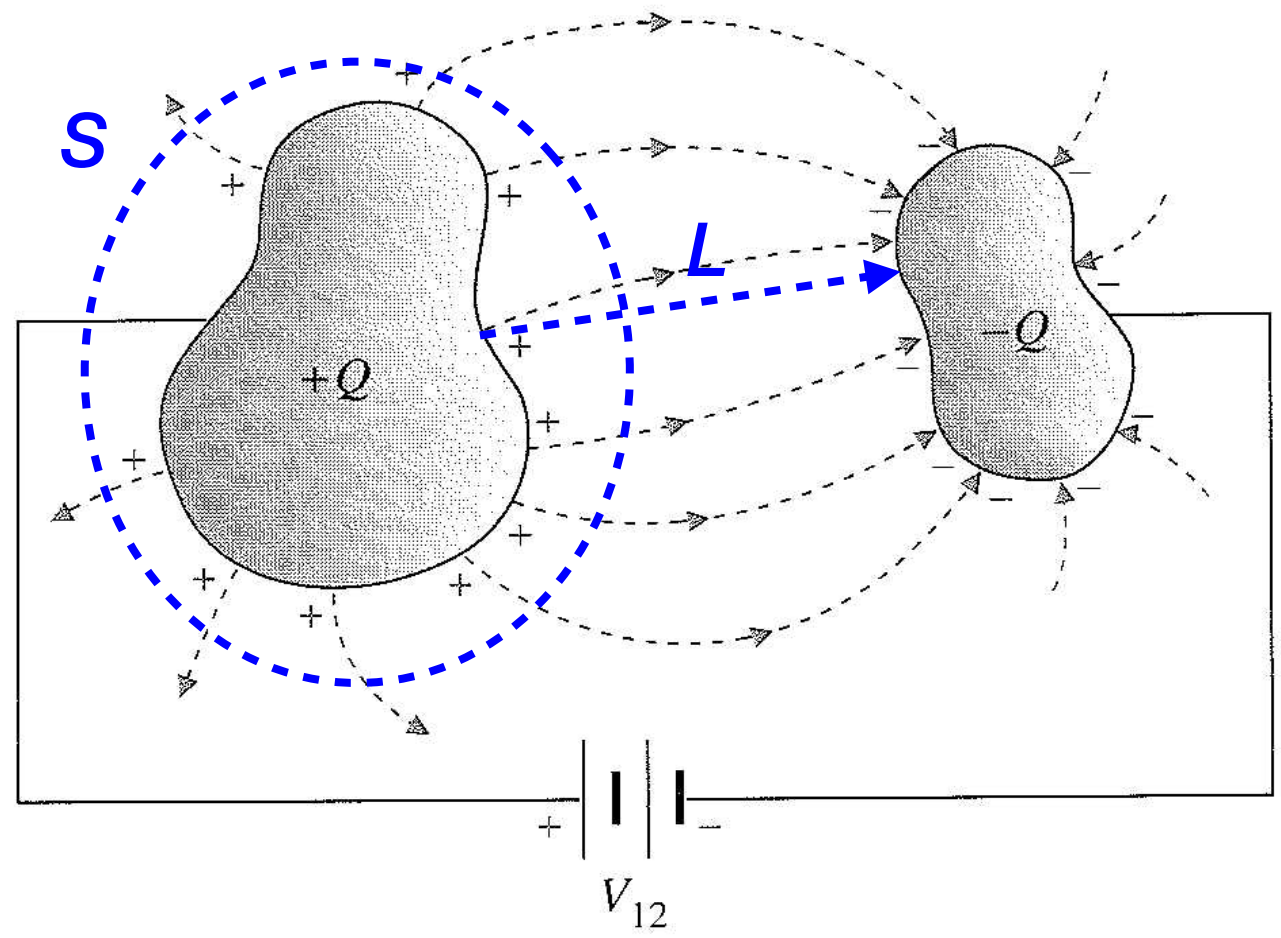where σ is the conductivity of the dielectric



$$C = \frac{Q}{V} = \frac{\oint_S \mathbf{D} \cdot d\mathbf{s}}{-\int_L \mathbf{E} \cdot d\mathbf{l}} = \frac{\oint_S \epsilon \mathbf{E} \cdot d\mathbf{s}}{-\int_L \mathbf{E} \cdot d\mathbf{l}}$$


$$R = \frac{V}{I} = \frac{-\int_L \mathbf{E} \cdot d\mathbf{l}}{\oint_S \mathbf{J} \cdot d\mathbf{s}} = \frac{-\int_L \mathbf{E} \cdot d\mathbf{l}}{\oint_S \sigma \mathbf{E} \cdot d\mathbf{s}}$$

$$\rightarrow RC = \frac{-\int_L \mathbf{E} \cdot d\mathbf{l}}{\sigma \oint_S \mathbf{E} \cdot d\mathbf{s}} \cdot \frac{\epsilon \oint_S \mathbf{E} \cdot d\mathbf{s}}{-\int_L \mathbf{E} \cdot d\mathbf{l}} = \frac{\epsilon}{\sigma} = \frac{C}{G}$$

Chap. 9 | Lossy TR lines: Equivalent circuit model (2/3)

- **Resistance (R) along the conductors per unit length**
 - In actual cases, conductivity of the plate is *finite* ($\sigma_c \neq \infty$)
 - ∴ **small, yet non-vanishing longitudinal field (E_z) “induced!”** ($H_x \rightarrow J_{su} \rightarrow E_z!$)
 - R obtained by relationship between power loss at the surface vs. surface current
 - Time-average power dissipated on unit surface [W/m^2] due to E_z

$$\mathbf{a}_y p_{\sigma_c} \text{ [W/m}^2\text{]} = \frac{1}{2} \text{Re}(\mathbf{a}_z E_z \times \mathbf{a}_x H_x^*) = \frac{1}{2} \text{Re}(\mathbf{a}_y |J_s|^2 Z_s) \quad \dots(1)$$

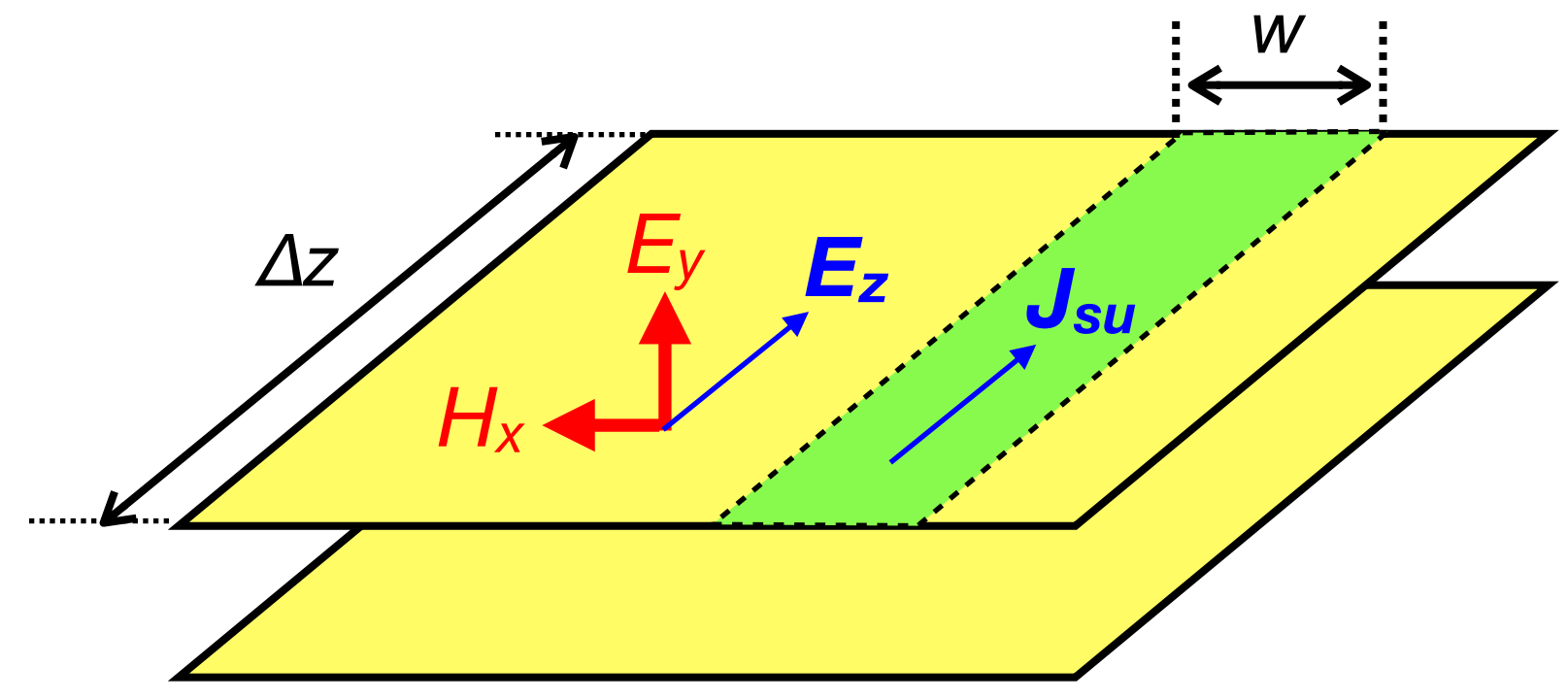

“Surface” impedance (Z_s) of the plate

$$Z_s = \frac{E_z}{H_x} = \frac{E_z}{J_{su}} = \eta_c \quad \dots(2) \quad (= \text{Intrinsic impedance of the plate})$$

$$\eta_c = R_s + jX_s = (1 + j) \sqrt{\frac{\pi f \mu_c}{\sigma_c}} \quad (\Omega) \quad \dots(3) \quad (\text{Refer to lecture note 3-2})$$

“Surface” current (J_s)
(∴ $f \uparrow \rightarrow$ skin depth \downarrow)

$$J_{su} = \mathbf{a}_z H_x = \mathbf{a}_z \sigma_c E_z \quad (\text{A/m})$$

$$J_{sl} = -J_{su}$$

- From **eqn. (2)**, we get

$$E_z = J_{su} Z_s \quad \text{and} \quad H_x = J_{su} \quad \dots(4)$$
- By plugging **eqn. (4)** and **(3)** into **eqn. (1)**, we get

$$p_{\sigma_c} = \frac{1}{2} \text{Re}(|J_s|^2 Z_s) = \frac{1}{2} |J_s|^2 R_s \quad (\text{W/m}^2)$$

- Power dissipated per unit length [W/m] through the plate of width w

$$P_{\sigma_c} = w p_{\sigma_c} = \frac{1}{2} w |J_s|^2 R_s \quad (\text{W/m})$$

$$= \frac{1}{2} |w J_s|^2 \left(\frac{R_s}{w} \right) = \frac{1}{2} I^2 \left(\frac{R_s}{w} \right)$$

$$\therefore R = R_u + R_l = 2 \left(\frac{R_s}{w} \right) = \frac{2}{w} \sqrt{\frac{\pi f \mu_c}{\sigma_c}} \quad (\Omega / m)$$

Chap. 9 | Lossy TR lines: Equivalent circuit model (3/3)

- How significant is E_z ?

$$\frac{|E_z|}{|E_y|} = \frac{|\eta_c H_x|}{|\eta H_x|} = \sqrt{\frac{\epsilon}{\mu}} |\eta_c| = \sqrt{\frac{\epsilon}{\mu}} \sqrt{2} \sqrt{\frac{\pi f \mu_c}{\sigma_c}} = \sqrt{\frac{2\pi f \epsilon}{\sigma_c}}$$

e.g.) For copper [$\sigma_c = 5.8 \times 10^7$ (S/m)] and $\epsilon = \epsilon_0$ for dielectric at $f = 3$ (GHz),


$$|E_z| \approx 5.3 \times 10^{-5} |E_y| \ll |E_y|$$

$\therefore E_z =$ a slight perturbation \rightarrow TEM approximation holds!

\rightarrow **“Quasi”-TEM mode in lossy transmission line!**

• Distributed parameters of parallel-plate transmission line (width = w , separation = d)

Parameter	Formula	Unit
R	$\frac{2}{w} \sqrt{\frac{\pi f \mu_c}{\sigma_c}}$	(Ω / m)
L	$\mu \frac{d}{w}$	(H / m)
G	$\sigma \frac{w}{d}$	(S / m)
C	$\epsilon \frac{w}{d}$	(F / m)

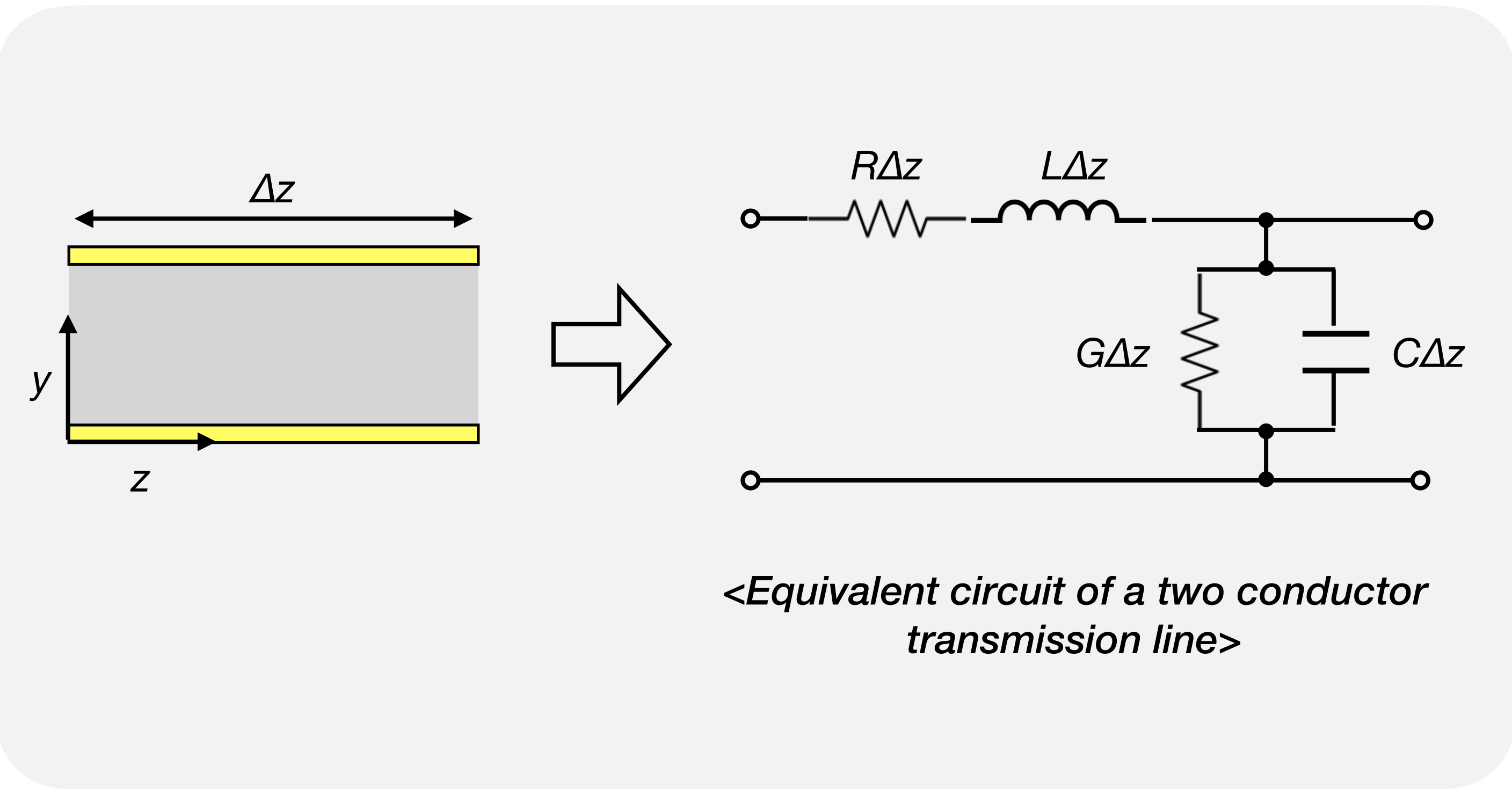

Chap. 9 | General TR-line equations (1a/4)


• General TR-line equations

- Generally applied to *parallel-plate, two-wire, coaxial* TR-lines

- “Disturbed-element” model

▸ TR-line = *infinite* series of an *infinitesimally short segment* (Δz) of the TR-line

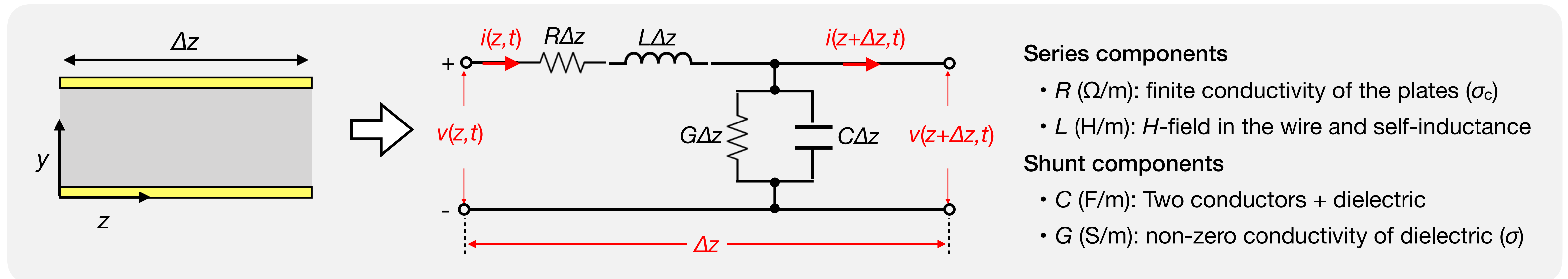▸ Short segment represented with *circuit-elements* (R, L, C, G) “*distributed*” *uniformly* throughout entire TR-line (R, L, C, G given per unit length)





- When used?

- **Very, very long TR-line** ($>240 \text{ km}$): AC voltage and current at one location different from those at other (\because signal speed $\neq \infty$)
- **At very high frequency**: physical dimension of circuit \sim wavelength of electrical signal
 - For these cases, wires or lines are not perfect conductors and their impedance matters (represented by R, L, C, G)
 - *c.f*) Lumped-element model (R, L, C, G NOT depending on length and concentrated at singular points) e.g. regular circuit we use


Chap. 9 | General TR-line equations (1b/4)

- Lumped-element model (low frequency)

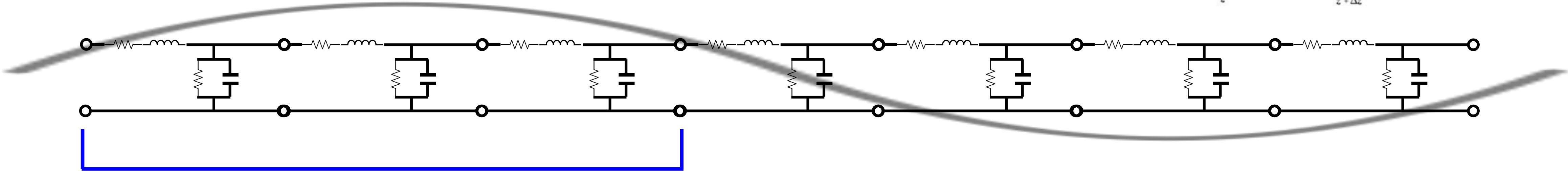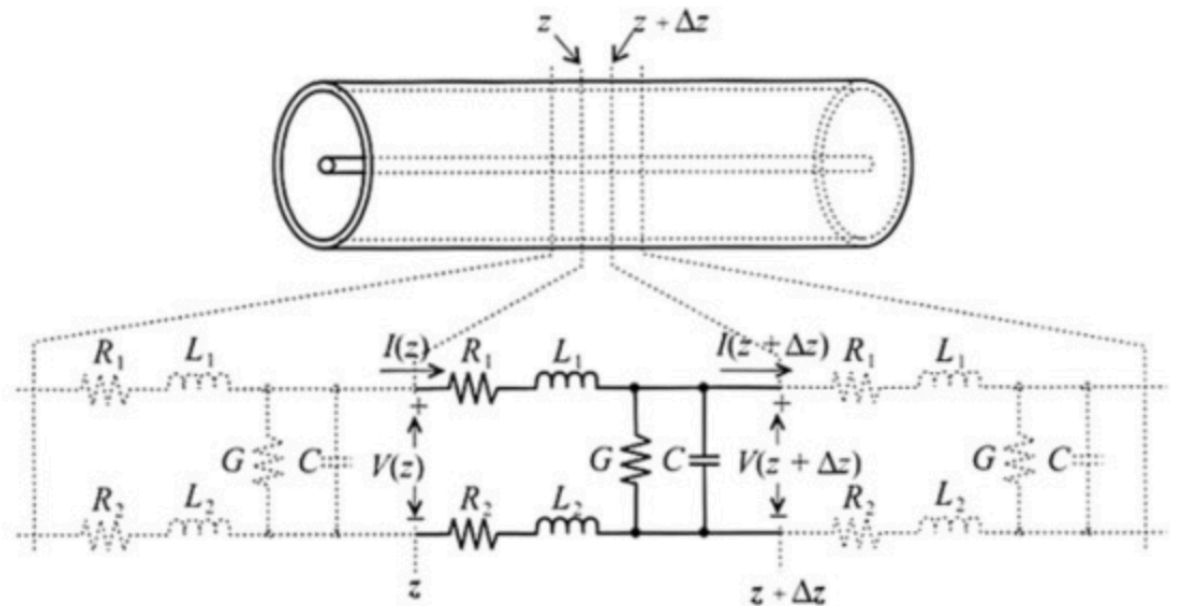


Can be lumped into single R, G, C, G
(.:not dependent on z)

- Disturbed-element model (high frequency)

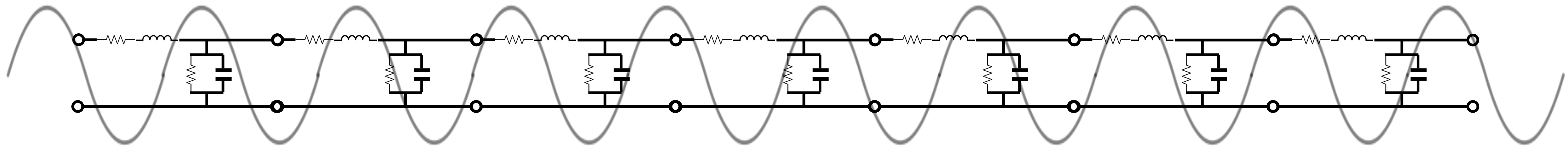

Chap. 9 | General TR-line equations (2/4)

• General TR-line equations

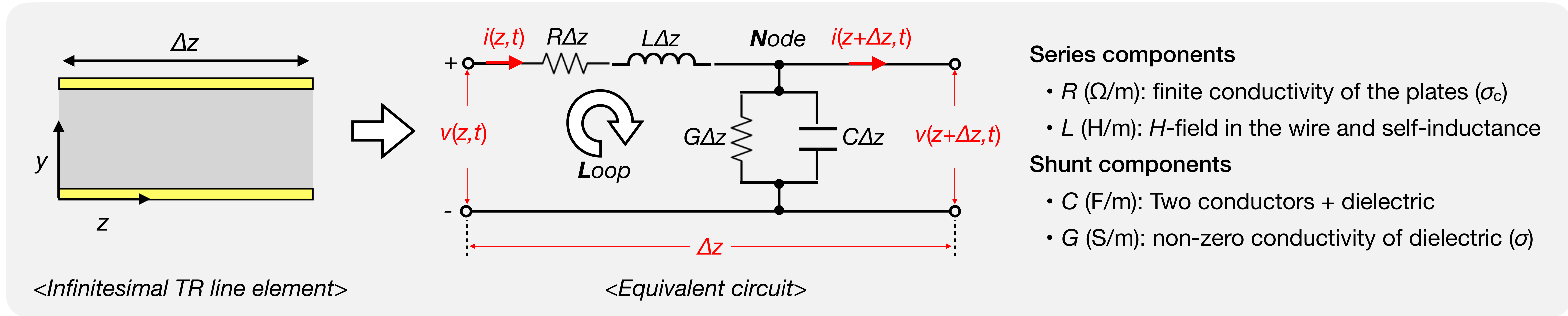

- Kirchoff's voltage law (around loop **L**)

$$-v(z,t) + R\Delta z \cdot i(z,t) + L\Delta z \frac{\partial i(z,t)}{\partial t} + v(z + \Delta z,t) = 0 \quad \rightarrow \quad \lim_{\Delta z \rightarrow 0} \frac{v(z + \Delta z,t) - v(z,t)}{\Delta z} = Ri(z,t) + L \frac{\partial i(z,t)}{\partial t}$$

- Kirchoff's current law (to node **M**)

$$i(z,t) - G\Delta z \cdot v(z + \Delta z,t) - C\Delta z \frac{\partial v(z + \Delta z,t)}{\partial t} - i(z + \Delta z,t) = 0 \quad \rightarrow \quad \lim_{\Delta z \rightarrow 0} \frac{i(z,t) - i(z + \Delta z,t)}{\Delta z} = Gv(z,t) + C \frac{\partial v(z,t)}{\partial t}$$

Chap. 9 | General TR-line equations (3/4)

• **General transmission-line equations**

: A pair of 1st-order PDEs in $v(z,t)$ and $i(z,t)$

$$\begin{cases} -\frac{\partial v(z,t)}{\partial z} = Ri(z,t) + L\frac{\partial i(z,t)}{\partial t} \\ -\frac{\partial i(z,t)}{\partial z} = Gv(z,t) + C\frac{\partial v(z,t)}{\partial t} \end{cases}$$

Time-harmonic TR-line equation

since $\begin{cases} v(z,t) = \text{Re}[V(z)e^{j\omega t}] \\ i(z,t) = \text{Re}[I(z)e^{j\omega t}] \end{cases}$,

$$\begin{cases} -\frac{dV(z)}{dz} = (R + j\omega L)I(z) \\ -\frac{dI(z)}{dz} = (G + j\omega C)V(z) \end{cases}$$

c.f.) Under lossless condition ($R = 0, G = 0$)
(where $\sigma_c \rightarrow \infty, \sigma \rightarrow 0$)

$$\begin{cases} -\frac{dV(z)}{dz} = j\omega LI(z) \\ -\frac{dI(z)}{dz} = j\omega CV(z) \end{cases}$$


*Consistent with ideal case!
(in previous class)*

• **Wave characteristics on an infinite TR line**

- To solve for $V(z)$ and $I(z)$, coupled time-harmonic TR equations combined as

(Double derivative)
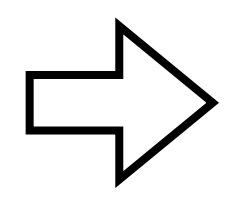
$$\begin{cases} -\frac{d^2V(z)}{dz^2} = (R + j\omega L)\frac{dI(z)}{dz} = -(R + j\omega L)(G + j\omega C)V(z) \\ -\frac{d^2I(z)}{dz^2} = (G + j\omega C)\frac{dV(z)}{dz} = -(G + j\omega C)(R + j\omega L)I(z) \end{cases}$$



$$\begin{cases} \frac{d^2V(z)}{dz^2} = \gamma^2 V(z) \\ \frac{d^2I(z)}{dz^2} = \gamma^2 I(z) \end{cases} \quad \text{where } \gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

Chap. 9 | General TR-line equations (4/4)

• Solution for an infinite TR-line

$$\begin{cases} V(z) = V_0 e^{-\gamma z} + \cancel{V_1 e^{\gamma z}} \\ I(z) = I_0 e^{-\gamma z} + \cancel{I_1 e^{\gamma z}} \end{cases} \dots(1) \quad (\because \text{No reflection!})$$

- If we plug (1) into (2),

$$\left[-\frac{d}{dz}(V_0 e^{-\gamma z}) = \gamma V_0 e^{-\gamma z} \right] = (R + j\omega L) I_0 e^{-\gamma z}$$

$$\rightarrow \frac{V_0}{I_0} \triangleq Z_0 = \frac{R + j\omega L}{\gamma} = \frac{\gamma}{G + j\omega C} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

First order ODEs

$$\begin{cases} -\frac{dV(z)}{dz} = (R + j\omega L) I(z) \\ -\frac{dI(z)}{dz} = (G + j\omega C) V(z) \end{cases} \dots(2)$$

Second order ODEs

$$\begin{cases} \frac{d^2 V(z)}{dz^2} = \gamma^2 V(z) \\ \frac{d^2 I(z)}{dz^2} = \gamma^2 I(z) \end{cases} \quad \text{where } \gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

Characteristic Impedance (Z_0) & propagation constant (γ)

- Z_0 is uniform across the TR-line (\because uniform cross-section)
- Both NOT depend on z (particular position TR-line)
- Both ONLY depend on distributed parameters (R, L, G, C) and ω

Chap. 9 | Special cases for TR-lines (1/3)

• 1) Lossless line ($R = 0, G = 0$)

- Ideal case → infinite conductor conductivity ($\sigma_c = \infty$), zero dielectric conductivity ($\sigma = 0$)

- Propagation constant:

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = j\omega\sqrt{LC}$$

$\alpha = 0$ (No attenuation)

$\beta = \omega\sqrt{LC}$ (a "linear" function of ω)

- Phase velocity:

$$u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} \text{ (constant)}$$

Non-dispersive!
(i.e. frequency-independent)
→ No signal distortion!

- Characteristic impedance:

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{L}{C}}$$

$$R_0 = \sqrt{\frac{L}{C}} \text{ (constant)}$$

$$X_0 = 0$$

• 2) Low-Loss line ($R \ll \omega L, G \ll \omega C$)

- Realistic case, easily satisfied at very high frequencies

- Propagation constant:

Binomial approx.

$$\lim_{x \rightarrow 0} (1 + x)^n \approx (1 + nx)$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{j\omega L \left(1 + \frac{R}{j\omega L}\right) j\omega C \left(1 + \frac{G}{j\omega C}\right)} \approx j\omega\sqrt{LC} \left(1 + \frac{R}{2j\omega L}\right) \left(1 + \frac{G}{2j\omega C}\right)$$

$$\approx j\omega\sqrt{LC} \left(1 + \frac{1}{2j\omega} \left(\frac{R}{L} + \frac{G}{C}\right) - \frac{1}{4\omega^2} \frac{RG}{LC}\right)$$

(Neglected at high frequency!)

$$\therefore \alpha \approx \frac{1}{2} \left(R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}} \right),$$

$$\beta \approx \omega\sqrt{LC} \text{ ("nearly" a linear function of } \omega)$$

Chap. 9 | Special cases for TR-lines (2/3)

- 2) *Low-Loss line* ($R \ll \omega L, G \ll \omega C$)

- *Phase velocity:*

$$u_p = \frac{\omega}{\beta} \simeq \frac{1}{\sqrt{LC}} \quad (\text{Approximately constant})$$

- *Characteristic impedance:*

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{j\omega L}{j\omega C} \left(1 + \frac{R}{j\omega L}\right)^{1/2} \left(1 + \frac{G}{j\omega C}\right)^{-1/2}} \simeq \sqrt{\frac{L}{C} \left(1 + \frac{R}{2j\omega L}\right) \left(1 - \frac{G}{2j\omega C}\right)}$$

$$\simeq \sqrt{\frac{L}{C} \left[1 + \frac{1}{2j\omega} \left(\frac{R}{L} - \frac{G}{C}\right) - \frac{1}{4\omega^2} \frac{RG}{LC}\right]}$$

(Neglected at high frequency!)

$$\therefore R_0 \simeq \sqrt{\frac{L}{C}},$$

$$X_0 \simeq -\sqrt{\frac{L}{C}} \frac{1}{2\omega} \left(\frac{R}{L} - \frac{G}{C}\right) \simeq 0 \quad (\text{minor phase shift between } E \text{ and } H)$$

Lossy transmission line

- At *high* frequency → “nearly” non-dispersive system (Good!)
 - At *low* frequency → dispersive system (Bad, **signal distortion!**)
- (Signal = a band of *multiple, continuous frequencies*)

i.e.) α, β : functions of frequency (ω)
→ attenuates differently vs. ω
→ travels differently vs. ω

Chap. 9 | Special cases for TR-lines (3/3)

• 3) “Distortionless” line

- If lossy TR-line satisfies the condition as $\frac{R}{L} = \frac{G}{C}$ or $G = \frac{RC}{L}$,

- *Propagation constant:*

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{(R + j\omega L)\left(\frac{RC}{L} + j\omega C\right)} = \sqrt{(R + j\omega L)(R + j\omega L)\frac{C}{L}} = \sqrt{\frac{C}{L}}(R + j\omega L)$$



$$\alpha = R\sqrt{\frac{C}{L}}$$



$$\beta = \omega\sqrt{LC} \quad (\text{A linear function of } \omega)$$

$$\rightarrow u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} \quad (\text{Constant})$$

- *Characteristic impedance:*

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{R + j\omega L}{RC/L + j\omega C}} = \sqrt{\frac{L}{C}} \quad (\text{Constant})$$

∴ *Distortionless TR line can be designed such that* $\frac{R}{L} = \frac{G}{C}$

Q: How would you minimize α (i.e. attenuation) though?

Series components

- R (Ω/m): finite conductivity of the plates (σ_c)
- L (H/m): H -field in the wire and self-inductance

Shunt components

- C (F/m): Two conductors + dielectric
- G (S/m): non-zero conductivity of dielectric (σ)

Chap. 9 | TR-line parameters (1/3)

• **TR-line parameters**

- Electrical properties of TR-line **COMPLETELY** explained by *distributed parameters* (**R, L, C, G**) at given ω
- For simplicity: $\sigma_c \rightarrow \infty$ (i.e. very good conductors) $\rightarrow R = 0$ so that waves **nearly TEM!**

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = j\omega\sqrt{LC} \left(1 + \frac{G}{j\omega C}\right)^{1/2}$$

$$= j\omega\sqrt{LC} \left(1 + \frac{\sigma}{j\omega\epsilon}\right)^{1/2} \dots(1) \quad \left(\because \frac{G}{C} = \frac{\sigma}{\epsilon} \dots(2)\right)$$

(From p.3 of this slide)

- By comparing (2) and (1), we know that $LC = \mu\epsilon \dots(4)$

• **Procedures to obtain R, L, C, G**

- If **L** is known, we know **C** from **equation (4)** and vice versa
- Once **C** is determined, we know **G** from **equation (2)**
- **R** can be obtained by introducing a small E_z as perturbation & by finding ohmic power dissipated in a unit length of the TR line (see right)

Propagation constant in lossy medium

$$\gamma = jk_c = j\omega\sqrt{\mu\epsilon_c} \quad \text{where } \epsilon_c = \epsilon + \frac{\sigma}{j\omega}$$

$$= j\omega\sqrt{\mu\left(\epsilon + \frac{\sigma}{j\omega}\right)}$$

$$= j\omega\sqrt{\mu\epsilon} \sqrt{1 + \frac{\sigma}{j\omega\epsilon}} \dots(3)$$

Intrinsic impedance of a good conductor

$$Z_s = R_s + jX_s = (1 + j) \sqrt{\frac{\pi f \mu_c}{\sigma_c}}$$

Ohmic power dissipated per unit area

$$p_\sigma = \text{Re}\left(\frac{1}{2}|J_s|^2 Z_s\right) = \frac{1}{2}|J_s|^2 R_s \quad (\text{W/m}^2)$$

where J_s : surface current (A/m)

Chap. 9 | TR-line parameters (2/3)

• Two-wire TR line

- **Capacitance** per unit length of a two-wire TR line

$$C = \frac{\pi\epsilon}{\cosh^{-1}(D/2a)} \quad (\text{Chap. 4-4; Image method})$$

- **Inductance** per unit length

$$L = \frac{\mu\epsilon}{C} = \frac{\mu}{\pi} \cosh^{-1}\left(\frac{D}{2a}\right) \quad (\because LC = \mu\epsilon)$$


- **Conductance** per unit length

$$G = C \frac{\sigma}{\epsilon} = \frac{\pi\sigma}{\cosh^{-1}(D/2a)} \quad \left(\because \frac{G}{C} = \frac{\sigma}{\epsilon}\right)$$

- **Resistance** per unit length of "single" conductor

$$\begin{aligned} P_{\sigma} \text{ (W/m)} &= 2\pi a \cdot p_{\sigma} = 2\pi a \frac{1}{2} |J_s|^2 R_s \\ &= \frac{1}{2} |2\pi a J_s|^2 \left(\frac{R_s}{2\pi a}\right) = \frac{1}{2} I^2 \left(\frac{R_s}{2\pi a}\right) \end{aligned}$$
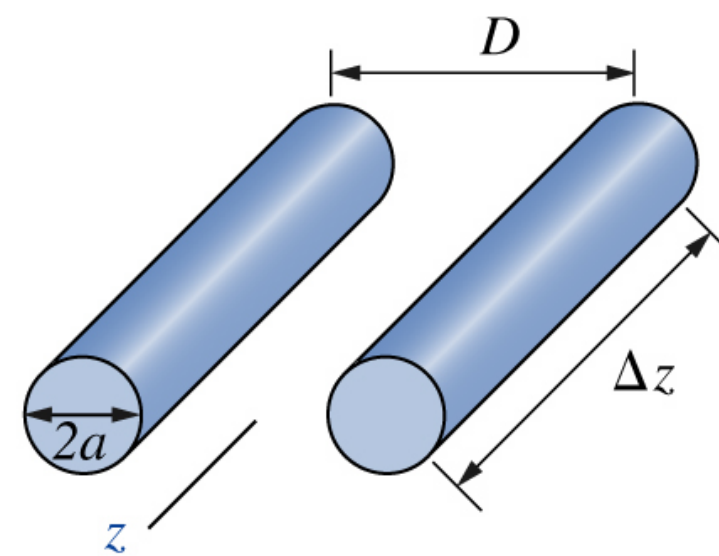
$$R = 2 \left(\frac{R_s}{2\pi a}\right) = \frac{1}{\pi a} \sqrt{\frac{\pi f \mu_c}{\sigma_c}}$$



• Coaxial TR line

- **Inductance** per unit length of a coaxial TR line

$$L = \frac{\mu}{2\pi} \ln\left(\frac{b}{a}\right) \quad (\text{Chap. 6-11; Mutual inductance})$$

- **Capacitance** per unit length

$$C = \frac{\mu\epsilon}{L} = \frac{2\pi\epsilon}{\ln(b/a)}$$


- **Conductance** per unit length

$$G = C \frac{\sigma}{\epsilon} = \frac{2\pi\sigma}{\ln(b/a)}$$

- **Resistance** per unit length of inner & outer conductors

$$\begin{aligned} P_{\sigma} \text{ (W/m)} &= 2\pi a \cdot p_{\sigma_i} + 2\pi b \cdot p_{\sigma_o} = 2\pi a \frac{1}{2} |J_{si}|^2 R_s + 2\pi b \frac{1}{2} |J_{so}|^2 R_s \\ &= \frac{1}{2} (2\pi a |J_{si}|)^2 \left(\frac{R_s}{2\pi a}\right) + \frac{1}{2} (2\pi b |J_{so}|)^2 \left(\frac{R_s}{2\pi b}\right) = \frac{1}{2} I^2 \frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b}\right) \end{aligned}$$


$$R = \frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b}\right)$$

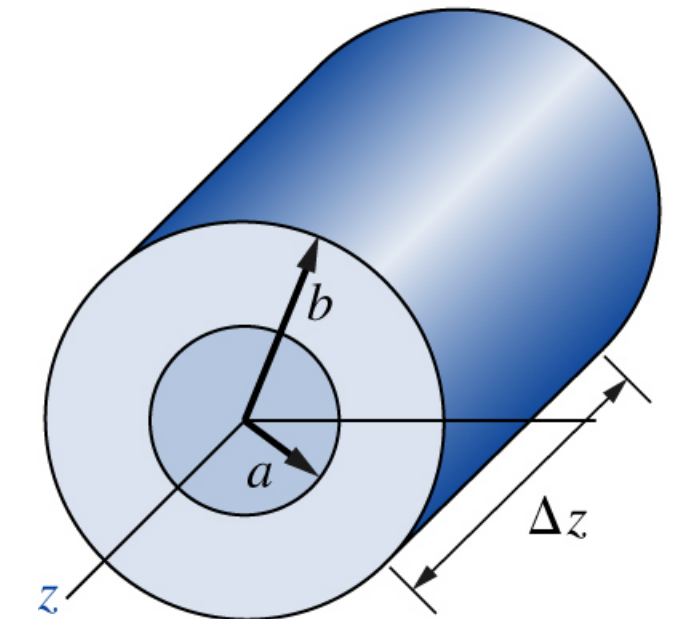

Chap. 9 | TR-line parameters (3/3)

• **Attenuation constant from power relations**
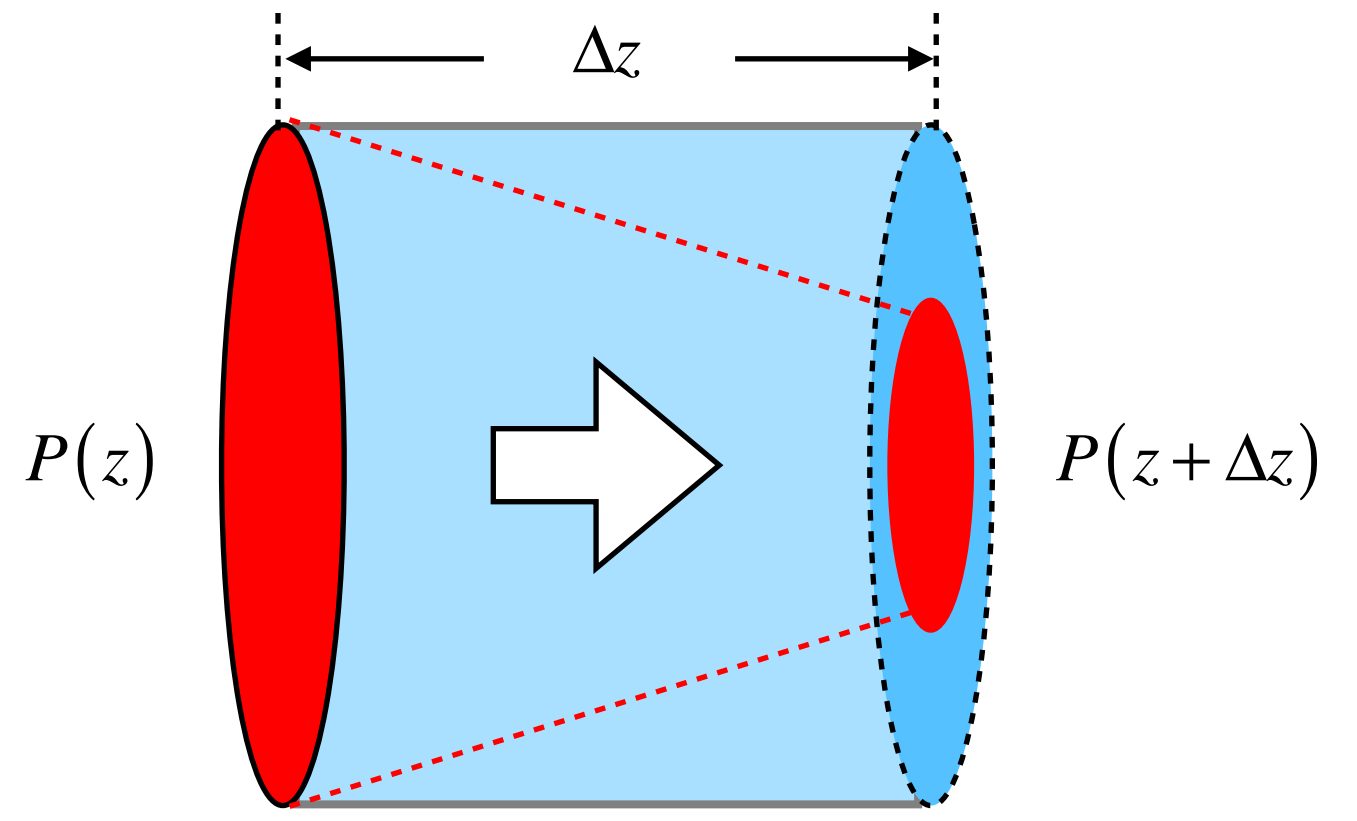
$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} \rightarrow \alpha = \text{Re} \left[\sqrt{(R + j\omega L)(G + j\omega C)} \right] \quad \text{(One method!)}$$



- Time-average power propagated along the TR line at any z

$$P(z) = \frac{1}{2} \text{Re} [V(z)I^*(z)] = \frac{V_0^2}{2|Z_0|^2} R_0 e^{-2\alpha z} \quad \text{where} \quad \begin{cases} V(z) = V_0 e^{-\gamma z} = V_0 e^{-(\alpha + j\beta)z} \\ I(z) = \frac{V_0}{Z_0} e^{-(\alpha + j\beta)z} \end{cases}$$

$$Z_0 = \frac{V_0}{I_0} = R_0 + jX_0 = \frac{R + j\omega L}{\gamma}$$

- Rate of power decrease along the line of length Δz

$$-\lim_{\Delta z \rightarrow 0} \frac{P(z + \Delta z) - P(z)}{\Delta z} \rightarrow -\frac{\partial P(z)}{\partial z} = 2\alpha P(z) = \frac{\alpha V_0^2}{|Z_0|^2} R_0 e^{-2\alpha z} \quad \dots(1)$$

- Rate of energy dissipation P_L per Δz

$$P_L(z) = \frac{1}{2} [|I(z)|^2 R + |V(z)|^2 G] = \frac{V_0^2}{2|Z_0|^2} (R + G|Z_0|^2) e^{-2\alpha z} \quad \dots(2)$$

- Since (1) = (2),

$$\therefore \alpha = \frac{P_L(z)}{2P(z)} = \frac{1}{2R_0} (R + G|Z_0|^2)$$

Consistent results as in pp. 9~11

- For a low-loss line $\left(Z_0 \cong R_0 = \sqrt{\frac{L}{C}} \right)$

$$\alpha = \frac{1}{2R_0} (R + G|Z_0|^2) = \frac{1}{2} \left(\frac{R}{R_0} + GR_0 \right) = \frac{1}{2} \left(R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}} \right)$$
- For a distortion-less line $\left(Z_0 = R_0 = \sqrt{\frac{L}{C}} \quad \text{and} \quad \frac{R}{L} = \frac{G}{C} \right)$

$$\alpha = \frac{1}{2} \left(R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}} \right) = \frac{1}{2} R\sqrt{\frac{C}{L}} \left(1 + \frac{G}{R} \cdot \frac{L}{C} \right) = R\sqrt{\frac{C}{L}}$$

Electromagnetics

<Chap. 9> Transmission Lines

Section 9.3 ~ 9.4

(2nd of week 10)

Jaesang Lee

Dept. of Electrical and Computer Engineering

Seoul National University

(email: jsanglee@snu.ac.kr)

Chap. 9 | Contents for 2nd class of week 10

Sec 4. Wave characteristics on Finite Transmission Lines

- Equivalent circuit model
- Impedance matching: load impedance & TR-line length
- Lossy finite-length TR-lines

Chap. 9 | Circuit model for "finite" TR-line (1/3)

• *General solution for finite-length transmission lines*

$$\begin{cases} \frac{d^2V(z)}{dz^2} = \gamma^2 V(z) \\ \frac{d^2I(z)}{dz^2} = \gamma^2 I(z) \end{cases} \Rightarrow \begin{cases} V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \\ I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \end{cases} \text{ where } \frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = Z_0 \text{ (Proof; HW)}$$

(Time-harmonic Helmholtz's equations)



• *Equivalent circuit model*


- Sinusoidal voltage V_g with an internal impedance Z_g
- TR-line characterized by γ (propagation constant) and Z_0 (characteristic impedance)
- Line of length l terminated in an arbitrary impedance Z_L

"Reflection-less" matching condition

$Z_L = Z_0$

Z_L : load impedance

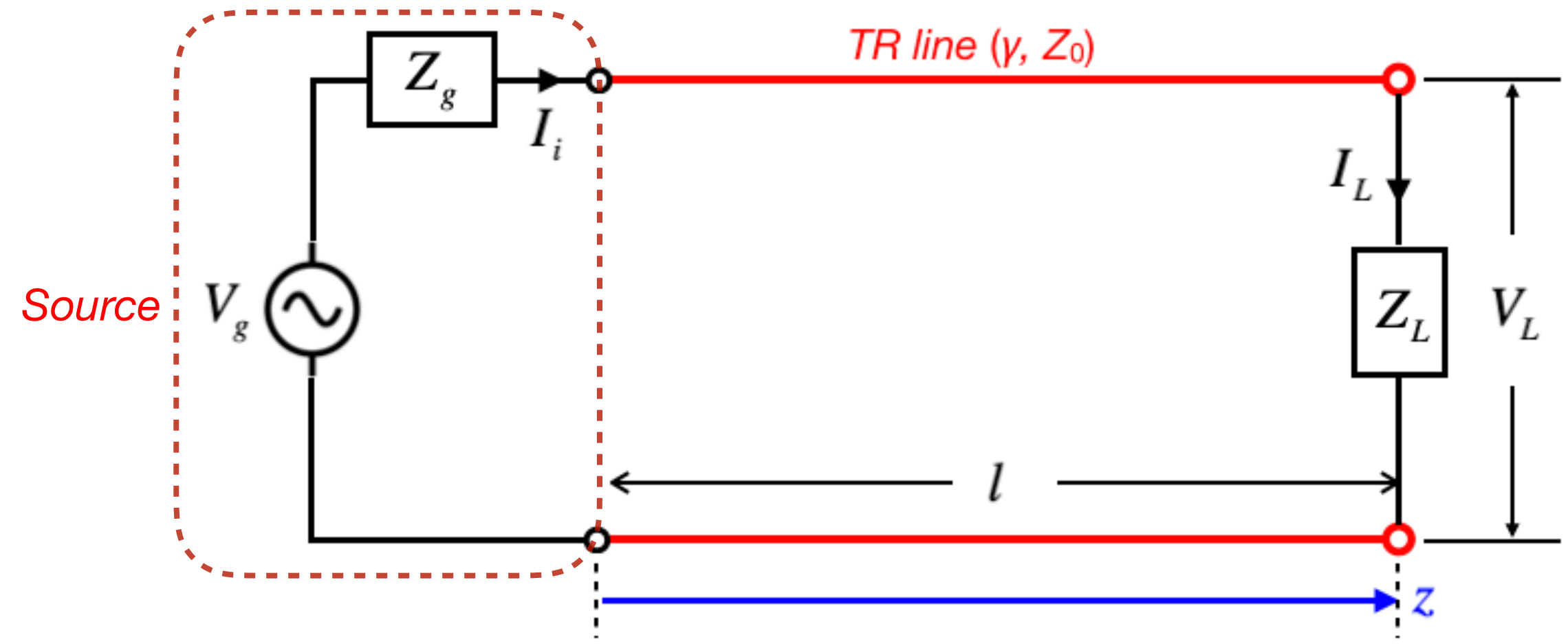Z_0 : characteristic impedance of TR line



<Equivalent circuit for finite transmission line>

• *What to do to know $V(z)$ and $I(z)$?*

- Solving for 4 unknowns (V_0^+ , V_0^- , I_0^+ , I_0^-)
- They are partly dependent on each other

Chap. 9 | Circuit model for “finite” TR-line (2/3)

• **General solution for finite-length transmission lines**

- 4 unknowns (V_0^+ , V_0^- , I_0^+ , I_0^-) should be identified

$$\begin{cases} V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \\ I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \end{cases} \dots(1)$$

- Express “unknowns” vs. V and I at the load end ($z = l$)


- At $z = l$, we have

$$\begin{cases} V(l) = V_L = V_0^+ e^{-\gamma l} + V_0^- e^{\gamma l} \\ I(l) = I_L = \frac{V_0^+}{Z_0} e^{-\gamma l} - \frac{V_0^-}{Z_0} e^{\gamma l} \end{cases} \text{ where } \frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = Z_0$$

- Express **unknown V_0^+ and V_0^-** vs. V_L and I_L

$$\begin{cases} V_0^+ = \frac{1}{2}(V_L + I_L Z_0) e^{\gamma l} = \frac{1}{2} I_L (Z_L + Z_0) e^{\gamma l} \\ V_0^- = \frac{1}{2}(V_L - I_L Z_0) e^{-\gamma l} = \frac{1}{2} I_L (Z_L - Z_0) e^{-\gamma l} \end{cases} \dots(2)$$

$$V_L = I_L Z_L$$

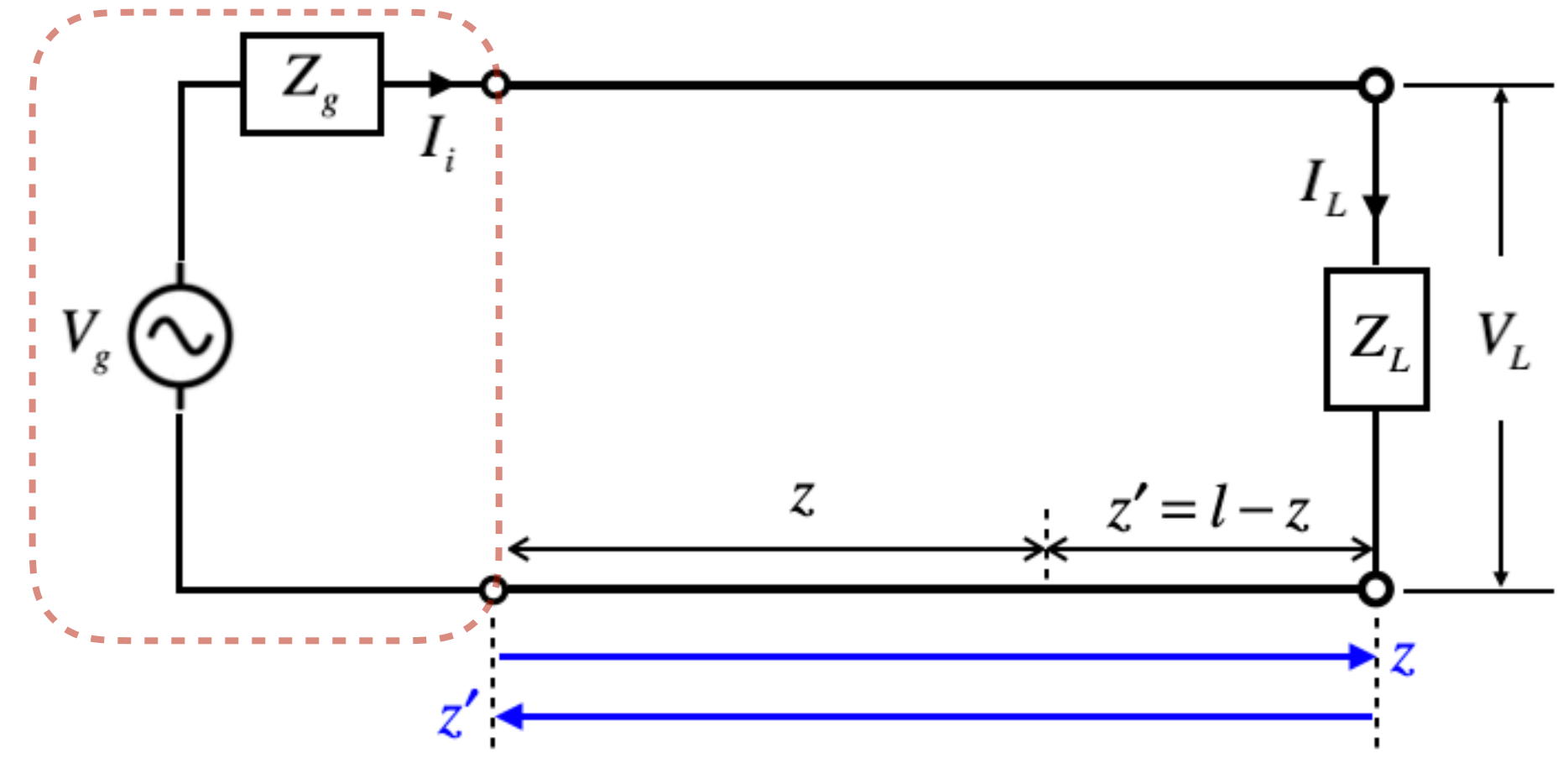

- If we substitute **eqn. (2)** into **(1)**, we get

$$\begin{cases} V(z) = \frac{I_L}{2} [(Z_L + Z_0) e^{\gamma(l-z)} + (Z_L - Z_0) e^{-\gamma(l-z)}] \\ I(z) = \frac{I_L}{2Z_0} [(Z_L + Z_0) e^{\gamma(l-z)} - (Z_L - Z_0) e^{-\gamma(l-z)}] \end{cases}$$

• Voltage and current at **z (distance from source)** are expressed in terms of Z_0 and Z_L and I

- Equivalent expression with **$z' = l - z$ (distance from load):**

$$\begin{cases} V(z') = \frac{I_L}{2} [(Z_L + Z_0) e^{\gamma z'} + (Z_L - Z_0) e^{-\gamma z'}] \\ I(z') = \frac{I_L}{2Z_0} [(Z_L + Z_0) e^{\gamma z'} - (Z_L - Z_0) e^{-\gamma z'}] \end{cases}$$


(Note: z and z' dependence on V and I are different!)

Chap. 9 | Circuit model for "finite" TR-line (3/3)

• **General solution for finite-length transmission lines**

- Simplified form by using hyperbolic functions
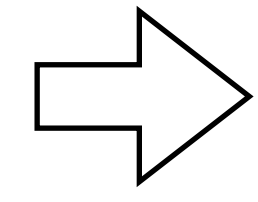
$$\begin{cases} V(z') = \frac{I_L}{2} [(Z_L + Z_0)e^{\gamma z'} + (Z_L - Z_0)e^{-\gamma z'}] \\ I(z') = \frac{I_L}{2Z_0} [(Z_L + Z_0)e^{\gamma z'} - (Z_L - Z_0)e^{-\gamma z'}] \end{cases}$$



($\because e^{\gamma z'} + e^{-\gamma z'} = 2 \cosh \gamma z'$ and $e^{\gamma z'} - e^{-\gamma z'} = 2 \sinh \gamma z'$)

$$\begin{aligned} V(z') &= I_L [Z_L \cosh \gamma z' + Z_0 \sinh \gamma z'] \\ I(z') &= \frac{I_L}{Z_0} [Z_L \sinh \gamma z' + Z_0 \cosh \gamma z'] \end{aligned}$$

Can find voltage and current at any z' using $I_L, Z_L, \gamma, Z_0!$



• **Input impedance**

- $Z(z') = V(z')/I(z')$: Impedance **looking "toward"** the load end from z'

$$\begin{aligned} Z(z') &= \frac{V(z')}{I(z')} = Z_0 \frac{Z_L \cosh \gamma z' + Z_0 \sinh \gamma z'}{Z_L \sinh \gamma z' + Z_0 \cosh \gamma z'} \\ &= Z_0 \frac{Z_L + Z_0 \tanh \gamma z'}{Z_0 + Z_L \tanh \gamma z'} \quad (\Omega) \end{aligned}$$

- At the source end ($z' = l$), the source sees an input impedance
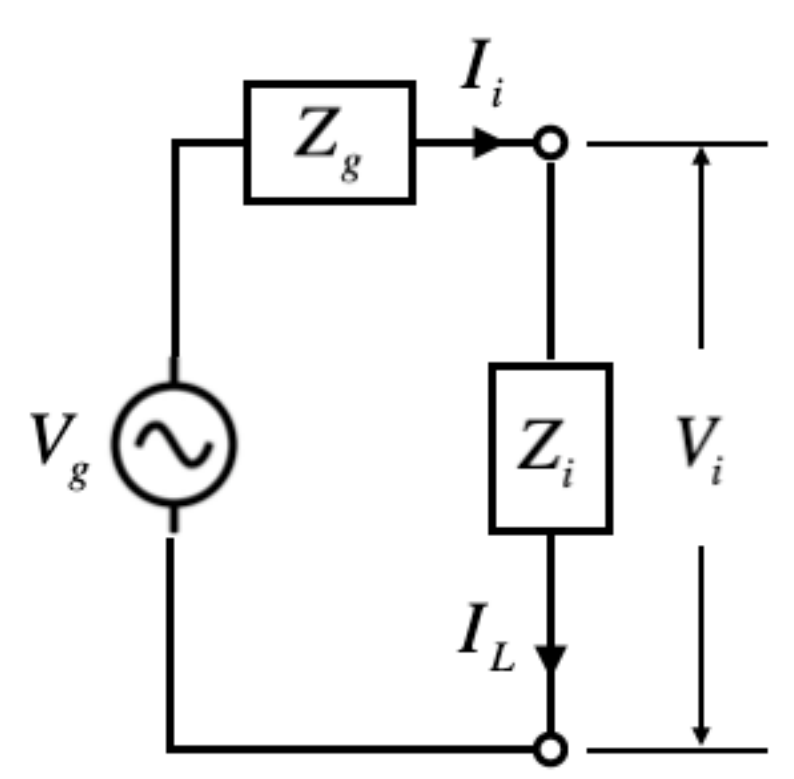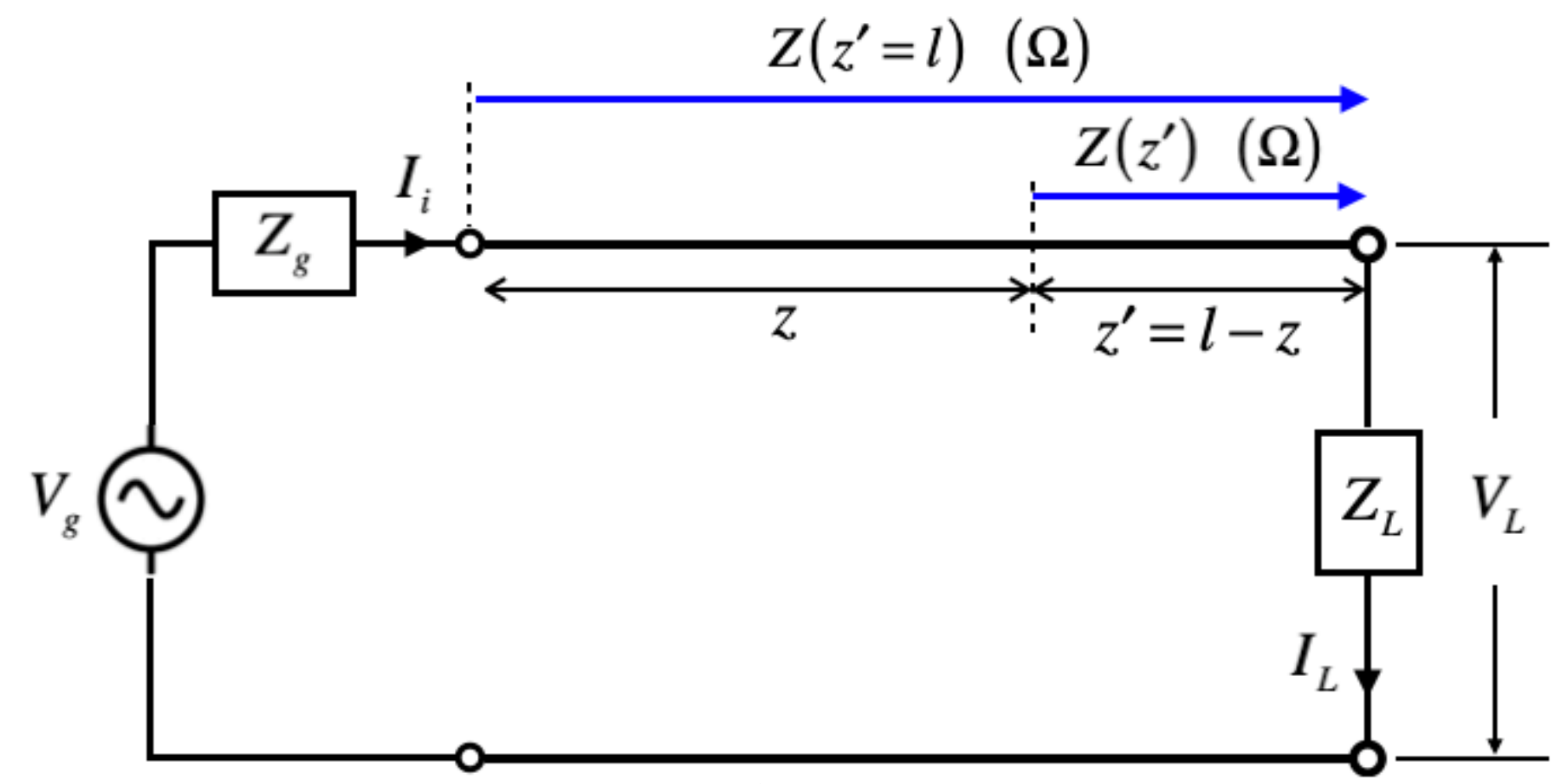
$$\left[(Z)_{z'=l} = (Z)_{z=0} \right] \triangleq Z_i = Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} \quad (\Omega)$$



- $Z_i =$ Finite TR-line + load L
- V_i and I_i easily obtainable!

Chap. 9 | Impedance matching condition 1: Reflection-less

- “Reflection-less” impedance-matching condition


- load impedance (Z_L) = characteristic impedance of the line (Z_0)

- input impedance Z_i becomes Z_0 as below

$$Z_i = Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} = Z_0 \quad (\Omega)$$

- Under such condition where $Z_L = Z_0$, Voltage and current expressions become
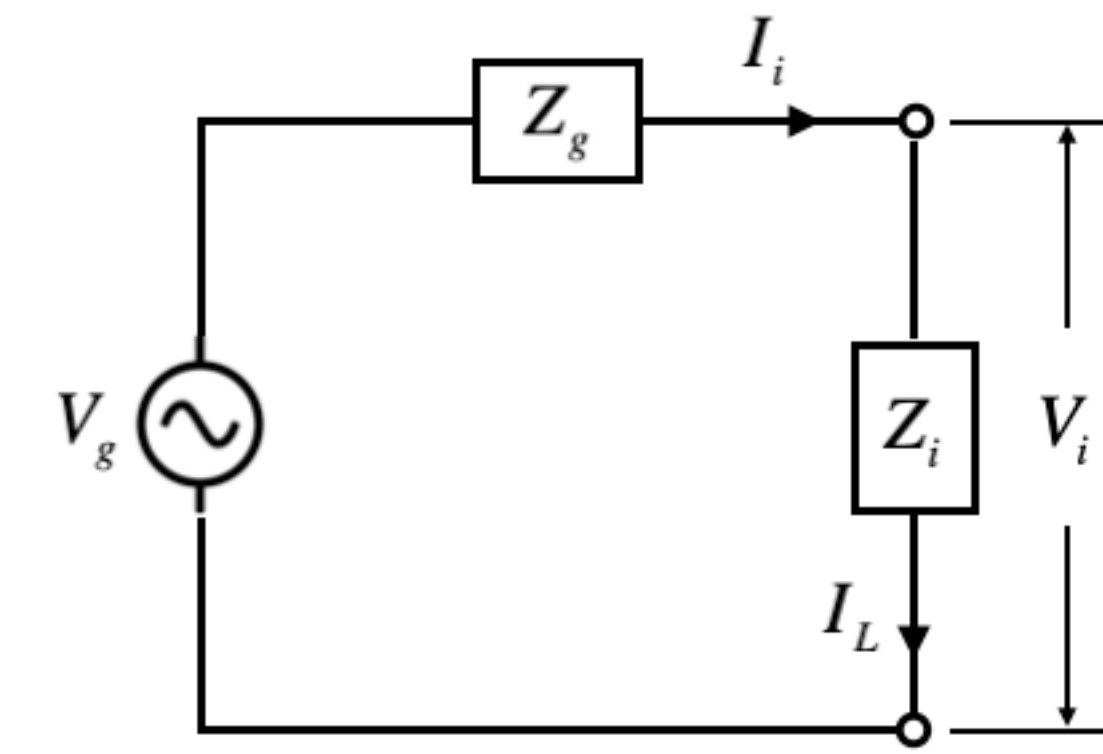
$$\begin{cases} V(z) = \frac{I_L}{2} [(Z_L + Z_0)e^{\gamma(l-z)} + (Z_L - Z_0)e^{-\gamma(l-z)}] = (I_L Z_0 e^{\gamma l}) e^{-\gamma z} = V_i e^{-\gamma z} \\ I(z) = \frac{I_L}{2Z_0} [(Z_L + Z_0)e^{\gamma(l-z)} - (Z_L - Z_0)e^{-\gamma(l-z)}] = (I_L e^{\gamma l}) e^{-\gamma z} = I_i e^{-\gamma z} \end{cases}$$



→ Wave only traveling in +z direction, **no reflected wave! (in -z direction)**

∴ When a finite TR-line terminated with its characteristic impedance ($Z_L = Z_0$), its $V(z)$ and $Z(z)$ are the same as if **the line is extended to infinity**

Reflection-less condition

$$Z_L = Z_0 \quad (\Omega)$$

Chap. 9 | Impedance matching condition 2: Maximum power transfer

• *Impedance matching for maximum power transfer*

- Input impedance (Z_i) = Complex conjugate of internal impedance of the source (Z_g^*)

→ *Maximum power transfer! (Proof as below)*

$(P_{av})_L = (P_{av})_i = \frac{1}{2} \text{Re}[V_i I_i^*]$ *Output power = Input power delivered to input terminal (assuming "lossless" TR-line)*


(see right figure →) $= \frac{1}{2} \text{Re} \left[\frac{V_g V_g^* Z_i}{(Z_g + Z_i)(Z_g + Z_i)^*} \right] = \frac{1}{2} \frac{|V_g|^2 R_i}{(R_g + R_i)^2 + (X_g + X_i)^2}$

where $Z_g = R_g + jX_g$ and $Z_i = R_i + jX_i$

To maximize output power: [i.e. $\max(P_{av})_L$]

$$\begin{cases} \frac{\partial(P_{av})_L}{\partial R_i} = 0 \rightarrow R_i = R_g \\ \frac{\partial(P_{av})_L}{\partial X_i} = 0 \rightarrow X_i = -X_g \end{cases}$$

Power dissipation: $(P_{av})_L = (P_{av})_G = \frac{|V_g|^2}{8R_g}$ *(50 % of the generated power!)*

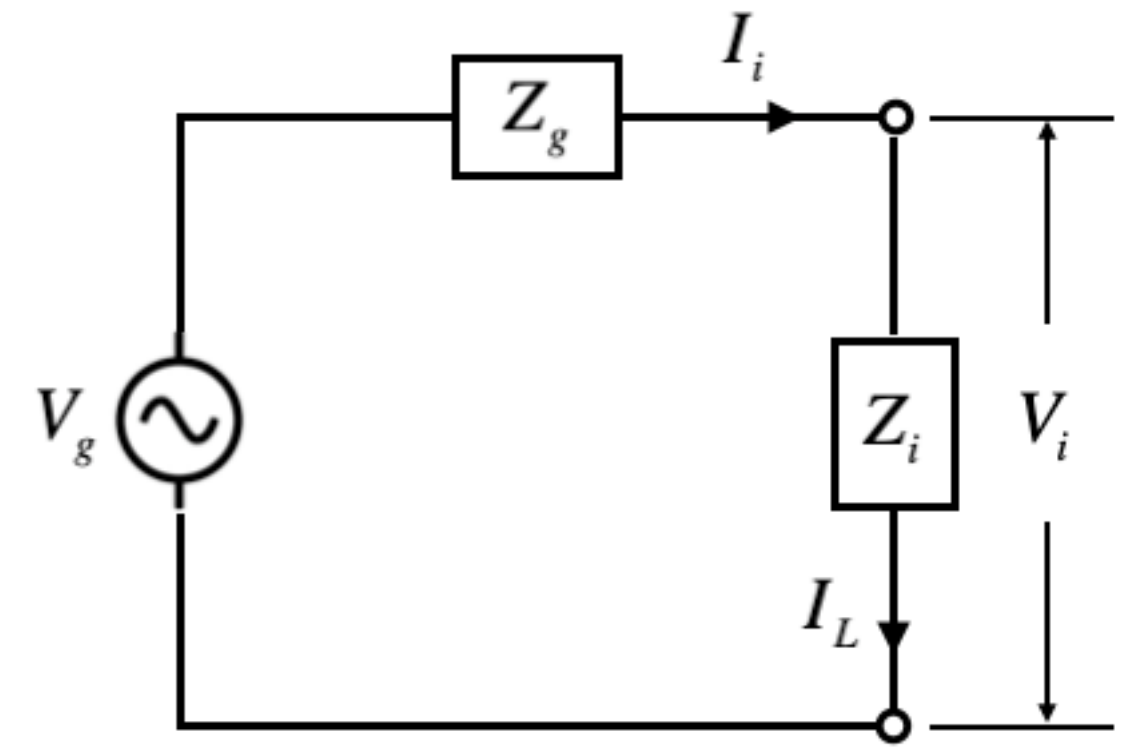

$$\begin{cases} V_i = \frac{Z_i}{Z_g + Z_i} V_g \\ I_i = \frac{V_g}{Z_g + Z_i} \end{cases}$$

Maximum power-transfer matching


$Z_i = R_i + jX_i = R_g - jX_g \triangleq Z_g^*$
 $\therefore Z_i = Z_g^*$

Chap. 9 | Input impedance vs. load impedance (Open-circuit)

• *Open-circuit = infinite load impedance* ($Z_L \rightarrow \infty$)

- For simplicity, let's assume "lossless" TR-line represented by
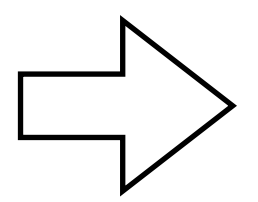
$$\begin{cases} \gamma = j\beta \\ Z_0 = R_0 \end{cases}$$



Then, input impedance given by


$$Z_i = Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} = R_0 \frac{Z_L + jR_0 \tan \beta l}{R_0 + jZ_L \tan \beta l} \quad (\Omega)$$

$$(\because \tanh(\gamma l) = \tanh(j\beta l) = j \tan(\beta l))$$

- Input impedance with $Z_L \rightarrow \infty$

$$\lim_{Z_L \rightarrow \infty} Z_i = \lim_{Z_L \rightarrow \infty} R_0 \frac{Z_L + jR_0 \tan \beta l}{R_0 + jZ_L \tan \beta l} = \frac{R_0}{j \tan \beta l} = -jR_0 \cot \beta l \quad (\Omega) \rightarrow \text{Purely imaginary [reactive] (either *capacitive* or *inductive*)}$$

$$Z_i = jX_i = -jR_0 \cot \beta l$$

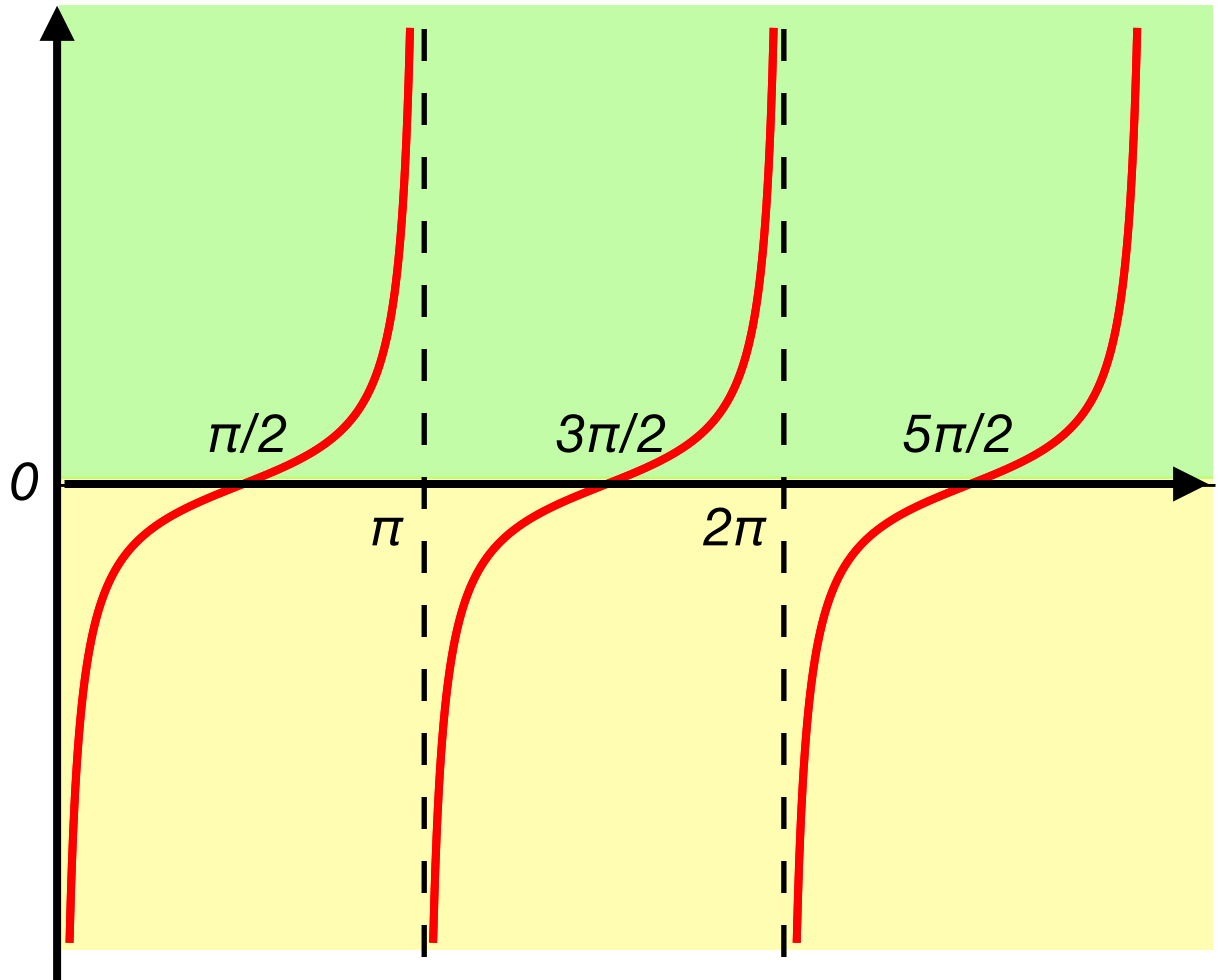

upper: inductive

upper: capacitive

- Depending on choice of length l , input impedance can be modified
- For **O.C. TR-line with very short length (l) comparable to wavelength,**

$$\beta l = \frac{2\pi l}{\lambda} \ll 1 \rightarrow \lim_{Z_L \rightarrow \infty} Z_i = \frac{R_0}{j \tan \beta l} \cong \frac{R_0}{j\beta l} = -j \frac{\sqrt{L/C}}{\omega \sqrt{LC} l} = -j \frac{1}{\omega C l}$$

$$\because \beta = \omega \sqrt{LC}, R_0 = \sqrt{\frac{L}{C}}$$


Purely Capacitive!

Chap. 9 | Input impedance vs. load impedance (short-circuit)

• Short circuit = zero load impedance ($Z_L = 0$)

- Input impedance with $Z_L = 0$
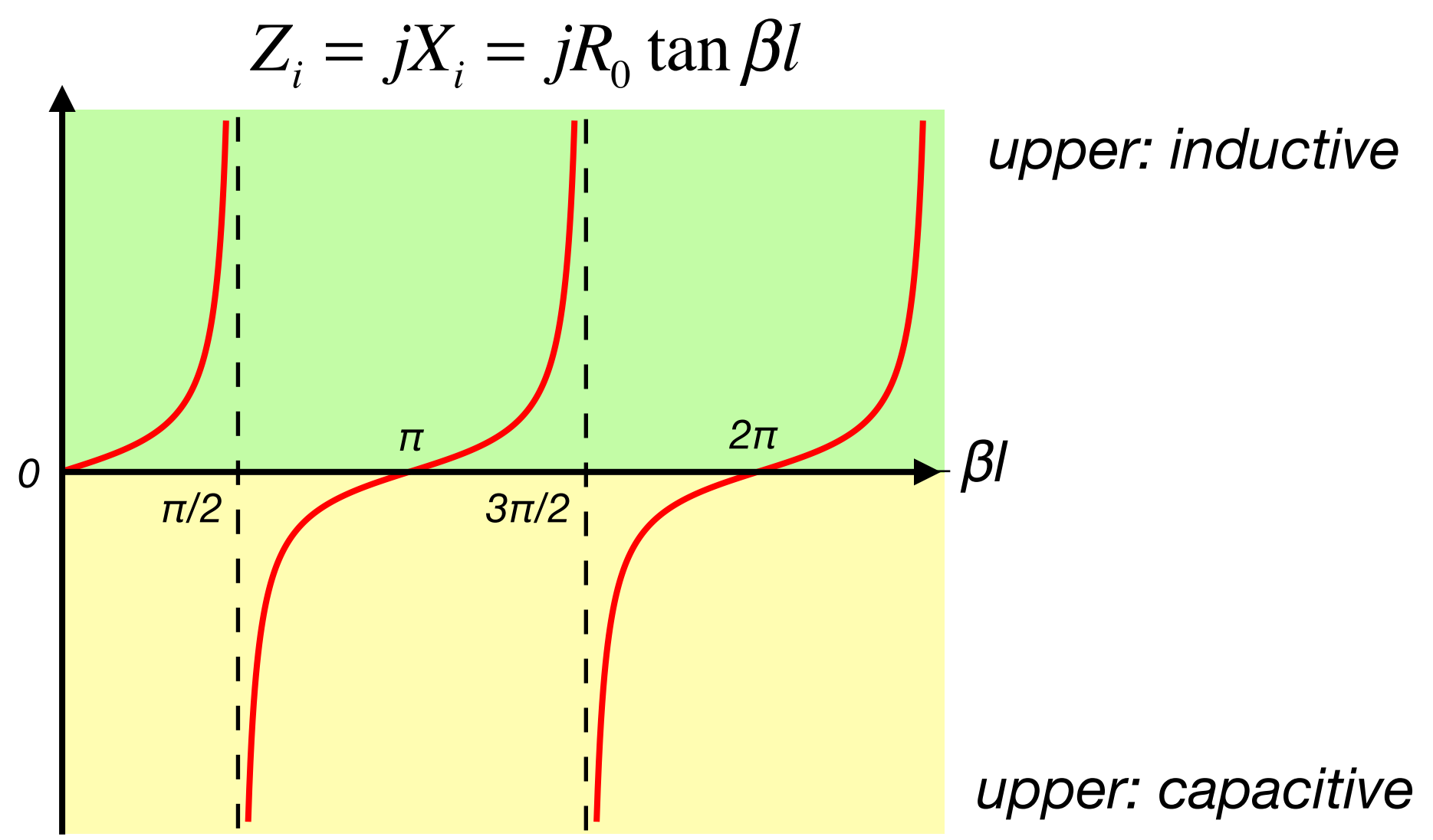
$$\lim_{Z_L \rightarrow 0} Z_i = \lim_{Z_L \rightarrow 0} R_0 \frac{Z_L + jR_0 \tan \beta l}{R_0 + jZ_L \tan \beta l} = jR_0 \tan \beta l \quad (\Omega)$$



- Depending on choice of length l , input impedance can be modified
- For S.C. TR-line with very short length (l) comparable to wavelength,

$$\beta l = \frac{2\pi l}{\lambda} \ll 1 \quad \rightarrow \quad \lim_{Z_L \rightarrow \infty} Z_i = jR_0 \tan \beta l \cong jR_0 \beta l = j \sqrt{\frac{L}{C}} \omega \sqrt{LC} l = \boxed{j\omega L l}$$

Purely inductive!

$\because \beta = \omega \sqrt{LC}, \quad R_0 = \sqrt{\frac{L}{C}}$

Chap. 9 | Input impedance vs. TR-line length

• “Quarter-wave” TR-line


- Length of the line, $l =$ odd multiple of $\lambda/4$

$$l = (2n - 1) \frac{\lambda}{4}, \quad (n = 1, 2, 3, \dots) \quad \text{Then, } \beta l = \frac{2\pi}{\lambda} \cdot (2n - 1) \frac{\lambda}{4} = (2n - 1) \frac{\pi}{2} \rightarrow \tan \beta l = \tan \left[(2n - 1) \frac{\pi}{2} \right] \rightarrow \pm\infty$$

$$\therefore \lim_{\tan(\beta l) \rightarrow \pm\infty} Z_i = \lim_{\tan(\beta l) \rightarrow \pm\infty} R_0 \frac{Z_L + jR_0 \tan \beta l}{R_0 + jZ_L \tan \beta l} = \frac{R_0^2}{Z_L} \quad (\Omega)$$

Quarter-wave lines
= Impedance inverter ($1/Z_L$)

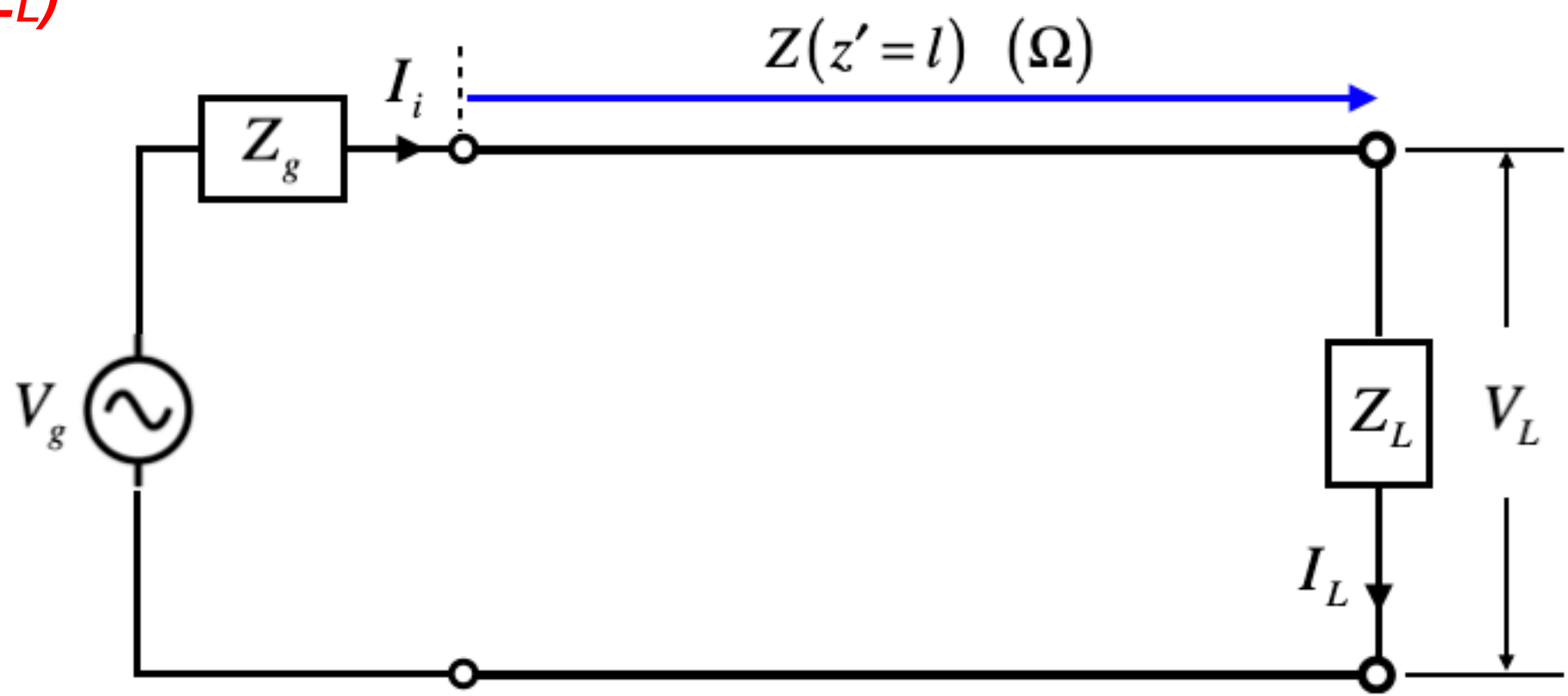- If load impedance $Z_L \rightarrow \infty$ (Open), $Z_i \rightarrow 0$ (Short)
- If load impedance $Z_L \rightarrow 0$ (short), $Z_i \rightarrow \infty$ (Open)




• “Half-wave” TR-line

- Length of the line, $l =$ integer multiple of $\lambda/2$

$$l = \frac{n}{2} \lambda, \quad (n = 1, 2, 3, \dots) \quad \text{Then, } \beta l = \frac{2\pi}{\lambda} \cdot \left(\frac{n\lambda}{2} \right) = n\pi \rightarrow \tan \beta l = 0$$

$$\therefore \lim_{\tan(\beta l) \rightarrow 0} Z_i = \lim_{\tan(\beta l) \rightarrow 0} R_0 \frac{Z_L + jR_0 \tan \beta l}{R_0 + jZ_L \tan \beta l} = Z_L \quad (\Omega)$$

half-wave lines

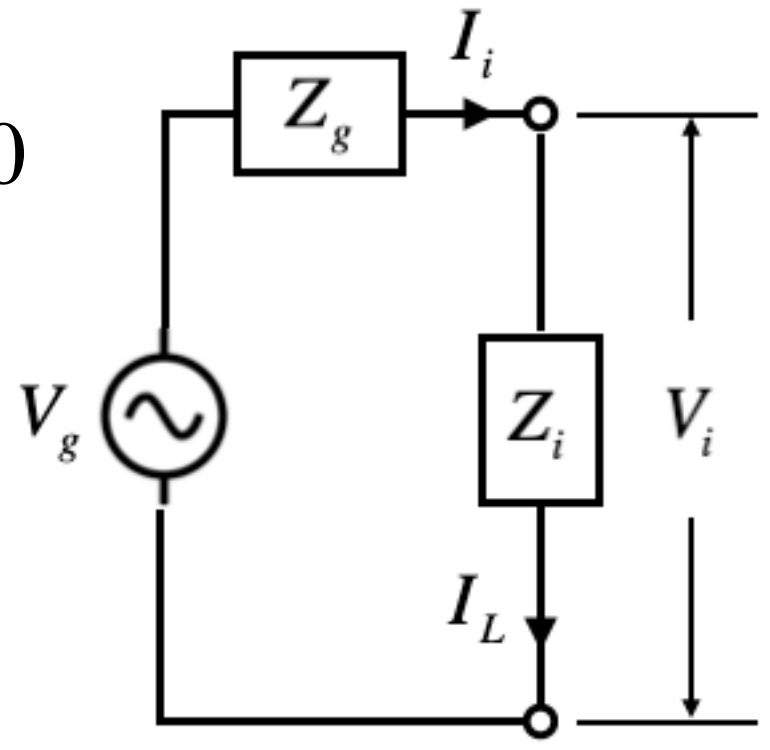

Chap. 9 | TR-line characteristics vs. input impedance

• Determination of TR-line characteristics

- TR-line represented by Z_0 (characteristic impedance) and γ (propagation constant)
- Can be obtained by measuring input impedance Z_i under open & short-circuit condition

$$\text{Open-circuit: } Z_L \rightarrow \infty \Rightarrow Z_{io} = Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} = Z_0 \coth \gamma l \quad (\Omega) \quad Z_{io} \cdot Z_{is} = Z_0^2 \tanh \gamma l \cdot \coth \gamma l = Z_0^2 \rightarrow \boxed{\therefore Z_0 = \sqrt{Z_{io} \cdot Z_{is}}}$$

$$\text{Short-circuit: } Z_L = 0 \Rightarrow Z_{is} = Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} = Z_0 \tanh \gamma l \quad (\Omega) \quad \frac{Z_{is}}{Z_{io}} = \tanh^2 \gamma l \rightarrow \boxed{\therefore \gamma = \frac{1}{l} \tanh^{-1} \sqrt{\frac{Z_{is}}{Z_{io}}}}$$

These apply to lossy TR-line as well!

• Input impedance for a “lossy” and “short-circuited” TR-line

- Lossy $\rightarrow \gamma = \alpha + j\beta$
- Short-circuit $\rightarrow Z_L = 0$

$$\begin{aligned} Z_{is} &= Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} = Z_0 \tanh \gamma l \\ &= Z_0 \frac{\sinh(\alpha + j\beta)l}{\cosh(\alpha + j\beta)l} \\ &= Z_0 \frac{\sinh(\alpha l) \cos(\beta l) + j \cosh(\alpha l) \sin(\beta l)}{\cosh(\alpha l) \cos(\beta l) + j \sinh(\alpha l) \sin(\beta l)} \end{aligned}$$

Simple hyperbolic math!

$$\begin{cases} \cosh(a+b) = \cosh(a)\cosh(b) + \sinh(a)\sinh(b) \\ \sinh(a+b) = \sinh(a)\cosh(b) + \cosh(a)\sinh(b) \end{cases}$$

$$\begin{cases} \cosh(ja) = \cos a \\ \sinh(ja) = j \sin a \end{cases}$$

Chap. 9 | Lossy TR-line

$$Z_{is} = Z_0 \frac{\sinh(\alpha l) \cos(\beta l) + j \cosh(\alpha l) \sin(\beta l)}{\cosh(\alpha l) \cos(\beta l) + j \sinh(\alpha l) \sin(\beta l)}$$

• **“lossy” and “short-circuited” TR-line (realistic case)**

- For a half-wave line

$$l = \frac{n}{2} \lambda, \quad (n = 1, 2, 3, \dots) \quad \beta l = \frac{2\pi}{\lambda} \cdot \left(\frac{n\lambda}{2}\right) = n\pi \quad \rightarrow \quad \sin \beta l = 0 \quad \rightarrow \quad Z_{is} = Z_0 \tanh(\alpha l) \cong \boxed{Z_0 \alpha l}$$

Small, but non-zero

- For a quarter-wave line

$$l = (2n-1) \frac{\lambda}{4}, \quad (n = 1, 2, 3, \dots) \quad \beta l = \frac{2\pi}{\lambda} \cdot (2n-1) \frac{\lambda}{4} = (2n-1) \frac{\pi}{2} \quad \rightarrow \quad \cos \beta l = 0 \quad \rightarrow \quad Z_{is} = \frac{Z_0}{\tanh(\alpha l)} \cong \boxed{\frac{Z_0}{\alpha l}}$$

Large, but finite

- Both assumed low loss condition, $\alpha l \ll 1$.

• **“lossless” and “short-circuited” TR-line (Ideal case)**

- For a half-wave line

$$\lim_{\tan(\beta l) \rightarrow 0} Z_i = \lim_{\tan(\beta l) \rightarrow 0} R_0 \frac{Z_L + jR_0 \tan \beta l}{R_0 + jZ_L \tan \beta l} = Z_L \quad \rightarrow \quad \boxed{0}$$

Zero

- For a quarter-wave line

$$\lim_{\tan(\beta l) \rightarrow \pm\infty} Z_i = \lim_{\tan(\beta l) \rightarrow \pm\infty} R_0 \frac{Z_L + jR_0 \tan \beta l}{R_0 + jZ_L \tan \beta l} = \frac{R_0^2}{Z_L} \quad \rightarrow \quad \boxed{\infty}$$

Infinity

	Half-wave line	Quarter-wave line
Impedance at resonance	Minimum (0 for lossless)	Maximum (∞ for lossless)
Frequency dependent	Band-pass	Band-stop
Similarity	Series-RLC resonant circuit	Parallel-RLC resonant circuit