

Electromagnetics

<Chap. 9> Transmission Lines

Section 9.4 ~ 9.5

(1st of week 11)

Jaesang Lee

Dept. of Electrical and Computer Engineering

Seoul National University

(email: jsanglee@snu.ac.kr)

Chap. 9 | Contents for 1st class of week 11

Sec 4. Wave characteristics on Finite Transmission Lines (Cont'd)

- Standing wave ratio
- Resistive termination & arbitrary termination of TR-line
- Wave behavior observed from source

Chap. 9 | Voltage reflection coefficient

- Voltage reflection coefficient

- Under non-matching condition ($Z_L \neq Z_0$)

$$V(z') = \frac{I_L}{2} \left[\underbrace{(Z_L + Z_0) e^{\gamma z'}}_{\text{Incident}} + \underbrace{(Z_L - Z_0) e^{-\gamma z'}}_{\text{Reflected}} \right]$$

$$= \frac{I_L}{2} (Z_L + Z_0) e^{\gamma z'} \left[1 + \frac{Z_L - Z_0}{Z_L + Z_0} e^{-2\gamma z'} \right]$$


$$\therefore V(z') = \frac{I_L}{2} (Z_L + Z_0) e^{\gamma z'} [1 + \Gamma e^{-2\gamma z'}]$$

Where $\Gamma \triangleq \frac{Z_L - Z_0}{Z_L + Z_0}$: **Voltage reflection coefficient**

Here, $\Gamma \triangleq \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma| e^{j\theta_\Gamma}$

- Ratio of complex amplitude of *reflected / incident wave*

- $|\Gamma| \leq 1$ (magnitude)

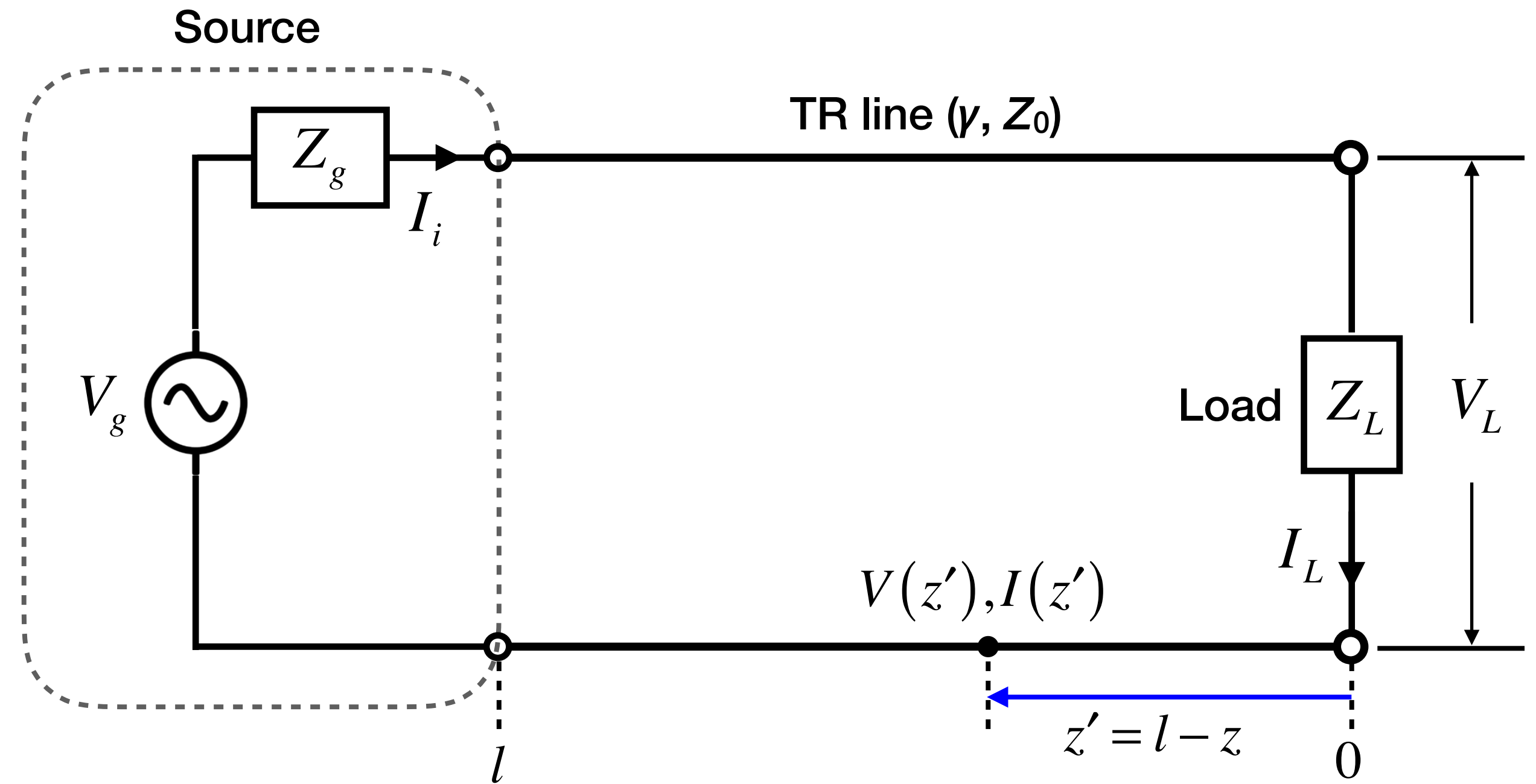

Chap. 9 | Standing wave ratio (SWR) [1/2]

- Standing wave ratio (SWR) for lossless TR-line

- Lossless TR-line $\rightarrow \gamma = j\beta$ and $Z_0 = R_0$


$$V(z') = \frac{I_L}{2}(Z_L + Z_0)e^{\gamma z'} [1 + \Gamma e^{-2\gamma z'}]$$

$$\begin{aligned} \rightarrow V(z') &= \frac{I_L}{2}(Z_L + R_0)e^{j\beta z'} [1 + \Gamma e^{-j2\beta z'}] \quad (\because \gamma = j\beta \text{ and } Z_0 = R_0) \\ &= \frac{I_L}{2}(Z_L + R_0)e^{j\beta z'} [1 + |\Gamma|e^{j(\theta_\Gamma - 2\beta z')}] \quad (\because \Gamma = |\Gamma|e^{-j\theta_\Gamma}) \end{aligned}$$

- Magnitude of voltage $V(z')$ oscillating between its maxima and minima

$$|V(z')| = \underbrace{\left|\frac{I_L}{2}\right|}_{\text{Const.}} \cdot \underbrace{|Z_L + R_0|}_{\text{Const.}} \cdot \underbrace{|e^{j\beta z'}|}_{?} \cdot \underbrace{|1 + |\Gamma|e^{j(\theta_\Gamma - 2\beta z')}|}_{\text{Oscillating due to } z'}$$

$$\begin{cases} \max|V(z')| = V_{\max} = \left|\frac{I_L}{2}\right| \cdot |Z_L + R_0| \cdot (1 + |\Gamma|) \\ \min|V(z')| = V_{\min} = \left|\frac{I_L}{2}\right| \cdot |Z_L + R_0| \cdot (1 - |\Gamma|) \end{cases}$$

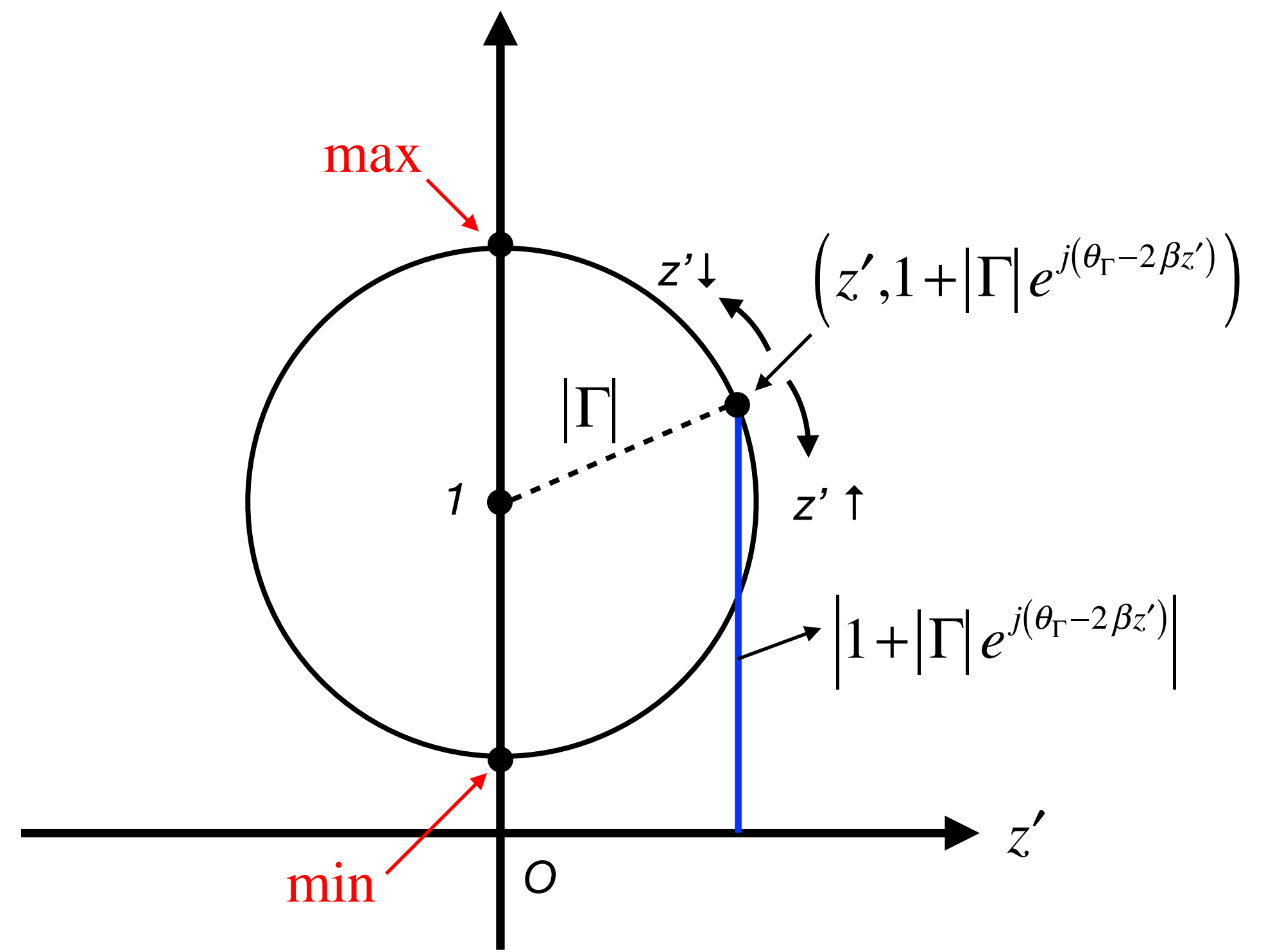

$|\Gamma|$: Radius of a circle

$|1 + |\Gamma|e^{j(\theta_\Gamma - 2\beta z')}|$: distance from origin to the circle

$$SWR \text{ or } S \triangleq \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \iff |\Gamma| = \frac{S - 1}{S + 1}$$

Chap. 9 | Standing wave ratio (SWR) [2/2]



- Standing wave ratio (S) vs. voltage reflection coefficient (Γ)
 - S can be expressed in terms of Γ
 - What is the relationship between two like?

$$S = \frac{V_{\max}}{V_{\min}} = \frac{1+|\Gamma|}{1-|\Gamma|} \rightarrow S = -1 + \frac{2}{1-|\Gamma|}$$

- S **monotonically increases from "1" to "infinity"** with $|\Gamma|$!
 - $|\Gamma| \uparrow \rightarrow S \uparrow$ (high reflection = high SWR)
 - $|\Gamma| \uparrow$: **High reflection** of the wave
 - ✓ **Low** TR-line efficiency
 - ✓ **High power loss** \rightarrow Undesirable!

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \begin{cases} Z_L = Z_0 : \Gamma = 0 \rightarrow S = 1 \text{ Minimum!} \\ \text{(matched)} \\ Z_L = \infty : \Gamma = 1 \rightarrow S = \infty \text{ Undesirable} \\ \text{(Open Circuit)} \\ Z_L = 0 : \Gamma = -1 \rightarrow S = \infty \text{ Undesirable} \\ \text{(Short Circuit)} \end{cases}$$

$\therefore S$ used as a measure how well impedance matched (i.e. $Z_L = Z_0$)

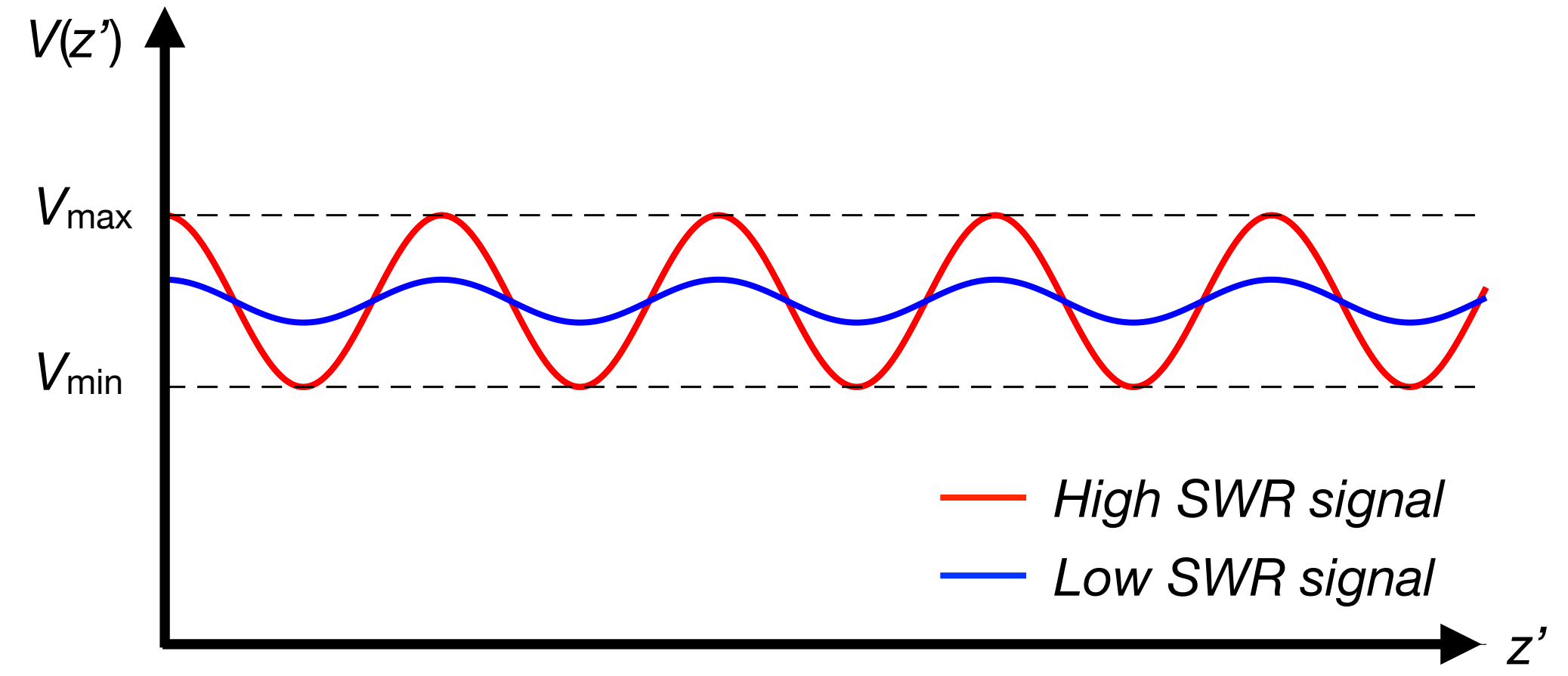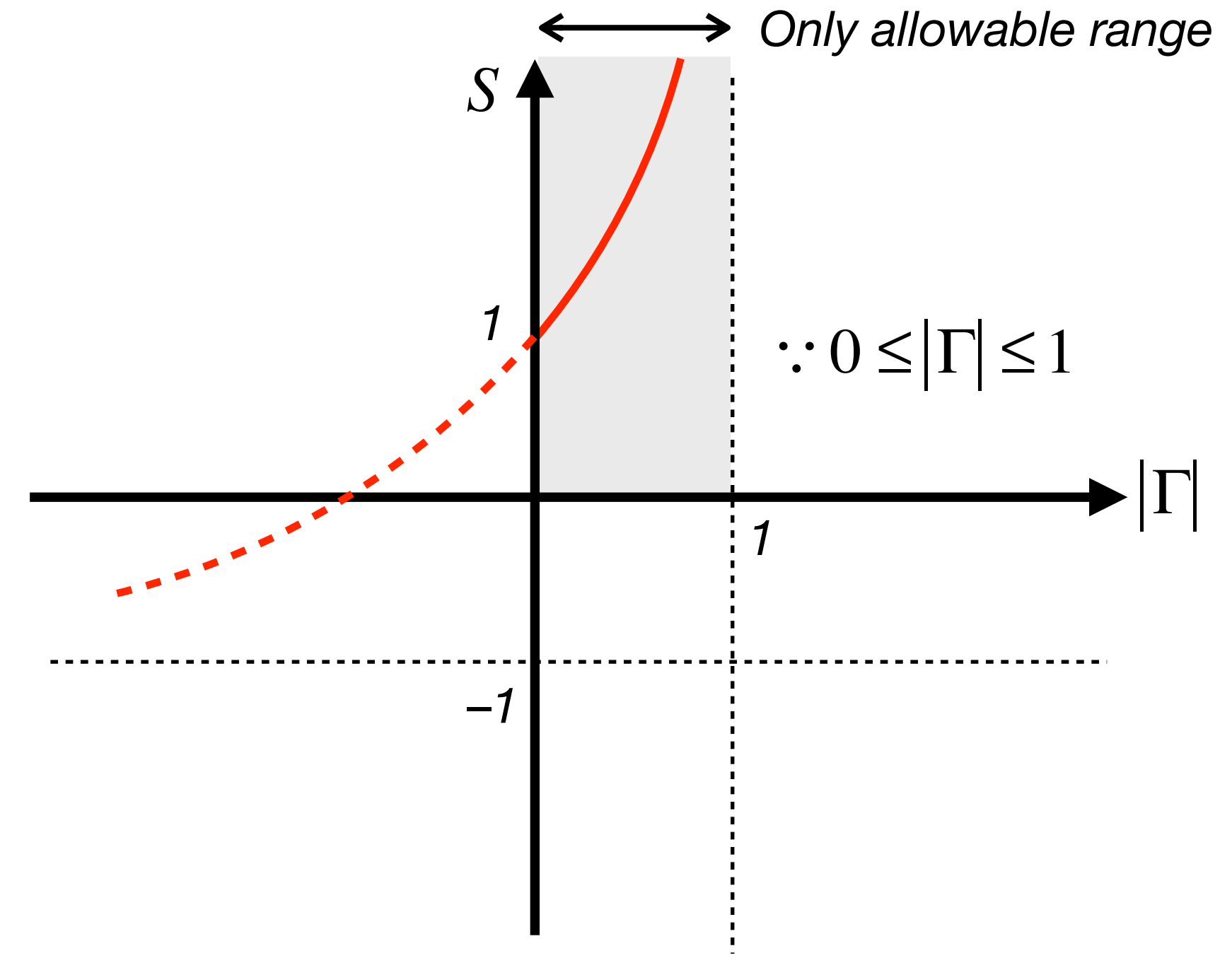

Chap. 9 | Periodicity of V and I [1/2]

- Periodicity of V_{\max} , V_{\min} , I_{\max} , I_{\min}

- V and I are periodic functions with respect to z'

$$\begin{cases} V(z') = \frac{I_L}{2}(Z_L + R_0)e^{j\beta z'} [1 + |\Gamma|e^{j(\theta_\Gamma - 2\beta z')}] \\ I(z') = \frac{I_L}{2R_0}(Z_L + R_0)e^{j\beta z'} [1 - |\Gamma|e^{j(\theta_\Gamma - 2\beta z')}] \end{cases}$$

Even multiple

(Cond. A) $\theta_\Gamma - 2\beta z'_M = -2n\pi, \quad (n = 0, 1, 2, \dots) \rightarrow V_{\max}, I_{\min}$

(Cond. B) $\theta_\Gamma - 2\beta z'_m = -(2n+1)\pi, \quad (n = 0, 1, 2, \dots) \rightarrow V_{\min}, I_{\max}$

Odd multiple

- Resistive termination ($Z_L = R_L$): On TR-line, where we have max and min?

$$\Gamma = \frac{Z_L - R_0}{Z_L + R_0} = \frac{R_L - R_0}{R_L + R_0}$$

Case 1) $R_L > R_0 \rightarrow \Gamma > 0$: Positive real & $\theta_\Gamma = 0$

- At $z' = 0$ (i.e. at the load end)

$\theta_\Gamma - 2\beta z' = 0 \rightarrow$ Satisfying (Cond. A) when $n = 0$
 \rightarrow First V_{\max}, I_{\min}

- At $z' \neq 0$

$\theta_\Gamma - 2\beta z' = -2n\pi, \quad (n = 1, 2, \dots)$

$\rightarrow z'_M = \frac{n\pi}{\beta} = \frac{\lambda\pi}{2\pi}n = n\frac{\lambda}{2}$

\rightarrow Higher order V_{\max}, I_{\min}

Case 2) $R_L < R_0 \rightarrow \Gamma < 0$: Negative real & $\theta_\Gamma = -\pi$

- At $z' = 0$ (i.e. at the load end)

$\theta_\Gamma - 2\beta z' = -\pi \rightarrow$ Satisfying (Cond. B) when $n = 0$
 \rightarrow First V_{\min}, I_{\max}

- At $z' \neq 0$

$\theta_\Gamma - 2\beta z' = -(2n+1)\pi, \quad (n = 1, 2, \dots)$


$\rightarrow z'_m = \frac{n\pi}{\beta} = \frac{\lambda\pi}{2\pi}n = n\frac{\lambda}{2}$

\rightarrow Higher order V_{\min}, I_{\max}

Chap. 9 | Periodicity of V and I [2/2]


Case 1) $R_L > R_0 \rightarrow \Gamma > 0$: Positive real & $\theta_\Gamma = 0$

- At $z' = 0$ (i.e. at the load end)
 - $\theta_\Gamma - 2\beta z' = 0 \rightarrow$ Satisfying (Cond. A) when $n = 0$
 - \rightarrow First V_{max}, I_{min}
- At $z' \neq 0$
 - $\theta_\Gamma - 2\beta z' = -2n\pi, (n = 1, 2, \dots)$
 - $\rightarrow z'_M = \frac{n\pi}{\beta} = \frac{\lambda\pi}{2\pi}n = n\frac{\lambda}{2}$
 - \rightarrow Higher order V_{max}, I_{min}

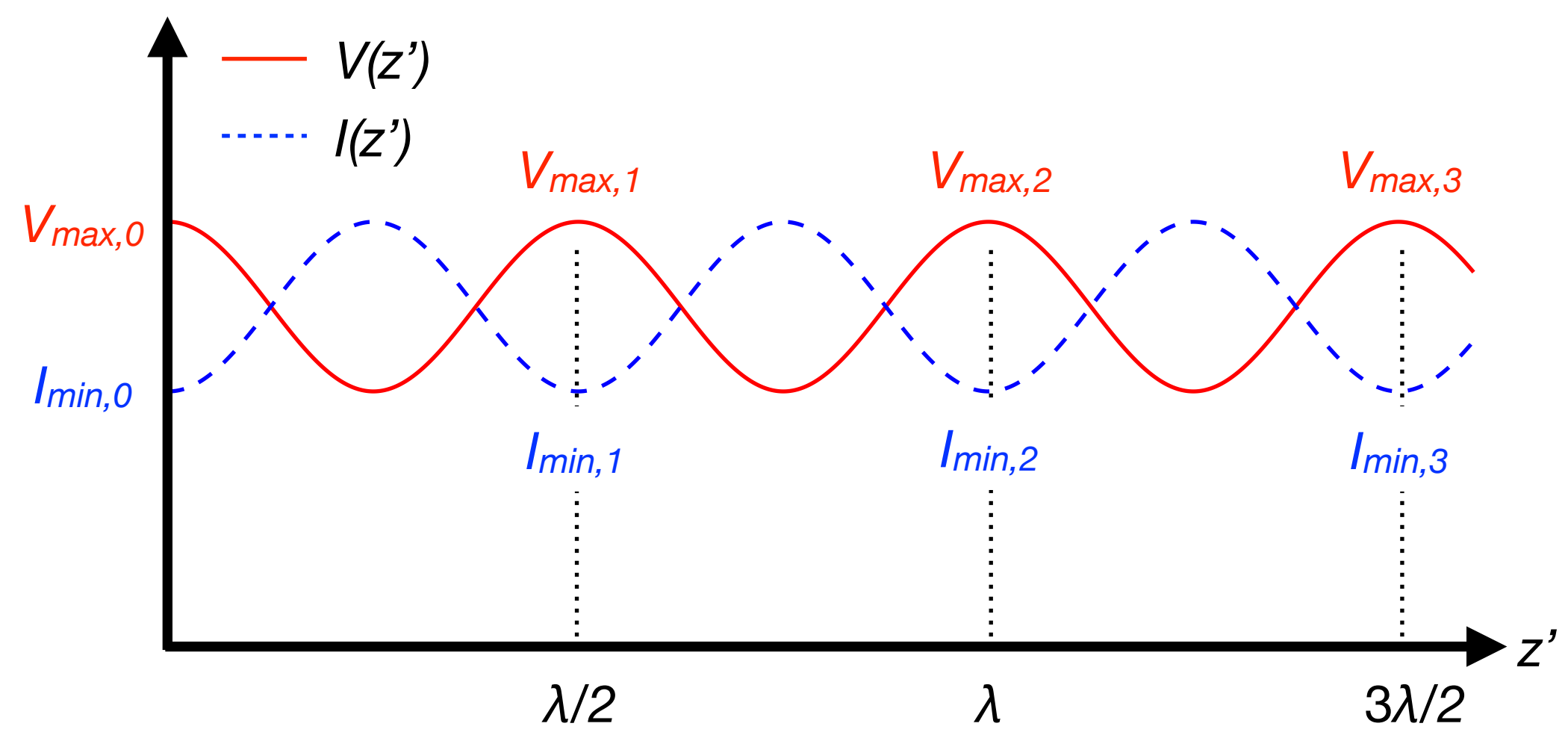

Case 2) $R_L < R_0 \rightarrow \Gamma < 0$: Negative real & $\theta_\Gamma = -\pi$

- At $z' = 0$ (i.e. at the load end)
 - $\theta_\Gamma - 2\beta z' = -\pi \rightarrow$ Satisfying (Cond. B) when $n = 0$
 - \rightarrow First V_{min}, I_{max}
- At $z' \neq 0$
 - $\theta_\Gamma - 2\beta z' = -(2n+1)\pi, (n = 1, 2, \dots)$
 - $\rightarrow z'_M = \frac{n\pi}{\beta} = \frac{\lambda\pi}{2\pi}n = n\frac{\lambda}{2}$
 - \rightarrow Higher order V_{min}, I_{max}

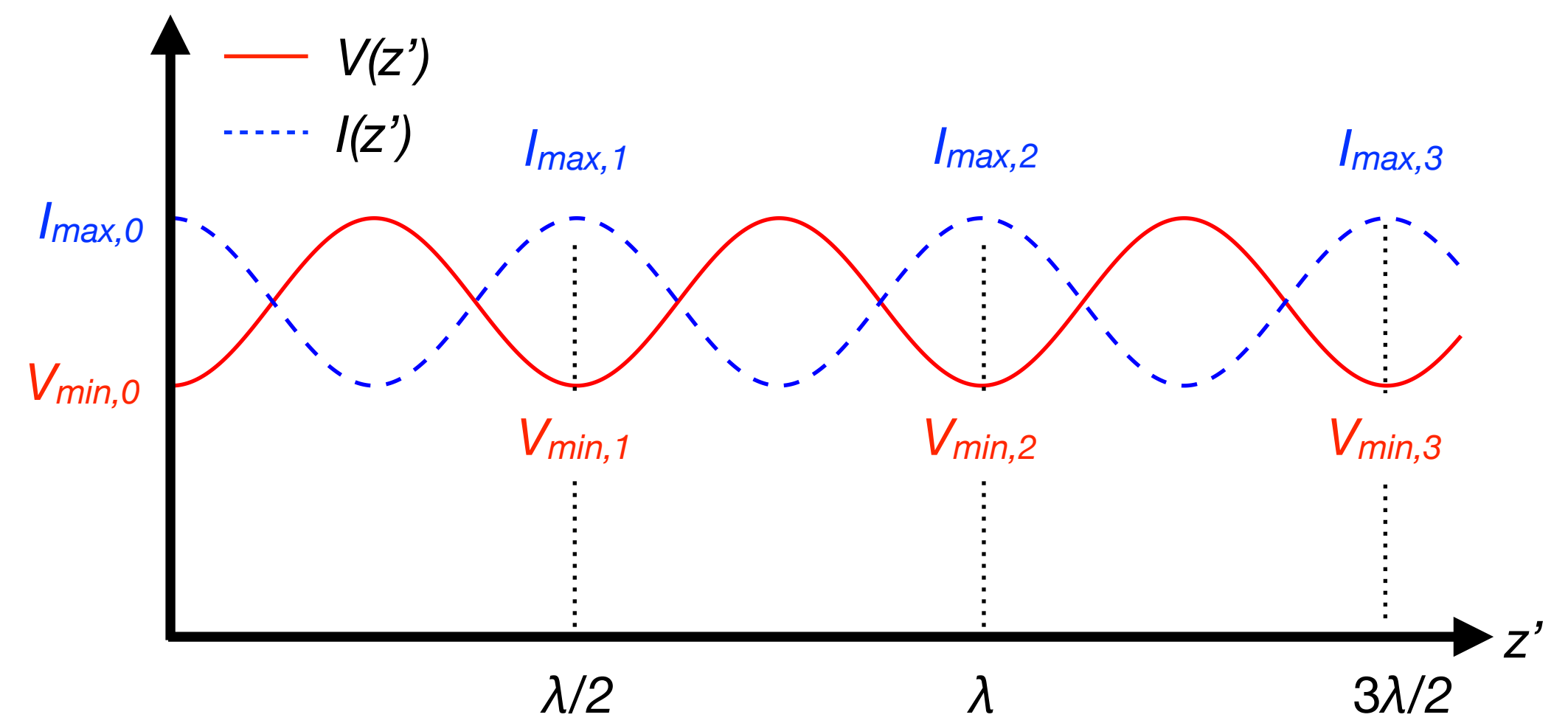

Chap. 9 | Standing wave ratio (SWR) Example

Engineering example We can easily *identify an arbitrary load* ($Z_L = R_L$) at the end of loss TR-line (with characteristic impedance of R_0) *by measuring S*. How to express R_L in terms of S and R_0 ?

$$V(z') = \frac{I_L}{2} [(Z_L + Z_0)e^{\gamma z'} + (Z_L - Z_0)e^{-\gamma z'}] \rightarrow V(z') = \frac{I_L}{2} [(R_L + R_0)e^{j\beta z'} + (R_L - R_0)e^{-j\beta z'}] = I_L (R_L \cos \beta z' + jR_0 \sin \beta z')$$

Case 1) If $R_L > R_0 \rightarrow \Gamma > 0$: Positive real & $\theta_\Gamma = 0$

- A first voltage **maxima**: $z' = 0$

$$\theta_\Gamma - 2\beta z' = 0 = -2n\pi \Big|_{n=0}$$

$$\beta z' = 0 \rightarrow \sin \beta z' = 0 \rightarrow V(0) = V_{\max} = I_L R_L$$

- A first voltage **minima**: $z' = \lambda/4$

$$\beta z' = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2} \rightarrow \cos \beta z' = 0 \rightarrow V\left(\frac{\lambda}{4}\right) = V_{\min} = I_L R_0$$

$$S = \frac{V_{\max}}{V_{\min}} = \frac{I_L R_L}{I_L R_0} = \frac{R_L}{R_0} \rightarrow \therefore R_L = S R_0$$

Case 2) If $R_L < R_0 \rightarrow \Gamma < 0$: Negative real & $\theta_\Gamma = -\pi$

- A first voltage **minima**: $z' = 0$

$$\theta_\Gamma - 2\beta z' = -\pi = -(2n+1)\pi \Big|_{n=0}$$

$$\beta z' = 0 \rightarrow \sin \beta z' = 0 \rightarrow V(0) = V_{\min} = I_L R_L$$

- A first voltage **maxima**: $z' = \lambda/4$

$$\beta z' = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2} \rightarrow \cos \beta z' = 0 \rightarrow V\left(\frac{\lambda}{4}\right) = V_{\max} = I_L R_0$$

$$S = \frac{V_{\max}}{V_{\min}} = \frac{I_L R_0}{I_L R_L} = \frac{R_0}{R_L} \rightarrow \therefore R_L = \frac{R_0}{S}$$

Chap. 9 | Arbitrary termination of TR-line

- “Resistive” termination ($Z_L = R_L$, Previous slides)
 - Voltage minima or maxima at the load end
- “Arbitrary” termination ($Z_L = R_L + jX_L$)
 - Voltage minima or maxima **shifted by d** from the load end
 - If, additional line extended by l_m with resistive termination (R_m)
 - voltage shape does not change! → *Circuit I* = *Circuit II* (Equivalent)


- How do we identify Z_L experimentally?
 - Given condition: we measured S (SWR) and already know R_0
 - **Step 1)** Express Z_L in terms of R_0 and voltage reflection coefficient Γ

$$Z_L = \frac{V(z')}{I(z')} \Big|_{z'=0} = R_0 \frac{1 + |\Gamma| e^{j\theta_\Gamma}}{1 - |\Gamma| e^{j\theta_\Gamma}}$$

- **Step 2)** By applying (Cond. B), we can find θ_Γ for first voltage minima

$$\theta_\Gamma - 2\beta d = -(2n + 1)\pi \Big|_{n=0} \quad \rightarrow \quad \theta_\Gamma = 2\beta d - \pi$$

- **Step 3)** By measuring S , we can get $|\Gamma|$ as $|\Gamma| = \frac{S - 1}{S + 1}$

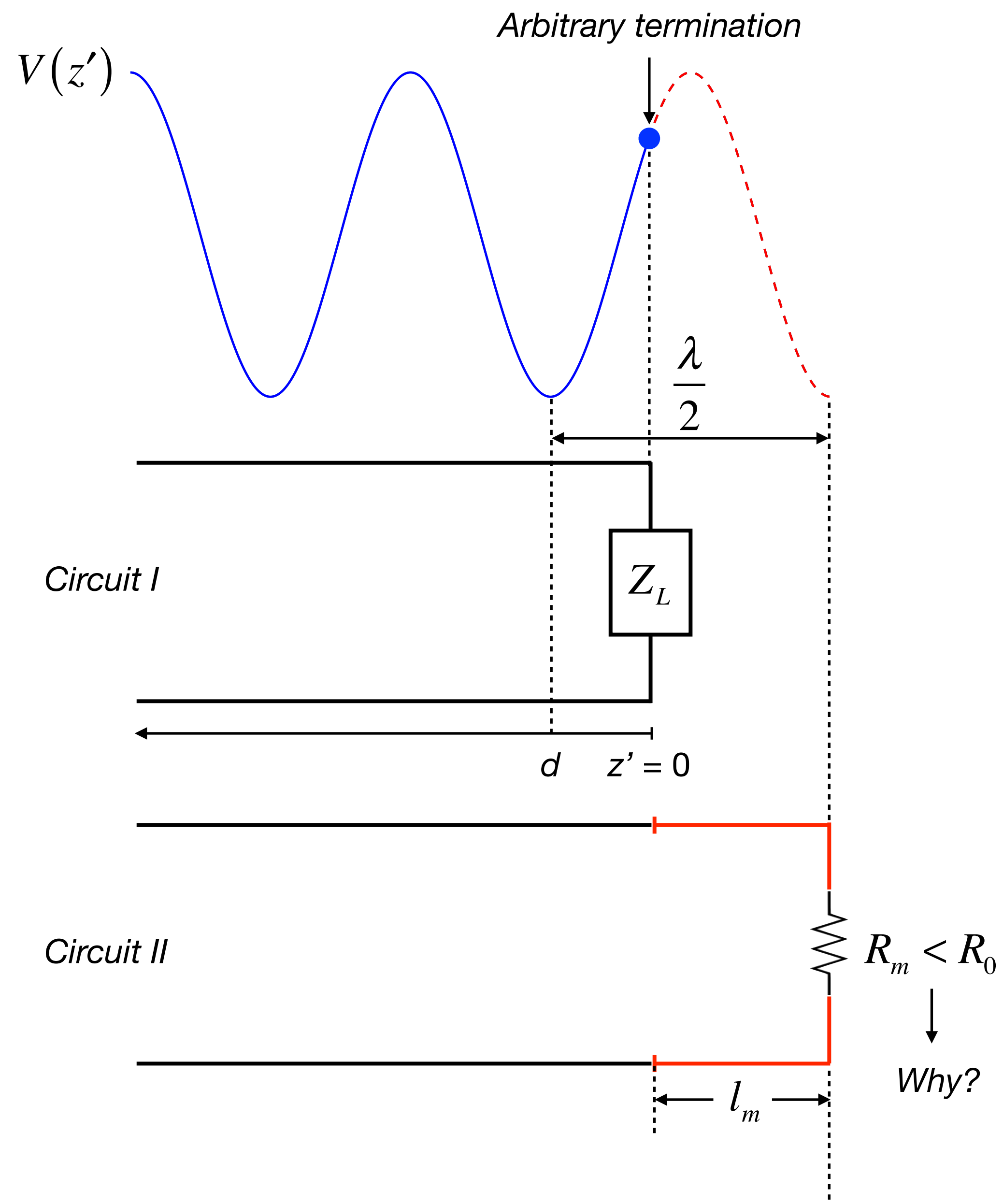

Chap. 9 | Arbitrary termination of TR-line

Engineering example

We measured $S = 3$ for lossless TR-line of $R_0 = 50 \text{ } (\Omega)$. $d = 5 \text{ (cm)}$ of the first voltage minima for arbitrary terminated TR-line. *Distance between successive voltage minima = 20 (cm)*. What is an arbitrary load impedance Z_L ? What is R_m and l_m for equivalent *Circuit II*?

- Step 1) Express Z_L in terms of R_0 and voltage reflection coefficient Γ

$$Z_L = \frac{V(z')}{I(z')} \Big|_{z'=0} = R_0 \frac{1 + |\Gamma| e^{j\theta_\Gamma}}{1 - |\Gamma| e^{j\theta_\Gamma}}$$

- Step 2) By applying (Cond. B), we can find θ_Γ for the first voltage minima

$$\theta_\Gamma - 2\beta d = -(2n + 1)\pi \Big|_{n=0} \rightarrow \theta_\Gamma = 2\beta d - \pi \quad \text{Here, } \beta = \frac{2\pi}{\lambda} \quad \text{where } \frac{\lambda}{2} = 20 \text{ (cm)}$$

Distance between successive voltage minima

$$= \frac{2\pi}{0.4} = 5\pi \text{ (rad/m)} \quad \rightarrow \theta_\Gamma = 2 \times 5\pi \times 0.05 - \pi = -0.5\pi \text{ (rad)}$$

- Step 3) By measuring S , we can get $|\Gamma|$ as

$$|\Gamma| = \frac{S - 1}{S + 1} = \frac{1}{2}$$

$$\therefore Z_L = R_0 \frac{1 + |\Gamma| e^{j\theta_\Gamma}}{1 - |\Gamma| e^{j\theta_\Gamma}} = 50 \frac{1 - j0.5}{1 + j0.5} = 30 - j40 \text{ } (\Omega)$$

- Recall Case 2) in slide p.8,

$$R_m = \frac{R_0}{S} = \frac{50}{3} = 16.7 \text{ } (\Omega)$$

- From the relation as below (see voltage graph in previous slide)


$$l_m + d = \frac{\lambda}{2} \rightarrow l_m = \frac{\lambda}{2} - d = 0.2 - 0.05 = 0.15 \text{ (m)}$$

Chap. 9 | Wave behavior observed from source

- Discussion so far
 - Effect of load (Z_L) on (V, I) characteristics
- Effect of source (V_g and Z_g) on (V, I) characteristics

Purpose

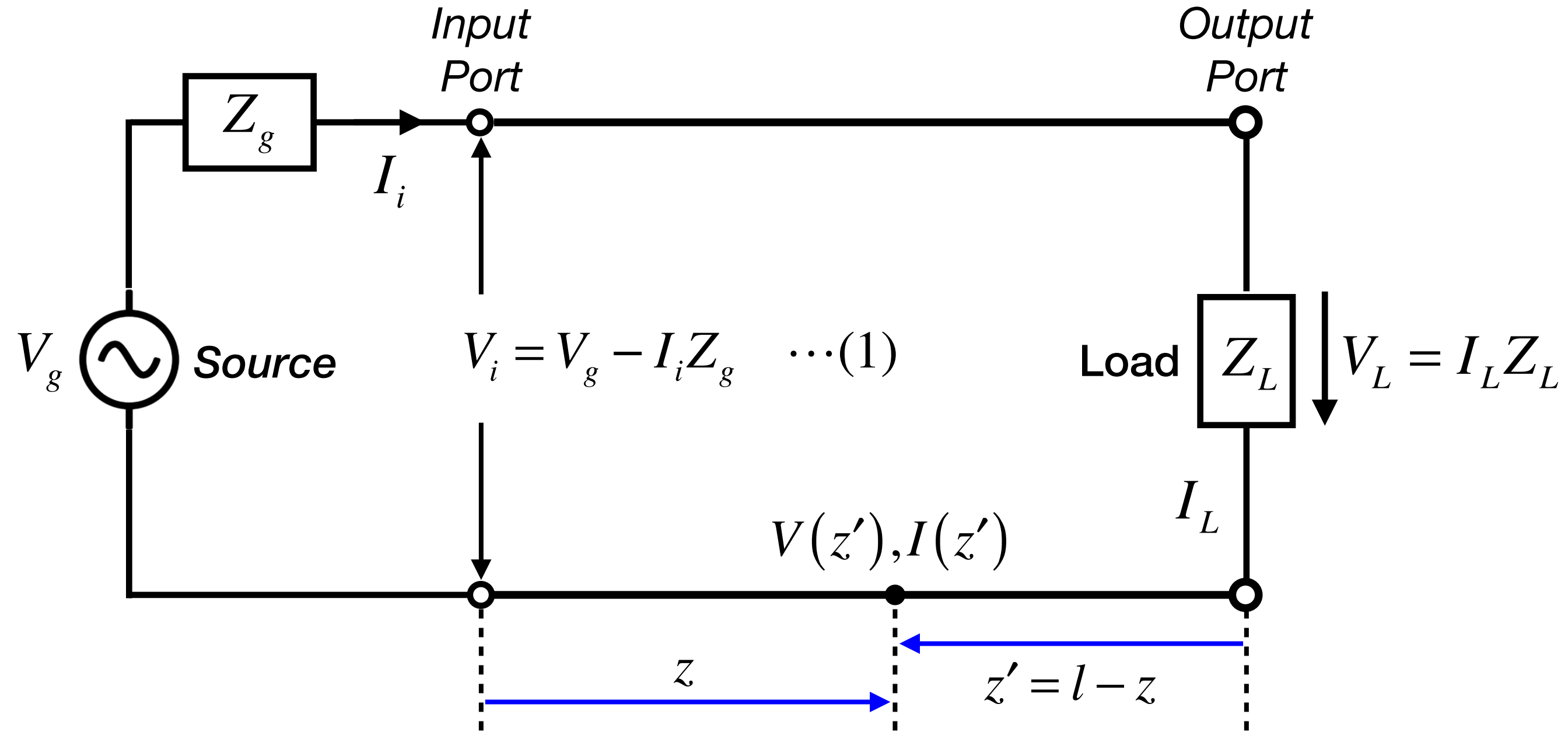By using source characteristics (V_g, Z_g) & line characteristics (γ, Z_0, l) & load impedance Z_L ,
 We want to determine V, I at any z of the line



$$\begin{cases} V(z') = \frac{I_L}{2}(Z_L + Z_0)e^{\gamma z'}(1 + \Gamma e^{-2\gamma z'}) \\ I(z') = \frac{I_L}{2Z_0}(Z_L + Z_0)e^{\gamma z'}(1 - \Gamma e^{-2\gamma z'}) \end{cases} \dots(2)$$

- At $z' = l$ (source end)

$$\begin{cases} V(l) \triangleq V_i = \frac{I_L}{2}(Z_L + Z_0)e^{\gamma l}(1 + \Gamma e^{-2\gamma l}) \\ I(l) \triangleq I_i = \frac{I_L}{2Z_0}(Z_L + Z_0)e^{\gamma l}(1 - \Gamma e^{-2\gamma l}) \end{cases} \dots(3)$$

- If we plug eqn. (3) into eqn. (1), we get

$$\frac{I_L}{2}(Z_L + Z_0)e^{\gamma l} = \frac{Z_0 V_g}{Z_0 + Z_g} \frac{1}{[1 - \Gamma_g \Gamma e^{-2\gamma l}]} \dots(4)$$

where $\Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0}$ **Reflection coefficient at the source end** c.f.) $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$

- If we plug eqn. (4) into $V(z')$ of eqn. (2), we get

$$V(z') = \frac{Z_0 V_g}{Z_0 + Z_g} e^{-\gamma z} \left(\frac{1 + \Gamma e^{-2\gamma z'}}{1 - \Gamma_g \Gamma e^{-2\gamma l}} \right)$$


Reflection coefficient at the load end

Chap. 9 | Wave behavior observed from source

$$\begin{aligned}
 V(z') &= \frac{Z_0 V_g}{Z_0 + Z_g} e^{-\gamma z} (1 + \Gamma e^{-2\gamma z'}) (1 - \Gamma_g \Gamma e^{-2\gamma l})^{-1} \\
 &= \frac{Z_0 V_g}{Z_0 + Z_g} e^{-\gamma z} (1 + \Gamma e^{-2\gamma z'}) \left[1 + \Gamma_g \Gamma e^{-2\gamma l} - (\Gamma_g \Gamma e^{-2\gamma l})^2 + \dots \right] \text{ Taylor expansion} \\
 &= \frac{Z_0 V_g}{Z_0 + Z_g} \left[e^{-\gamma z} + (\Gamma e^{-\gamma l}) e^{-\gamma z'} + \Gamma_g (\Gamma e^{-2\gamma l}) e^{-\gamma z} + \dots \right]
 \end{aligned}$$

$$V(z') = V_1^+ + V_1^- + V_2^+ + V_2^- + \dots = \begin{cases} V_1^+ = \frac{Z_0 V_g}{Z_0 + Z_g} e^{-\gamma z} = V_M e^{-\gamma z}, \\ V_1^- = (\Gamma V_M e^{-\gamma l}) e^{-\gamma z'}, \\ V_2^+ = \Gamma_g (\Gamma V_M e^{-2\gamma l}) e^{-\gamma z}, \\ \vdots \end{cases} \text{ where } V_M = \frac{Z_0 V_g}{Z_0 + Z_g}$$

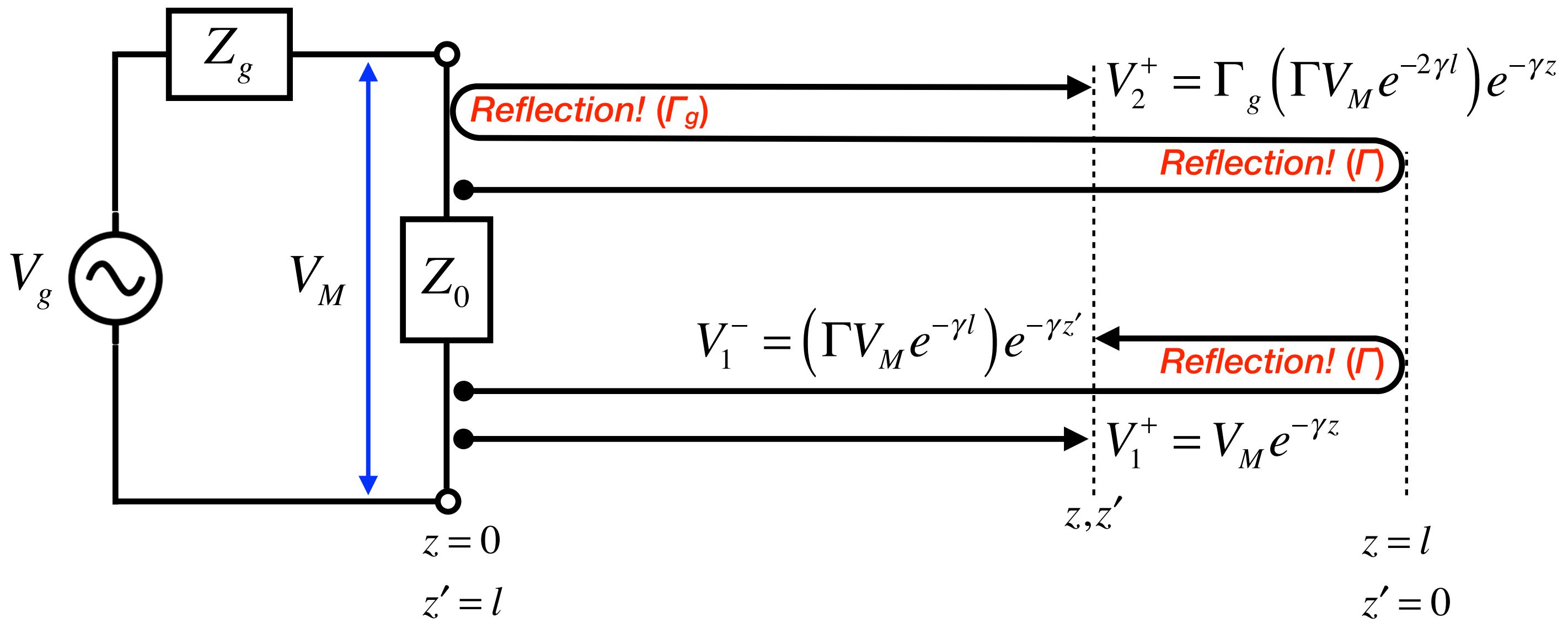Voltage initially sent down to TR-line at the input port



Trajectory of each voltage wave

- V_1^+ : Initial wave traveling by z in $+z$ direction
- V_1^- : V_1^+ reached at $z = l$ (or $z' = 0$), reflected (Γ), and then traveling by z' in $-z$ direction
- V_2^+ : V_1^- reached at $z' = l$ (or $z = 0$), reflected (Γ_g), and then traveling by z in $+z$ direction
- ...

\therefore Resulting standing wave $V(z')$ \rightarrow
 = Sum of all waves traveling in both directions!

* In the real case ($\gamma = \alpha + j\beta$)

- ▶ Amplitude of reflected waves diminishes each time it transverses the line

Some special cases

- * Matched condition ($Z_L = Z_0$)
 - ▶ $\Gamma = 0 \rightarrow$ Only V_1^+ exists, **no reflected wave**
- * $Z_L \neq Z_0$, but $Z_g = Z_0$
 - ▶ $\Gamma_g = 0 \rightarrow V_1^+$ and V_1^- exists, **no higher-order reflected waves**

Question

Distortionless line에서 리액턴스가 0이라는 말이 $i(z)$ 와 $v(z)$ 의 phasor차이가 없이 동등하게 진행됨은 이해를 했습니다.
 그런데 $I(z)$ 와 $v(z)$ 의 phasor차이가 없다는 사실이 어떤 물리적인 의미를 갖고 전송선에서 이것이 어떤 profit을 가지는지 궁금합니다.

Lossy TR-line

- Propagation constant (γ)

$$\begin{aligned} \gamma &= \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{(RG - \omega^2 LC) + j\omega(LG + RC)} \\ &= \left[\kappa(\omega) e^{j\Theta(\omega)} \right]^{\frac{1}{2}} = \sqrt{\kappa(\omega)} e^{j\frac{\Theta(\omega)}{2}} \\ &= \sqrt{\kappa(\omega)} \left(\cos \frac{\Theta(\omega)}{2} + j \sin \frac{\Theta(\omega)}{2} \right) = \alpha(\omega) + j\beta(\omega) \end{aligned}$$

- Phase velocity

$$u_p = \frac{\omega}{\beta(\omega)} = \frac{\omega}{\sqrt{\kappa(\omega)} \sin \frac{\Theta(\omega)}{2}} \rightarrow \text{“Dispersive system”}$$

signal at different ω travel at different u_p
 \rightarrow Signal distortion

- Characteristic impedance (Z_0)

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \Re(\omega) + j\Lambda(\omega) \rightarrow \text{Phase shift between } V \text{ and } I$$

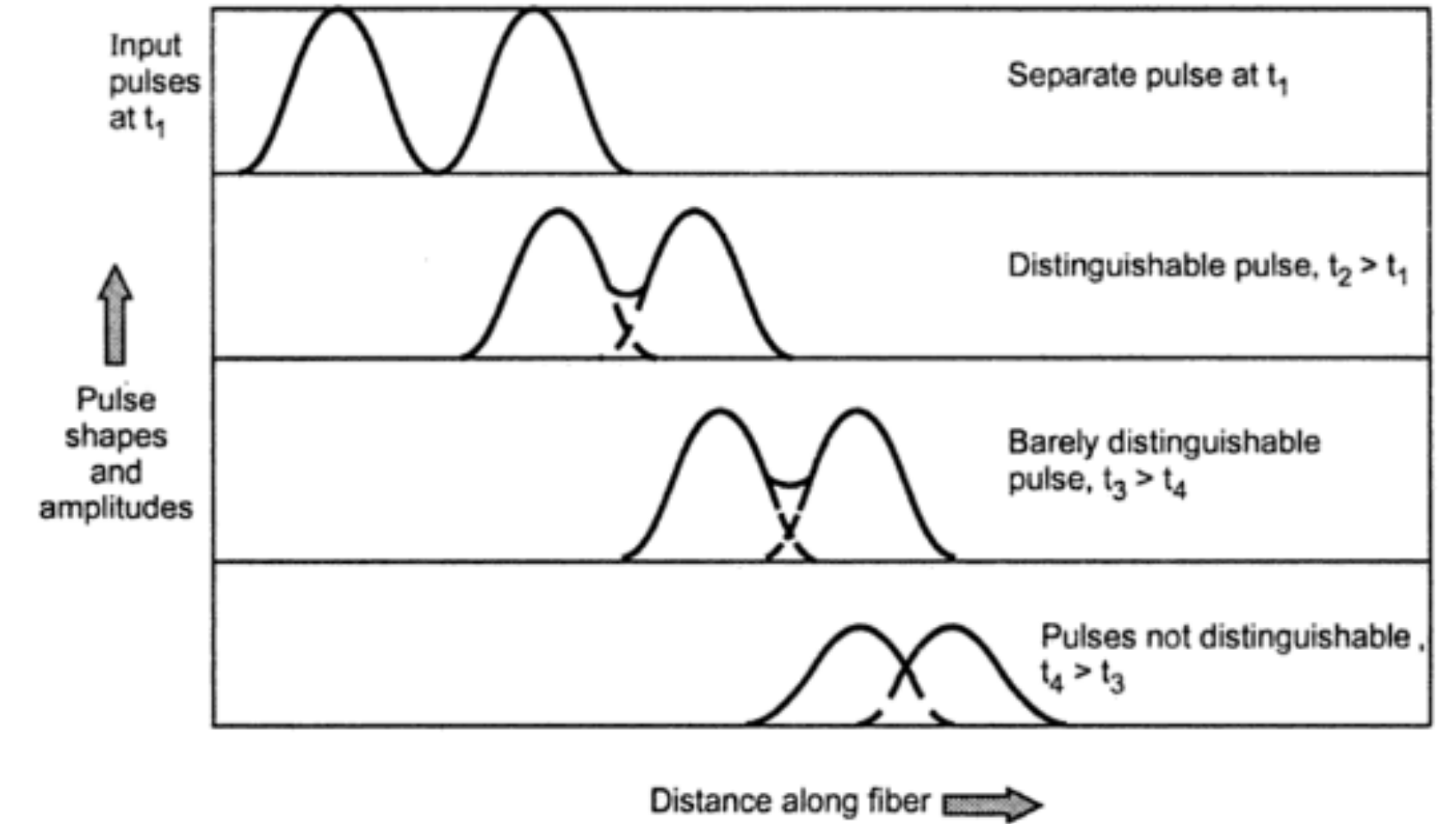


Fig. 1 Dispersion and attenuation in fiber

<Signal distortion>

Question

Distortionless line에서 리액턴스가 0이라는 말이 $i(z)$ 와 $v(z)$ 의 phasor차이가 없이 동등하게 진행됨은 이해를 했습니다.

그런데 $I(z)$ 와 $v(z)$ 의 phasor차이가 없다는 사실이 어떤 물리적인 의미를 갖고 전송선에서 이것이 어떤 profit을 가지는지 궁금합니다.

Distortionless TR-line ($R/L = G/C$)


$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{\frac{C}{L}}(R + j\omega L) \rightarrow u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} \quad \text{Non-dispersive}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{L}{C}} \quad \text{No phase shift}$$

From characteristic impedance (Z_0)

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{(R + j\omega L)(G - j\omega C)}{(G + j\omega C)(G - j\omega C)}} = \sqrt{\frac{RG + \omega^2 LC + j\omega(LG - RC)}{G^2 + \omega^2 C^2}} \rightarrow \text{To have reactance to be zero, } LG - RC = 0 \rightarrow \boxed{\therefore \frac{R}{L} = \frac{G}{C}}$$

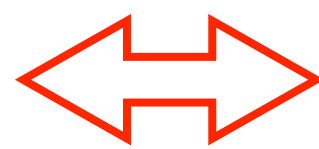\therefore Zero reactance condition
(no phase shift between V and I)



Distortionless condition
($u_p = \text{constant}$)

Electromagnetics

<Chap. 9> Transmission Lines

Section 9.4 ~ 9.5

(2nd of week 11)

Jaesang Lee

Dept. of Electrical and Computer Engineering

Seoul National University

(email: jsanglee@snu.ac.kr)

Chap. 9 | Contents for 2nd class of week 11


Sec 5. Transients on Transmission Lines

- Signal reflection at source & load ends
- Non-oscillating signals (step-function, pulse)
- Transient response for TR-line with resistive vs. reactive termination

Chap. 9 | Wave behavior observed from source (1/2)

- Discussion so far
 - Effect of load (Z_L) on (V, I) characteristics
- Effect of source (V_g and Z_g) on (V, I) characteristics

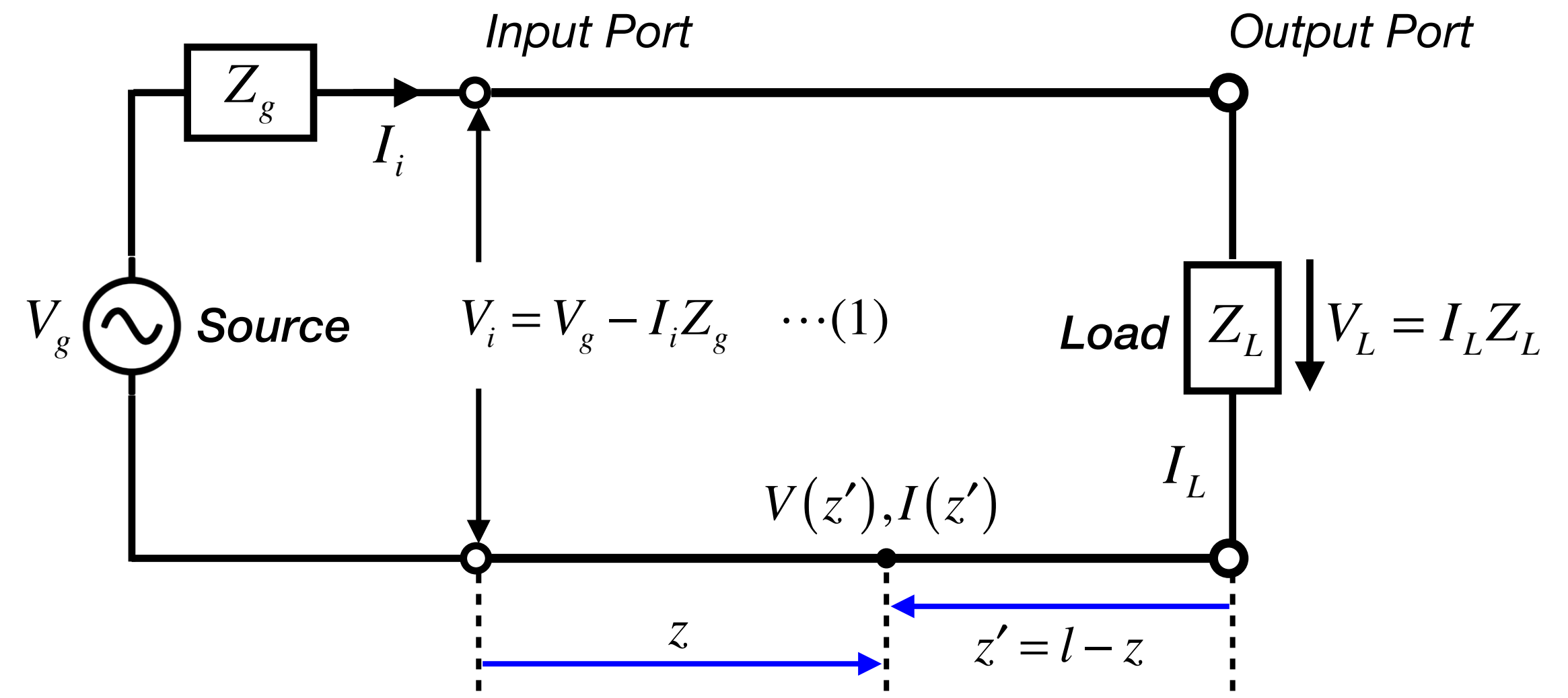Purpose
 By using source characteristics (V_g, Z_g) & line characteristics (γ, Z_0, l) & load impedance Z_L ,
 We want to determine (V, I) at any z of the line



$$\begin{cases} V(z') = \frac{I_L}{2}(Z_L + Z_0)e^{\gamma z'}(1 + \Gamma e^{-2\gamma z'}) \\ I(z') = \frac{I_L}{2Z_0}(Z_L + Z_0)e^{\gamma z'}(1 - \Gamma e^{-2\gamma z'}) \end{cases} \dots(2)$$

- At $z' = l$ (source end)

$$\begin{cases} V(l) \triangleq V_i = \frac{I_L}{2}(Z_L + Z_0)e^{\gamma l}(1 + \Gamma e^{-2\gamma l}) \\ I(l) \triangleq I_i = \frac{I_L}{2Z_0}(Z_L + Z_0)e^{\gamma l}(1 - \Gamma e^{-2\gamma l}) \end{cases} \dots(3)$$

- If we plug eqn. (3) into eqn. (1), we get

$$\frac{I_L}{2}(Z_L + Z_0)e^{\gamma l} = \frac{Z_0 V_g}{Z_0 + Z_g} \frac{1}{[1 - \Gamma_g \Gamma e^{-2\gamma l}]} \dots(4)$$

where $\Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0}$ **Reflection coefficient at the source end** c.f.) $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$

Reflection coefficient at the load end

- If we plug eqn. (4) into $V(z')$ of eqn. (2), we get


$$V(z') = \frac{Z_0 V_g}{Z_0 + Z_g} e^{-\gamma z} \left(\frac{1 + \Gamma e^{-2\gamma z'}}{1 - \Gamma_g \Gamma e^{-2\gamma l}} \right)$$

Chap. 9 | Wave behavior observed from source (2/2)

$$\begin{aligned}
 V(z') &= \frac{Z_0 V_g}{Z_0 + Z_g} e^{-\gamma z} (1 + \Gamma e^{-2\gamma z'}) (1 - \Gamma_g \Gamma e^{-2\gamma l})^{-1} \\
 &= \frac{Z_0 V_g}{Z_0 + Z_g} e^{-\gamma z} (1 + \Gamma e^{-2\gamma z'}) \left[1 + \Gamma_g \Gamma e^{-2\gamma l} - (\Gamma_g \Gamma e^{-2\gamma l})^2 + \dots \right] \text{ Taylor expansion} \\
 &= \frac{Z_0 V_g}{Z_0 + Z_g} \left[e^{-\gamma z} + (\Gamma e^{-\gamma l}) e^{-\gamma z'} + \Gamma_g (\Gamma e^{-2\gamma l}) e^{-\gamma z} + \dots \right]
 \end{aligned}$$

$$V(z') = V_1^+ + V_1^- + V_2^+ + V_2^- + \dots = \begin{cases} V_1^+ = \frac{Z_0}{Z_0 + Z_g} V_g e^{-\gamma z} = V_M e^{-\gamma z}, \\ V_1^- = (\Gamma V_M e^{-\gamma l}) e^{-\gamma z'}, \\ V_2^+ = \Gamma_g (\Gamma V_M e^{-2\gamma l}) e^{-\gamma z}, \\ \vdots \end{cases} \text{ where } V_M = \frac{Z_0}{Z_0 + Z_g} V_g$$

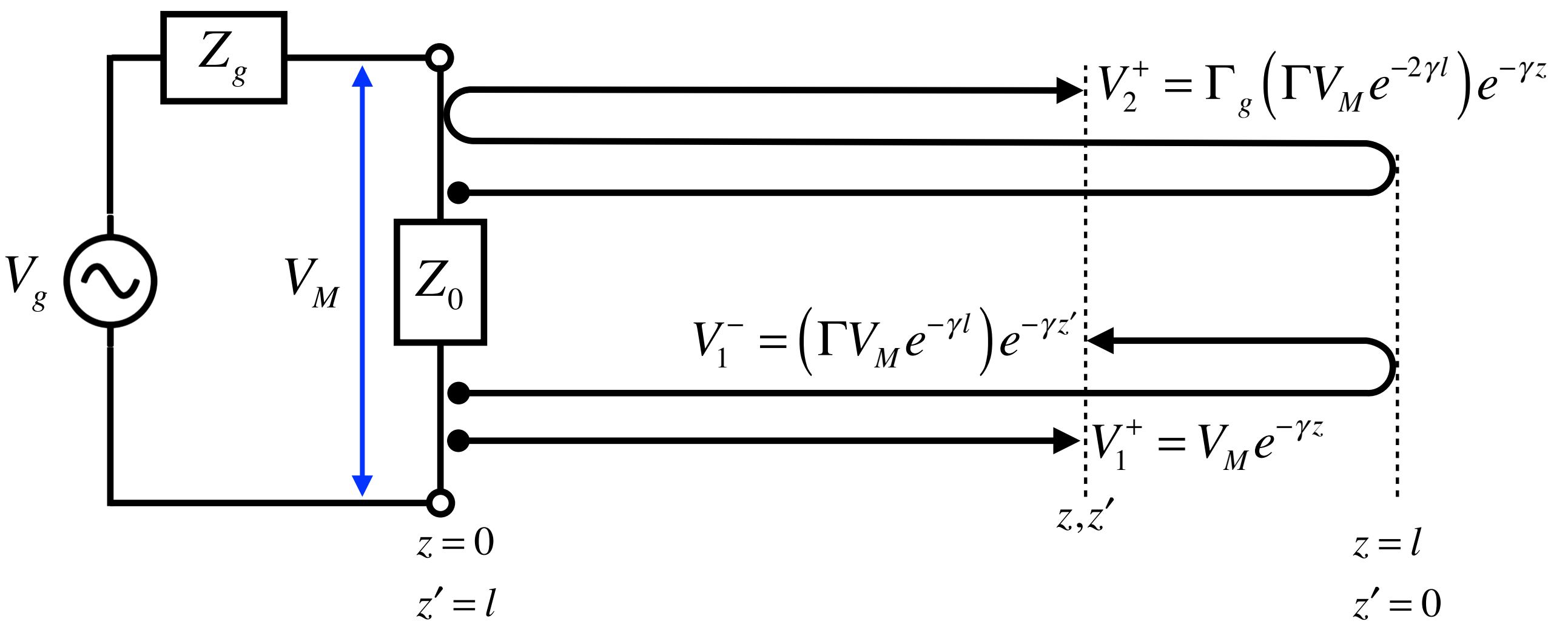Voltage initially sent down to TR-line at the input port



Trajectory of each voltage wave

- V_1^+ : Initial wave traveling by z in $+z$ direction
- V_1^- : V_1^+ reached at $z = l$ (or $z' = 0$), reflected (Γ), and then traveling by z' in $-z$ direction
- V_2^+ : V_1^- reached at $z' = l$ (or $z = 0$), reflected (Γ_g), and then traveling by z in $+z$ direction
-

\therefore Resulting standing wave $V(z')$ \rightarrow
 = Sum of all waves traveling in both directions!

* Amplitude of reflected waves decreases each time it transverses the line
 $\therefore |\Gamma| < 1, |\Gamma_g| < 1, \text{ and } \gamma = \alpha + j\beta$

Special cases

- * $Z_L = Z_0$ (Matched)
 - $\Gamma = 0 \rightarrow$ Only V_1^+ exists, **no reflected wave**
- * $Z_L \neq Z_0, \text{ but } Z_g = Z_0$
 - $\Gamma_g = 0 \rightarrow V_1^+$ and V_1^- exists, **no higher-order reflected waves**

Chap. 9 | Transient response: step-function (1/3)

- Discussion so far
 - Steady-state, single-frequency *time-harmonic* (i.e. *oscillating*) input & output
- Transient response for *non-harmonic* signals
 - Example: Pulse, step-function, ramp, and so on
 - Reactance (X), λ , k , β (due to oscillation) lose their meanings

- **Simplest example: step-function signal**

- DC voltage V_0 applied at $t = 0$
- R_g : internal (series) resistance


- <Case 1> $R_L = R_0$

- **Matched condition** → **No reflection**
- Impedance looking into TR-line: R_0 (independent of z)


∴ Voltage signal traveling in +z-direction (V_1^+) with velocity of u

$$V_1^+ = \frac{R_0}{R_0 + R_g} V_0 \quad \text{and} \quad u = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\mu\epsilon}}$$

Switch closed at $t = 0$ [Step-function]

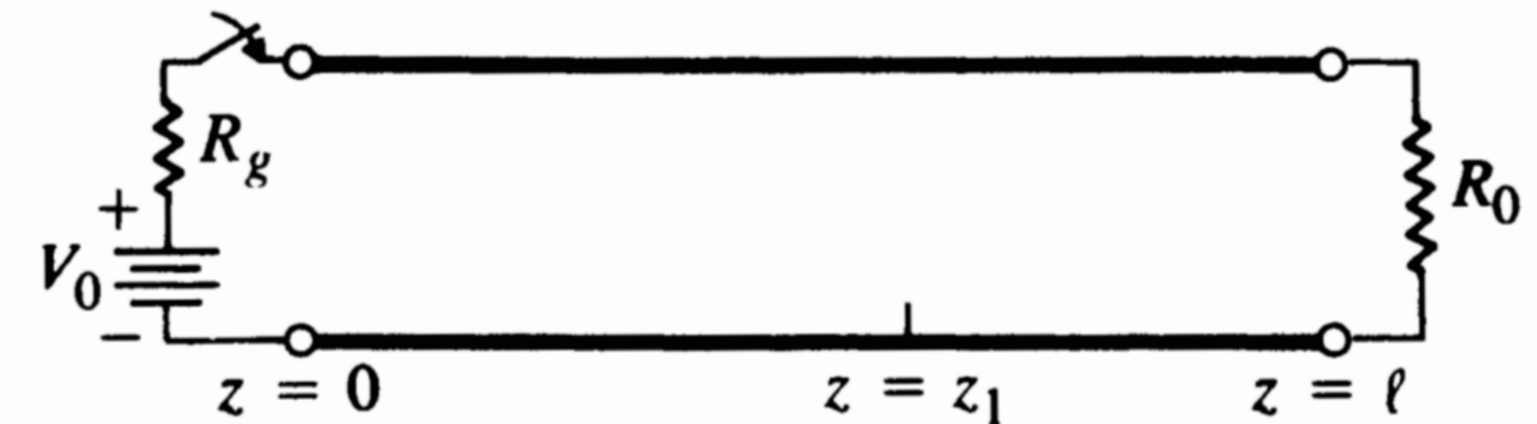

Voltage vs. time at $z = z_1$

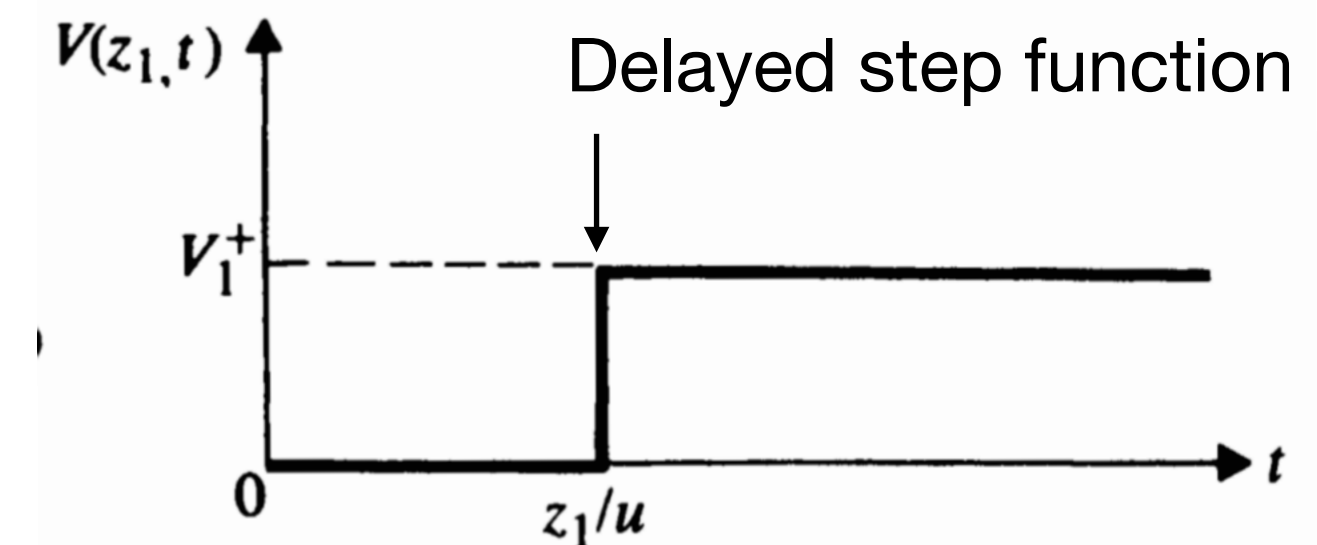

- Takes $t = \frac{z_1}{u}$ for V_1^+ traveling from $z = 0$ to z_1

- When V_1^+ reaches $z = l$ (load end)

▸ **No reflected wave** $\left(\because \Gamma_L = \frac{R_L - R_0}{R_L + R_0} \right)$

- Entire line charged at V_1^+ (i.e. *steady-state* established)

Chap. 9 | Transient response: step-function (2/3)


- Simplest example: step-function signal

- <Case 2> $R_g \neq R_0$ and $R_L \neq R_0$


At $t = 0$: $V_1^+ = \frac{R_0}{R_0 + R_g} V_0$ travels in +z direction with $u = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\mu\epsilon}}$

At $t = T$: V_1^+ reaches at $z = l$ and reflected $\left(\Gamma_L = \frac{R_L - R_0}{R_L + R_0} \right)$. Then, $V_1^- = \Gamma_L V_1^+$ travels in -z direction with u
 $\left(T = \frac{l}{u} \right)$

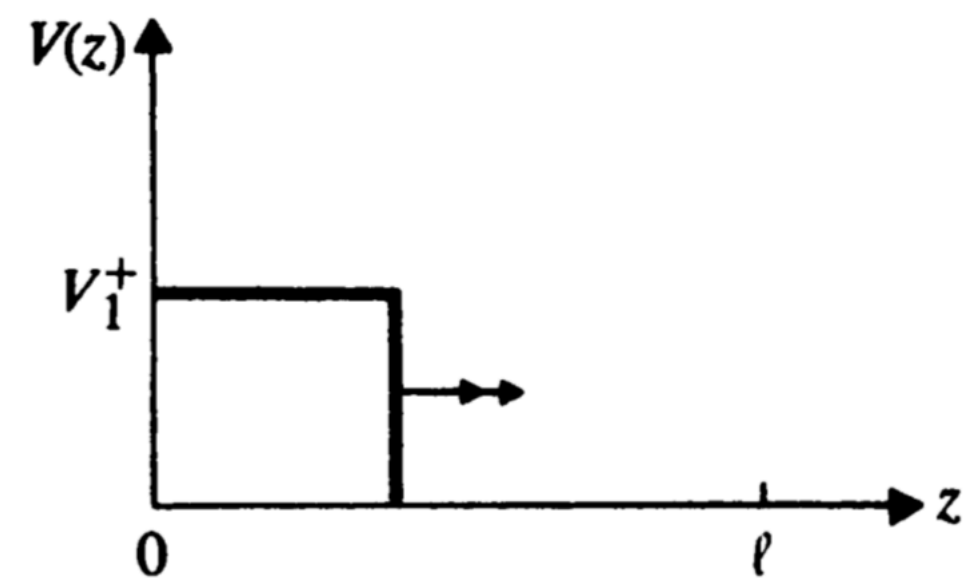
At $t = 2T$: V_1^- reaches at $z = 0$ and reflected $\left(\Gamma_g = \frac{R_g - R_0}{R_g + R_0} \right)$. Then, $V_2^+ = \Gamma_g V_1^- = \Gamma_g \Gamma_L V_1^+$ travels in +z direction with u



$0 \leq t \leq T$

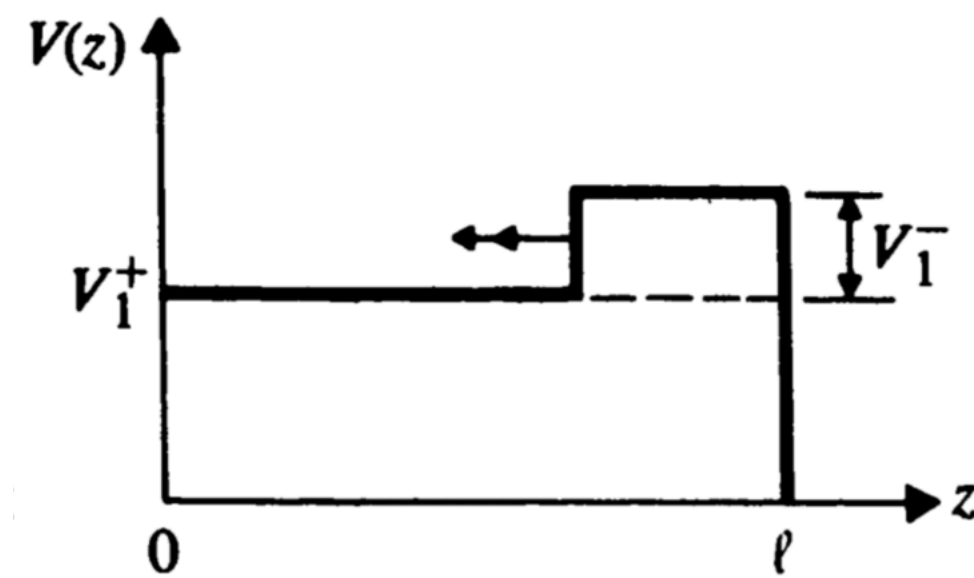

$T \leq t \leq 2T$

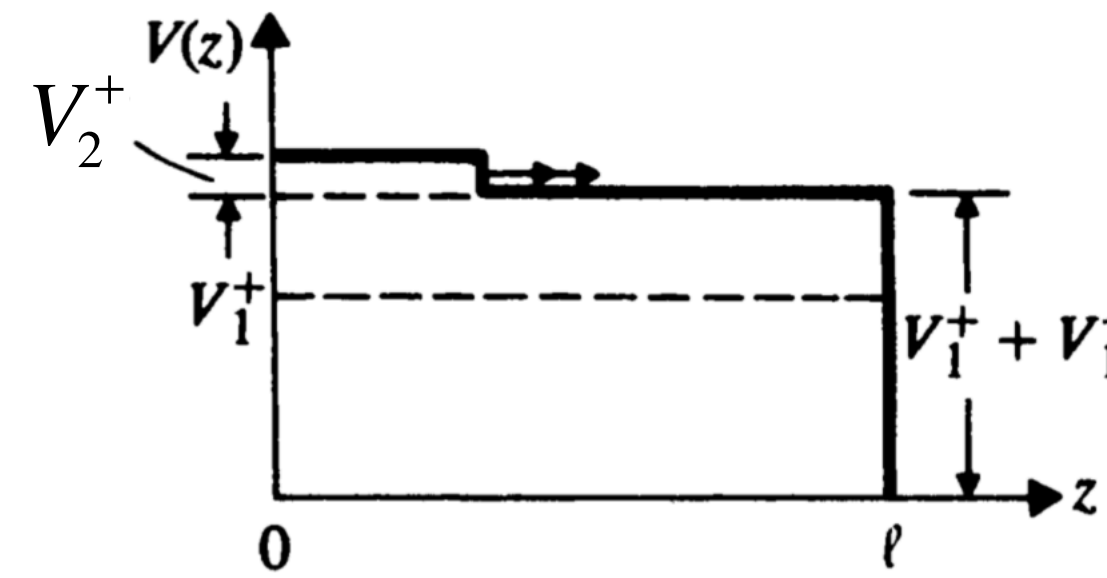

$2T \leq t \leq 3T$

$$|\Gamma_L| < 1 \text{ and } |\Gamma_g| < 1$$

Chap. 9 | Transient response: step-function (3/3)

- Simplest example: step-function signal

- <Case 2> $R_g \neq R_0$ and $R_L \neq R_0$

At $t = \infty$: At a load end ($z = l$), we have the **steady-state voltage** as

$$\begin{aligned}
 V_L &= V_1^+ + V_1^- + V_2^+ + V_2^- + V_3^+ + V_3^- + \dots \\
 &= V_1^+ \left(1 + \Gamma_L + \Gamma_g \Gamma_L + \Gamma_g \Gamma_L^2 + \Gamma_g^2 \Gamma_L^2 + \Gamma_g^2 \Gamma_L^3 + \dots \right) \\
 &= V_1^+ (1 + \Gamma_L) \left(1 + \Gamma_g \Gamma_L + \Gamma_g^2 \Gamma_L^2 + \dots \right) \\
 &= V_1^+ \left(\frac{1 + \Gamma_L}{1 - \Gamma_g \Gamma_L} \right) \quad (\because |\Gamma_L \Gamma_g| < 1)
 \end{aligned}$$

We have the **steady-state current** as

$$\begin{aligned}
 I_L &= I_1^+ + I_1^- + I_2^+ + I_2^- + I_3^+ + I_3^- + \dots \\
 &= \frac{V_1^+}{R_0} \left(1 - \Gamma_L + \Gamma_g \Gamma_L - \Gamma_g \Gamma_L^2 + \Gamma_g^2 \Gamma_L^2 - \Gamma_g^2 \Gamma_L^3 + \dots \right) \\
 &= \frac{V_1^+}{R_0} (1 - \Gamma_L) \left(1 + \Gamma_g \Gamma_L + \Gamma_g^2 \Gamma_L^2 + \dots \right) \\
 &= \frac{V_1^+}{R_0} \left(\frac{1 - \Gamma_L}{1 - \Gamma_g \Gamma_L} \right)
 \end{aligned}$$

Recall the relation


$$\frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = Z_0$$

Phase of current changed by π upon reflection


$$\begin{cases}
 V(z') = \frac{I_L}{2} (Z_L + R_0) e^{j\beta z'} \left[1 + |\Gamma| e^{j(\theta_\Gamma - 2\beta z')} \right] \\
 I(z') = \frac{I_L}{2R_0} (Z_L + R_0) e^{j\beta z'} \left[1 - |\Gamma| e^{j(\theta_\Gamma - 2\beta z')} \right]
 \end{cases}$$

Chap. 9 | Reflection diagram

- Reflection diagram

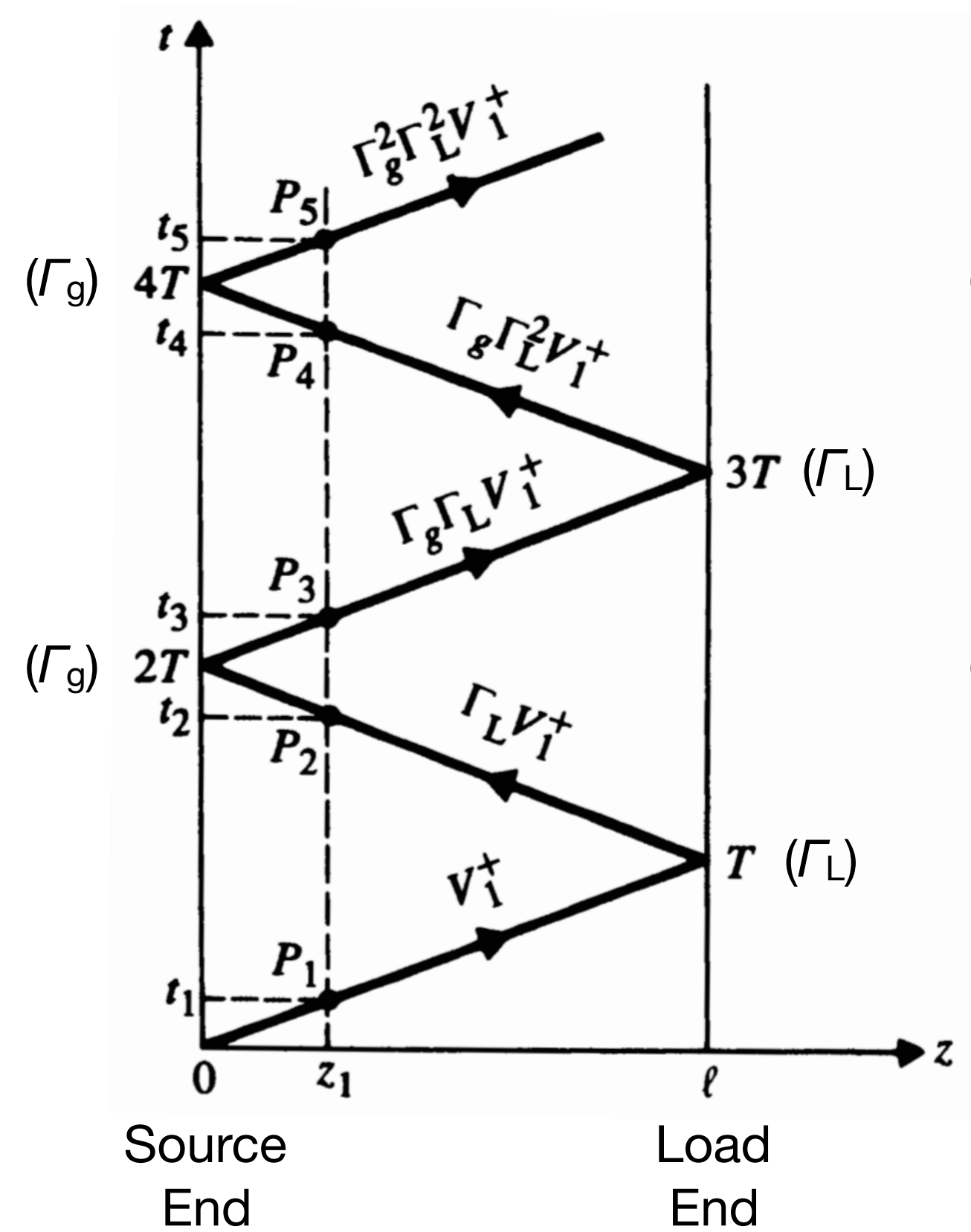

<Voltage reflection diagram>

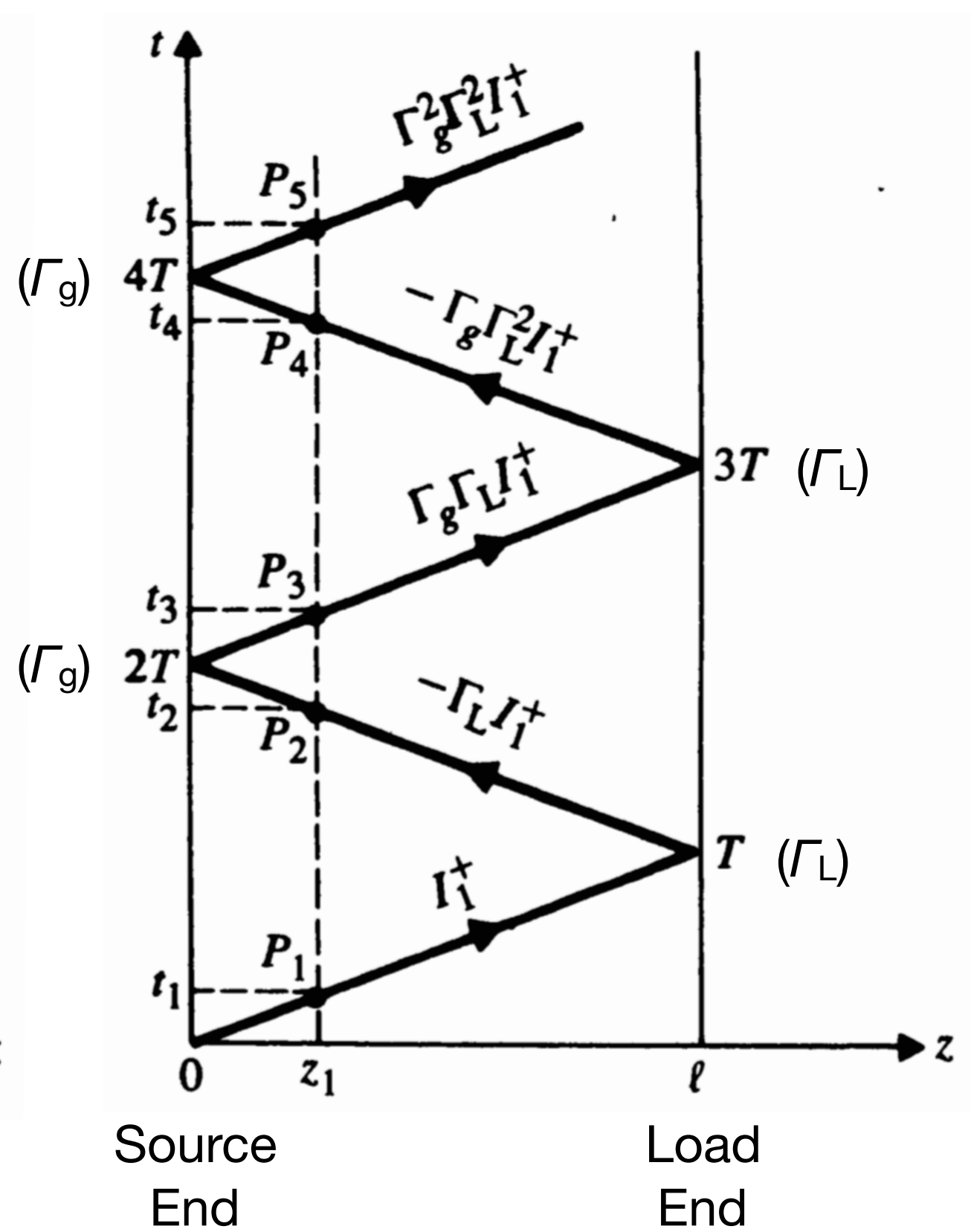

<Current reflection diagram>

- Graphical representation of (V, I) propagation vs. t or z
- At $0 \leq t \leq T$
 - V_{1+} travels in +z direction from $z = 0$ to l
 - I_{1+} travels in +z direction from $z = 0$ to l
- At $T \leq t \leq 2T$
 - $V_{1-} = \Gamma_L V_{1+}$ travels in -z direction from $z = l$ to 0
 - $I_{1-} = -\Gamma_L I_{1+}$ travels in -z direction from $z = l$ to 0
- At $2T \leq t \leq 3T$
 - $V_{2+} = \Gamma_g \Gamma_L V_{1+}$ travels in +z direction from $z = 0$ to l
 - $I_{1-} = \Gamma_g \Gamma_L I_{1+}$ travels in +z direction from $z = 0$ to l
- (V, I) vs. time (t) at any location: algebraic sum *along vertical line!*
- (V, I) vs. location (z) at any given time: algebraic sum *below horizontal line!*



Chap. 9 | Transient response: Example

- voltage, current variation vs. **time (at $z = z_1$)**



- If $R_L = 3R_0$ ($\Gamma_L = 1/2$) and $R_g = 2R_0$ ($\Gamma_g = 1/3$),

$$V_L = V_1^+ \left(\frac{1 + \Gamma_L}{1 - \Gamma_g \Gamma_L} \right) = \frac{R_0}{R_0 + R_g} V_0 \left(\frac{1 + \Gamma_L}{1 - \Gamma_g \Gamma_L} \right) = \frac{3}{5} V_0$$
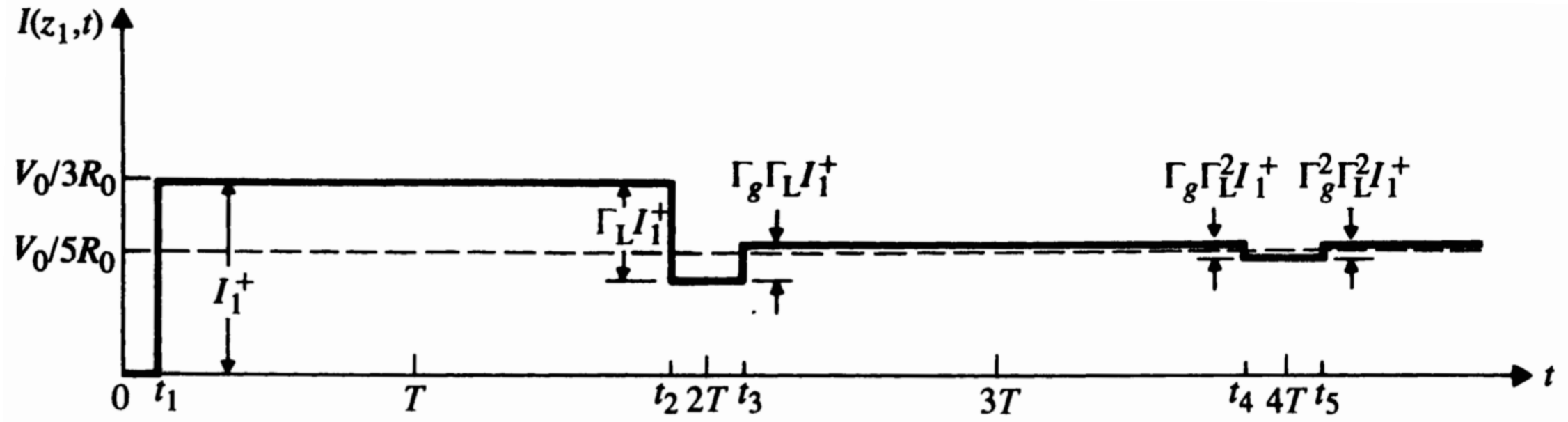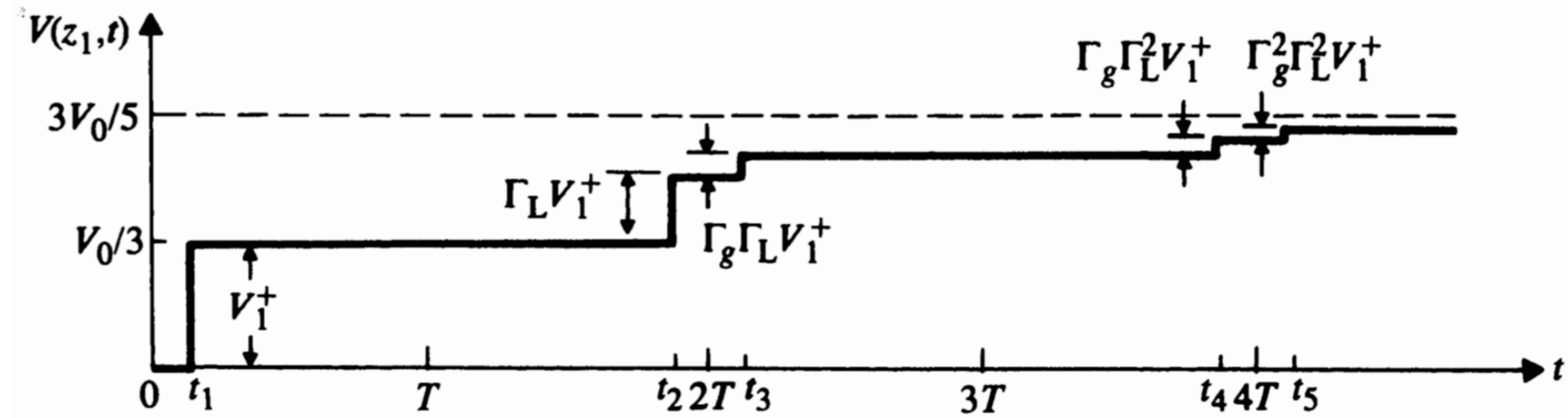
$$I_L = \frac{V_1^+}{R_0} \left(\frac{1 + \Gamma_L}{1 - \Gamma_g \Gamma_L} \right) = \frac{V_0}{R_0 + R_g} \left(\frac{1 - \Gamma_L}{1 - \Gamma_g \Gamma_L} \right) = \frac{V_0}{5R_0}$$



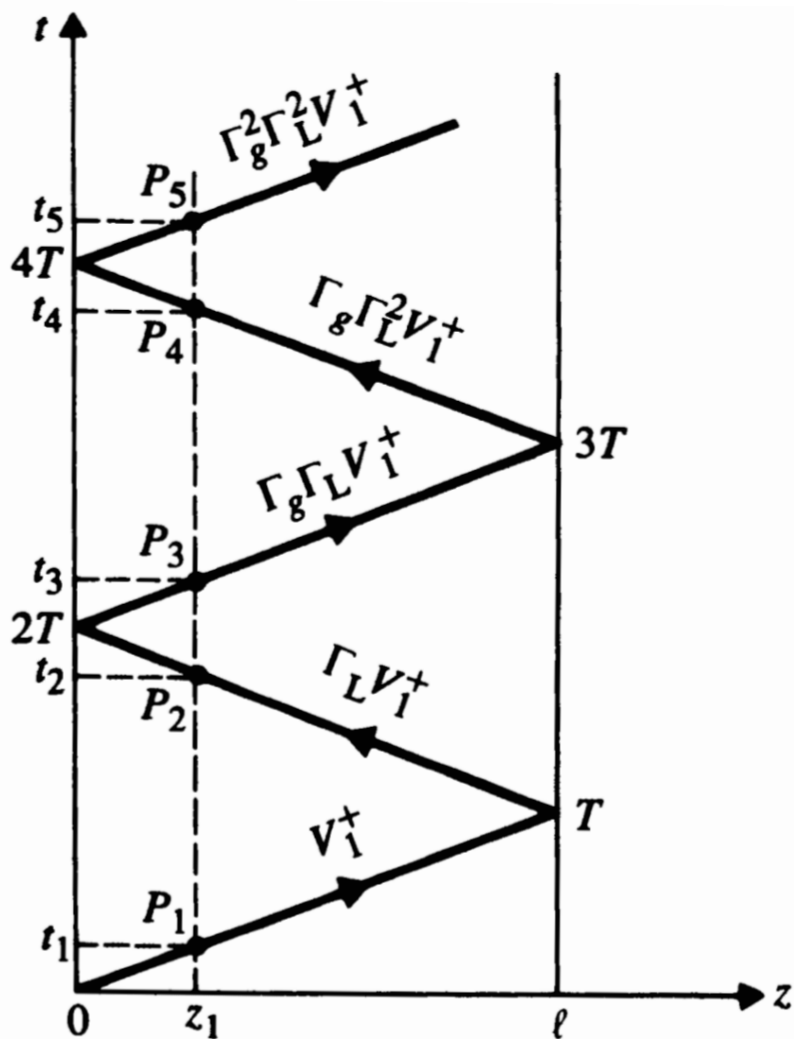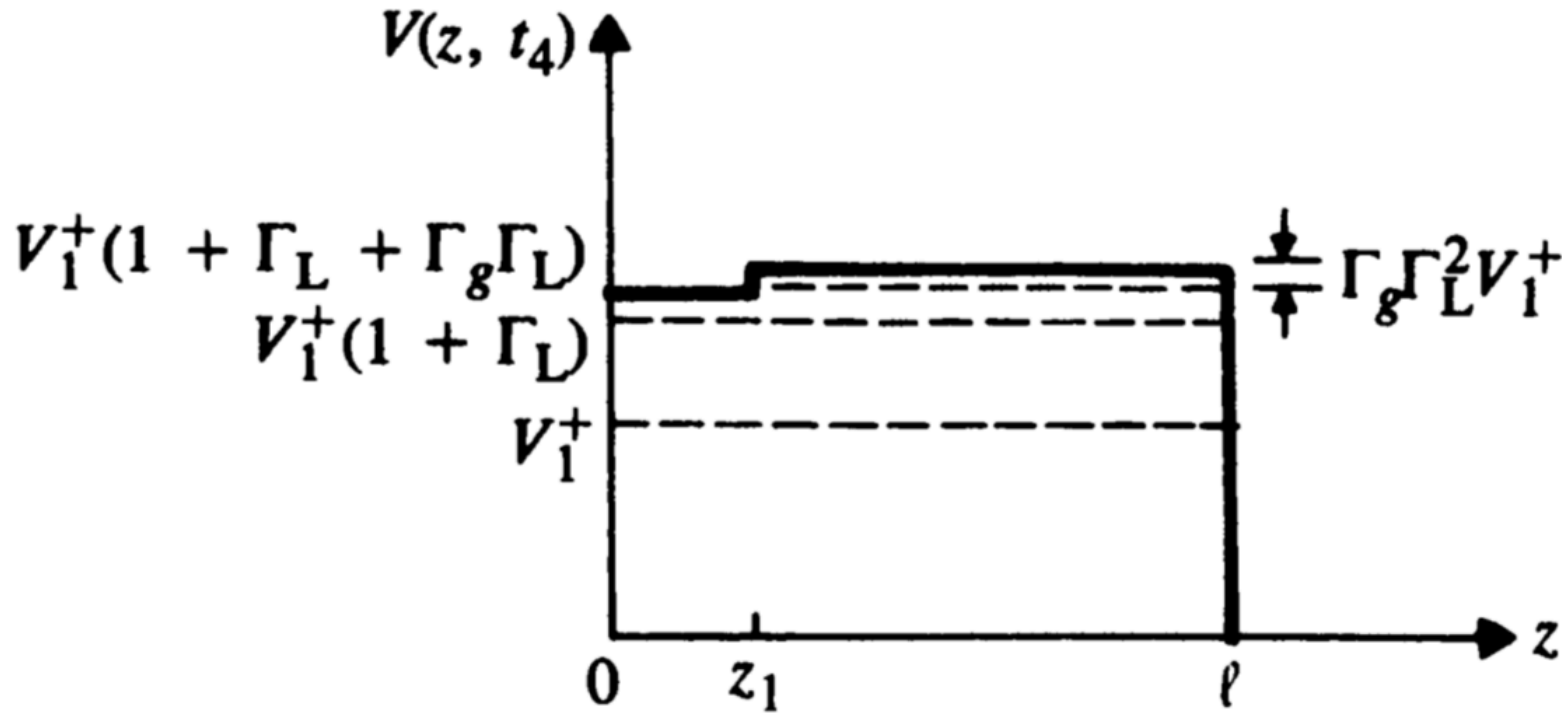- voltage distribution vs. **location (at $t = t_4$)**




- Some special cases

- I. $R_L = R_0$
 - $\Gamma_L = 0 \rightarrow$ No reflection at load end
 - After $t = T = l/u$, only V_1^+ and I_1^+ exist
- II. $R_L \neq R_0, R_g = R_0$
 - $\Gamma_g = 0 \rightarrow$ No reflection at source end
 - After $t = 2T$, only (V_1^+, V_1^-) and (I_1^+, I_1^-) exist

Chap. 9 | Transient response: pulse signal (1/2)

- Discussion so far

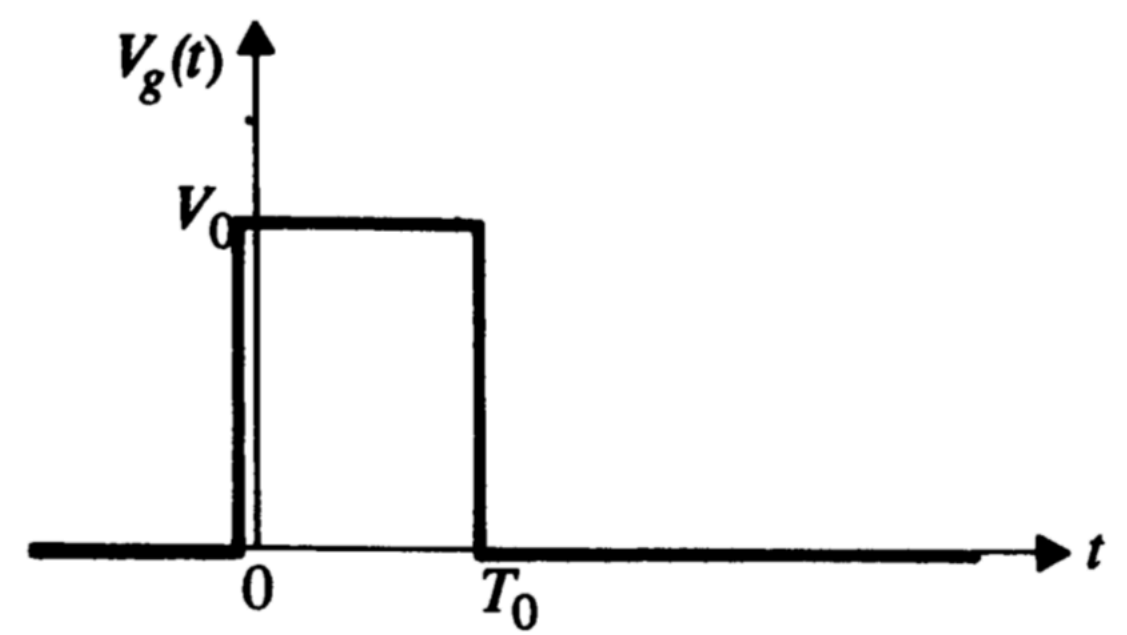- Transient response for *step-function signal* represented by $v_g(t) = V_0 U(t) = \begin{cases} 0, & t < 0 \\ V_0, & t > 0 \end{cases}$



- Pulse signal

- *superposition of two step-functions*: $v_g(t) = V_0 [U(t) - U(t - T_0)]$

- Example

- Given condition

- Magnitude: $V_0 = 15$ (V), duration: $T_0 = 1$ (μ s)

$$v_g(t) = 15 [U(t) - U(t - 10^{-6})] \text{ (V)}$$

- Series resistance: $R_g = 25$ (Ω)

- Characteristic impedance of TR-line: $R_0 = 50$ (Ω)

- $l = 400$ (m), material within TR-line $\epsilon = 2.25$

- Load impedance: $Z_L = R_L = 0$ (Ω) (\rightarrow Short-circuited!)

- **Q:** Voltage change at $z = l/2 = 200$ (m) between $0 \leq t \leq 8$ (μ s)?

- Reflection coefficient


$$\Gamma_L = \frac{R_L - R_0}{R_L + R_0} = -1, \quad \Gamma_g = \frac{R_g - R_0}{R_g + R_0} = \frac{25 - 50}{75} = -\frac{1}{3}$$

- Propagation speed & transverse time

$$u = \frac{1}{\sqrt{\mu\epsilon}} = \frac{c}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{\sqrt{2.25}} = 2 \times 10^8 \text{ (m/s)}, \quad T = \frac{l}{u} = 2 \text{ (\mu s)}$$

- Voltage sent down to TR-line


$$V_1^+ = \frac{R_0}{R_g + R_0} V_0 = \frac{25}{25 + 50} \times 15 = 10 \text{ (V)}$$

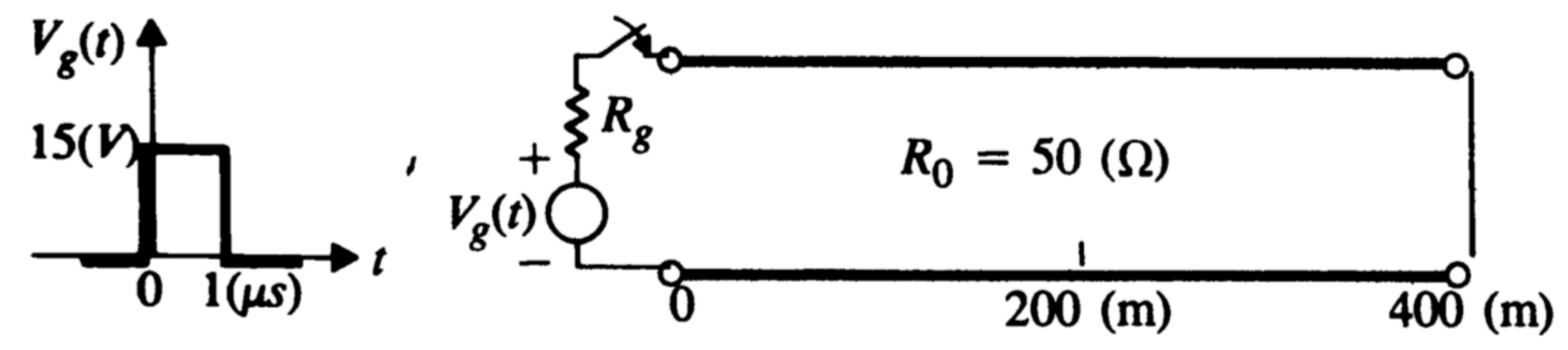

Chap. 9 | Transient response: pulse signal (2/2)



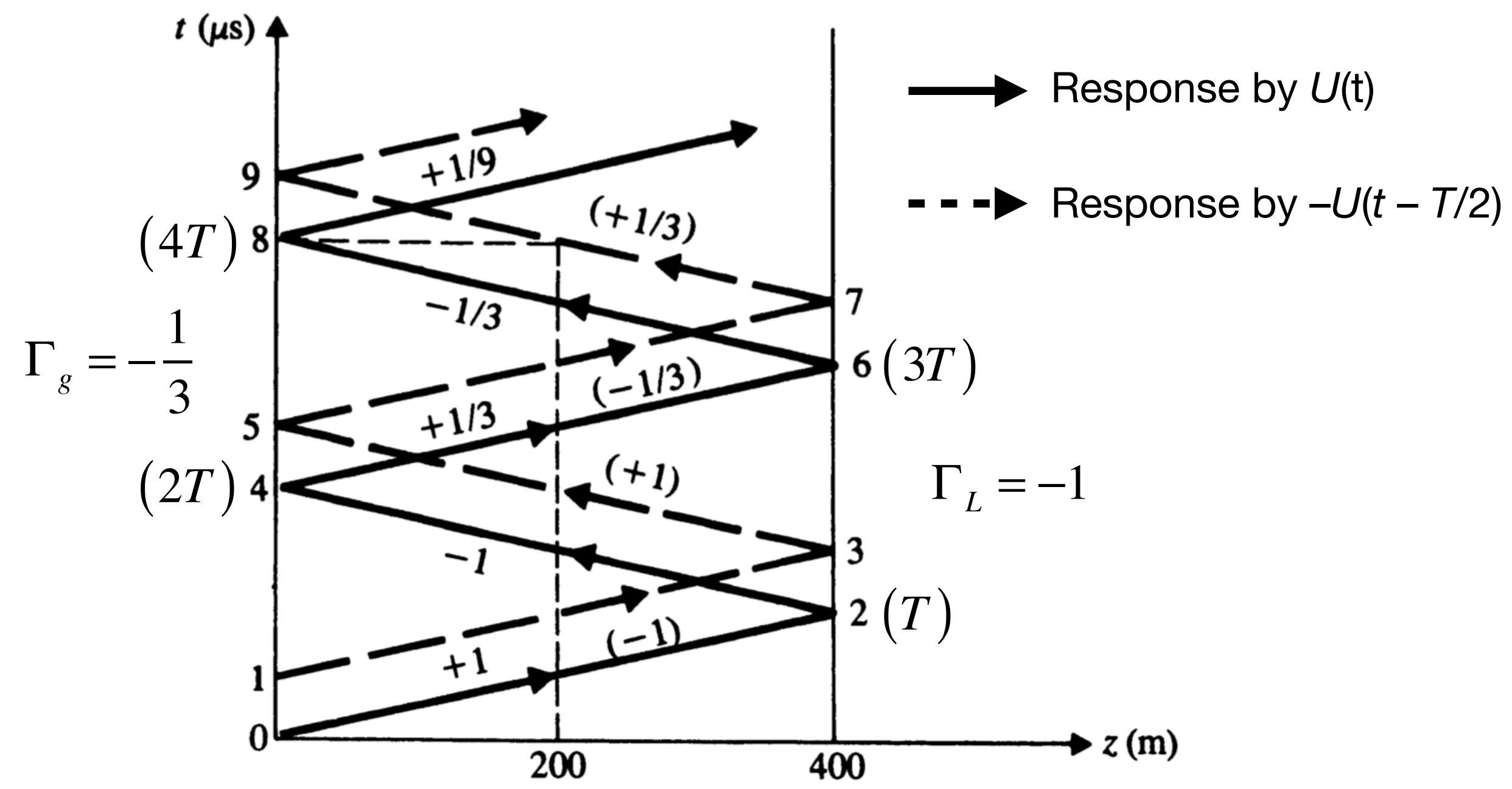
- Example: pulse signal

<Reflection diagram for $U(t)$ and $-U(t - T/2)$ >



$$v_g(t) = 15 \left[U(t) - U\left(t - \frac{T}{2}\right) \right] \text{ (V)}$$

$$\begin{cases} T = 2 \text{ (}\mu\text{s)} \\ V_1^+ = 10 \text{ (V)} \end{cases}$$

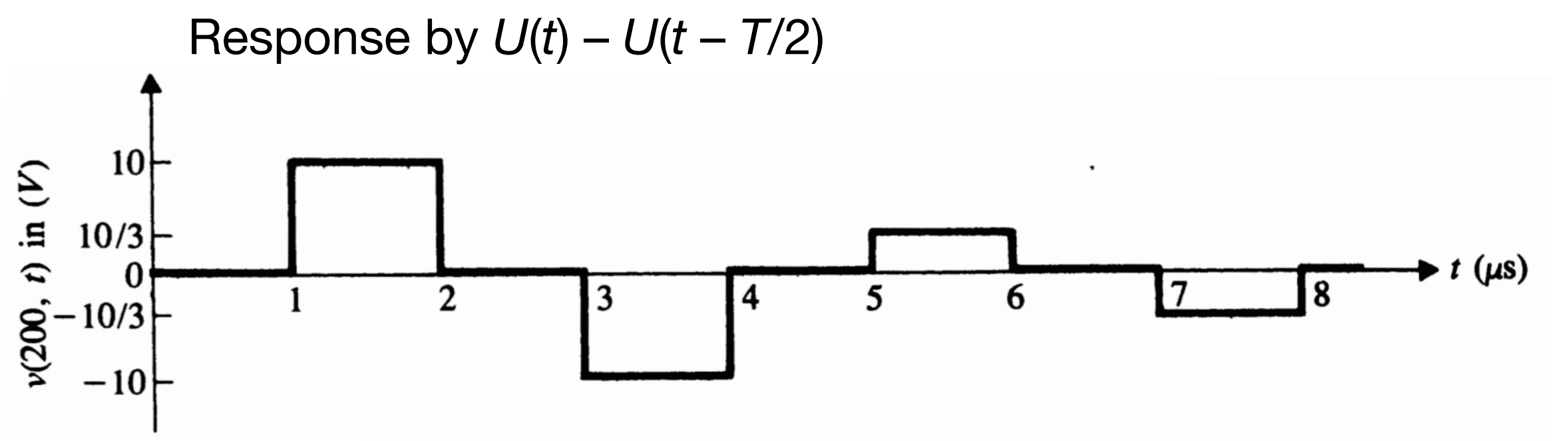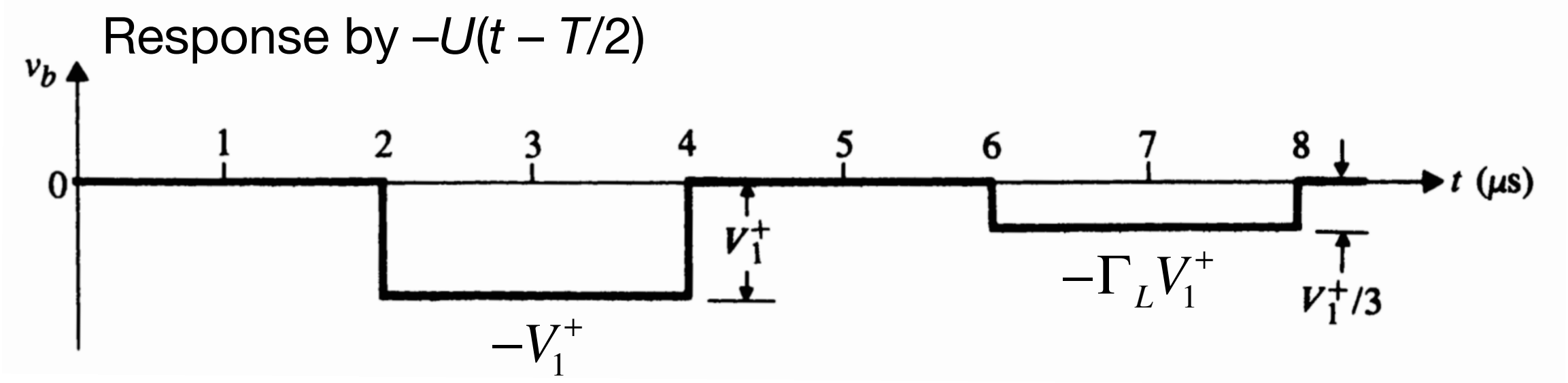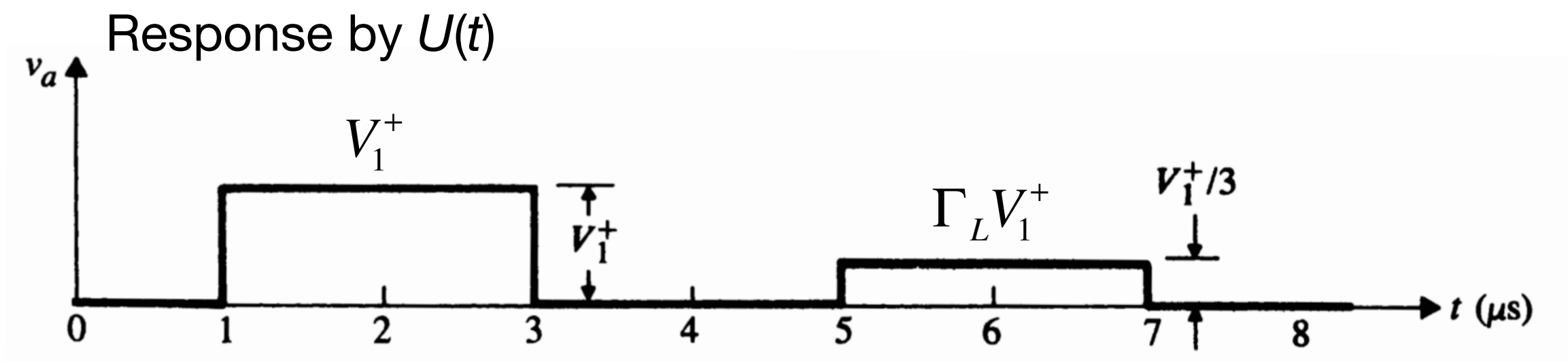


Chap. 9 | TR-line with reactive termination (1/2)

- TR-line terminated with reactive load

- $Z_L = R_L + jX_L$ (Due to X_L , phase shift introduced upon reflection)
- Time-dependence of incident wave \neq reflected wave
- Not simple as the resistive termination
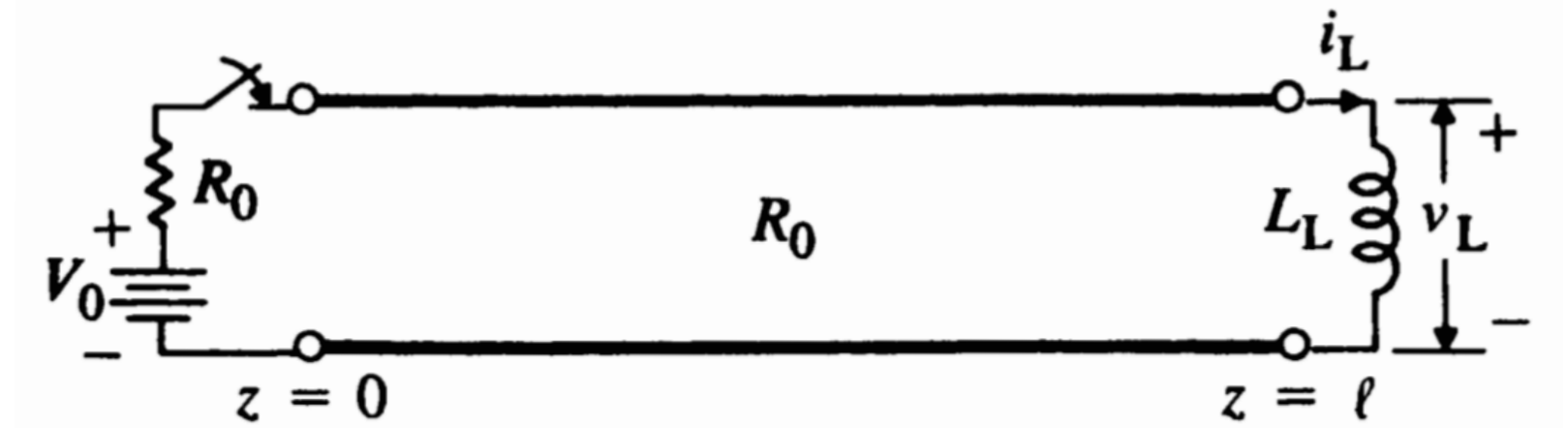
$$\left(\because \Gamma_L = \frac{Z_L - R_0}{Z_L + R_0} \right)$$



- Inductive termination ($X_L > 0$)

- Condition

- TR-line terminated with an inductor load (L_L)
- Internal (or series) impedance $R_g = R_0$ (What does it mean?)
- Voltage initially sent down to TR-line:

$$V_1^+ = \frac{R_0}{R_g + R_0} V_0$$

- At $t = T (= u/l)$

- V_1^+ reached at $z = l$, reflected by inductor (Γ_L)
- $V_1^- = \Gamma_L V_1^+$ generated and travel in $-z$ direction
(\rightarrow Because Γ_L complex, V_1^- no longer constant, but *time-dependent!*)

- At $z = l$ after reflection (i.e. $t \geq T$)

$$v_L(t) = V_1^+ + V_1^-(t) \quad \dots(1)$$

- Equivalently, $v_L(t) = L_L \frac{di_L(t)}{dt} \quad \dots(2)$

$$\text{where } i_L(t) = \frac{V_1^+}{R_0} - \frac{V_1^-(t)}{R_0} \rightarrow R_0 i_L(t) = V_1^+ - V_1^-(t) \quad \dots(3)$$

- By eliminating $V_1^-(t)$ by combining **eqns. (1) and (3)**, we have

$$v_L(t) = 2V_1^+ - R_0 i_L(t) \quad \dots(4)$$

- By substituting **eqn. (2)** into **eqn. (4)**, we have

$$L_L \frac{di_L(t)}{dt} + R_0 i_L(t) = 2V_1^+, \quad (t \geq T)$$

Chap. 9 | TR-line with reactive termination (2/2)

- Inductive termination ($X_L > 0$)
 - IVP for first-order differential equation

$$\frac{di_L(t)}{dt} + \frac{R_0}{L_L} i_L(t) = \frac{2V_1^+}{L_L}, \quad (t \geq T) \quad \text{and} \quad i_L(T) = 0$$

- By applying Laplacian operator,

$$sI(s) - \cancel{i_L(T)} + \frac{R_0}{L_L} I(s) = \frac{2V_1^+}{L_L s} \quad \rightarrow \quad I(s) = \frac{2V_1^+}{L_L} \frac{1}{s(s + R_0/L_L)} = \frac{2V_1^+}{R_0} \left[\frac{1}{s} - \frac{1}{s + R_0/L_L} \right]$$

- By applying inverse Laplacian operator, we get $i_L(t)$ (Current variation at load end)


$$i_L(t) = \frac{2V_1^+}{R_0} \left[1 - e^{-\frac{R_0}{L_L}(t-T)} \right]$$






$$v_L(t) = L_L \frac{di_L(t)}{dt} = 2V_1^+ e^{-\frac{R_0}{L_L}(t-T)}$$



$$V_1^-(t) = V_1^+ - v_L(t)$$

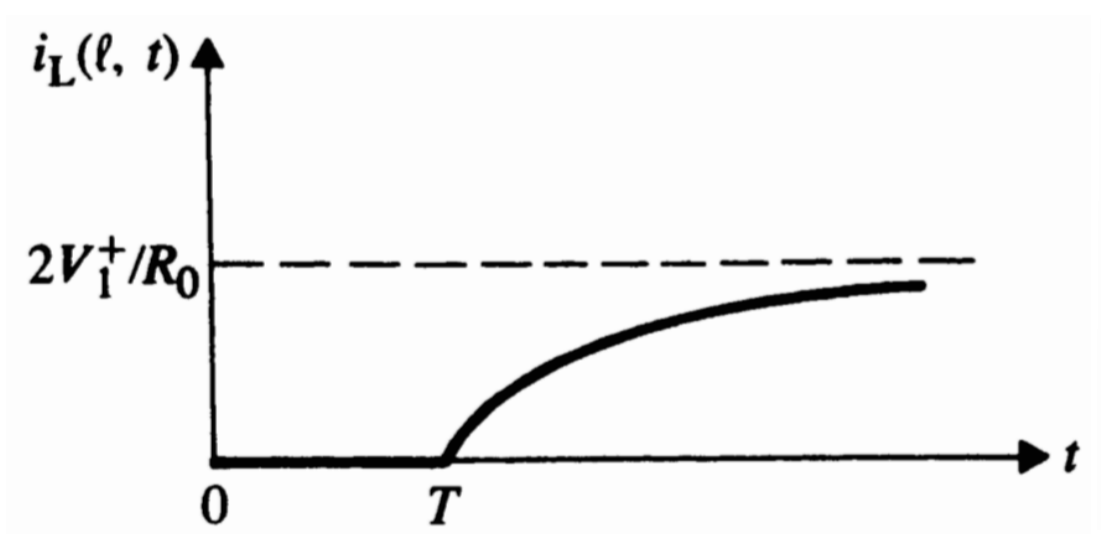

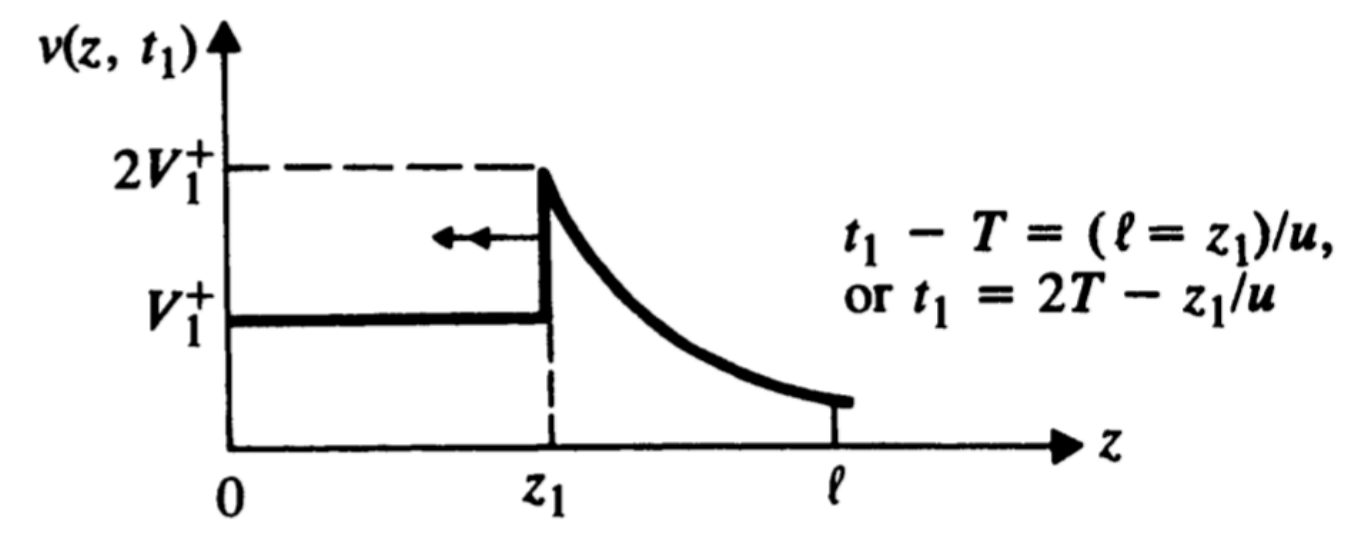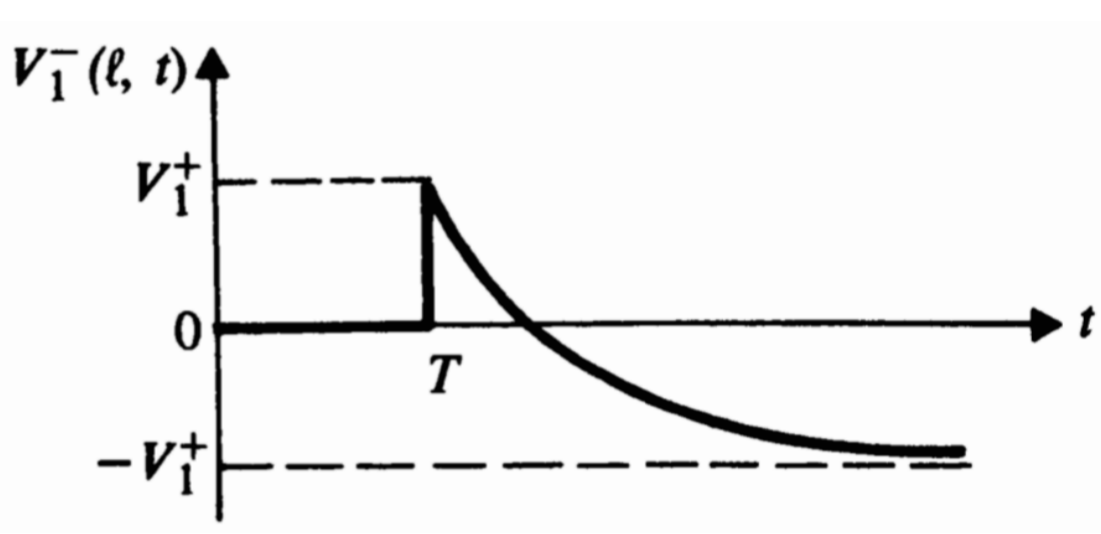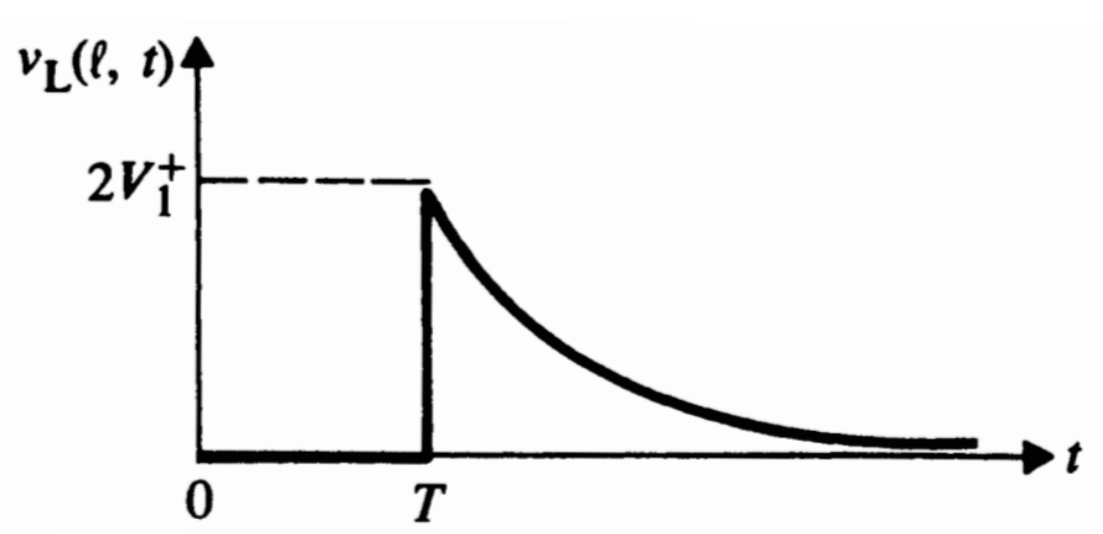↑
Current increases after V_1^+ arrived at $z = l$



<Voltage distribution vs. z at $t = t_1$ >
($T < t_1 < 2T$)