 


Chapter 3


Single-Stage Amplifiers

Analog Design



Non-linear system

Tradeoffs

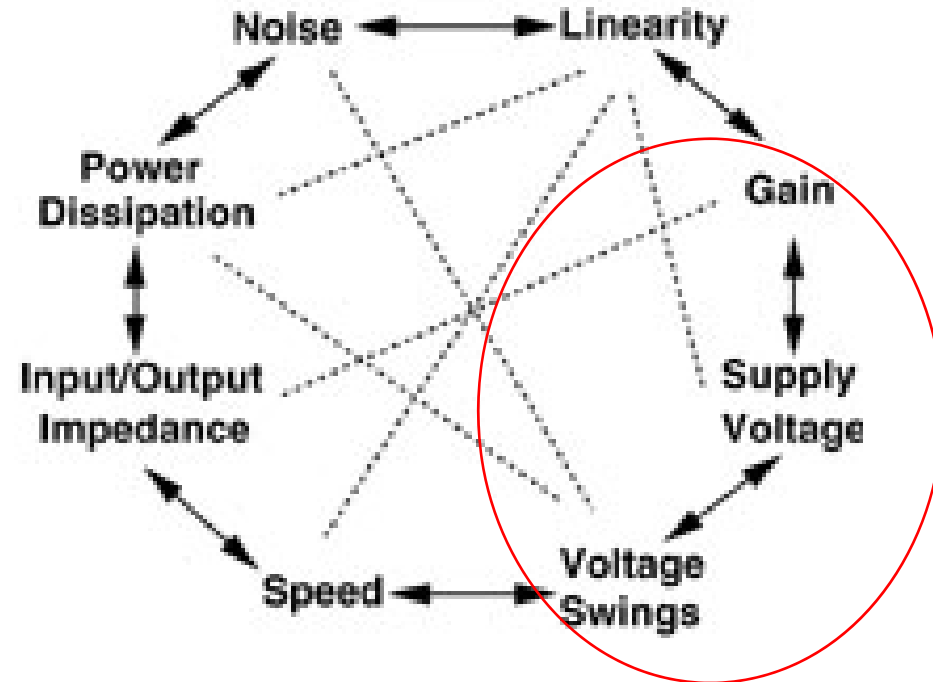

Common-Source (CS) Amplifier With R_D Load

Design Method, Constraints and
Tradeoffs-L5

Simple CS Amplifier

- Given: k_n', V_{TH}, λ
- Need: Specific voltage gain $A_v = -g_m R_D$

Design Parameters:


$$V_{DD}, I_D, V_G, W/L, R_D$$

Constraints:


Saturation Mode

Current-Voltage relationship


Swing

 


(a)

 

(b)

 


(c)

 


(d)


Common Source – Large Signal Analysis

 


(a)

 

(b)

 


(c)

 


(d)

- If V_{in} is low (below threshold) transistor is OFF
- For V_{in} not-too-much-above threshold, transistor is in Saturation, and V_{out} decreases.
- For large enough input ($V_{in} > V_{in1}$) – Triode Mode.

Common Source (cont.)

 

(a)


 


(b)

$$A_v = -g_m R_D$$

$$A_v = -\sqrt{2\mu_n C_{ox} \frac{W}{L}} \frac{V_{RD}}{\sqrt{I_D}}$$



Design Tradeoffs

  

$$A_v = -\sqrt{2\mu_n C_{ox} \frac{W}{L}} \frac{V_{RD}}{\sqrt{I_D}}$$

- Gain is determined by 3 factors: W/L , R_D DC voltage and I_D
- If current and R_D are kept constant, an increase of W/L increases the gain, but it also increases the gate capacitance – lower bandwidth



Design Tradeoffs

  

$$A_v = -\sqrt{2\mu_n C_{ox} \frac{W}{L}} \frac{V_{RD}}{\sqrt{I_D}}$$

- If I_D and W/L are kept constant, and we increase R_D , then V_{DS} becomes smaller. Operating Point gets closer to the borderline of Triode Mode.
- It means – less “swing” (room for the amplified signal)


Design Tradeoffs

  

$$A_v = -\sqrt{2\mu_n C_{ox} \frac{W}{L}} \frac{V_{RD}}{\sqrt{I_D}}$$

- If I_D decreases and W/L and V_{RD} are kept constant, then we must increase R_D
- Large R_D consumes too much space, increases the noise level and slows the amplifier down (time constant with input capacitance of next stage).


Common Source Tradeoffs

 

$$A_v = -g_m r_o \parallel R_D$$

- Larger R_D values increase the influence of channel-length modulation (r_o term begins to strongly affect the gain)

Common Source Maximum Gain

 


$$A_v = -g_m r_o \parallel R_D$$


$$A_v = -g_m r_o$$

"intrinsic gain"

 CS Amplifier with Diode-Connected Load-L6




(a)

 

(b)

- “Diode-Connected” MOSFET is only a name. In BJT if Base and Collector are short-circuited, then the BJT acts exactly as a diode.


CS Amplifier with Diode-Connected Load

 

- We want to replace R_D with a MOSFET that will operate like a small-signal resistor.

$$V_1 = V_X \Rightarrow I_X = \frac{V_X}{r_o} + g_m V_X$$
$$\Rightarrow R_d = \frac{1}{g_m} \parallel r_o \approx \frac{1}{g_m}$$

 
Common Source with Diode-Connected NMOS Load (Body Effect included)



$$(g_m + g_{mb})V_x + \frac{V_x}{r_o} = I_x$$

$$\frac{V_x}{I_x} = \frac{1}{g_m + g_{mb}} \parallel r_o \approx \frac{1}{g_m + g_{mb}}$$

 CS with Diode-Connected NMOS Load Voltage Gain Calculation




$$A_v = -g_{m1} \frac{1}{g_{m2} + g_{mb2}} = -\frac{g_{m1}}{g_{m2}} \frac{1}{1 + \eta}$$

$$A_v = -\sqrt{\frac{2\mu_n C_{OX} (W/L)_1 I_{D1}}{2\mu_n C_{OX} (W/L)_2 I_{D2}}} \frac{1}{1 + \eta}$$

$$A_v = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta}$$

 
CS with Diode-Connected NMOS Load Voltage Gain Calculation



$$A_v = - \sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta}$$

- If variations of η with the output voltage are neglected, the gain is independent of the bias currents and voltages (as long as M_1 stays in Saturation)
- The point: Gain does not depend on V_{in} (as we do in the case of R_D load)

 
Amplifier is relatively linear (even for large signal analysis!)



$$0.5\mu_n c_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = 0.5\mu_n c_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{out} - V_{TH2})^2$$

$$\sqrt{\left(\frac{W}{L}\right)_1} (V_{in} - V_{TH1}) = \sqrt{\left(\frac{W}{L}\right)_2} (V_{DD} - V_{out} - V_{TH2})$$


Assumptions made along the way:

 


$$\sqrt{\left(\frac{W}{L}\right)_1} (V_{in} - V_{TH1}) = \sqrt{\left(\frac{W}{L}\right)_2} (V_{DD} - V_{out} - V_{TH2})$$

- We neglected channel-length modulation effect
- We neglected V_{TH} voltage dependent variations
- We assumed that two transistors are matching in terms of C_{OX} .

Comment about “cutting off”

 



(a)

 

(b)


- If I_1 is made smaller and smaller, what happens to V_{out} ?
- It should be equal to V_{DD} at the end of the current reduction process, or is it?

Comment about “cutting off” (cont’d)

  


- If I_1 is made smaller and smaller, V_{GS} gets closer and closer to V_{TH} .
- Very near $I_1=0$, if we neglect sub-threshold conduction, we should have $V_{GS} \approx V_{TH2}$, and therefore $V_{out} \approx V_{DD} - V_{TH2}$!

Cutoff conflict resolved:

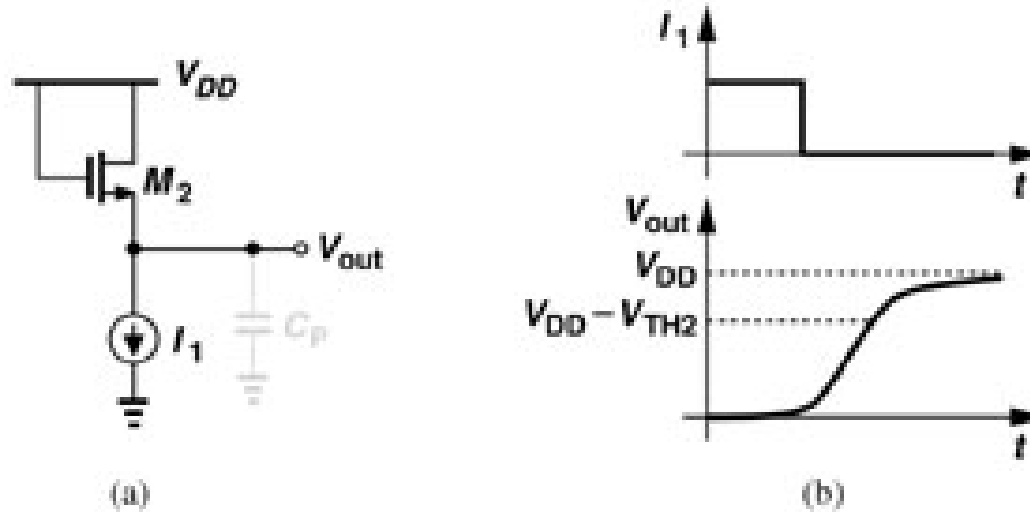


- In reality, sub-threshold conduction, at a very low current, eventually brings V_{out} to the value V_{DD} .
- Output node capacitance slows down this transition.
- In high-speed switching, sometimes indeed V_{out} doesn't make it to V_{DD}

 
Back to large-signal behavior of the CS amplifier with diode-connected NMOS load:


 
$$\sqrt{\left(\frac{W}{L}\right)_1} (V_{in} - V_{TH1}) = \sqrt{\left(\frac{W}{L}\right)_2} (V_{DD} - V_{out} - V_{TH2})$$




 Large signal behavior of CS amplifier with diode-connected load



- When $V_{in} < V_{TH1}$ (but near), we have the above “imperfect cutoff” effect.
- Then we have a, more or less, linear region.
- When V_{in} exceeds $V_{out} + V_{TH1}$ amplifier enters the Triode mode, and becomes nonlinear.

 
CS with Diode-Connected PMOS Load Voltage Gain



$$A_v = - \sqrt{\frac{\mu_n (W / L)_1}{\mu_p (W / L)_2}}$$

No body effect!

Numerical Example

 

- Say that we want the voltage gain to be 10.
Then:

$$A_v = -\sqrt{\frac{\mu_n (W/L)_1}{\mu_p (W/L)_2}} = -10$$

$$\Rightarrow \frac{\mu_n (W/L)_1}{\mu_p (W/L)_2} = 100$$

Example continued

$$\frac{\mu_n (W / L)_1}{\mu_p (W / L)_2} = 100$$

- Typically $\mu_n \approx 2\mu_p$

Example continued


$$\frac{(W / L)_1}{(W / L)_2} \approx 50$$

- Need a “strong” input device, and a “weak” load device.
- Large dimension ratios lead to either a larger input capacitance (if we make input device very wide $(W/L)_1 \gg 1$) or to a larger output capacitance (if we make the load device very narrow $(W/L)_2 \ll 1$).
- Latter option (narrow load) is preferred from bandwidth considerations.

CS with Diode-Connected Load Swing Issues

$$ID1 = ID2, \quad \therefore$$
 
$$\mu_n \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{TH1})^2 \approx \mu_p \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{TH2})^2$$




$$A_v = - \sqrt{\frac{\mu_n (W/L)_1}{\mu_p (W/L)_2}} \approx \frac{|V_{GS2} - V_{TH2}|}{(V_{GS1} - V_{TH1})}$$

This implies substantial voltage swing constraint. Why?

Numerical Example to illustrate the swing problems


- Assume for instance $V_{DD}=3V$
- Let's assume that $V_{GS1}-V_{TH1}=200mV$ (arbitrary selection, consistent with current selection)
- Assume also that $|V_{TH2}|=0.7V$ (for PMOS load $V_{TH2}=-0.7V$)
- For a gain of 10, we now need $|V_{GS2}|=2.7V$ (for PMOS load $V_{GS2}<-2.7V$)
- Therefore because $V_{GD2}=0$: $V_{DS2}=V_{GS2}=-2.7V$.
- Now $V_{DS1}=V_{DD}-V_{SD2}<3-2.7=0.3V$, and recall that $V_{DS1}>V_{GS1}-V_{TH1}=0.2V$. Not much room left for the amplified signal v_{ds1} .

DC Q-Point of the Amplifier

 


- V_{G1} determines the current and the voltage V_{GS2}
- If we neglect the effect of the transistors' λ , the error in predicting the Q-point solution may be large!

 CS with Diode-Connected Load –How do we take into account λ ?



 
$$A_v = -g_{m1} \left(\frac{1}{g_{m2} + g_{mb2}} \parallel r_{o1} \parallel r_{o2} \right)$$




$$A_v = -g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{o1} \parallel r_{o2} \right)$$

 Example as Introduction to Current Source Load



- M_1 is biased to be in Saturation and have a current of I_1 .
- A current source of $I_S=0.75I_1$ is hooked up in parallel to the load – does this addition ease up the amplifier's swing problems?

 
Example as Introduction to Current Source Load



- Now $I_{D2} = I_1/4$. Therefore (from the ratio of the two transconductances with different currents):

$$A_v \approx - \sqrt{\frac{4\mu_n (W/L)_1}{\mu_p (W/L)_2}}$$

Example: Swing Issues

 


$$I_{D1} = 4I_{D2}, \quad \therefore$$

$$\mu_n \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{TH1})^2 \approx 4\mu_p \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{TH2})^2$$


$$\frac{A_v}{4} \approx \frac{|V_{GS2} - V_{TH2}|}{(V_{GS1} - V_{TH1})}$$

It sure helps in terms of swing.

CS Amplifier with Current-Source Load-L7

 

 
How can V_{in} change the current of M_1 if I_1 is constant?




$$I_{D1} = 0.5\mu_n c_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 (1 + \lambda V_{out}) = I_1$$

- As V_{in} increases, V_{out} must decrease

 Simple Implementation: Current Source obtained from M_2 in Saturation




CS with Current Source Load

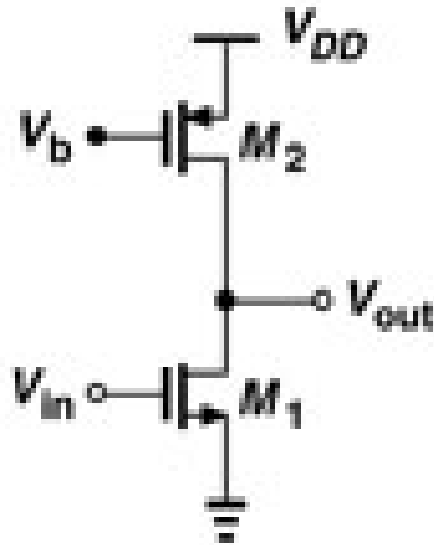

$$A_v = -g_m (r_{o1} \parallel r_{o2})$$


DC Conditions

 

$$\begin{aligned} I_{D1} &= 0.5\mu_n c_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 (1 + \lambda_1 V_{out}) = I_{D2} \\ &= 0.5\mu_p c_{ox} \left(\frac{W}{L}\right)_2 (V_b - V_{DD} - V_{TH2})^2 (1 + \lambda_2 [V_{out} - V_{DD}]) \end{aligned}$$

- $\{(W/L)_1, V_{G1}\}$ and $\{(W/L)_2, V_b\}$ need to be more or less consistent, if we wish to avoid too much dependence on λ values.
- Need DC feedback to fix better the DC V_{out}


Swing Considerations

 

$$\begin{aligned} I_{D1} &= 0.5\mu_n c_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 (1 + \lambda_1 V_{out}) = I_{D2} \\ &= 0.5\mu_p c_{ox} \left(\frac{W}{L}\right)_2 (V_b - V_{DD} - V_{TH2})^2 (1 + \lambda_2 [V_{out} - V_{DD}]) \end{aligned}$$

- We can make $|V_{DS2}| > |V_{GS2} - V_{TH2}|$ small (say a few hundreds of mV), if we compensate by making W_2 wider.

How do we make the gain large?

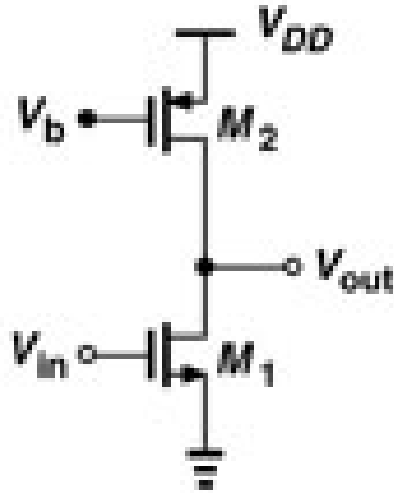


$$A_v = -g_m (r_{o1} \parallel r_{o2})$$

- Recall: λ is inversely proportional to the channel length L .
- To make λ values smaller (so that r_o be larger) need to increase L . In order to keep the same current, need to increase W by the same proportion as the L increase.

CS Amplifier with Current-Source Load Gains


- Typical gains that such an amplifier can achieve are in the range of -10 to -100.
- To achieve similar gains with a R_D load would require much larger V_{DD} values.
- For low-gain and high-frequency applications, R_D load may be preferred because of its smaller parasitic capacitance (compared to a MOSFET load)

Numerical Example

 


- Let W/L for both transistors be $W/L = 100\mu\text{m} / 1.6\mu\text{m}$
- Let $\mu_n C_{ox} = 90\mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 30\mu\text{A}/\text{V}^2$
- Bias current is $I_D = 100\mu\text{A}$

Numerical Example (Cont'd)

 

- Let $r_{o1} = 8000L/I_D$ and $r_{o2} = 12000L/I_D$ where L is in μm and I_D is in mA .
- What is the gain of this stage?

Numerical Example (Cont'd)

 

$$g_{m1} = \sqrt{2\mu_n C_{OX} (W/L)_1 I_D} = 1.06 \text{ mA/V}$$


$$r_{o1} = 8000 \cdot 1.6 / 0.1 = 128 \text{ K}\Omega$$

$$r_{o2} = 12000 \cdot 1.6 / 0.1 = 192 \text{ K}\Omega$$

$$A_V = -g_{m1} (r_{o1} \parallel r_{o2}) = -81.4$$

How does L influence the gain?


$$A_v = -g_m r_{o1} \parallel r_{o2}$$

 

Assuming r_{o2} large,

$$A_v \approx -g_m r_{o1} = -\sqrt{2\mu_n C_{ox} I_D} \left(\frac{W}{L}\right)_1 \frac{1}{\lambda I_D}$$


How does L influence the gain?

 

$$A_v \approx -g_m r_{o1} = -\sqrt{2\mu_n C_{ox} I_D} \left(\frac{W}{L}\right)_1 \frac{1}{\lambda_1 I_D}$$

- As L_1 increases the gain increases, because λ_1 depends on L_1 more strongly than g_{m1} does!
- As I_D increases the gain decreases.
- Increasing L_2 while keeping W_2 constant increases r_{o2} and the gain, but $|V_{DS2}|$ necessary to keep M_2 in Saturation increases.


CS with Triode Region Load

 

$$A_v = -g_{m1} R_{ON2}$$

$$R_{ON2} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_b + V_{TH2})}$$

How should V_b be chosen?

 

- M_2 must conduct: $V_b - V_{DD} \leq V_{TH2}$, or $V_b \leq V_{DD} + V_{TH2}$
- M_2 must be in Triode Mode: $V_{out} - V_{DD} \leq V_b - V_{DD} - V_{TH2}$, or $V_b \geq V_{out} + V_{TH2}$
- M_2 must be “deep inside” Triode Mode: $2(V_b - V_{DD} - V_{TH2}) \gg V_{out} - V_{DD}$, or: $V_b \gg V_{DD}/2 + V_{TH2} + V_{out}/2$
- Also V_b and $(W/L)_2$ determine the desired value of R_{on2}



It's not easy at all to determine
(and implement) a working value
for V_b

CS Amplifiers with Triode Region
load is rarely used

CS Amplifier with Source Degeneration-L9

The effects of adding a resistor R_S between Source and ground.

CS Amplifier with Source Degeneration

  


$$G_m \approx \frac{g_m}{1 + g_m R_S}$$

$$A_v = -G_m R_D$$


$$A_v \approx \frac{-g_m R_D}{1 + g_m R_S}$$

Summary of key formulas,
Neglecting
Channel-Length Modulation and
Body Effect


Linearizing effect of R_S :

 
 
$$A_v = \frac{-g_m R_D}{1 + g_m R_S} = -\frac{R_D}{1/g_m + R_S}$$




(a)

 

(b)

Linearizing effect of R_S :
 
$$A_v = \frac{-g_m R_D}{1 + g_m R_S} = -\frac{R_D}{1/g_m + R_S}$$



- For low current levels $1/g_m \gg R_S$ and therefore $G_m \approx g_m$.
- For very large V_{in} , if transistor is still in Saturation, G_m approaches $1/R_S$.


Estimating Gain by Inspection




$$A_v = \frac{-g_m R_D}{1 + g_m R_S} = -\frac{R_D}{1/g_m + R_S}$$

- Denominator: Resistance seen the Source path, “looking up” from ground towards Source.
- Numerator: Resistance seen at Drain.

Example to demonstrate method:

 


(a)

 

(b)

- Note that M_2 is “diode-connected”, thus acting like a resistor $1/g_{m2}$
- $A_V = -R_D / (1/g_{m1} + 1/g_{m2})$

 CS Amplifier with Source Degeneration Key Formulas with λ and Body-Effect Included




$$G_m = \frac{g_m}{\frac{R_S}{r_o} + [1 + (g_m + g_{mb})R_S]}$$

$$R_{OUT} = [1 + (g_m + g_{mb})r_o]R_S + r_o$$

$$A_v = -G_m (R_D \parallel R_{OUT})$$

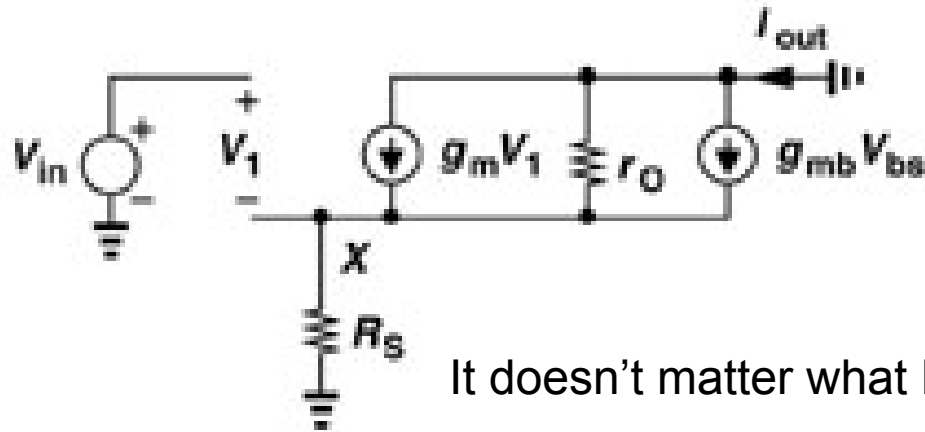
Derivation is similar to that of the simplified case – generalized transconductance



It doesn't matter what R_D is because we treat I_D as "input"

$$\begin{aligned}
 I_D &= g_m V_1 + g_{mb} V_{bs} + I_{ro} \\
 &= g_m V_1 - g_{mb} V_X - \frac{I_D R_S}{r_o} \\
 &= g_m (V_{in} - I_D R_S) + g_{mb} (-I_D R_S) - \frac{I_D R_S}{r_o} \\
 \Rightarrow G_m &= \frac{I_D}{V_{in}} = \frac{g_m r_o}{R_S + [1 + (g_m + g_{mb}) R_S] r_o}
 \end{aligned}$$


R_S effect on CS Output Resistance

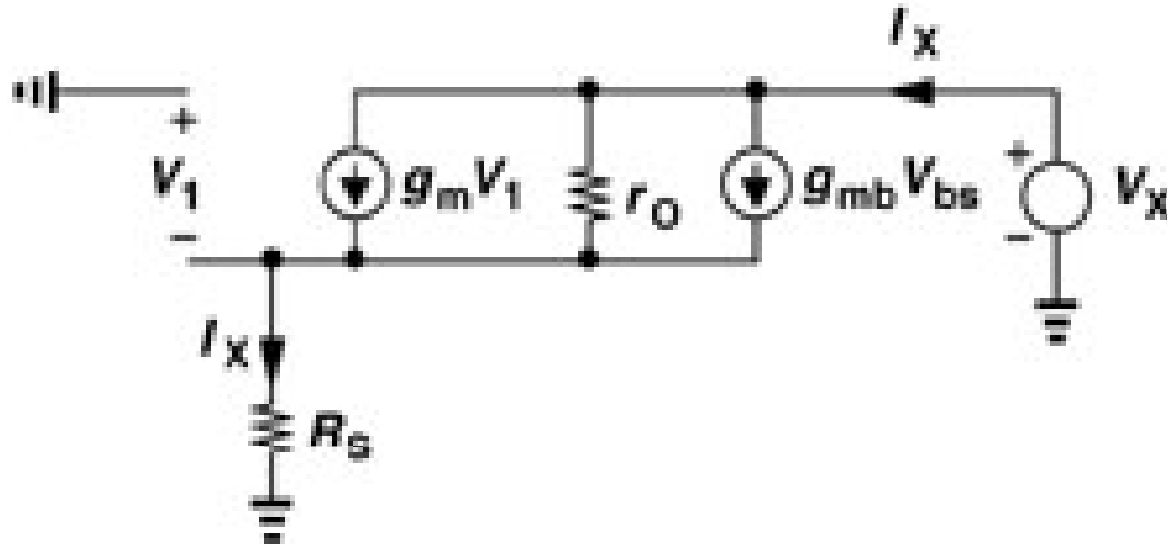

$$\begin{aligned} I_X &= g_m V_1 + g_{mb} V_{bs} + I_{r_o} \\ &= g_m (-I_X R_S) - g_{mb} I_X R_S + I_{r_o} \end{aligned}$$

$$V_X = r_o (I_X + (g_m + g_{mb}) R_S I_X) + I_X R_S$$

CS Output Resistance

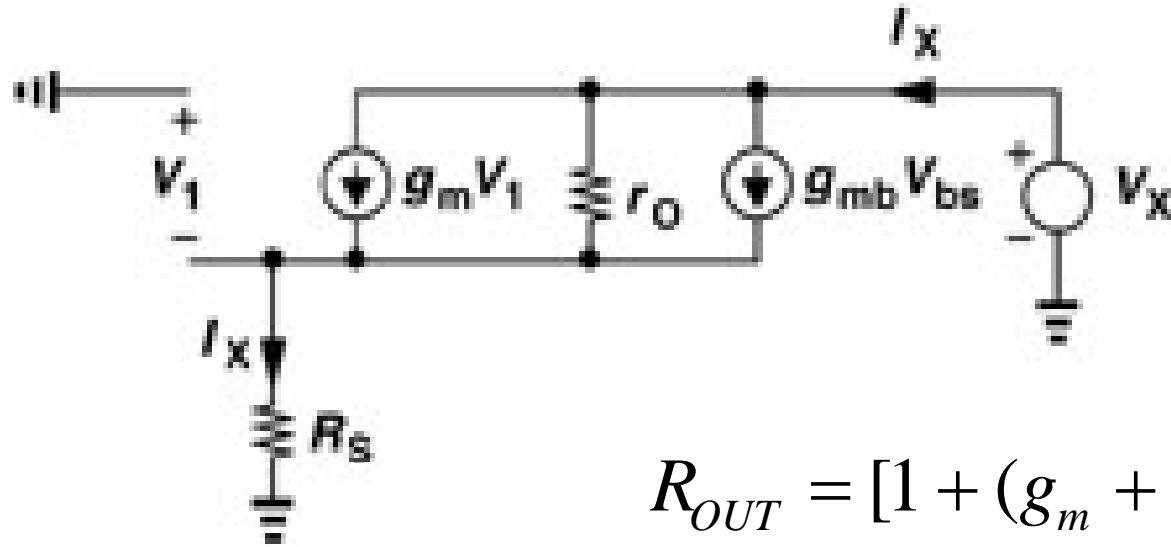


$$R_{OUT} = [1 + (g_m + g_{mb})r_o]R_S + r_o$$

$$R_{OUT} = r_o' \approx r_o [1 + (g_m + g_{mb})R_S]$$

R_S causes a significant increase in the output resistance of the amplifier

 CS Amplifier with Source Degeneration Gain Formula with λ and Body-Effect Included



$$G_m = \frac{g_m}{\frac{R_S}{r_o} + [1 + (g_m + g_{mb})R_S]}$$

$$R_{OUT} = [1 + (g_m + g_{mb})r_o]R_S + r_o$$

$$A_v = -G_m (R_D \parallel R_{OUT})$$

Source Follower



Main use: Voltage Buffer

- To achieve a high voltage gain with limited supply voltage, in a CS amplifier, the load impedance must be as large as possible.
- If such a stage is to drive a low impedance load, then a “buffer” must be placed after the amplifier so as to drive the load with negligible loss of the signal level.
- The source follower (also called the “common-drain” stage) can operate as a voltage buffer.

Buffering Action



- Input resistance of source follower is large.
- CS amplifier, connected to a Source Follower, will see as a load R_{in} of the Source Follower.
- R_{in} of the Source Follower is unaffected by R_L of the Source Follower. Variations in R_L has no effect on R_{in} of the MOSFET.

Source Follower with R_S resistance

  



- Source Follower: Input signal comes into the Gate; Output signal comes out of the Source.
- Load connected between Source and ground.

  Source Follower with R_S resistance: Large Signal Behavior





- If $V_{in} < V_{TH}$ M_1 is off.
- As V_{in} exceed V_{TH} M_1 is in Saturation.
- M_1 goes into Triode Mode only when V_{in} exceeds V_{DD} .

Why V_{out} follows V_{in} ?

  

- Source followers exhibit a Body Effect: As I_D increases, $V_S = I_D R_S$ increases. As V_{SB} increases, V_{TH} increases.


Why V_{out} follows V_{in} ? (Cont'd)

  


- If V_{in} slightly increases, I_D slightly increases and therefore V_{out} slightly increases.
- As I_D increases V_{TH} increases due to Body Effect.
- FACT: V_{GS} increases but not at the same rate that V_{in} increases.

Source Follower Gain

Source Follower Gain

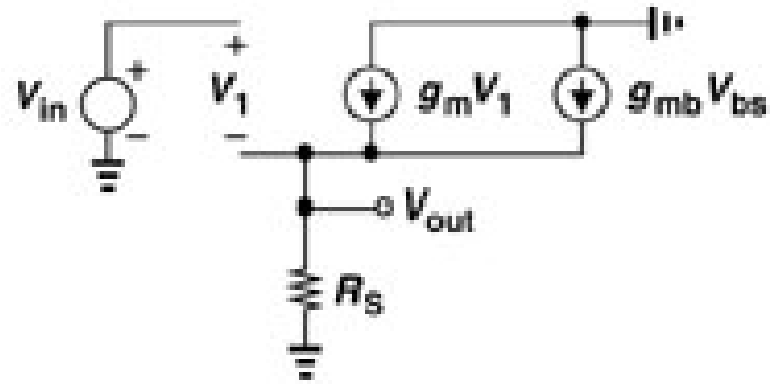


Gain Dependence on V_G

 



- When V_G is slightly above V_{TH} , g_m is very small, and therefore A_v is small.
- When g_m becomes large enough (i.e. $g_m R_S \gg 1$), then A_v approaches $1/(1+\eta)$.

Gain Dependence on V_G (cont'd)

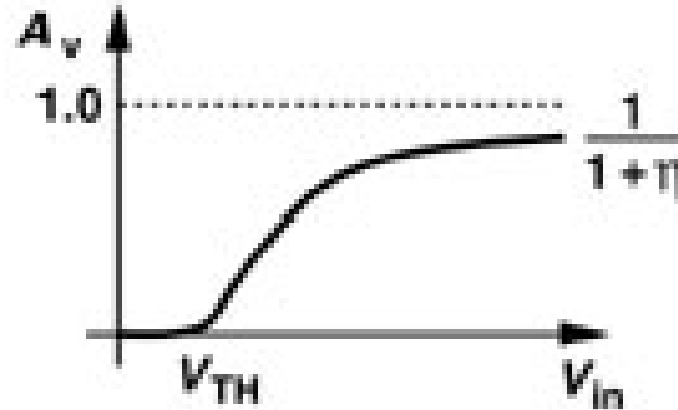



- Recall $\eta = \gamma / (2(2\Phi_F + V_{SB})^{1/2}) = \gamma / (2(2\Phi_F + V_{out})^{1/2})$
- As V_G increases, and V_{out} increases, η decreases, and the gain may approach 1.
- In most practical circuits η remains >0.2 .

Source Follower with Current Source Load

  


- Left: Conceptual diagram
- Right: Actual implementation, using a NMOS operating in Saturation Mode.

Example

  

- Let $(W/L)_1=20/0.5$, $I_1=200\mu\text{A}$, $V_{THO}=0.6\text{V}$, $2\Phi_F=0.7\text{V}$, $\mu_n C_{OX}=50\mu\text{A}/\text{V}^2$, $\gamma=0.4\text{V}^{1/2}$
- Let $V_{in}=1.2\text{V}$, what is V_{out} ?

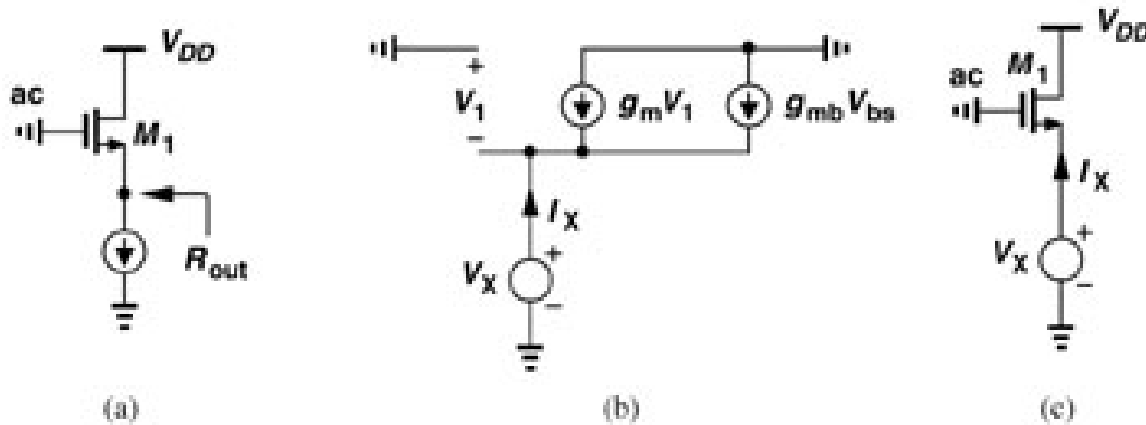
Output Resistance of the Ideal Source Follower with Current Source Load



$$V_1 = -V_X \Rightarrow I_X - g_m V_X - g_{mb} V_X = 0$$


$$R_{out} = \frac{1}{g_m + g_{mb}}$$

 Output Resistance of the Ideal Source Follower with Current Source Load becomes smaller with the help of the Body Effect!




- Only in a Source Follower the current source $g_{mb} V_{bs}$ is equivalent to a resistor $1/g_{mb}$ in parallel to the output.

 Gain of Source Follower with Ideal Current Source Load




$$A_V = \frac{g_m}{g_m + g_{mb}}$$

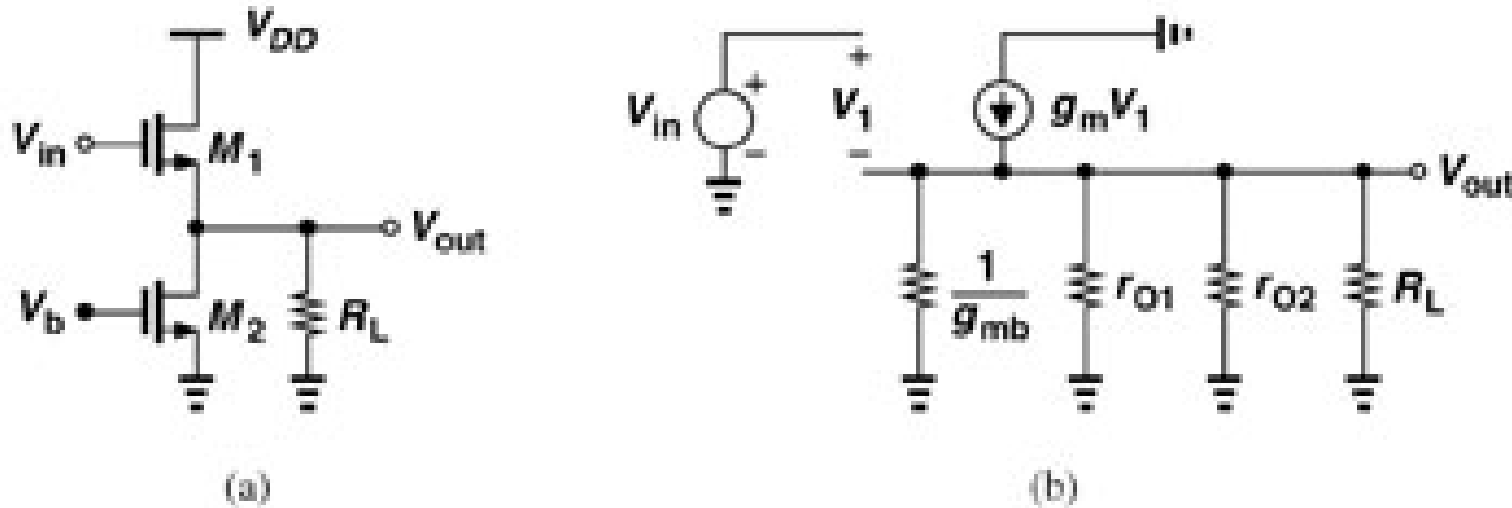Gain Formula: NMOS Source Follower with NMOS Current Source and R_L Loads



$$A_v = \frac{\frac{1}{g_{mb1}} \parallel r_{o1} \parallel r_{o2} \parallel R_L}{\left(\frac{1}{g_{mb1}} \parallel r_{o1} \parallel r_{o2} \parallel R_L\right) + \frac{1}{g_{m1}}}$$

 Gain Formula: NMOS Source Follower with PMOS Current Source Load




$$A_v = \frac{\frac{1}{g_{mb1}} \parallel r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}}}{\left(\frac{1}{g_{mb1}} \parallel r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right) + \frac{1}{g_{m1}}}$$

Sources of Nonlinearities in NMOS Source Followers


- Body Effect in the driving NMOS transistor causes V_{TH} to vary with V_{in}
- Are we allowed to connect substrate to source in the driving NMOS? (to eliminate the body effect). Answer: No! All NMOS transistors in the entire circuit share the same substrate, so it has to be grounded!
- r_o resistors vary with V_{DS} . Problem becomes more and more aggravated as L becomes smaller and smaller

PMOS Source Follower

 


- Key idea: PMOS transistors have each a separate substrate. Each can be powered differently

 CMOS fabrication process: All NMOS share the same substrate, each PMOS has a separate substrate




(a)

 


(b)

PMOS Source Follower Advantage

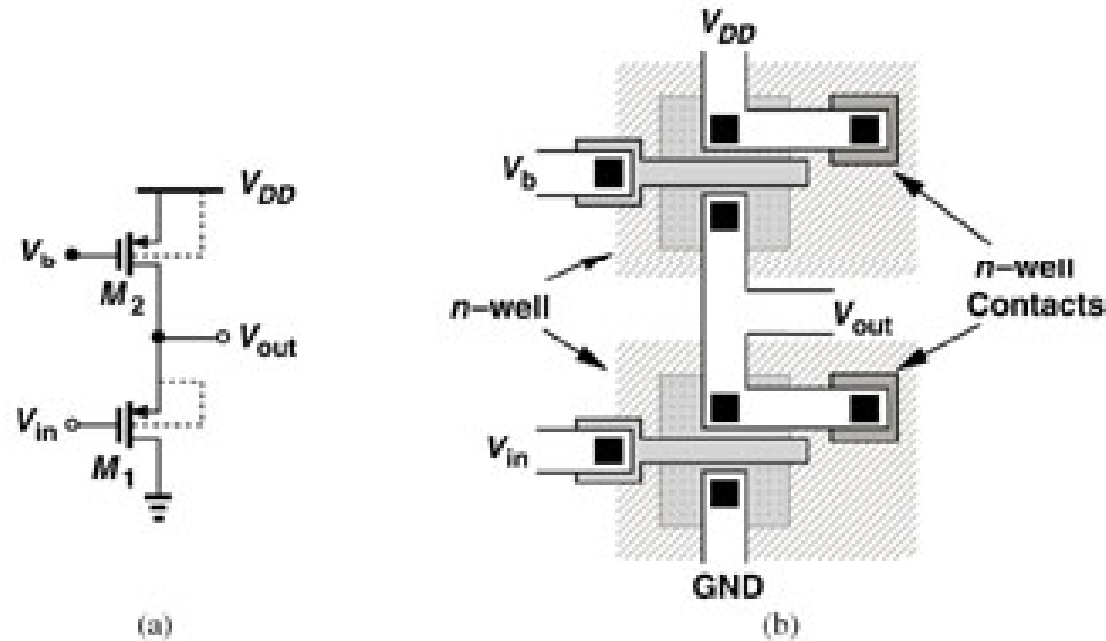


- Body Effects eliminated – device is more linear than NMOS Source Follower

PMOS Source Follower Drawbacks

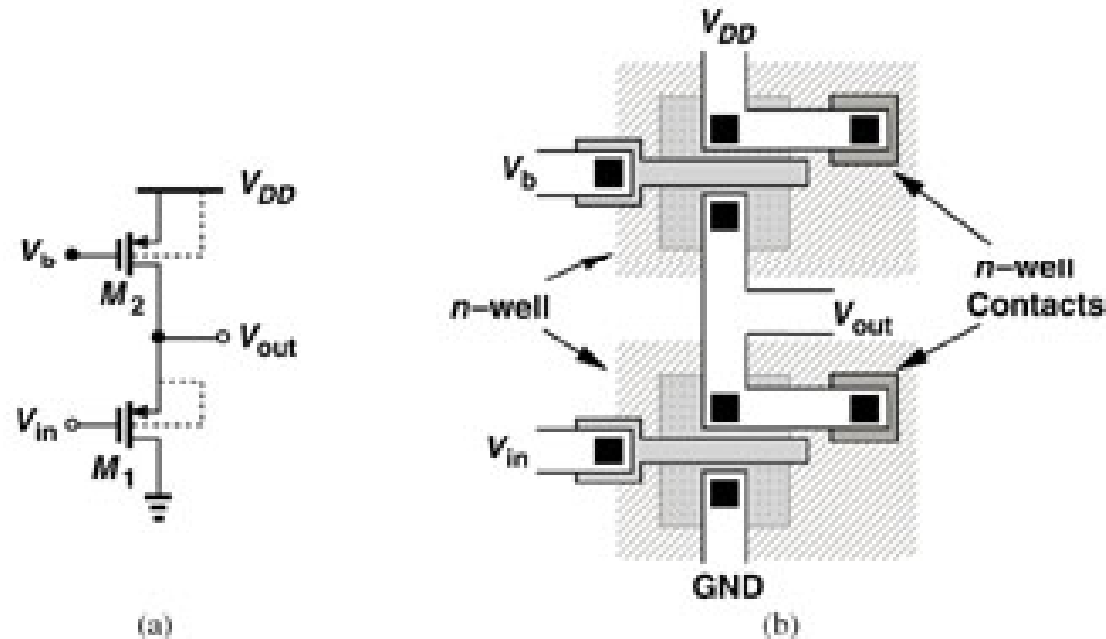


- PMOS carriers mobility is smaller than that of NMOS.
- As a result of mobility differences: PMOS source followers have larger output resistance, than NMOS followers.

 CS Amplifier directly driving a Source Follower: DC levels considerations




- CS Amplifier alone: $V_X \geq V_{GS1} - V_{TH1}$ to assure that M_1 is in Saturation.
- With Source Follower: $V_X \geq V_{GS2} + (V_{GS3} - V_{TH3})$ to assure that M_3 is in Saturation.

 CS Amplifier directly driving a Source Follower: DC levels considerations




- If $V_{GS1} - V_{TH1} \approx V_{GS3} - V_{TH3}$ then $V_{X, \text{with Source Follower}}$ must be bigger than $V_{X, \text{without Source Follower}}$ by about V_{GS2} .
- Swing of CS reduces by V_{GS2} .

Source Followers as Level Shifters

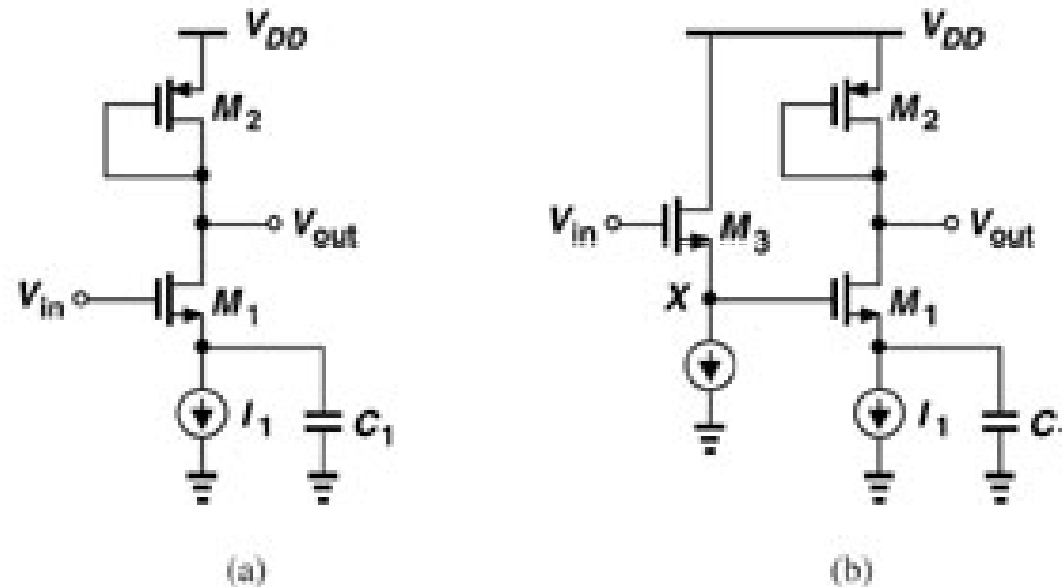


- Example (a): DC level of V_{in} cannot exceed $V_{DD} - |V_{GS2}| + V_{TH1}$
- Example (b): If V_{in} has a DC level of around V_{DD} , we put first a Source Follower.

Source Followers as Level Shifters

 



(a)

 


(b)

- If $V_{in} \approx V_{DD}$, then for M_1 to be in Saturation, we need: $V_{DD} - V_{GS3} - V_{TH1} \leq V_{DD} - |V_{GS2}|$

Common-Gate Amplifier-L12

  


CG Amplifier: Input-Output Structure

 

- Input signal goes into Source
- Output signal comes out of Drain.
- It is called Common-Gate because in the small signal model Gate is grounded.

 CG Amplifier: Two types of input signal interface




- (a): Direct coupling: DC bias current of M_1 flows through the input signal source.
- (b): Coupling (large) capacitor: Bias current is independent of the input signal source.


CG Amplifier's Properties

- Voltage gain comparable to that of a CS amplifier.
- Current gain of 1 – amplifier is used as current buffer.
- Small input resistance
- Large output resistance
- Bandwidth much larger than that of a CS amplifier.

 
CG Amplifier with R_D load – Large Signal Analysis



(a)

 


(b)

 


- In (a), if DC part of $V_{in} \geq V_b - V_{TH}$ transistor is in Cutoff.
- If M_1 in Saturation, and V_{in} decreasing, then V_{out} decreasing too.

 
CG Amplifier with R_D load – Large Signal Analysis



(a)

 


(b)

 


- Saturation:
- $V_{out} = V_{DD} - 0.5\mu_n C_{OX}(W/L)(V_b - V_{in} - V_{TH})^2 R_D$
- Small-Signal Voltage Gain derivation:
- $dV_{out}/dV_{in} = -\mu_n C_{OX}(W/L)(V_b - V_{in} - V_{TH})(-1 - dV_{TH}/dV_{in})R_D$
- Note: $dV_{TH}/dV_{in} = dV_{TH}/dV_{SB} = \eta$

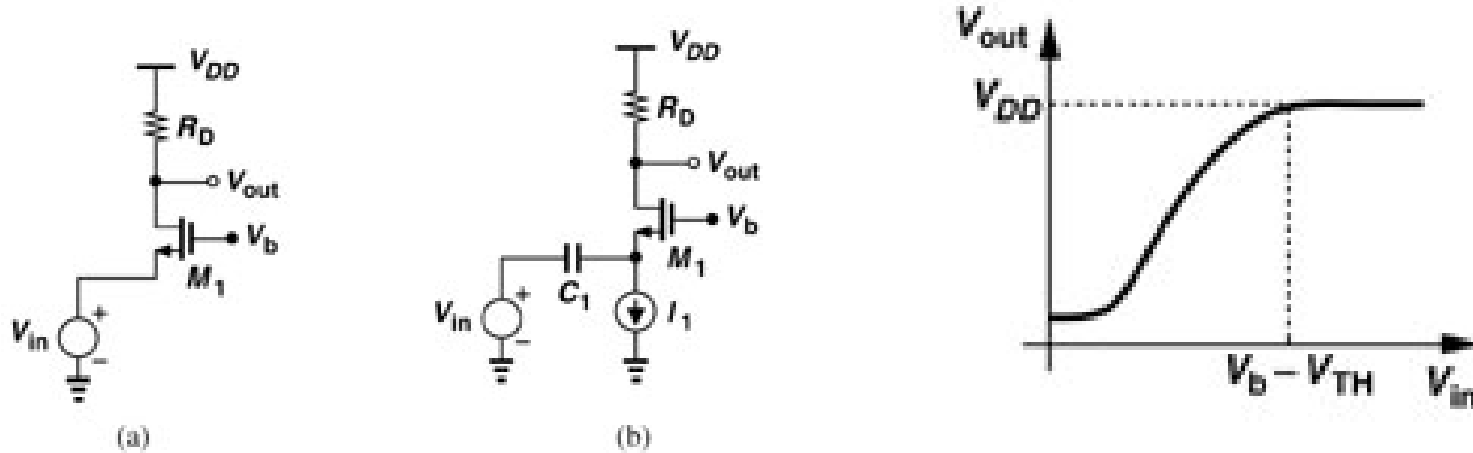CG Amplifier with R_D load – Small-Signal Voltage Gain




- $dV_{out}/dV_{in} = \mu_n C_{OX}(W/L)(V_b - V_{in} - V_{TH})(1 + \eta)R_D$
- $A_V = dV_{out}/dV_{in} = g_m(1 + \eta)R_D$
- Same order of magnitude as CS gain, however it is positive.
- Can you derive it from the small-signal model?

 
CG Amplifier with R_D load – Small-Signal Input Resistance



(a)

 


(b)

 


- If $\lambda=0$ then
- $R_{in} = 1/(g_m + g_{mb}) = 1/[g_m(1 + \eta)]$
- Body effect makes gain larger and R_{in} smaller – this is good! However – it adds nonlinearity.

 Low R_{in} of CG Amplifiers is useful if signal comes from a transmission line






- Assume: 50Ω transmission line
- If $\lambda=\gamma=0$, then theoretically both circuits have the same voltage gain $A_V \approx -g_m R_D$.
- In (a): If $R_D \neq 50\Omega$ there will be reflections (see simulations)

 Low R_{in} of CG Amplifiers is useful if signal comes from a transmission line




- In (b): R_{in} of M_2 is set to 50Ω to prevent reflections.
- R_D can be much larger to determine the desired gain.

 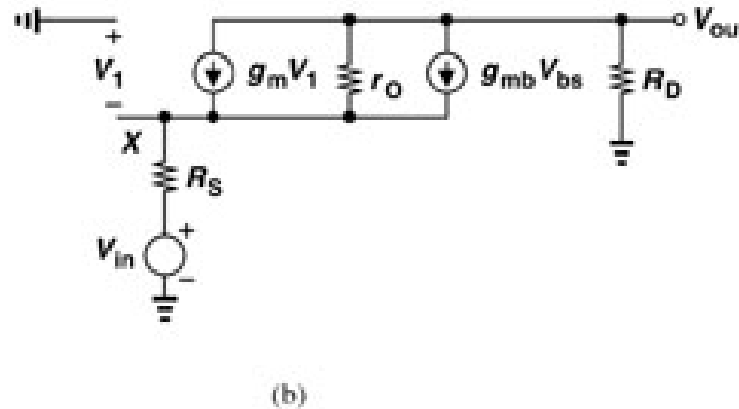 Common Gate Amplifier – Output Resistance



$$R_{out} = \{ [1 + (g_m + g_{mb})r_o]R_S + r_o \} \parallel R_D$$

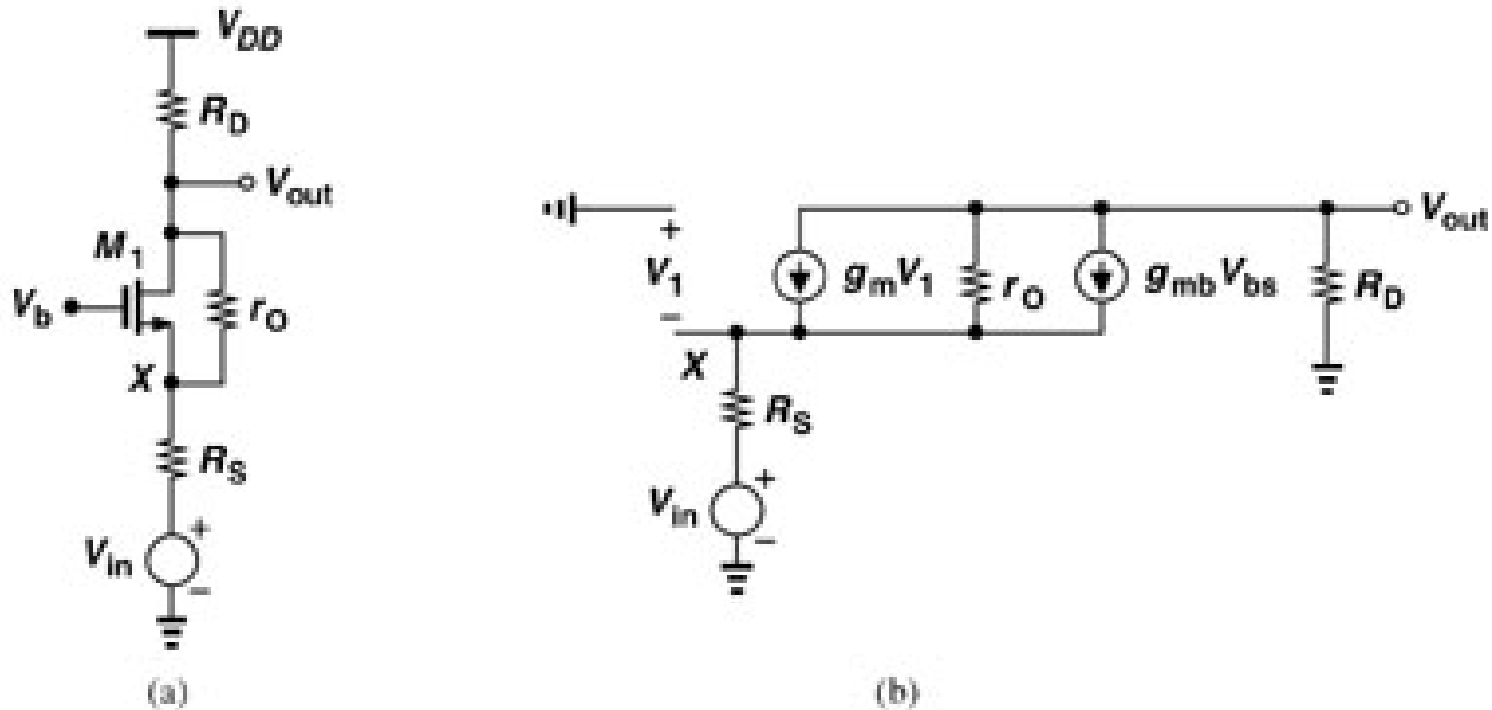Common Gate Voltage Gain, taking into account r_o and V_{in} source resistance



$$A_v = \frac{(g_m + g_{mb})r_o + 1}{r_o + (g_m + g_{mb})r_o R_S + R_S + R_D} R_D$$


Common Gate Gain and R_{in} taking r_o into account, and assuming ideal signal source

$$A_v = \frac{(g_m + g_{mb})r_o + 1}{r_o + (g_m + g_{mb})r_o R_S + R_S + R_D} R_D$$


$$A_v \approx (g_m + g_{mb})(r_o \parallel R_D), \quad R_S = 0$$

$$R_{in} = r_o \parallel \frac{1}{g_m} \parallel \frac{1}{g_{mb}}$$

Cascode Amplifier-L13,L14

 


Cascode Amplifier

 

- M_1 generates small-signal drain current proportional to V_{in} .
- M_2 routes the current to the load R_D

Cascode Amplifier

 


- M_1 is the **input device** (CS amplifier with small load resistance)
- M_2 is the **Cascode device**

Properties of Cascode Amplifiers


- Same voltage gain and input resistance as a CS amplifier.
- Output resistance much larger than that of CS or CG amplifiers.
- Bandwidth much larger than that of a CS amplifier.

 Cascode amplifier – Bias Conditions: How big should V_b be?




- M_1 in Saturation: $V_X \geq V_{in} - V_{TH1}$. That is:
- $V_b - V_{GS2} \geq V_{in} - V_{TH1}$

 Cascode amplifier – Bias Conditions: How big should V_{out} be?





- M_2 in Saturation: $V_{out} \geq V_b - V_{TH2}$. That is:
- $V_{out} \geq V_{in} - V_{TH1} + V_{GS2} - V_{TH2}$ if V_b places M_1 at edge of Triode Mode. This is the minimum V_{out}

Cascode amplifier – Reduced Swing

 



- Tradeoff: For all the nice properties of Cascode, the “stacking” of M_2 on top of M_1 reduces the swing.

Cascode Large Signal Analysis - Cutoff

  



- If $V_{in} \leq V_{TH1}$ both transistors are off.
- $V_{out} = V_{DD}$
- If no sub-threshold conduction, then $V_x \approx V_b - V_{TH2}$! (as explained for CS with diode-connected load)

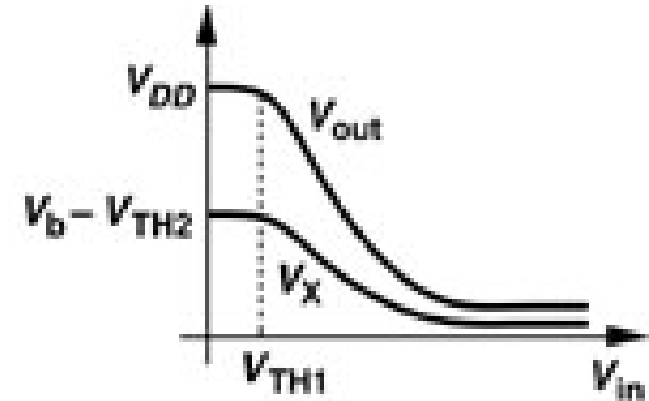 Cascode Large Signal Analysis – Saturation Mode





- As $V_{in} \geq V_{TH1}$ a current develops. V_{out} must drop.
- As I_D increases, V_{GS2} increases, causing V_x to fall.
- As we keep increasing V_{in} which transistor enters Triode Mode first?

  Cascode Large Signal Analysis – Edge of Triode Mode




- As we keep increasing V_{in} which transistor enters Triode Mode first?
- Either one may, depending on the parameters and R_D, V_b

  Cascode Large Signal Analysis – Edge of Triode Mode



- If V_x falls below $V_{in} - V_{TH1}$ then M_1 goes into Triode Mode.
- If V_{out} drops below $V_b - V_{TH2}$ then M_2 goes into Triode Mode.
- For instance, if V_b is low, M_1 enters Triode first.

 
Cascode Voltage Gain Formula if we neglect λ effects




$$A_V \approx -g_{m1} R_D$$

Gain independent of g_{m2} and body effect of M_2 !

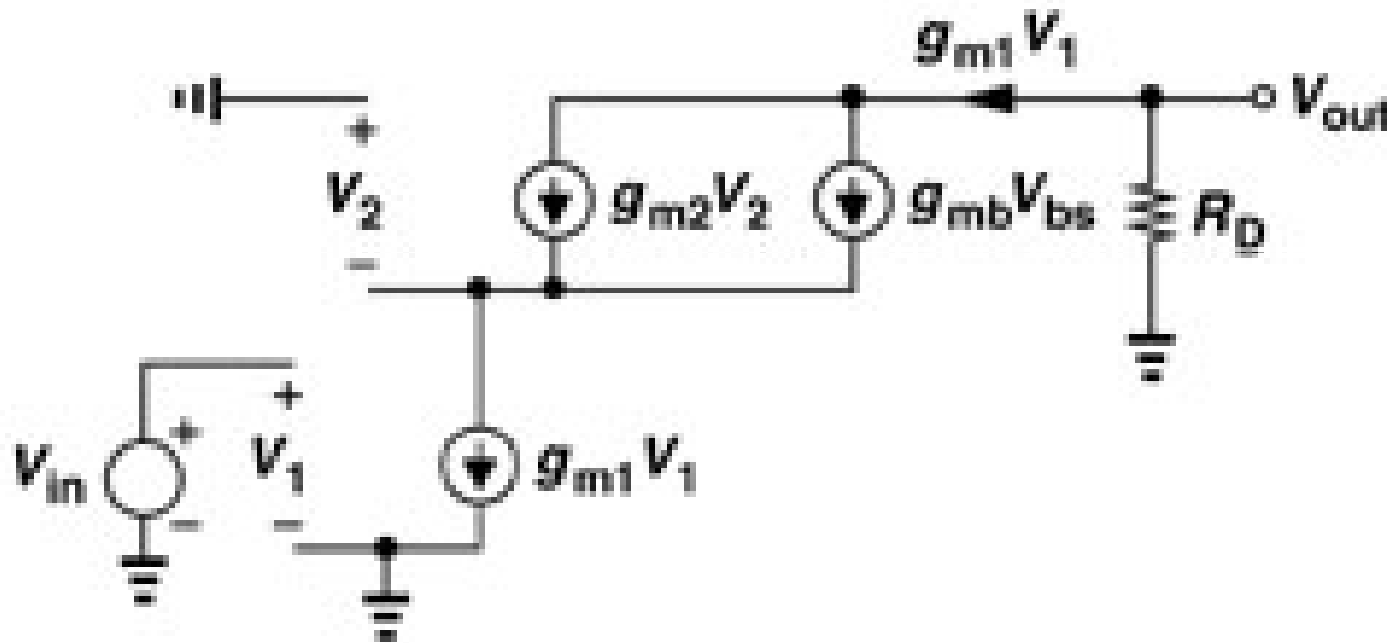Small-Signal Equivalent Circuit of Cacode Stage




Cascode's Output Resistance

 

$$R_{out} = [1 + (g_{m2} + g_{mb2})r_{o2}]r_{o1} + r_{o2}$$
$$\approx r_{o1}r_{o2}(g_{m2} + g_{mb2})$$

Cascode Gain taking into account r_o resistors

 Recall the generalized gain formula $A_V = G_m R_{out}$ discussed in the context of CS amplifier with R_S




$$R_{out} = \{ [1 + (g_{m2} + g_{mb2})r_{o2}]r_{o1} + r_{o2} \} \parallel R_D$$

$$\approx [r_{o1}r_{o2}(g_{m2} + g_{mb2})] \parallel R_D$$

$$A_V \approx -g_{m1} \{ [r_{o1}r_{o2}(g_{m2} + g_{mb2})] \parallel R_D \}$$


Cascode Gain Example

 

$$R_{out} = [1 + (g_{m2} + g_{mb2})r_{o2}]r_{o1} + r_{o2}$$
$$\approx r_{o1}r_{o2}(g_{m2} + g_{mb2})$$


$$A_V \approx -g_{m1}r_{o1}r_{o2}(g_{m2} + g_{mb2})$$

Cascoding extended

 


Can achieve phenomenal R_{out} values, at the expense of a much reduced swing


CS and Cascode Size vs. Swing Comparison

 

(a)

 


(b)

 

(c)

- What happens to a CS amplifier if we quadruple L without changing W and I_D ?
- The “overdrive” $V_{GS} - V_{TH}$ doubles, and as a result, swing will be similar to that of Cascode (c).

 CS and Cascode Size vs. Output Resistance Comparison




Recall that λ is proportional to $1/L$. Quadrupling of L only doubles the value of $g_m r_o$.

Output resistance of (b) is four times bigger than that of (a).



Output resistance of (c) is approximately $(g_m r_o)^2$, much bigger than (b).

CS and Cascode Noise Comparison

 


g_m in (b) is half of that of (c). As a result the CS amplifier with quadrupled L is noisier than the Cascode amplifier (We'll learn about device noise later on).

  PMOS Cascode as Current Source Load for an NMOS Cascode amplifier




$$R_{out, current_source} = [1 + (g_{m3} + g_{mb3})r_{o3}]r_{o4} + r_{o3}$$

 PMOS Cascode as Current Source Load for an NMOS Cascode amplifier - Swing



If all gates' DC voltages are properly chosen, the maximum output swing equals $V_{DD} - (V_{GS1} - V_{TH1}) - (V_{GS2} - V_{TH2}) - |V_{GS3} - V_{TH3}| - |V_{GS4} - V_{TH4}|$

 PMOS Cascode as Current Source Load for an NMOS Cascode amplifier – Gain



$$A_V \approx g_{m1} [(r_{o1} r_{o2} g_{m2}) \parallel (r_{o3} r_{o4} g_{m3})]$$


Explanation:

$$A_V = G_m R_{out}$$

$$G_m \approx g_{m1}$$


$$R_{out} = \{ [1 + (g_{m2} + g_{mb2})r_{o2}]r_{o1} + r_{o1} \} \parallel \{ [1 + (g_{m3} + g_{mb3})r_{o3}]r_{o4} + r_{o3} \}$$

Current Mirror Current Sources

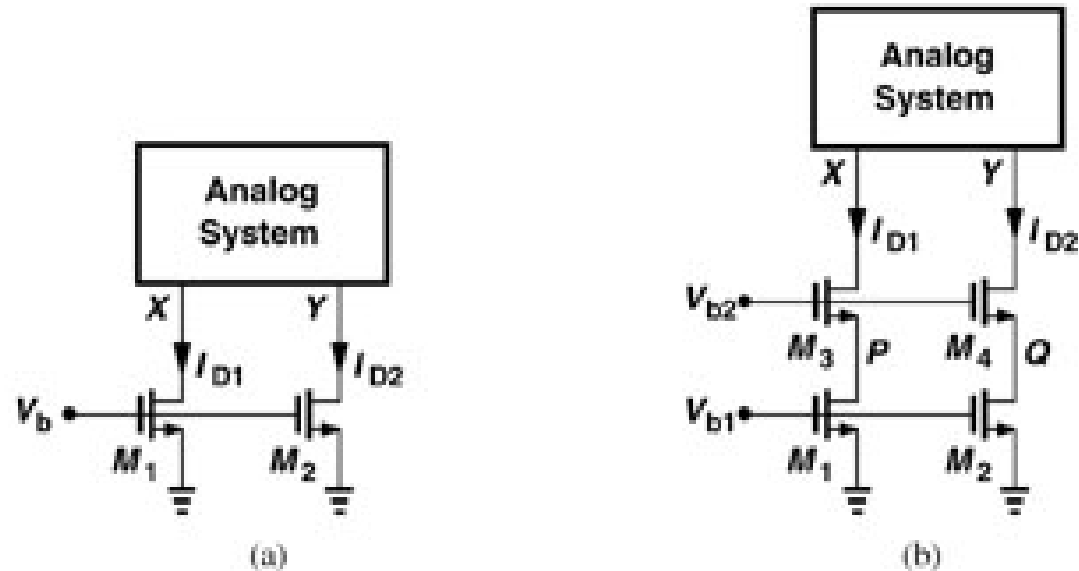


- Assume that I_{D1} is the reference current, and I_{D2} is the desired current source.
- If $\lambda \neq 0$ and if $V_X \neq V_Y$ then there may be a significant error between the two currents.

Current Mirror Current Sources

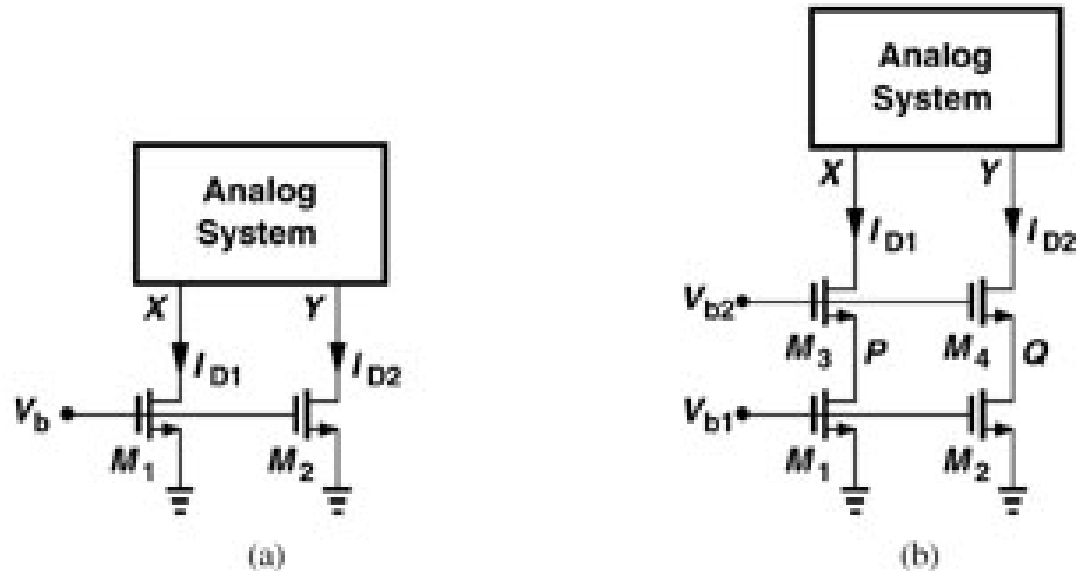


- Error in (a): (assuming that both transistors have the same W/L ratio)
- $I_{D1} - I_{D2} = 0.5k_n'(W/L)(V_b - V_{TH})^2\lambda(V_X - V_Y)$

Current Mirror Current Sources

 

- In (b) it can be shown that $I_{D1} - I_{D2} \approx 0.5k_n'(W/L)(V_b - V_{TH})^2\lambda(V_X - V_Y)/[(g_{m3} + g_{mb3})r_{o3}]$
- Cascoding significantly reduces the mismatch between the two mirrored currents

Folded Cascode

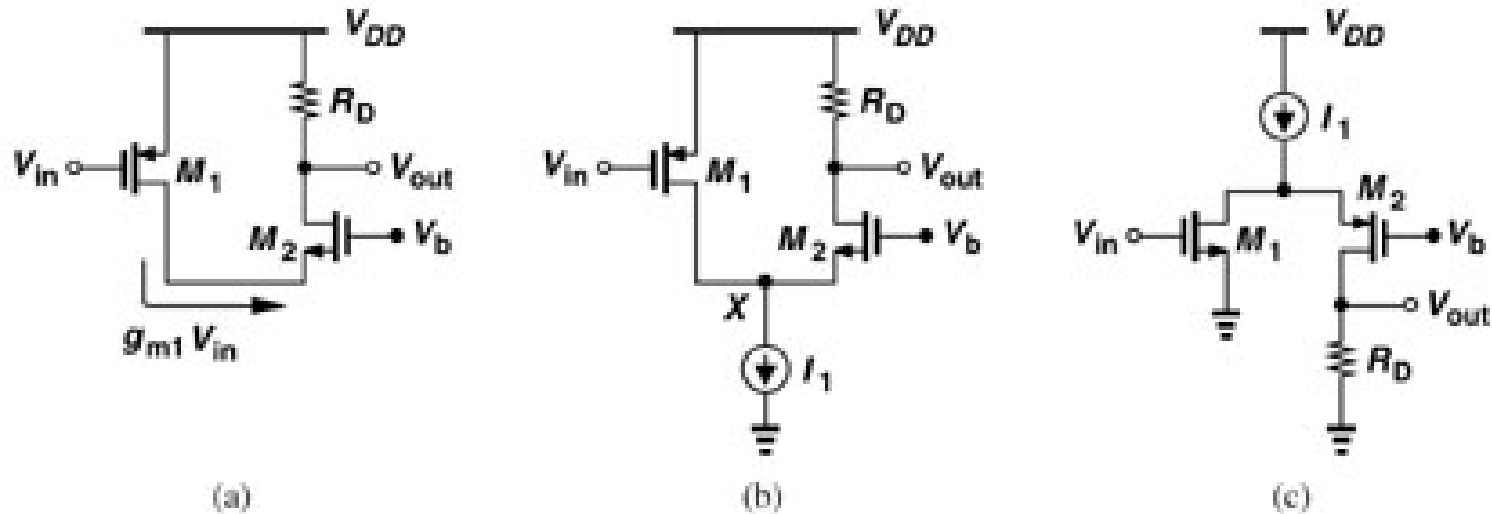

- Folded Cascode: NMOS CS feeding into PMOS CG, or vice versa.
- Biasing by a DC current source is necessary.