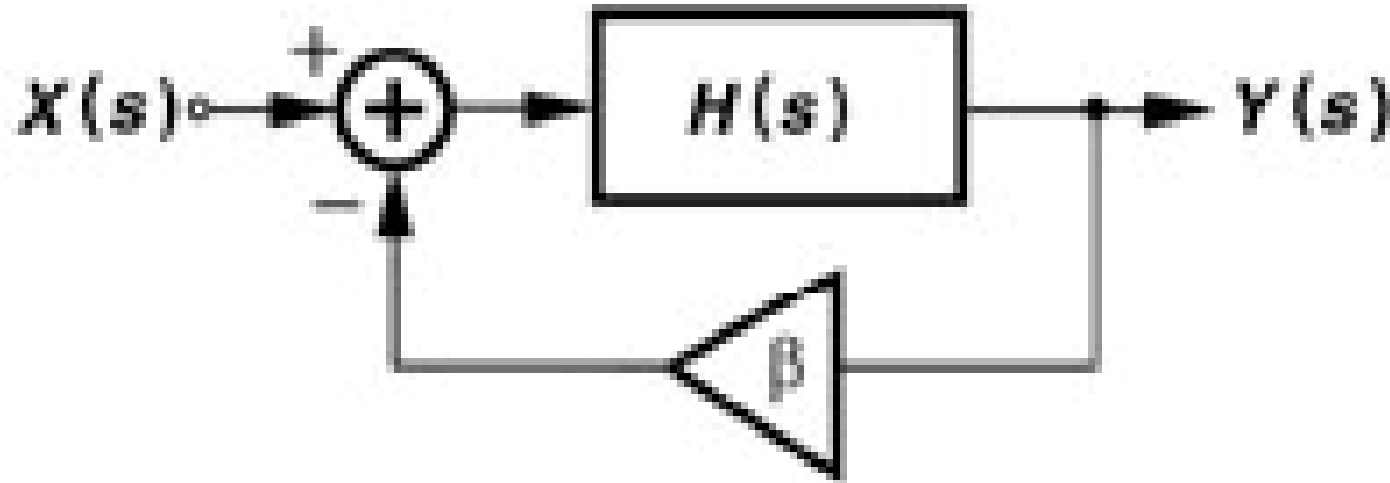


# Chapter 10

## Stability and Frequency Compensation


# Basic Stability




$$\frac{Y}{X}(s) = \frac{H(s)}{1 + \beta H(s)}$$

*May oscillate at  $\omega$  if  $|\beta H(j\omega)| = 1$  and  $\angle \beta H(j\omega) = -180$  (Barkhausen criteria)*




# Stable and Unstable Systems

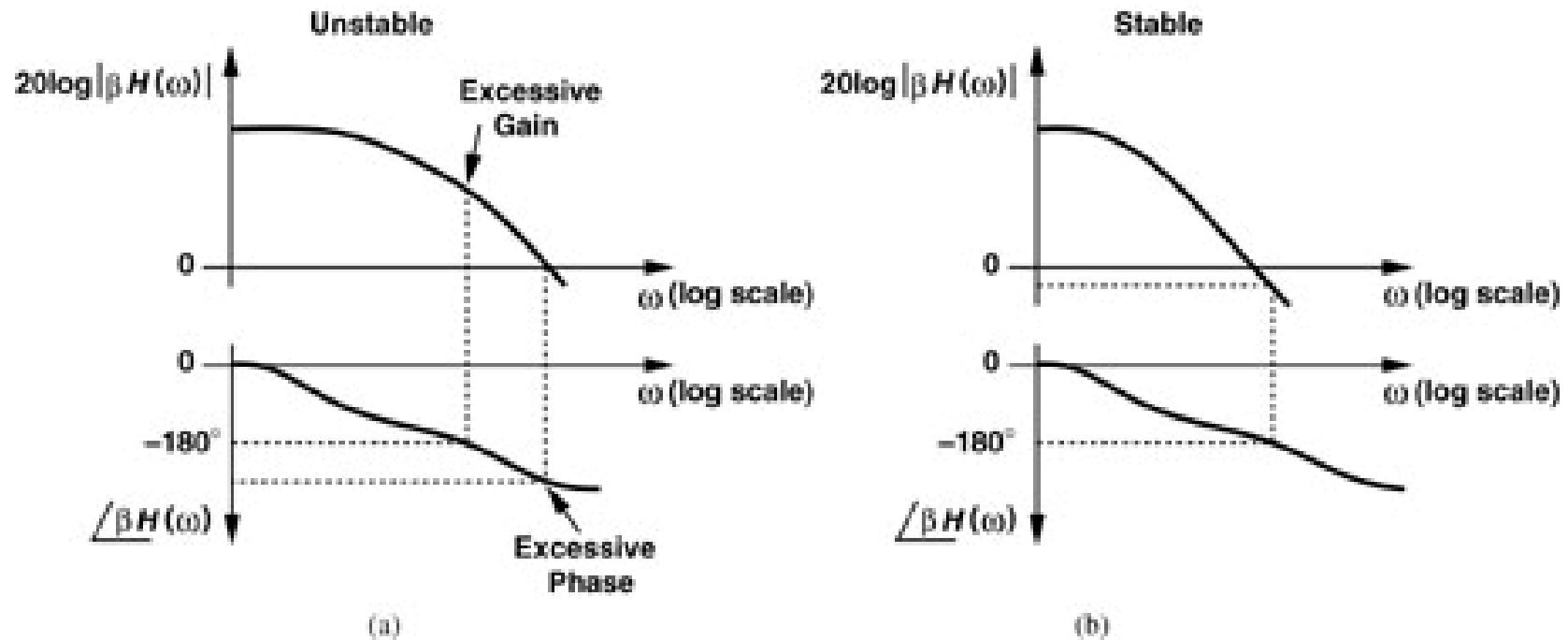


# Stability and Complex Poles

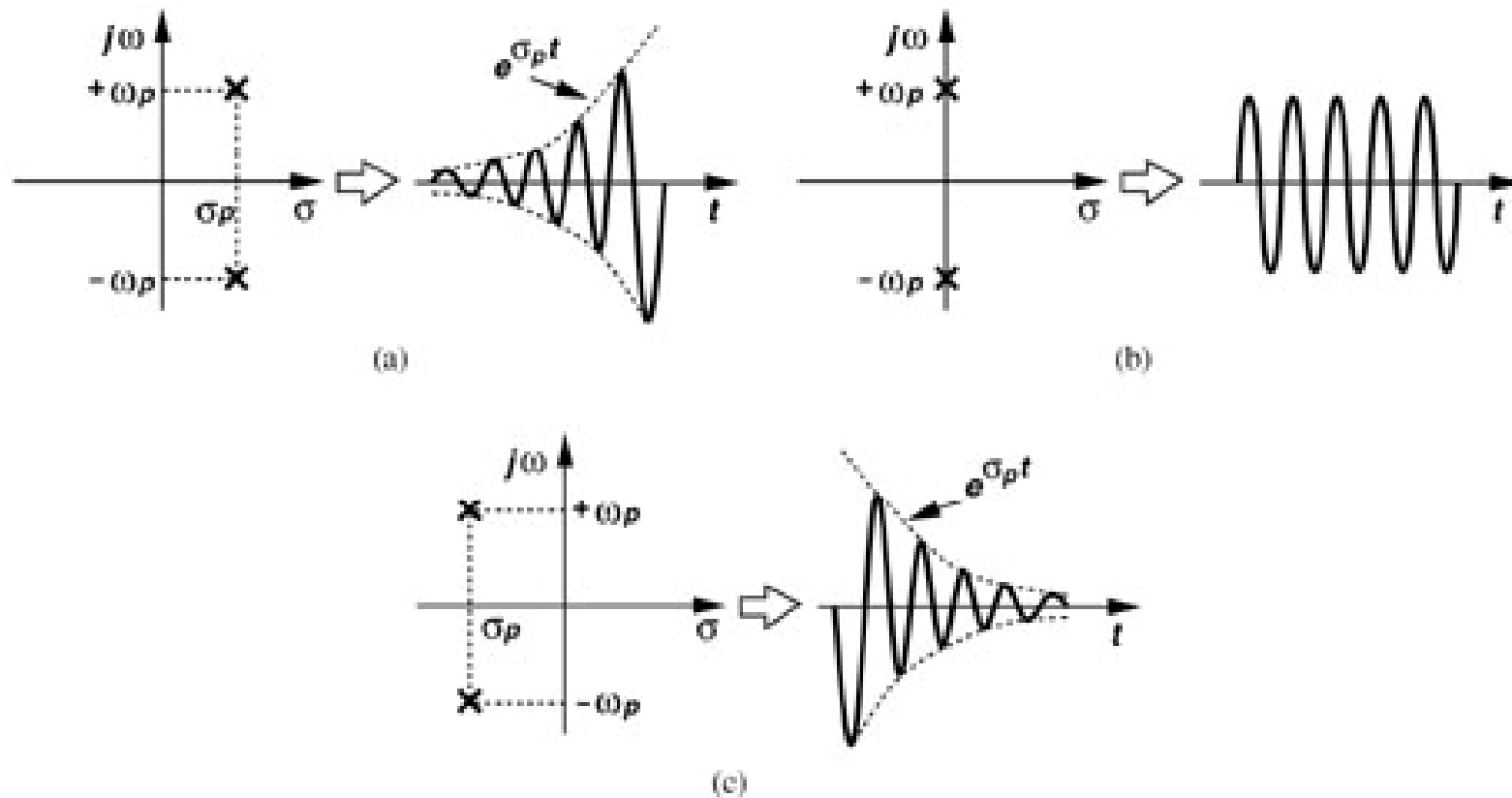


# Basic One Pole Bode Plot

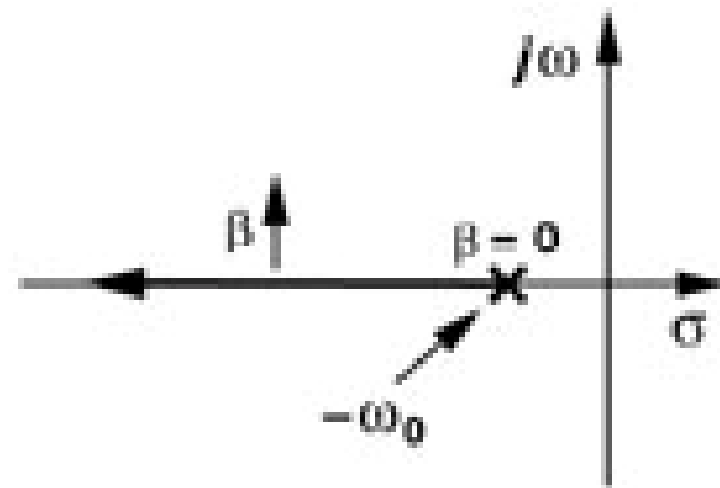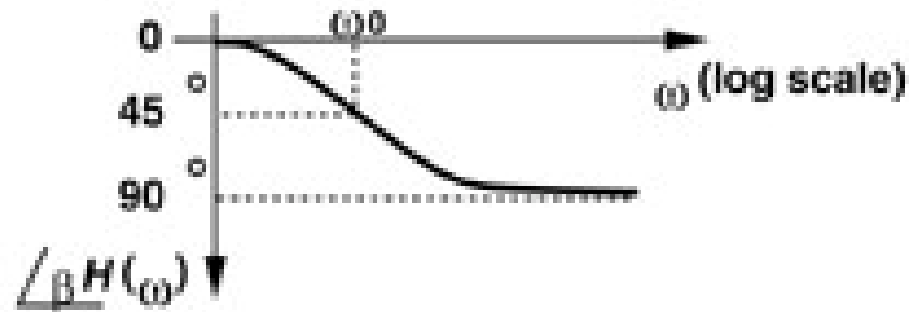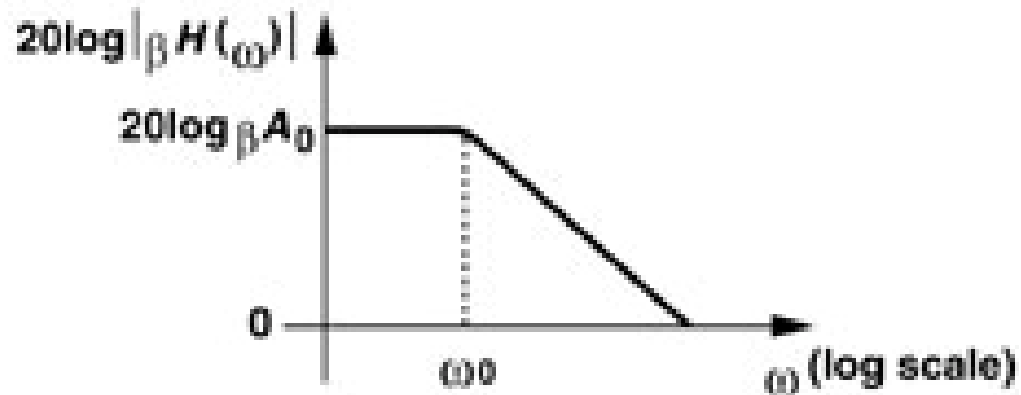

# Multipole Systems

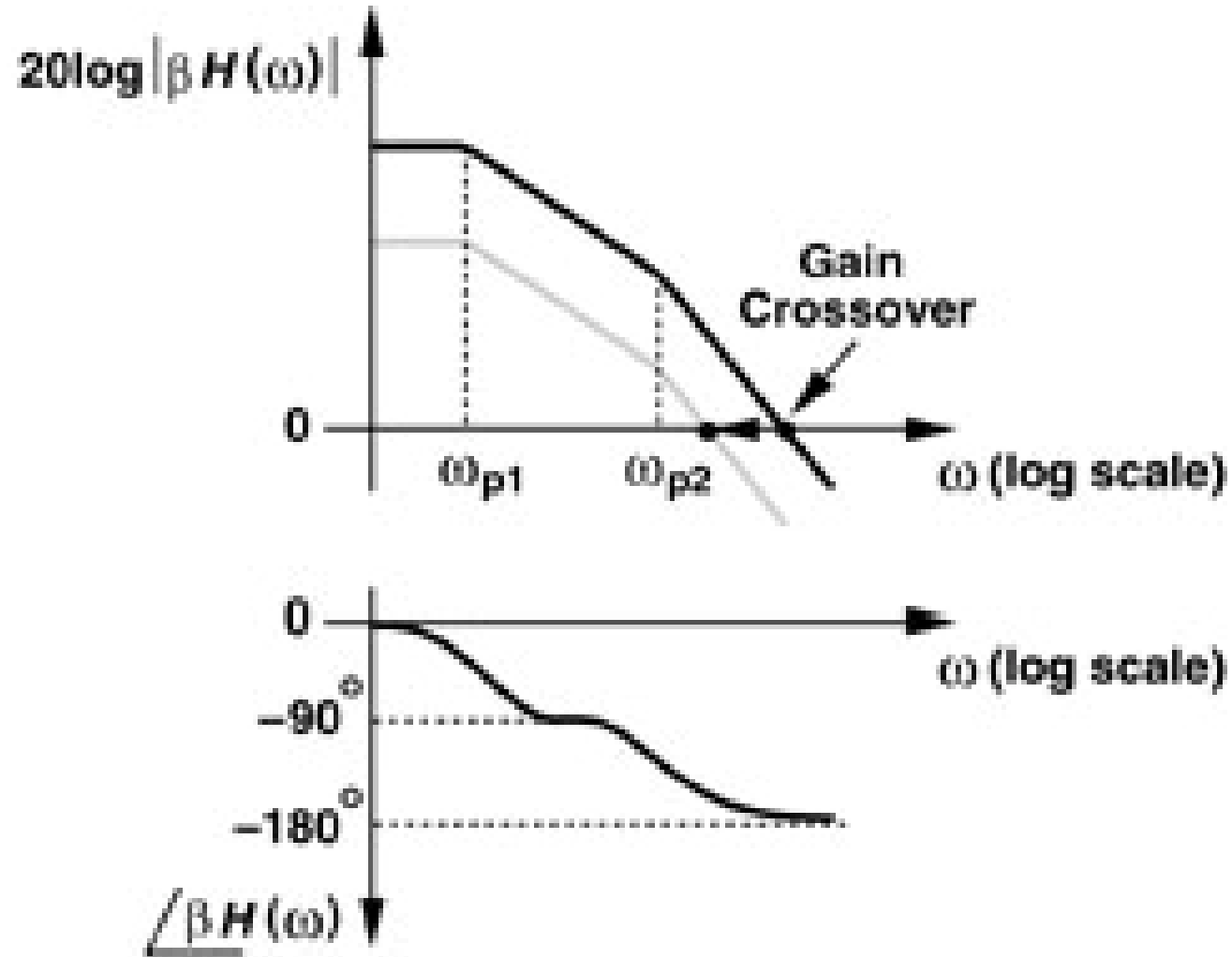

# Root Locus for a 2-Pole System

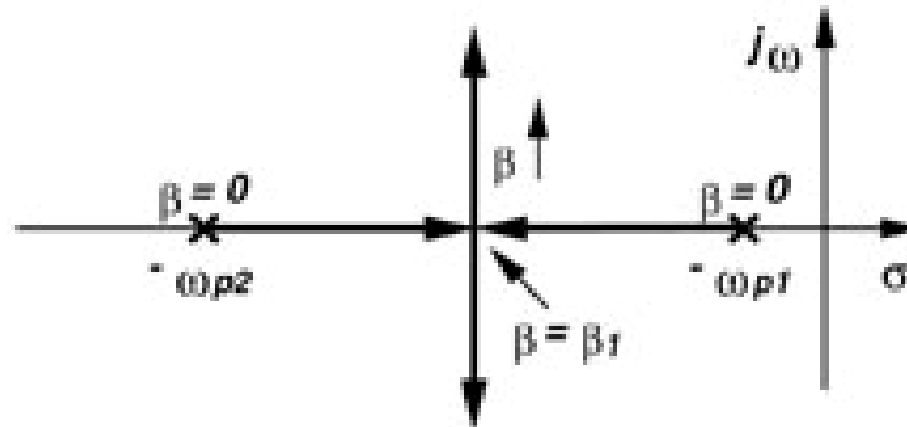

$$H_{open}(s) = \frac{A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

$$H_{closed}(s) = \frac{H_{open}(s)}{1 + \beta H_{open}(s)} = \frac{A_0 \omega_{p1} \omega_{p2}}{s^2 + (\omega_{p1} + \omega_{p2})s + (1 + \beta A_0) \omega_{p1} \omega_{p2}}$$



$$s_{1,2} = -\frac{1}{2}(\omega_{p1} + \omega_{p2}) \pm \frac{1}{2}\sqrt{(\omega_{p1} + \omega_{p2})^2 - 4(1 + \beta A_0) \omega_{p1} \omega_{p2}}$$

$$s_{1,2}|_{\beta=0} = -\omega_{p1}, -\omega_{p2}$$

$$s_{1,2}|_{\beta=\beta_1} = \frac{(\omega_{p1} - \omega_{p2})^2}{4A_0\omega_{p1}\omega_{p2}} = -\frac{1}{2}(\omega_{p1} + \omega_{p2})$$

$$s_{1,2}|_{\beta > \beta_1} = \text{Complex Values}$$

# Phase Margin

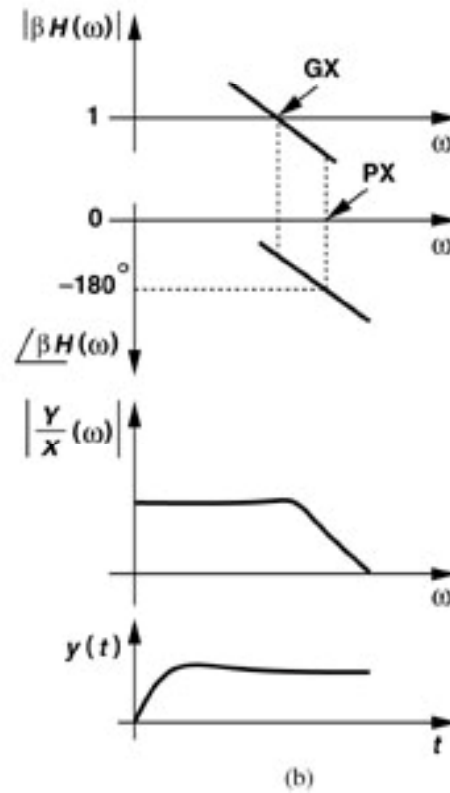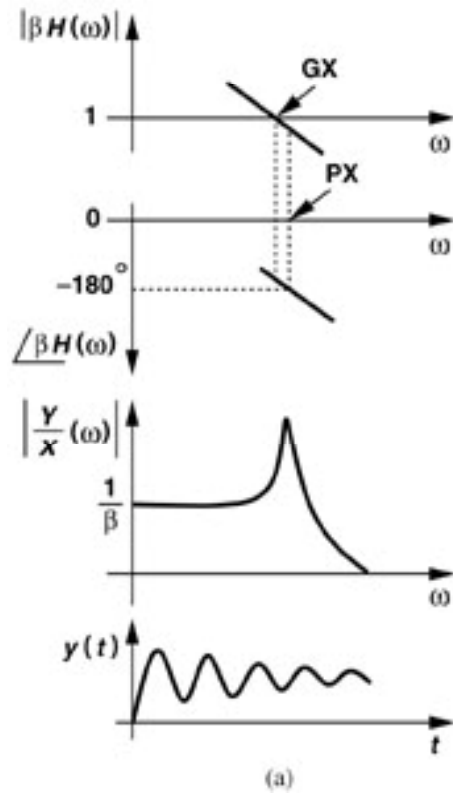


$$\frac{Y}{X} = \frac{H(j\omega)}{1 + \beta H(j\omega)}$$




$$\begin{aligned} \left| \frac{Y}{X} \right| &= \left| \frac{H(j\omega_{GX})}{1 + \beta H(j\omega_{GX})} \right| \\ &= \left| \frac{1/\beta}{1 + \exp[j(-180^\circ + PM)]} \right| \\ &= \frac{1}{\beta |1 + \cos(180^\circ - PM) - j \sin(180^\circ - PM)|} \end{aligned}$$




# Phase Margin (cont.)

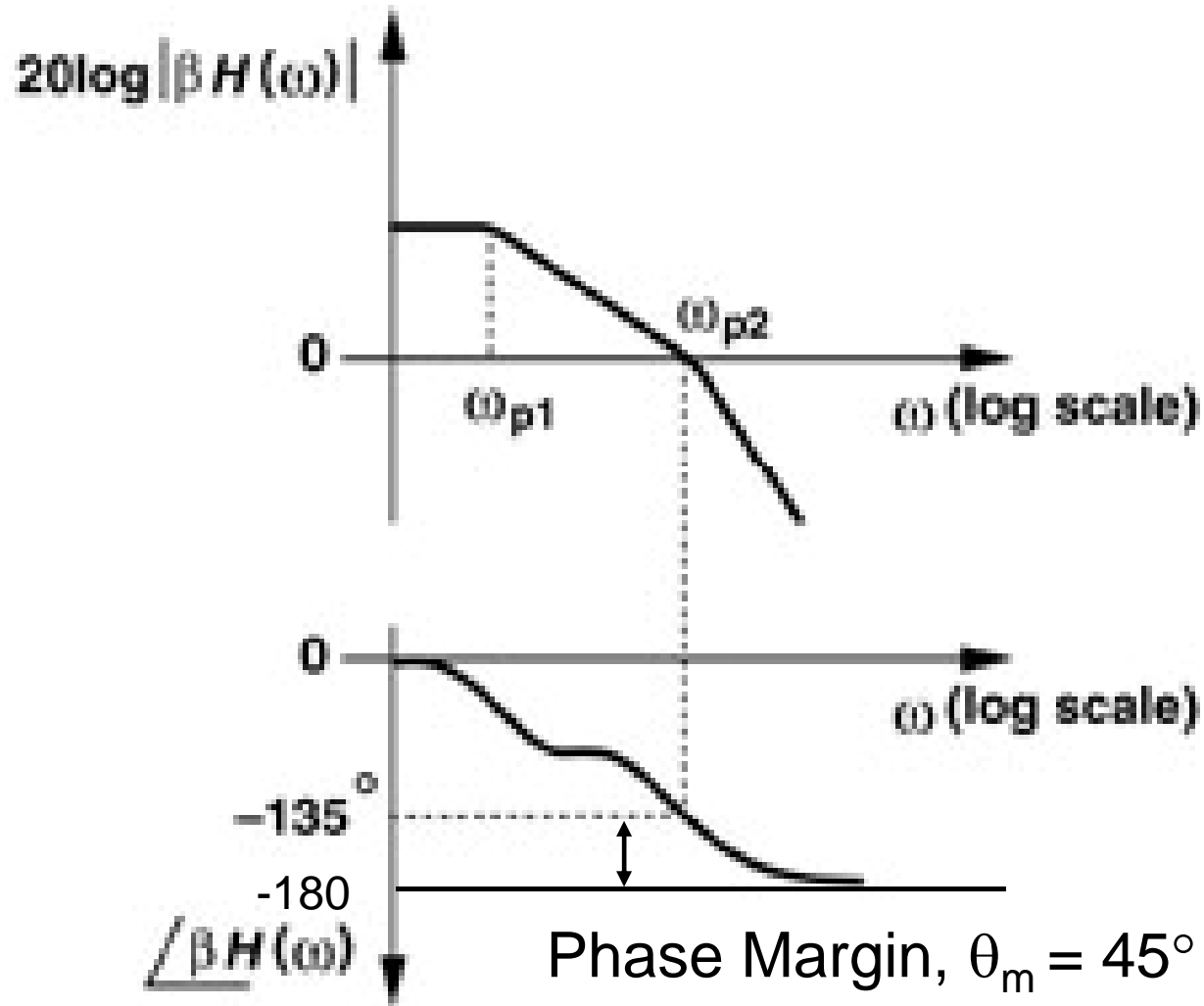

# Phase Margin (cont.)

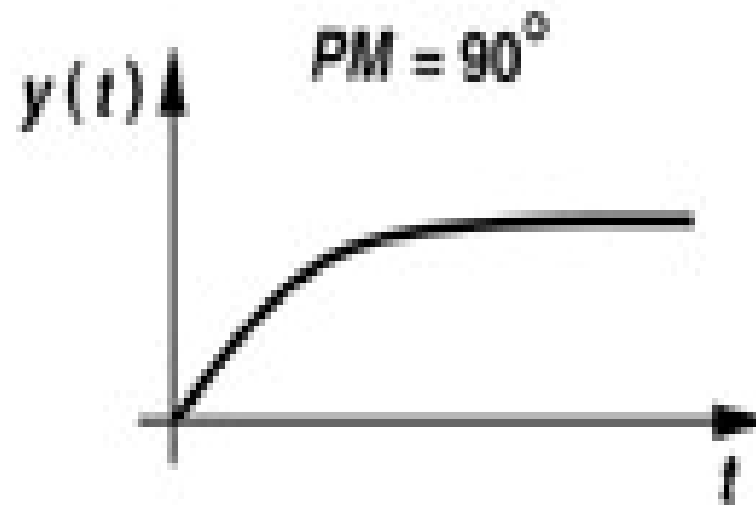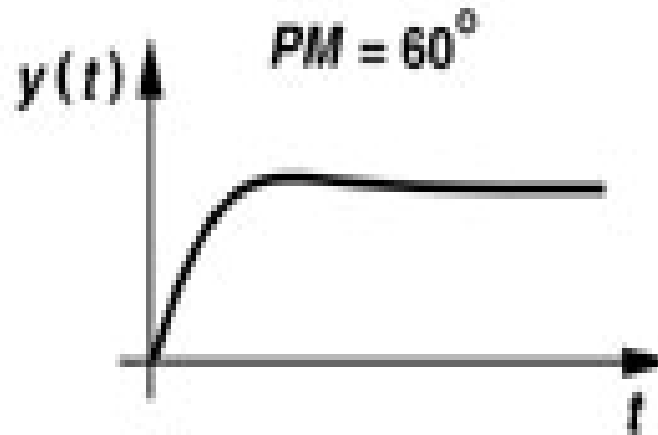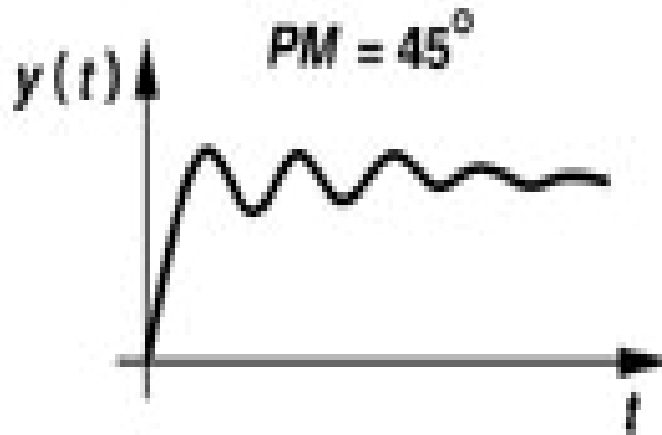


# Small Signal Analysis Limitations

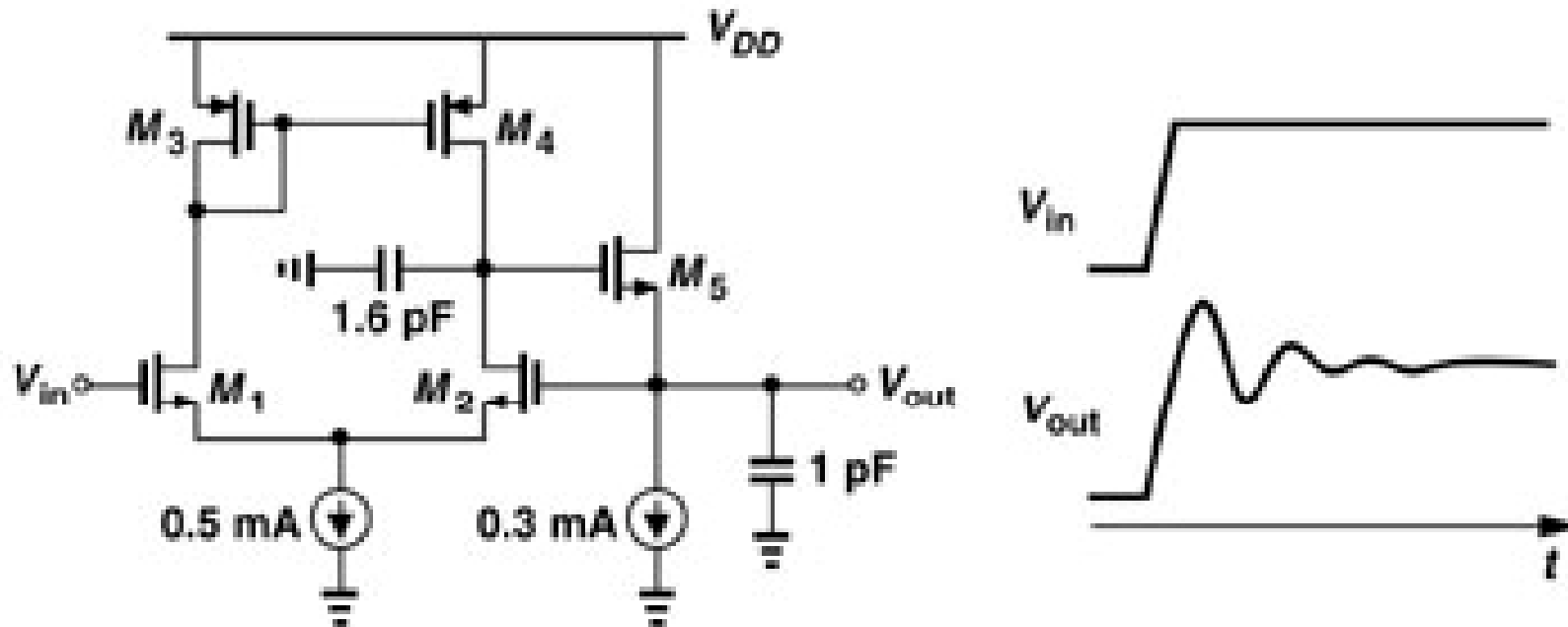


Small signal analysis yields  $65^\circ$  of  $\theta_m$ , but large signal transient response is different. Large signal simulation includes effects not seen in small signal analysis.

# Frequency Compensation

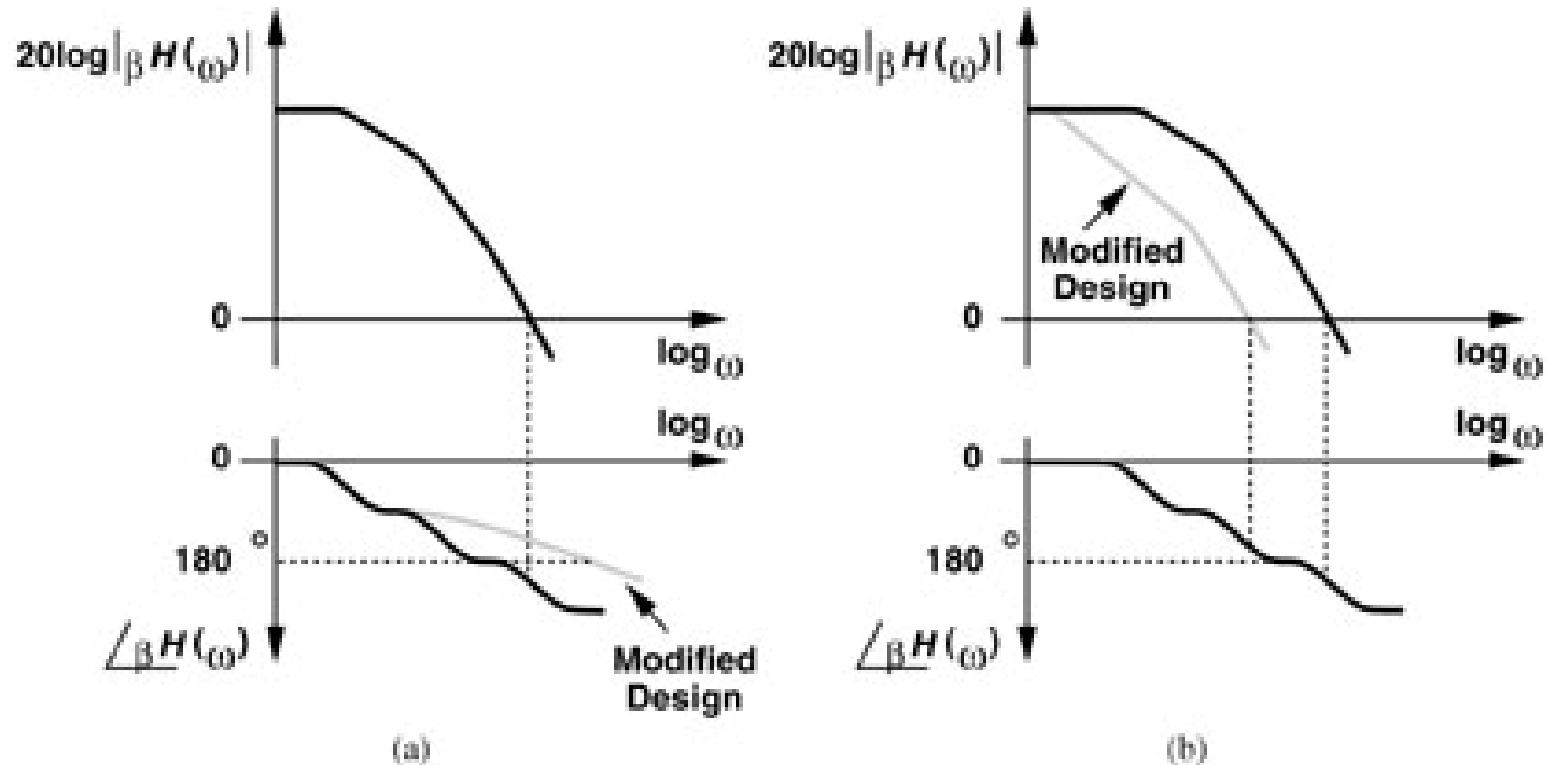


Compensation is the manipulation of gain and/or pole positions to improve phase margin.


# Compensation (cont.)

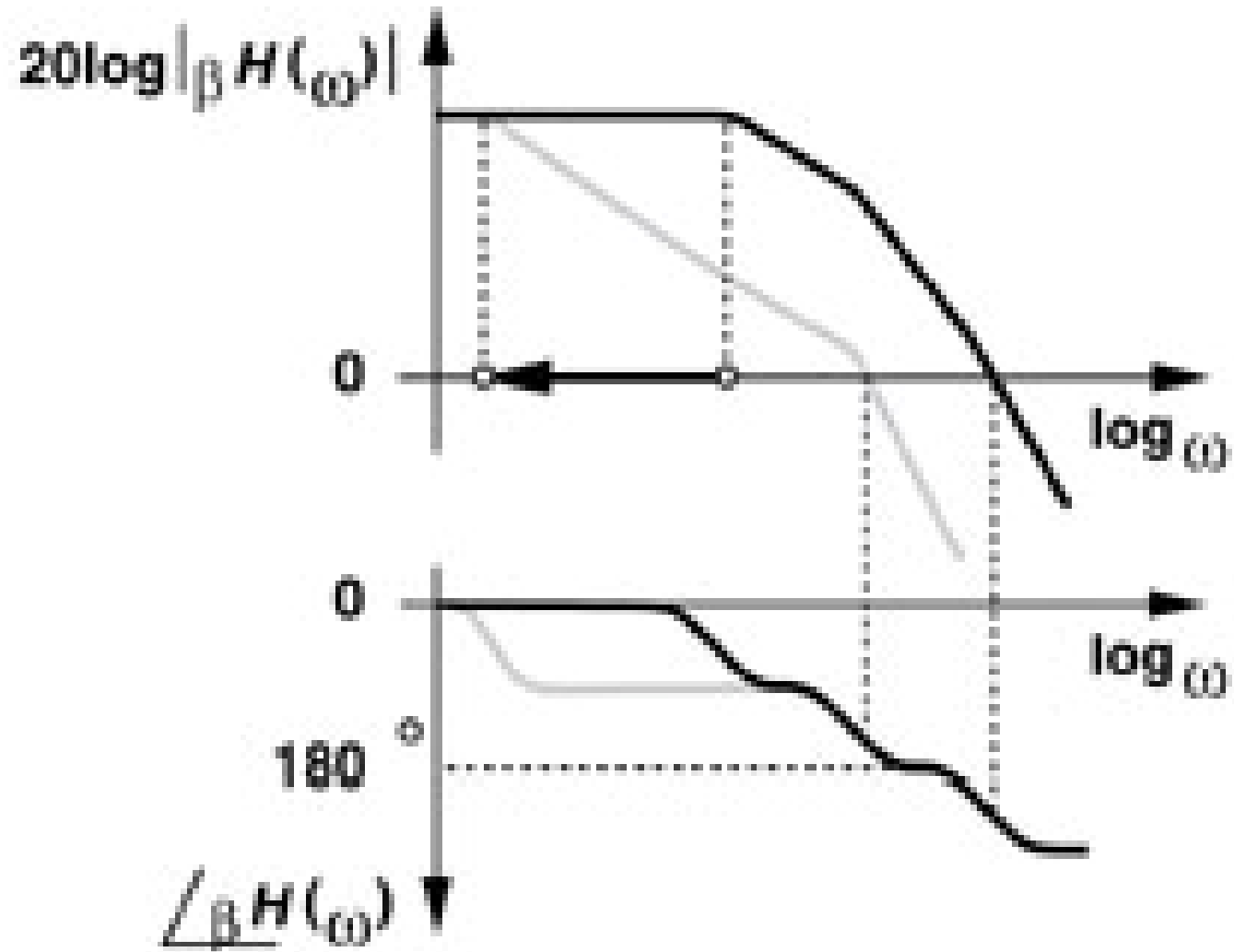



# Single Ended Single Stage Amp

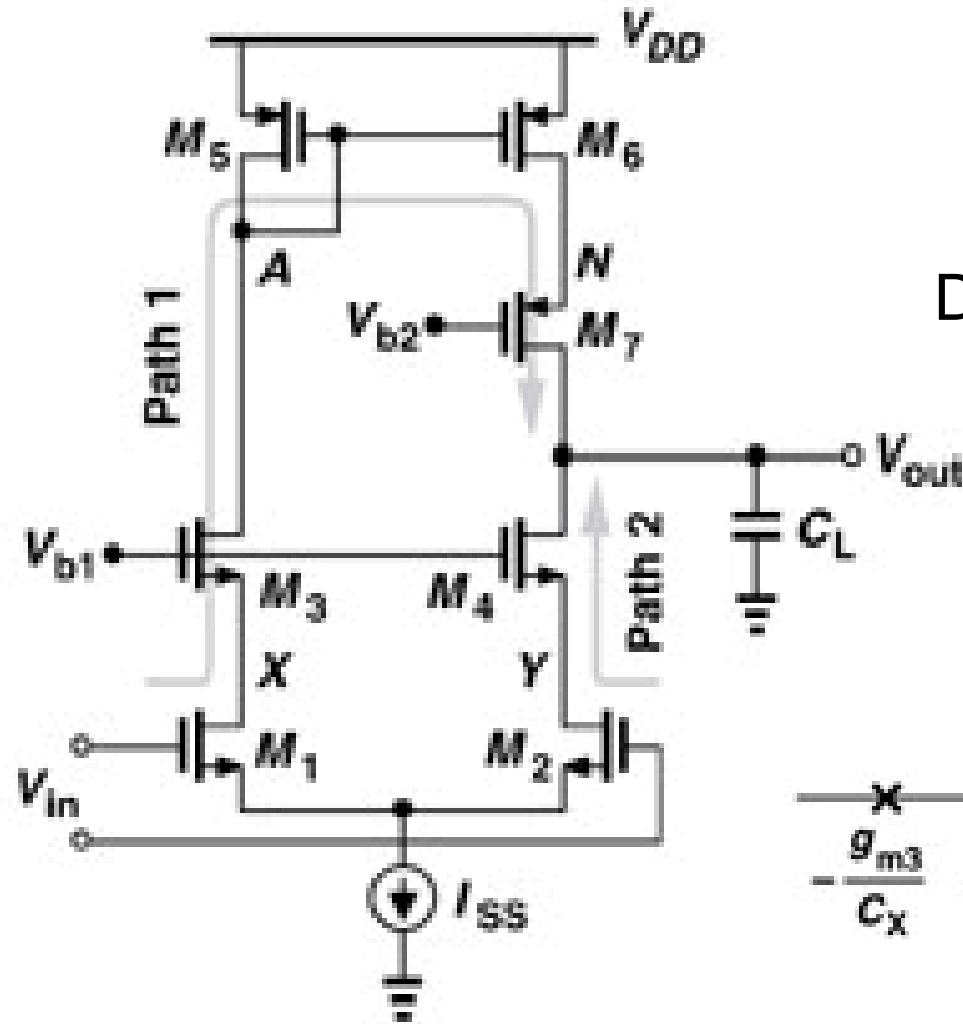



Dominant Pole at Output

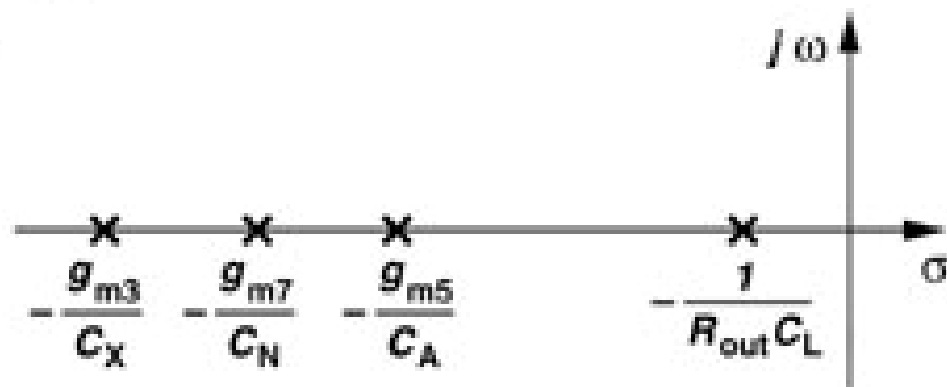

# Pre- and Post-Compensation

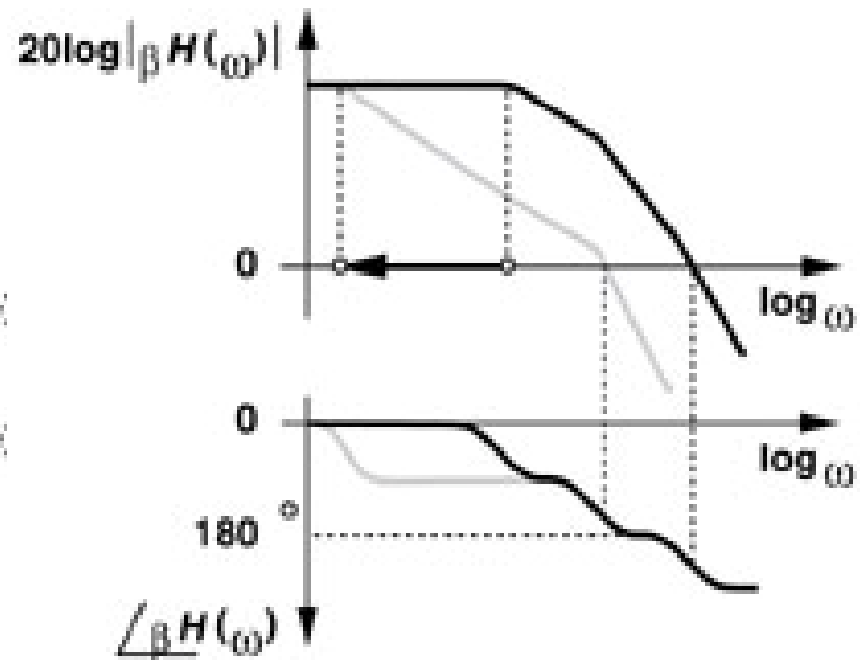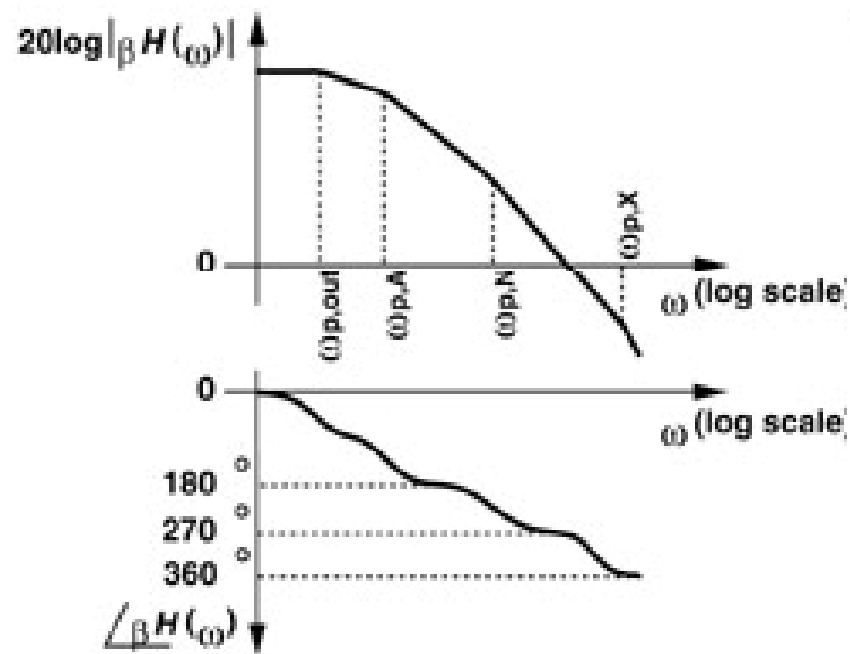

# Compensation (cont.)

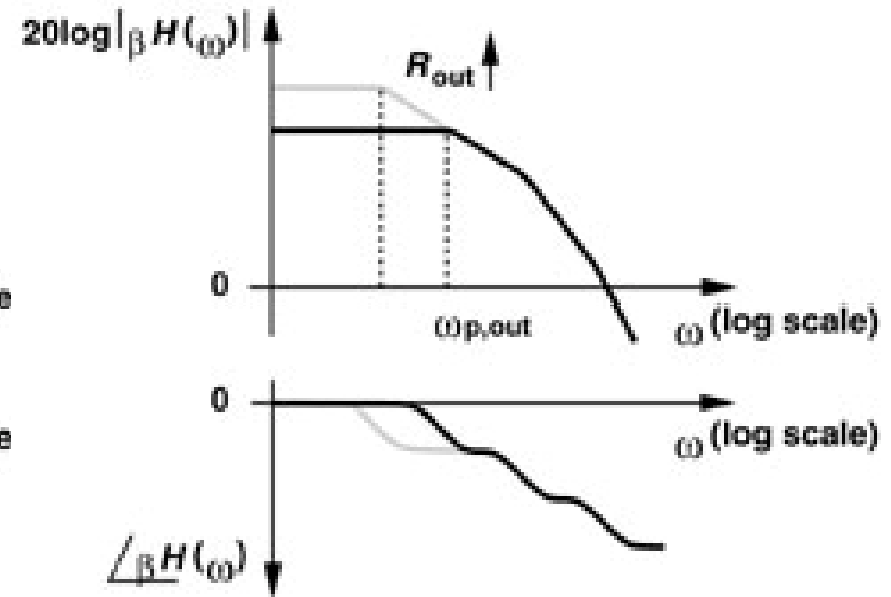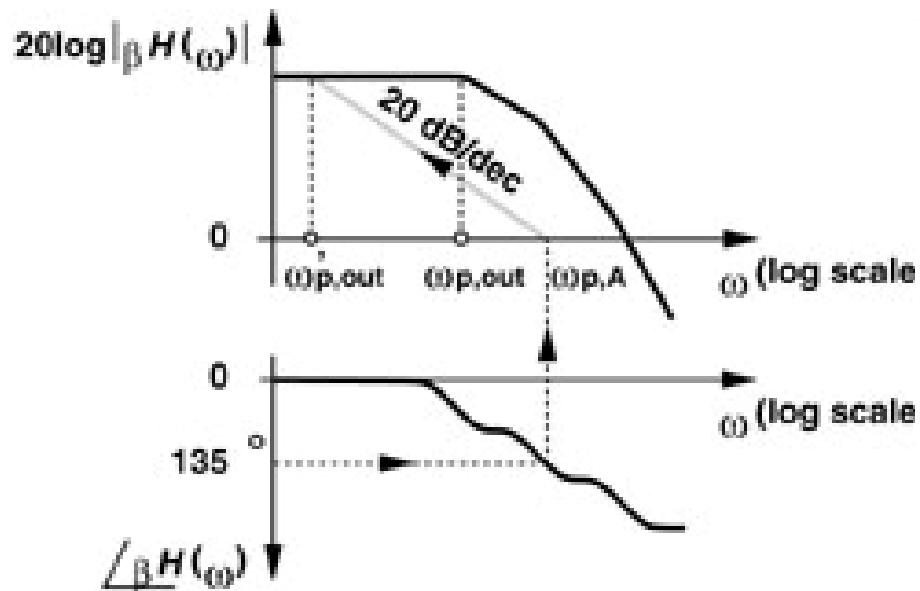



# Compensation Example

Given  $T_0 = 5000V/V$ ,  $f_{p1} = 2MHz$ ,  $f_{p2} = 25MHz$ ,  $f_{p3} = 50MHz$

Desire  $\phi_m = 70^\circ$ , find  $f_{0db}$  and new  $f_{p1} \therefore$


$$70^\circ = 180^\circ - \tan^{-1}\left(\frac{f_{0db}}{f_{p1}}\right) - \tan^{-1}\left(\frac{f_{0db}}{f_{p2}}\right) - \tan^{-1}\left(\frac{f_{0db}}{f_{p2}}\right)$$

$$70^\circ = 90 - \tan^{-1}\left(\frac{f_{0db}}{f_{p2}}\right) - \tan^{-1}\left(\frac{f_{0db}}{f_{p2}}\right), \text{ assume } 90^\circ \text{ from } f_{p1}$$


$$f_{0db} \approx 6MHz$$

$$f_{0db} = T_0 f_{p1} \rightarrow f_{p1} = f_{0db} / T_0 = 1.2KHz$$


# Fully Differential Telescopic Op-Amp

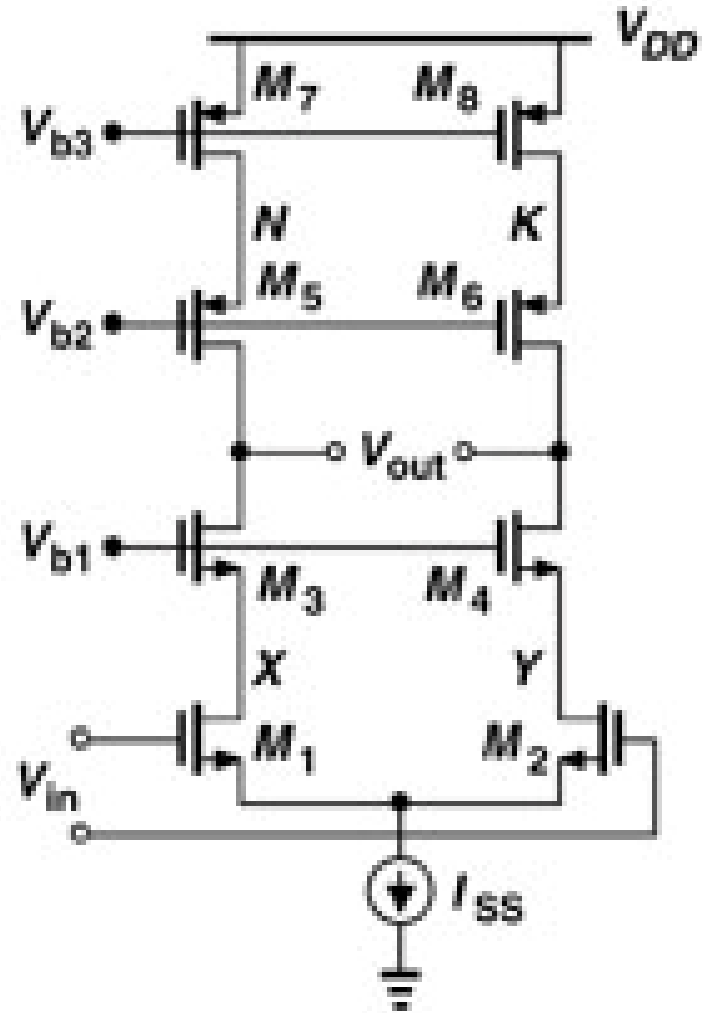

# Cascode Current Source Impedance


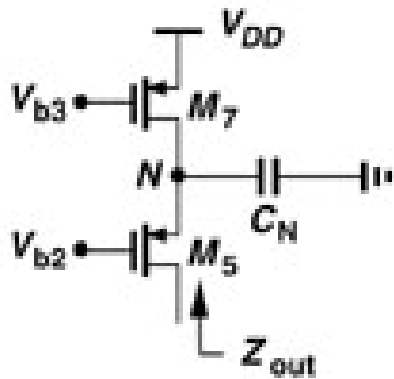


(a)

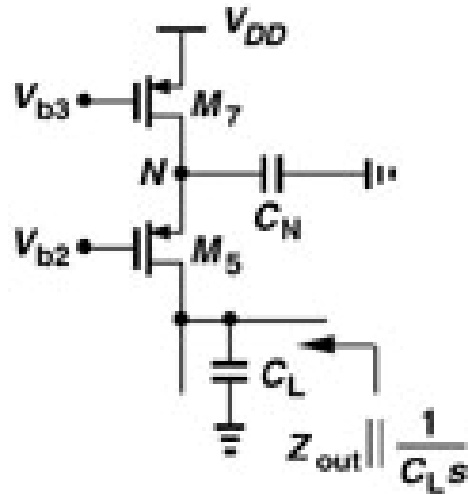


$$\begin{aligned}
 Z_{out} \parallel \frac{1}{sC_L} &= \frac{(1 + g_{m5}r_{o5}) \frac{r_{o7}}{1 + sr_{o7}C_N} \frac{1}{sC_L}}{(1 + g_{m5}r_{o5}) \frac{r_{o7}}{1 + sr_{o7}C_N} + \frac{1}{sC_L}} \\
 &= \frac{(1 + g_{m5}r_{o5})r_{o7}}{1 + s[(1 + g_{m5}r_{o5})r_{o7}C_L + r_{o7}C_N]}
 \end{aligned}$$

# Compensation of Two-Stage Op Amps

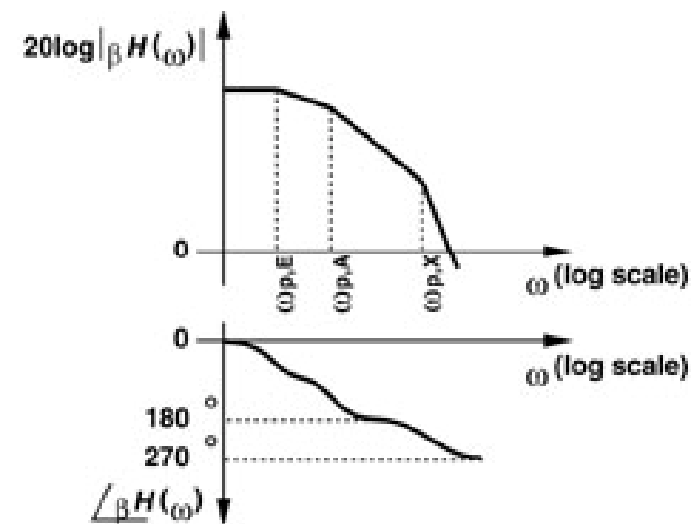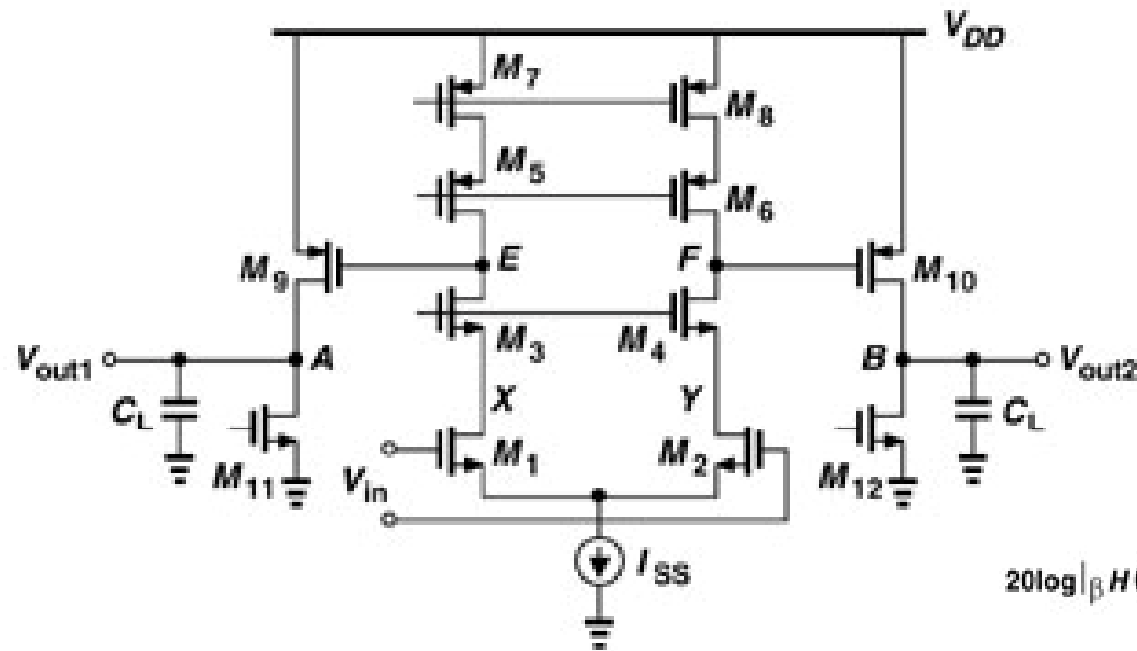

# Compensation (cont.)

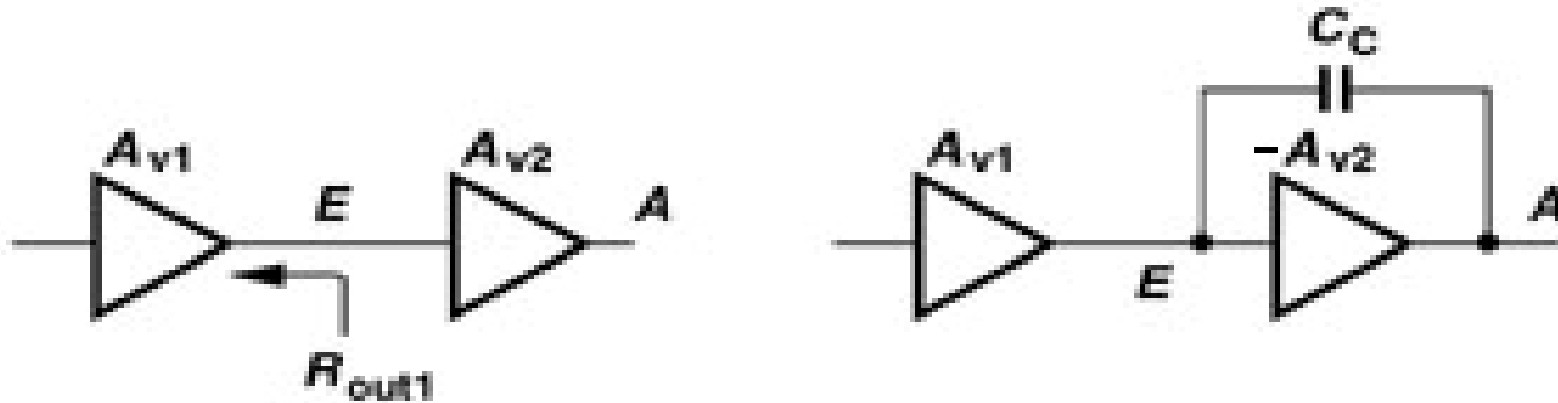


*Miller Effect*      $C_{eq} = C_E + (1 + A_{v2})C_C$

$$f_{pE} = \frac{1}{2\pi R_{out} [C_E + (1 + A_{v2})C_C]}$$

Pro: Need a smaller capacitor

Con: Exact effect of bridging capacitor involve a zero. If open-loop gain is high, zero may prevent -20db/dec curve from going all the way to 0db

# Compensation (cont.)

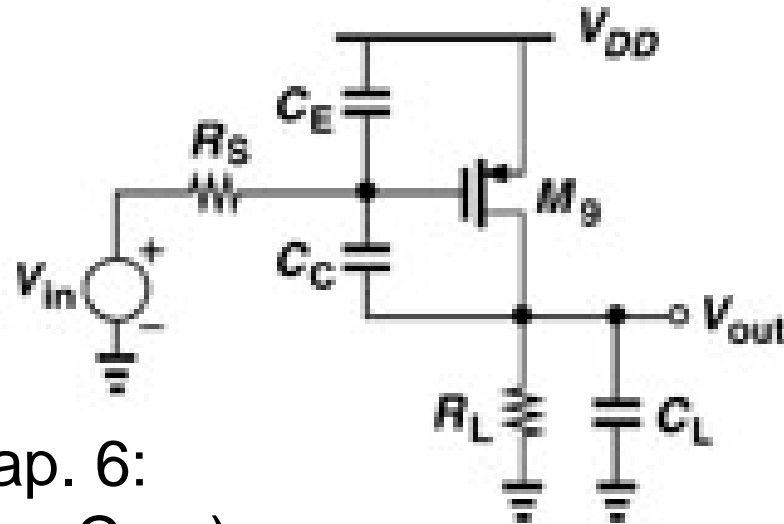

Recall, from Chap. 6:  
(assume  $C_C$  includes  $C_{GD9}$ )

$$f_{p,in} = \frac{1}{2\pi(R_S [C_E + (1 + g_m R_L)C_C] + R_L (C_C + C_L))}$$

$$f_{p,in} \approx \frac{1}{2\pi R_S [C_E + (1 + g_m R_L)C_C]}$$


# Compensation (cont.)

$$f_{p,out} = \frac{R_S(1 + g_{m9}R_L)C_C + R_S C_E + R_L(C_C + C_L)}{2\pi R_S R_L (C_E C_C + C_E C_L + C_C C_L)}$$

$$f_{p,out} \approx \frac{R_S g_{m9} R_L C_C + R_L C_C}{2\pi R_S R_L (C_E C_C + C_C C_L)} = \frac{g_{m9}}{2\pi(C_E + C_L)}$$



# Compensation (cont.)

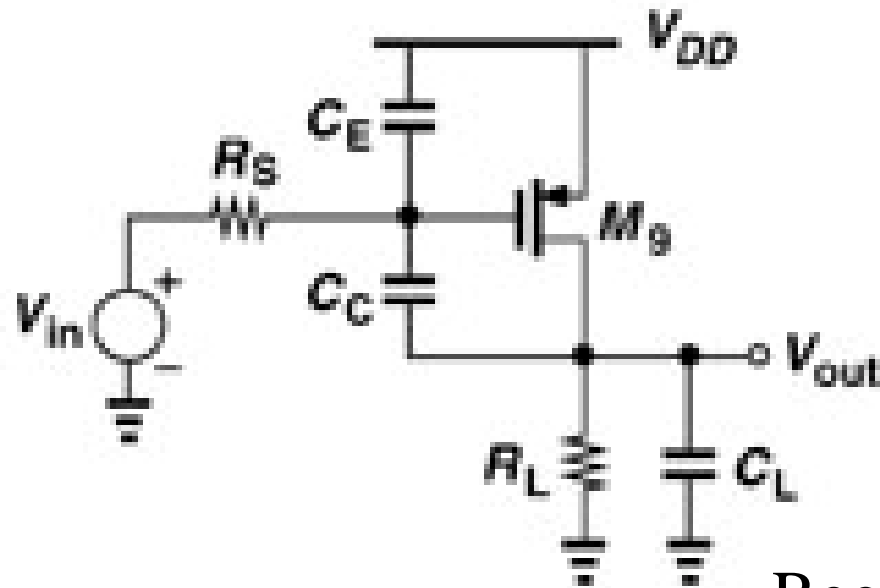


Recall, transfer function includes  
 $(1 - s/\omega_z)$  numerator term and


$$f_z(RHP) = \frac{g_{m9}}{2\pi C_C}$$



# Phase and Magnitude of RHP Zero

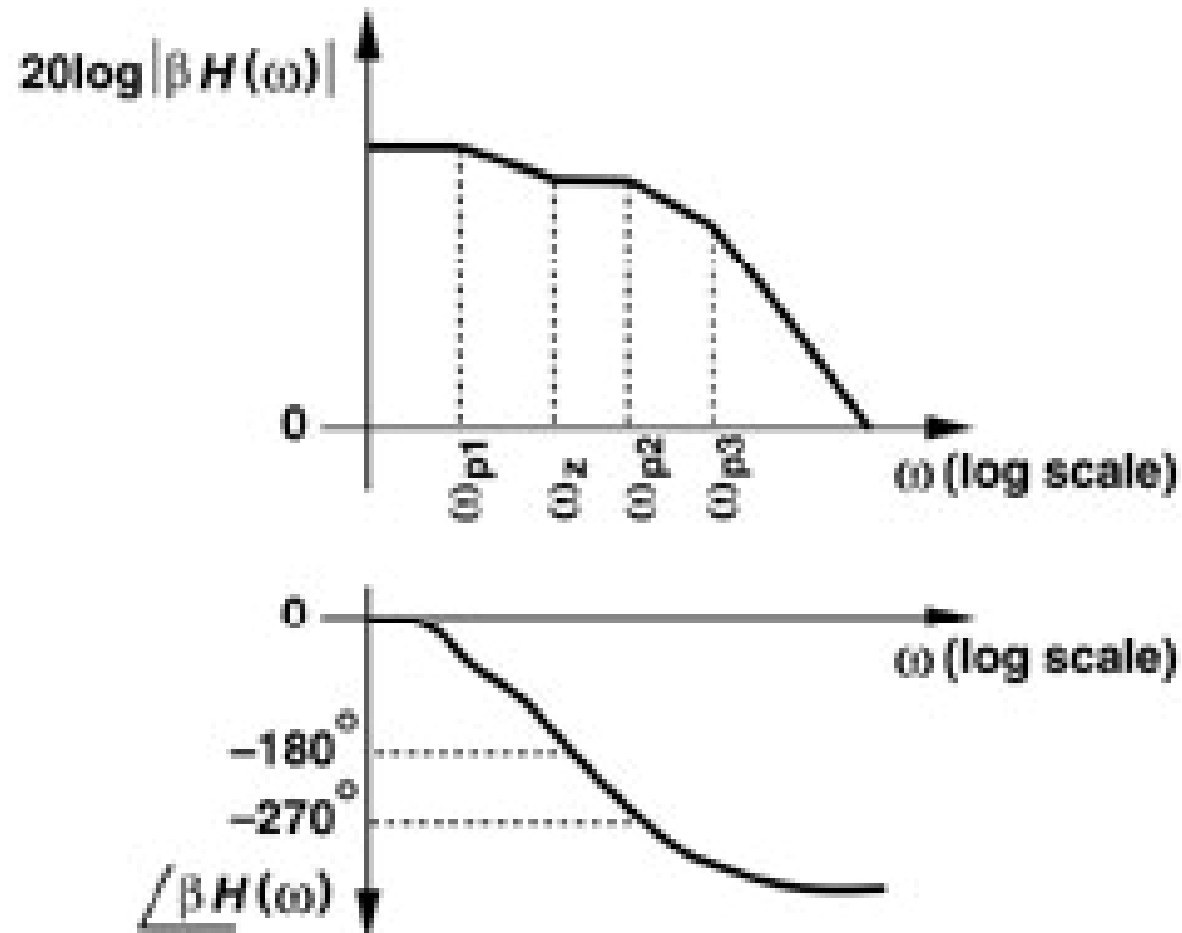

# RHP Zero Removal

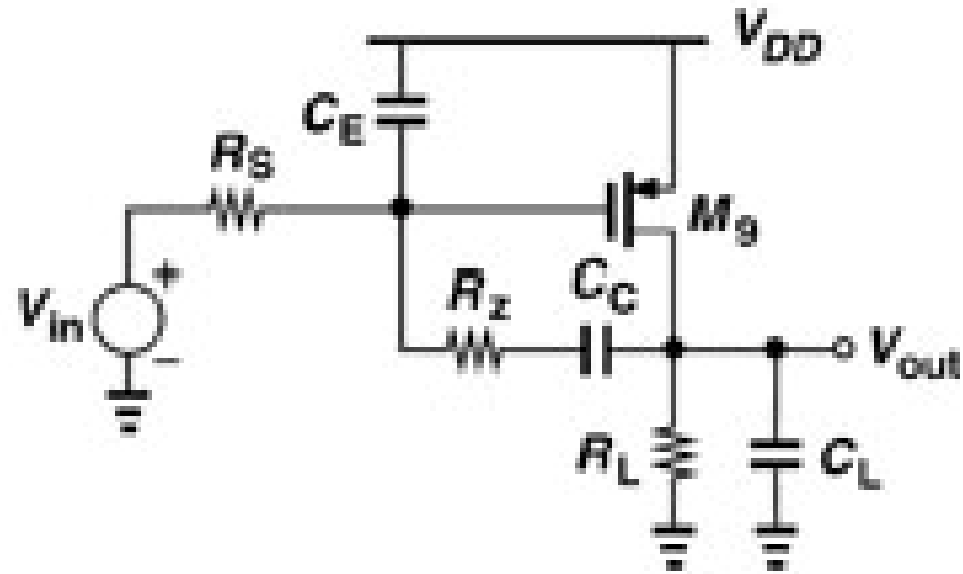

$$f_z = \frac{g_{m9}}{2\pi C_C (1/g_{m9} - R_Z)}$$


# RHP Zero Removal (cont.)

$$f_Z = \frac{1}{2\pi C_C (1/g_{m9} - R_Z)}$$


Could set  $R_Z = 1/g_{m9}$ , or cancel  
other non - dominant pole

$$\frac{1}{C_C (1/g_{m9} - R_Z)} = \frac{-g_{m9}}{C_L + C_E}$$
$$R_Z = \frac{C_L + C_E + C_C}{g_{m9} C_C} \approx \frac{C_L + C_C}{g_{m9} C_C}$$

# Miller Compensation (cont.)

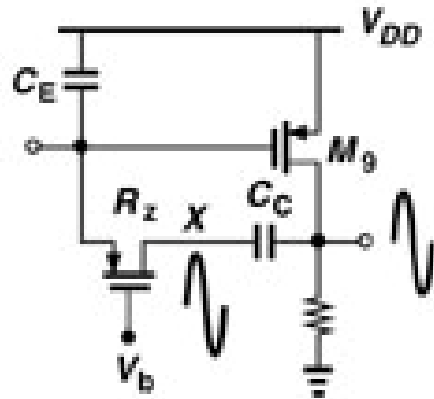

Temp. and Process Tracking

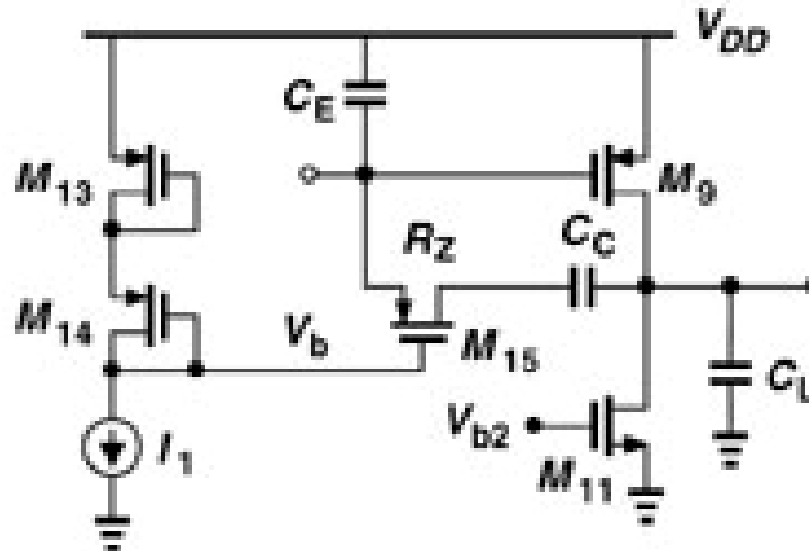


$$R_{\text{out}} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{15} (V_{GS15} - V_{TH15})}$$

$$= \frac{(W/L)_{15}}{g_{m15} (W/L)_{15}} \quad \text{because } g_{m15} = \mu_p C_{ox} \left(\frac{W}{L}\right)_{15} (V_{GS15} - V_{TH15})$$

$$g_{m15}^{-1} \frac{(W/L)_{15}}{(W/L)_{15}} = g_{m15}^{-1} \left(1 + \frac{C_L}{C_E}\right)$$


$$\left(\frac{W}{L}\right)_{15} = \sqrt{(W/L)_{15} (W/L)_9} \cdot \sqrt{\frac{I_{D9}}{I_1}} \cdot \frac{C_E}{C_E + C_L}$$

# Miller Compensation (cont.)

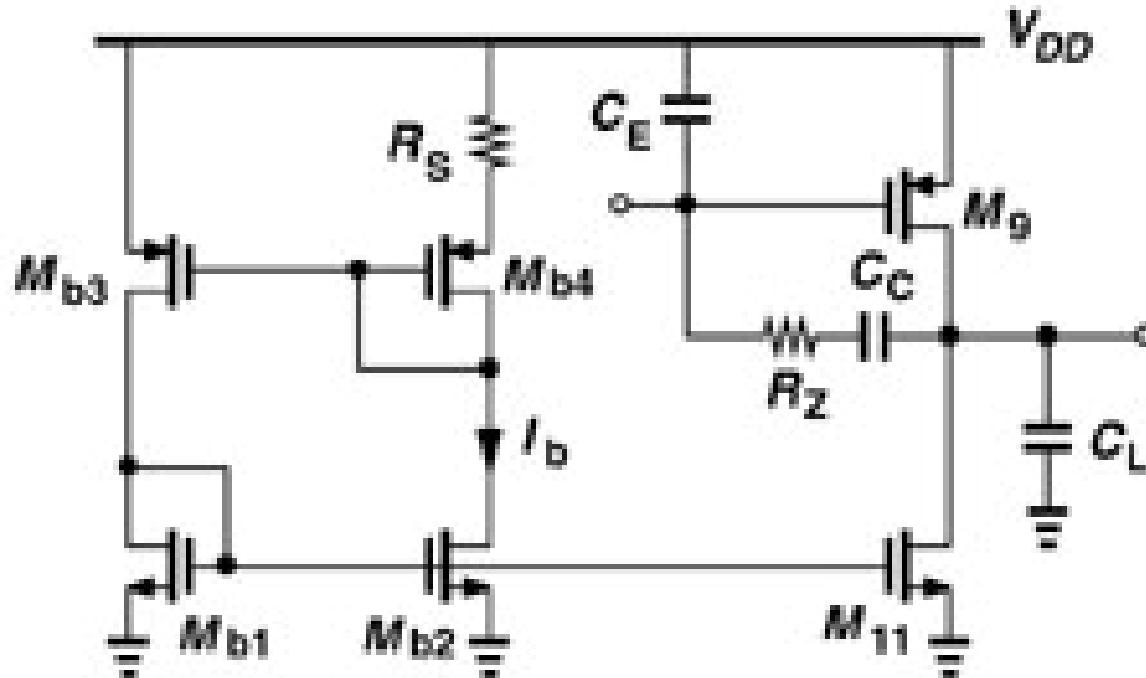




$$g_{m9} \propto \sqrt{I_{D9}} \propto \sqrt{I_{D11}} \propto 1/R_S$$

# Load Capacitance Effects

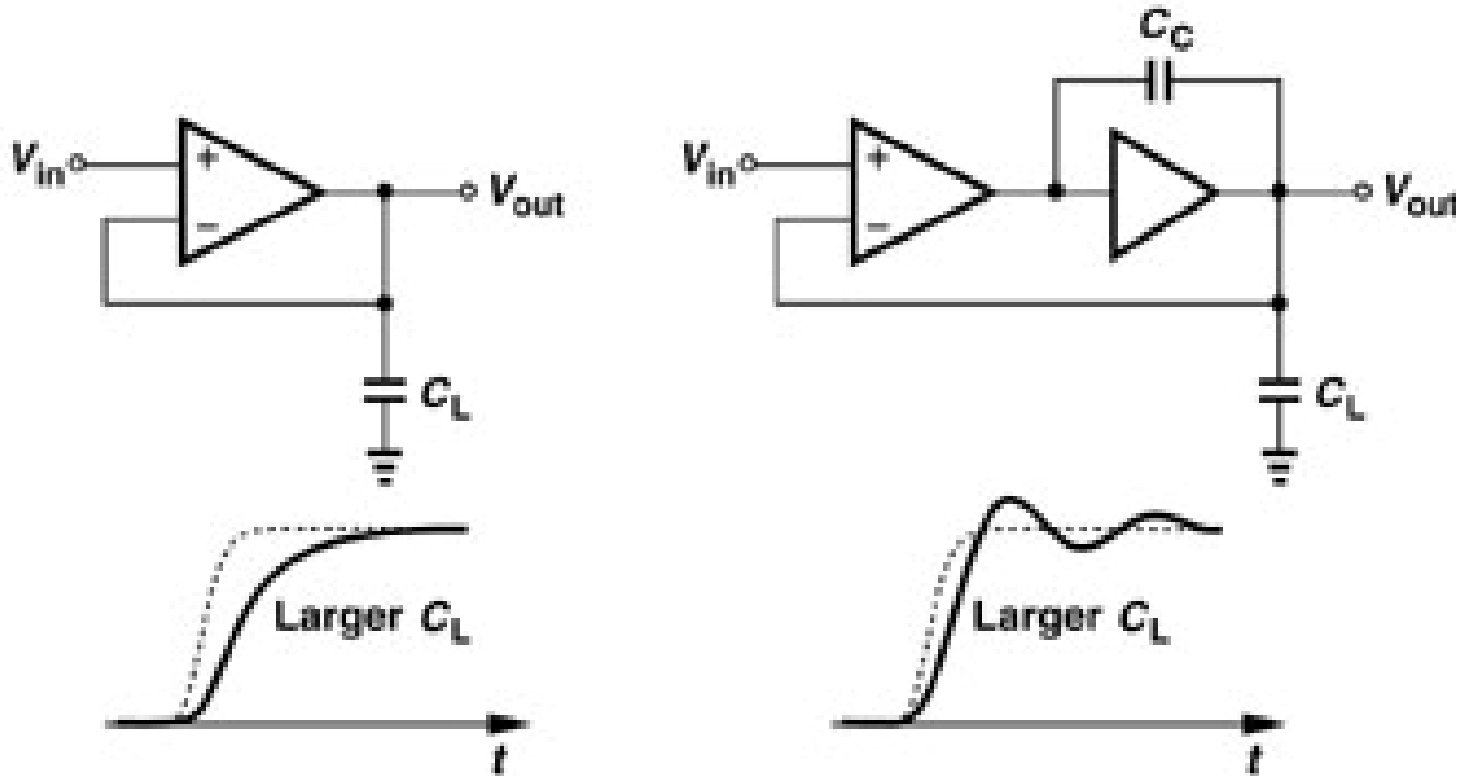





# Slewing in Two-Stage Op Amp

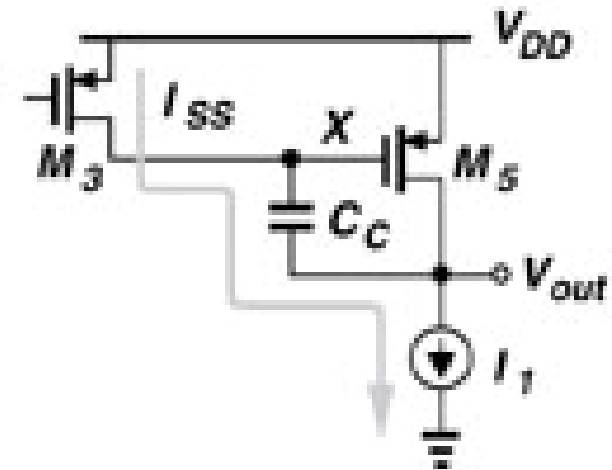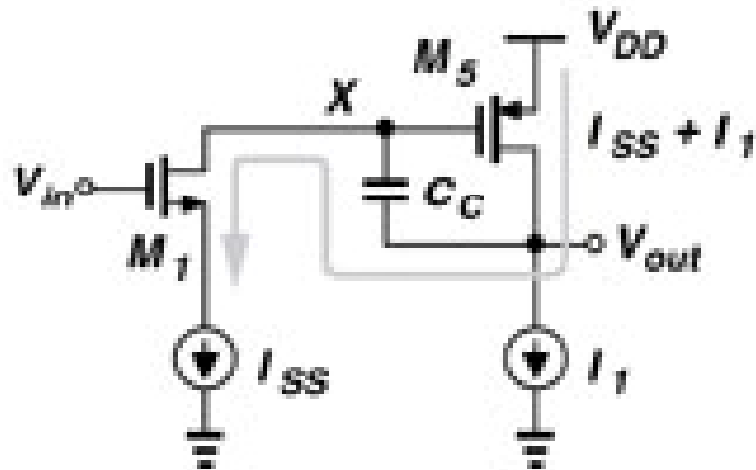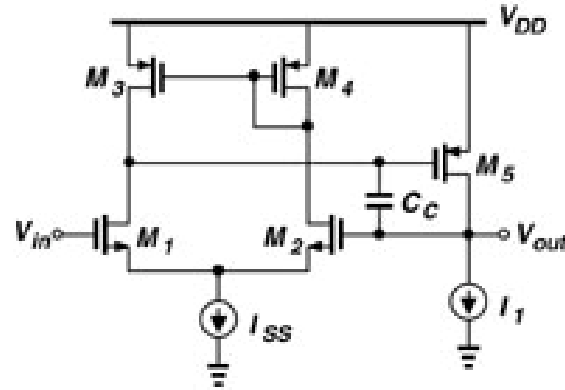




# Other Compensation Techniques

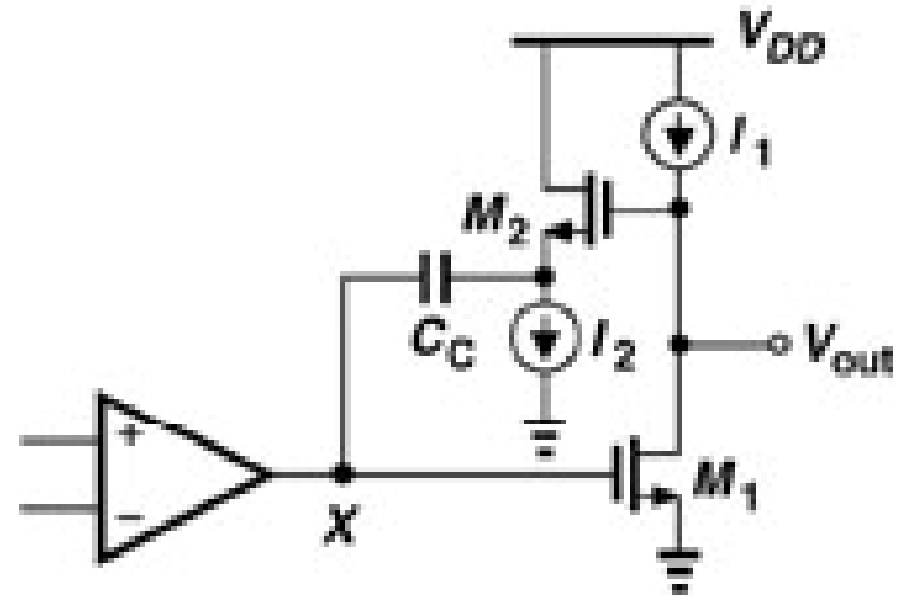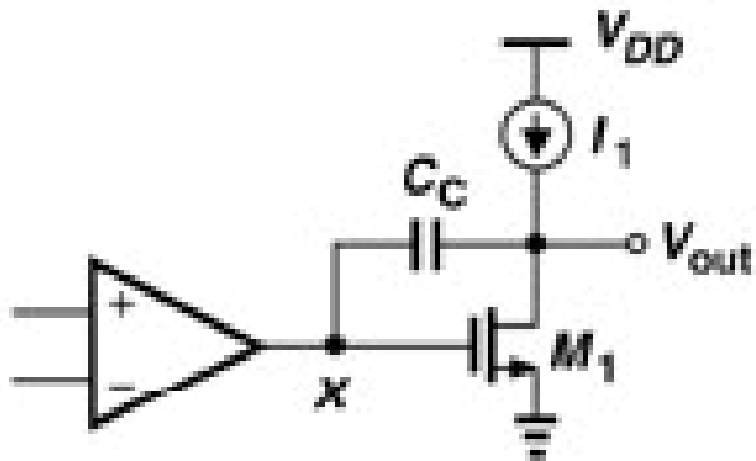

# Other Compensation Techniques (cont.)

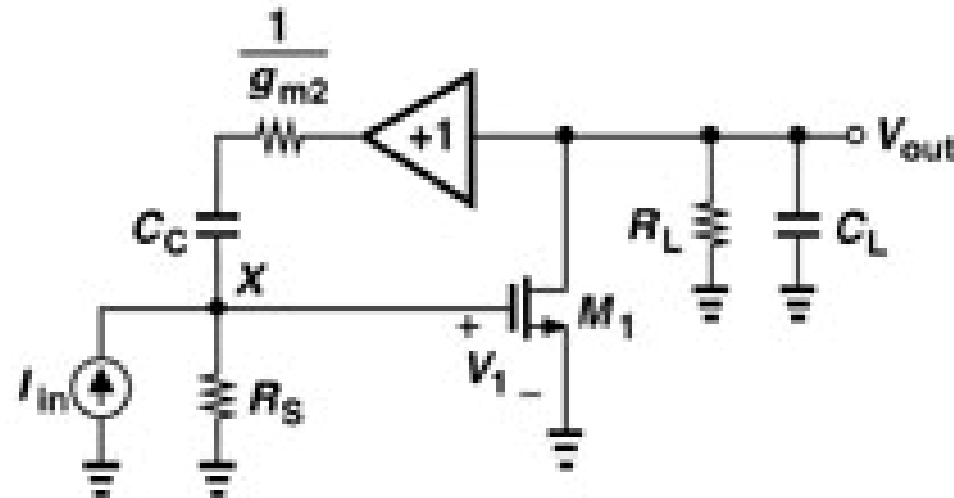


$$\frac{V_{out}}{I_{in}} = - \frac{g_{m1} R_L R_S (g_{m2} + C_L s)}{R_L C_L C_C (1 + g_{m2} R_S) s^2 + [(1 + g_{m1} g_{m2} R_L R_S) C_C + g_{m2} R_L C_L] s + g_{m2}}$$

$$1 + g_{m2} R_S \gg 1, \quad (1 + g_{m1} g_{m2} R_L R_S) C_C \gg g_{m2} R_L C_L$$

$$\omega_{p1} \approx \frac{1}{g_{m1} R_L R_S C_C}, \quad \omega_{p2} \approx \frac{g_{m1}}{C_L}$$


# Other Compensation Techniques (cont.)

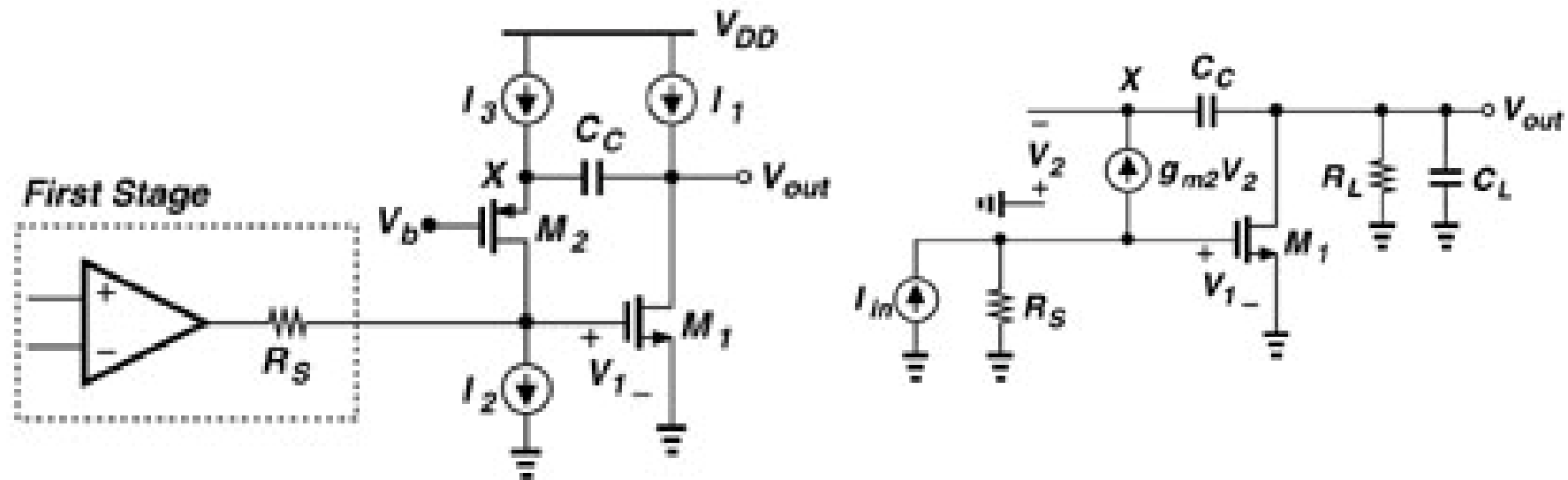


$$\frac{V_{out}}{I_{in}} = - \frac{g_{m1} R_S R_L (g_{m2} + C_C s)}{R_L C_L C_C s^2 + [(1 + g_{m1} R_S) g_{m2} R_L C_C + C_C + g_{m2} R_L C_L] s + g_{m2}}$$

$$\omega_{p1} \approx \frac{1}{g_{m1} R_L R_S C_C}, \quad \omega_{p2} \approx \frac{g_{m2} R_S g_{m1}}{C_L}$$

# Slewing with Common-Gate Compensation


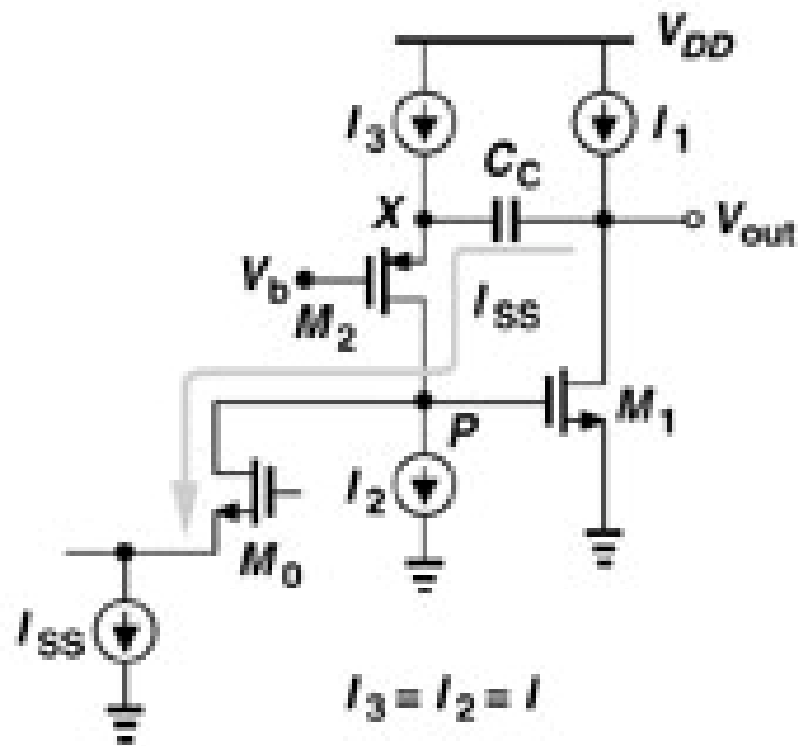


(a)

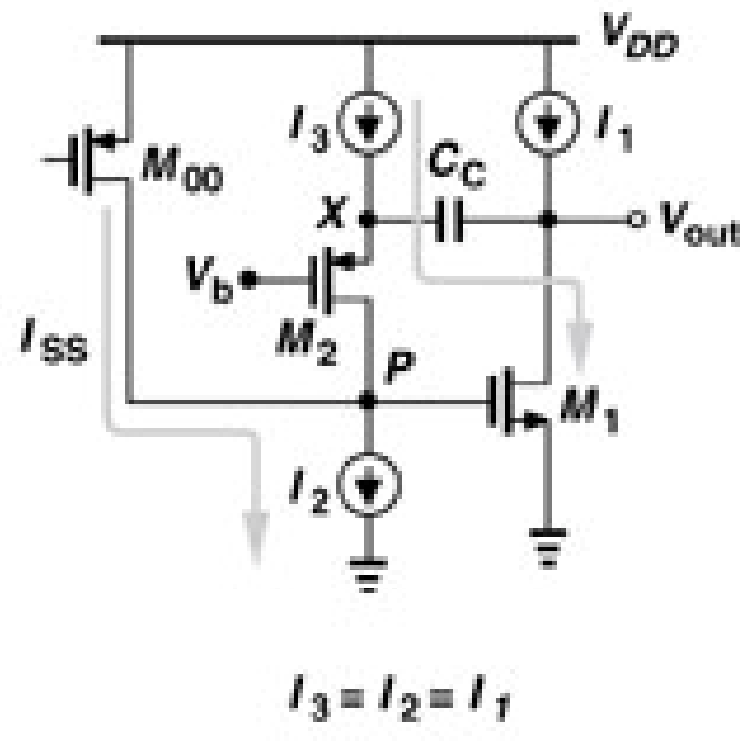

(b)

# Other Compensation Techniques (cont.)

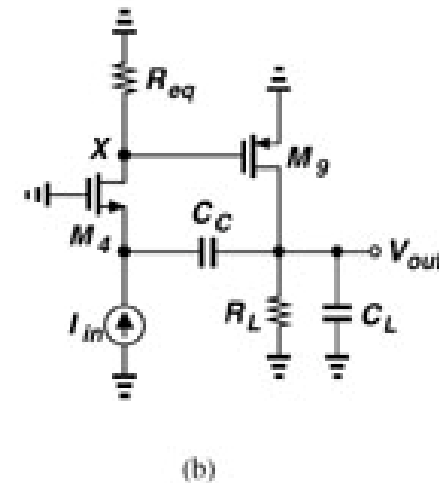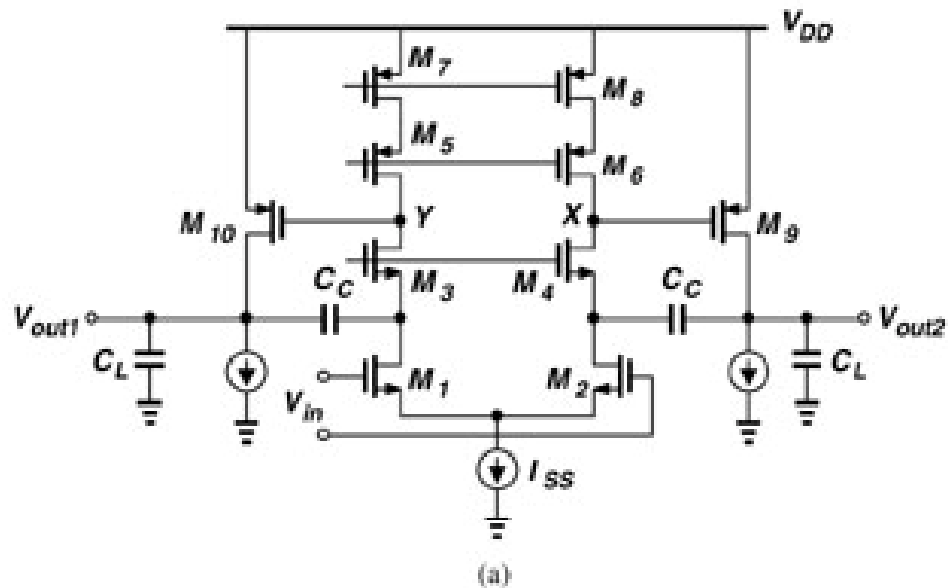

$$\omega_T \approx g_{m4} R_{eq} \cdot \frac{g_{m9}}{C_C}$$

$$\omega_{p1} \approx \frac{1}{g_{m9} R_{eq} R_L C_C}$$

$$\omega_{p2} \approx \frac{g_{m4} R_{eq} g_{m9}}{C_L}$$