


4. Amplifiers

Operational Amplifier
Instrumentation Amplifier
Analog Computation
Active Filter
Grounding
Isolation



Function of Amplifiers

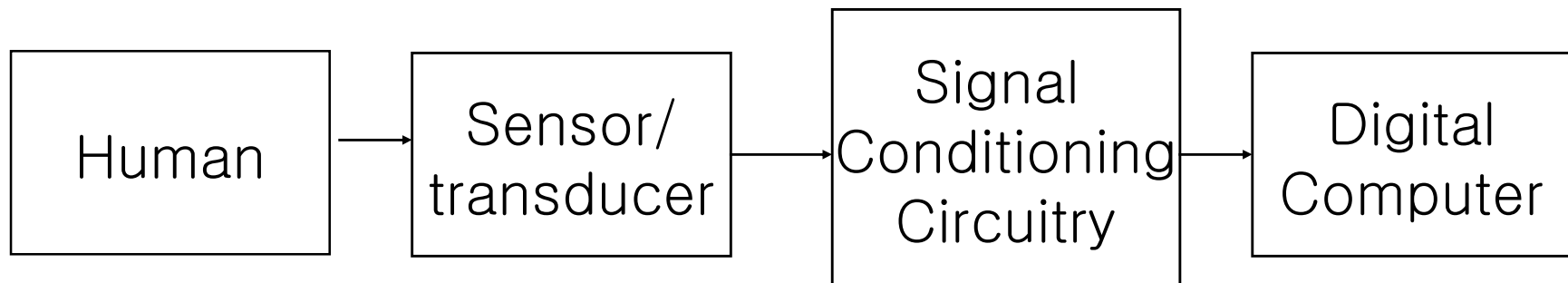- Amplifiers provides
 - GAIN
 - Filtering, Signal processing, Correction for Nonlinearities



Ideal Amps

- Assumptions

- Open loop Gain = Infinity

- Input Impedance $R_d =$
Infinity


- Output Impedance $R_o = 0$

- Bandwidth = Infinity

- Infinite Frequency Response

- $v_o = 0$ when $v_1 = v_2$

- No Offset Voltage



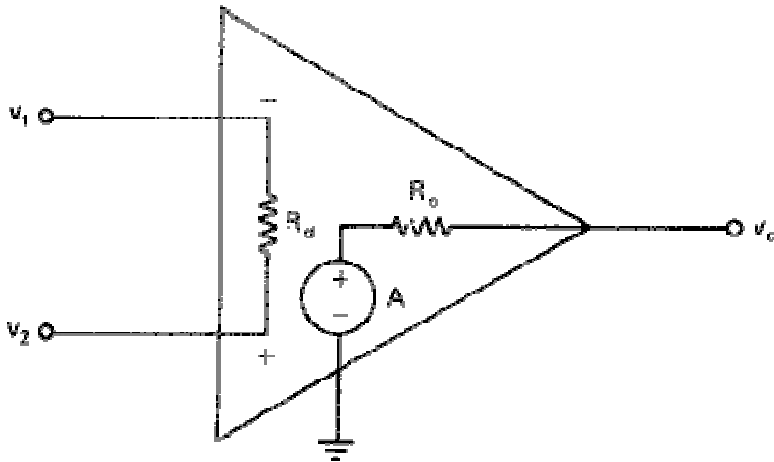


OP Amplifier Properties

Ideal Op. Amp.	ideally	means
gain(open-loop)	∞	$\geq 10^4$
open-loop BW	∞	Dominant Pole at 10Hz
CMRR	∞	$\geq 70\text{dB}$
Ri	∞	$\geq 10\text{M}\Omega$
Ro	0	$< 500\Omega$
I B	0	$< 0.5\mu\text{A}$
Vos	0	$< 10\text{mV}$
Ios	0	$< 0.2\mu\text{A}$



How do we achieve these properties?

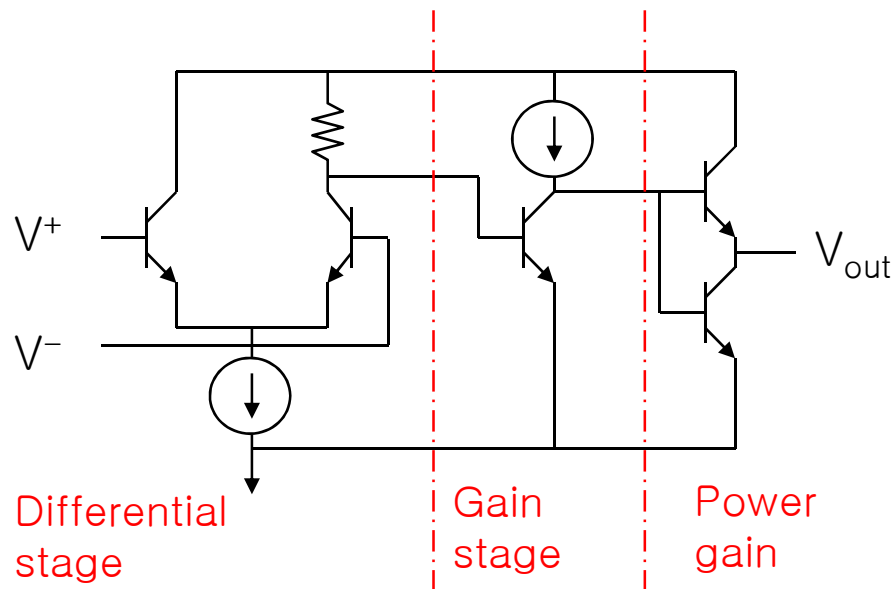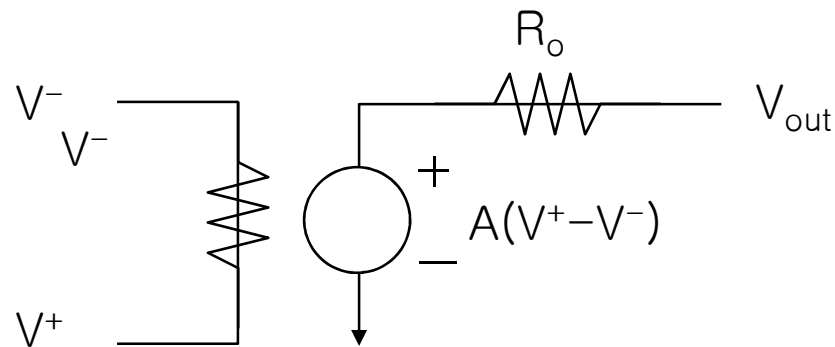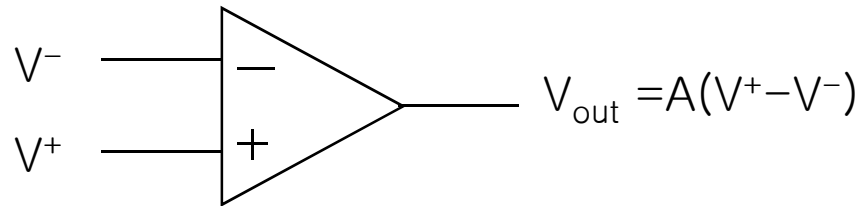

741인 경우
 (Stage 1) $R=1.6M\Omega$
 Gain=1200
 (Stage 2) V_{tg} gain=220
 (Stage 3) $R_o=60\Omega$
 V_{tg} gain=1
 Overall Gain=108dB




Ideal OP Amps

- Note
 - $v_0 = A(v_2 - v_1)$
 - If $v_0 = \infty$, $A = \infty$ (Typically 100,000)
 - Then $v_2 - v_1 = 0 \Rightarrow v_2 = v_1$
 - Since $v_2 = v_1$ and $R_d = \infty$
 - We can neglect the current in R_d
- Rule 1
 - When the OP Amp is in linear range the two inputs are at the same voltage (Virtual Ground)
- Rule 2
 - No Current flows into either terminal of the OP Amp



Thus, The Two rules of Ideal OP Amp.

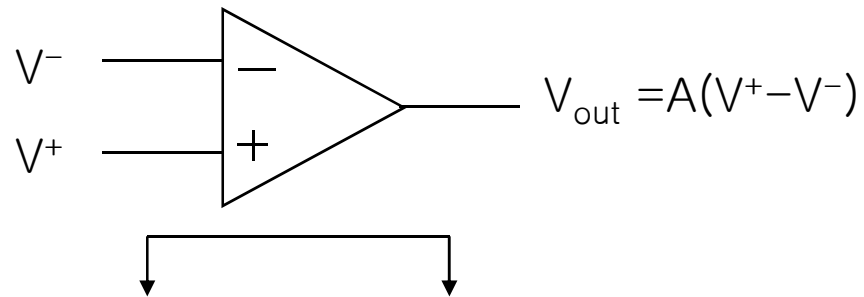

Rule 1: Op Amp의 output이 Linear Stage에 있을 때,
두 input은 동 전위에 있다. (Virtual Ground)

Rule 2: Op Amp의 input 단자에 입력되는 전류는 없다.
(infinite input impedance)




Basic OP Amp Circuit Blocks


- Inverting Amplifier
- Noninverting Amplifier
- Unity–Gain Amplifier
- Differential Amplifier
- Instrumental Amplifier
- The ECG(Electrocardiogram) Amplifier



Inverting Amp.

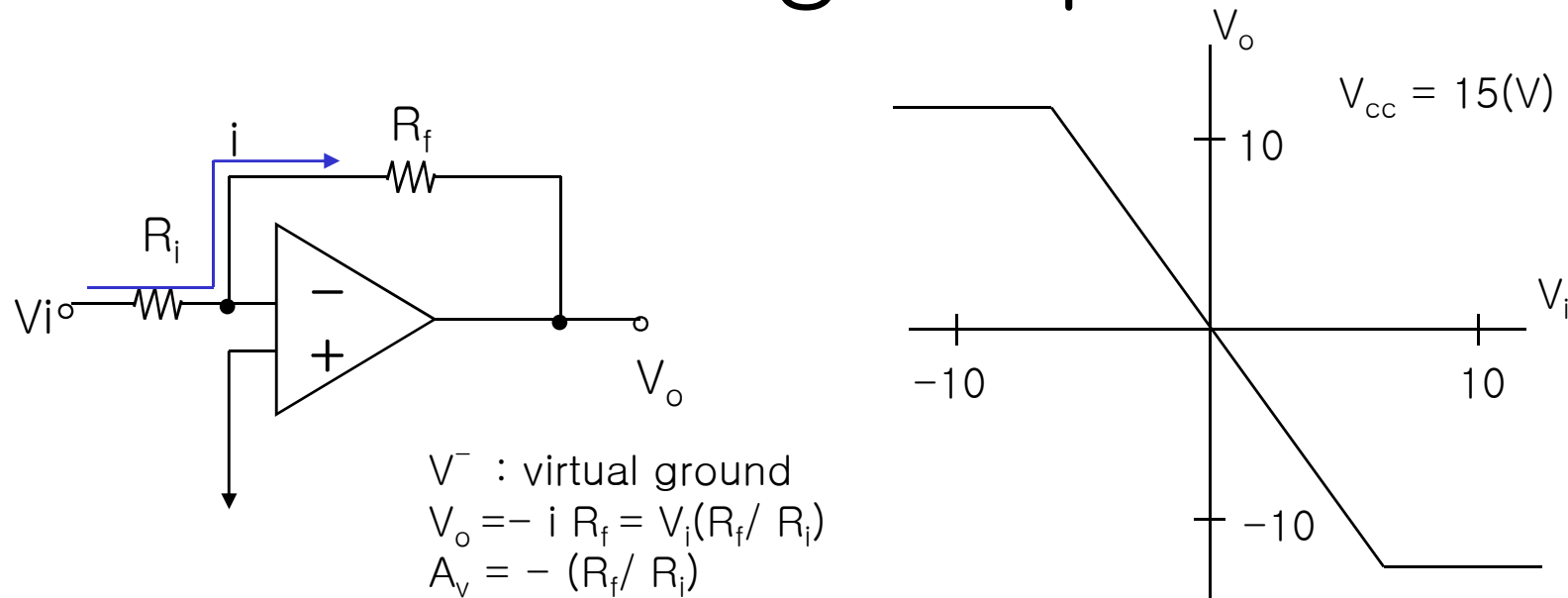


■ Summing

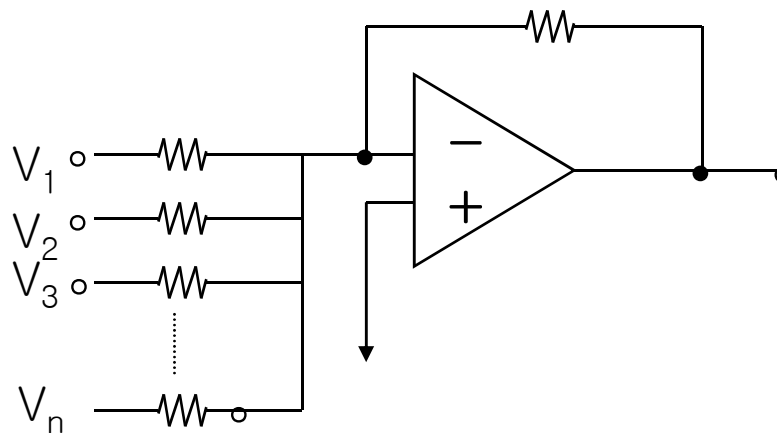

Inverting Amplifier (Cont.)

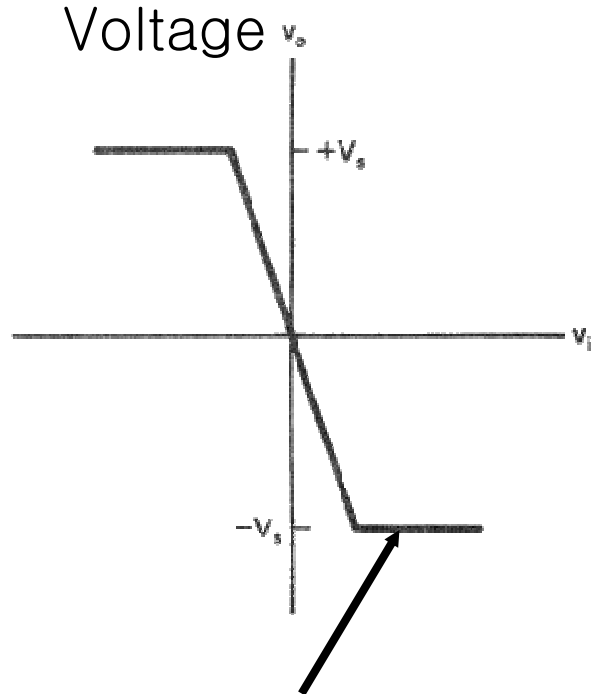- Linear Range
 - By Power Supply Voltage




Saturation

- Input Impedance
 - Low (R_i)
 - Increasing $R_i \rightarrow$ Decreasing Gain
 - Increasing Gain by increasing R_f
 - But there is practical limit




Why High Input Impedance ?

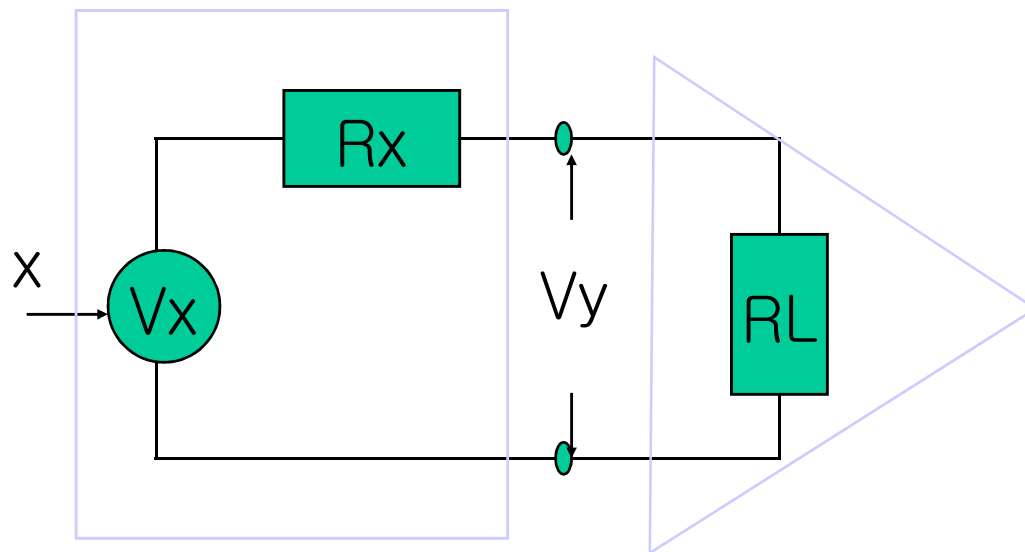- Concept of Loading
 - 계측기가 Sensor의 출력에 영향을 주고 싶지 않음
 - Sensor의 출력이 amplitude 인 경우에만 중요함.
Frequency 혹은 Digital 출력 인 경우에는 영향 없음
- Open Loop Output
 - V_x
- Voltage Drop by Load
 - $V_y = V_x - V_x \times R_x / (R_L + R_x)$
- Let $R_L \gg R_x$
 - $V_y = V_x$
 - Amp 혹은 계측기의 영향을 제거할 수 있음



Noninverting Amplifiers

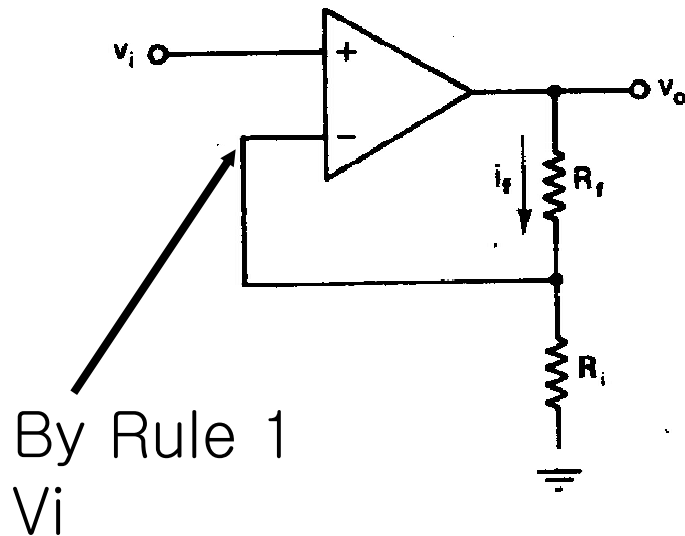- Noninverting Amp
 - Gain = $(R_f + R_i) / R_f$




- By Rule 2
 - $V_o = I_f \times (R_f + R_i)$
 - $V_i = I_f \times R_i$
 - $V_o = V_i \times (R_f + R_i) / R_i$
- Gain: $V_o / V_i = 1 + R_f / R_i$
- Gain ≥ 1 , Always
- Input Impedance
 - Very Large (Infinite)



Unity-Gain Amplifier

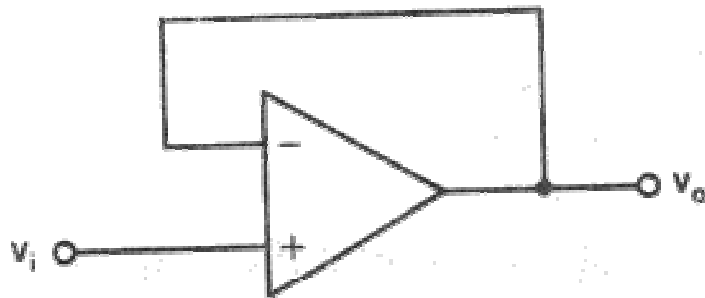- Homework #2-1
 - Verify that the Gain of Unity-Gain Amp is 1




- $V_o = V_i$
- Applications
 - Buffer amplifier
 - Isolate one circuit from the loading effects of a following stage
 - Impedance converter
 - Data conversion System (ADC or DAC) where constant impedance or high impedance is required




Differential Amplifiers

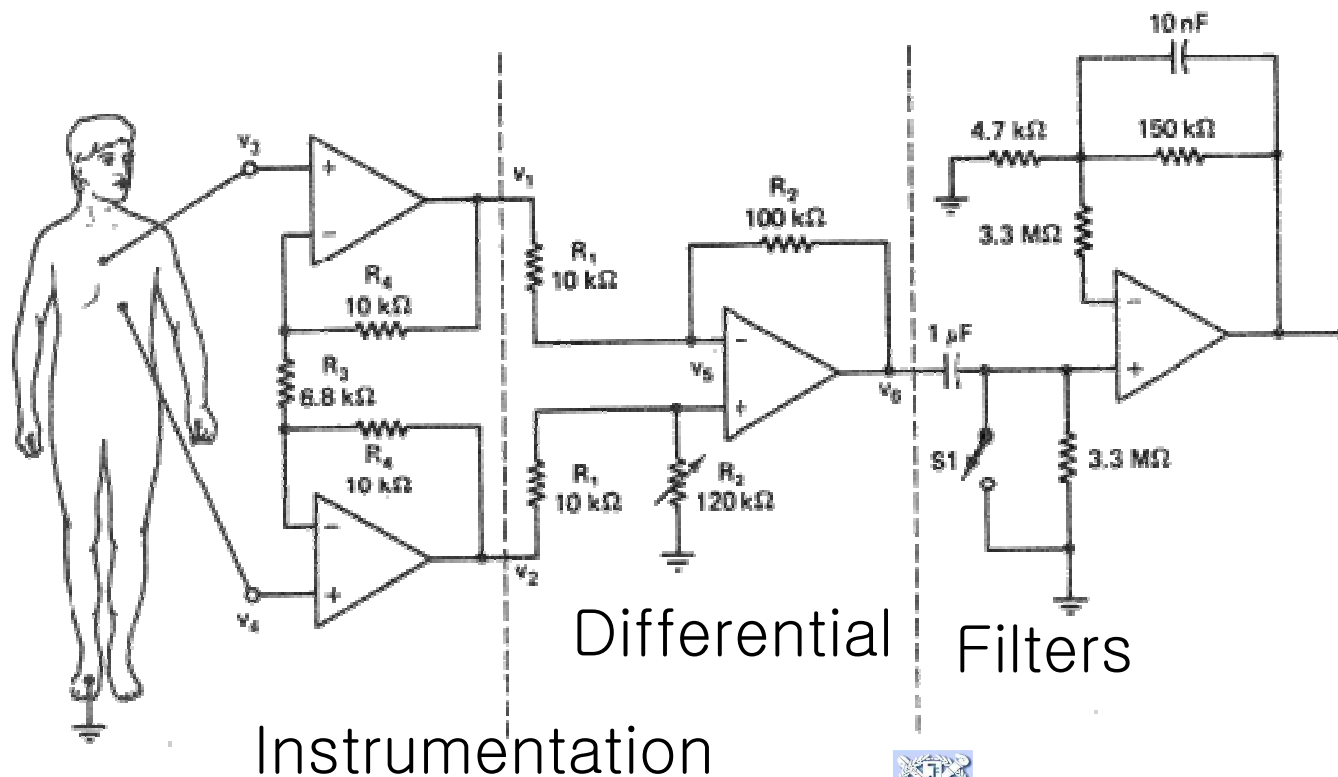- Combination of Inverting and Noninverting Amp
- Can reject 60Hz interference
- Example Use of Diff. Amp. In ECG amplifier




Non Inverting Amp.

- Follower

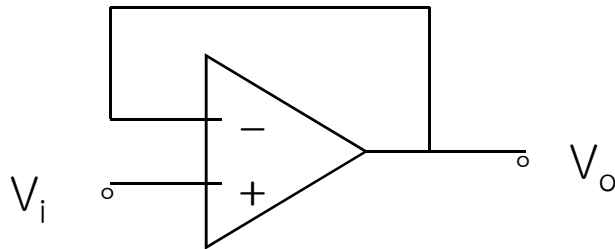

Buffer, Impedance Converter

- Non-inverting Amp.

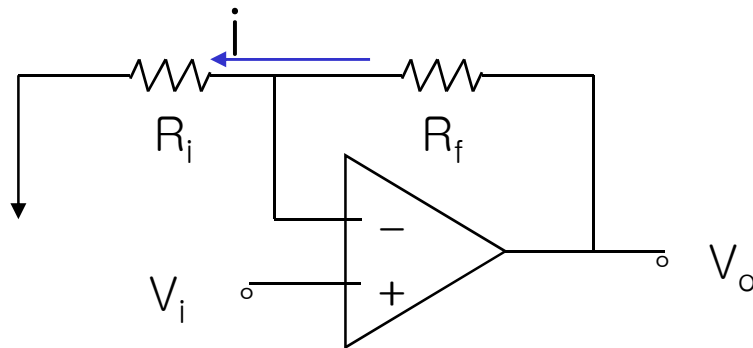

$$\begin{aligned} V_o &= i \cdot (R_i + R_f) \\ V_i &= i \cdot R_i \end{aligned}$$

$$\Rightarrow A_v = \frac{R_i + R_f}{R_i}$$




Instrumentation Amp– Differential Amp.

- High gain DC coupled differential amp with single ended output.

High Z_{in} , CMRR

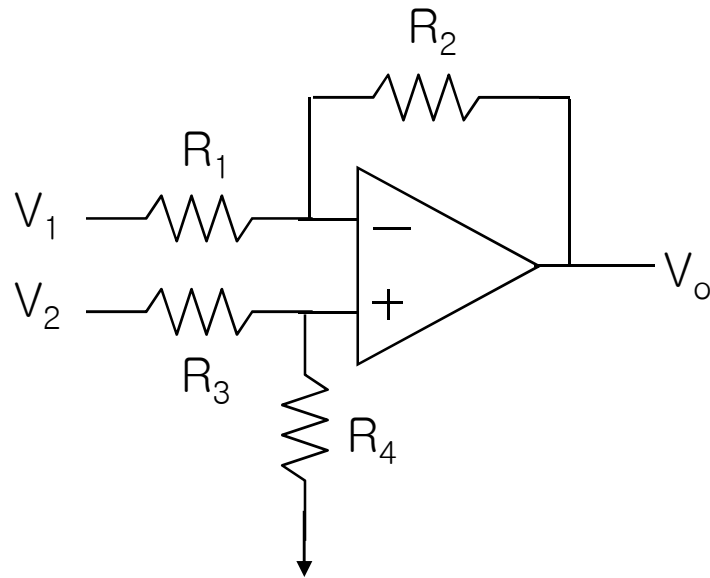Used to Amplify small differential signals from transducer where there may be a large common signal.



$$V^+ = V_2 \cdot \frac{R_4}{R_3 + R_4}, \quad V^- = (V_o - V_1) \frac{R_1}{R_1 + R_2} + V_1$$

$V^+ = V^-$ 로부터

$$V_o = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) V_2 - \frac{R_2}{R_1} V_1$$

$$\text{if } \frac{R_3}{R_4} = \frac{R_1}{R_2} \rightarrow V_o = \frac{R_2}{R_1} (V_2 - V_1), \quad G_d = \frac{R_2}{R_1}$$

Common mode $V_1 = V_2 \rightarrow V_o = 0 \rightarrow G_c = 0$

CMRR = G_d / G_c



Another look at the gain


- Gain of Differential Amp

- By Rule 2

- $V_5 = I_2 * R_2$
- $V_2 = I_2 * R_1 + V_5 = V_5 * R_1 / R_2 + V_5$
- $V_5 = R_2 * V_2 / (R_1 + R_2)$

- By Rule 1

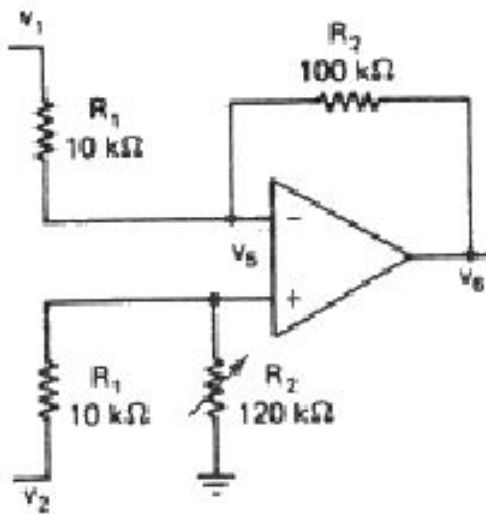- $V_1 = R_1 * I_1 + V_5$
- $V_5 = R_2 * I_1 + V_6$
- $V_6 = (V_2 - V_1) * R_2 / R_1$




Differential Amplifiers (Cont.)

- CMV (Common Mode Voltage)
 - If $V_1 = V_2$, then $V_6 = 0$
- CMG (Common Mode Gain) = 0
- DG (Differential voltage Gain)
 - If $V_1 \neq V_2$, then $V_6 = (V_2 - V_1) * (R_2 / R_1)$
- In practice, $CMG \neq 0$
- CMRR (Common Mode Rejection Ratio)
 - Measure of the ability to reject CMV
 - $CMRR = DG / CMG$
 - The Higher CMRR, the better quality
 - Typically, $100 \sim 10,000$
 - 60Hz noise common to V_1 and V_2 can be rejected



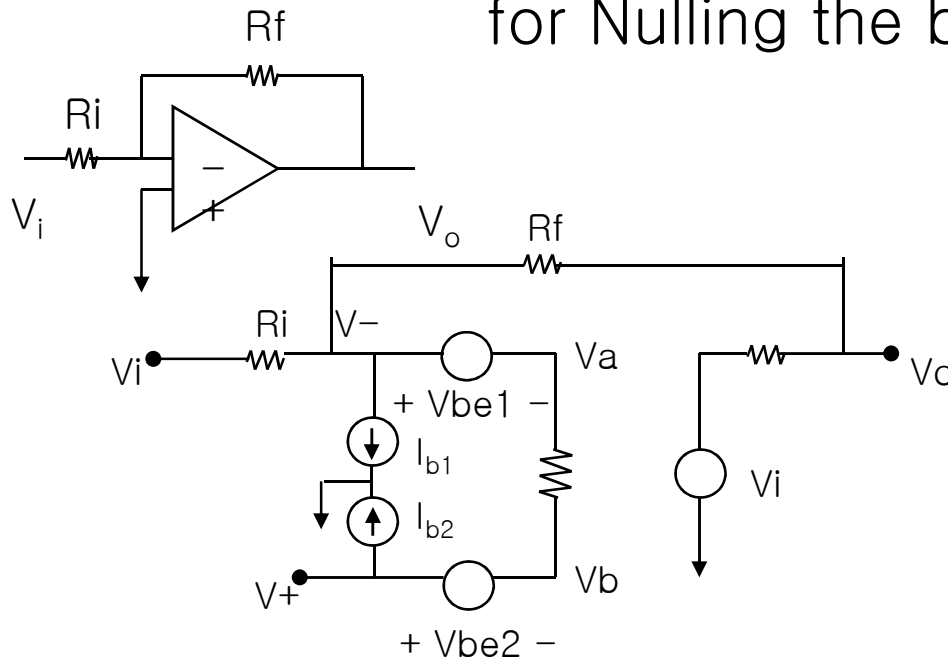Choice of resistors (R3 and R4) for Nulling the bias current



Assume

$$V^+ = V^-$$

$$I_{b1} = I_{b2} = I_b$$


$$\frac{V_o - V^-}{R_f} + \frac{V_i - V^-}{R_i} = I_b \quad (\text{eq 1})$$

Ideally we want, $V_o/R_f = -V_i/R_i$ (eq 2)

Comparing eq 1 and 2,

$$I_b + V^+ / (R_f // R_i) = 0$$

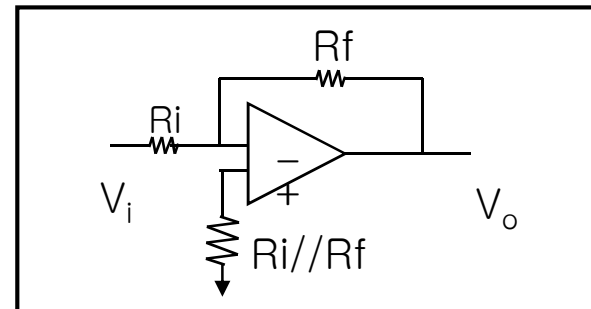This condition can be satisfied by the next circuit.




Instrumentation Amplifiers

- The One OP Amp Differential Amplifier is not desirable.
 - Input Impedance is not so High
 - Good for Low impedance source
 - Strain gage Bridge
 - Bad for High impedance source
- Thus An Instrumentation Amplifier consists of
 - Differential Amp with High Input Impedance and Low Output Impedance
 - Two Noninverting Amp + One Differential Amp



For High Input Impedance

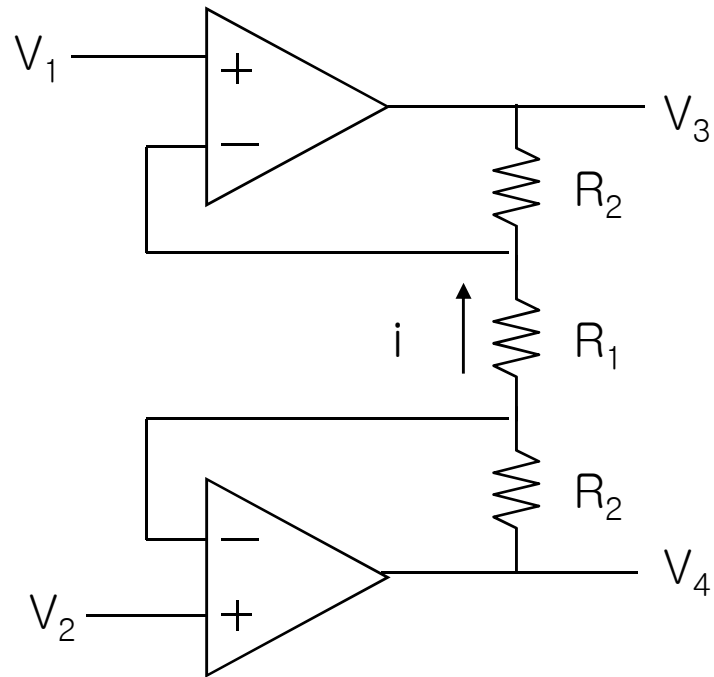

If $V_1 = V_2$ (CMG)
 $\rightarrow i = 0$
 $\rightarrow V_1 = V_2 = V_3 = V_4$
 $\rightarrow G_c$ (CMG) = 0

If $V_1 \neq V_2$ (DMG)
 $\rightarrow i = (V_2 - V_1) / R_1$


$$\frac{V_4 - V_3}{V_2 - V_1} = \frac{R_1 + 2R_2}{R_1} = 1 + 2 \cdot \frac{R_2}{R_1}$$



Complete Design of Instrumentation Amp.


$$V_{out} - V_{ref} = G(v_2 - v_1)$$
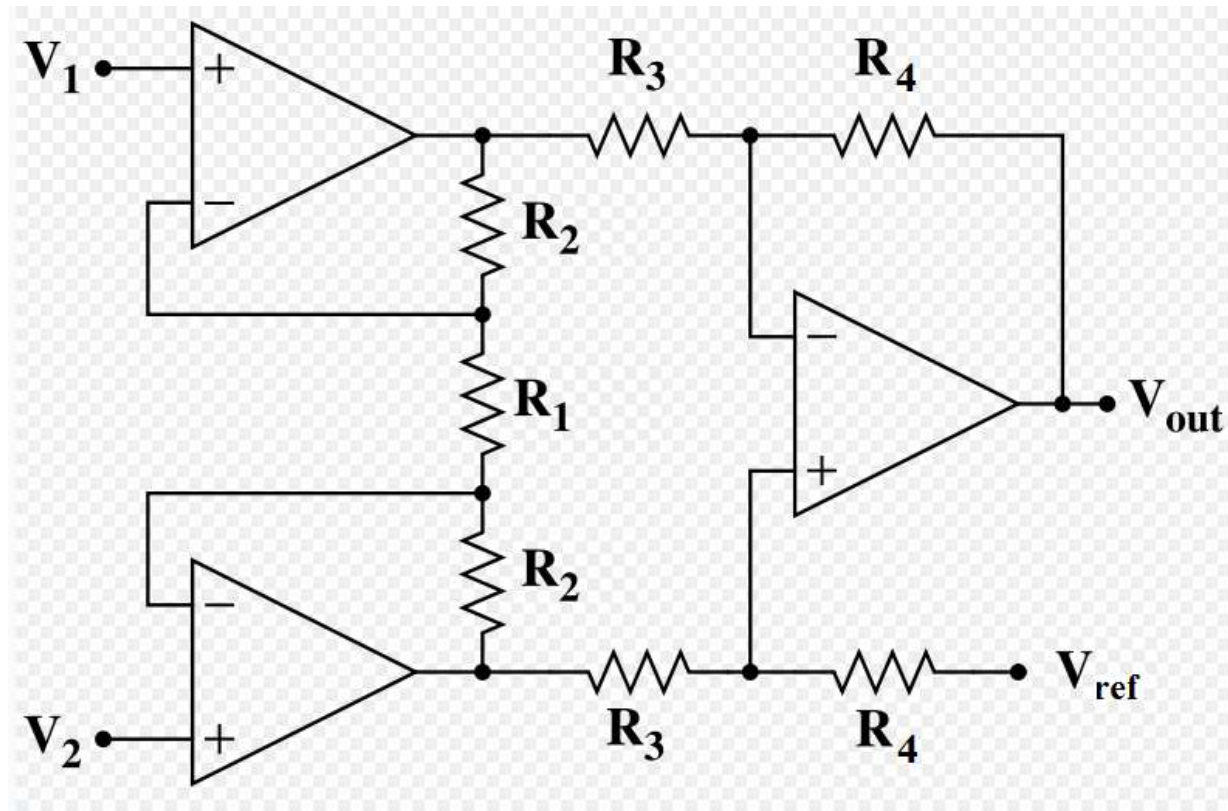
$$G = \frac{R_4}{R_3} \left(1 + 2 \frac{R_2}{R_1} \right)$$



Instrumentation Amplifiers (Cont.)

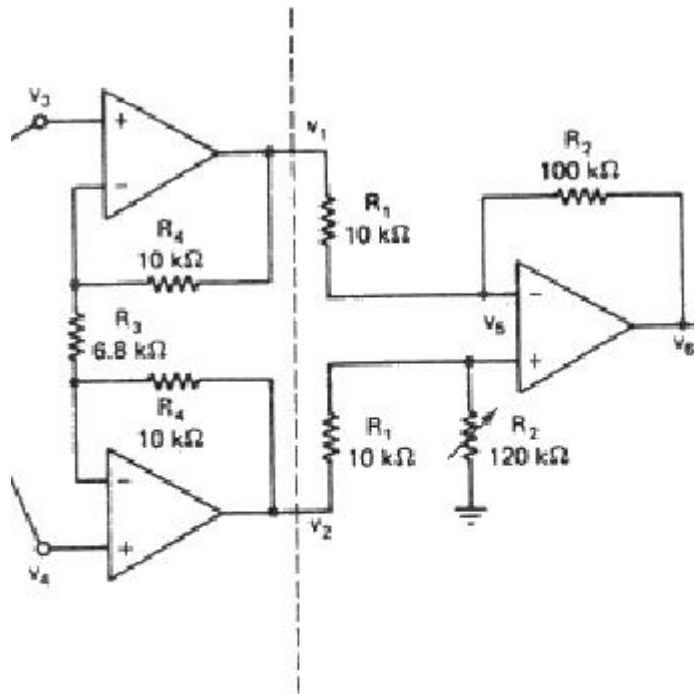- Instrumentation Amp =
Noninverting Amp +
Differential Amp



- $DG = (V1 - V2) / (V3 - V4)$
 $= (2 \cdot R4 + R3) / R3$
- $V6 = (V3 - V4) \cdot DG \cdot R2 / R1$

- First Stage CMRR
 - $CMRR = DG / CMG = DG$
- Overall $CMG = 0$
 - High CMRR
- High Input Impedance
- Gain is adjustable by changing $R3$




Analog Computation

- Digital Signal Processing is preferred
 - Flexibility
 - Easy to Change
 - Elimination of hardware
- Analog Signal Processing
 - Is preferred when DSP consumes too much time



Inverter and Scale Changer

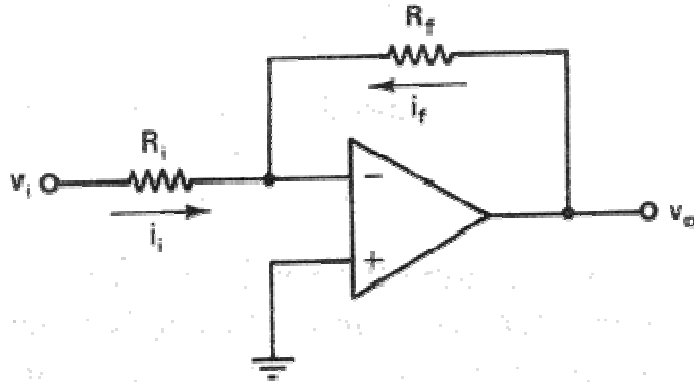- Inverting Amp with Gain = $- R_f / R_i$




- Inverter
 - $R_f / R_i = 1$
- Inverter and Scale Changer
 - Proper choice of R_f / R_i
- Application
 - Use of inverter to scale the output of DAC



Adders (Summing Amplifiers)

- Adder
 - Inverter with Several inputs

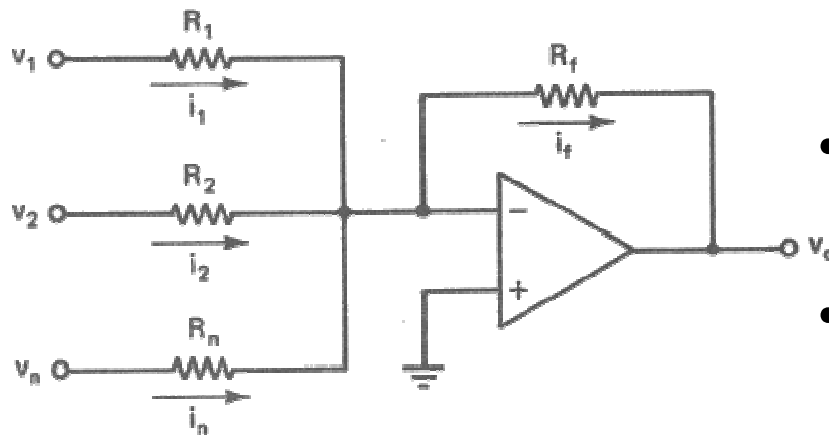


- $V_o = -R_f(V_1/R_1 + V_2/R_2 + \dots + V_n/R_n)$
 - $I_f = I_1 + I_2 + I_n$
 - $I_1 = V_1/R_1, \dots$
 - $V_o = -I_f * R_f$
- R_f determines overall Gain
- R_i determines weighting factor and input impedance



Integrator

- Self homework
 - Show that
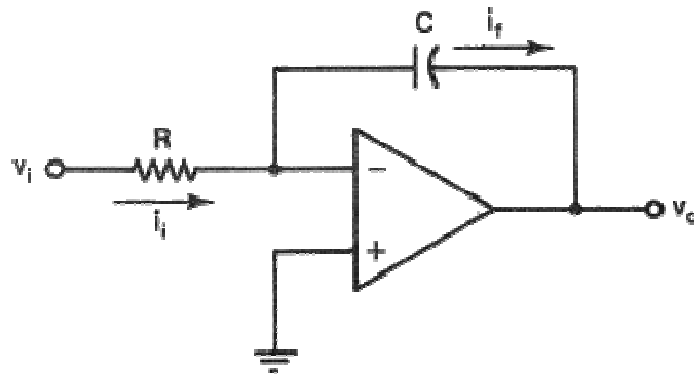
$$v_o = \frac{-1}{RC} \int_0^{t_1} v_i dt + v_{ic}$$




- Drawbacks
 - V_o will reach saturation voltage, if V_i is left connected indefinitely
 - Integrator operates as an open-loop amplifier for DC inputs



Differentiators


- Self Homework
- Show that

$$v_o = -RC \frac{dv_i}{dt}$$

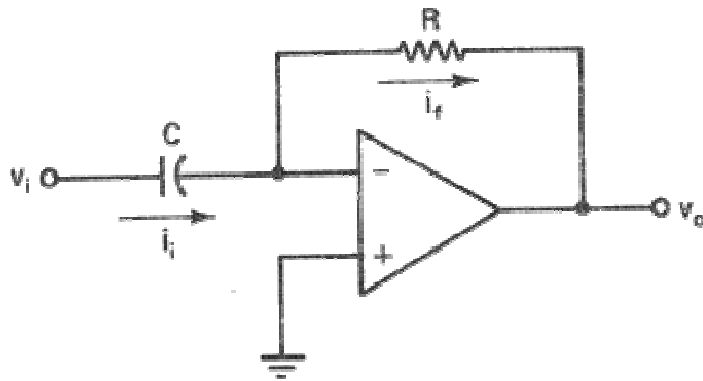

- Drawbacks
 - Instability at High frequencies
- Practical Differentiator

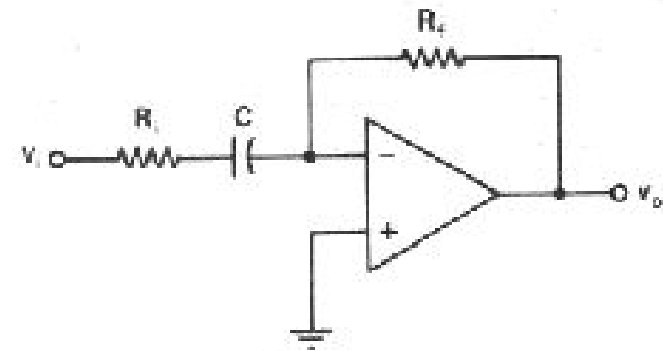
- To Stable $R_i = \sqrt{\frac{R}{A_0 \omega_0 C}}$



Comparators


- Compare Two Inputs

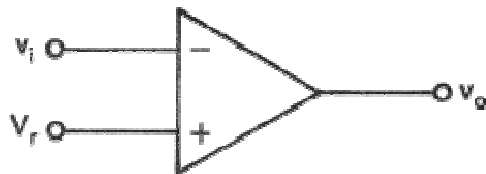- $V_i > V_r$
 - $V_o = -V_s$
- $V_i < V_r$
 - $V_o = V_s$



- Drawbacks

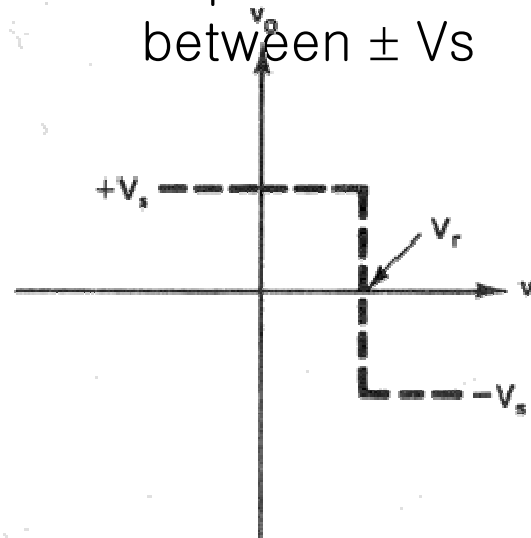- If $V_i = V_r + \text{small noise}$
 - Rapid fluctuation between $\pm V_s$



Comparators with Hysteresis



- Positive Feedback
 - Hysteresis loop
 - Can remove the effect of Small Noise
 - Reduce Fluctuation

- Homework

- Show that


$$V_r + \Delta V_r = V_r + \frac{(V_S - V_r)R_1}{R_1 + R_2}$$
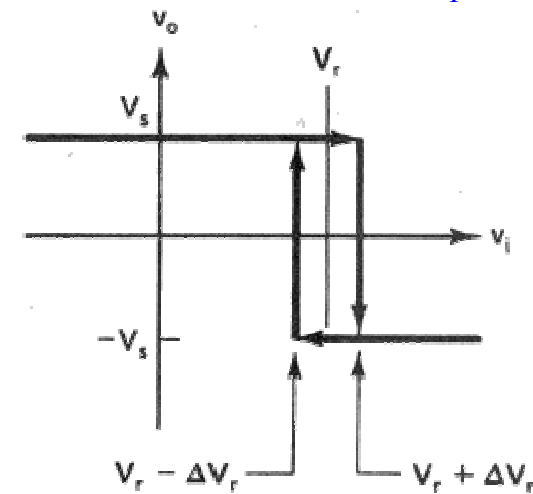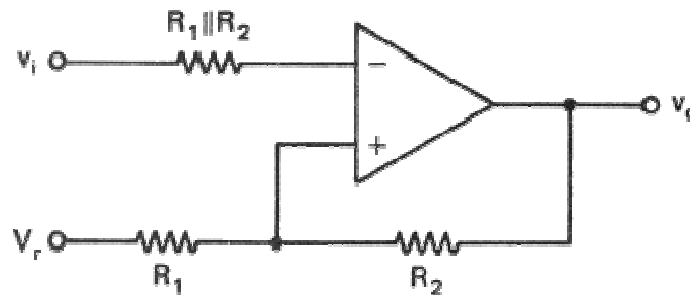
$$V_r - \Delta V_r = V_r + \frac{(-V_S - V_r)R_1}{R_1 + R_2}$$




Rectifiers


- Precision Half Wave Rectifier

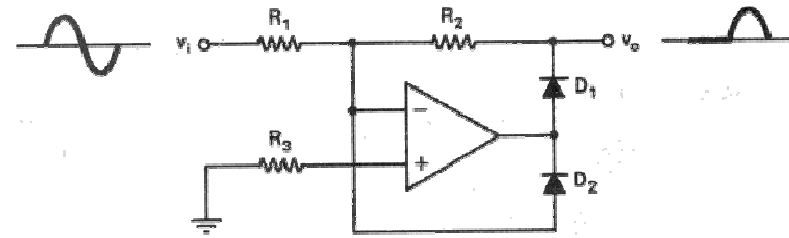

- Precision Full Wave Rectifier

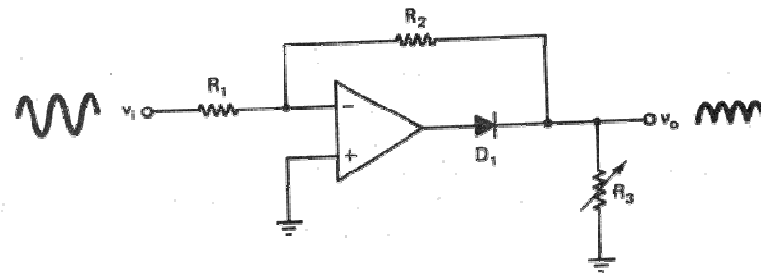

- Limiters

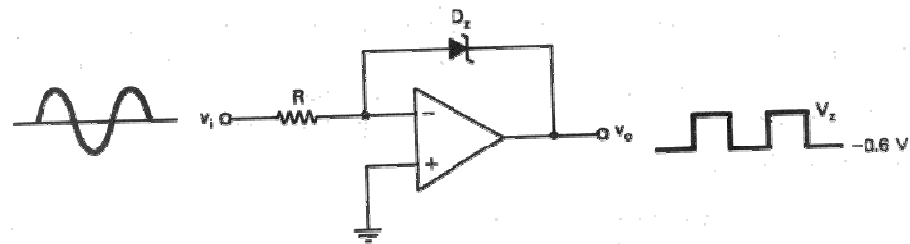

Practical OP Amp Considerations

- Effects of Nonlinear characteristics
 - Compensation
 - Undesirable Oscillation at High frequency
 - Add external Capacitance according to Spec sheet
 - GBW (Gain Bandwidth Product)
 - $\text{Gain} \times \text{Bandwidth} = \text{Constant}$ (Typically 1MHz)
 - For Noninverting Amp: $\text{Bandwidth} = \text{GBW} / \text{Gain}$
 - Input Offset Voltage
 - Practical OP Amp
 - Zero input Does NOT give Zero output
 - Input Offset Voltage
 - Applied input voltage to obtain Zero output
 - Nulling the offset Voltage
 - Adding External Resister according to Spec sheet



OP Amp Considerations (Cont.)

- Input Bias Current
 - Practical OP amp
 - Current flowing into the terminal is NOT Zero
 - To keep the input Tr of OP amp turned on
 - Causes errors proportional to feedback network R
 - To minimize errors
 - feedback R should be low ($<10\text{K}\Omega$)
- Slew Rate
 - Maximal rate of change of amplifier output voltage
 - Ex: Slew rate of 741 = $0.5\text{ V} / \mu\text{s}$
 - » Time to output change from -5V to 5V = $20\ \mu\text{s}$
 - To Minimize slew rate problem
 - Use OP amp with smaller external compensating C



OP Amp Considerations (Cont.)

- Power Supply
 - Usually $\pm 15V$
 - Linear Range $\pm 13V$
 - Reducing power supply voltage
 - Results reduced linear range
 - Device does not work $< 4V$
- Different OP Amps
 - Bipolar Op Amps
 - Good input offset stability
 - Moderate input bias current and Input resistances
 - FET
 - Very Low input bias current and Very High Input resistances
 - Poor Input offset voltage stability



OP Amps on the market

- Common OP amps, Typical Specifications

Figure 1.18 shows characteristics of commonly used op amps.

Type	Feature	Input bias current	Offset voltage	GBW	Price
741	Low cost	80 nA	2 mV	1 MHz	\$0.35
308	Low bias current	3 nA	2 mV	1 MHz	0.69
ICL8007	FET input	50 pA	50 mV	1 MHz	5.00
CA3130	FET input	6 pA	20 mV	4 MHz	0.89
OP-07	Low offset	1 nA	30 μ V	800 kHz	1.99
LH0052	Low offset	0.5 pA	0.1 μ V	1 MHz	5.00
LF351	High GBW	50 pA	5 mV	4 MHz	0.62
LM312	Low bias current	3 nA	0.7 mV	1 MHz	2.49
UC4250	Programmable	7.5 nA	4 mV	800 kHz	1.84




Filters

- Passive Circuits
 - Contains only passive elements
 - Resistors, Capacitors and Inductors
 - Examples
 - Bridge Circuit
 - Voltage Divider
 - Filters
- Filters
 - Eliminate unwanted signal from the loop
 - Low Pass, High Pass, Band Pass, Notch, ...




Passive first-order Low pass Filter

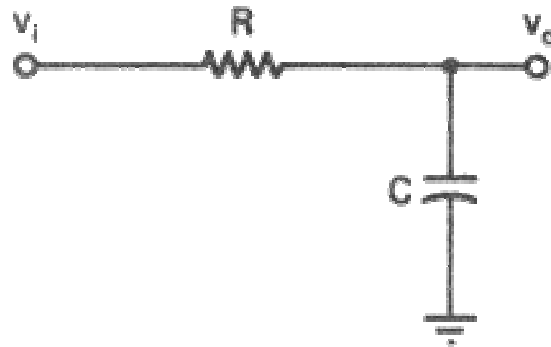- Pass desired Audio signal and reject undesired RF
- Order of Filter
 - Number of C and L



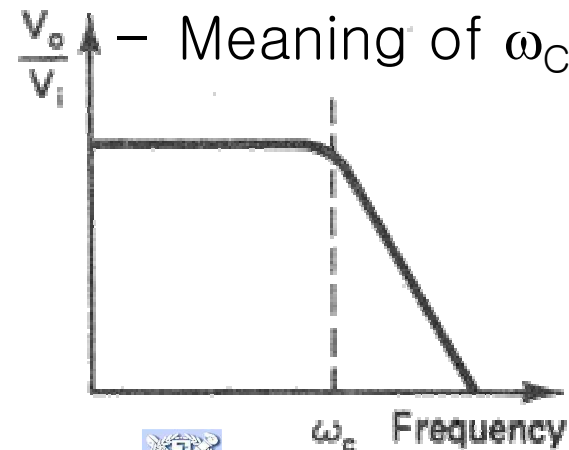- - Show that
$$\frac{V_o}{V_i} = \frac{1}{1 + j\omega\tau}, \quad \tau = RC$$
 - Plot Magnitude and Phase plot (Bode plot)





Passive first-order High pass Filter

- Pass desired High frequency signal and reject undesired low frequency signal

- ◆ Show that

$$\frac{V_o}{V_i} = \frac{j\omega\tau}{1+j\omega\tau}, \quad \tau = RC$$

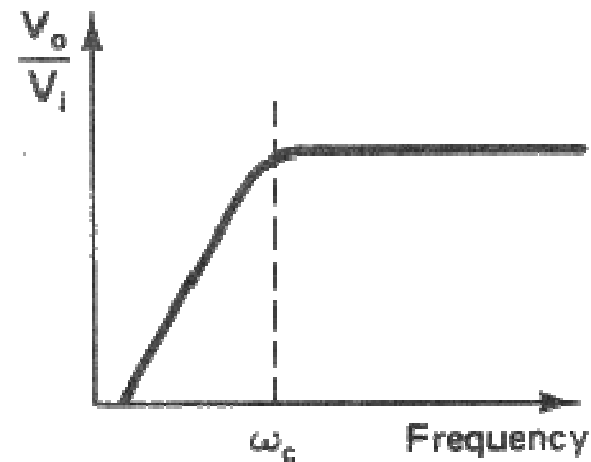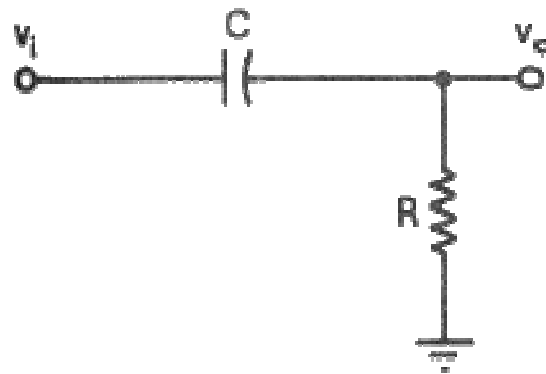- ◆ Plot Magnitude and Phase plot (Bode plot)
- ◆ Meaning of ω_c



Passive second-order Low pass Filter

- To increase the attenuation of transfer function
- Order of Filter
 - ◆ Number of C and L



◆ Show that

$$\frac{V_o}{V_i} = \frac{1}{(j\omega/\omega_c)^2 + (2\zeta j\omega/\omega_c) + 1}$$

$$\omega_c = \sqrt{\frac{1}{LC}}, \zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

◆ Meaning of Quality factor
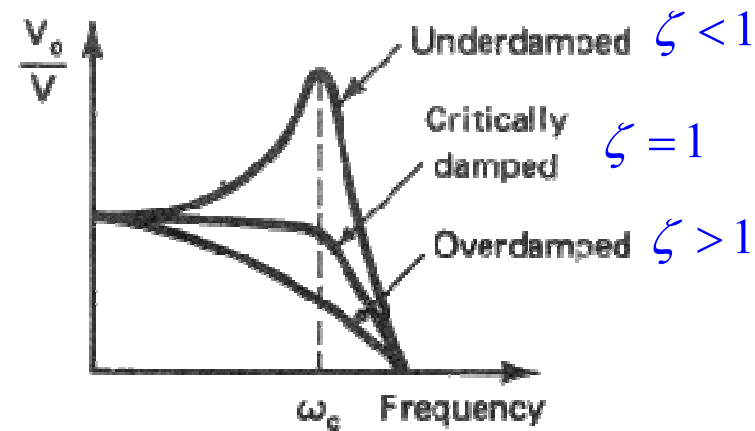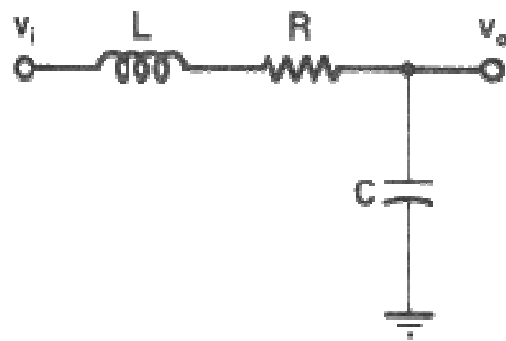
$$Q = \frac{1}{2\zeta} = \frac{\omega_c}{\Delta\omega}, \Delta\omega = 3dB BW$$





Passive second-order High pass Filter

- To increase the attenuation of transfer function
- Order of Filter
 - ◆ Number of C and L

◆ Show that



$$\frac{V_o}{V_i} = \frac{\omega^2}{(j\omega/\omega_c)^2 + (2\zeta j\omega/\omega_c) + 1}$$
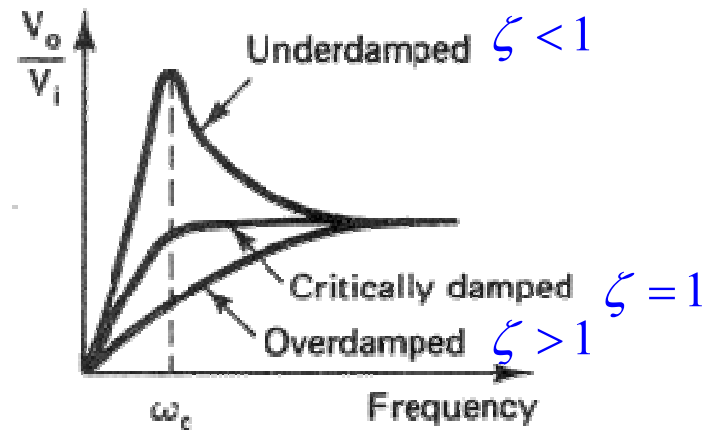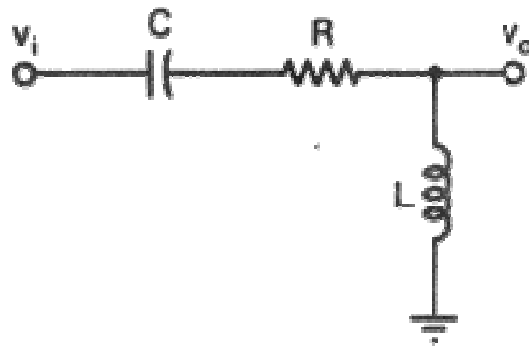
$$\omega_c = \sqrt{\frac{1}{LC}}, \zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$





Active First-order Low Pass Filter

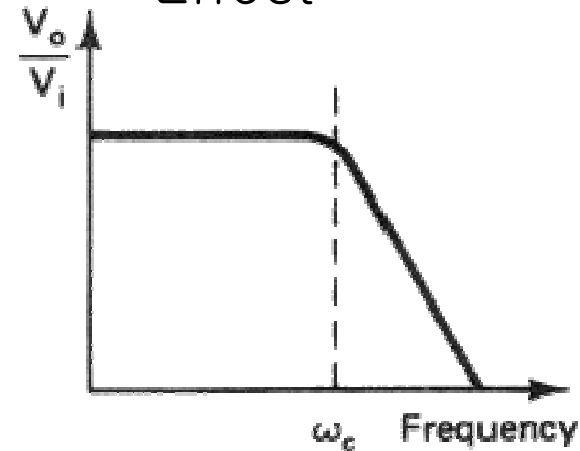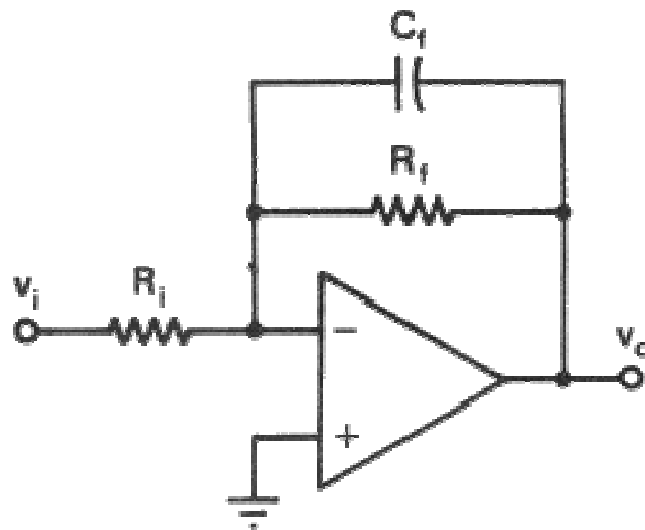- Inverting Amp + Feedback Capacitor
- Identical frequency response with Passive filter
- Very Low Output impedance
 - Negligible Loading Effect





Active First-order High Pass Filter

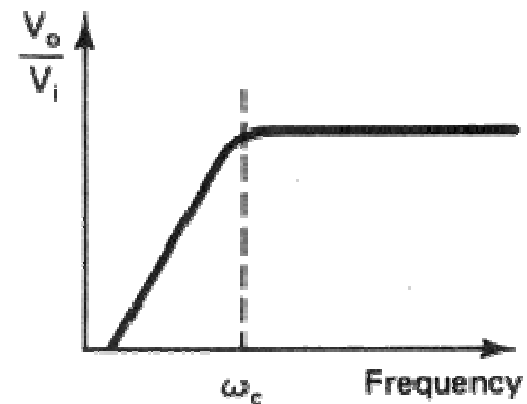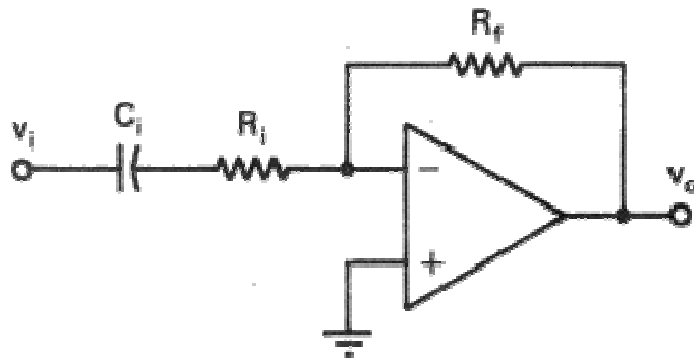- Inverting Amp + Input Capacitor
- Identical frequency response with Passive filter
- Very Low Output impedance
 - ◆ Negligible Loading Effect





Active High-order Filters

- Low Pass Filters

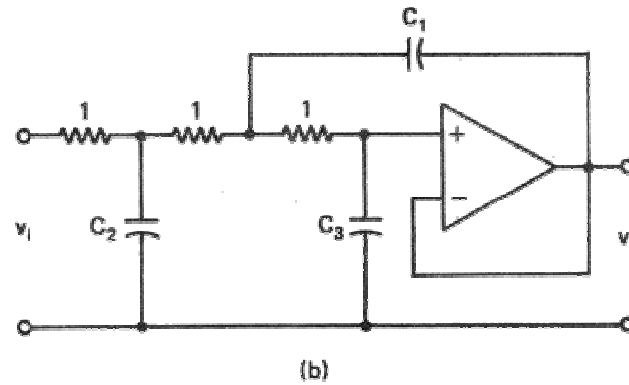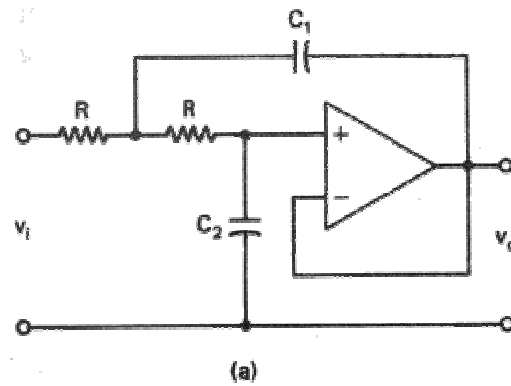

- High Pass Filters

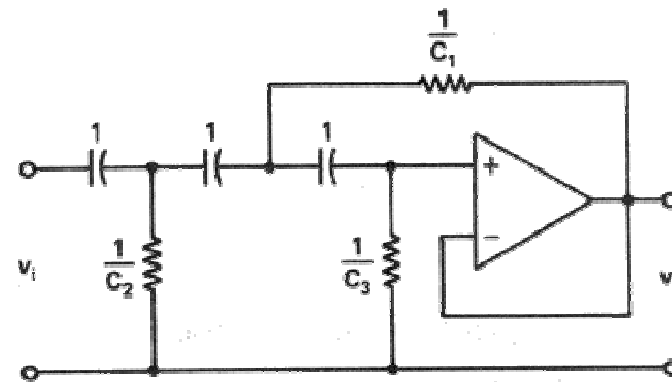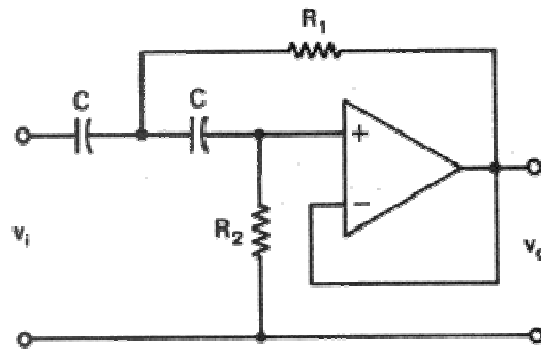

Bandpass and Band-reject Filters

- Butterworth Filters
 - Maximally Flat Magnitude response in pass band
 - High Attenuation Rate
- Chebyshev Filters
 - Maximum Attenuation Rate
 - Ripple in pass band
- Bessel Filters
 - Maximally flat time delay in response to step input
 - Attenuation Rate is very gradual



Filter Design Table


- C when $\omega_0 = R_0 = 1$

Poles	C_1	C_2	C_3	C_1	C_2	C_3
	Bessel			Butterworth		
2	9.066 -1	6.799 -1		1.414 +0	7.071 -1	
3	1.423 +0	9.880 -1	2.538 -1	3.546 +0	1.392 +0	2.024 -1
4	7.351 -1	6.746 -1		1.082 +0	9.241 -1	
	1.012 +0	3.900 -1		2.613 +0	3.825 -1	
5	1.009 +0	8.712 -1	3.095 -1	1.753 +0	1.354 +0	4.214 -1
	1.041 +0	3.098 -1		3.235 +0	3.089 -1	
6	6.352 -1	6.098 -1		1.035 +0	9.660 -1	
	7.225 -1	4.835 -1		1.414 +0	7.071 -1	
	1.073 +0	2.561 -1		3.863 +0	2.588 -1	
	2-dB Chebyshev			0.25-dB Chebyshev		
2	2.672 +0	5.246 -1		1.778 +0	6.789 -1	
3	2.782 +1	3.113 +0	3.892 -2	8.551 +0	2.018 +0	1.109 -1
4	4.021 +0	1.163 +0		2.221 +0	1.285 +0	
	9.707 +0	1.150 -1		5.363 +0	2.084 -1	
5	1.240 +1	4.953 +0	1.963 -1	5.543 +0	2.898 +0	3.425 -1
	1.499 +1	7.169 -2		8.061 +0	1.341 -1	
6	5.750 +0	1.769 +0		3.044 +0	1.875 +0	
	7.853 +0	2.426 -1		4.159 +0	4.296 -1	
	2.146 +1	4.902 -2		1.136 +1	9.323 -2	




Filter Design Example

- Low pass five-pole Butterworth filter with a corner frequency of 200Hz and input resistance of 50K Ω
 - Economic Solution = 3rd order + 2nd order
 - Desired R and C ?
 - $C_{1A} = (\omega_0 R_0 C_0) / (\omega R)$
 $= 1 \times 1 \times 1.753 / 2\pi \times 200 \times 50K = 27.9 \text{ nF}$
 - $C_{2A} = 21.6 \text{ nF}$, $C_{3A} = 6.7 \text{ nF}$, $C_{1B} = 51.5 \text{ nF}$, $C_{2B} = 4.9 \text{ nF}$

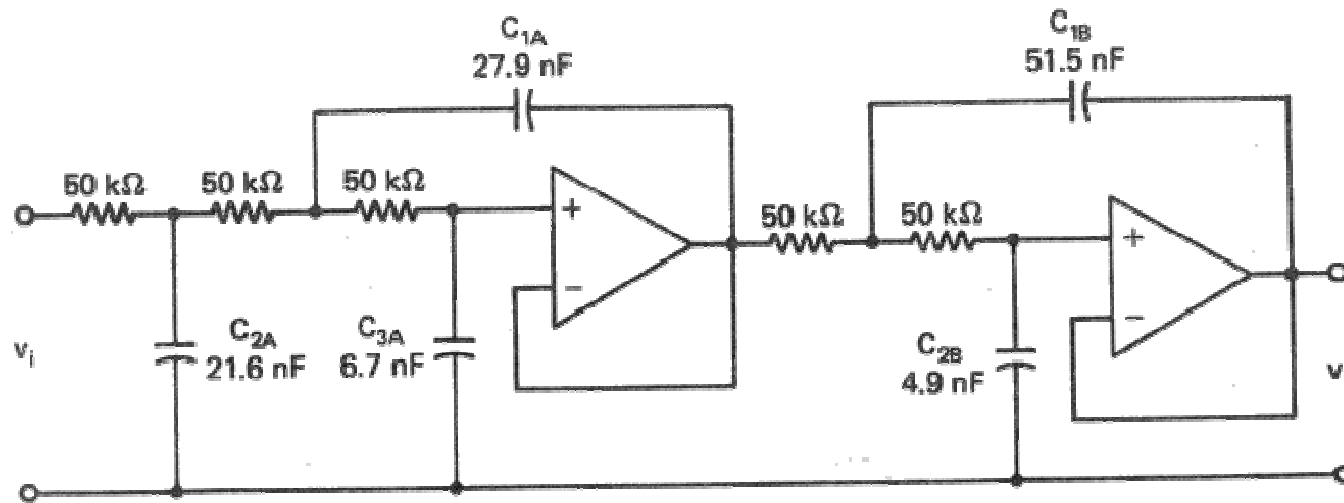

The Electrocardiogram Amplifier

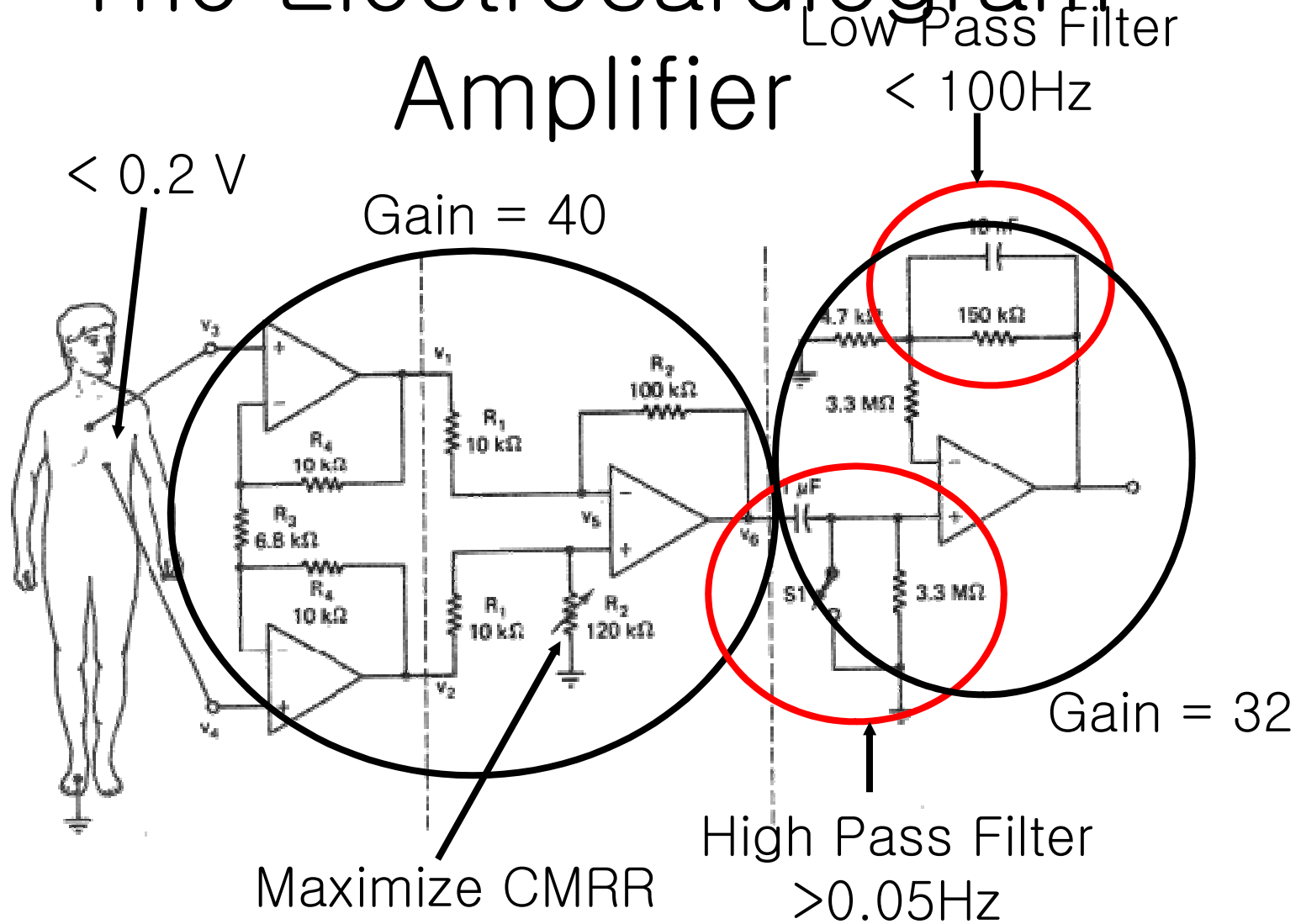

Low Pass Filter

$< 100 Hz$

$< 0.2 V$

Gain = 40

Gain = 32


High Pass Filter

$> 0.05 Hz$

Maximize CMRR



Frequency Stability

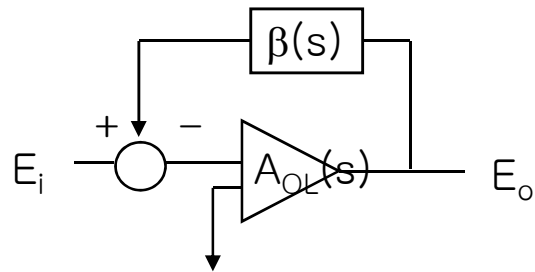

$$A_{CL}(S) = E_o/E_i = A_{OL}(S)/(1 + A_{OL}(s) \beta(s))$$
$$= A_{OL}(s)/(1 + A_L(S))$$

Instability : $A_L(s) = A_{OL}(s)B(s) = 1 \angle 180 = -1$ 일 때.

Critical condition : $A_{OL}(j\omega) = \{1/\beta(j\omega)\} \angle 180$

즉,

$|A_{OL}(j\omega)| = 1/|\beta(j\omega)|$ 이고 $\Phi_{OL} - \Phi_{CL} = 180^\circ$


가 되는 freq.에서 oscillation



Frequency Stability

- 흔히 우리는 $|A_L(j\omega)| = |A_{oL}(j\omega)\beta(j\omega)| = 1$ 이 되는 ω 를 구하고 이 때의 $A_L(j\omega)$ 의 phase를 보아, 이것이 $+180^\circ$ 로부터 떨어진 정도를 측정하며 이를 Φ_M (Phase margin) 이라고 한다.
 - $\Phi_M \sim 90^\circ$ 정도일 때 stable system
 - Φ_M 은 크면 클수록 유리하다.


- OP Amp 의 경우

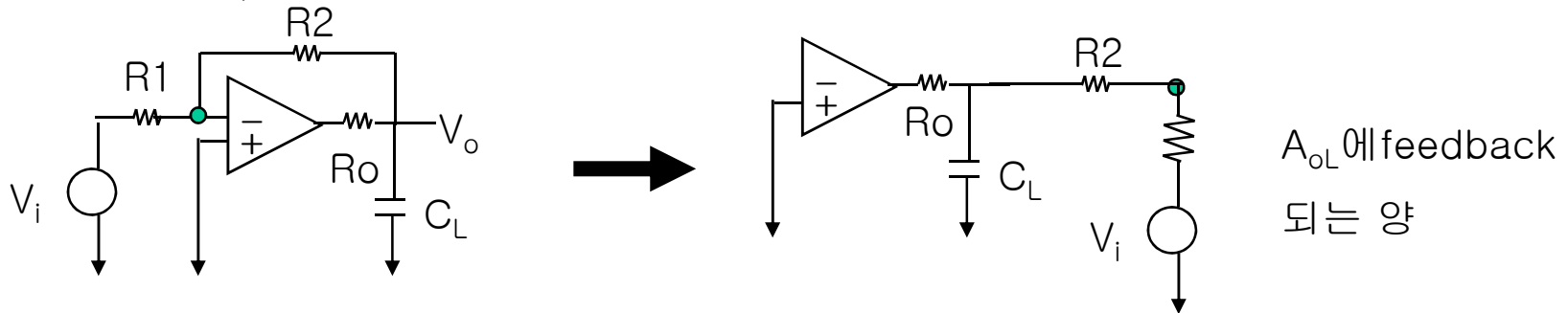

$C_L=0$, V_i 가 없을 때,
 $\beta = R_1/(R_o+R_2+R_1) \approx R_1/(R_2+R_1)$
 즉 $A_{oL}(j\omega)$ 에 $\beta = R_1/(R_2+R_1)$ 을 곱해 $A_L(j\omega)$ 를 구하고
 이의 Bode Diagram 에서 Φ_M 을 구한다



Frequency Stability

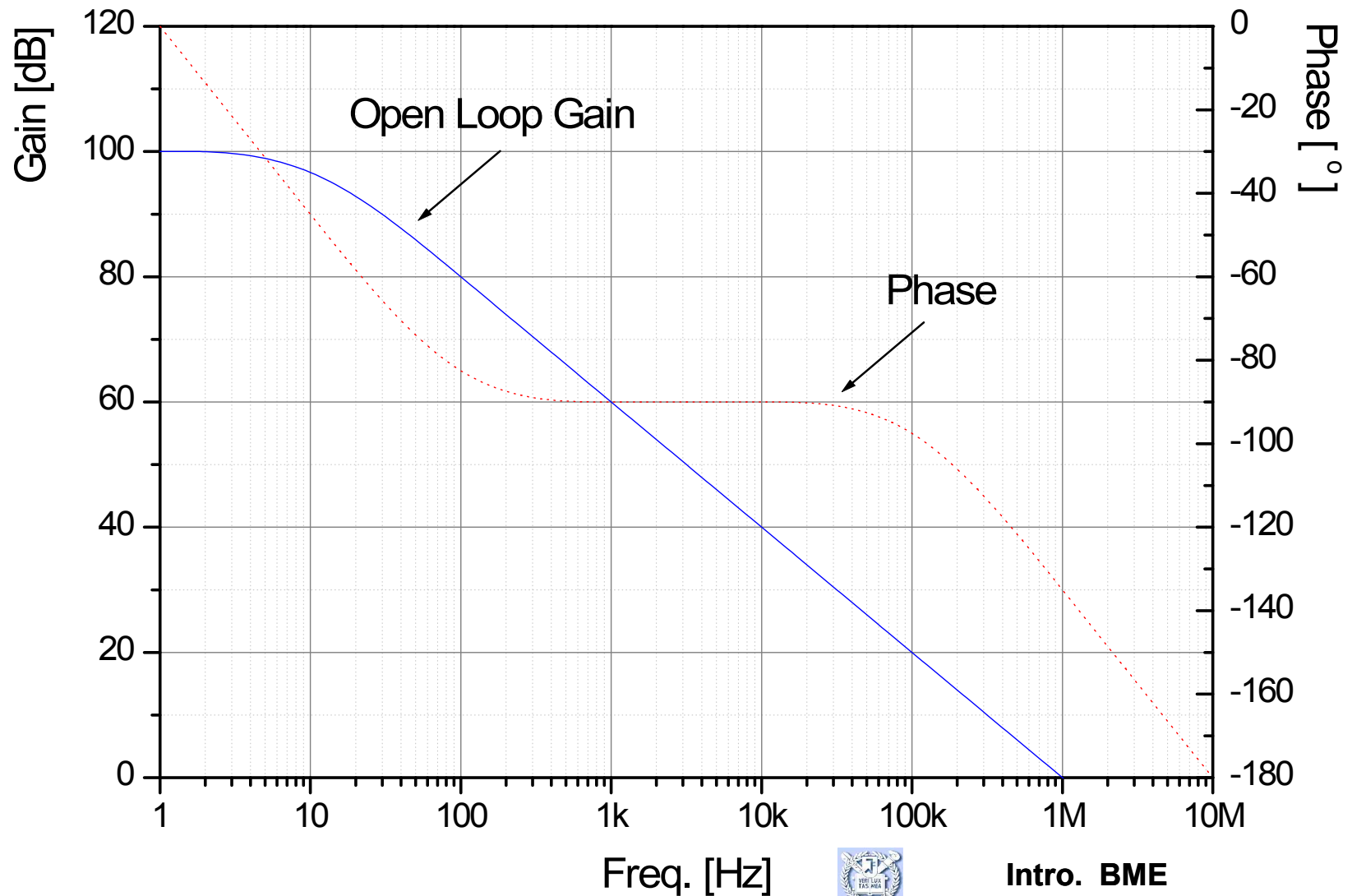


Interference

- Noise : random
- Interference : not random, comes from a known source
- Dominant interference : 60Hz
 - Thru. ① AC capacitive coupling
 ② AC inductive coupling
 ③ Ground loops
 - Solutions
 - (1) Elimination at the source
 - Use of Instrumentation Amps and Isolation Amps.
 - Star Ground (one true ground)
 - (2) (Adaptive) Filtering




Grounding & Instrumentation Amp.

- Ground Loop is a problem.

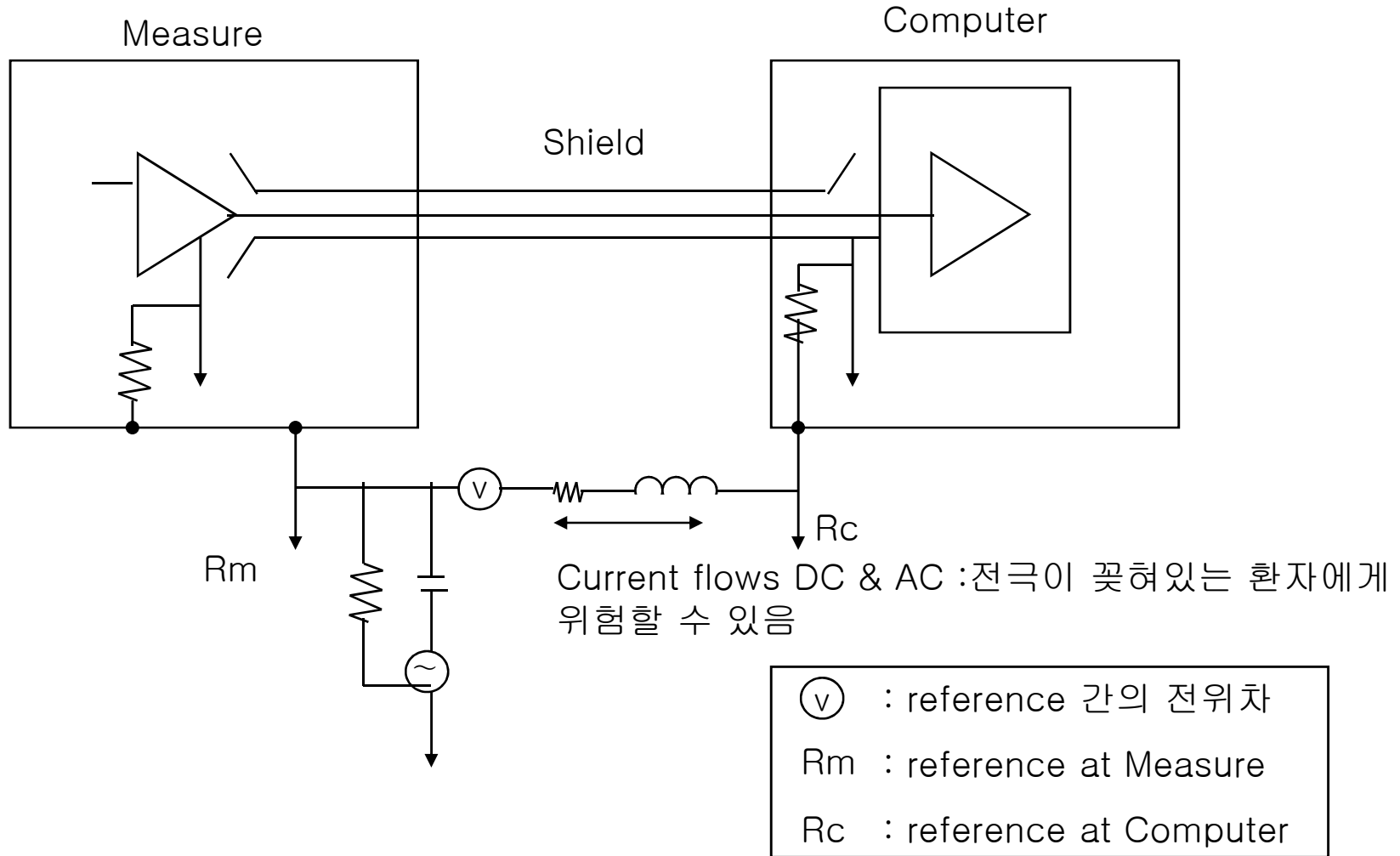

Grounding & Instrumentation Amp.

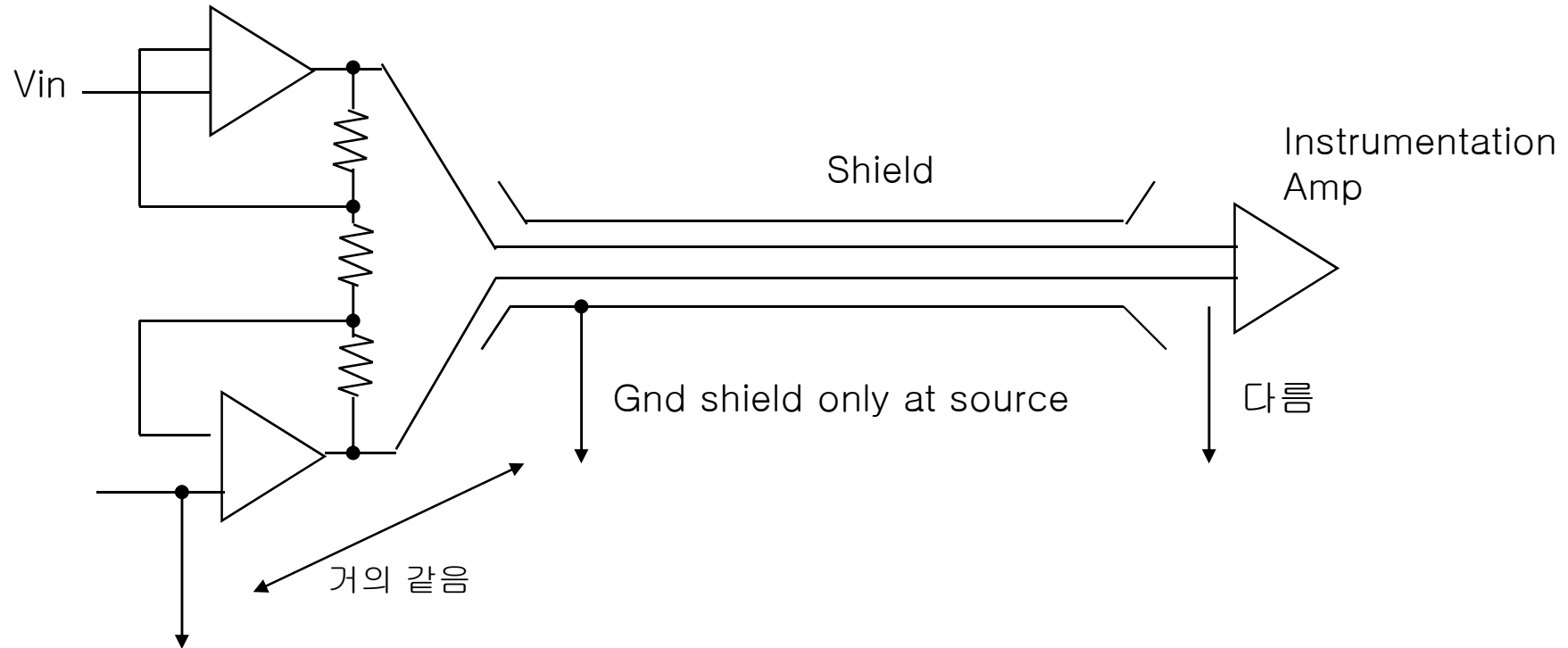- Solution : Differential Transmission :
- Grounding only at source to prevent the group loop.



모든 noise는 common mode로 처리





Grounding & Instrumentation Amp.

- Ground Loop => safety
ECG 측정시 ground loop current는 전극이 꽂혀있는 환자를 통하여 흐르게 되므로 위험
- Bias current => safety
특별히 I_B 가 작은 소자
Ex) AD55L max $I_B = 75\text{fA}$
AD00L max $I_B = 10\text{fA}$



Grounding & Instrumentation Amp.

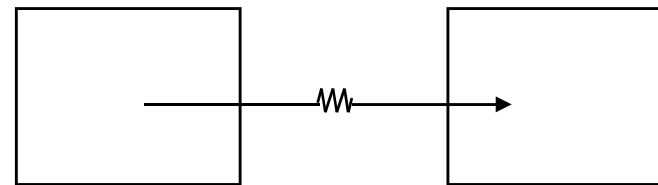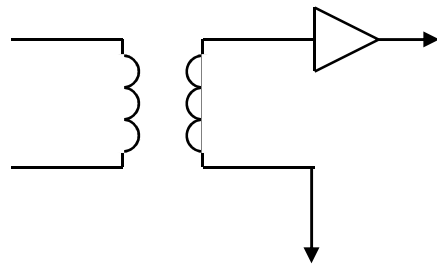- Solution(II) : Isolation between Measure and Computer stations.
 - By transformer



Optics, RF

- Optical coupling : optical isolator : (LED/LD)–PD 조합
- Radio link
 - Signal – Modulator – Transmitter ...– Receiver – Demodulator





Low Cost, Miniature Isolation Amplifiers

AD202/AD204

FEATURES

- Small Size: 4 Channels/Inch
- Low Power: 35 mW (AD204)
- High Accuracy: $\pm 0.025\%$ max Nonlinearity (K Grade)
- High CMR: 130 dB (Gain = 100 V/V)
- Wide Bandwidth: 5 kHz Full-Power (AD204)
- High CMV Isolation: ± 2000 V pk Continuous (K Grade) (Signal and Power)

Isolated Power Outputs

Uncommitted Input Amplifier


APPLICATIONS

- Multichannel Data Acquisition
- Current Shunt Measurements
- Motor Controls
- Process Signal Isolation
- High Voltage Instrumentation Amplifier

GENERAL DESCRIPTION

The AD202 and AD204 are general purpose, two-port, transformer-coupled isolation amplifiers that may be used in a broad range of applications where input signals must be measured, these industry standard isolation amplifiers offer a complete isolation function, with both signal and power isolation provided

FUNCTIONAL BLOCK DIAGRAM

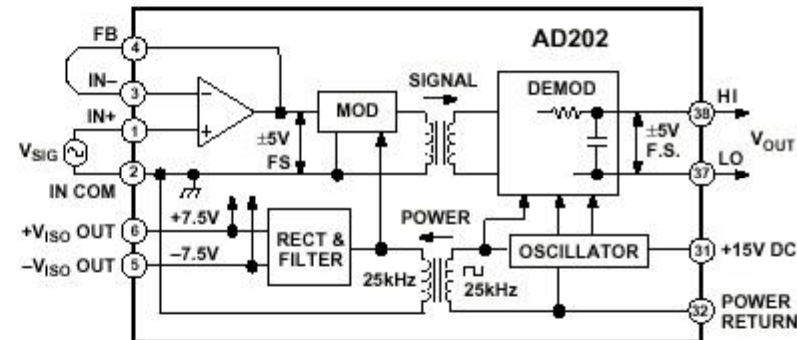

Isolation mode rejection ratio(IMRR):105dB@60Hz

ing. For applications requiring a low profile, the DIP package provides a height of just 0.350".

High Accuracy: With a maximum nonlinearity of $\pm 0.025\%$ for the AD202K/AD204K ($\pm 0.05\%$ for the AD202J/AD204J) and low drift over temperature, the AD202 and AD204 provide high isolation without loss of signal integrity.

Low Power: Power consumption of 35 mW (AD204) and 75 mW (AD202), over the full signal range makes these isolators power budgets.



Intro. BME