

## 2. Wave Propagation on Transmission Lines

### A. General Solutions of Transmission-Line Equations

#### 1) Wave solutions in the phasor domain

For uniform transmission lines with time-harmonic variation  $e^{j\omega t}$ ,  
Transmission-line equations:

$$\frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) = 0 \quad (8-10)$$

$$\frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) = 0 \quad (8-11)$$

$$\text{where } \gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{ZY} \quad (\text{m}^{-1}) \quad (8-12)$$

$$\alpha = \text{Re}[\sqrt{(R + j\omega L)(G + j\omega C)}] \quad (\text{Np/m}) \quad (8-12a)$$

$$\beta = \text{Im}[\sqrt{(R + j\omega L)(G + j\omega C)}] \quad (\text{rad/m}) \quad (8-12b)$$

General solutions of (8-10, 11):

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z} \quad (\text{V}) \quad (8-33, 62)$$

$$I(z) = I_o^+ e^{-\gamma z} + I_o^- e^{+\gamma z} \quad (\text{A}) \quad (8-34, 63)$$

where unknown amplitudes ( $V_o^+$ ,  $V_o^-$ ,  $I_o^+$ ,  $I_o^-$ ) are to be determined by BCs.

Generally,  $V_o^+$ ,  $V_o^-$ ,  $I_o^+$ ,  $I_o^-$  are complex quantities, like  $V_o^\pm = |V_o^\pm| e^{j\phi^\pm}$

(8-33) in (8-8):

$$I(z) = \frac{\gamma}{(R + j\omega L)} [V_o^+ e^{-\gamma z} - V_o^- e^{+\gamma z}] \quad (8-34)*$$

#### 2) Characteristic impedance

Comparison of (8-34)\* with (8-34) leads to

$$\frac{V_o^+}{I_o^+} = -\frac{V_o^-}{I_o^-} = \frac{R + j\omega L}{\gamma} \equiv Z_o = R_o + jX_o \quad (8-35, 64)$$

Define the **Characteristic Impedance**  $Z_o$  of the transmission line by

$$Z_o = \frac{R + j\omega L}{\gamma} = \frac{\gamma}{G + j\omega C} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{Z}{Y}} \quad (\Omega) \quad (8-38)$$

*Notes)*

- i)  $Z_o$  and  $\gamma$  are independent of  $z$  and the length of the line, but depends only on distributed parameters ( $R$ ,  $L$ ,  $G$ ,  $C$ ) and frequency ( $\omega$ ).
- ii) Phasor solution in terms of  $Z_o$  from (8-34)\*:

$$I(z) = \frac{V_o^+}{Z_o} e^{-\gamma z} - \frac{V_o^-}{Z_o} e^{+\gamma z} \quad (8-34)**$$

iii) Instantaneous wave solutions in the cosine-reference time domain:

$$\begin{aligned}
 v(z,t) &= \text{Re}[V(z)e^{j\omega t}] = \text{Re}[(V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z})e^{j\omega t}] \\
 &= \text{Re}[|V_o^+| e^{j\omega t - (\alpha + j\beta)z + j\phi^+} + |V_o^-| e^{j\omega t + (\alpha + j\beta)z + j\phi^-}] \\
 &= |V_o^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi^+) + |V_o^-| e^{\alpha z} \cos(\omega t + \beta z + \phi^-) \quad (8-33)* \\
 &\quad \text{FTW}(\omega\beta < 0: +z \text{ direction}) \quad \text{BTW}(\omega\beta > 0: -z \text{ direction}) \\
 &\quad \text{attenuation of } +z \text{ propagating wave} \quad \text{attenuation of } -z \text{ propagating wave}
 \end{aligned}$$

$$\begin{aligned}
 i(z,t) &= \text{Re}\left[\left(\frac{V_o^+}{Z_o} e^{-\gamma z} - \frac{V_o^-}{Z_o} e^{+\gamma z}\right)e^{j\omega t}\right] = \text{Re}\left[\left(\frac{V_o^+}{|Z_o|} e^{-\gamma z} - \frac{V_o^-}{|Z_o|} e^{+\gamma z}\right)e^{j\omega t}\right] \\
 &= \frac{|V_o^+|}{|Z_o|} e^{-\alpha z} \cos(\omega t - \beta z + \phi^+ - \phi_{Z_o}) - \frac{|V_o^-|}{|Z_o|} e^{\alpha z} \cos(\omega t + \beta z + \phi^- - \phi_{Z_o}) \quad (8-34)***
 \end{aligned}$$

iv) Phase velocity:  $u_p = \frac{\omega}{\beta} = \frac{\omega}{k} = f\lambda$  (7-10, 50, 58)

## B. Wave Characteristics on an *Infinite* Transmission Line

### 1) Wave solutions

For an *infinite* uniform transmission line,  $\exists$  no reflection waves (BTW).

Then,  $V(z) = V^+(z) = V_o^+ e^{-\gamma z}$  (8-36)

$$I(z) = I^+(z) = I_o^+ e^{-\gamma z} = \frac{V_o^+}{Z_o} e^{-\gamma z} \quad (8-37)$$

or  $v(z,t) = |V_o^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi^+)$  (8-36)\*

$$i(z,t) = \frac{|V_o^+|}{|Z_o|} e^{-\alpha z} \cos(\omega t - \beta z + \phi^+ - \phi_{Z_o}) \quad (8-37)*$$

$\Rightarrow$  The transmission line is characterized by two fundamental properties,  $\gamma$  and  $Z_o$  which are specified by R, L, G, C, and  $\omega$ .

### 2) Characteristics in the *lossless* line

For lossless ( $R=0, G=0$ ) or high frequency ( $\omega L \gg R, \omega C \gg G$ ),

#### a) Propagation constant

$$(8-12) \Rightarrow \gamma = \alpha + j\beta = j\omega \sqrt{LC} \quad (8-39)$$

i.e.,  $\alpha = 0$  (no attenuation),  $\beta = \omega \sqrt{LC}$  (8-40, 41)

(cf) For lossless unbounded medium,  $\gamma = jk, k = \beta = \omega \sqrt{\mu\epsilon}$  (7-4, 42)

#### b) Characteristic impedance

$$(8-38) \Rightarrow Z_o = R_o + jX_o = \sqrt{L/C} \quad (8-43)$$

i.e.,  $R_o = \sqrt{L/C}$  (constant),  $X_o = 0$  (8-44, 45)

(cf) For lossless unbounded medium,  $\eta = \sqrt{\mu/\epsilon}$  (7-14)

c) Phase velocity

$$(8-41) \text{ in } (7-50) \Rightarrow u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} \quad (\text{constant: ind. of } f) \quad (8-42)$$

$\Rightarrow$  Distortionless (or nondispersive) line

$$(cf) \text{ For lossless unbounded medium, } u_p = \frac{1}{\sqrt{\mu\epsilon}} = \frac{c}{\sqrt{\mu_r\epsilon_r}}$$

3) Characteristics in the **distortionless lossy** line

$$\text{For the (distortionless) condition of } \frac{R}{L} = \frac{G}{C} \quad (8-46)$$

a) Propagation constant

$$(8-46) \text{ in } (8-12) \Rightarrow \gamma = \alpha + j\beta = \sqrt{C/L} (R + j\omega L) \quad (8-47)$$

$$\text{i.e., } \alpha = R\sqrt{C/L} \quad (\text{attenuation}), \quad \beta = \omega\sqrt{LC} \quad (8-48, 49)$$

b) Characteristic impedance

$$(8-46) \text{ in } (8-38) \Rightarrow Z_o = R_o + jX_o = \sqrt{L/C} \quad (8-51)$$

$$\text{i.e., } R_o = \sqrt{L/C} \quad (\text{constant}), \quad X_o = 0 \quad (8-52, 53)$$

c) Phase velocity

$$(8-49) \text{ in } (7-50) \Rightarrow u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} \quad (\text{constant: ind. of } f) \quad (8-42)$$




$\Rightarrow$  Distortionless (or nondispersive) lossy line

4) Characteristics in the **lossy** line

For the lossy transmission line,

$$(8-12), (8-38), (7-50) \Rightarrow \text{All of } \gamma, \alpha, \beta, Z_o \text{ are functions of } f$$

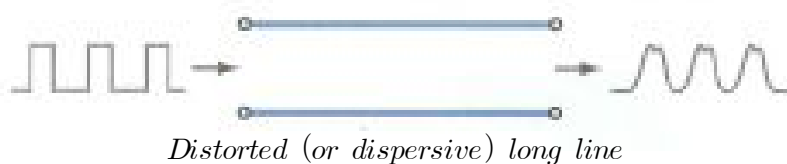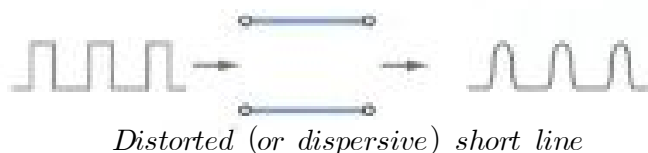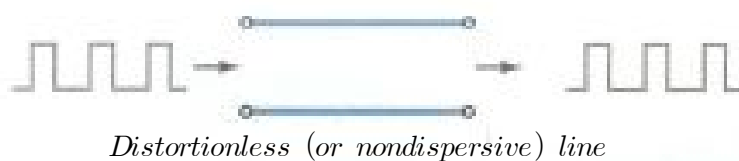$\Rightarrow$  **Distorted (or dispersive) lossy** line



For small losses ( $\omega L \gg R$ ,  $\omega C \gg G$ )

$$(8-38) : Z_o = \sqrt{\frac{j\omega L \left( \frac{-jR/\omega L + 1}{-jG/\omega C + 1} \right)}{j\omega C}} \cong \sqrt{\frac{L}{C}} \left( 1 - \frac{1}{2} j \frac{R}{\omega L} \right) \left( 1 + \frac{1}{2} j \frac{G}{\omega C} \right)$$


$$\cong \sqrt{\frac{L}{C}} \left[ 1 + j \left( \frac{G}{2\omega C} - \frac{R}{2\omega L} \right) \right] = R_o + jX_o = |Z_o| \angle \phi_{Z_o} \quad (8-51)^*$$

In most practical transmission lines of good conductors and very low leakage dielectrics,

$$\frac{G}{C} < \frac{R}{L} \text{ in (8-51)*} \Rightarrow X_o < 0 \text{ (capacitive reactance)}$$

Therefore, from (8-36) and (8-37),

$$V(z) = Z_o I(z) = (R_o - j|X_o|) I(z)$$
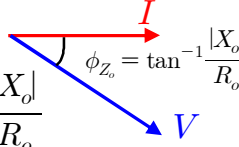
$$\Rightarrow V(z) \text{ lags behind } I(z) \text{ by } \phi_{Z_o} = \tan^{-1} \frac{|X_o|}{R_o}$$


### Attenuation constant from power relation

From (8-36) and (8-37),

$$V(z) = V_o e^{-(\alpha + j\beta)z}, \quad I(z) = \frac{V_o}{Z_o} e^{-(\alpha + j\beta)z} \quad (8-54, 55)$$

Time-average power along the line (like time-ave Poynting vector 7-79):

$$P(z) = \mathcal{P}_{av}(z) = \frac{1}{2} \text{Re}[V(z)I^*(z)] = \frac{V_o^2 e^{-2\alpha z}}{2} \text{Re}\left[\frac{1}{Z_o}\right]$$

$$= \frac{V_o^2 e^{-2\alpha z}}{2} \text{Re}\left[\frac{1}{R_o + jX_o}\right] = \frac{V_o^2 e^{-2\alpha z}}{2} \text{Re}\left[\frac{R_o - jX_o}{R_o^2 + X_o^2}\right] = \frac{V_o^2 R_o e^{-2\alpha z}}{2|Z_o|^2} \quad (8-56)$$

From energy conservation law,

Decrease rate of  $P(z)$  along  $z$  = Time-ave. power loss per length

$$-\frac{\partial P(z)}{\partial z} = P_L(z) \stackrel{(8-56)}{\Rightarrow} 2\alpha P(z) = P_L(z),$$

from which the attenuation constant can be found by

$$\alpha = \frac{P_L(z)}{2P(z)} \quad (\text{Np/m}) \quad (8-57)$$

For lossy line,  $P_L(z) = (1/2)(I^2 R + V^2 G) \stackrel{(8-54, 55)}{=} (V_o^2 / 2|Z_o|^2) (R + G|Z_o|^2) e^{-2\alpha z}$  (8-58)

$$(8-58) \text{ in } (8-57) : \alpha = \frac{1}{2R_o} (R + G|Z_o|^2) \quad (8-59)$$


For a low loss line with  $Z_o \cong R_o = \sqrt{L/C}$ ,

$$(8-59) \text{ becomes } \alpha \cong \frac{1}{2} (R\sqrt{C/L} + G\sqrt{L/C}) \quad (\text{cf } (7-47)) \quad (8-60)$$

For a distortionless lossy line with  $Z_o = R_o = \sqrt{L/C}$  using (8-46),

$$(8-60) \text{ yields } \alpha = R\sqrt{\frac{C}{L}} \quad (8-61) = (8-48)$$
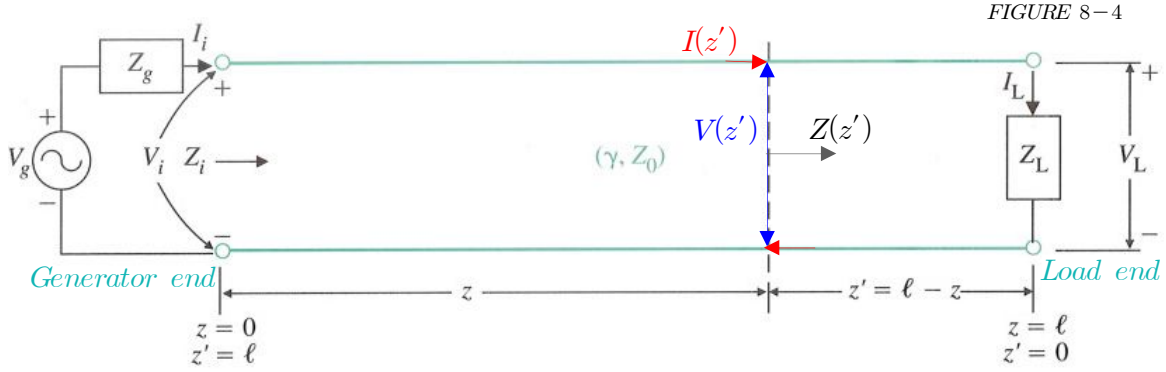
## B. Wave Characteristics on Finite (Terminated) Transmission Lines



### 1) General solutions

For **finite** uniform transmission lines,  $\exists$  reflection waves (BTW).

General solutions of (8-10, 11):

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z} \quad (8-33, 62)$$

$$I(z) = I_o^+ e^{-\gamma z} + I_o^- e^{+\gamma z} = Z_o^{-1} [V_o^+ e^{-\gamma z} - V_o^- e^{+\gamma z}] \quad (8-34, 63)$$

↑ FTW      ↑ BTW (reflected wave)

where  $\frac{V_o^+}{I_o^+} = -\frac{V_o^-}{I_o^-} \equiv Z_o = R_o + jX_o$  : characteristic impedance (8-64)

BCs : (8-62, 63) at the load end ( $z=l$ ) using (8-64),

$$V_L = V_o^+ e^{-\gamma l} + V_o^- e^{+\gamma l}, \quad I_L = \frac{V_o^+}{Z_o} e^{-\gamma l} - \frac{V_o^-}{Z_o} e^{+\gamma l} \quad (8-66, 67)$$

Solution of (8-66, 67) in (8-62, 63) with change of variable  $z' = l - z$ ,

$$V(z') = \frac{I_L}{2} [(Z_L + Z_o) e^{\gamma z'} + (Z_L - Z_o) e^{-\gamma z'}] = \frac{I_L}{2} (Z_L + Z_o) e^{\gamma z'} [1 + \Gamma e^{-2\gamma z'}] \quad (8-72, 87)$$

$$= I_L (Z_L \cosh \gamma z' + Z_o \sinh \gamma z') \quad (8-74)$$

$$I(z') = \frac{I_L}{2Z_o} [(Z_L + Z_o) e^{\gamma z'} - (Z_L - Z_o) e^{-\gamma z'}] = \frac{I_L}{2Z_o} (Z_L + Z_o) e^{\gamma z'} [1 - \Gamma e^{-2\gamma z'}] \quad (8-73, 89)$$

$$= \frac{I_L}{Z_o} (Z_L \sinh \gamma z' + Z_o \cosh \gamma z') \quad (8-75)$$

where  $\Gamma \equiv \frac{V_o^-}{V_o^+} = \frac{Z_L - Z_o}{Z_L + Z_o} = |\Gamma| e^{j\theta_\Gamma} =$  (voltage) reflection coeff. of  $Z_L$  (8-88)

: complex value with  $|\Gamma| \leq 1$

Notes)

i) Current reflection coeff.  $\equiv \frac{I_o^-}{I_o^+} = -\Gamma$  (out of phase) (8-63, 88)

ii) For  $Z_L = Z_o$ ,  $\Gamma = 0$  and  $V_o^- = 0$  (no reflection wave)

$\Rightarrow$  The transmission line is said to be **matched** to the load.

- iii) For an **open-circuit** line ( $Z_L \rightarrow \infty$ ),  $\Gamma = 1$  and  $V_o^- = V_o^+$  (in phase)
- iv) For a **short-circuit** line ( $Z_L = 0$ ),  $\Gamma = -1$  and  $V_o^- = -V_o^+$  (out of phase)
- v) For  $Z_L \neq Z_o$ ,  $\exists$  standing voltage and current waves along the line,

standing-wave ratio (SWR):  $S = \frac{|V_{\max}|}{|V_{\min}|} = \frac{1+|\Gamma|}{1-|\Gamma|}$  or  $20\log_{10} S$  in (dB) (8-90)

$$\Rightarrow |\Gamma| = \frac{S-1}{S+1} \quad (8-87) \quad (8-91)$$

$|\Gamma| = 0$  : *matched*  $\swarrow$   
 $1 \leq S < \infty$   $\nearrow$   $|\Gamma| = 1$  : *o.c.* or *s.c.*

- vi) For a **lossless** ( $\alpha = 0, X_o = 0$ ;  $\gamma = j\beta, Z_o = R_o$ ) line, (8-87, 89) become

$$V(z') = \frac{I_L}{2}(Z_L + R_o)e^{j\beta z'} [1 + |\Gamma|e^{j(\theta_r - 2\beta z')}] \quad (8-92)$$

$$I(z') = \frac{I_L}{2R_o}(Z_L + R_o)e^{j\beta z'} [1 - |\Gamma|e^{j(\theta_r - 2\beta z')}] \quad (8-93)$$

## 2) Input impedance


**Impedance**  $Z(z')$  looking toward the load end at  $z'$  from the load:

$$Z(z') \equiv \frac{V(z')}{I(z')} = Z_o \frac{Z_L + Z_o \tanh \gamma z'}{Z_o + Z_L \tanh \gamma z'} = Z_o \frac{1 + \Gamma e^{-2\gamma z'}}{1 - \Gamma e^{-2\gamma z'}} \quad (\Omega) \quad (8-77)$$

$\frac{(8-74)}{(8-75)} \quad \swarrow \quad \searrow \quad \frac{(8-87)}{(8-89)}$

**Input impedance**  $Z_i$  looking into the line from the source at  $z' = l$ :
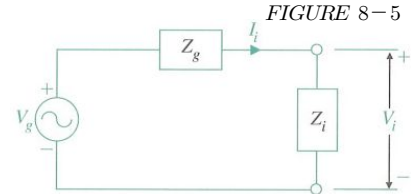
$$Z_i \equiv \frac{V_i}{I_i} = (Z)_{z'=l, z=0} = Z_o \frac{Z_L + Z_o \tanh \gamma l}{Z_o + Z_L \tanh \gamma l} = Z_o \frac{1 + \Gamma e^{-2\gamma l}}{1 - \Gamma e^{-2\gamma l}} \quad (8-78)$$



Note) When  $Z_L = Z_o$ ,  $Z_i = Z_o$  irrespective of the length  $l$

$\Rightarrow$  The transmission line is **matched**

For a **lossless** ( $\alpha = 0, X_o = 0$ ;  $\gamma = j\beta, Z_o = R_o$ ) line, (8-78) become

$$Z_i = R_o \frac{Z_L + jR_o \tan \beta l}{R_o + jZ_L \tan \beta l} \quad (8-79)$$

From the standpoint of the generator circuit,

$$V_i = Z_i I_i = \frac{Z_i V_g}{Z_g + Z_i} = V_g - I_i Z_g \quad (8-94)$$

If  $Z_L \neq Z_o$  but  $Z_g = Z_o$ , reflected at the load and ending at the generator

If  $Z_L \neq Z_o$  but  $Z_g \neq Z_o$ , reflected at both the load and generator

repeating indefinitely

### 3) Standing waves

For lossless lines ( $\gamma = j\beta$ ), (8-62, 63) with (8-88) becomes


$$V(z') = V_o^+ (e^{j\beta z'} + \Gamma e^{-j\beta z'}) \quad (8-62)^*$$

$$I(z') = \frac{V_o^+}{Z_o} (e^{j\beta z'} - \Gamma e^{-j\beta z'}) \quad (8-63)^*$$

Polar expression of (8-88) in (8-62)\* using  $|V(z')| = [V(z')V^*(z')]^{1/2}$  gives

$$\begin{aligned} |V(z')| &= \{ [V_o^+ (e^{j\beta z'} + |\Gamma| e^{j\theta_\Gamma} e^{-j\beta z'})] \cdot [(V_o^+)^* e^{-j\beta z'} + |\Gamma| e^{-j\theta_\Gamma} e^{j\beta z'}] \}^{1/2} \\ &= |V_o^+| [1 + |\Gamma|^2 + |\Gamma| (e^{j(2\beta z' - \theta_\Gamma)} + e^{-j(2\beta z' - \theta_\Gamma)})]^{1/2} \\ &= |V_o^+| [1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta z' - \theta_\Gamma)]^{1/2} \quad (8-62)^{**} \end{aligned}$$

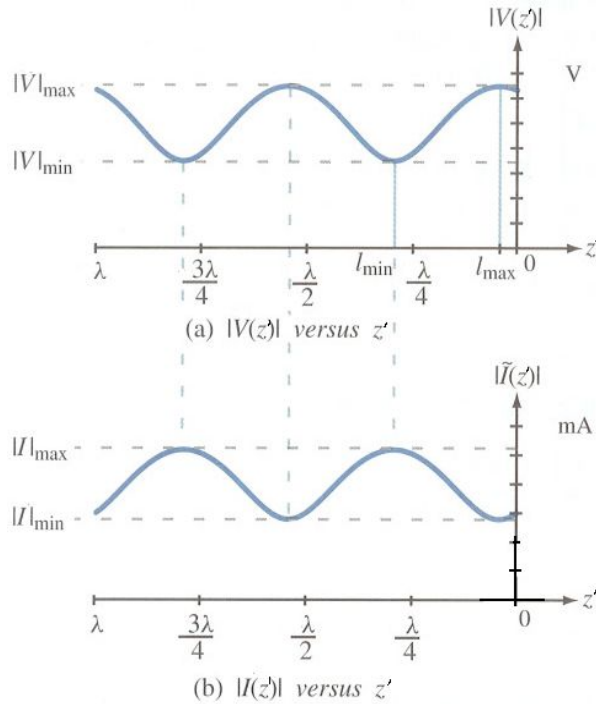$\Rightarrow$  **Standing-wave pattern** resulted from interference of incid. and reflec. waves



$$|V|_{\max} = |V_o^+| (1 + |\Gamma|) \quad (3)$$

$$\text{when } \cos(2\beta z'_{\max} - \theta_\Gamma) = 1 \quad \Rightarrow \quad 2\beta z'_{\max} - \theta_\Gamma = 2n\pi$$

$$\Rightarrow z'_{\max} = (\theta_\Gamma + 2n\pi) / 2\beta = \left( \frac{\theta_\Gamma}{4\pi} + \frac{n}{2} \right) \lambda \quad \text{for } \begin{cases} n = 1, 2, \dots & \text{for } \theta_\Gamma < 0 \\ n = 0, 1, 2, \dots & \text{for } \theta_\Gamma > 0 \end{cases} \quad (4)$$

$$|V|_{\min} = |V_o^+| (1 - |\Gamma|) \quad -\pi \leq \theta_\Gamma \leq \pi, \quad \beta = 2\pi/\lambda \quad (5)$$

$$\text{when } \cos(2\beta z'_{\min} - \theta_\Gamma) = -1 \quad \Rightarrow \quad 2\beta z'_{\min} - \theta_\Gamma = (2n+1)\pi$$


$$\Rightarrow z'_{\min} = \left( \frac{\theta_\Gamma}{4\pi} + \frac{2n+1}{4} \right) \lambda \quad n = 0, 1, 2, \dots \quad (6)$$

$$\text{1st minimum position } (n=0): \quad l_{\min} = \left( \frac{\theta_\Gamma}{\pi} + 1 \right) \frac{\lambda}{4} \quad (7)$$



$$\text{1st maximum position } (n=0 \text{ or } 1): \quad l_{\max} = \frac{\theta_\Gamma \lambda}{4\pi} \quad \text{or} \quad \frac{\theta_\Gamma \lambda}{4\pi} + \frac{\lambda}{2} \quad (8)$$

Using  $|z'_{\min} - z'_{\max}| = \lambda/4$ ,

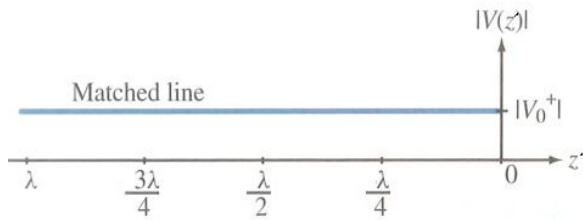
$$l_{\min} = \begin{cases} l_{\max} + \lambda/4 & \text{for } l_{\max} < \lambda/4 \\ l_{\max} - \lambda/4 & \text{for } l_{\max} \geq \lambda/4 \end{cases} \quad (9)$$



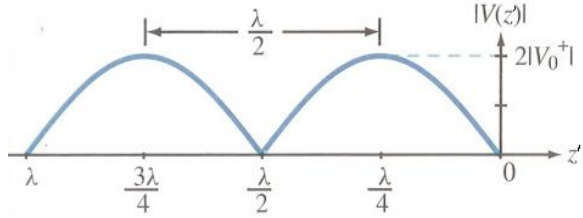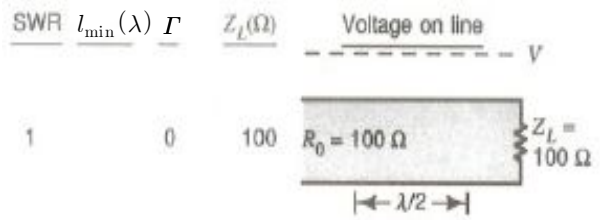(a)  $Z_L = Z_0$  (matched line) :  $\Gamma = 0$



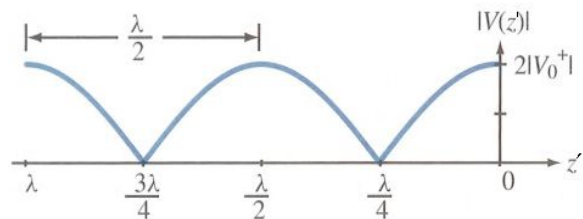
(b)  $Z_L = 0$  (short circuit) :  $\Gamma = -1$



(c)  $Z_L = \infty$  (open circuit) :  $\Gamma = 1$



Determination SWR,  $|\Gamma|$ ,  $\theta_\Gamma$  and  $Z_L$  by a slotted-line probe:

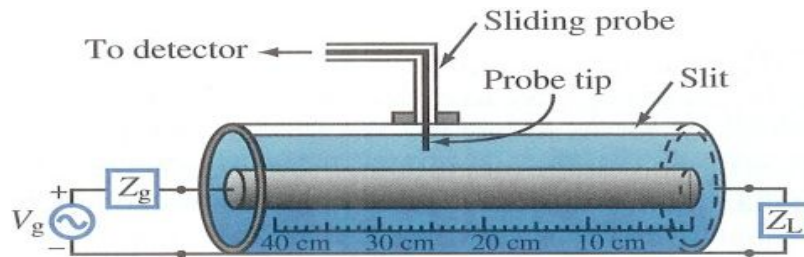

Measurements of  $|V_{\max}|$ ,  $|V_{\min}|$ , and  $l_{\min}$

$$\Rightarrow \text{Determine } S \text{ and } |\Gamma| \text{ from } S = \frac{|V_{\max}|}{|V_{\min}|} \quad (8-90), \quad |\Gamma| = \frac{S-1}{S+1} \quad (8-91)$$

$$\theta_\Gamma \text{ from } l_{\min} = \left( \frac{\theta_\Gamma}{\pi} + 1 \right) \frac{\lambda}{4} \quad (7)$$

$$\Gamma \text{ and } Z_L \text{ from } \Gamma = |\Gamma| e^{j\theta_\Gamma} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (8-88)$$

(e.g. 8-5) For a lossless terminated transmission line,

given  $Z_0 = R_o = 50 (\Omega)$ ,  $S = 3$ ,  $l_{\min} = 5$  (cm), volt. min. dist. = 20 (cm)

a)  $\Gamma = ?$  and b)  $Z_L = ?$

a)  $\lambda = 2 \times 0.2 = 0.4$ ,  $|\Gamma| = (3-1)/(3+1) = 0.5$

$$l_{\min} = \left( \frac{\theta_\Gamma}{\pi} + 1 \right) \frac{\lambda}{4} \Rightarrow \theta_\Gamma = \pi(4l_{\min}/\lambda - 1) = \pi(4 \times 0.05/0.4 - 1) = -\pi/2$$


$$\therefore \underline{\Gamma = |\Gamma| e^{j\theta_\Gamma} = 0.5 e^{-j\pi/2} = -j0.5}$$

b)  $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \Rightarrow -j0.5 = \frac{Z_L - 50}{Z_L + 50} \Rightarrow \underline{Z_L = 30 - j40 (\Omega)}$



4) Characteristics in **lossless** finite lines ( $\alpha = 0, X_o = 0; \gamma = j\beta, Z_o = R_o$ )

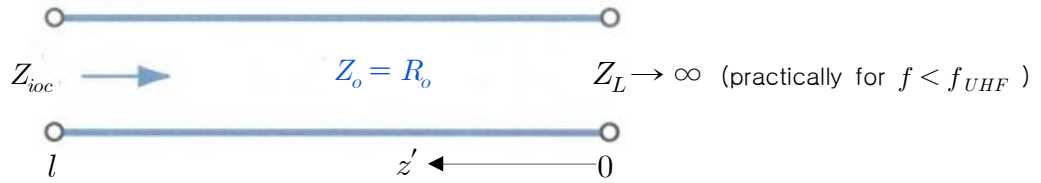a) **Open-circuited** line ( $Z_L \rightarrow \infty, \Gamma = 1, S \rightarrow \infty$ )




$$(8-62)* \Rightarrow V_{oc}(z') = V_o^+(e^{j\beta z'} + e^{-j\beta z'}) = 2V_o^+ \cos \beta z' \quad (8-62)*_{oc}$$

$$(8-63)* \Rightarrow I_{oc}(z') = \frac{V_o^+}{R_o} (e^{j\beta z'} - e^{-j\beta z'}) = \frac{2jV_o^+}{R_o} \sin \beta z' \quad (8-63)*_{oc}$$


$$(8-79) \Rightarrow Z_{ioc} = \frac{V_{oc}(l)}{I_{oc}(l)} = jX_{ioc} = \frac{-jR_o}{\tan \beta l} = -jR_o \cot \beta l \quad (\text{purely reactive}) \quad (8-80)$$

For very short line ( $\beta l = 2\pi l/\lambda \ll 1$ ),
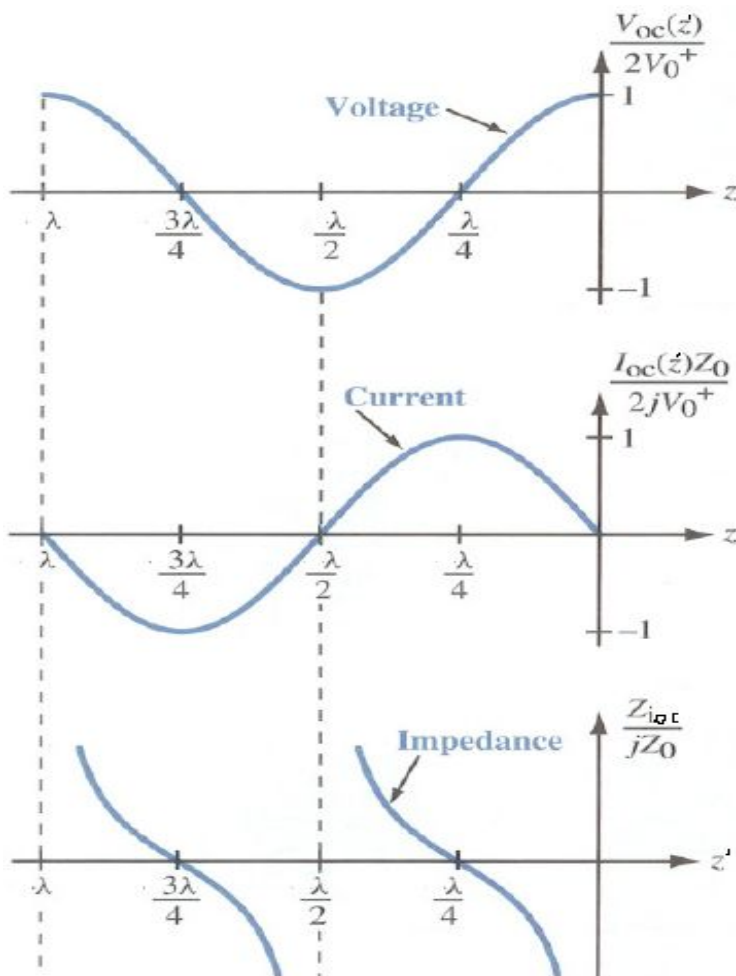
$$Z_{ioc} = jX_{ioc} \cong \frac{-jR_o}{\beta l} = -j \frac{\sqrt{L/C}}{\omega \sqrt{LC}l} = -j \frac{1}{\omega Cl} : \text{capacitively reactive} \quad (8-81)$$



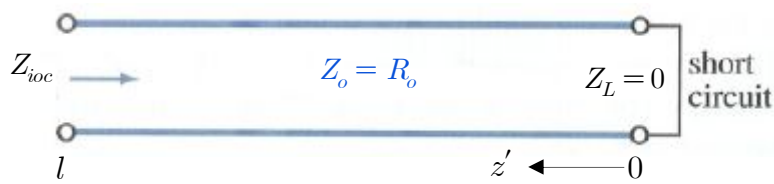b) Short-circuited line ( $Z_L = 0$ ,  $\Gamma = -1$ ,  $S \rightarrow \infty$ )



$$(8-62)* \Rightarrow V_{oc}(z') = V_o^+ (e^{j\beta z'} - e^{-j\beta z'}) = 2jV_o^+ \sin\beta z' \quad (8-62)*_{sc}$$

$$(8-63)* \Rightarrow I_{oc}(z') = \frac{V_o^+}{R_o} (e^{j\beta z'} + e^{-j\beta z'}) = \frac{2V_o^+}{R_o} \cos\beta z' \quad (8-63)*_{sc}$$

$$(8-79) \Rightarrow Z_{isc} = \frac{V_{sc}(l)}{I_{sc}(l)} = jX_{isc} = jR_o \tan\beta l = jR_o \tan\left(\frac{2\pi l}{\lambda}\right) \quad (8-82)$$

$\Rightarrow$  purely reactive (inductive or capacitive depending on  $\tan\beta l$ )


$\Rightarrow$  Proper choice of  $l$  of s.c. line can substitute for inductors and capacitors.

For very short line ( $\beta l = 2\pi l/\lambda \ll 1$ ),

$$Z_{isc} = jX_{isc} \cong jR_o \beta l = j\sqrt{L/C}\omega\sqrt{LC}l = j\omega Ll : \text{inductively reactive} \quad (8-83)$$

For  $\beta l = \pi/2$ , i.e.,  $l = \lambda/4$ ,  $Z_{isc} \rightarrow \infty$

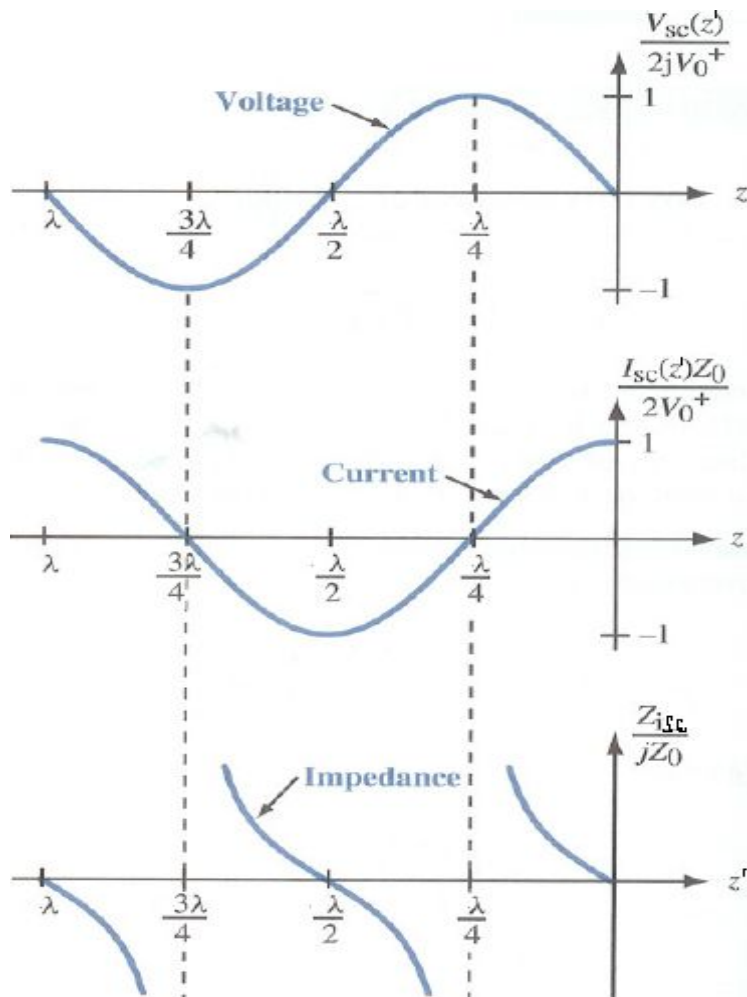$\Rightarrow$  A s.c. quarter-wavelength line is effectively an o.c. line.



### Input impedance of terminated transmission line<sup>†</sup>

Load condition	General case ( $\alpha \neq 0$ )	Lossless case ( $\alpha = 0$ )
Any value of load $Z_L$	$Z_i = Z_0 \frac{Z_L + Z_0 \tanh \gamma x}{Z_0 + Z_L \tanh \gamma x}$	$Z_i = Z_0 \frac{Z_L + jZ_0 \tan \beta x}{Z_0 + jZ_L \tan \beta x}$
Open-circuited line ( $Z_L = \infty$ )	$Z_i = Z_0 \coth \gamma x$	$Z_i = -jZ_0 \cot \beta x$
Short-circuited line ( $Z_L = 0$ )	$Z_i = Z_0 \tanh \gamma x$	$Z_i = jZ_0 \tan \beta x$

<sup>†</sup>  $\gamma = \alpha + j\beta$ , where  $\alpha$  = attenuation constant in nepers per meter,  $\beta = 2\pi/\lambda$  = phase constant in radians per meter, and  $\lambda$  = wavelength.

#### c) Half-wavelength lossless line ( $l = n\lambda/2$ )

For  $l = n\lambda/2$  ( $n = 1, 2, 3, \dots$ ),  $\tan \beta l = \tan\left(\frac{2\pi l}{\lambda}\right) = \tan n\pi = 0$  in (8-79):

$$Z_i = Z_L \quad \text{for } l = n\lambda/2 \quad (n = 1, 2, 3, \dots) \quad (10)$$

⇒ A half-wave lossless line transfers a load impedance to the generator end without change.

⇒ The generator induce the same  $V$  and  $I$  across the load as when the line does not exist there.


#### d) Quarter-wavelength lossless line ( $l = \lambda/4 + n\lambda/2$ )

For  $l = \lambda/4 + n\lambda/2$  ( $n = 0, 1, 2, 3, \dots$ ),

$$\tan \beta l = \tan\left(\frac{2\pi l}{\lambda}\right) = \tan(\pi/2 + n\pi) \rightarrow \infty \quad \text{in (8-79):}$$

$$Z_i = \frac{Z_0^2}{Z_L} \quad \text{for } l = \lambda/4 + n\lambda/2 \quad (n = 0, 1, 2, 3, \dots) \quad (8-111)$$

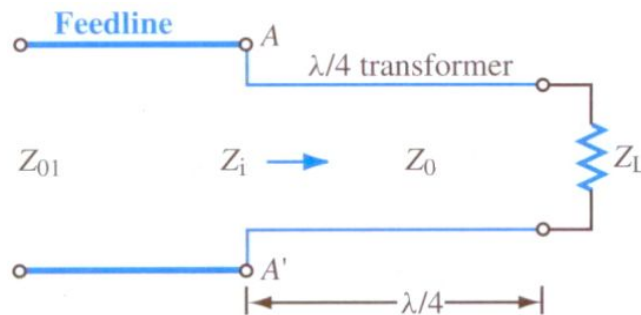⇒ Quarter-wave transformer to eliminate reflections at the load terminal.



If  $Z_i = Z_{01}$ , no reflections at the terminal  $AA'$ .

$$\text{By (8-111), } Z_{01} = Z_0^2 / Z_L \quad \Rightarrow \quad Z_0 = \sqrt{Z_{01} Z_L} \quad (11)$$

Therefore, if a quarter-wave lossless line having a characteristic impedance

of  $Z_0 = \sqrt{Z_{01} Z_L}$  is inserted between the feedline and the load,

there are **no reflections at the terminal** and **all the incident power is transferred into the load**.

e) **Determination of  $Z_o$  and  $\gamma$  by input impedance measurements**

From (8-78)  $Z_i(l) = Z_o \frac{Z_L + Z_o \tanh \gamma l}{Z_o + Z_L \tanh \gamma l}$ ,

$$Z_{ioc} = Z_o \coth \gamma l \text{ for } Z_L \rightarrow \infty \text{ and } Z_{isc} = Z_o \tanh \gamma l \text{ for } Z_L = 0 \quad (8-84a, b)$$

$$\Rightarrow Z_o = \sqrt{Z_{ioc} Z_{isc}} \quad (\Omega) \quad (8-85)$$

$$\gamma = \frac{1}{l} \tanh^{-1} \sqrt{\frac{Z_{isc}}{Z_{ioc}}} \quad (\text{m}^{-1}) \quad (8-86)$$

d) **Power flow along the transmission lines**

Time-average power flow along the line by analogy with (7-79),

$$P(z') = \mathcal{P}_{av}(z') = \frac{1}{2} \text{Re}[V I^*] \quad (12)$$

For lossless lines ( $\gamma = j\beta$ ),

$$V(z') = V_o^+ (e^{j\beta z'} + \Gamma e^{-j\beta z'}) \quad (8-62)*$$

$$I(z') = \frac{V_o^+}{Z_o} (e^{j\beta z'} - \Gamma e^{-j\beta z'}) \quad (8-63)*$$

At the load ( $z' = 0$ ), the incident and reflected waves are

$$V_i(0) = V_o^+, \quad I_i(0) = V_o^+ / Z_o \quad (13)$$

$$V_r(0) = \Gamma V_o^+, \quad I_r(0) = -\Gamma V_o^+ / Z_o \quad (14)$$

(13), (14) in (12) :

$$P_i = \frac{1}{2} \text{Re}[V_o^+ V_o^{+*} / Z_o] = \frac{|V_o^+|^2}{2Z_o} \quad (12)_i$$

$$P_r = \frac{1}{2} \text{Re}[\Gamma V_o^+ (-\Gamma^* V_o^{+*} / Z_o)] = -|\Gamma|^2 \frac{|V_o^+|^2}{2Z_o} \quad (12)_r$$

**Net average power** delivered to the load :

$$P = P_i + P_r = \frac{|V_o^+|^2}{2Z_o} (1 - |\Gamma|^2) \quad (\text{cf } (7-104)) \quad (15)$$

## Homework Set 4

1) P.8-5

2) P.8-7

3) P.8-9

4) P.8-11

5) P.8-13

6) P.8-15