

Embedded System Application

4190.303C

2010 Spring Semester

Power Supply Regulators

Naehyuck Chang
Dept. of EECS/CSE
Seoul National University
naehyuck@snu.ac.kr



Power Supply Overview

- Voltage regulation
 - Remove input noise
 - Ripple voltage
 - IR and inductive drop
 - Device protection
 - Surge protection
 - Maintain operating condition
 - Keep the legal operating range
- Lossless power conversion
 - Change the voltage and the current of power into useful range

Source \ Output	AC	DC
AC	Transformer	Rectifier
DC	Inverter	Switching mode DC-DC converter

Power Supply Overview


- Purpose of power supply
 - Voltage and current requirement of digital systems
 - Voltage ranges from 0.8 V to 5 V
 - Digital circuits need DC supply
 - Some devices requires 12 V or negative voltages
 - Current ranges from a few mili-amperes to hundreds of amperes
 - Multiple voltages are required in most cases
 - Power supplies supply multiple voltages
 - Onboard power supply circuits generate multiple voltages
- Power sources
 - DC sources
 - Batteries, solar panels, fuel cells, super capacitors, etc.
 - AC sources
 - Outlets, generators (before rectification), etc.

Power Supply Overview

- Power sources
 - Regulated
 - Voltage is constant and does not change by the load current
 - Unregulated
 - Voltage changes by itself and/or changes by the load current
 - Voltage source
 - Typical power source
 - Voltage is fixed, but the current varies by the load resistance according to the Ohm's Law
 - Current source
 - Not a typical power source
 - Current is fixed, but the voltage varies by the load resistance according to the Ohm's Law


Power Supply Overview

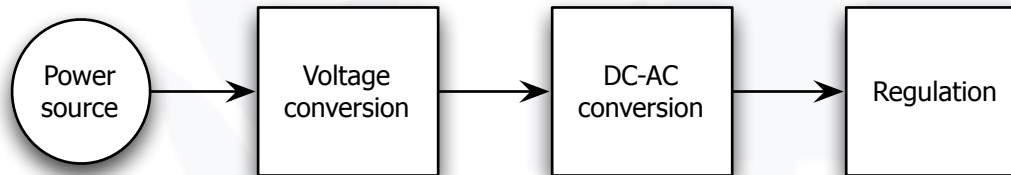- Typical legacy power supply architecture
 - Use of a linear regulator
 - Switching power supply has a different architecture, but beyond the scope
 - Computer Systems Design course will cover it





Power Supply Overview

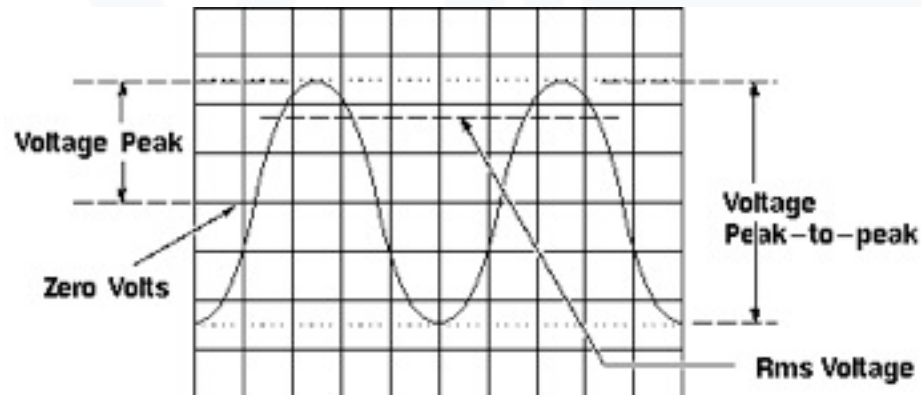- Power Source
 - Typical power source for indoor applications
 - AC outlet
 - 110 to 220 V depending on the location
 - 60 Hz in general, but 50 Hz is also used
 - 110 and 220 V means the RMS (root mean square) voltage
 - Sinusoidal waveform
 - Peak to peak voltage




Power Supply Overview

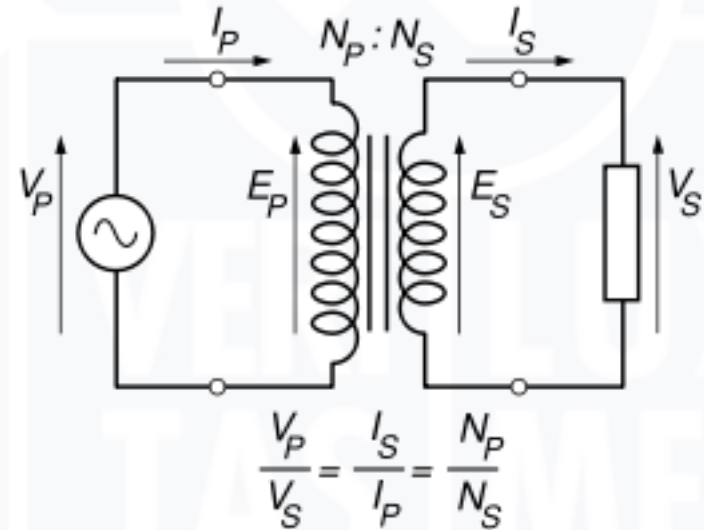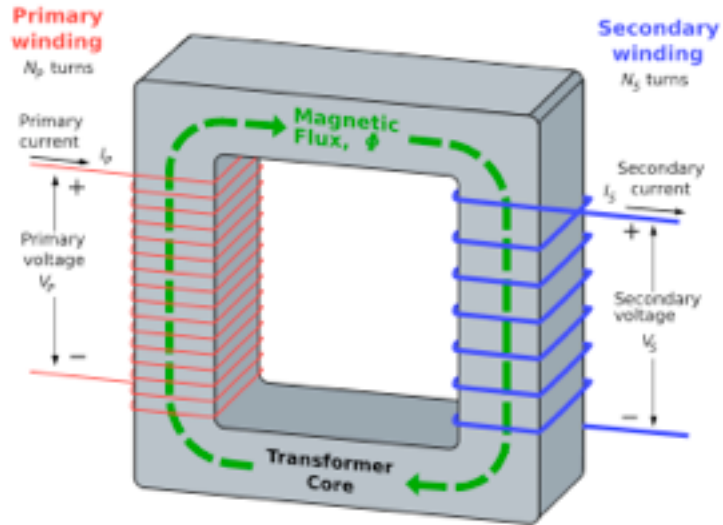- Voltage conversion of an AC power source
 - Use of a transformer





Power Supply Overview

- Typical EI core transformers

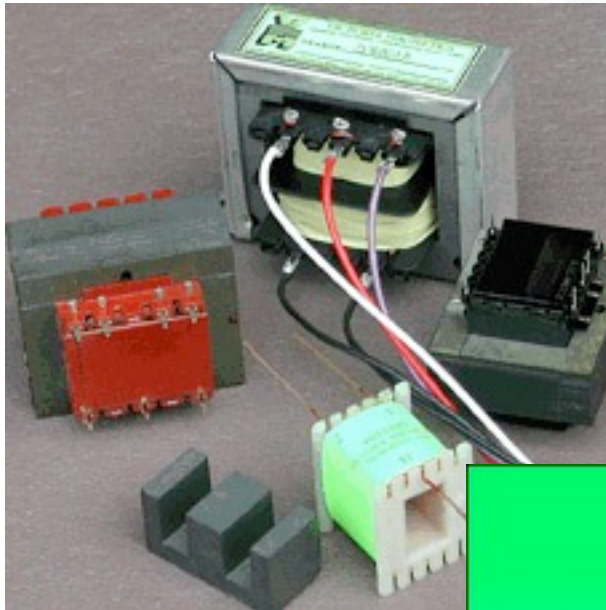


Transformers

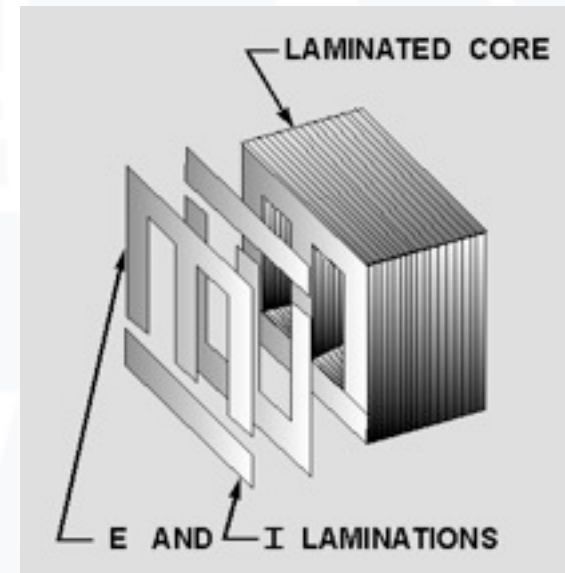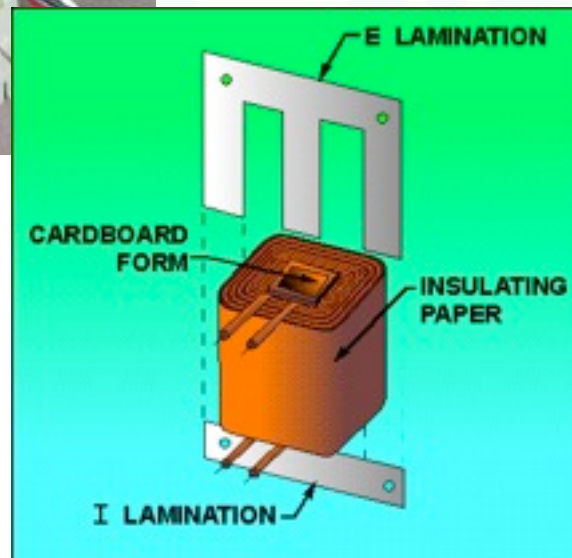

EI cores

Power Supply Overview

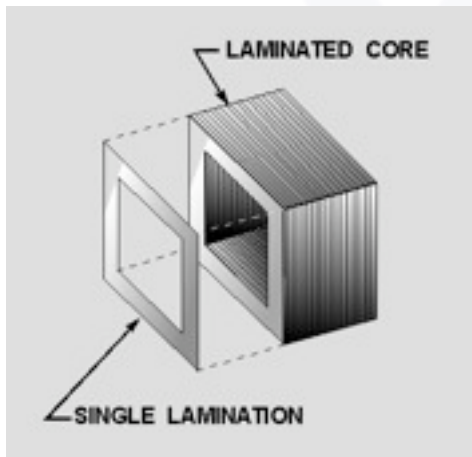- Transformer cores
 - Iron: low frequency (audio frequency, below 20 KHz)
 - Ferrite: high frequency
 - Air: very high frequency
- Types
 - EI
 - Hollow
 - Ring



Hollow core




Power Supply Overview

- Toroidal-core transformer
 - Ideal design for a transformer
 - Faraday designed and wound the first transformer on a toroidal core
 - Very low loss levels and high induction saturation
 - Magnetic flow is evenly spread in the core and due to the absence of intermediate metal parts, vibrations are eliminated
 - All the wound coils are spread over the surface of the core
 - Noise caused by magnetostriction practically disappear
 - a property of ferromagnetic materials that causes them to change their shape when subjected to a magnetic field




Power Supply Overview

- Basic power transformer

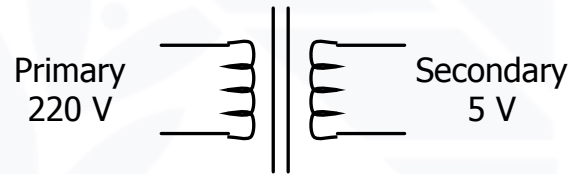


- Multiple secondary windings

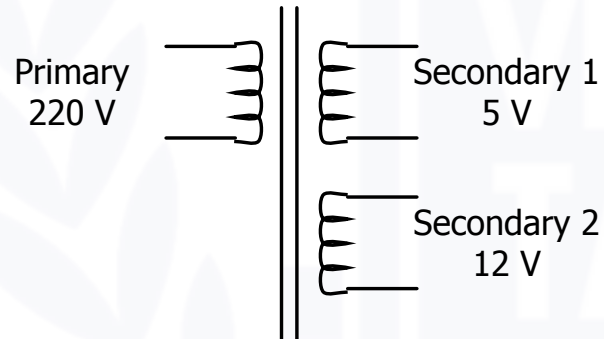


Voltage Conversion

- Center-tapped secondary winding

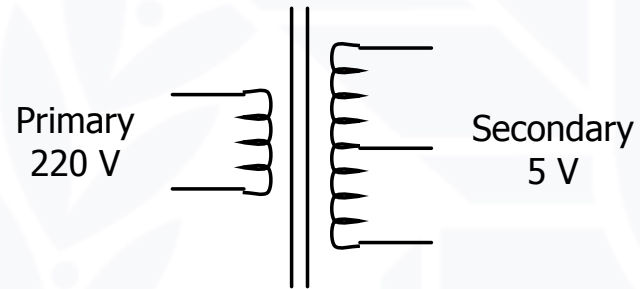


- Split dual primary windings

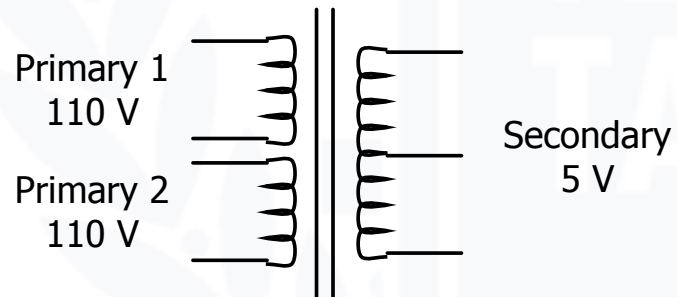


Voltage Conversion

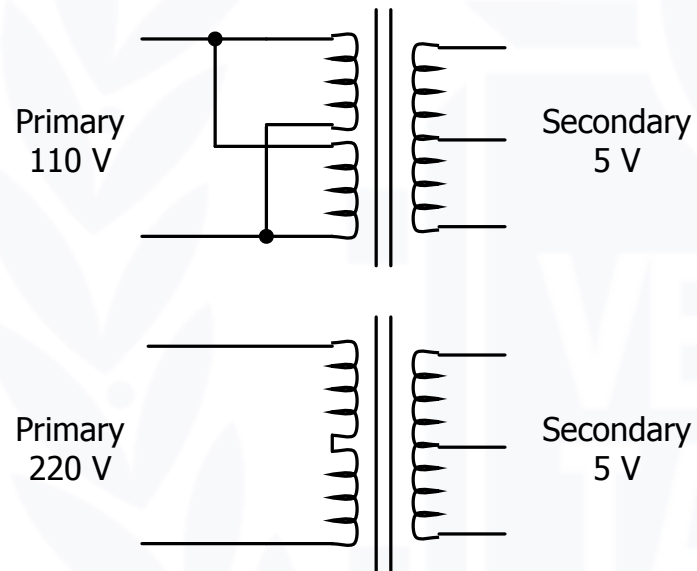- 110 V and 220 V dual input
 - Use of a selection switch to configure both wiring
 - Should be careful for the winding direction




Voltage Conversion

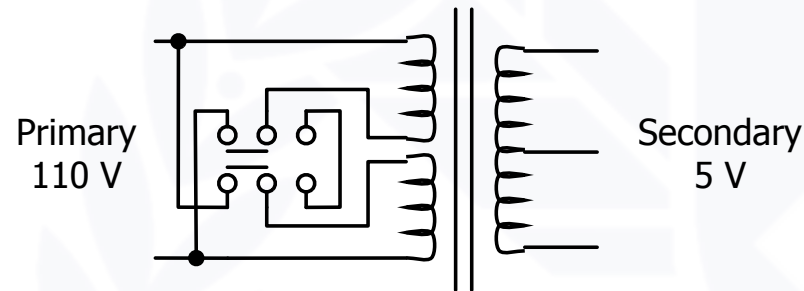- How to make a switch configuration for the dual primary winding?



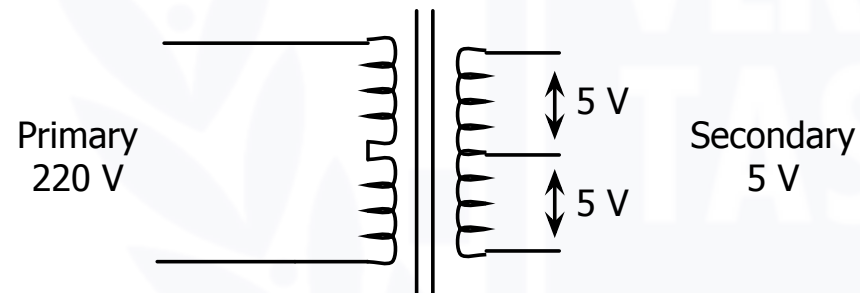- How to use the center-tapped secondary winding?



Voltage Conversion

- Transformers on the market



9V AC 500 mA with Center Tap Power / Filament Transformer Philmore # TR034


Output voltage given are across the entire secondary. Center tapped leads provide 1/2 that voltage from the center to either lead wire. Classic style with metal bracket with mounting holes.

- With Wire Leads
- Input Voltage: 110-120 VAC 60Hz
- Nominal Output at full load, 9 VAC
- Center Tap Voltage at full load: 4.5 VAC

Price: \$4.79


AC-DC Conversion

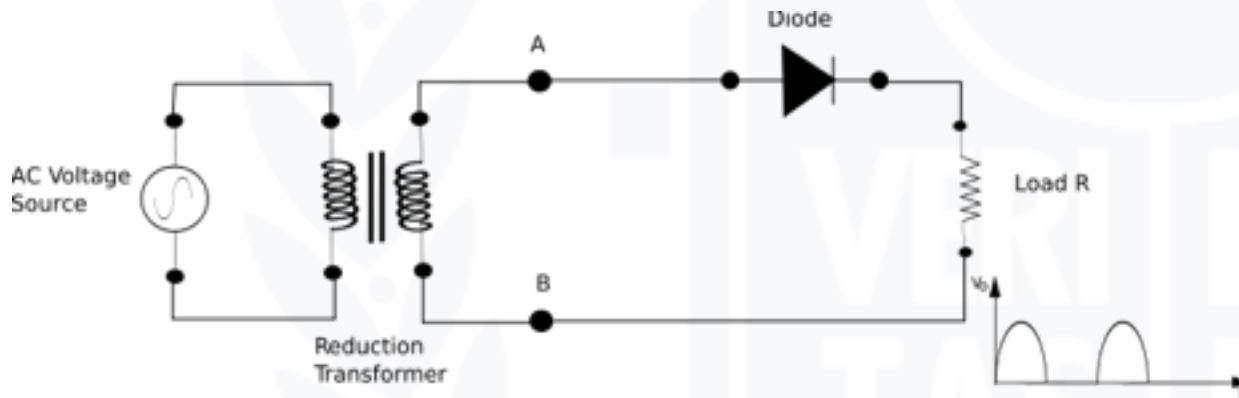- Half-wave rectifier
 - Use of one diode
 - Very simple but high ripple





AC-DC Conversion

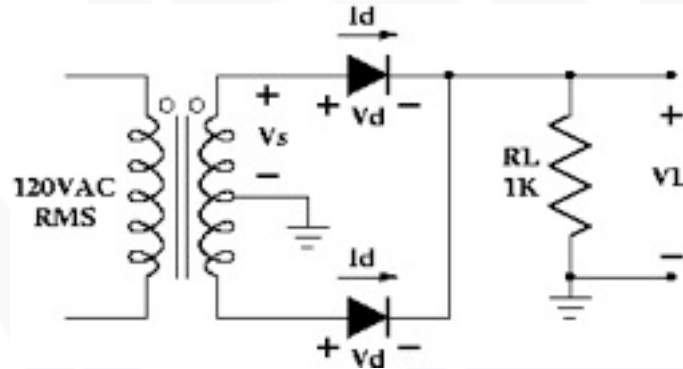- Full-wave rectifiers
 - Use of a center-tapped transformer





- Use if a bridge diode

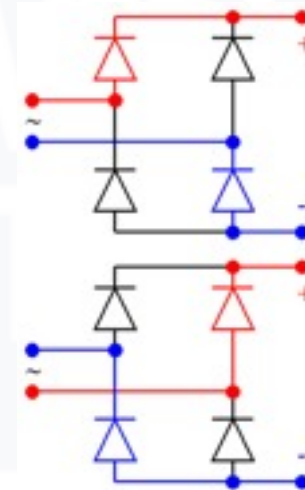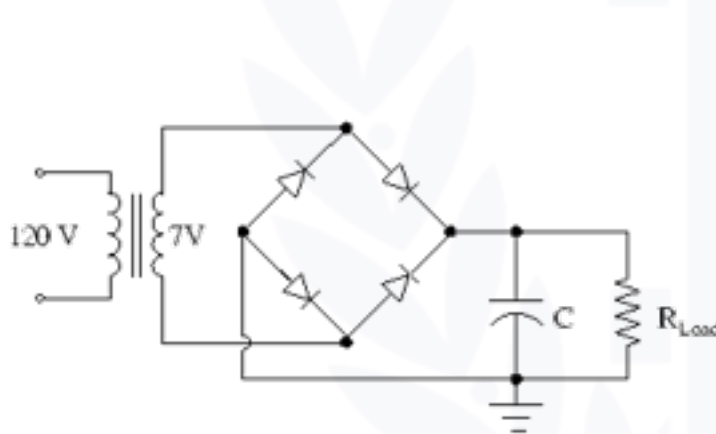

AC-DC Conversion


- Reducing the ripple voltage
 - The diode rectifier generates a DC output with ripple
 - Should be flattened by a bulk capacitor
 - Typically 4,700 μF to 22,000 μF aluminum electrolytic capacitor
 - Use of 2X or higher voltage ratings

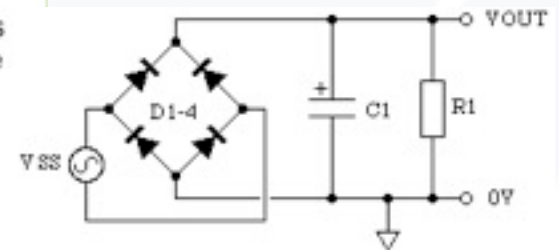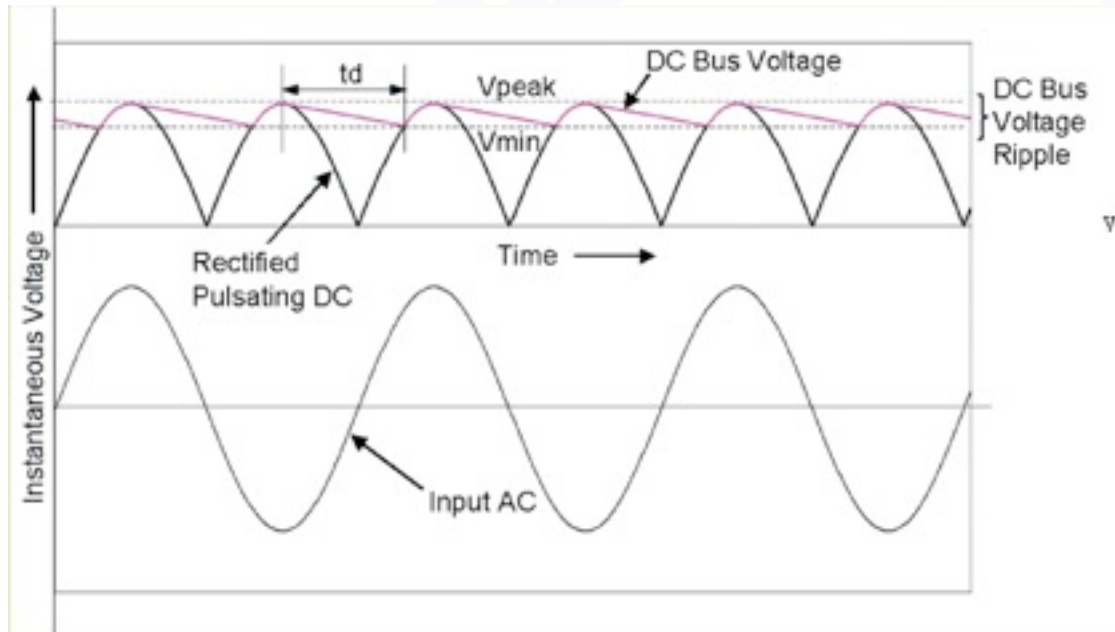

Circuit 14.2 Full-wave rectifier


AC-DC Conversion

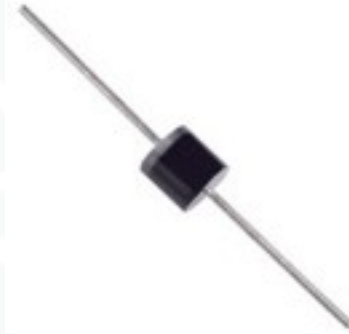- Typically 3X rating
 - Minimum 50 V
 - 2 to 6 A
 - Single, dual and bridge




AC-DC Conversion

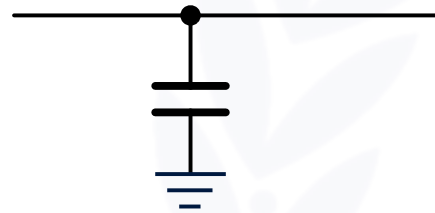
- Why parallel multiple electrolytic capacitors rather than a single capacitor?



Single 10,000 μF

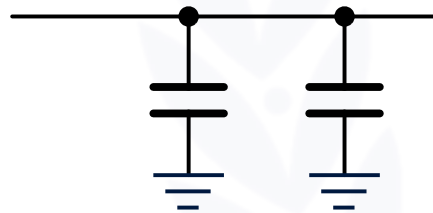

Dual 4,700 μF

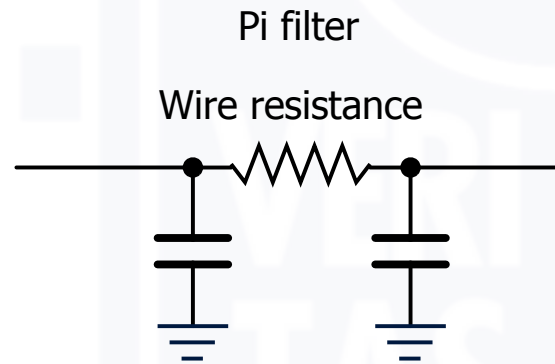

Dual 4,700 μF

AC-DC Conversion

- For digital systems
 - Low equivalent series inductance (ESL) and low equivalent series resistance (ESR) capacitors

AC-DC Conversion

- For digital systems
 - Low equivalent series inductance (ESL) and low equivalent series resistance (ESR) capacitors



a) Ideal



b) real condition


AC-DC Conversion

- Aluminum electrolytic capacitors
 - Polarity
 - Negative marking
 - Long wire is positive
 - Tolerance
 - +100%
 - Rating
 - 6.3 V to high voltages
 - High capacity over 100,000 μF
- Tantalum capacitors
 - Polarity
 - Positive marking
 - Long wire is positive
 - Better frequency response
 - Larger than 100 μF is not cost effective



AC-DC Conversion

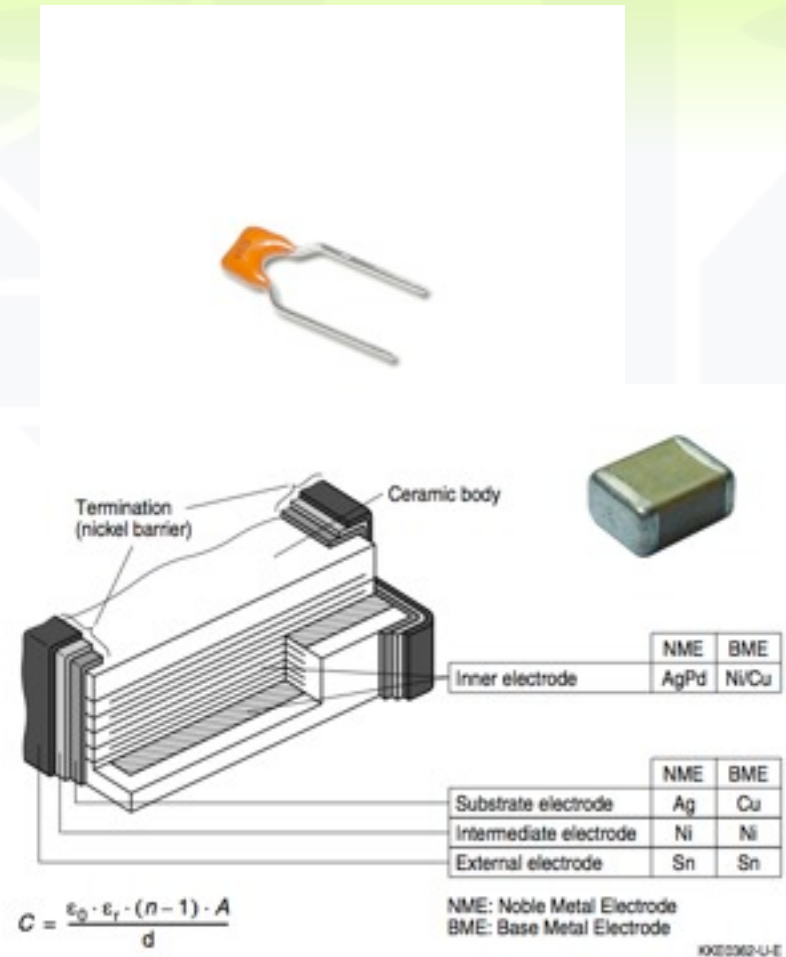- Monolithic capacitors
 - No polarity
 - Very good frequency response
 - Smaller than 1 uF
- Multilayer ceramic capacitor
 - Extremely low ESR
 - High capacitance such as 22 μF
- Parallel connection of two or more different capacitors are desirable
 - Not for the capacity, but for the frequency response




Linear Voltage Regulators

- Voltage divider structure
 - Input current is the same to the output current
 - Only step down is feasible
- Inherently low efficiency
 - Efficiency = output power/input power
 - Input current = output current
 - Voltage difference means power loss!
 - Efficiency = output voltage/input voltage
- True DC output
 - Very low ripple
 - No switching noise
 - Suitable for
 - low-cost systems
 - Analog circuits
 - Low-power systems


Zener Diode Regulator

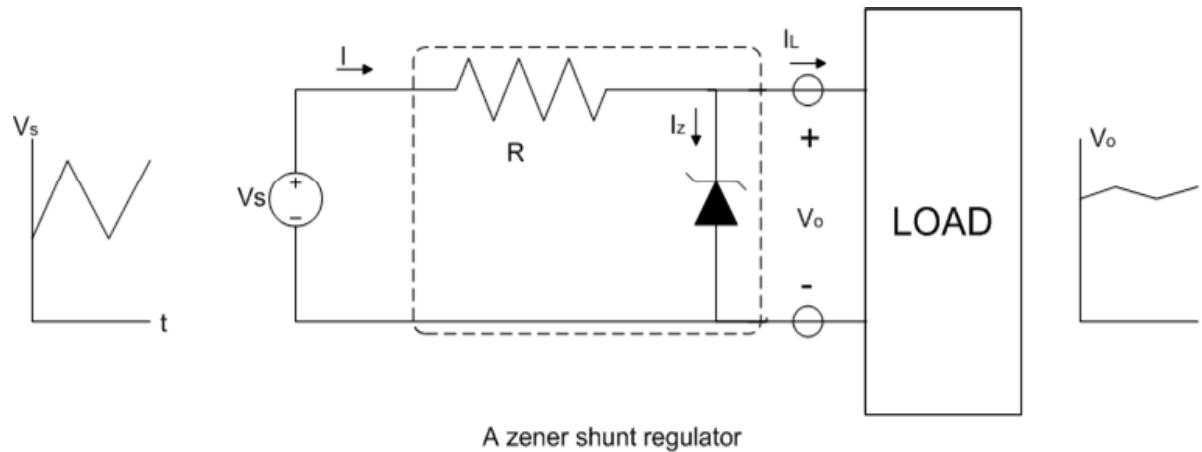- Output voltage regulation using the breakdown voltage of a zener diode
 - Applicable to a very small load
 - Loss through the zener diode is very large





Voltage regulator using OP-amp

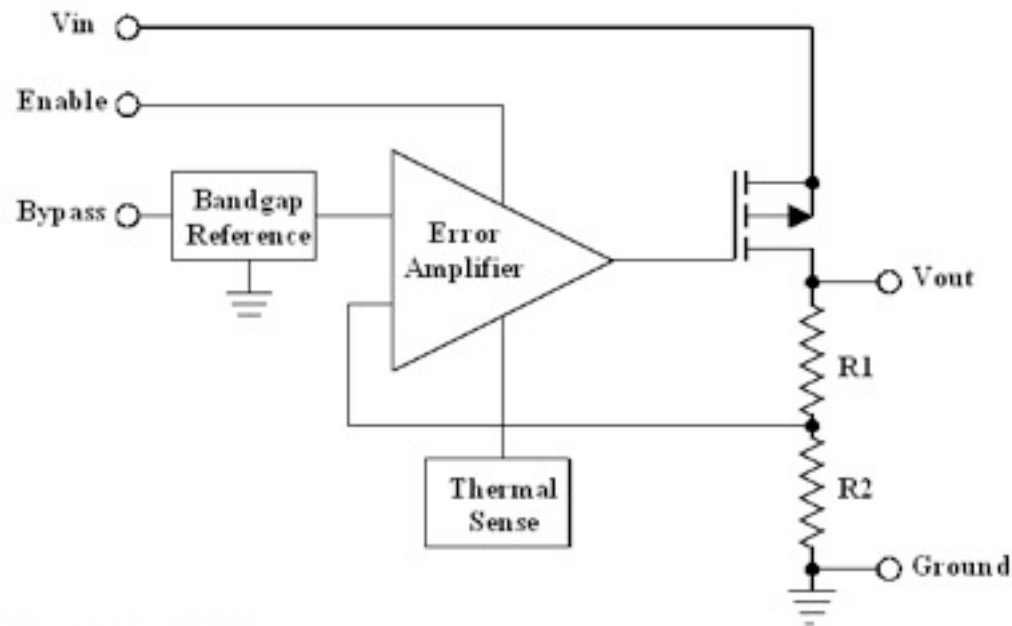- The essential circuit elements
 - A zener reference, a pass or shunt transistor, a sensing circuit, and an error/amplifier circuit
- V_{out} depends on the feedback resistors
 - V_{out} is determined by R_1 and R_2
 - V_{in} must be greater than V_{out}




Three Terminal Voltage Regulator

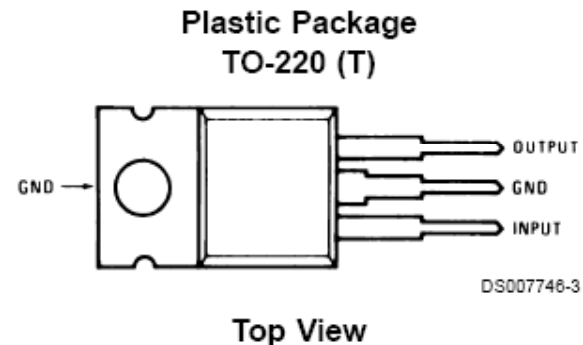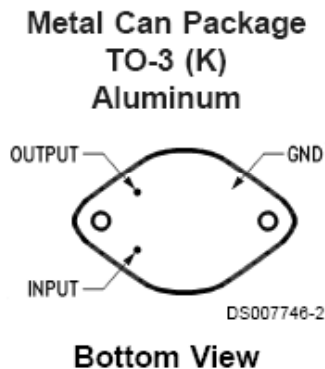- Less flexible, but extremely simple to use
- Come in standard TO-3 (20 W) or TO-220 (15 W) transistor packages
- 78/79XX series regulators are commonly available with 5, 6, 8, 12, 15, 18, or 24 V output
 - Maximum output current with heat sink is 1 A
 - Built-in thermal shutdown protection
 - 3-V dropout voltage; maximum input of 37 V



Three Terminal Voltage Regulator

- 3-terminal variable regulator

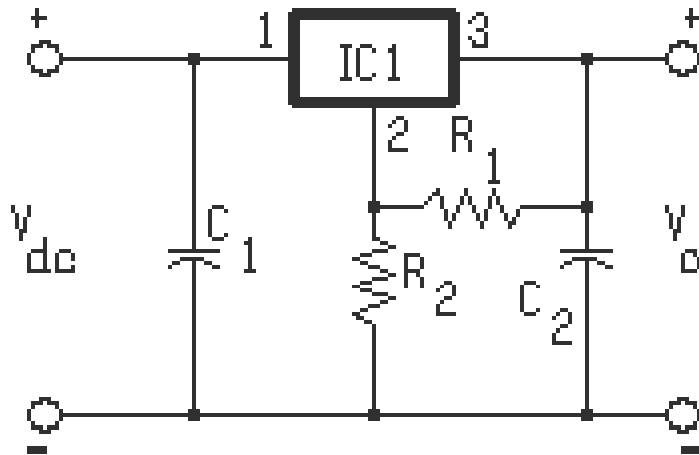


$$V_o = V_{reg} + \left(\frac{V_{reg}}{R_1} + I_Q \right) R_2$$

- 3-terminal regulator could be made into a variable regulator with feedback resistors
- Power dissipation in Resistors can in some cases be quite large resulting in bulky and expensive equipment
- A variety of 3-terminal variable regulators are available, e.g. LM317 (for $+V_{EE}$ output) or LM 337 (for $-V_{EE}$ output)


Low Dropout Regulator (LDO)

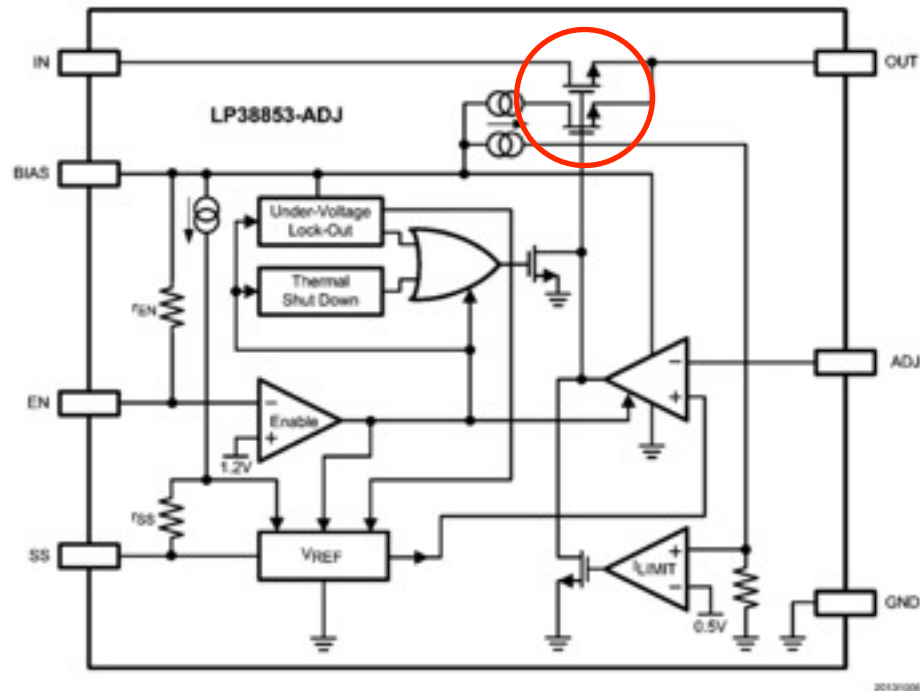- Low dropout due to PMOS output
 - Dropout is typically less than 250 mV (2V dropout for LM78xx)
 - (Potentially) much more efficient than normal NMOS linear regulators
 - If the input and output voltages are the same, an LDO and a regular linear regulator efficiency is the same!




Dual Power Supply

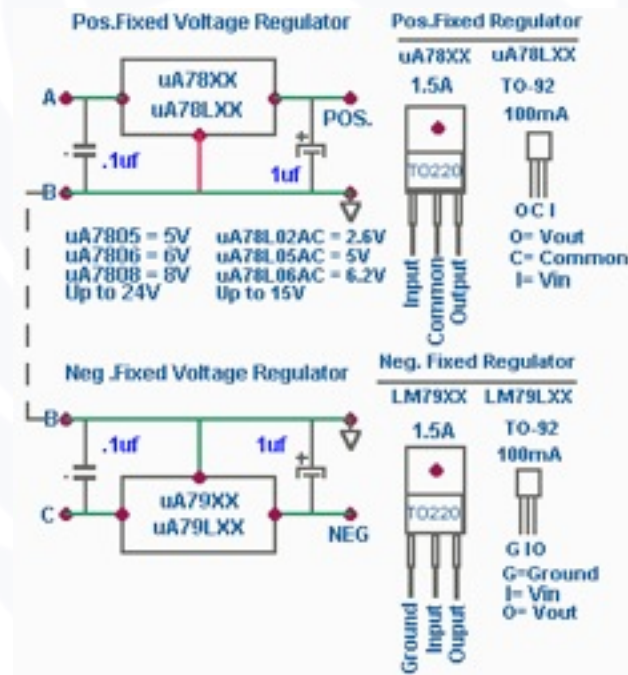- Provide $+V_{EE}$ or $-V_{EE}$ output voltages
- Common in direct coupled amplifiers
- Can be implemented by two independent opposite polarity linear regulators




Dual Power Supply

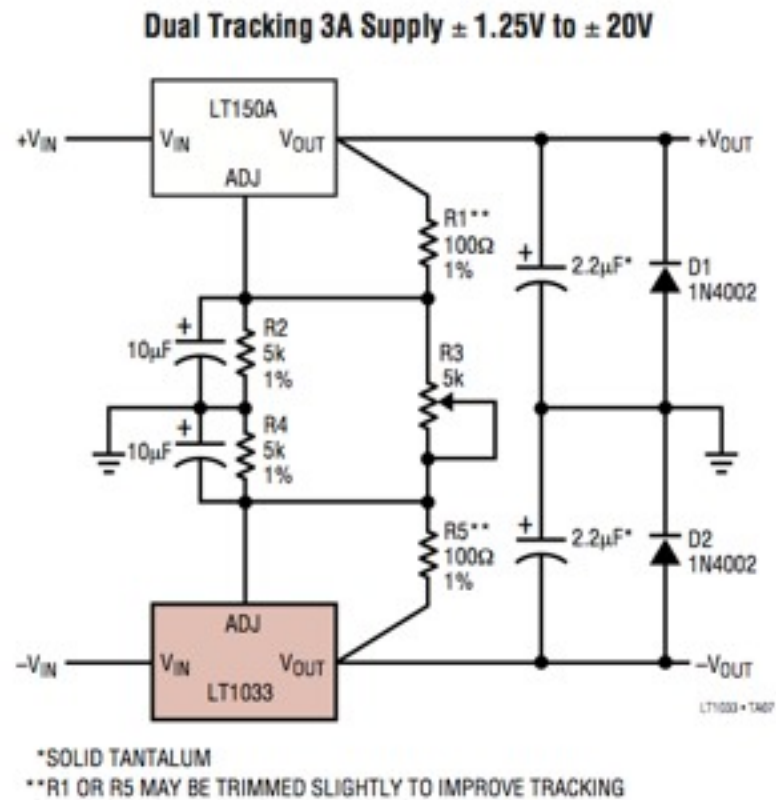- Dual tracking power supply
 - Symmetrical voltage output regardless of V_+ and V_- output current
 - If V_+ output drops due to IR drop, V_- output also drops



Switching Mode DC-DC Converter

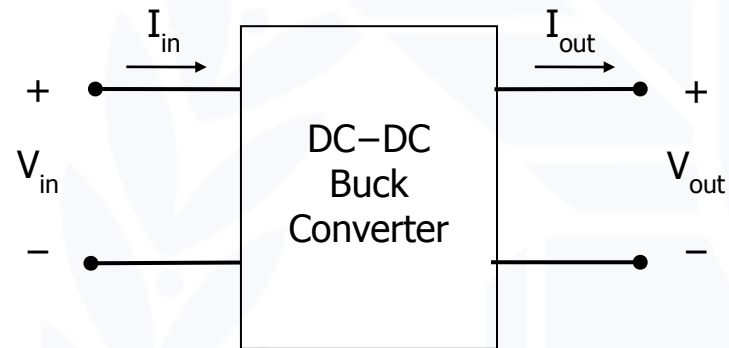
- Objective: to efficiently reduce DC voltage



- The DC equivalent of an AC transformer
- Lossless objective: $P_{in} = P_{out}$

Switching Mode DC-DC Converter

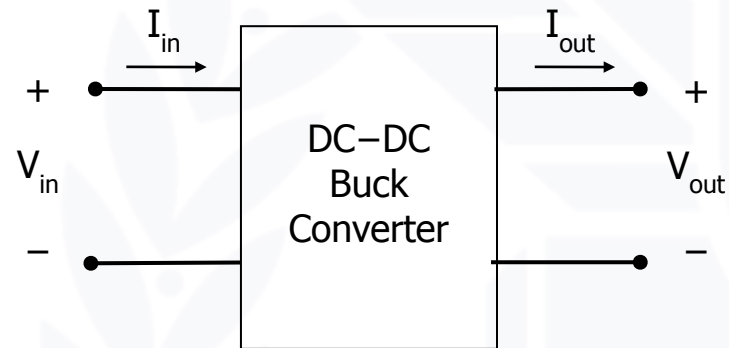- Objective: to efficiently reduce DC voltage




- The DC equivalent of an AC transformer
- Lossless objective: $P_{in} = P_{out}$

$$\frac{V_{out}}{V_{in}} = \frac{I_{in}}{I_{out}}$$

Switching Mode DC-DC Converter

- Voltage divider

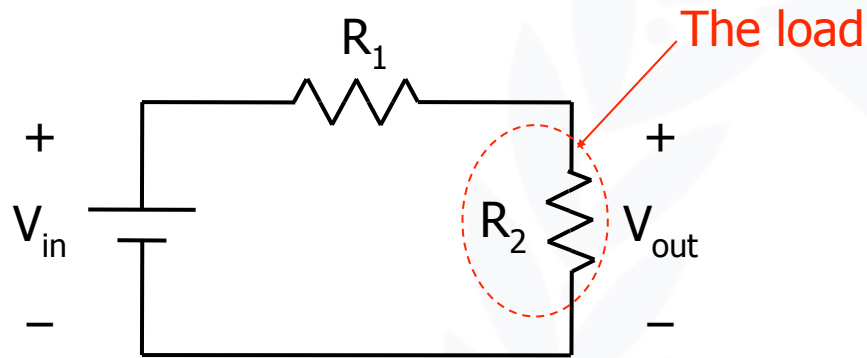


$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

$$\eta = \frac{R_2}{R_1 + R_2} = \frac{V_{out}}{V_{in}}$$

- The most naive approach
- If $V_{in} = 39V$, and $V_{out} = 13V$, efficiency η is only 0.33
- Unacceptable except in very low power applications

Switching Mode DC-DC Converter

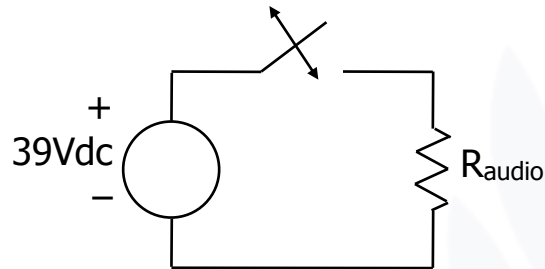
- Convert voltage by switching: 39V to 13V for a car audio



Switch state, Stereo voltage




Closed, 39Vdc

Open, 0Vdc

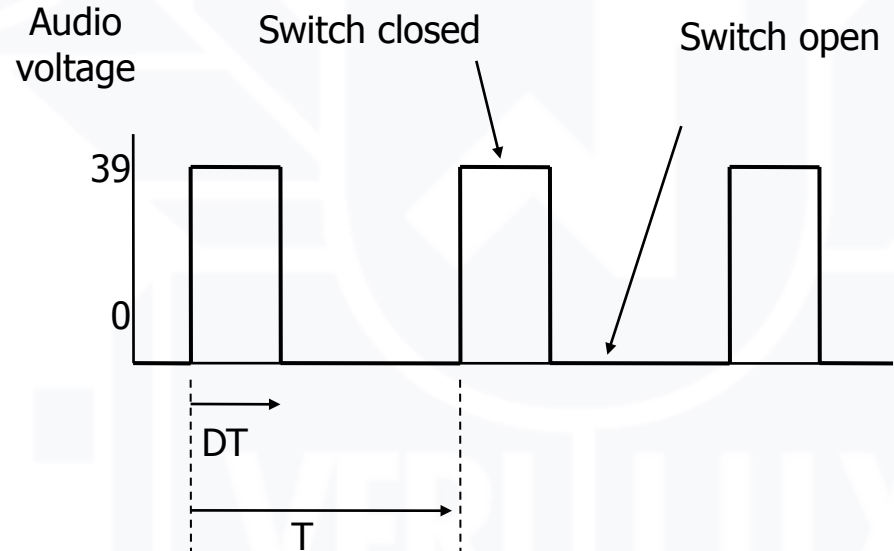


- The DC equivalent of an AC transformer
- If the duty cycle D of the switch is 0.33, then the average voltage to the expensive car stereo is $39 \bullet 0.33 = 13\text{Vdc}$
- This is lossless conversion, but is it acceptable?
 - If it is a light bulb or a heater, it is acceptable

Switching Mode DC-DC Converter

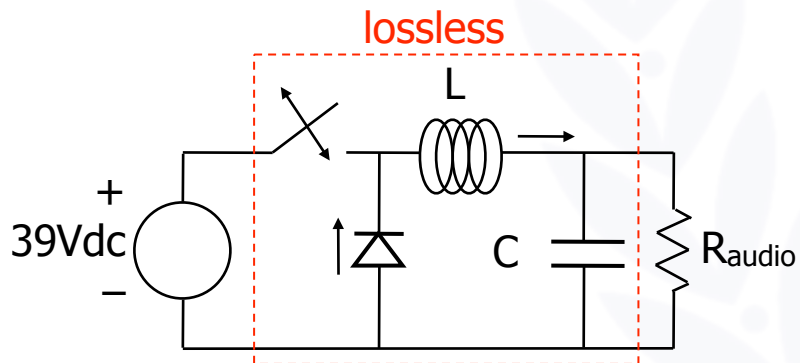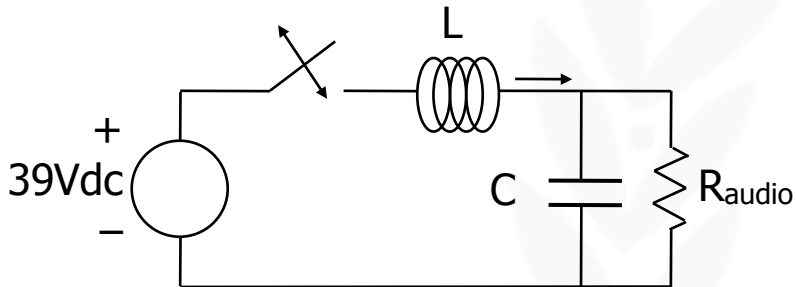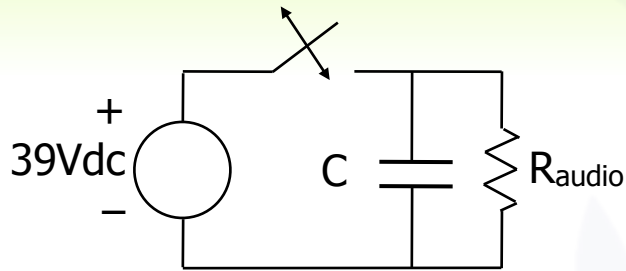


A DC-DC Buck Converter


Switching Mode DC-DC Converter

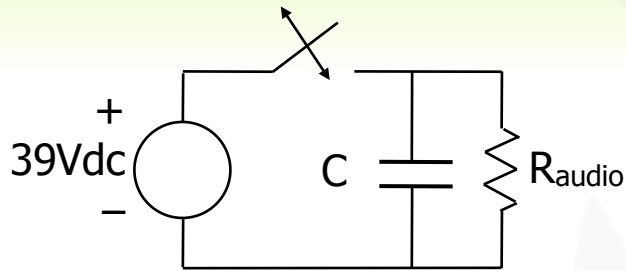

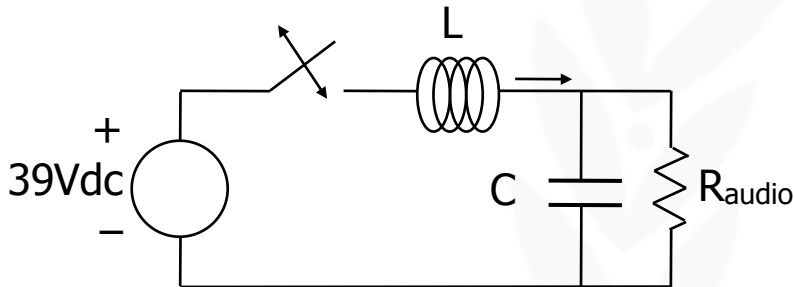Try adding a large C in parallel with the load to control ripple. But if the C has 13Vdc, then when the switch closes, the source current spikes to a huge value and **burns out the switch**.



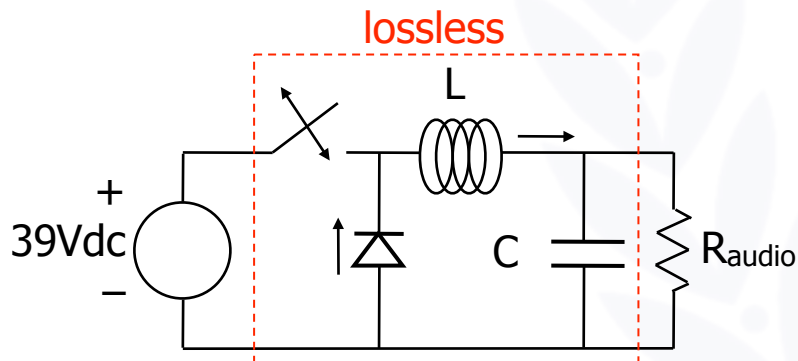Try adding an L to prevent the huge current spike. But now, if the L has current when the switch attempts to open, the inductor's current momentum and resulting $L di/dt$ **burns out the switch**.



A DC-DC Buck Converter

By adding a "free wheeling" diode, the switch can open and the inductor current can continue to flow. With high-frequency switching, the load voltage ripple can be reduced to a small value.

Switching Mode DC-DC Converter


- In capacitors: The voltage cannot change instantaneously
- Capacitors tend to keep the voltage constant (voltage “inertia”)
 - An ideal capacitor with infinite capacitance acts as a constant voltage source
 - A capacitor cannot be connected in parallel with a voltage source or a switch (otherwise KVL would be violated, i.e. there will be a short-circuit)
- In inductors:
 - The current cannot change instantaneously
 - Inductors tend to keep the current constant (current “inertia”)
 - An ideal inductor with infinite inductance acts as a constant current source
 - **Thus, an inductor cannot be connected in series with a current source or a switch (otherwise KCL would be violated)**

Switching Mode DC-DC Converter

- In capacitors: $i(t) = C \frac{dv(t)}{dt}$ The voltage cannot change instantaneously
- Capacitors tend to keep the voltage constant (voltage “inertia”)
 - An ideal capacitor with infinite capacitance acts as a constant voltage source
 - A capacitor cannot be connected in parallel with a voltage source or a switch (otherwise KVL would be violated, i.e. there will be a short-circuit)
- In inductors: $v(t) = L \frac{di(t)}{dt}$
 - The current cannot change instantaneously
 - Inductors tend to keep the current constant (current “inertia”)
 - An ideal inductor with infinite inductance acts as a constant current source
 - **Thus, an inductor cannot be connected in series with a current source or a switch (otherwise KCL would be violated)**

Buck Converter

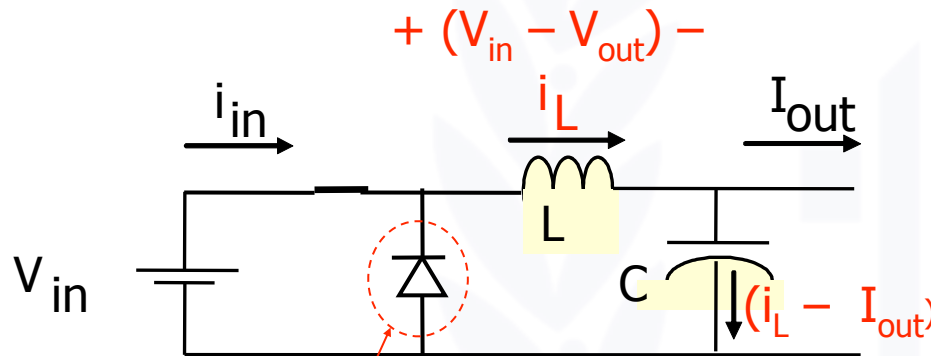- The input/output equation for DC-DC converters usually comes by examining inductor voltages
- Switch closed for DT seconds



Reverse biased, thus the diode is open


$$+ \\ V_{out} \\ -$$

$$v_L = V_{in} - V_{out},$$

for DT seconds

Buck Converter

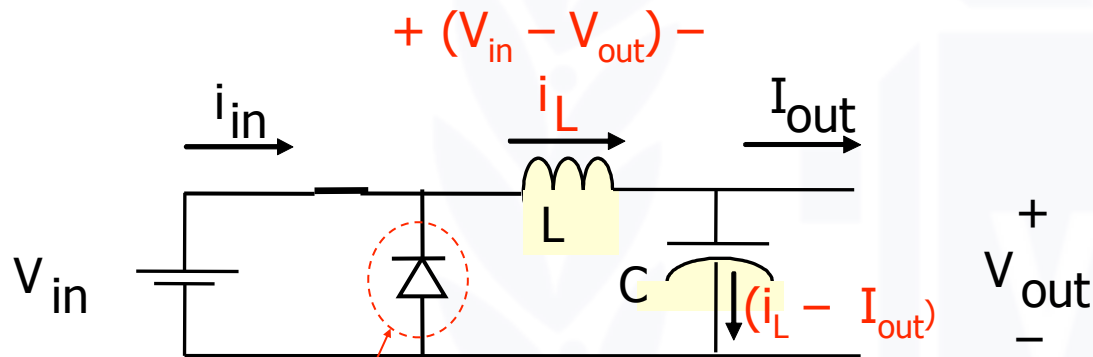- The input/output equation for DC-DC converters usually comes by examining inductor voltages
- Switch closed for DT seconds



Reverse biased, thus the diode is open

$$v_L = L \frac{di_L}{dt},$$


$$v_L = V_{in} - V_{out},$$

for DT seconds

$$\frac{di_L}{dt} = \frac{V_{in} - V_{out}}{L}$$

Buck Converter

- Switch open for $(1 - D)T$ seconds

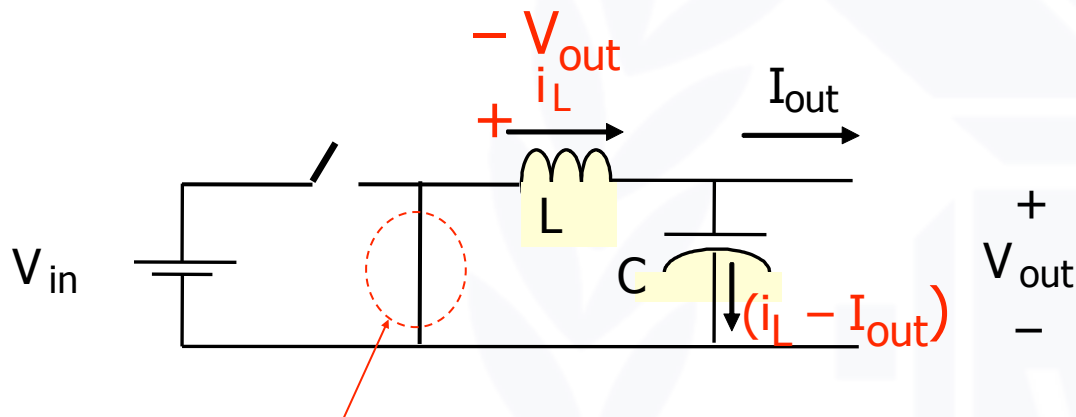


$$v_L = -V_{out},$$

for $(1-D)T$ seconds

i_L continues to flow, thus the diode is closed. This is the assumption of "continuous conduction" in the inductor which is the normal operating condition.

Buck Converter

- Switch open for $(1 - D)T$ seconds

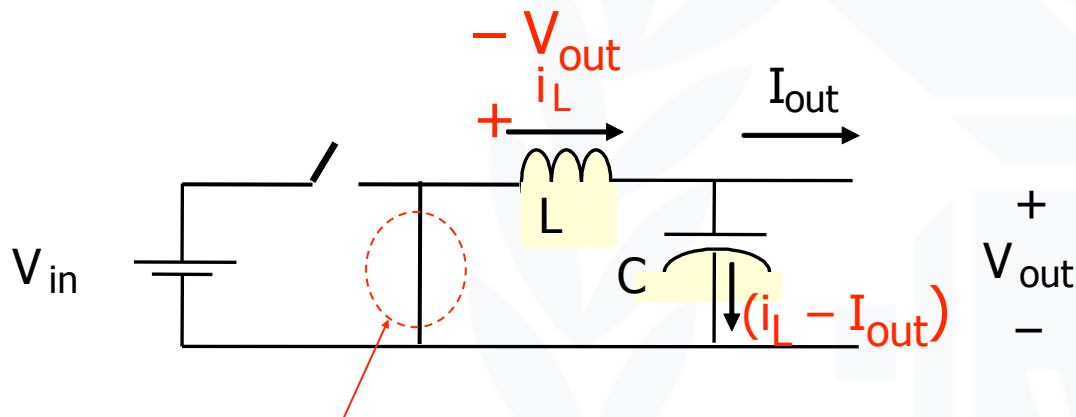

$$v_L = L \frac{di_L}{dt},$$

$$v_L = -V_{out},$$

for $(1-D)T$ seconds

i_L continues to flow, thus the diode is closed. This is the assumption of "continuous conduction" in the inductor which is the normal operating condition.

$$\frac{di_L}{dt} = \frac{-V_{out}}{L}$$

Buck Converter

- Since the average voltage across L is zero,

$$V_{Lavg} = D \cdot (V_{in} - V_{out}) + (1 - D) \cdot (-V_{out}) = 0$$

- From power balance,

- Output voltage and current become

$$I_{out} = \frac{I_{in}}{D}$$

$$V_{out} = DV_{in}$$

Buck Converter

- Since the average voltage across L is zero,

$$V_{Lavg} = D \cdot (V_{in} - V_{out}) + (1 - D) \cdot (-V_{out}) = 0$$

- From power balance,

$$V_{in}I_{in} = V_{out}I_{out}$$


- Output voltage and current become

$$I_{out} = \frac{I_{in}}{D}$$

$$V_{out} = DV_{in}$$

Buck Converter

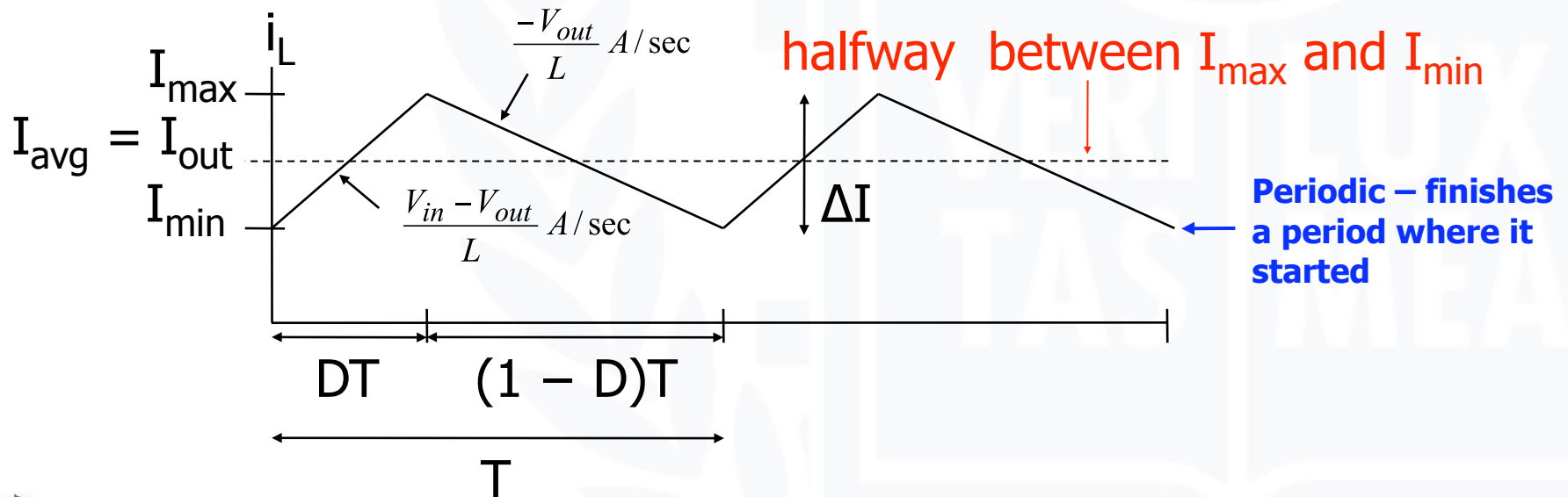- Examine the inductor current
- Switch closed
- Switch open



Buck Converter


- Examine the inductor current
- Switch closed
- Switch open

$$v_L = V_{in} - V_{out}, \frac{di_L}{dt} = \frac{V_{in} - V_{out}}{L}$$

$$v_L = -V_{out}, \frac{di_L}{dt} = \frac{-V_{out}}{L}$$


From geometry, $I_{avg} = I_{out}$ is

halfway between I_{max} and I_{min}

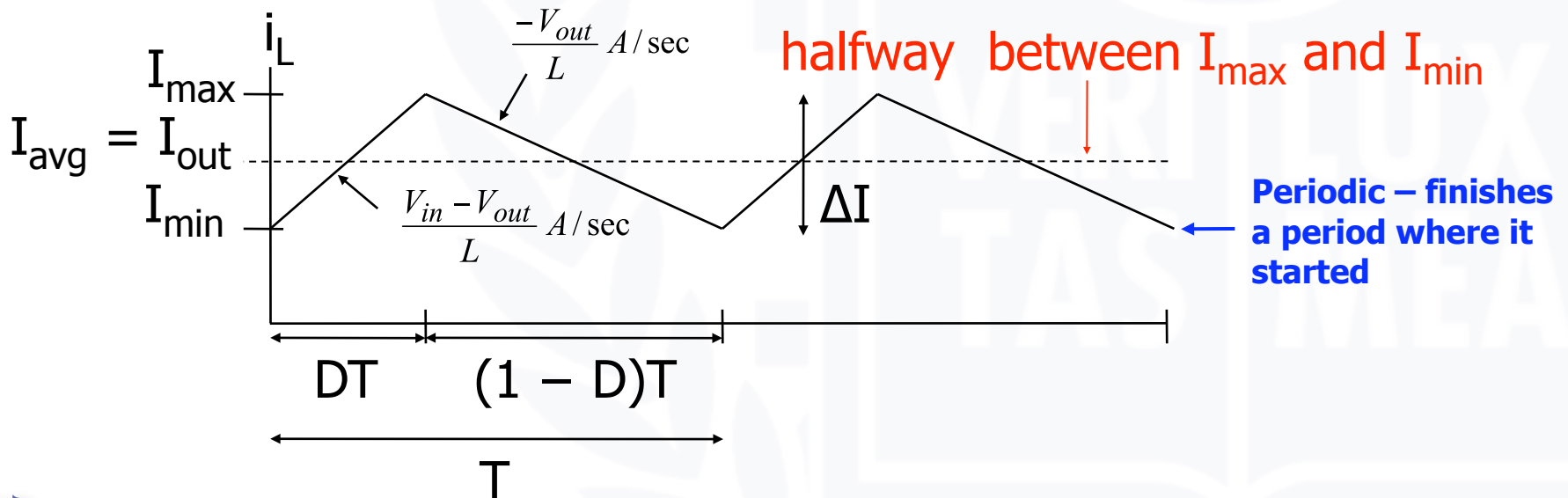

Buck Converter

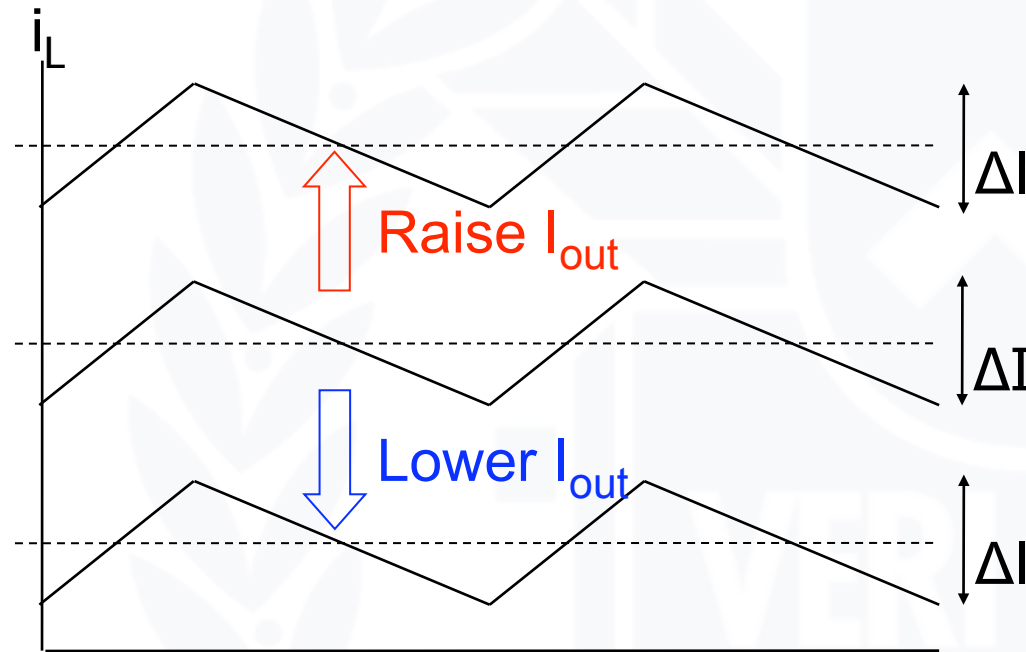
- Effect of raising and lowering I_{out} while holding V_{in} , V_{out} , f , and L constant



- ΔI is unchanged
- Lowering I_{out} (and, therefore, P_{out}) moves the circuit toward discontinuous operation

Buck Converter

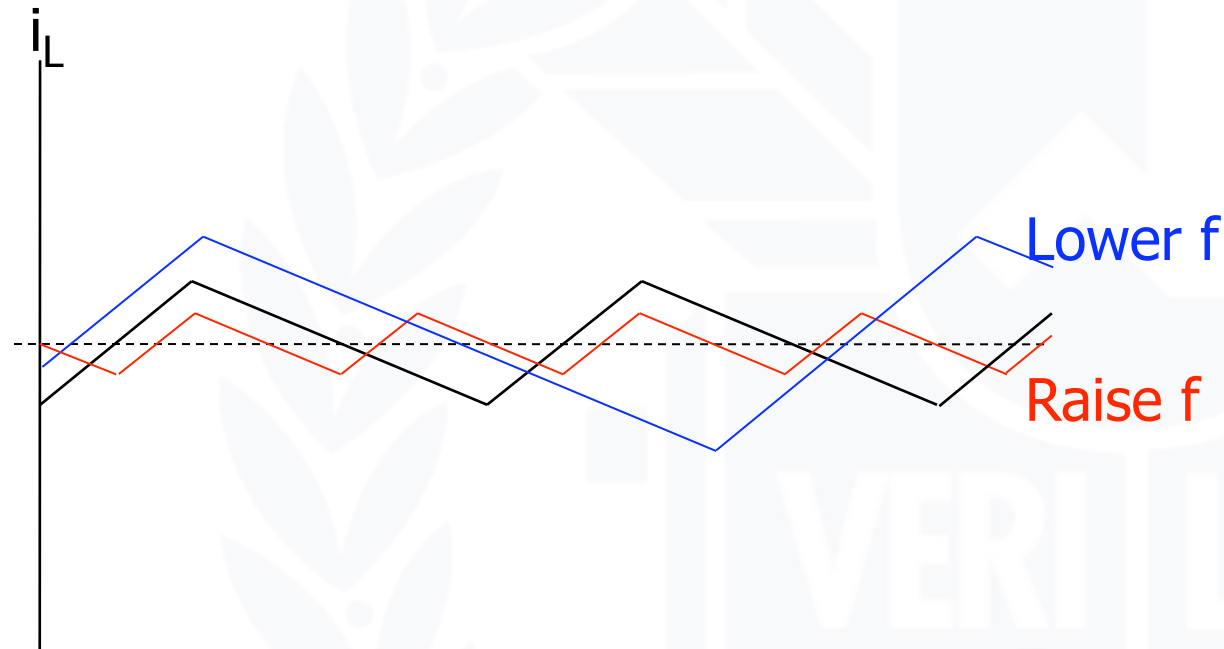
- Effect of raising and lowering f while holding V_{in} , V_{out} , I_{out} , and L constant



- Slopes of i_L are unchanged
- Lowering f increases ΔI and moves the circuit toward discontinuous operation

Buck Converter

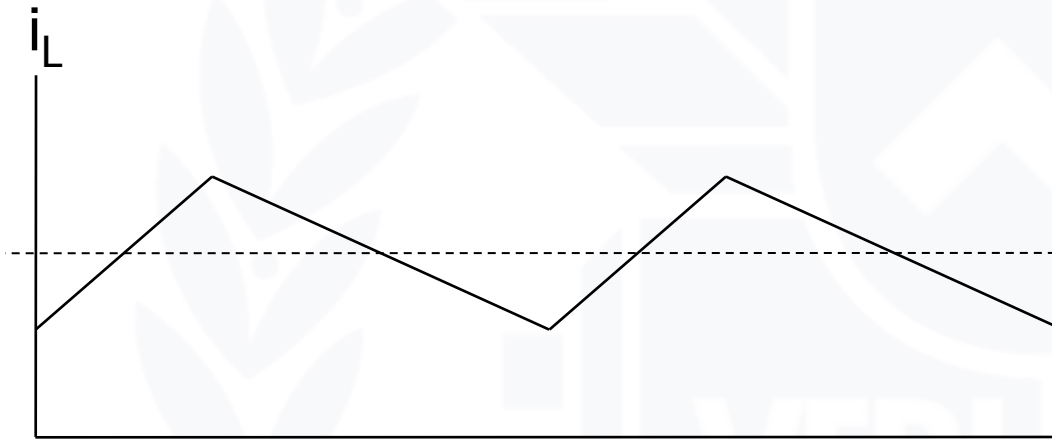
- Effect of raising and lowering L while holding V_{in} , V_{out} , I_{out} and f constant



- Lowering L increases ΔI and moves the circuit toward discontinuous operation

Buck Converter

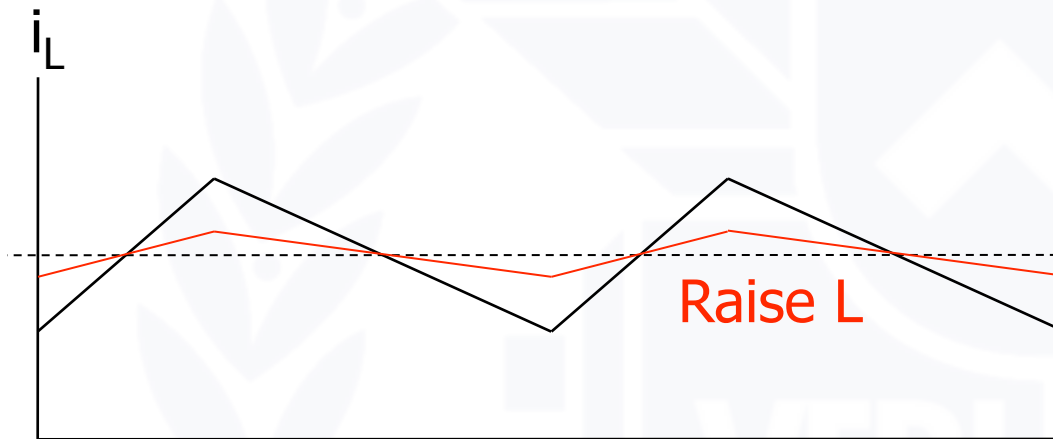
- Effect of raising and lowering L while holding V_{in} , V_{out} , I_{out} and f constant



- Lowering L increases ΔI and moves the circuit toward discontinuous operation

Buck Converter

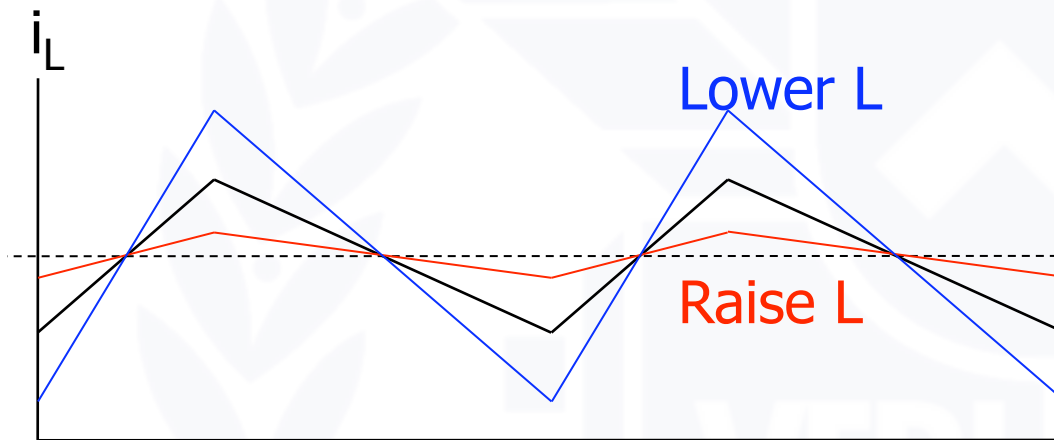
- Effect of raising and lowering L while holding V_{in} , V_{out} , I_{out} and f constant




- Lowering L increases ΔI and moves the circuit toward discontinuous operation

Boost Converter

● Buck converter

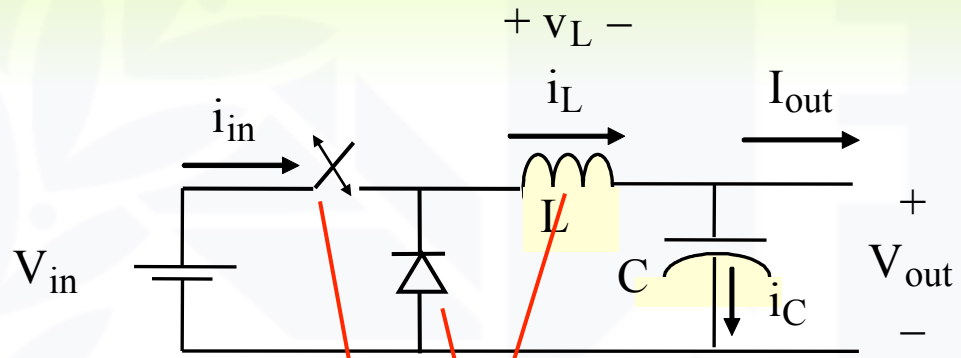


● Boost converter

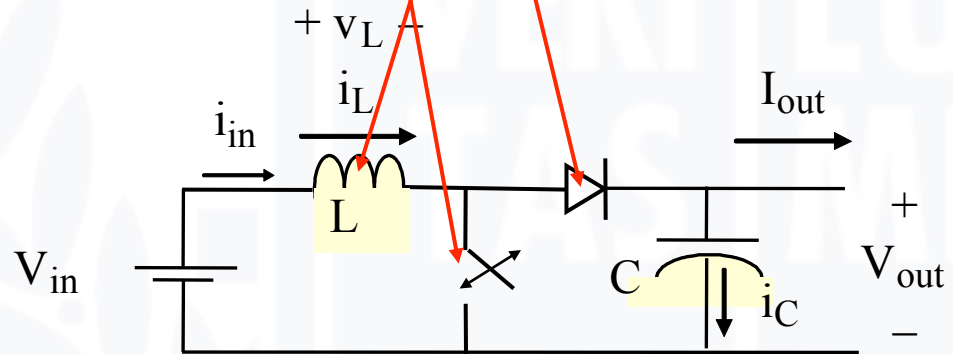

Boost Converter

- Switch closed for DT seconds

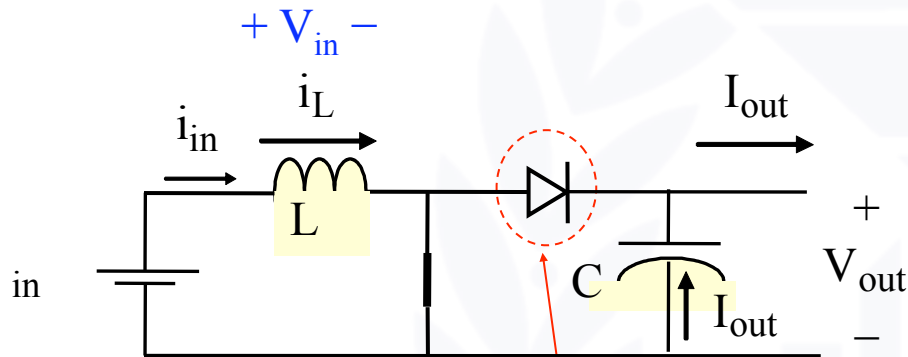

$$\frac{di_L}{dt} = \frac{V_{in}}{L}$$


for DT
seconds

Reverse biased, thus the diode is open

- If the switch stays closed, the input is short circuited!

Boost Converter

- Switch open for $(1 - D)T$ seconds

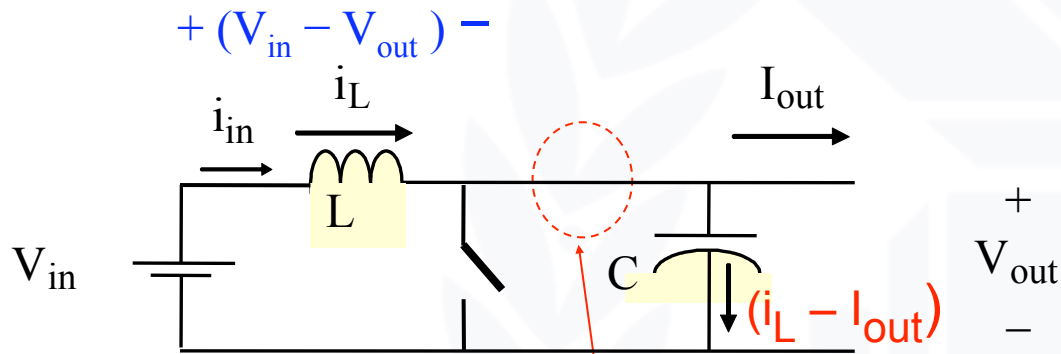

$$\frac{di_L}{dt} = \frac{V_{in} - V_{out}}{L}$$

for $(1-D)T$ seconds

Diode closed. Assume continuous conduction.

Boost Converter

- Since the average voltage across L is zero

$$V_{Lavg} = D \cdot V_{in} + (1 - D) \cdot (V_{in} - V_{out}) = 0$$

- The input/output equation becomes

Boost Converter

- Since the average voltage across L is zero

$$V_{Lavg} = D \cdot V_{in} + (1 - D) \cdot (V_{in} - V_{out}) = 0$$

$$V_{out} \cdot (1 - D) = V_{in} + \cancel{D \cdot V_{in}} - \cancel{D \cdot V_{in}}$$

- The input/output equation becomes

Boost Converter

- Since the average voltage across L is zero

$$V_{Lavg} = D \cdot V_{in} + (1 - D) \cdot (V_{in} - V_{out}) = 0$$

$$V_{out} \cdot (1 - D) = V_{in} + \cancel{D \cdot V_{in}} - \cancel{D \cdot V_{in}}$$


- The input/output equation becomes

$$V_{out} = \frac{V_{in}}{1 - D}$$

A realistic upper limit on boost is 5 times

Boost Converter

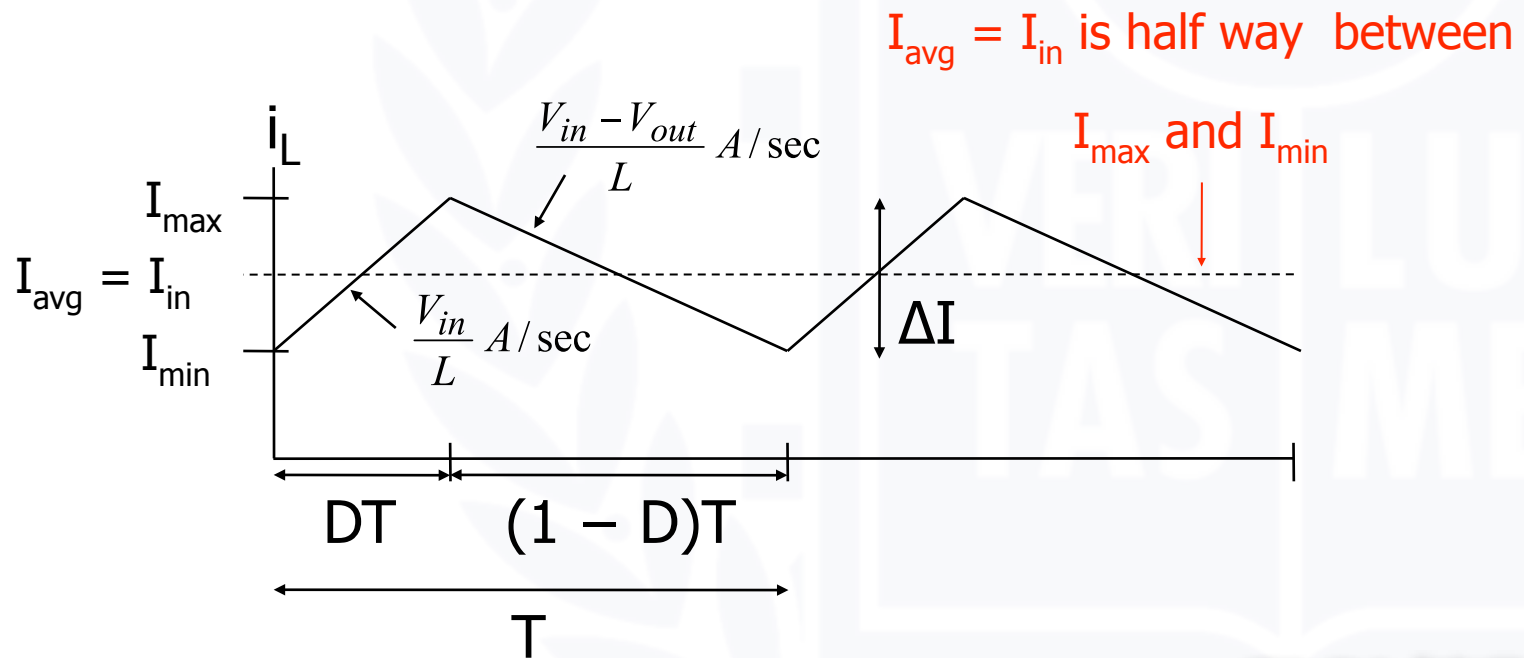- Examine the inductor current
- Switch closed
- Switch open




Boost Converter

- Examine the inductor current
- Switch closed
- Switch open

$$v_L = V_{in}, \frac{di_L}{dt} = \frac{V_{in}}{L}$$

$$v_L = V_{in} - V_{out}, \frac{di_L}{dt} = \frac{V_{in} - V_{out}}{L}$$

$I_{avg} = I_{in}$ is half way between

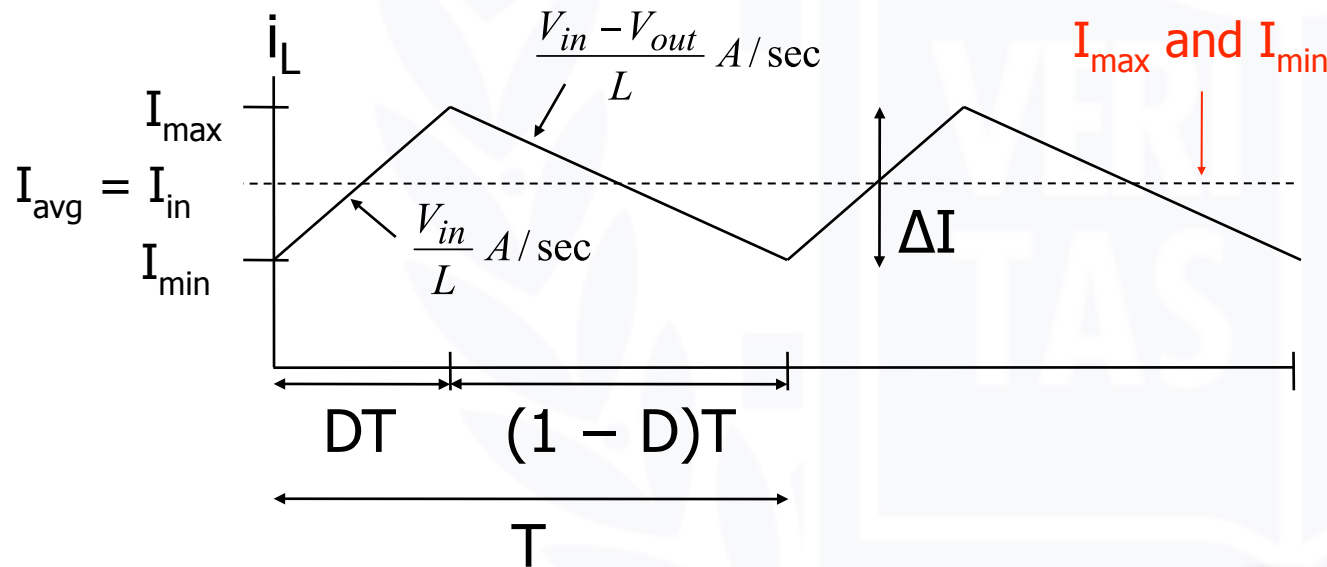

Embedded System Application

4190.303C

2010 Spring Semester

**Simultaneous Optimization of Battery-aware Voltage Regulator
Scheduling with Dynamic Voltage and Frequency Scaling**

Naehyuck Chang
Dept. of EECS/CSE
Seoul National University
naehyuck@snu.ac.kr




Contents

- Motivation
- Paper contribution
- Problem statement
- Real device modeling
- DRS cost function
- Solution method
- Experimental results
- Conclusions




Motivation

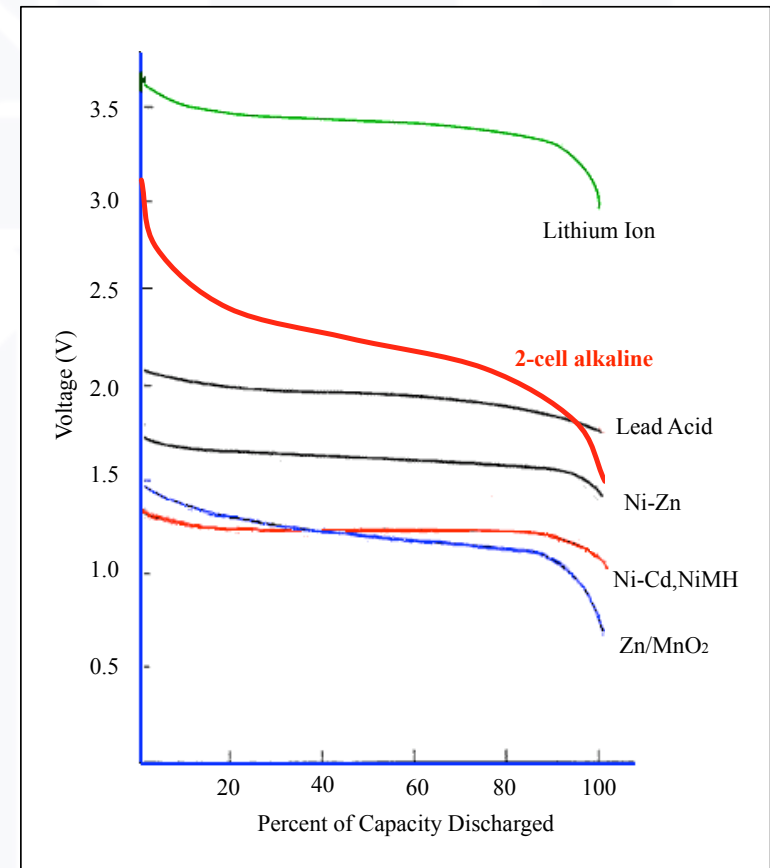- Why voltage regulators?
 - To obtain a proper supply voltage level
 - Battery cell voltages do not always match with the CPU VDD
 - To compensate the IR drop of the battery
 - Battery internal resistance
 - Power delivery network
 - To compensate the terminal voltage drop due to the state of charge loss




Motivation

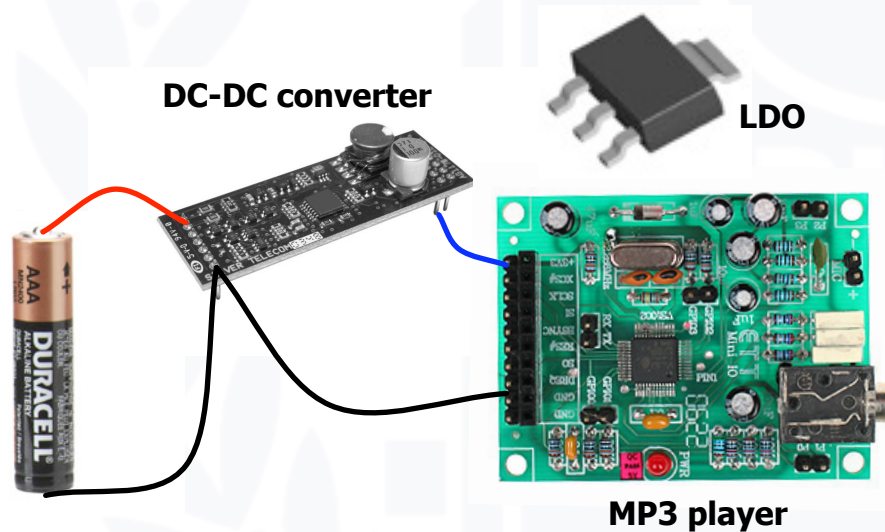- Typical power supply and management systems
 - Voltage regulation is not free
 - 10% to 40% system energy loss from voltage regulators, typically DC-DC converters or LDOs




Motivation

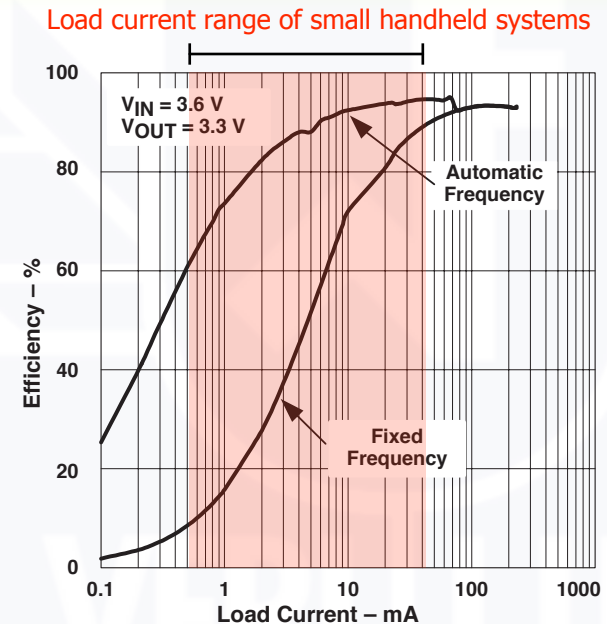- DC-DC converter
 - Buck, boost and flyback
 - DC → AC → voltage change → AC → DC
 - Voltage regulator loss becomes significant in light load applications
- Linear regulator
 - High drop out
 - $V_{IN} > V_{OUT} + 2\text{ V}$ (7805)
 - Low drop out
 - $V_{IN} > V_{OUT} + 150\text{ mV}$
 - Power loss
 - Load current × drop out voltage
 - Naturally the loss is high




DC-DC converter

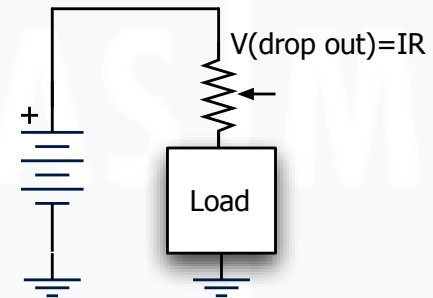

LDO

Motivation

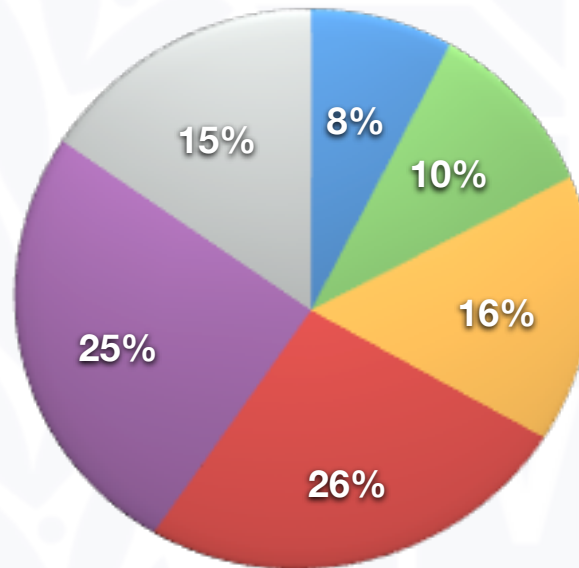
- Where does the power go?
 - Power breakdown of a portable MPEG4 player



- Hojun Shim, Youngjin Cho and Naehyuck Chang, "Power Saving in Hand-held Multimedia Systems Using MPEG-21 Digital Item Adaptation," in ESTIMedia, 2004


Motivation

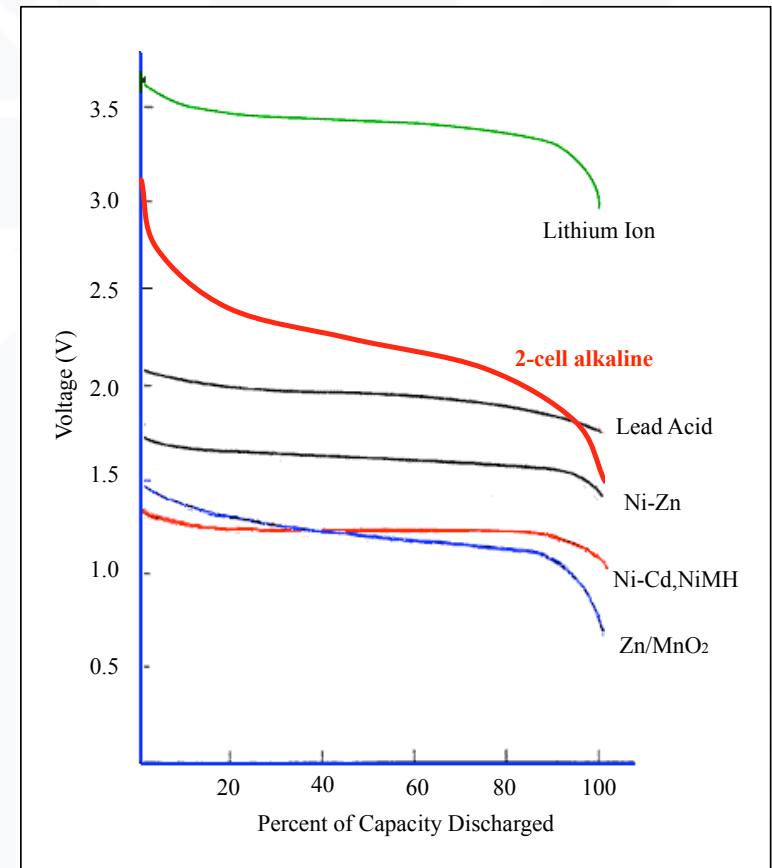- Question: why voltage regulators?
 - To obtain a proper supply voltage level
 - To compensate the IR drop of the battery
 - To compensate the terminal voltage drop due to the state of charge loss
- Alkaline battery discharge characteristics
 - Battery voltage may match with V_{DD} of the microprocessor
 - IR drop is tolerable for low-power applications
 - Wide voltage range while alive (3.0 to 1.7 V)
 - Direct battery drive is feasible




Motivation

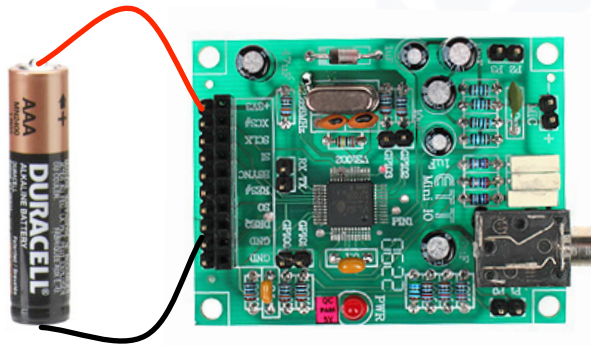
- Previous direct battery drive methods
 - Voltage regulator elimination




Direct drive without a voltage regulator

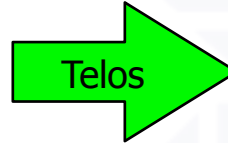

IPSN 2005

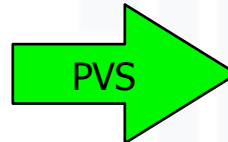

ISLPED 2007

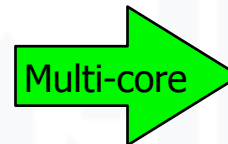


CODES+ISSS 2007


- Operation of the CPU at the lowest clock frequency w/o clock scaling
- Guaranteed constant performance
- Waste of potential CPU performance
- CPU clock frequency decreases as the battery voltage decreases in a passive manner
- Performance decreases as the battery voltage decreases
- Networked operation maintain a guaranteed performance
- Frequency scaling in a passive manner
- Progressive wake-up of a multi-core CPU to maintain a guaranteed performance

Motivation


- Comparison among previous direct battery drive methods
 - It is not a good idea to waste potential CPU performance to provide a guaranteed performance to the end

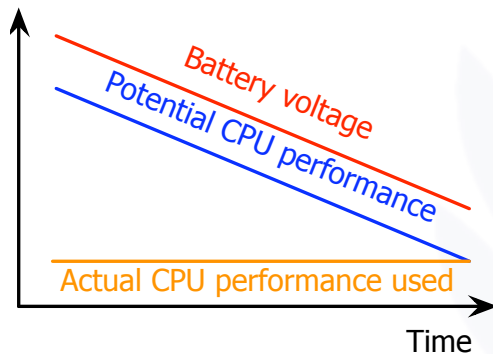

ISPN 2005

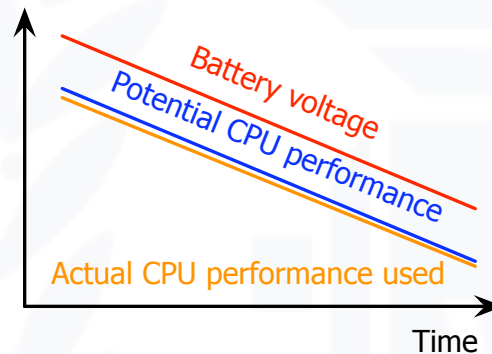

ISLPED 2007

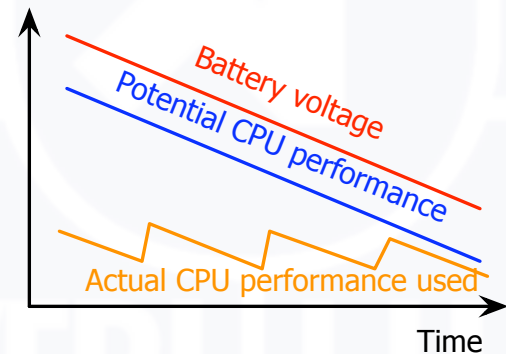


CODES+ISSS 2007

Motivation


- Which voltage regulation is the best?
 - DC-DC converter
 - Can be applicable w/o limitation
 - Best when the battery voltage and V_{DD} difference is big
 - Inefficient when the load current is light
 - When the battery voltage $< V_{DD}$, this is the only feasible method
 - LDO (low-dropout linear regulator)
 - Applicable only when the battery voltage $< V_{DD} + \text{dropout}$
 - In general inefficient when the load current is large and the battery voltage and V_{DD} difference is big
 - Sometimes more efficient than DC-DC converter when the load current is very light and the battery voltage and V_{DD} difference is appropriate
 - Direct battery drive
 - Applicable only when the battery voltage is similar to V_{DD}
 - The most efficient when it is feasible (zero loss)
 - No single voltage regulation method is always the best!

Paper Contribution

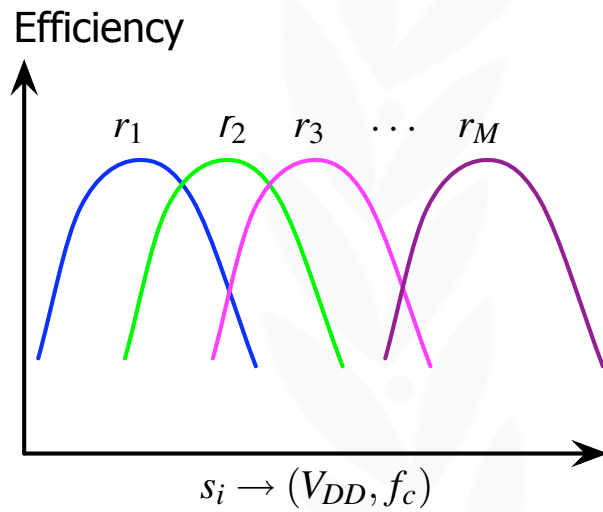- DRS: Dynamic regulator scheduling
 - Switch among heterogeneous voltage regulators dynamically for the best efficiency





(a) Heterogeneous voltage regulators

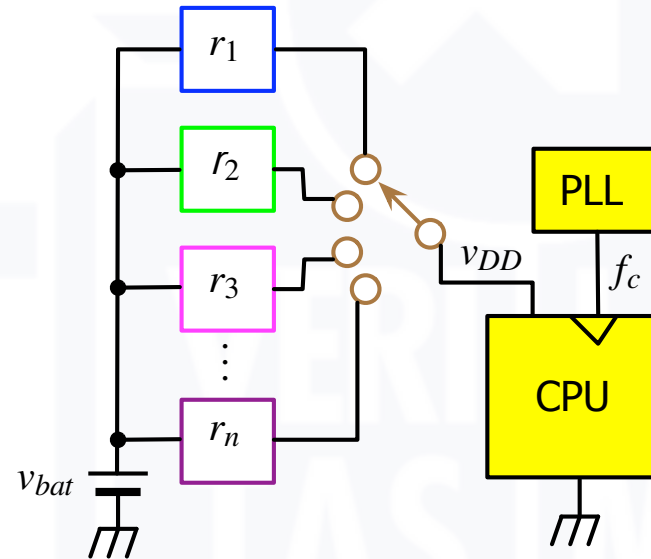

(b) DRS

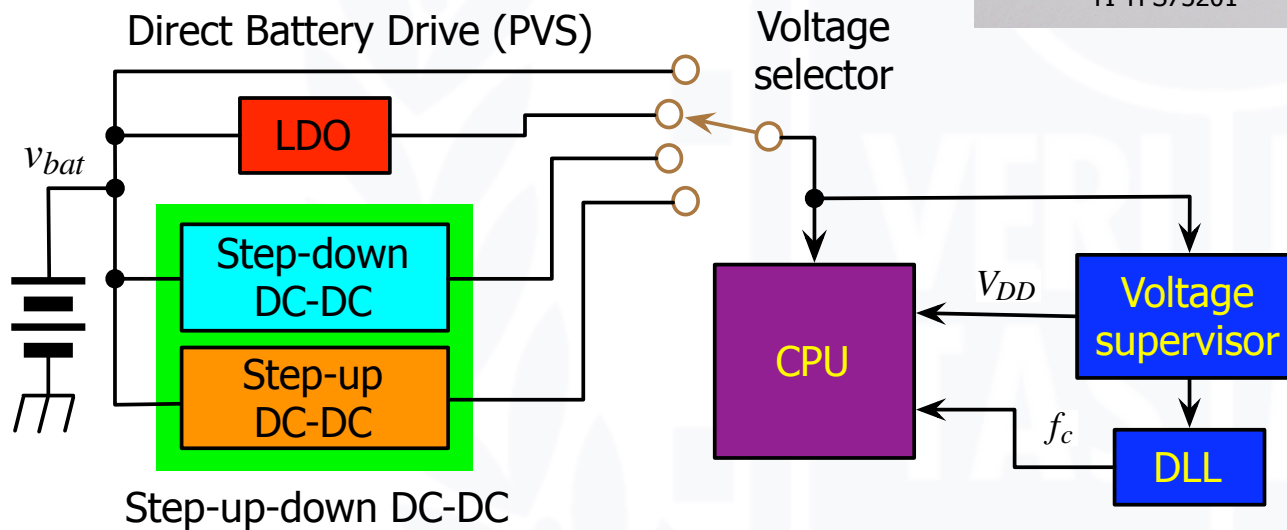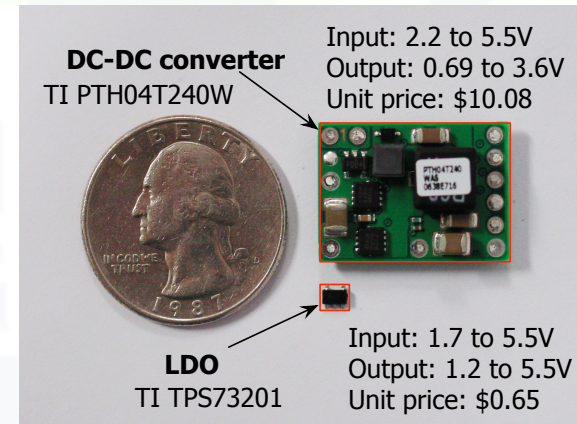Problem Statement

- Is DRS a practical approach?
 - YES!
 - Adding an LDO and a voltage switch is not that expensive
 - DRS is an affordable method



DRS Cost Function

- Characterization of the cost function of the power consumption of the system:

$$P(V_{bat}, S_j)$$

v_{bat} (V)	Clock frequency (MHz)							
	8	7	6	5	4	3	2	1
3.3	13.11	10.81	8.83	7.00	5.61	5.25	4.68	4.02
3.2	13.55	10.48	8.56	6.92	5.54	5.09	4.54	3.90
3.1	12.69	10.15	8.30	6.71	5.47	4.93	4.40	3.78
3.0	11.83	9.82	8.03	6.49	5.32	4.77	4.26	3.66
2.9	14.30	10.10	7.76	6.27	5.15	4.61	4.11	3.53
2.8	14.26	9.41	7.49	6.06	4.97	4.46	3.97	3.41
2.7	14.22	8.76	7.22	5.84	4.79	4.30	3.83	3.29
2.6	14.18	10.94	7.39	5.62	4.61	4.14	3.69	3.17
2.5	14.14	10.90	6.86	5.41	4.44	3.98	3.55	3.05
2.4	14.11	10.85	6.35	5.19	4.26	3.82	3.41	2.93
2.3	14.08	10.81	8.25	5.27	4.08	3.66	3.26	2.80
2.2	14.05	10.77	8.21	4.87	3.90	3.50	3.12	2.68
2.1	14.02	10.74	8.16	4.48	3.73	3.34	2.98	2.56
2.0	14.00	10.70	8.12	6.11	3.73	3.30	2.89	2.44
1.9	13.99	10.68	8.08	6.07	3.43	3.05	2.69	2.29
1.8	13.98	10.65	8.04	6.02	3.14	2.81	2.50	2.14

DC-DC


PVS

LDO




Experimental Results

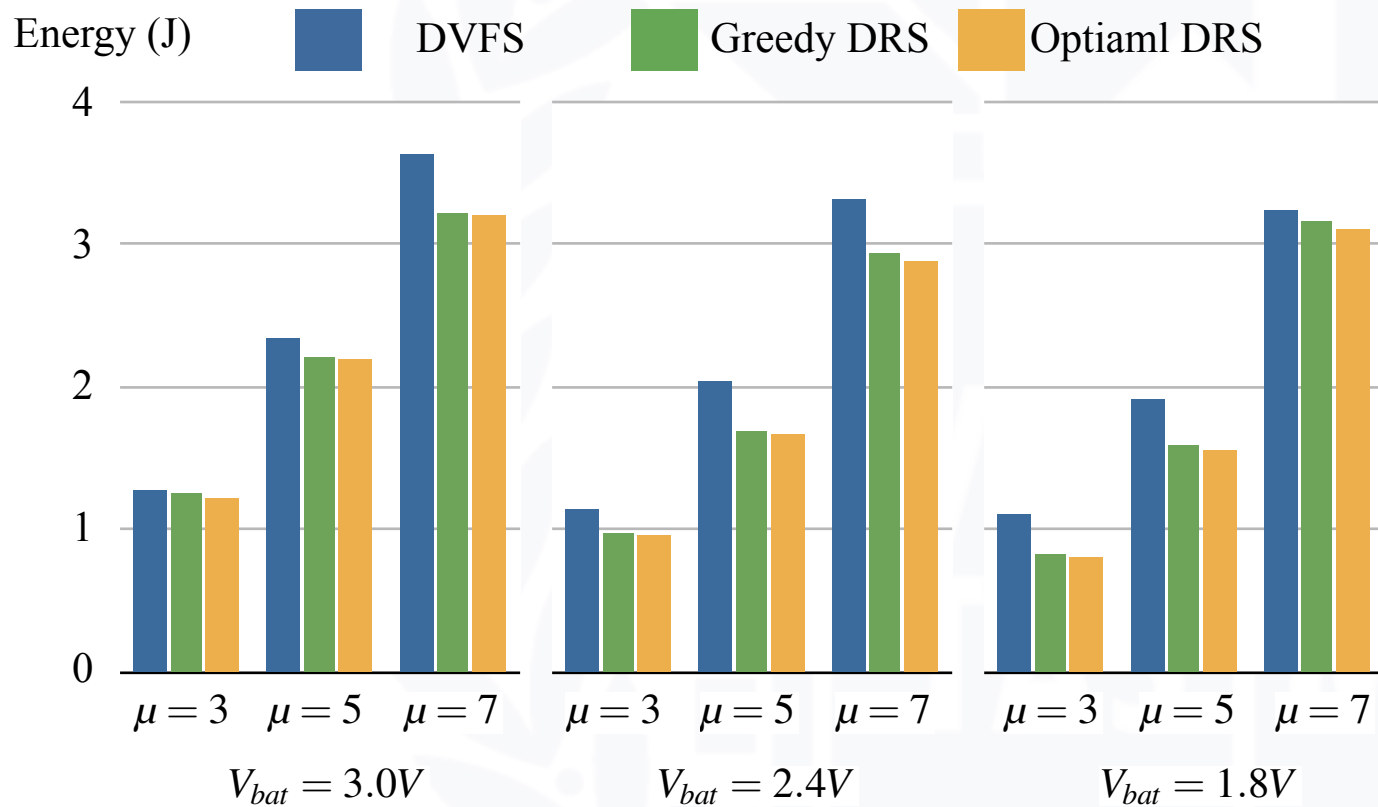- Energy consumption of optimal DRS, greedy DRS and conventional DVFS with $N = 40$ and $\lambda^{-1} = 10$ sec




Experimental Results

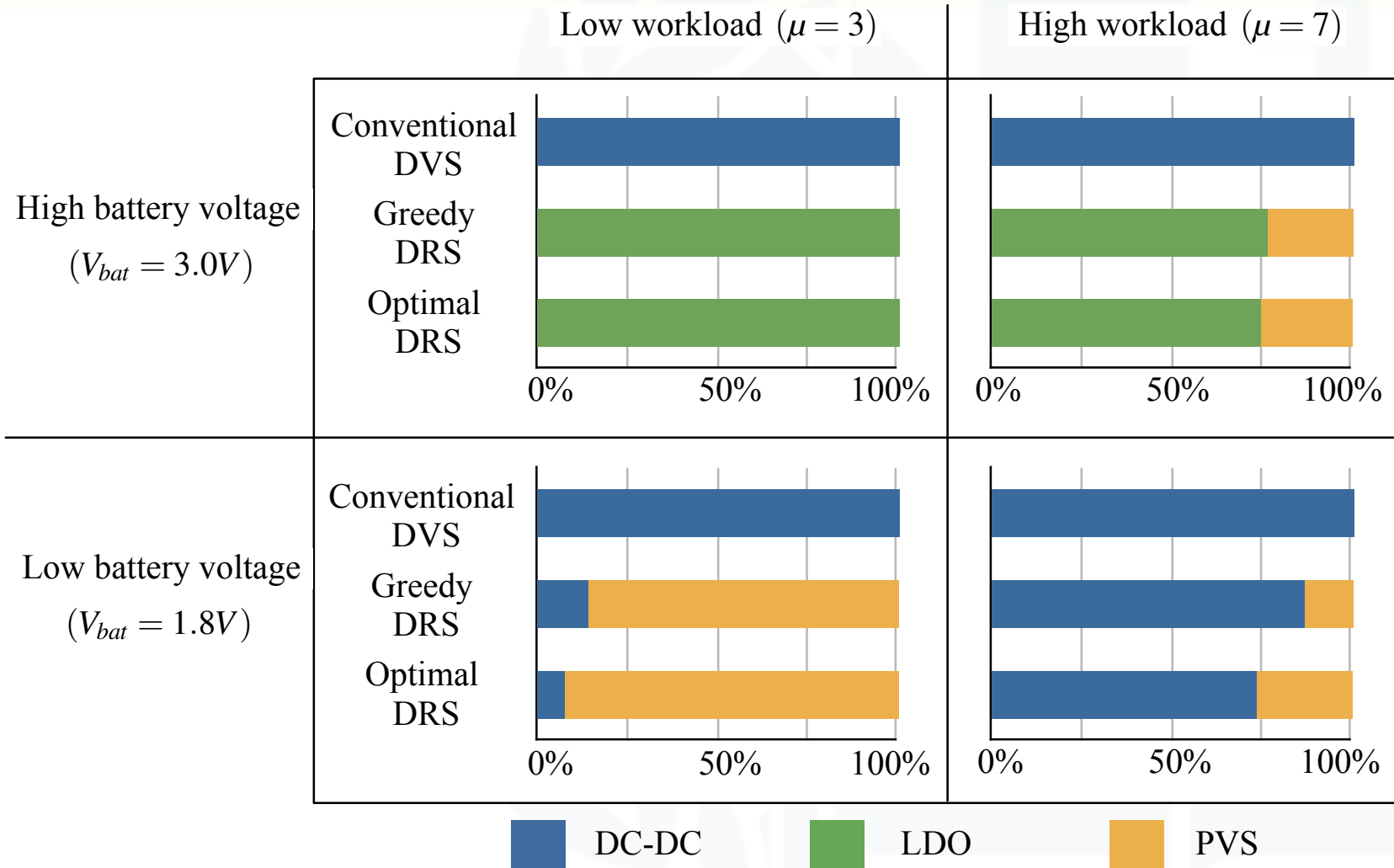Relative utilization of DC-DC and LDO regulators and PVS



Experimental Results

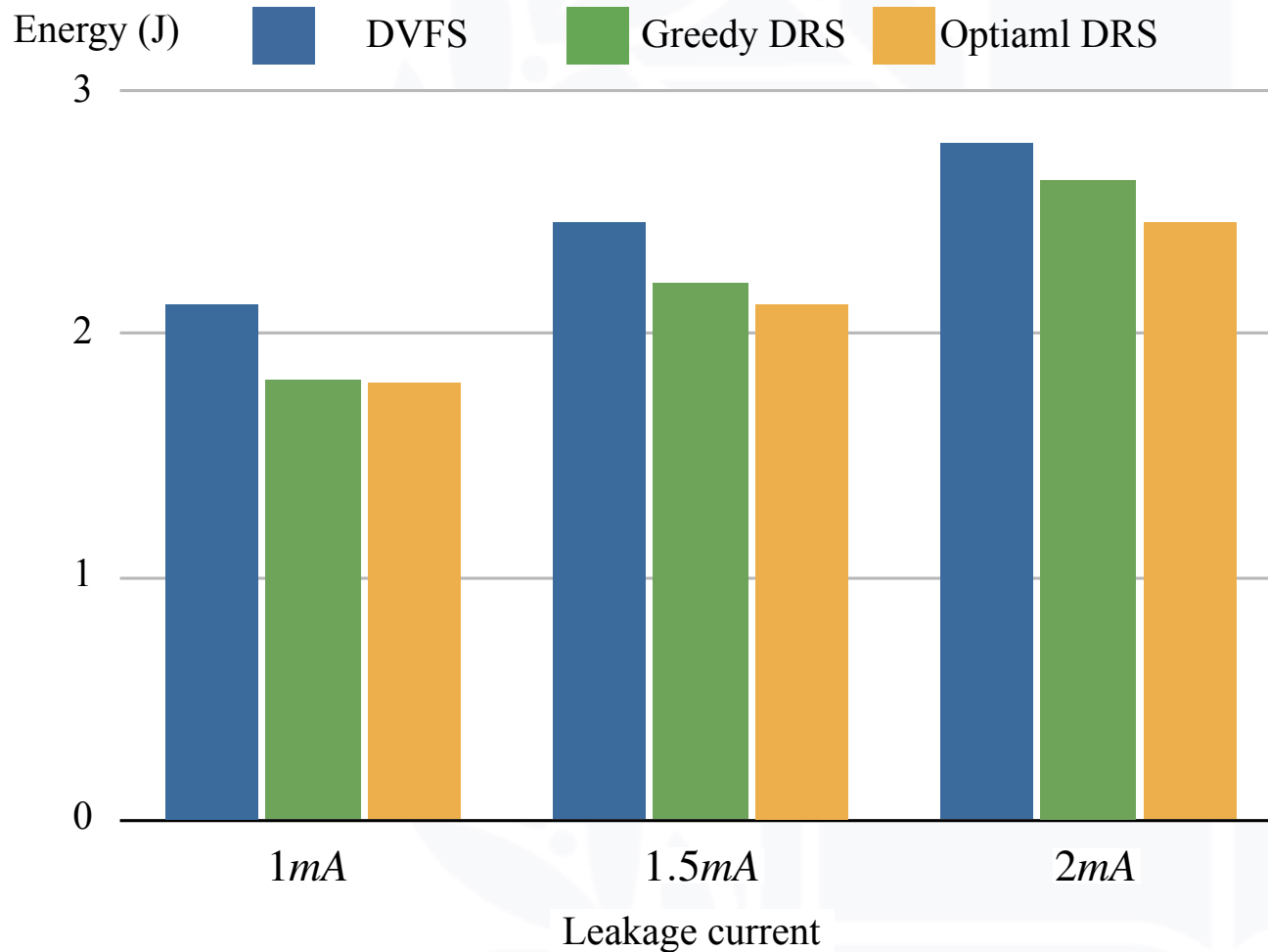- Energy consumption by the leakage power portion when $N = 40$, $\mu = 5$ sec and $\lambda^{-1} = 10$ sec.



Conclusions

- We introduced a new high-level low-power technique called DRS (Dynamic voltage regulator scheduling)
 - Joint regulator scheduling and the DVS scaling factor decision
- Load drive from multiple heterogeneous voltage regulators including the direct drive method (PVS)
- The greedy DRS:
 - Additional final regulator selection
 - 5.4% to 14.6% energy reduction
- The optimal DRS:
 - Simultaneous optimization of DVFS and regulator selection
 - 11.5% to 15.5% energy reduction
- DRS continues to perform well with a CPU with more leakage power consumption