

# Digital Logic Design

4190.201.001

2010 Spring Semester

## 6. Case Studies in Combinational Logic Design

**Naehyuck Chang**  
Dept. of EECS/CSE  
Seoul National University  
[naehyuck@snu.ac.kr](mailto:naehyuck@snu.ac.kr)



# Combinational logic design case studies

- General design procedure
- Case studies
  - BCD to 7-segment display controller
  - Logical function unit
  - Process line controller
  - Calendar subsystem
- Arithmetic circuits
  - Integer representations
  - Addition/subtraction
  - Arithmetic/logic units





# General design procedure for combinational logic

- Step 1. Understand the problem
  - What is the circuit supposed to do?
  - Write down inputs (data, control) and outputs
  - Draw block diagram or other picture
- Step 2. Formulate the problem using a suitable design representation
  - Truth table or waveform diagram are typical
  - May require encoding of symbolic inputs and outputs
- Step 3. Choose implementation target
  - ROM, PAL, PLA
  - Mux, decoder and OR-gate
  - Discrete gates
- Step 4. Follow implementation procedure
  - K-maps for two-level, multi-level
  - Design tools and hardware description language (e.g., Verilog)


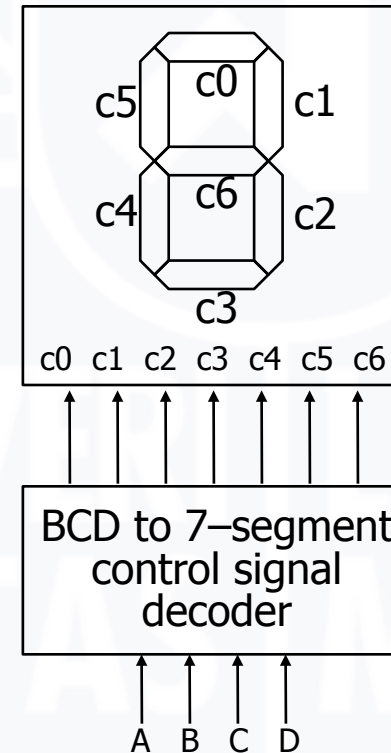 
# BCD to 7-segment display controller

- Understanding the problem
  - input is a 4 bit bcd digit (A, B, C, D)
  - output is the control signals for the display (7 outputs C0 – C6)
- Block diagram



# Formalize the problem

- Truth table
  - Show don't cares
- Choose implementation target
  - If ROM, we are done
  - Don't cares imply PAL/PLA may be attractive
- Follow implementation procedure
  - Minimization using K-maps

A	B	C	D	C0	C1	C2	C3	C4	C5	C6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	—	—	—	—	—	—	—	—
1	1	—	—	—	—	—	—	—	—	—



# Implementation as minimized sum-of-products

- 15 unique product terms when minimized individually

		A		
	1	0	X	1
	0	1	X	1
C	1	1	X	X
	1	1	X	X
		B		

		A		
	1	1	X	1
	1	0	X	1
C	1	1	X	X
	1	0	X	X
		B		

		A		
	1	1	X	1
	1	1	X	1
C	1	1	X	X
	0	1	X	X
		B		

		A		
	1	0	X	1
	0	1	X	0
C	1	0	X	X
	1	1	X	X
		B		

		A		
	1	0	X	1
	0	0	X	0
C	0	0	X	X
	1	1	X	X
		B		

		A		
	1	1	X	1
	0	1	X	1
C	0	0	X	X
	0	1	X	X
		B		

		A		
	0	1	X	1
	0	1	X	1
C	1	0	X	X
	1	1	X	X
		B		

$$\begin{aligned}
 C0 &= A + B D + C + B' D' \\
 C1 &= C' D' + C D + B' \\
 C2 &= B + C' + D \\
 C3 &= B' D' + C D' + B C' D + B' C \\
 C4 &= B' D' + C D' \\
 C5 &= A + C' D' + B D' + B C' \\
 C6 &= A + C D' + B C' + B' C
 \end{aligned}$$



# Implementation as minimized S-o-P (cont'd)

- Can do better
  - 9 unique product terms (instead of 15)
  - Share terms among outputs
  - Each output not necessarily in minimized form

		A			
C2		1	1	X	1
	D	1	1	X	1
	C	1	1	X	X
		0	1	X	X
		B			


		A			
C2		1	1	X	1
	D	1	1	X	1
	C	1	1	X	X
		0	1	X	X
		B			

$$\begin{aligned}
 C0 &= A + B D + C + B' D' \\
 C1 &= C' D' + C D + B' \\
 C2 &= B + C' + D \\
 C3 &= B' D' + C D' + B C' D + B' C \\
 C4 &= B' D' + C D' \\
 C5 &= A + C' D' + B D' + B C' \\
 C6 &= A + C D' + B C' + B' C
 \end{aligned}$$

$$\begin{aligned}
 C0 &= B C' D + C D + B' D' + B C D' + A \\
 C1 &= B' D + C' D' + C D + B' D' \\
 C2 &= B' D + B C' D + C' D' + C D + B C D' \\
 C3 &= B C' D + B' D + B' D' + B C D' \\
 C4 &= B' D' + B C D' \\
 C5 &= B C' D + C' D' + A + B C D' \\
 C6 &= B' C + B C' + B C D' + A
 \end{aligned}$$



# PLA implementation

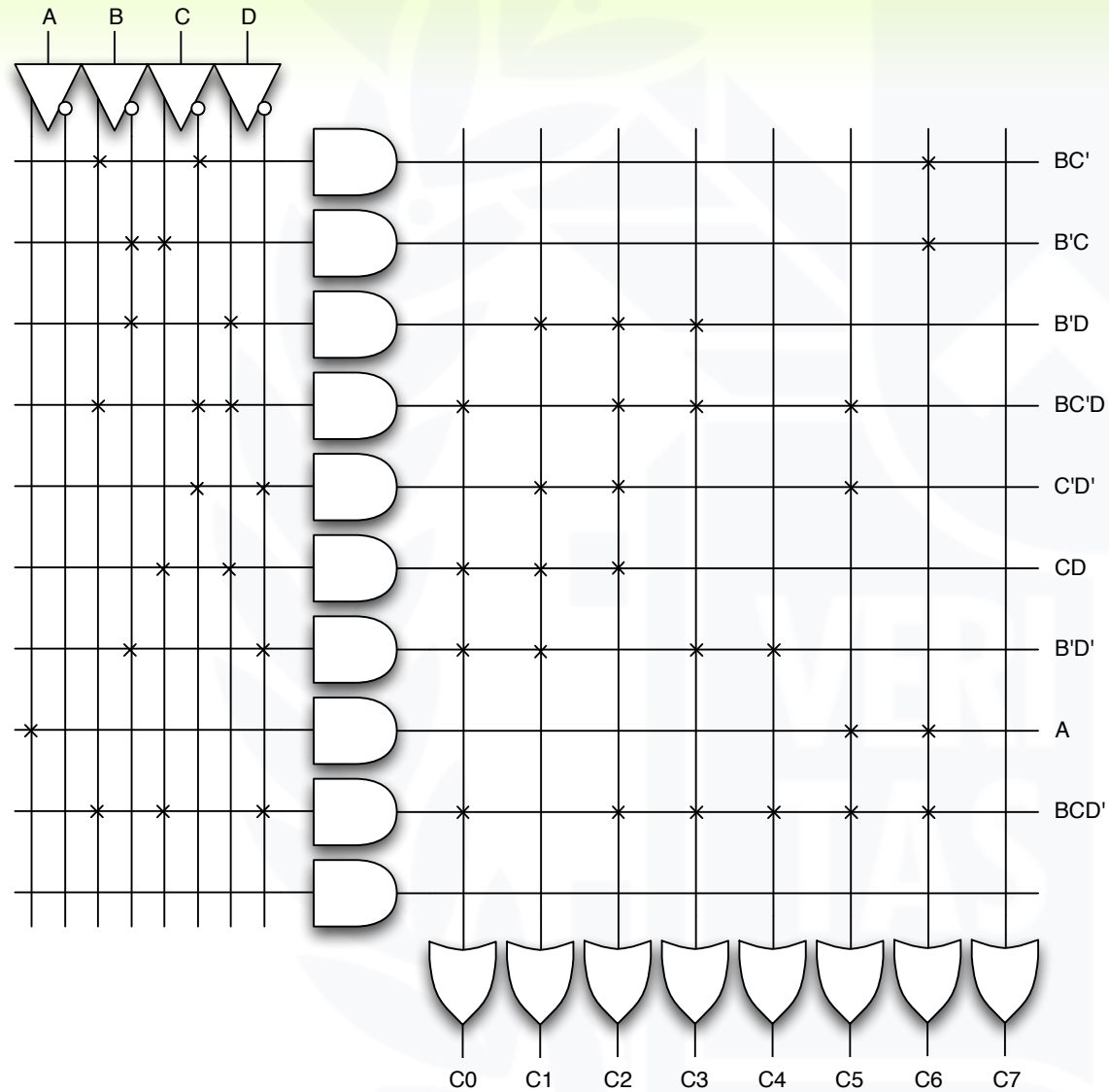



# PAL implementation vs. Discrete gate implementation

- Limit of 4 product terms per output
  - Decomposition of functions with larger number of terms
  - Do not share terms in PAL anyway (although there are some with some shared terms)

$$C2 = B + C' + D$$

$$C2 = B' D + B C' D + C' D' + C D + B C D'$$

$$C2 = B' D + B C' D + C' D' + W$$

$$W = C D + B C D'$$

need another input and another output

- Decompose into multi-level logic (hopefully with CAD support)
  - Find common sub-expressions among functions

$$C0 = C3 + A' B X' + A D Y$$

$$C1 = Y + A' C5' + C' D' C6$$

$$C2 = C5 + A' B' D + A' C D$$

$$C3 = C4 + B D C5 + A' B' X'$$

$$C4 = D' Y + A' C D'$$

$$C5 = C' C4 + A Y + A' B X$$

$$C6 = A C4 + C C5 + C4' C5 + A' B' C$$

$$X = C' + D'$$

$$Y = B' C'$$



# Logical function unit

- Multi-purpose function block
  - 3 control inputs to specify operation to perform on operands
  - 2 data inputs for operands
  - 1 output of the same bit-width as operands

C0	C1	C2	Function	Comments
0	0	0	1	always 1
0	0	1	$A + B$	logical OR
0	1	0	$(A \cdot B)'$	logical NAND
0	1	1	$A \text{ xor } B$	logical xor
1	0	0	$A \text{ xnor } B$	logical xnor
1	0	1	$A \cdot B$	logical AND
1	1	0	$(A + B)'$	logical NOR
1	1	1	0	always 0


3 control inputs: C0, C1, C2  
2 data inputs: A, B  
1 output: F



# Formalize the problem



C0	C1	C2	A	B	F
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0
1	1	1	1	0	0
1	1	1	1	1	0

 Choose implementation technology  
 5-variable K-map to discrete gates  
 multiplexor implementation



# 74LS247
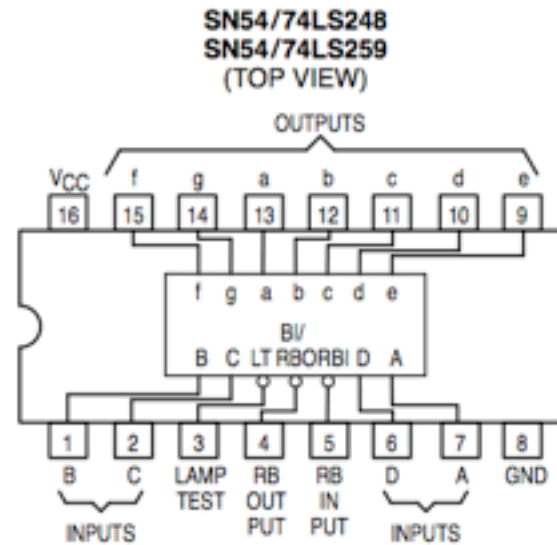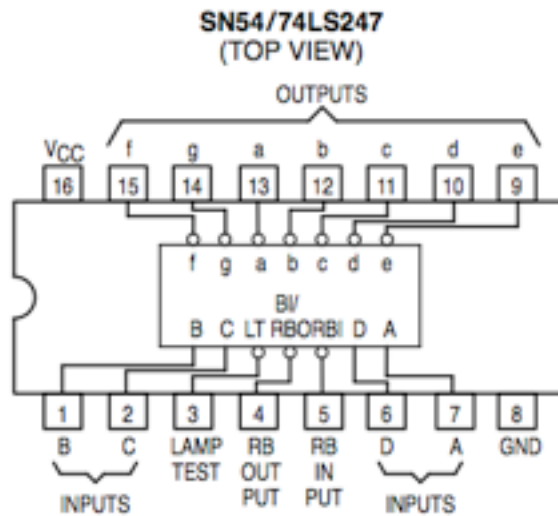
## SN54/74LS247 • SN54/74LS248 • SN54/74LS249




# Production line control

- Rods of varying length ( $\pm 10\%$ ) travel on conveyor belt
  - Mechanical arm pushes rods within spec ( $\pm 5\%$ ) to one side
  - Second arm pushes rods too long to other side
  - Rods that are too short stay on belt
  - 3 light barriers (light source + photocell) as sensors
  - Design combinational logic to activate the arms
- Understanding the problem
  - Inputs are three sensors
  - Outputs are two arm control signals
  - Assume sensor reads "1" when tripped, "0" otherwise
  - Call sensors A, B, C


 
# Sketch of problem

- Position of sensors
  - A to B distance = specification - 5%
  - A to C distance = specification + 5%



# Formalize the problem

- Truth table
  - Show don't cares

A	B	C	Function
0	0	0	do nothing
0	0	1	do nothing
0	1	0	do nothing
0	1	1	do nothing
1	0	0	too short
1	0	1	don't care
1	1	0	in spec
1	1	1	too long

Logic implementation now straightforward  
just use three 3-input AND gates

"too short" =  $AB'C'$   
(only first sensor tripped)

"in spec" =  $A B C'$   
(first two sensors tripped)

"too long" =  $A B C$   
(all three sensors tripped)



# Calendar subsystem

- Determine number of days in a month (to control watch display)
  - Used in controlling the display of a wrist-watch LCD screen
  - Inputs: month, leap year flag
  - Outputs: number of days
- Use software implementation to help understand the problem


```
integer number_of_days ( month, leap_year_flag) {  
    switch (month) {  
        case 1: return (31);  
        case 2: if (leap_year_flag == 1)  
                then return (29)  
                else return (28);  
  
        case 3: return (31);  
        case 4: return (30);  
        case 5: return (31);  
        case 6: return (30);  
        case 7: return (31);  
        case 8: return (31);  
        case 9: return (30);  
        case 10: return (31);  
        case 11: return (30);  
        case 12: return (31);  
        default: return (0);  
    }  
}
```




 
# Formalize the problem

- Encoding:
  - Binary number for month: 4 bits
  - 4 wires for 28, 29, 30, and 31  
one-hot – only one true at any time
- Block diagram:



month	leap	28	29	30	31
0000	–	–	–	–	–
0001	–	0	0	0	1
0010	0	1	0	0	0
0011	–	0	1	0	0
0100	–	0	0	1	0
0101	–	0	0	0	1
0110	–	0	0	1	0
0111	–	0	0	0	1
1000	–	0	0	0	1
1001	–	0	0	1	0
1010	–	0	0	0	1
1011	–	0	0	1	0
1100	–	0	0	0	1
1101	–	–	–	–	–
111–	–	–	–	–	–



# Choose implementation target and perform mapping

- Discrete gates

- $28 = m8' m4' m2 m1' leap'$

- $29 = m8' m4' m2 m1' leap$

- $30 = m8' m4 m1' + m8 m1$

- $31 = m8' m1 + m8 m1'$

- Can translate to S-o-P or P-o-S

month	leap	28	29	30	31
0000	-	-	-	-	-
0001	-	0	0	0	1
0010	0	1	0	0	0
0010	1	0	1	0	0
0011	-	0	0	0	1
0100	-	0	0	1	0
0101	-	0	0	0	1
0110	-	0	0	1	0
0111	-	0	0	0	1
1000	-	0	0	0	1
1001	-	0	0	1	0
1010	-	0	0	0	1
1011	-	0	0	1	0
1100	-	0	0	0	1
1101	-	-	-	-	-
111-	-	-	-	-	-



# Leap year flag

- Determine value of leap year flag given the year
  - For years after 1582 (Gregorian calendar reformation),
  - Leap years are all the years divisible by 4,
  - Except that years divisible by 100 are not leap years,
  - But years divisible by 400 are leap years.
- Encoding the year:
  - Binary – easy for divisible by 4, but difficult for 100 and 400 (not powers of 2)
  - BCD – easy for 100, but more difficult for 4, what about 400?
- Parts:
  - Construct a circuit that determines if the year is divisible by 4
  - Construct a circuit that determines if the year is divisible by 100
  - Construct a circuit that determines if the year is divisible by 400
  - Combine the results of the previous three steps to yield the leap year flag



# Activity: divisible-by-4 circuit

- BCD coded year
  - YM8 YM4 YM2 YM1 – YH8 YH4 YH2 YH1 – YT8 YT4 YT2 YT1 – YO8 YO4 YO2 YO1
- Only need to look at low-order two digits of the year  
all years ending in 00, 04, 08, 12, 16, 20, etc. are divisible by 4
  - If tens digit is even, then divisible by 4 if ones digit is 0, 4, or 8
  - If tens digit is odd, then divisible by 4 if the ones digit is 2 or 6.
- Translates into the following Boolean expression  
(where YT1 is the year's tens digit low-order bit,  
YO8 is the high-order bit of year's ones digit, etc.):
  - $YT1' (YO8' YO4' YO2' YO1' + YO8' YO4 YO2' YO1' + YO8 YO4' YO2' YO1' )$   
 $+ YT1 (YO8' YO4' YO2 YO1' + YO8' YO4 YO2 YO1' )$
- Digits with values of 10 to 15 will never occur, simplify further to yield:
  - $YT1' YO2' YO1' + YT1 YO2 YO1'$



# Divisible-by-100 and divisible-by-400 circuits

- Divisible-by-100 just requires checking that all bits of two low-order digits are all 0:
  - $YT8' YT4' YT2' YT1' \bullet YO8' YO4' YO2' YO1'$
- Divisible-by-400 combines the divisible-by-4 (applied to the thousands and hundreds digits) and divisible-by-100 circuits
  - $(YM1' YH2' YH1' + YM1 YH2 YH1') \bullet (YT8' YT4' YT2' YT1' \bullet YO8' YO4' YO2' YO1' )$




# Combining to determine leap year flag

- Label results of previous three circuits: D4, D100, and D400

$$\begin{aligned}\text{leap\_year\_flag} &= D4 (D100 \bullet D400')' \\ &= D4 \bullet D100' + D4 \bullet D400 \\ &= D4 \bullet D100' + D400\end{aligned}$$



# Implementation of leap year flag

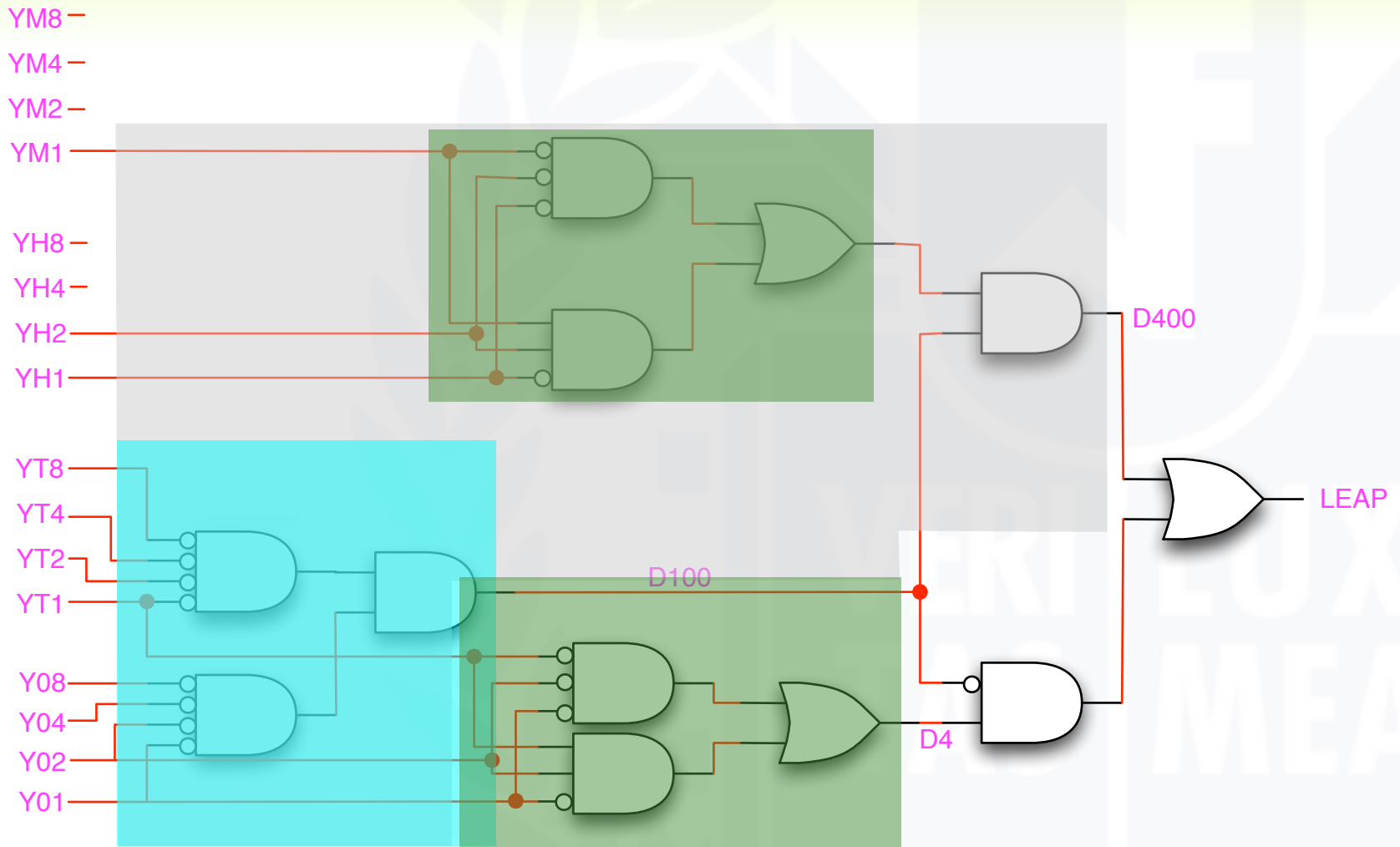

# Arithmetic circuits

- Excellent examples of combinational logic design
- Time vs. space trade-offs
  - Doing things fast may require more logic and thus more space
  - Example: carry lookahead logic
- Arithmetic and logic units
  - General-purpose building blocks
  - Critical components of processor datapaths
  - Used within most computer instructions





# Number systems

- Representation of positive numbers is the same in most systems
- Major differences are in how negative numbers are represented
- Representation of negative numbers come in three major schemes
  - Sign and magnitude
  - 1s complement
  - 2s complement
- Assumptions
  - We'll assume a 4 bit machine word
  - 16 different values can be represented
  - Roughly half are positive, half are negative




# Sign and magnitude

- One bit dedicate to sign (positive or negative)
  - Sign: 0 = positive (or zero), 1 = negative
- Rest represent the absolute value or magnitude
  - Three low order bits: 0 (000) thru 7 (111)
- Range for n bits
  - $\pm 2^{n-1} - 1$  (two representations for 0)
- Cumbersome addition/subtraction
  - Must compare magnitudes to determine sign of result

$$0\ 100 = +4$$

$$1\ 100 = -4$$

 

# 1s complement

- If N is a positive number, then the negative of N (its 1s complement or N' ) is  $N' = (2^n - 1) - N$
- Example: 1s complement of 7

$$2^4 = 10000$$

$$1 = 00001$$

$$2^4 - 1 = \underline{1111}$$

$$7 = \underline{0111}$$


$$1000 = -7 \text{ in 1s complement form}$$

- Shortcut: simply compute bit-wise complement ( 0111  $\rightarrow$  1000 )


 
# 1s complement (cont'd)

- Subtraction implemented by 1s complement and then addition
- Two representations of 0
  - Causes some complexities in addition
- High-order bit can act as sign bit




# 2s complement

- 1s complement with negative numbers shifted one position clockwise
  - Only one representation for 0
  - One more negative number than positive numbers
  - High-order bit can act as sign bit

$$0\ 100 = +4$$

$$1\ 100 = -4$$

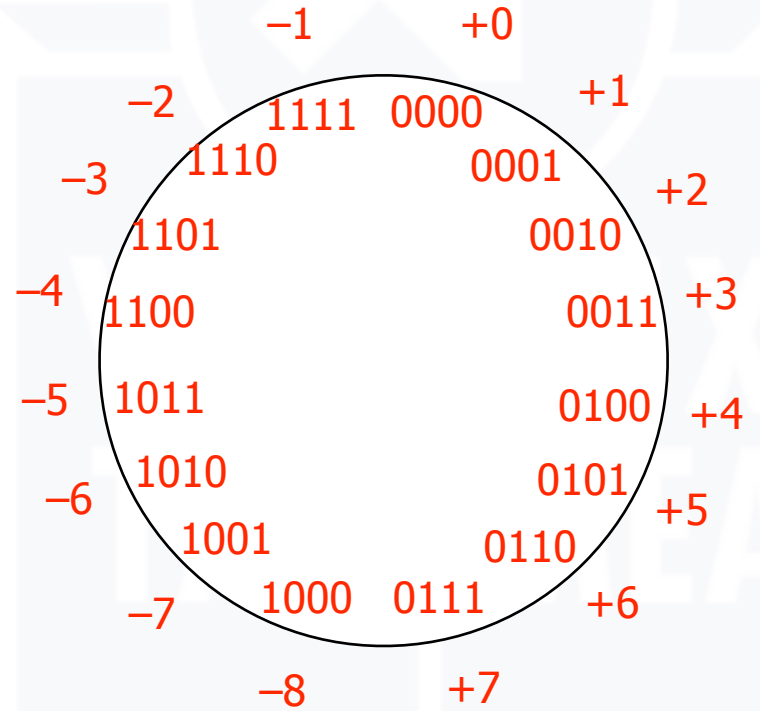

# 2s complement (cont'd)

- If N is a positive number, then the negative of N (its 2s complement or  $N^*$ ) is  $N^* = 2^n - N$

- Example: 2s complement of 7

$$\begin{array}{r} 2^4 = 10000 \\ \text{subtract } 7 = \underline{0111} \\ 1001 = \text{repr. of } -7 \end{array}$$

- Example: 2s complement of -7

$$\begin{array}{r} 2^4 = 10000 \\ \text{subtract } -7 = \underline{1001} \\ 0111 = \text{repr. of } 7 \end{array}$$

- Shortcut: 2s complement = bit-wise complement + 1

- $0111 \rightarrow 1000 + 1 \rightarrow 1001$  (representation of -7)

- $1001 \rightarrow 0110 + 1 \rightarrow 0111$  (representation of 7)



# 2s complement addition and subtraction

- Simple addition and subtraction
  - Simple scheme makes 2s complement the virtually unanimous choice for integer number systems in computers

$$\begin{array}{r} 4 \quad 0100 \\ + 3 \quad 0011 \\ \hline 7 \quad 0111 \end{array} \qquad \begin{array}{r} -4 \quad 1100 \\ + (-3) \quad 1101 \\ \hline -7 \quad 11001 \end{array}$$

$$\begin{array}{r} 4 \quad 0100 \\ - 3 \quad 1101 \\ \hline 1 \quad 10001 \end{array} \qquad \begin{array}{r} -4 \quad 1100 \\ + 3 \quad 0011 \\ \hline -1 \quad 1111 \end{array}$$



# Why can the carry-out be ignored?

- Can't ignore it completely
  - Needed to check for overflow (see next two slides)
- When there is no overflow, carry-out may be true but can be ignored

–  $M + N$  when  $N > M$ :

$$M^* + N = (2n - M) + N = 2n + (N - M)$$

ignoring carry-out is just like subtracting  $2n$

–  $M + -N$  where  $N + M \leq 2n-1$

$$(-M) + (-N) = M^* + N^* = (2n - M) + (2n - N) = 2n - (M + N) + 2n$$



ignoring the carry, it is just the 2s complement representation for  $-(M + N)$




  
# Overflow in 2s complement addition/subtraction

- Overflow conditions
  - Add two positive numbers to get a negative number
  - Add two negative numbers to get a positive number



# Overflow conditions

- Overflow when carry into sign bit position is not equal to carry-out

$$\begin{array}{r} 5 \\ 3 \\ \hline -8 \\ \text{overflow} \end{array}$$

$$\begin{array}{r} 0111 \\ 0101 \\ \hline 0011 \\ 1000 \end{array}$$

$$\begin{array}{r} -7 \\ -2 \\ \hline 7 \\ \text{overflow} \end{array}$$

$$\begin{array}{r} 1000 \\ 1001 \\ \hline 1110 \\ 10111 \end{array}$$

$$\begin{array}{r} 5 \\ 2 \\ \hline 7 \\ \text{no overflow} \end{array}$$

$$\begin{array}{r} 0000 \\ 0101 \\ \hline 0010 \\ 0111 \end{array}$$

$$\begin{array}{r} -3 \\ -5 \\ \hline -8 \\ \text{no overflow} \end{array}$$

$$\begin{array}{r} 1111 \\ 1101 \\ \hline 1011 \\ 11000 \end{array}$$



# Circuits for binary addition

- Half adder (add 2 1-bit numbers)
  - $\text{Sum} = A_i' B_i + A_i B_i' = A_i \text{ xor } B_i$
  - $\text{Cout} = A_i B_i$
- Full adder (carry-in to cascade for multi-bit adders)
  - $\text{Sum} = C_i \text{ xor } A \text{ xor } B$
  - $\text{Cout} = B C_i + A C_i + A B = C_i (A + B) + A B$

Ai	Bi	Sum	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1


Ai	Bi	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



# Full adder implementations

- Standard approach


- 6 gates
- 2 XORs, 2 ANDs, 2 ORs

 

- Alternative implementation


- 5 gates
- Half adder is an XOR gate and AND gate
- 2 XORs, 2 ANDs, 1 OR
 
$$Cout = A B + Cin (A \text{ xor } B) = A B + B Cin + A Cin$$




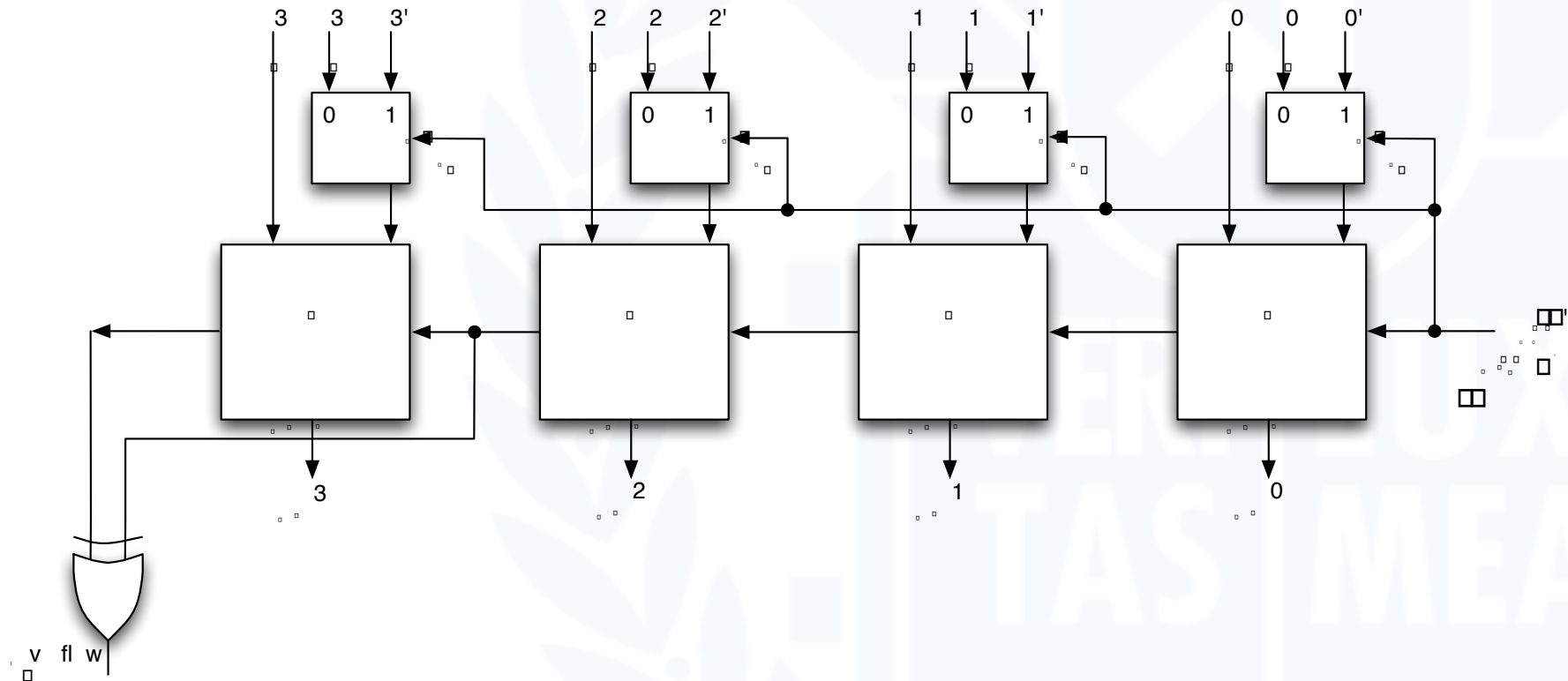
# Adder/subtractor

- Use an adder to do subtraction thanks to 2s complement representation
  - $A - B = A + (-B) = A + B' + 1$
  - Control signal selects B or 2s complement of B



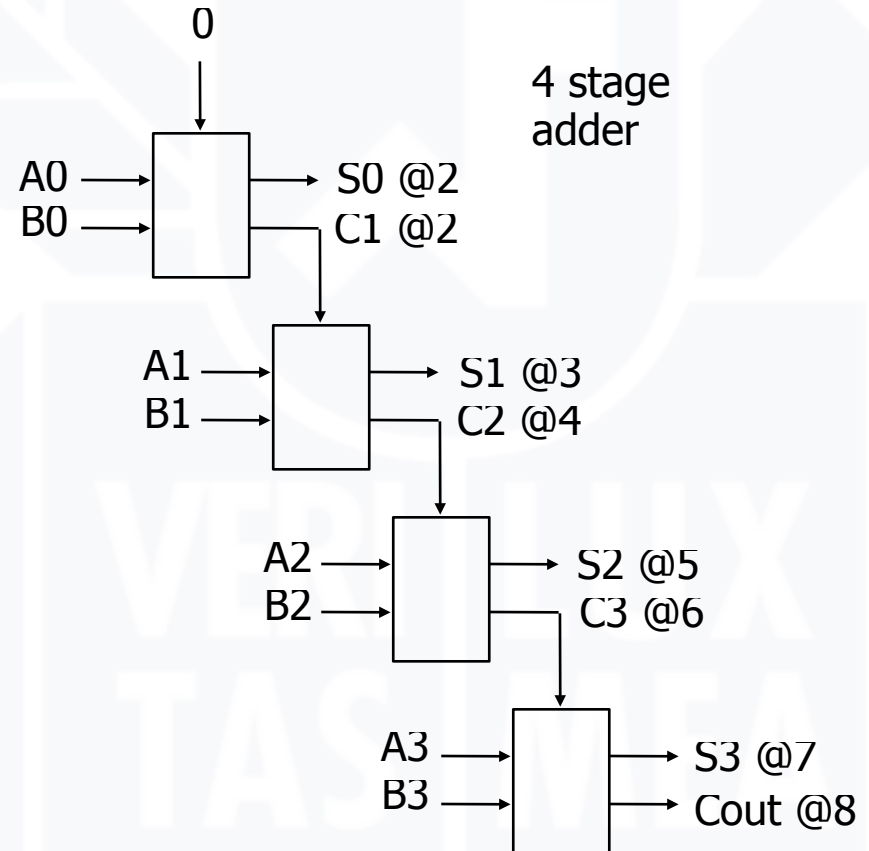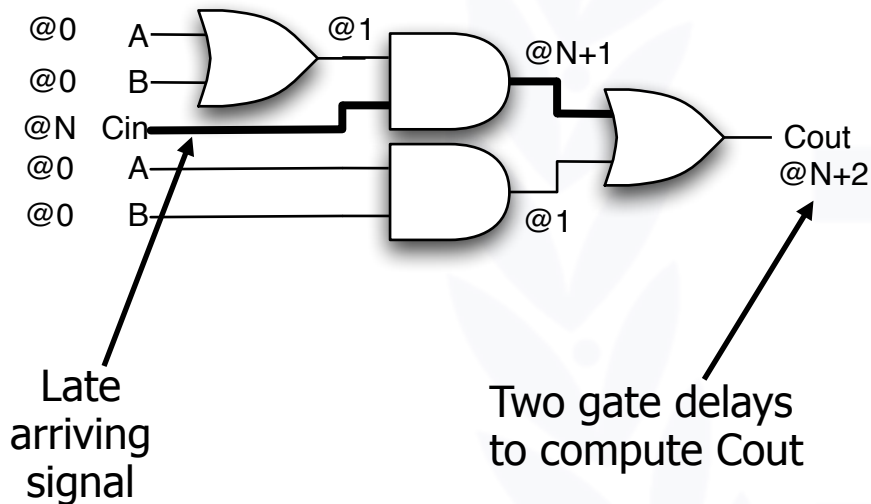
# Ripple-carry adders

- Critical delay
  - The propagation of carry from low to high order stages


 
# Ripple-carry adders (cont'd)

- Critical delay
  - The propagation of carry from low to high order stages
  - 1111 + 0001 is the worst case addition
  - Carry must propagate through all bits



# Carry-lookahead logic

- Carry generate:  $G_i = A_i B_i$ 
  - Must generate carry when  $A = B = 1$
- Carry propagate:  $P_i = A_i \text{ xor } B_i$ 
  - Carry-in will equal carry-out here
- Sum and Cout can be re-expressed in terms of generate/propagate:
  - $S_i = A_i \text{ xor } B_i \text{ xor } C_i$   
 $= P_i \text{ xor } C_i$
  - $C_{i+1} = A_i B_i + A_i C_i + B_i C_i$   
 $= A_i B_i + C_i (A_i + B_i)$   
 $= A_i B_i + C_i (A_i \text{ xor } B_i)$   
 $= G_i + C_i P_i$










# Carry-lookahead logic (cont'd)

- Re-express the carry logic as follows:
  - $C_1 = G_0 + P_0 C_0$
  - $C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$
  - $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$
  - $C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$
- Each of the carry equations can be implemented with two-level logic
  - All inputs are now directly derived from data inputs and not from intermediate carries
  - This allows computation of all sum outputs to proceed in parallel



    
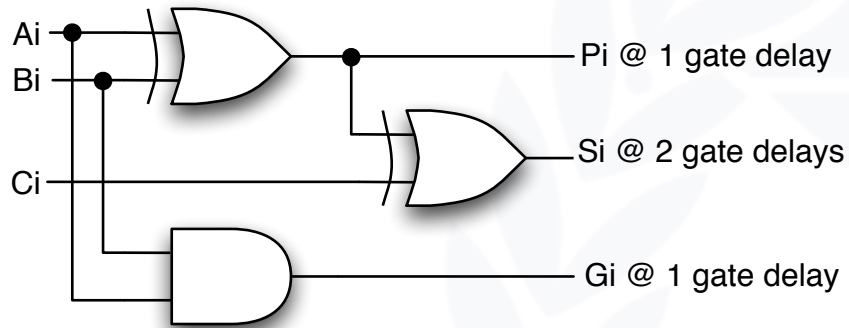
# Carry-lookahead implementation

- Adder with propagate and generate outputs


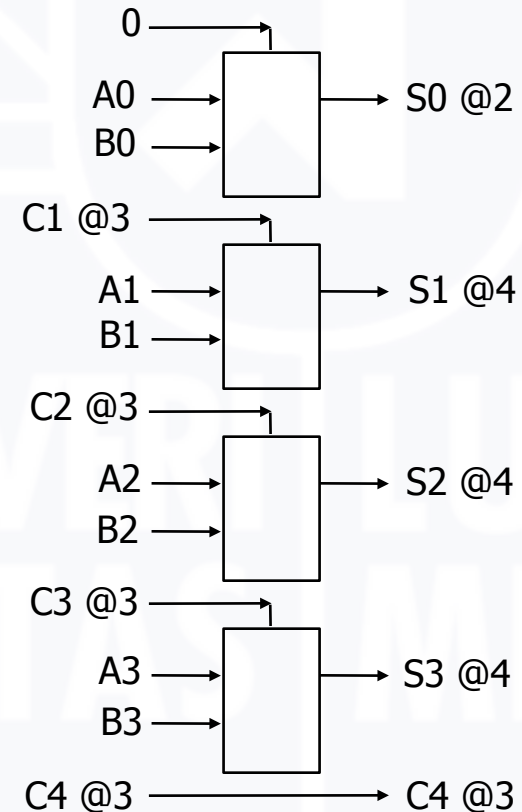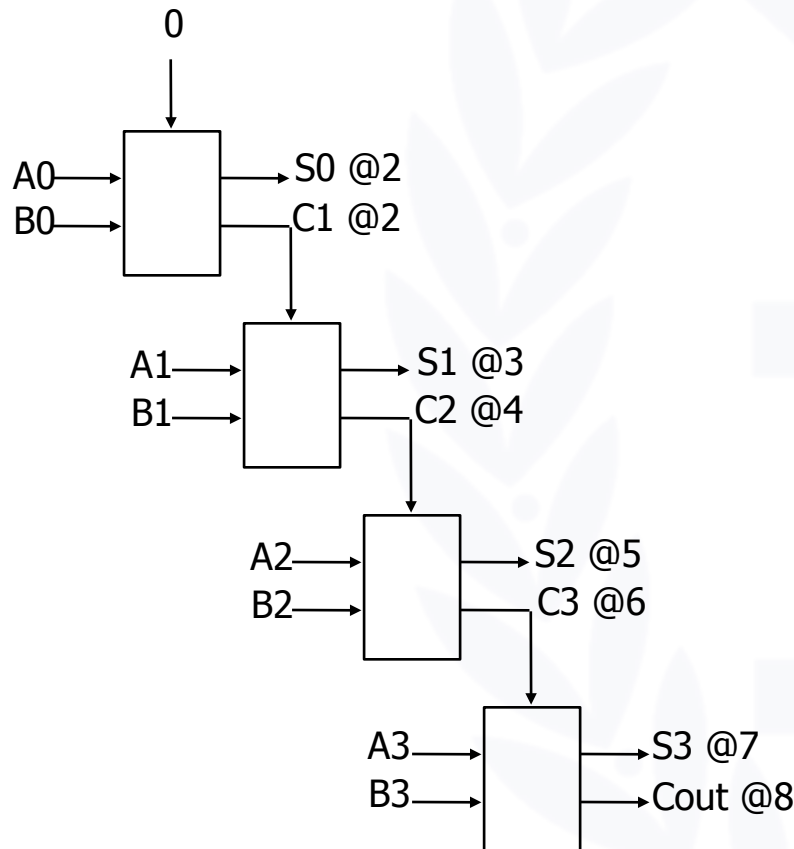
# Carry-lookahead implementation (cont'd)

- Carry-lookahead logic generates individual carries
  - Sums computed much more quickly in parallel
  - However, cost of carry logic increases with more stages




# Carry-lookahead adder with cascaded carry-lookahead logic

- Carry-lookahead adder
  - 4 four-bit adders with internal carry lookahead
  - Second level carry lookahead unit extends lookahead to 16 bits


$$G = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$$

$$P = P_3 P_2 P_1 P_0$$

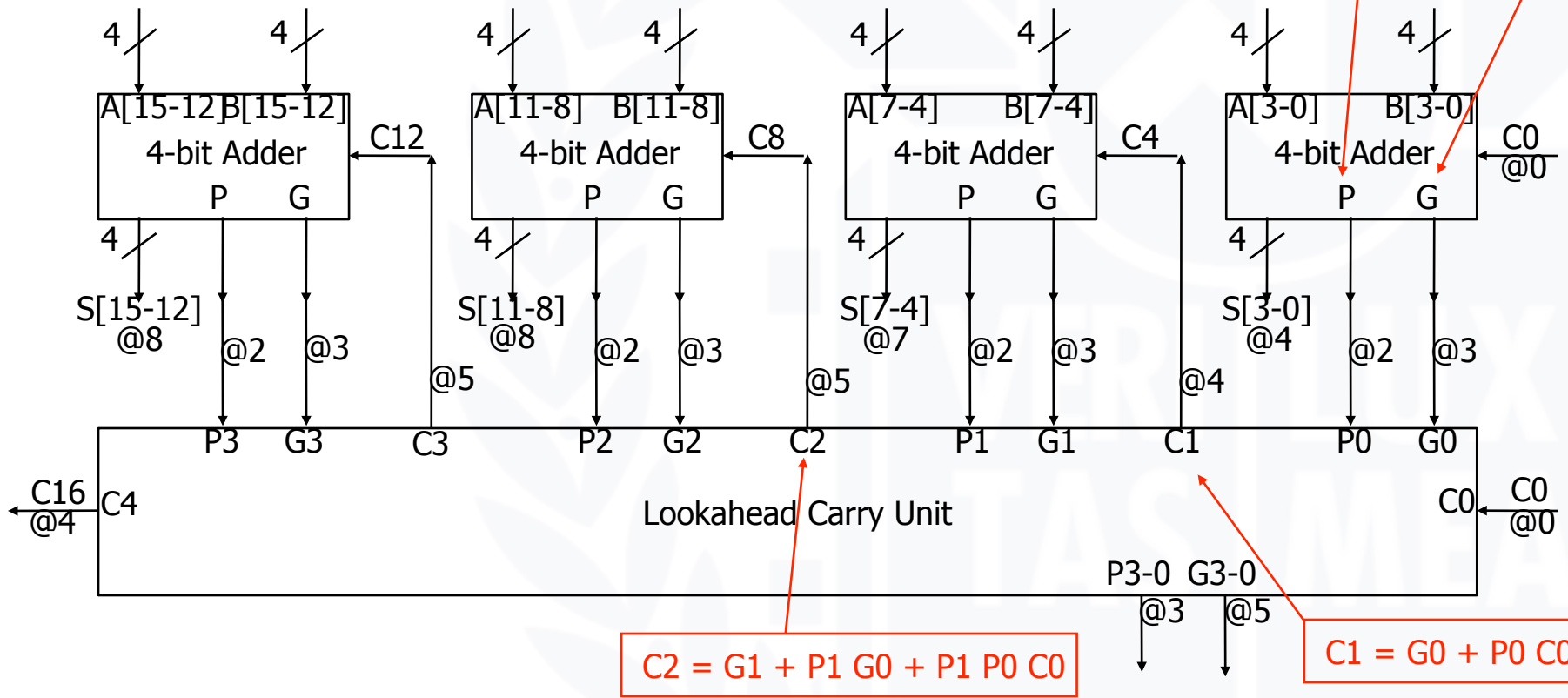
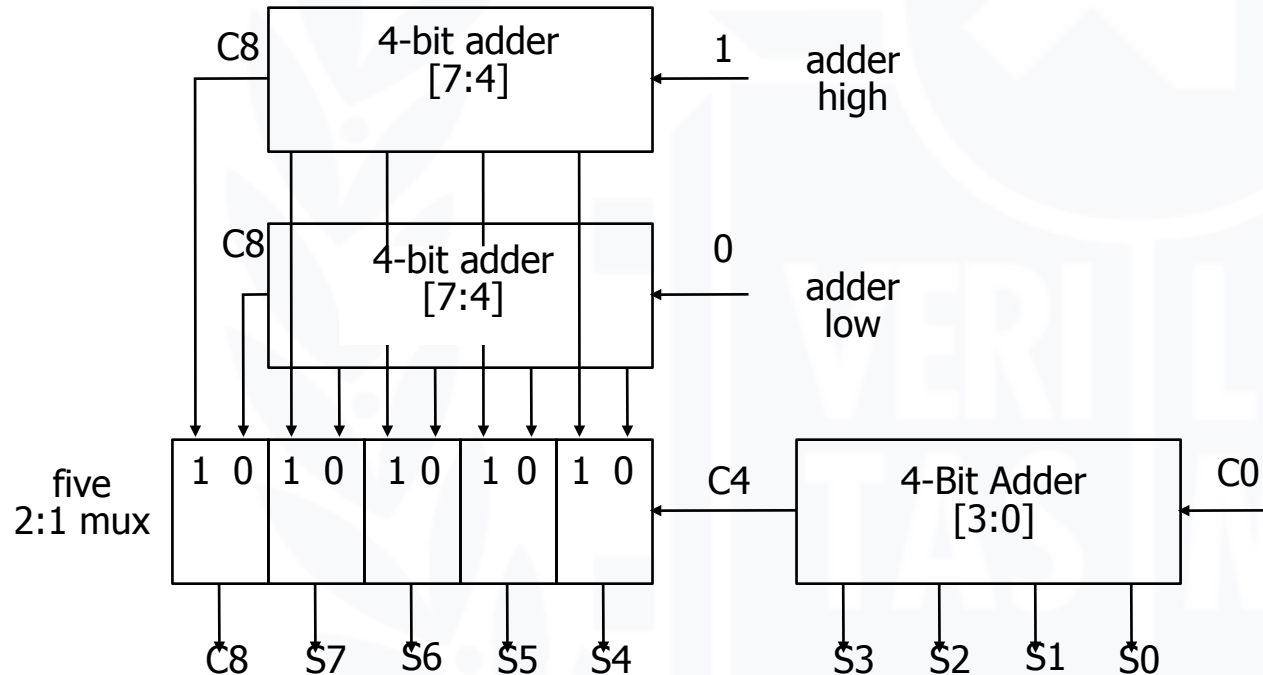
# Carry-select adder

- Redundant hardware to make carry calculation go faster
  - Compute two high-order sums in parallel while waiting for carry-in
  - One assuming carry-in is 0 and another assuming carry-in is 1
  - Select correct result once carry-in is finally computed



# Arithmetic logic unit design specification

## M = 0, logical bitwise operations

S1	S0	Function	Comment
0	0	$F_i = A_i$	input $A_i$ transferred to output
0	1	$F_i = \text{not } A_i$	complement of $A_i$ transferred to output
1	0	$F_i = A_i \text{ xor } B_i$	compute XOR of $A_i, B_i$
1	1	$F_i = A_i \text{ xnor } B_i$	compute XNOR of $A_i, B_i$

## M = 1, C0 = 0, arithmetic operations

0	0	$F = A$	input A passed to output
0	1	$F = \text{not } A$	complement of A passed to output
1	0	$F = A \text{ plus } B$	sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B$	sum of B and complement of A

## M = 1, C0 = 1, arithmetic operations

0	0	$F = A \text{ plus } 1$	increment A
0	1	$F = (\text{not } A) \text{ plus } 1$	twos complement of A
1	0	$F = A \text{ plus } B \text{ plus } 1$	increment sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B \text{ plus } 1$	B minus A

Logical and arithmetic operations  
not all operations appear useful, but "fall out" of internal logic



# Arithmetic logic unit design (cont'd)


- Sample ALU – truth table

M	S1	S0	Ci	Ai	Bi	Fi	Ci+1	
0	0	0	X	0	X	0	X	
			X	1	X	1	X	
	0	1	X	0	X	1	X	
			X	1	X	0	X	
	1	0	X	0	0	0	X	
			X	1	1	1	X	
	1	1	1	X	0	0	1	X
				X	1	1	0	X
		0	0	X	0	1	0	X
				X	1	0	1	X
0		1	X	0	1	0	X	
			X	1	0	1	X	
1	0	0	0	0	X	0	X	
			0	1	X	1	X	
	0	1	0	0	X	1	X	
			0	1	X	0	X	
	1	0	0	0	0	0	0	
			0	1	0	1	0	
	1	1	0	0	0	1	0	
			0	1	0	1	0	
	0	0	0	0	1	1	0	0
				0	1	1	0	0
0		1	0	0	1	0	0	
			0	1	0	1	0	
1		0	0	0	0	1	0	
			0	1	0	1	0	
1	1	0	0	0	1	0		
		0	1	0	1	0		


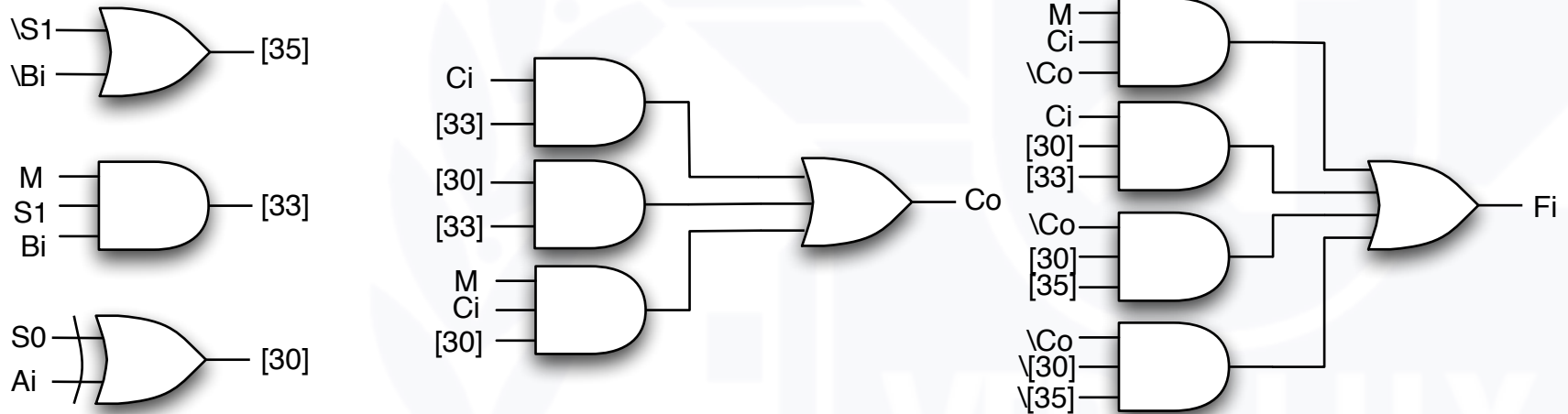
# Arithmetic logic unit design (cont'd)

- Sample ALU – multi-level discrete gate logic implementation




12 gates



# Arithmetic logic unit design (cont'd)
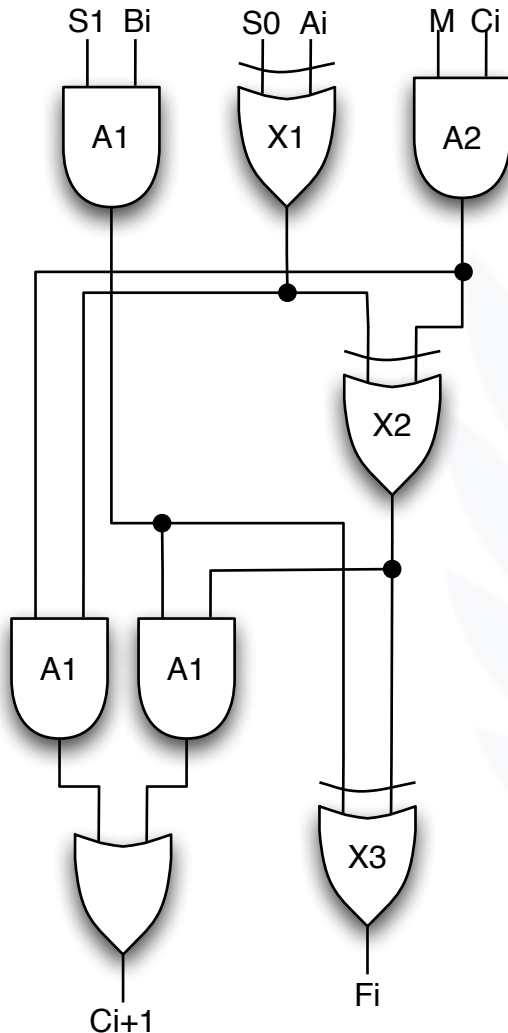
## Sample ALU – clever multi-level implementation



### First-level gates

use S0 to complement Ai

S0 = 0 causes gate X1 to pass Ai

S0 = 1 causes gate X1 to pass Ai'

use S1 to block Bi

S1 = 0 causes gate A1 to make Bi go forward as 0  
(don't want Bi for operations with just A)

S1 = 1 causes gate A1 to pass Bi

use M to block Ci

M = 0 causes gate A2 to make Ci go forward as 0  
(don't want Ci for logical operations)

M = 1 causes gate A2 to pass Ci

### Other gates

for M=0 (logical operations, Ci is ignored)

$$F_i = S_1 B_i \text{ xor } (S_0 \text{ xor } A_i)$$

$$= S_1' S_0' (A_i) + S_1' S_0 (A_i') +$$

$$S_1 S_0' (A_i B_i' + A_i' B_i) + S_1 S_0 (A_i' B_i' + A_i B_i)$$

for M=1 (arithmetic operations)

$$F_i = S_1 B_i \text{ xor } ((S_0 \text{ xor } A_i) \text{ xor } C_i) =$$

$$C_{i+1} = C_i (S_0 \text{ xor } A_i) + S_1 B_i ((S_0 \text{ xor } A_i) \text{ xor } C_i) =$$

just a full adder with inputs S0 xor Ai, S1 Bi, and Ci



# Summary for examples of combinational logic

- Combinational logic design process
  - Formalize problem: encodings, truth-table, equations
  - Choose implementation technology (ROM, PAL, PLA, discrete gates)
  - Implement by following the design procedure for that technology
- Binary number representation
  - Positive numbers the same
  - Difference is in how negative numbers are represented
  - 2s complement easiest to handle: one representation for zero, slightly complicated complementation, simple addition
- Circuits for binary addition
  - Basic half-adder and full-adder
  - Carry lookahead logic
  - Carry-select
- ALU Design
  - Specification, implementation

