

# Lecture 12. Aperture and Noise Analysis of Clocked Comparators

---

Jaeha Kim

Mixed-Signal IC and System Group (MICS)


Seoul National University

jaeha@ieee.org


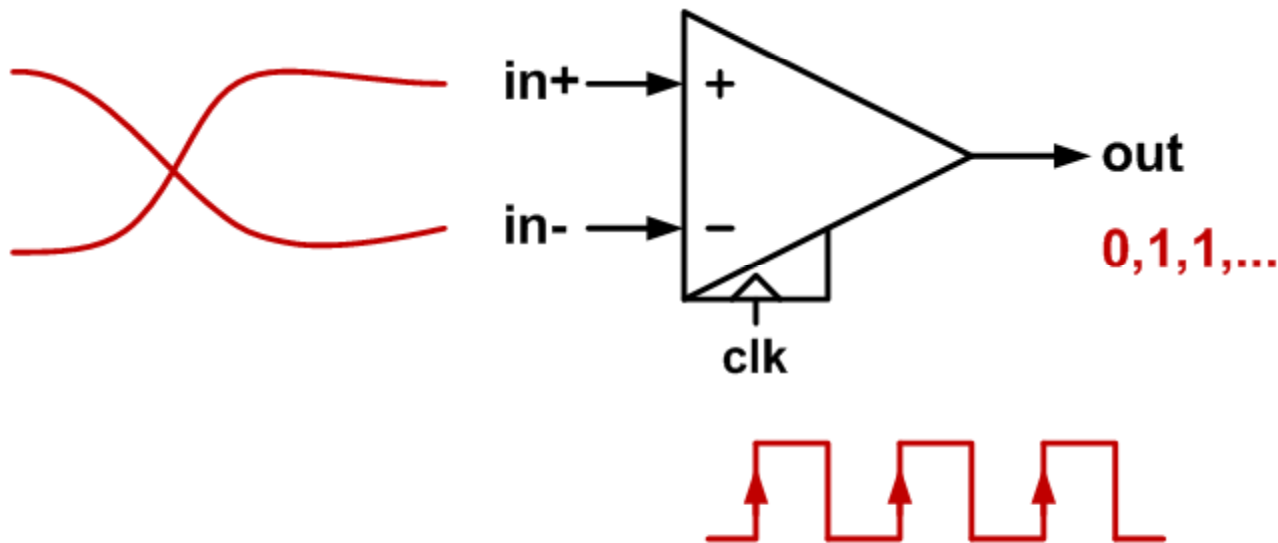
# Clocked Comparators

- a.k.a. regenerative amplifier, sense-amplifier, flip-flop, latch, etc.
- At every clock edge, sample the input (continuous) and decide whether it is 0 or 1 (binary)
  - Therefore, it's inherently nonlinear operation




# Comparator Characteristics

---


- Offset and hysteresis
  - Sampling aperture, timing resolution, uncertainty window
  - Regeneration gain, voltage sensitivity, metastability
  - Random decision errors, input-referred noise
- ⇒ *Can be analyzed and simulated based on a linear, time-varying (LTV) model of the comparator*

# Clocked Comparator Operation

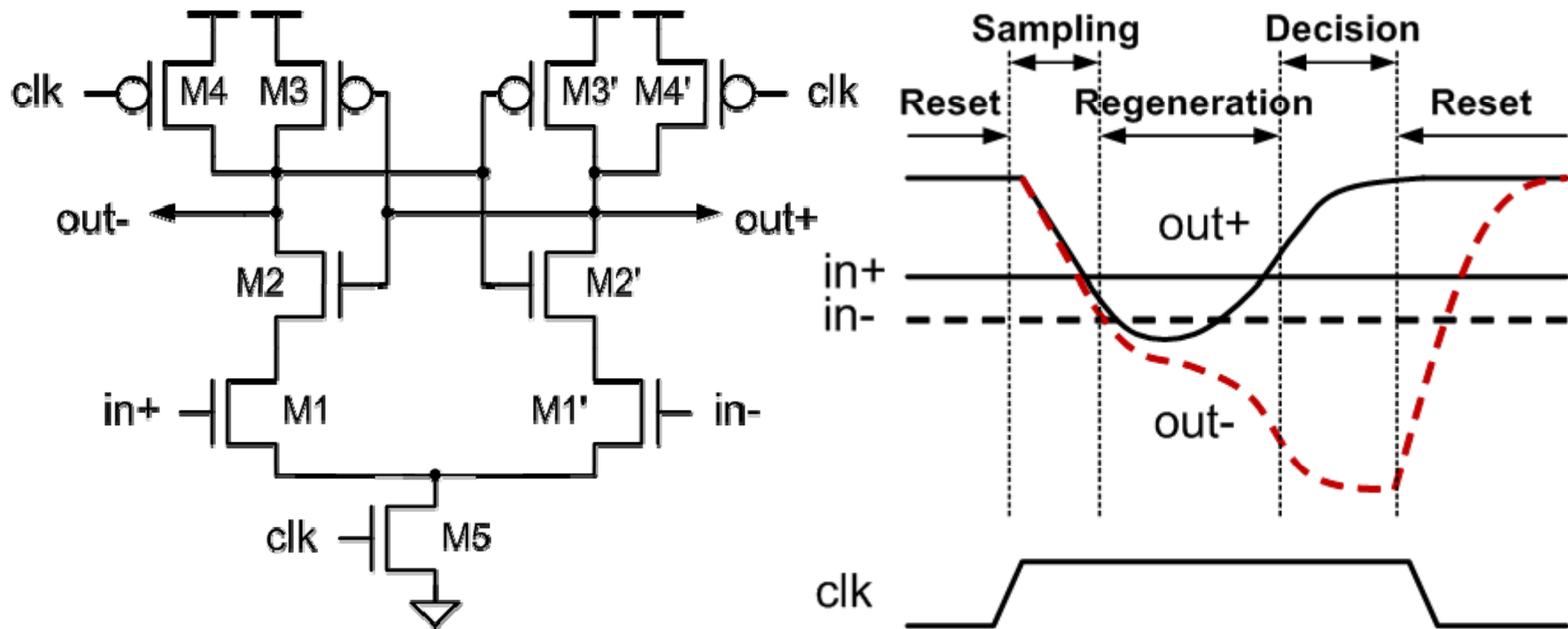


- 4 operating phases: reset, sample, regeneration & decision
- Sampling & regeneration phases can be modeled as LTV

# An Ideal Comparator Model

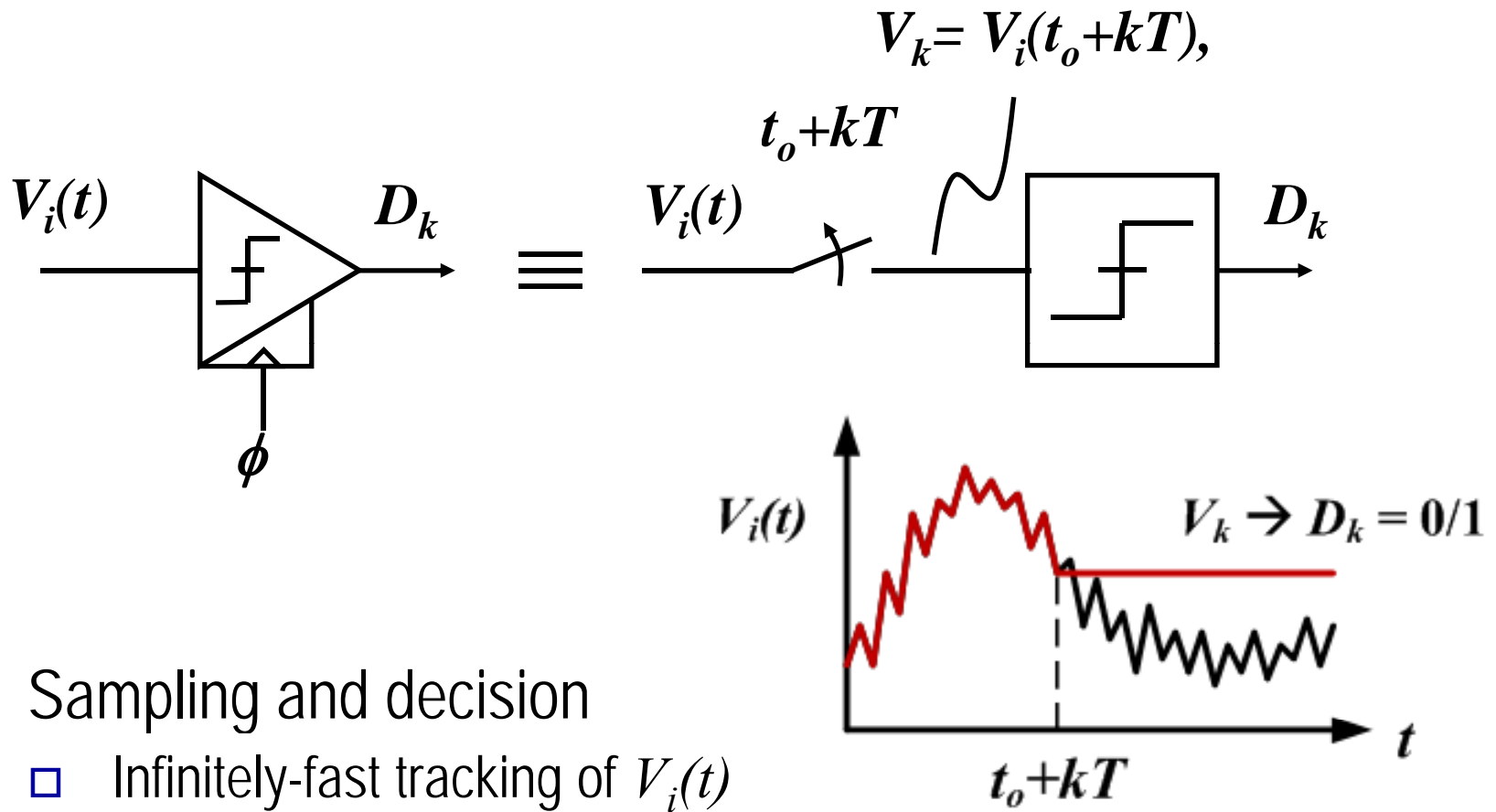

- Sampling and decision
  - Infinitely-fast tracking of  $V_i(t)$
- A realistic comparator acts on a filtered version of  $V_i(t)$

# LTV Model for Clocked Comparator

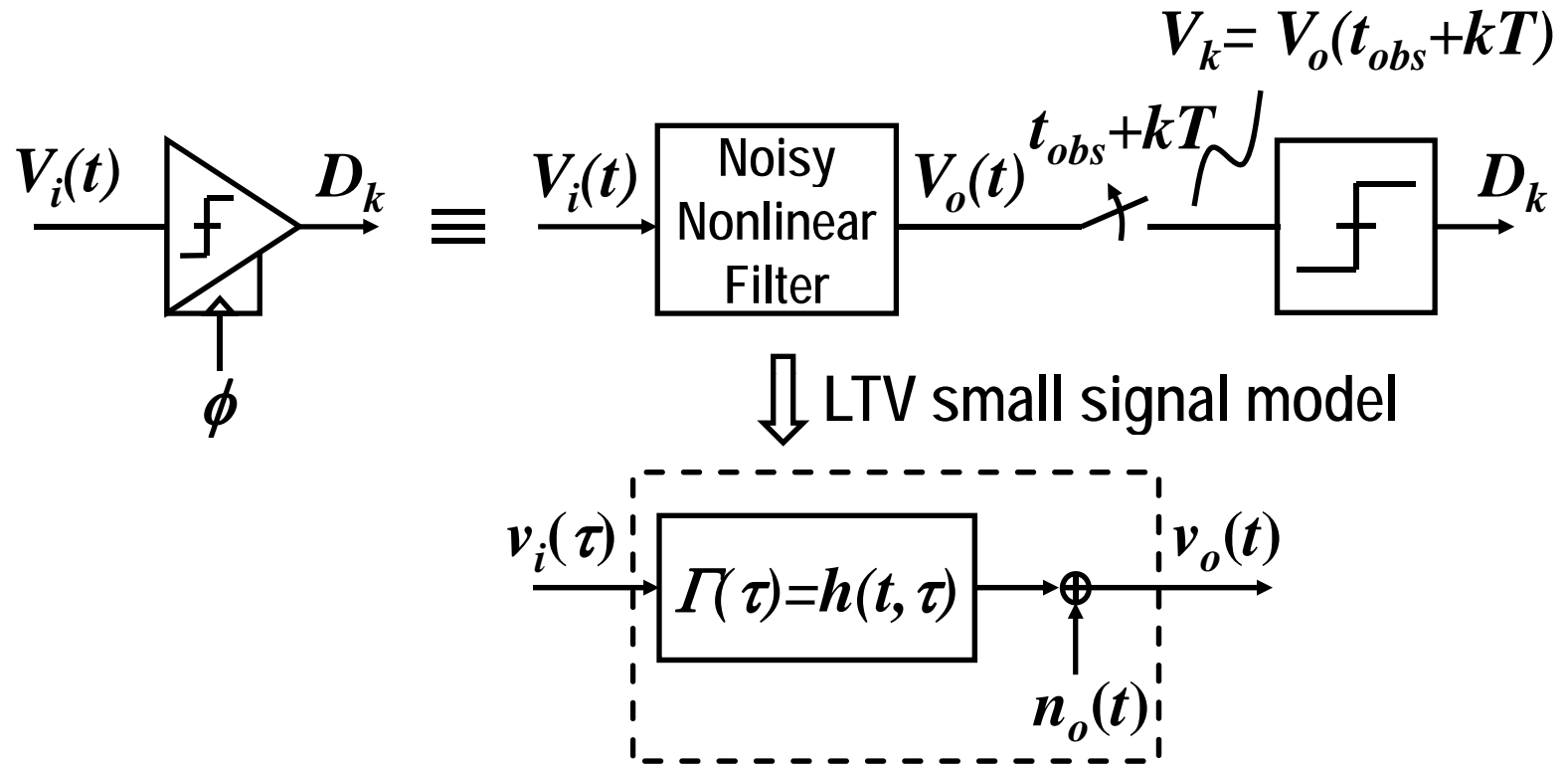

- Assumes a noisy, nonlinear filter before the sampling
- The filter's small-signal response is modeled with ISF  $\Gamma(\tau)$




\* J. Kim, et al., "Simulation and Analysis of Random Decision Errors in Clocked Comparators," IEEE TCAS-I, 08/2009.
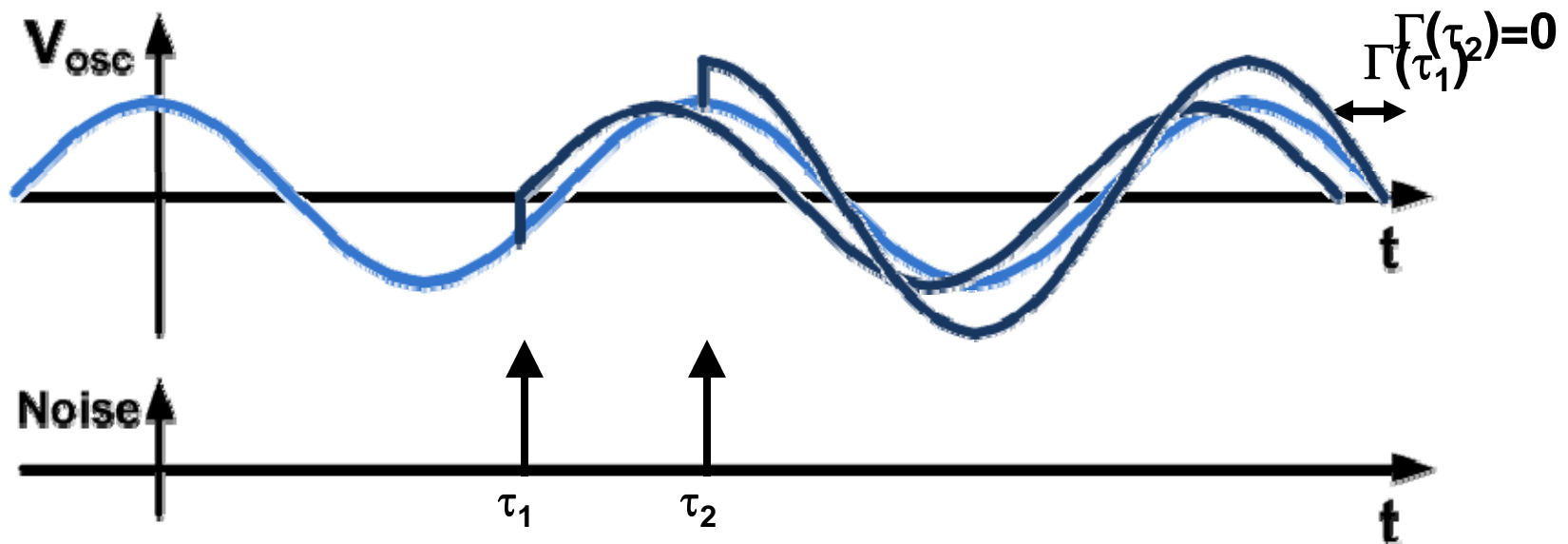
# ISF for Oscillators

- Impulse sensitivity function (ISF)  $\Gamma(\tau)$  is defined as:

$\Gamma(\tau)$  = the final shift in the oscillator phase due to a unit impulse arriving at time  $\tau$



\* A. Hajimiri and T. H. Lee, "A General Theory of Phase Noise in Electrical Oscillators," IEEE JSSC, Feb. 1998.

# ISF for Oscillators (2)

---

- ISF describes the time-varying response of a oscillator
  - Responses to each impulse add up via superposition
  - For arbitrary noise input  $n(t)$ , the resulting phase shift  $\Delta\phi$  is:

$$\Delta\phi = \int_{-\infty}^{\infty} \Gamma(\tau) \cdot n(\tau) d\tau$$

- ISF led to some key oscillator design idioms:
  - Sharpen the clock edge to lower ISF (i.e. minimize  $\Gamma_{\text{RMS}}$ )
  - Align noise events within low-ISF period
  - Balance ISF (i.e.  $\Gamma_{\text{DC}}=0$ ) to prevent 1/f-noise up-conversion



# ISF for Samplers and Comparators

---

- For sample-and-hold circuits, the sampled voltage  $V_s$  can be expressed via a “sampling function”  $f(t)$ :

$$V_s = \int_{-\infty}^{\infty} f(\tau) \cdot V_i(\tau) d\tau$$

\* H. O. Johansson, C. Svensson, “Time Resolution of NMOS Sampling Switches Used on Low-Swing Signals,” JSSC, Feb. 1998.

- For clocked comparators, we simply add the “decision”:

$$D_k = \text{sgn}(V_k) = \text{sgn}\left(\int_{-\infty}^{\infty} \Gamma(\tau) \cdot V_i(\tau) d\tau\right)$$


\* P. Nuzzo, et al., “Noise Analysis of Regenerative Comparators for Reconfigurable ADC Architectures,” TCAS-I, July 2008.




# ISF for Clocked Comparators

- ISF shows sampling aperture, i.e. timing resolution
- In frequency domain, it shows sampling gain and BW

ISF  $\Gamma(\tau)$

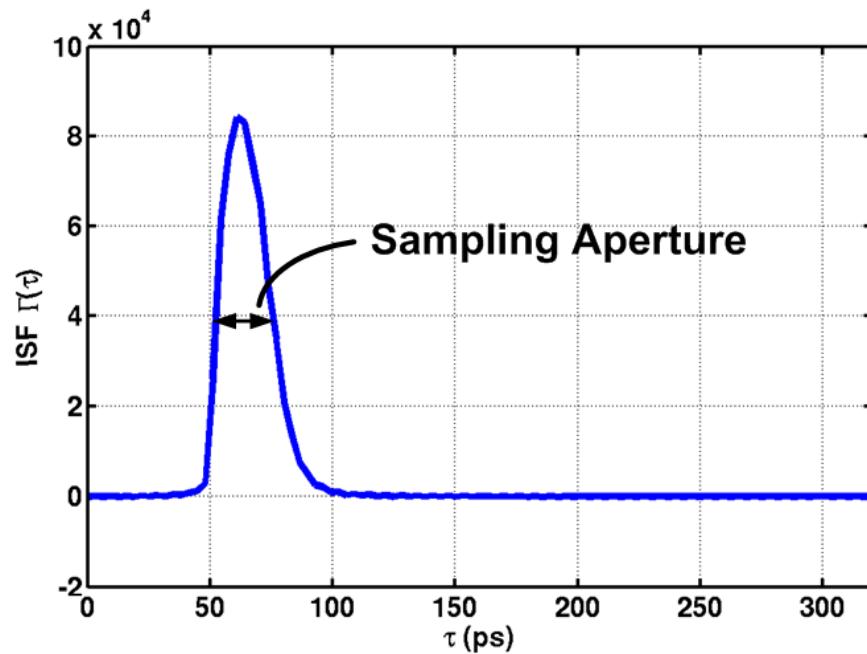

F.T.  $\{ \Gamma(-\tau) \}$

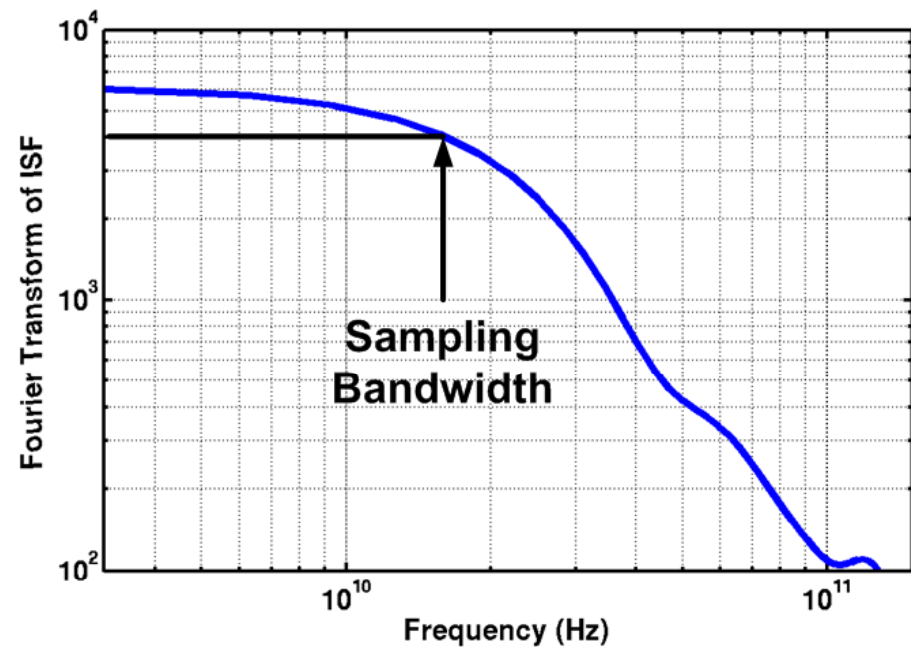

# Generalized ISF

---

- In general, ISF is a subset of a so-called *time-varying impulse response*  $h(t, \tau)$  for LTV systems\*:

$$y(t) = \int_{-\infty}^{\infty} h(t, \tau) \cdot x(\tau) d\tau$$

- $h(t, \tau)$ : the system response at  $t$  to a unit impulse arriving at  $\tau$
  - For LTI systems,  $h(t, \tau) = h(t-\tau) \rightarrow$  convolution
- ISF  $I(\tau) = h(t_0, \tau)$ 
    - $t_0$ : the time at which the system response is observed
    - For oscillators,  $t_0 = +\infty$
    - For comparators,  $t_0$  is before the decision is made (more later)




\* L. Zadeh, "Frequency Analysis of Variable Networks," Proc. I.R.E. Mar. 1950.
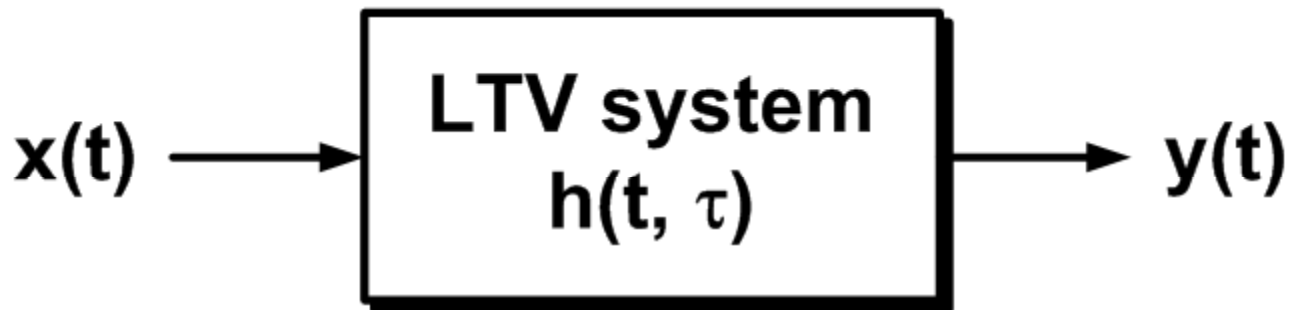
# Noise in LTV Systems

---

- If the input  $x(t)$  to an LTV system is a noise process, then the output  $y(t)$  is a time-varying noise in general
  - Expressions become very complex (cyclo-stationary at best)
- We can keep things simple if we are interested in the noise only at one time point (in our case:  $t_0 = t_{obs} + kT$ )



# LTV Output Noise at $t = t_0$

---

$$\begin{aligned}\sigma_y^2(t_0) &= \mathbb{E}[y^2(t_0)] = \mathbb{E}[y(t_0) \cdot y(t_0)] \\ &= \mathbb{E}\left[\left(\int_{-\infty}^{\infty} h(t_0, u) \cdot x(u) du\right) \cdot \left(\int_{-\infty}^{\infty} h(t_0, v) \cdot x(v) dv\right)\right] \\ &= \int_{-\infty}^{\infty} \int_{-\infty}^{\infty} \mathbb{E}[x(u) \cdot x(v)] \cdot h(t_0, u) \cdot h(t_0, v) du dv \\ &= \int_{-\infty}^{\infty} \int_{-\infty}^{\infty} R_{xx}(u, v) \cdot h(t_0, u) \cdot h(t_0, v) du dv\end{aligned}$$

- $R_{xx}(u, v)$  is the auto-correlation of the input noise  $x(t)$

# Response to White and 1/f Noises

---

- If the input  $x(t)$  is white noise, i.e.  $R_{xx}(u, v) = \sigma_x^2 \cdot \delta(u-v)$ :

$$\sigma_y^2(t_0) = \sigma_x^2 \cdot \int_{-\infty}^{\infty} h^2(t_0, u) du = \sigma_x^2 \cdot \int_{-\infty}^{\infty} \Gamma^2(\tau) d\tau$$

- If the input  $x(t)$  is 1/f noise, i.e.  $R_{xx}(u, v) = \sigma_x^2$ :

$$\sigma_y^2(t_0) = \sigma_x^2 \cdot \left[ \int_{-\infty}^{\infty} h(t_0, u) du \right]^2 = \sigma_x^2 \cdot \left[ \int_{-\infty}^{\infty} \Gamma(\tau) d\tau \right]^2$$

- Agrees with Hajimiri/Lee's low-noise design idioms:
  - To minimize contribution of white noise, minimize  $\Gamma_{RMS}$
  - To minimize contribution of 1/f noise, make  $\Gamma_{DC} = 0$

# Random Decision Error Probability

---

- If we have multiple noise sources, their contributions add up via RMS sum assuming they are independent:

$$\sigma_{y,total}^2(t_o) = \sum_j \sigma_{y,j}^2(t_o)$$


- If the comparator has signal  $V_o$  and noise  $\sigma_{n,o}$  at  $t_{obs}$ , the decision error probability  $P(error)$  can be estimated as:

$$\sqrt{SNR} = V_o(t_{obs}) / \sigma_{n,o}(t_{obs})$$

$$P(error) = Q(\sqrt{SNR}) = \frac{1}{\sqrt{2\pi}} \int_{\sqrt{SNR}}^{\infty} \exp(-x^2 / 2) dx$$
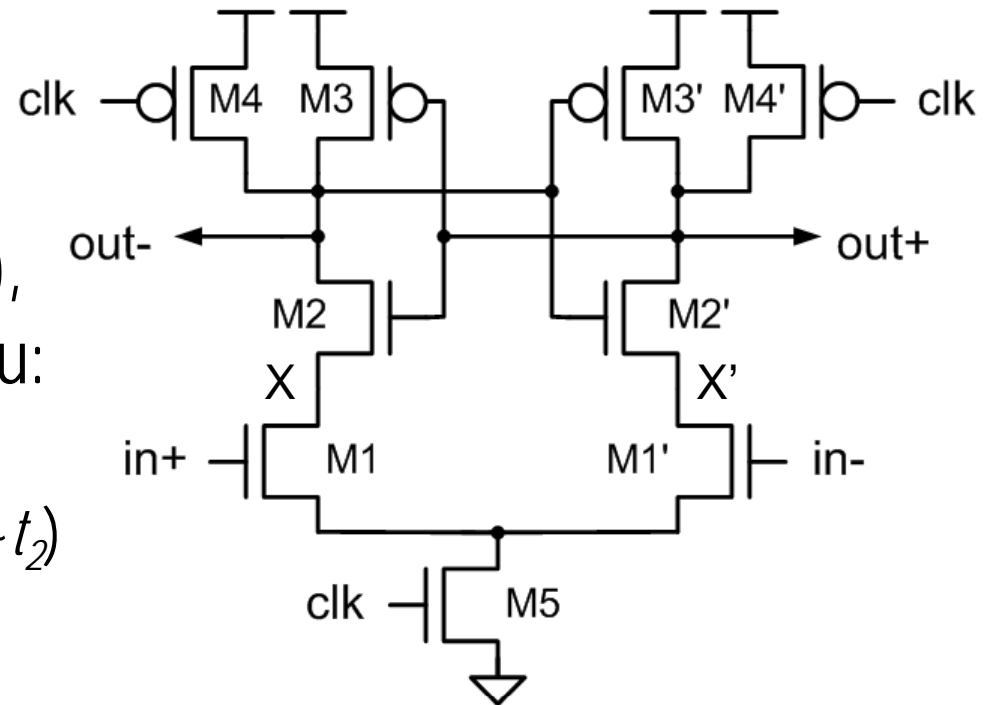
# Circuit Analysis Example

- A variant of StrongARM comparator
- When clk is low, the comparator is in reset
  - out+/- are at  $V_{dd}$
  - X/X' are  $\sim V_{dd} - V_{TN}$
- When clk rises (say  $t=t_0$ ), the comparator goes thru:
  - Sampling phase ( $t_0 \sim t_1$ )
  - Regeneration phase ( $t_1 \sim t_2$ )





# 1. Sampling Phase ( $t = t_0 \sim t_1$ )



- While out+/- remain high:
  - M1-pair discharges X/X'
  - M2-pair discharges out+/-
- S.S. transfer from  $v_{in}$  to  $v_{out}$ :

$$\frac{v_{out}(s)}{v_{in}(s)} = \frac{g_{m1} \cdot g_{m2}}{s C_{out} C_x (s + g_{m2} (C_{out} - C_x) / C_{out} C_x)}$$

$$\cong \frac{g_{m1} \cdot g_{m2}}{s^2 C_{out} C_x} = \frac{1}{s^2 \tau_{s1} \tau_{s2}}$$

- The ISF w.r.t.  $v_{in}$  is:
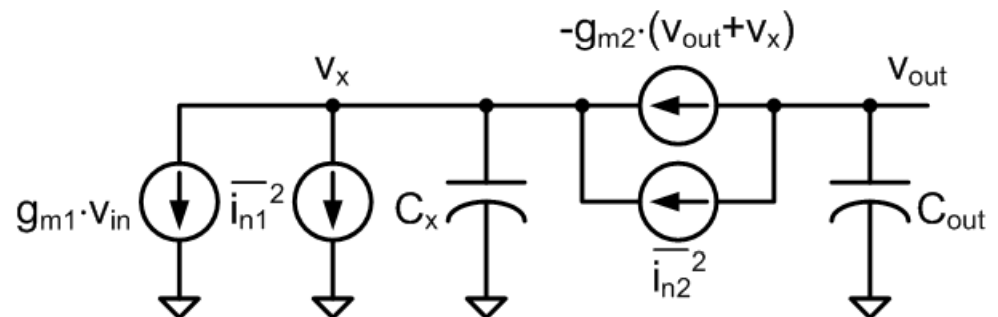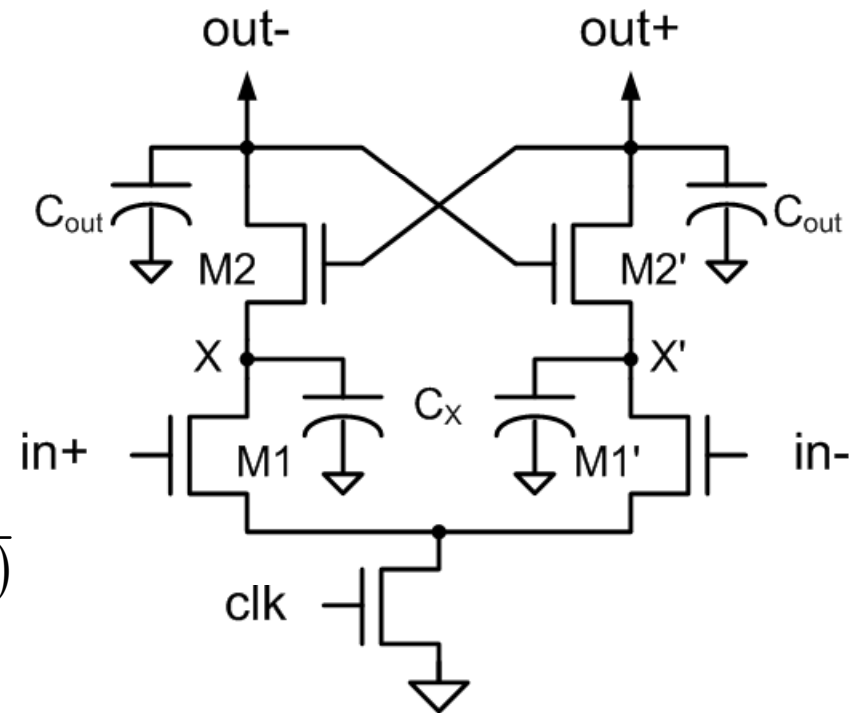
$$\Gamma(t) \cong \frac{t_1 - t}{\tau_{s1} \tau_{s2}} \cdot G_R$$



# 1. Sampling Phase ( $t = 0 \sim t_1$ )

- S.S. response to M1 noise:



$$\frac{v_{out}(s)}{i_{n1}(s)} \cong \frac{g_{m2}}{s^2 C_{out} C_x}$$

$$\Gamma_{n1}(t) \cong \frac{t_1 - t}{g_{m1} \tau_{s1} \tau_{s2}} \cdot G_R$$

- S.S. response to M2 noise:


$$\frac{v_{out}(s)}{i_{n2}(s)} \cong \frac{1}{s C_{out}}$$
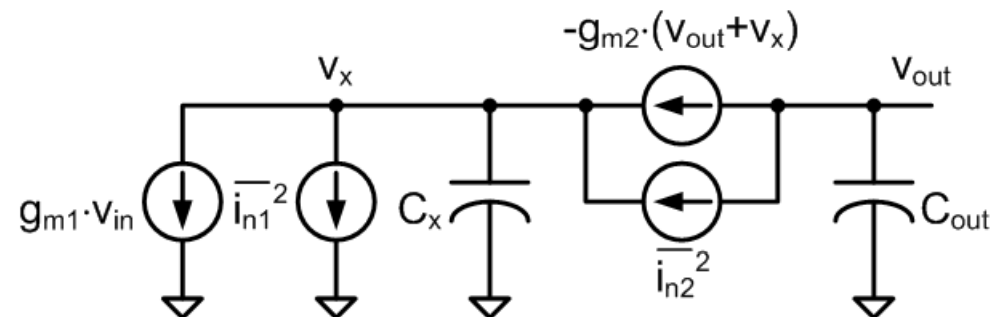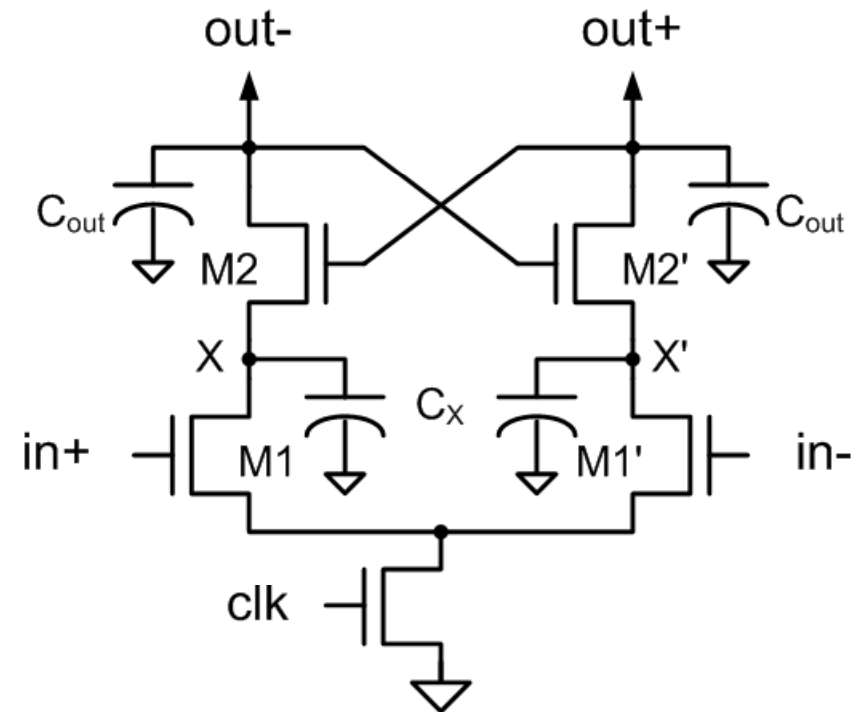
$$\Gamma_{n2}(t) \cong \frac{1}{C_{out}} \cdot G_R$$



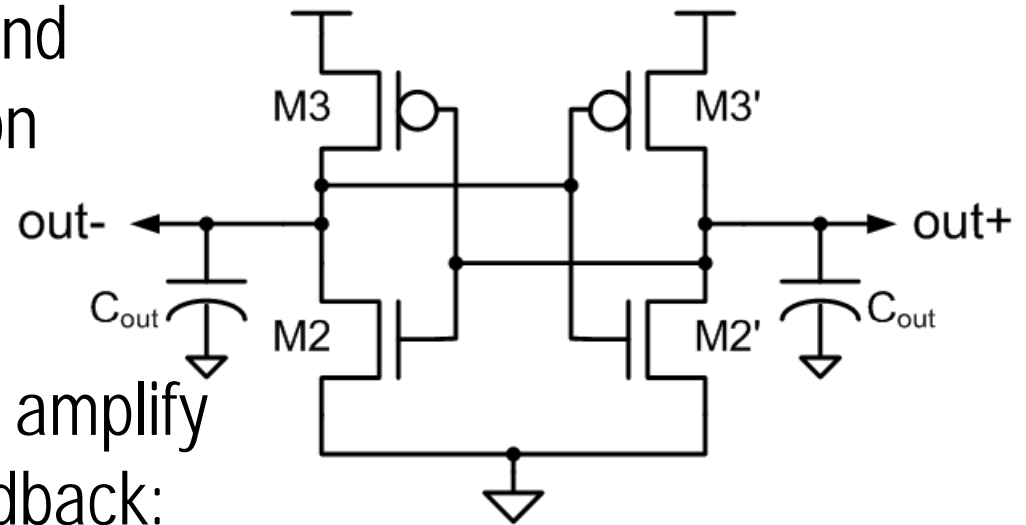
## 2. Regeneration Phase ( $t = t_1 \sim t_2$ )

- We assume  $X/X' \sim 0V$  and M1-pair is in linear region
  - The circuit is no longer sensitive to  $v_{in}$  (ISF=0)
- Cross-coupled inverters amplify signals via positive-feedback:



$$G_R = \exp\left(\frac{t_2 - t_1}{\tau_R}\right)$$
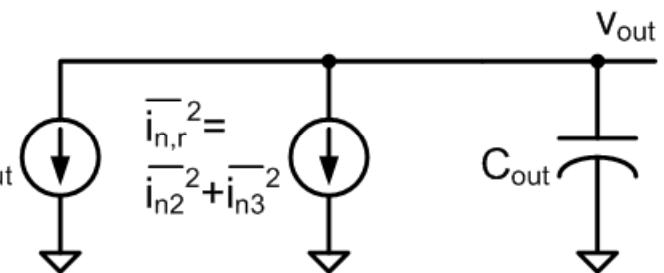
$$\tau_R = C_{out} / (g_{m2,r} + g_{m3,r}) \quad -(g_{m2,r} + g_{m3,r}) \cdot V_{out}$$



- The ISF w.r.t. noise is:

$$\Gamma_{n,r}(t) \cong \frac{1}{C_{out}} \cdot \exp\left(\frac{t_2 - t}{\tau_R}\right)$$

# Putting It All Together

- The overall gain  $G$  is:


$$G = v_o(t_{obs}) / v_{i,dc} = \int_{-\infty}^{\infty} \Gamma(t) dt$$

$$= \frac{(t_0 - t_1)^2}{2\tau_{s1}\tau_{s2}} \cdot \exp\left(\frac{t_2 - t_1}{\tau_R}\right)$$

- The total input-referred noise is:

$$\sigma_{n,i}^2 = \sigma_{n,o}^2 / G^2$$
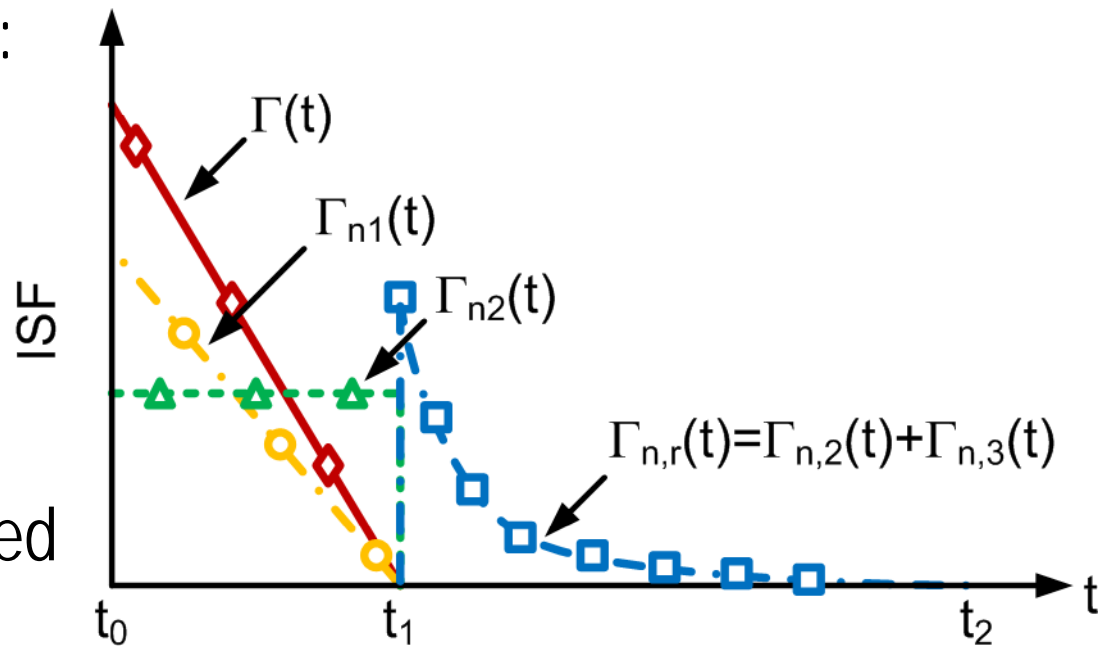
$$\cong \frac{16kT\gamma}{3C_x} \cdot \frac{\tau_{s1}}{t_1 - t_0} + \frac{16kT\gamma}{C_{out}} \cdot \frac{\tau_{s1}^2 \cdot \tau_{s2}}{(t_1 - t_0)^3}$$



- Most of the noise is contributed by M1 and M2 pairs during the sampling phase

# Design Trade-Offs

---

- The input-referred noise can be approximated as:

$$\sigma_{n,i}^2 \cong \frac{16kT\gamma}{3C_x} \cdot \frac{\tau_{s1}}{t_1 - t_0} + \frac{16kT\gamma}{C_{out}} \cdot \frac{\tau_{s1}^2 \cdot \tau_{s2}}{(t_1 - t_0)^3}$$

where

$$\frac{\tau_{s1}}{t_1 - t_0} \cong \frac{C_x}{C_{out}} \bigg/ \left( \frac{g_{m1}}{I_{d1}} \cdot V_{Tp} \right), \quad \frac{\tau_{s2}}{t_1 - t_0} \cong 1 \bigg/ \left( \frac{g_{m2}}{I_{d2}} \cdot V_{Tp} \right)$$

- Therefore, noise improves with larger  $g_m/I_d$  ratios and wider sampling aperture ( $t_1 - t_0$ )
- However, sampling bandwidth and/or gain may degrade
  - Controlling the tail turn-on rate is a good way to keep high gain


# Simulating Aperture & Noise

---

- RF simulators (e.g. SpectreRF) can simulate small-signal LPTV response and noise efficiently:
  - Simulates linearized responses around a periodic steady-state
  - PAC analysis gives  $H(j\omega;t) = \text{Fourier transform of } h(t, \tau)^*$
  - PNOISE analysis can give the noise PSD at one time point
  
- The remaining question is how to choose  $t_{obs}$ ?
  - We'd like to choose it to mark the end of the regeneration
  - Since  $I(\tau)$  in our LTV model captures sampling + regeneration


\* J. Kim, et al., "Impulse Sensitivity Function Analysis of Periodic Circuits," ICCAD'08.

# Comparator Periodic Steady-State (PSS)

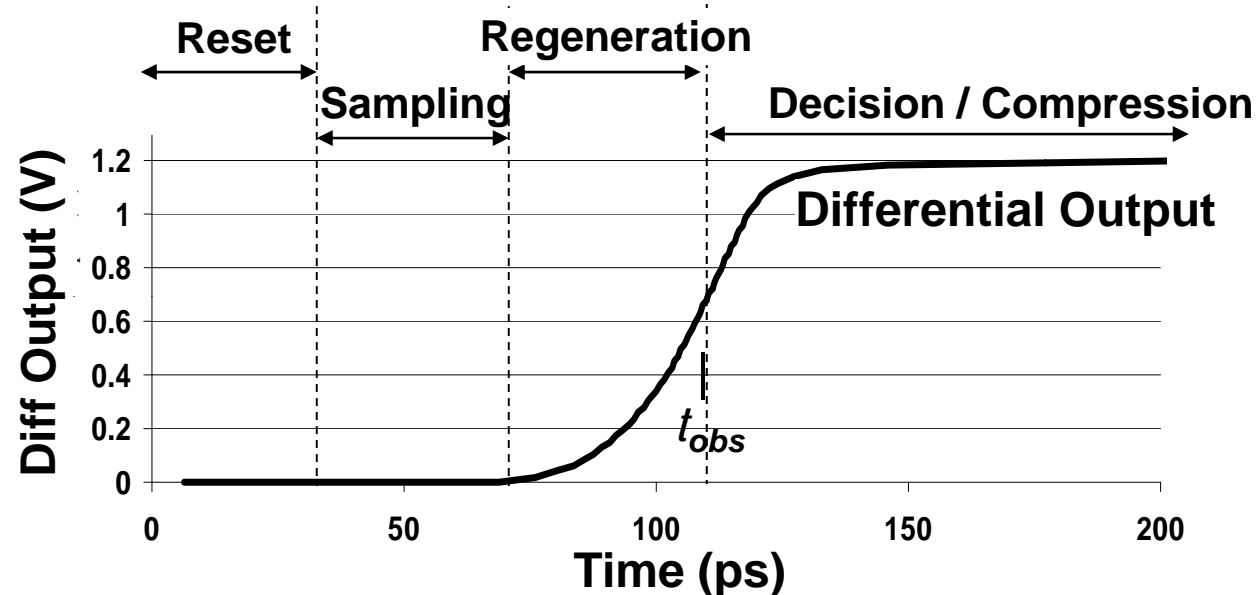


- PSS response of the comparator for a small DC input
  - Near the clock's rising edge; return to reset not shown

# Comparator Sampling Aperture (PAC)

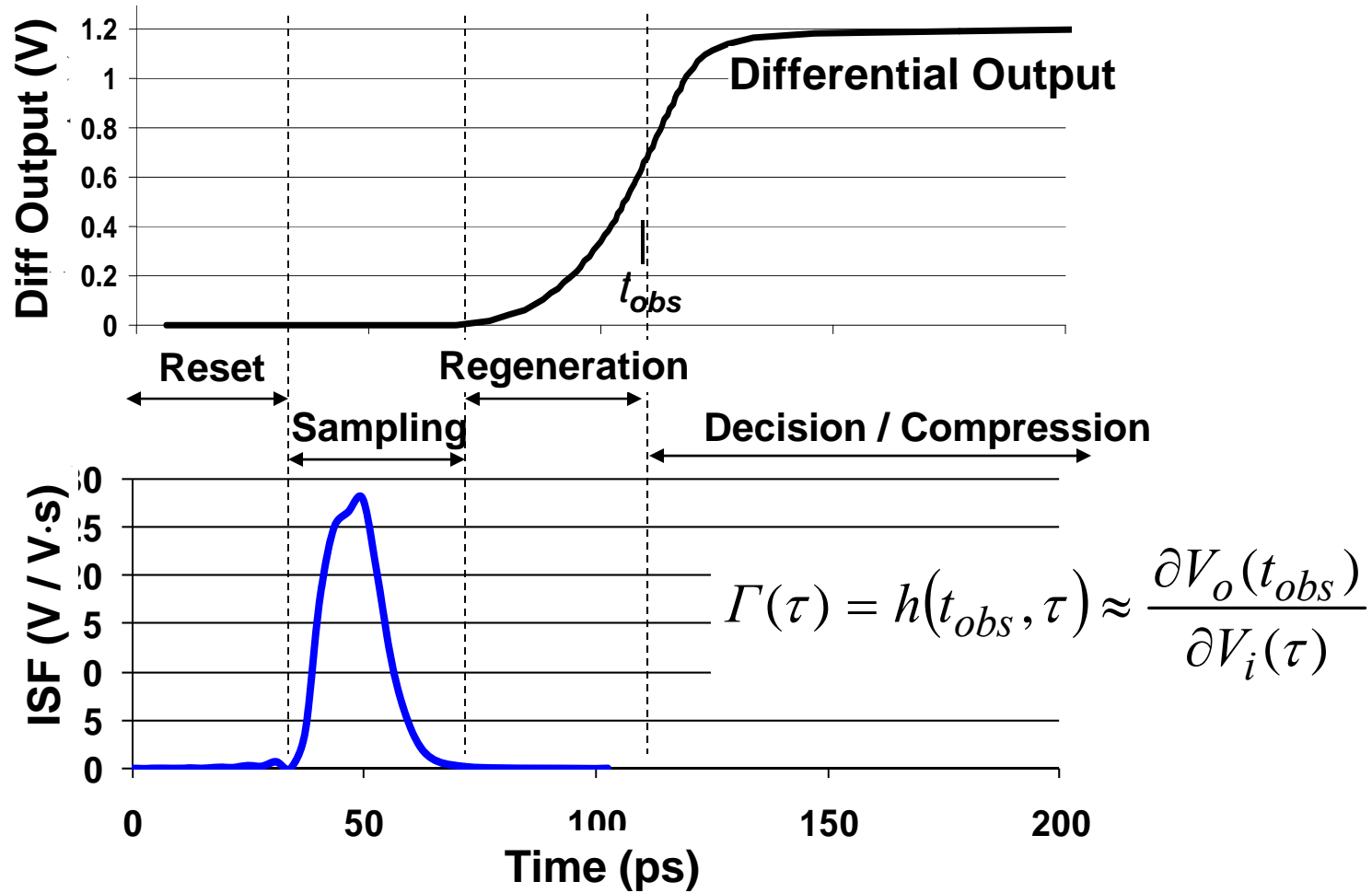




# Comparator Noise (PNOISE)

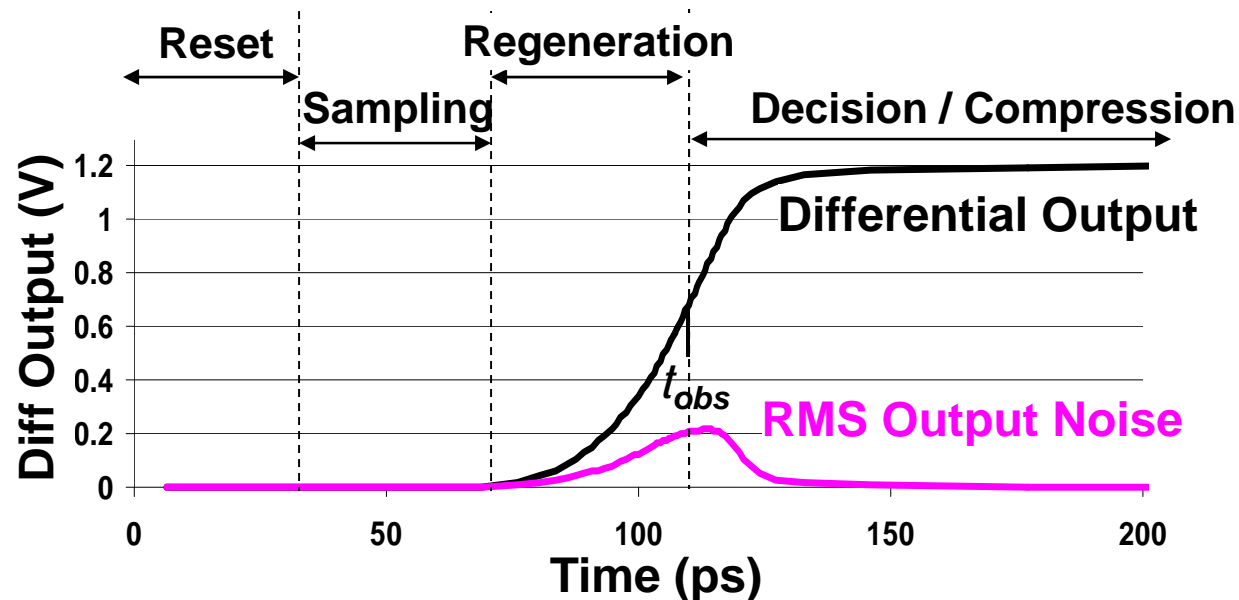

- Magenta line plots the rms output noise  $\sigma(t)$  vs. time, obtained by integrating the noise PSD at each time point
- This is *not* "transient noise analysis" – it's a time sample of cyclo-stationary noise (much more efficient)

# Comparator Output SNR

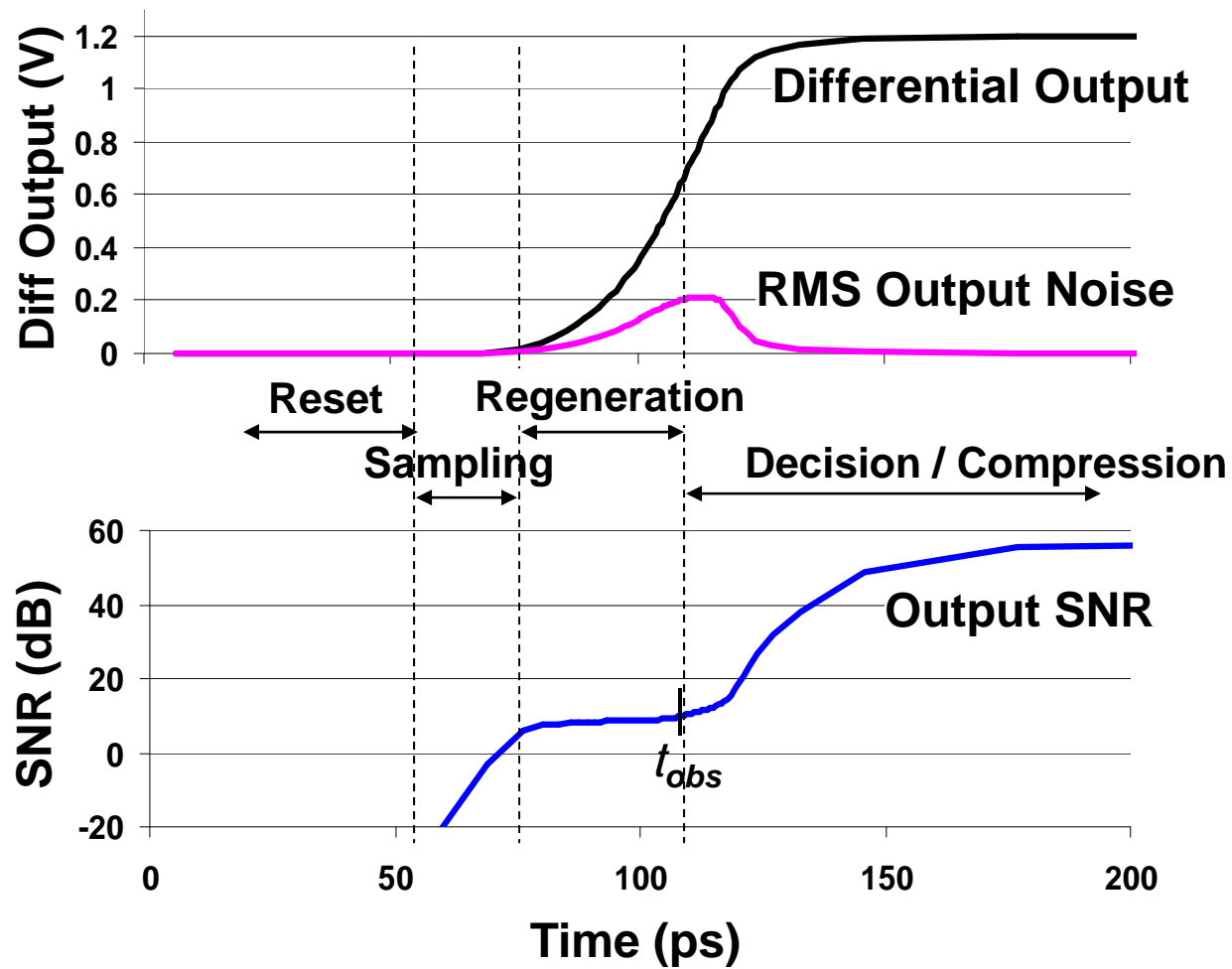


# Deciding on $t_{obs}$


---

- How to choose  $t_{obs}$  that marks the end of regeneration
- Most of the noise is contributed during the sampling phase
  - Noise that enters during the sampling phase sees the full gain
  - Noise that enters later during the regeneration phase sees an exponentially decreasing gain with time
- For the purpose of estimating decision errors, selection of  $t_{obs}$  is not critical as long as it's within regeneration phase
  - The SNR and decision error probability stay ~constant
  - I choose  $t_{obs}$  when the comparator has the max. small-signal gain (i.e. before the nonlinearity starts suppressing the gain)

# Measurement Results

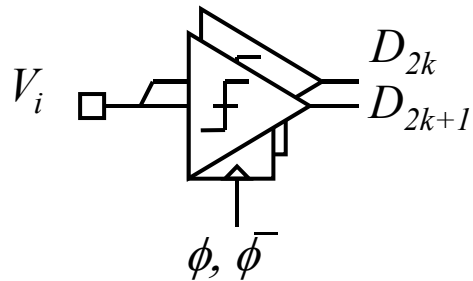


Receiver A (90nm)

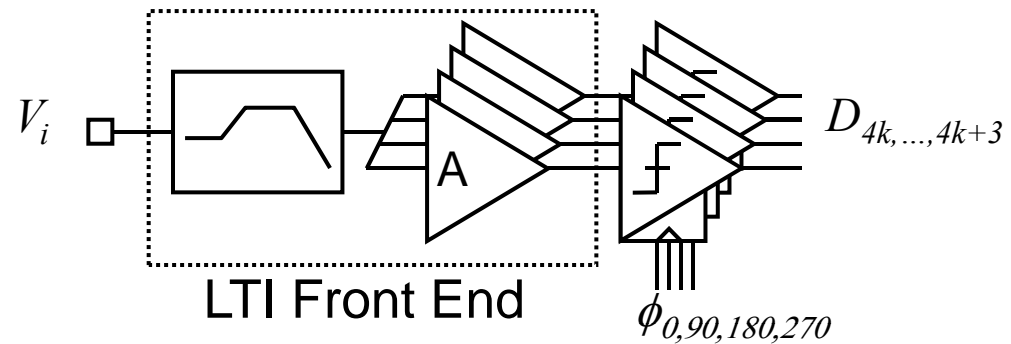

Receiver B (65nm)


- Both receivers are based on StrongARM comparators
- Differential  $C_{in} \sim 2\text{pF} \Rightarrow$  thermal noise from the input termination resistors  $< 100\mu\text{V}_{rms}$
- Excess noise factor  $\gamma$  not spec'd by foundries  $\Rightarrow$  simulated at multiple values

# Receiver A – Direct Sampling Front-End

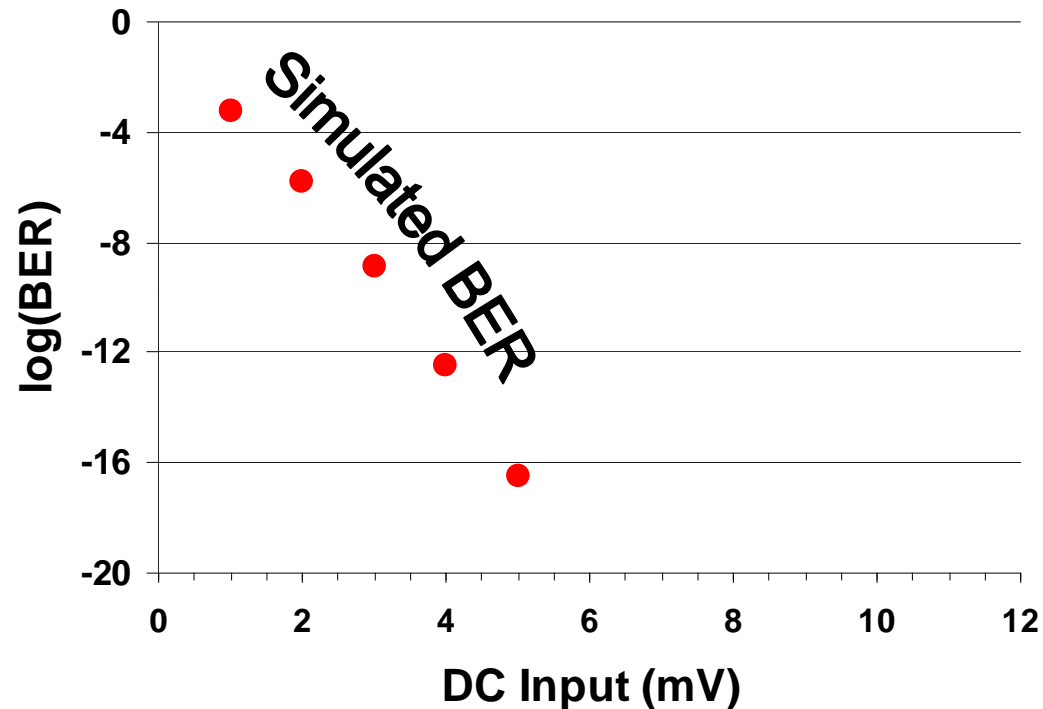


- Simulation of the decision error (BER) =  $Q(V_o(t_{obs})/\sigma_o(t_{obs}))$  versus the DC input level (excess noise factor  $\gamma=2$ )

# Receiver A – Direct Sampling Front-End

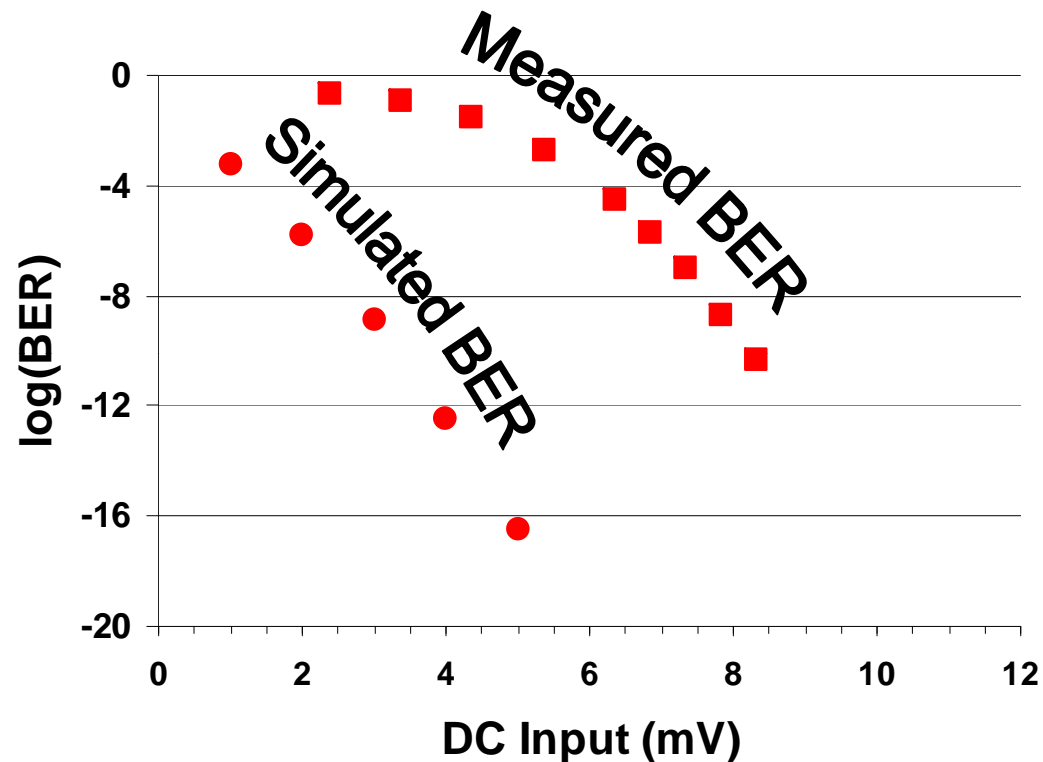

- Measurement of the decision errors (BER) based on the density of the wrong outputs (0's) versus the DC input level

# Receiver A – Direct Sampling Front-End

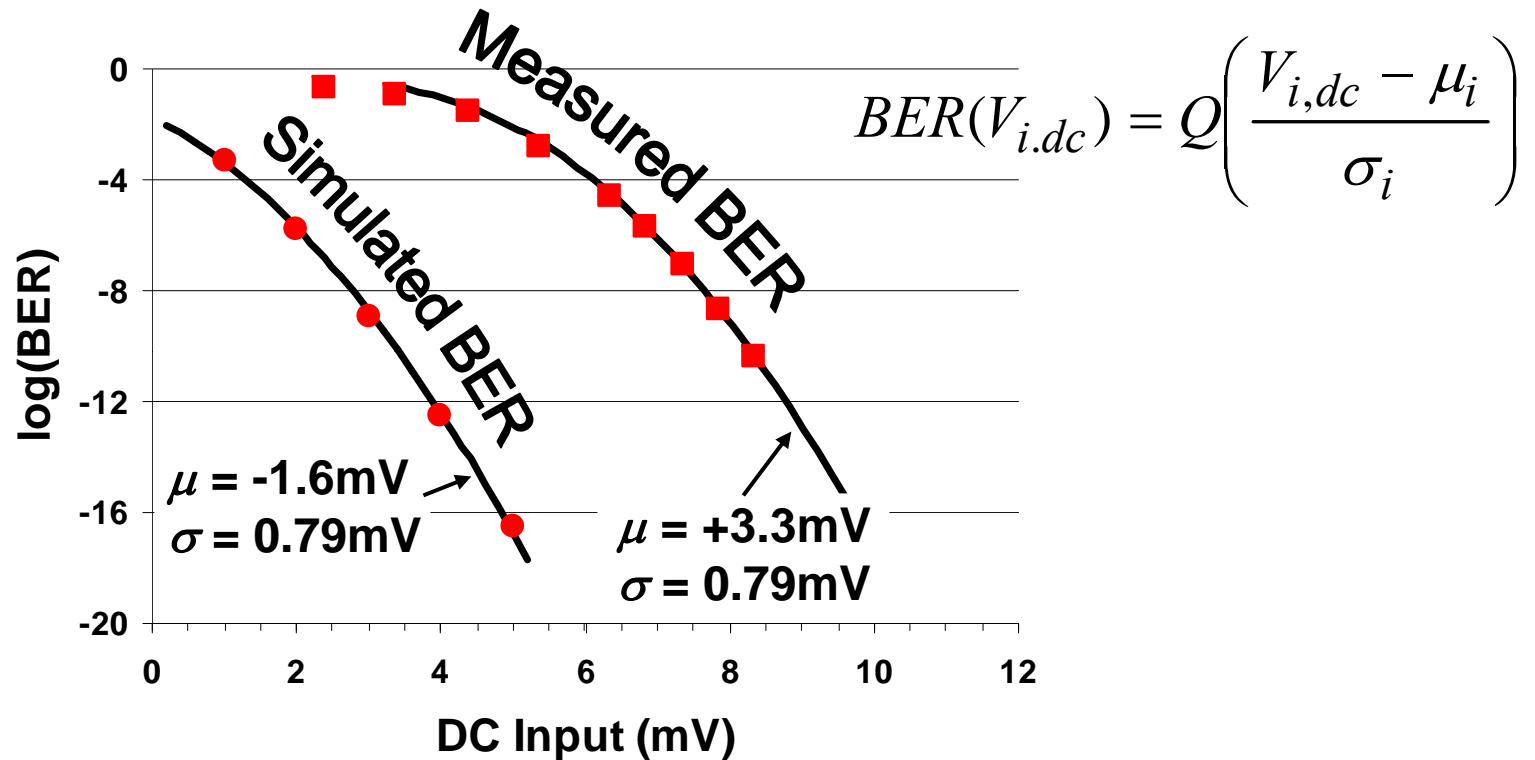

- Fit both sets of points to the Gaussian BER model
- Compare the estimated  $\sigma$ 's (input-referred rms noise)


# Simulation vs. Measurement

Receiver	Simulated (mV,rms)				Measured (mV,rms) (Pos. / Neg. / Avg.)
	$\gamma=1$	$\gamma=2$	$\gamma=3$	$\gamma=4$	
(A) 90nm Direct Sampling Front-End	0.59	0.79	0.94		0.79 / 0.65 / 0.72
(B) 65nm w/ Linear Front-End		0.62	0.73	0.83	0.87 / 0.83 / 0.85

- (Pos. / Neg. / Avg.) refers to measurement results for positive  $V_{IN}$ , negative  $V_{IN}$ , and their average


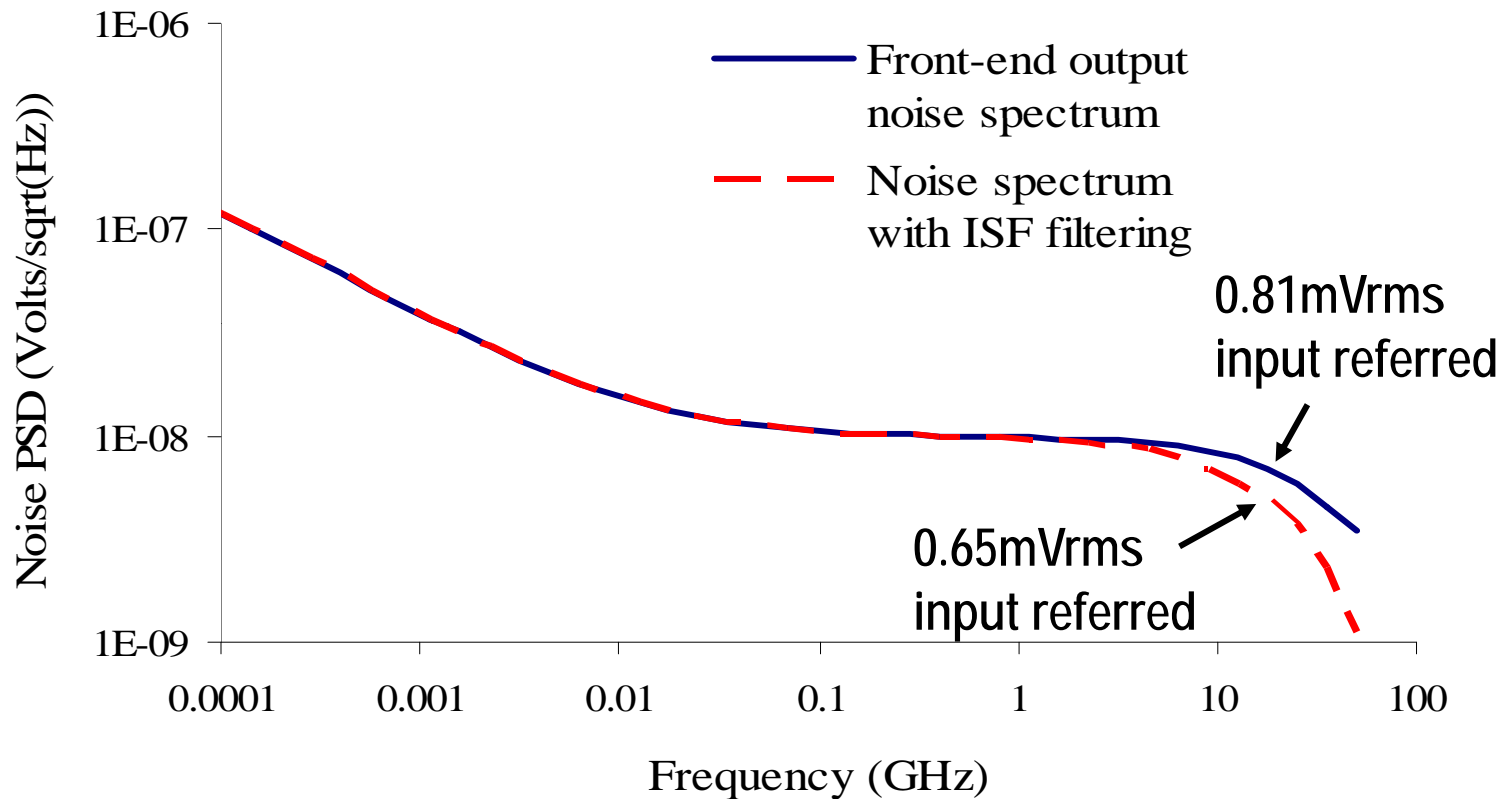
# Noise Filtering via Finite Aperture (ISF)



- In receiver B, the noise contributed by the linear front-end is filtered by the finite aperture of the comparator

# Conclusions

---

- The linear time-varying (LTV) system model is a good tool for understanding the key characteristics of clocked comparators
  - Sampling aperture and bandwidth
  - Regeneration gain and metastability
  - Random decision errors and input-referred noise
- The impulse sensitivity function (ISF) has a central role in it:
  - As it did for oscillators
  - Guides design trade-offs between noise, bandwidth, gain, etc.
- The LTV framework is demonstrated on the analysis, simulation, and measurement of clocked comparators



# Back-Up Slides

---



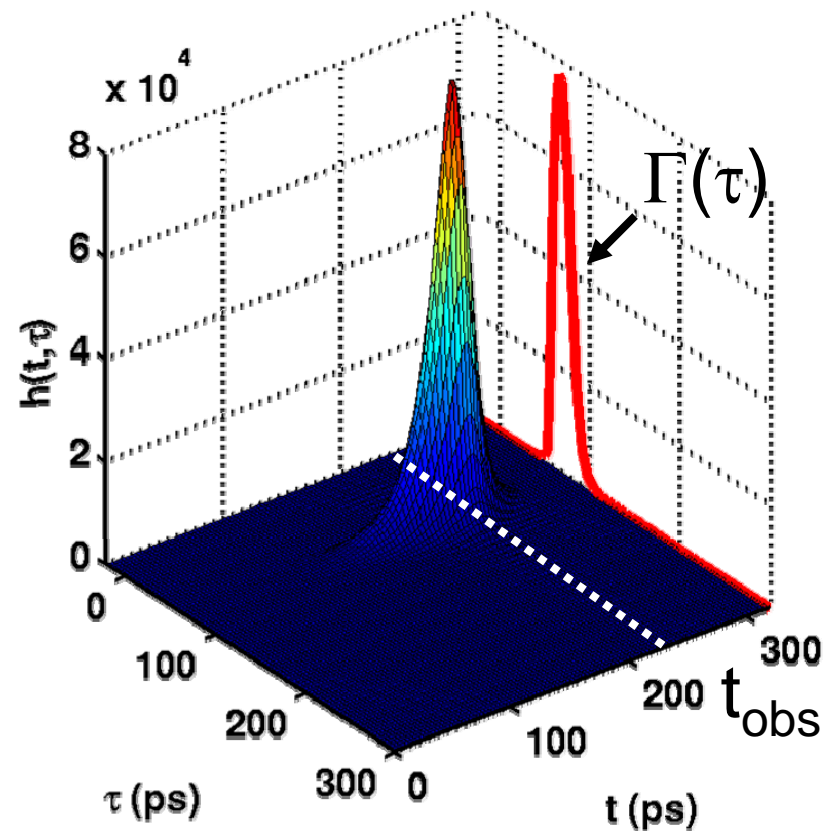
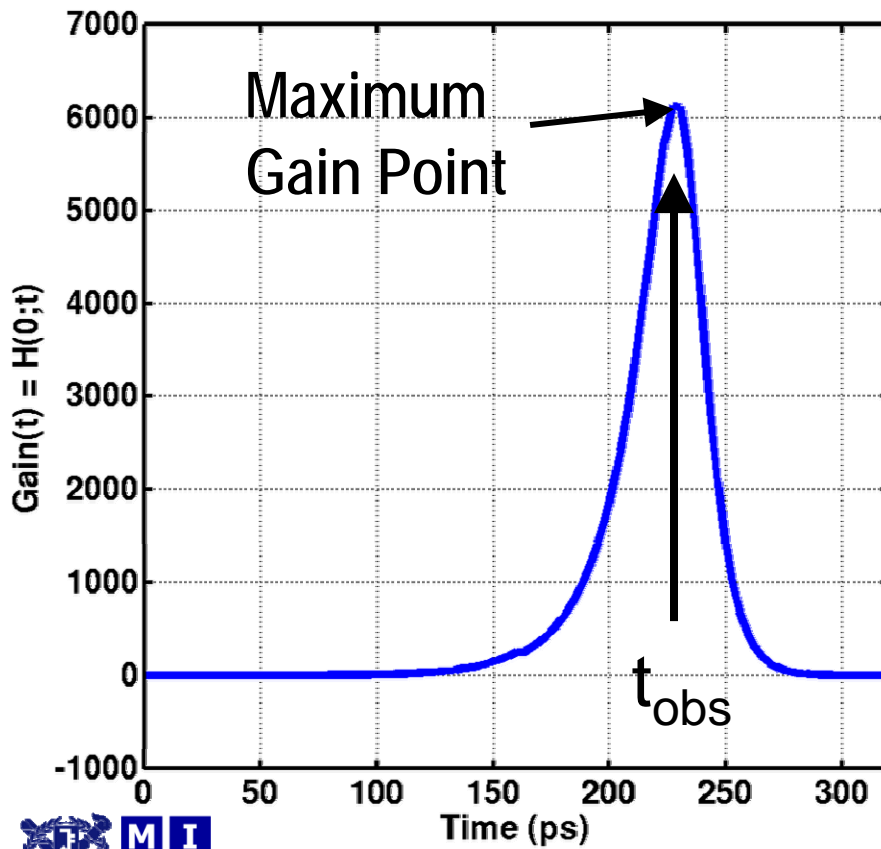
# Extracting ISF from $h(t, \tau)$

- Choose  $t_{\text{obs}}$  as the maximum small-signal gain point
- ISF:  $\Gamma(\tau) = h(t_{\text{obs}}, \tau)$



# Effects of the Bridging Device

- Improves hold time and metastability

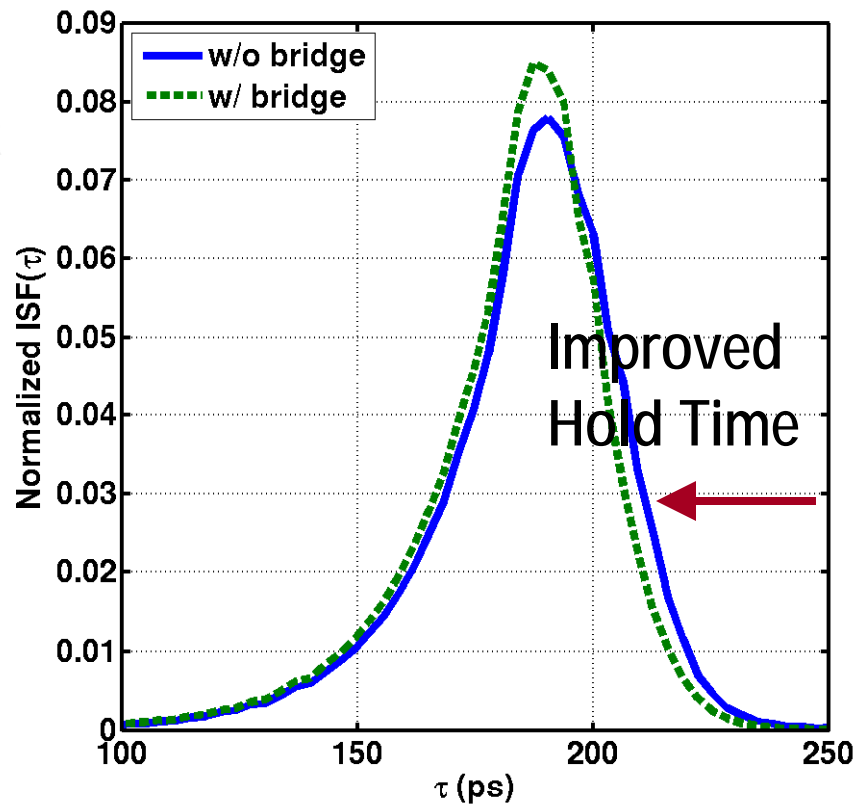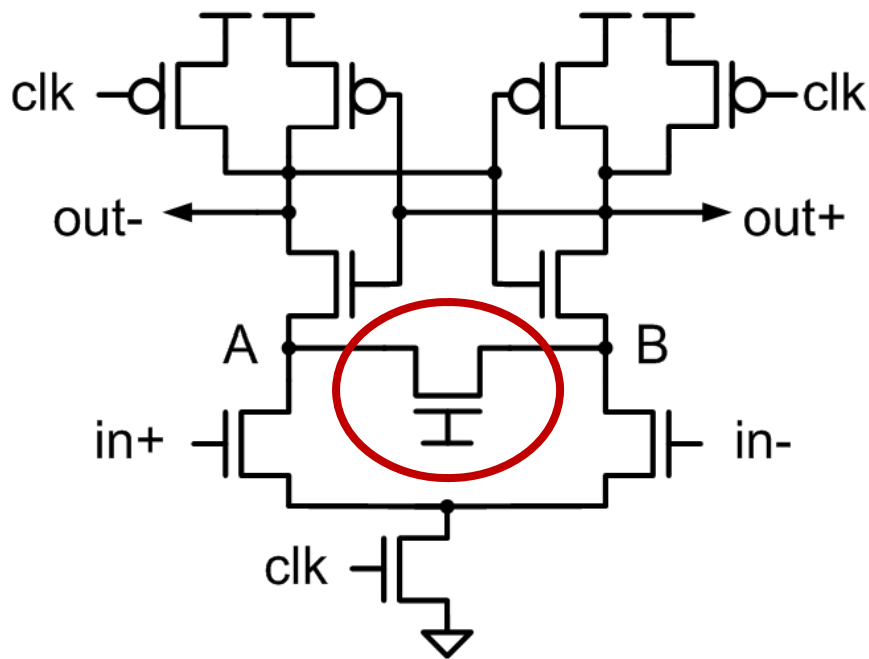

# Effects of Input and Output Loading

