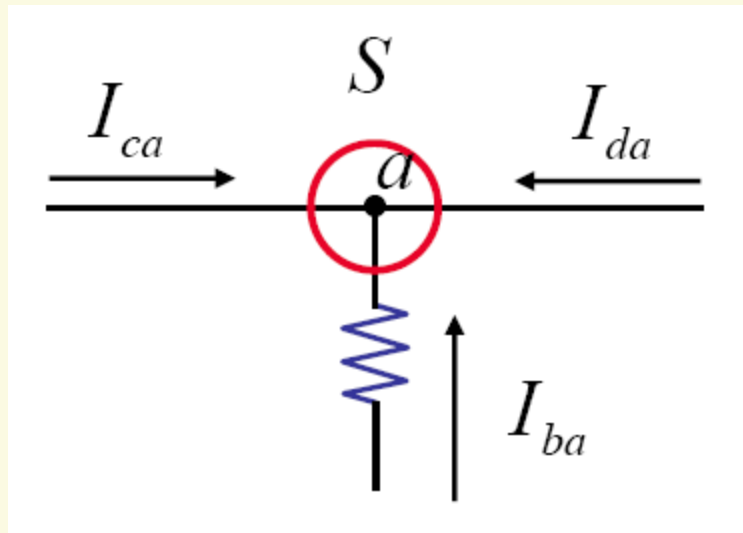


Chap. 2 Fundamentals of Electric Circuits

Kirchhoff's laws
Circuit Analysis: Basic Methods
Dependent Sources



KCL (Kirchhoff's Current Law)

- 📄 The sum of all branch currents flowing into a node is zero - charge conservation.



$$I_{ca} + I_{ba} + I_{da} = 0$$

Illustration of Kirchhoff's current law

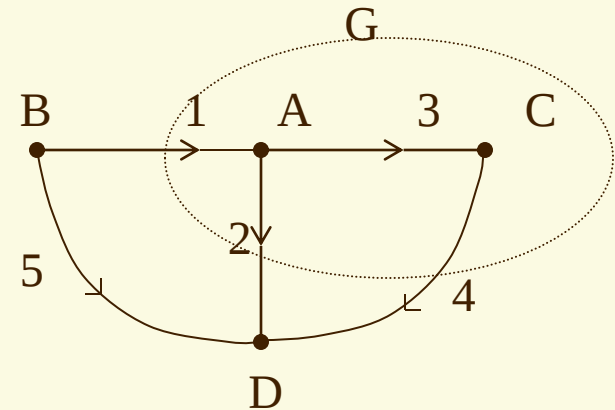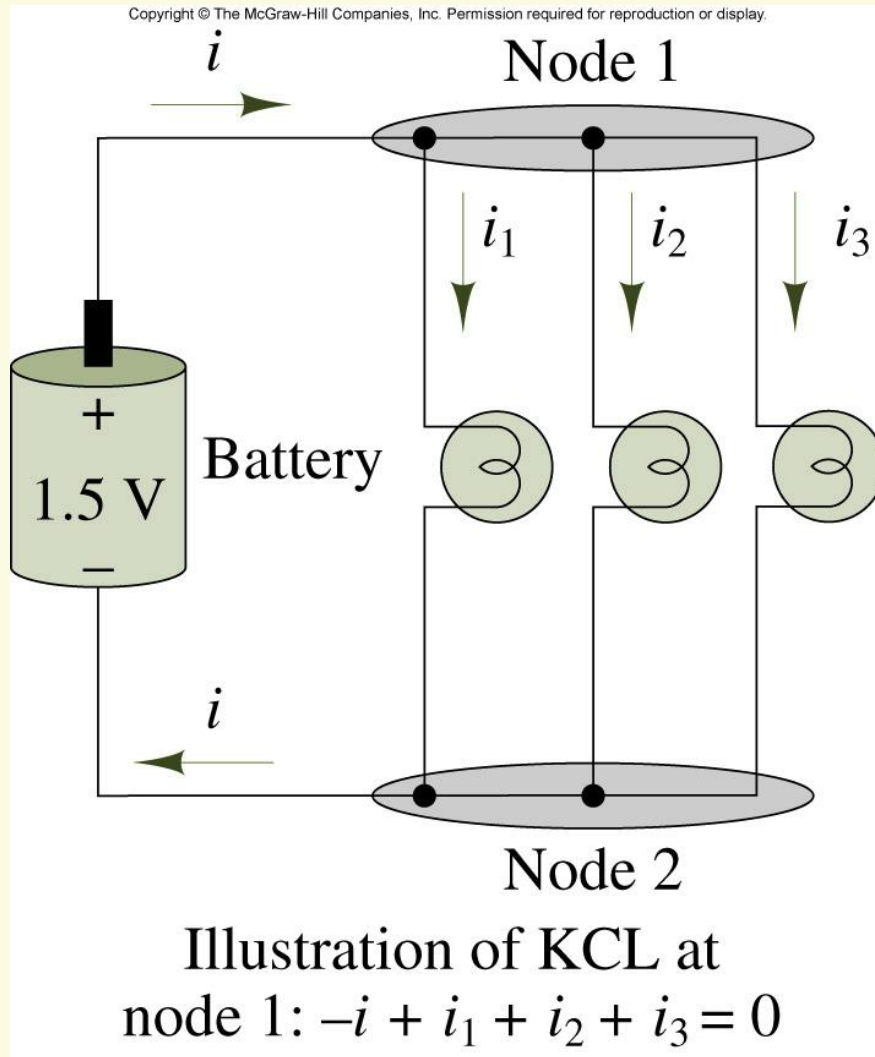


Node: $i_1 - i_2 - i_3 = 0$

G: $i_1 - i_2 - i_4 = 0$

Demonstration of KCL

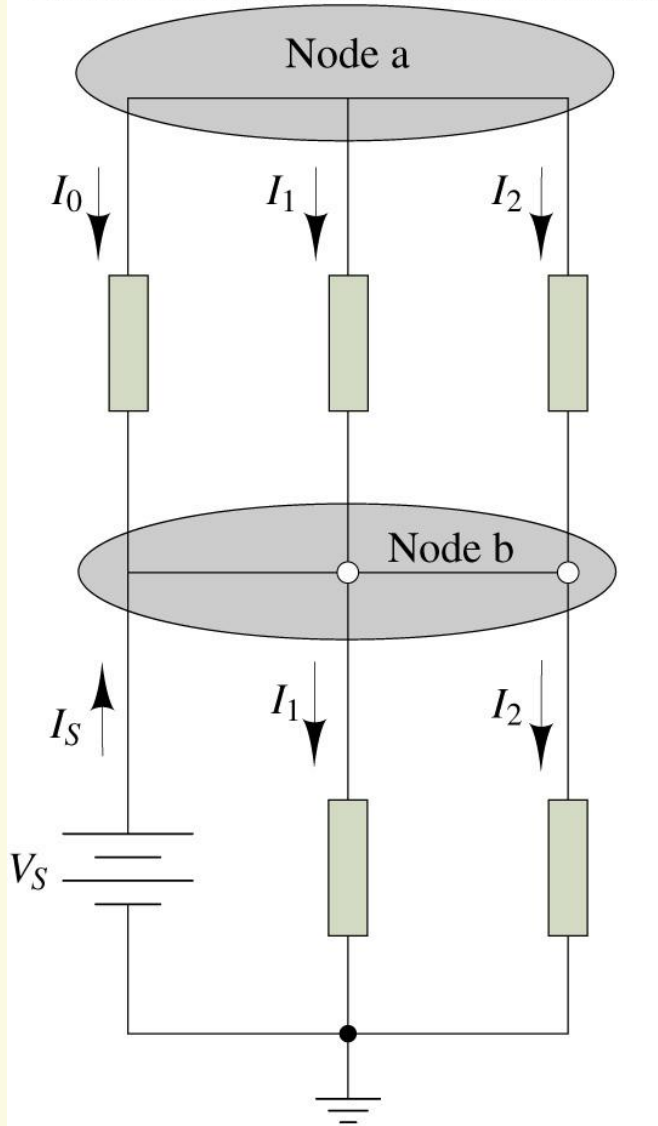
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$I_S = 5A, I_1 = 2A, I_2 = -3A, I_3 = 1.5A$$


Find I_0 and I_4

Example

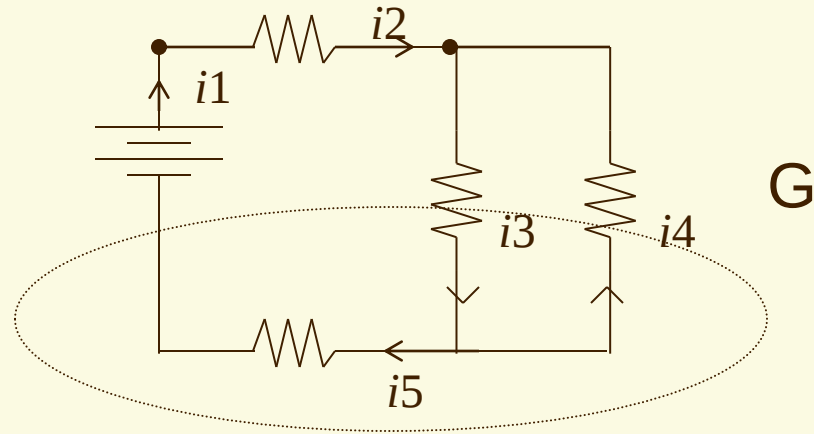


KVL (Kirchhoff's Voltage Law)

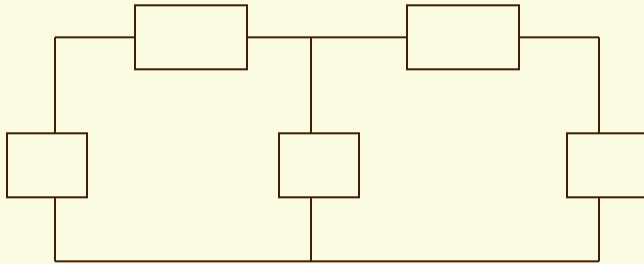- 📄 The algebraic sum of the branch voltages around any closed path in a network must be zero



(a)

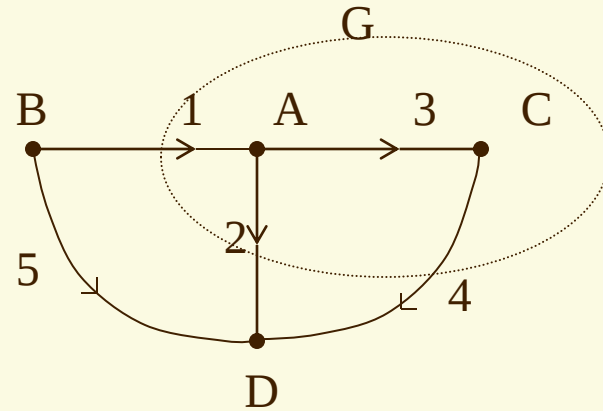


(b)

Node sequence B,A,D,B: $v_{BA} + v_{AD} + v_{DB} = 0$

Using node voltages: $v_{BA} = e_B - e_A$, $e_D = 0$

(reference node = D, reference voltage = 0)

Example

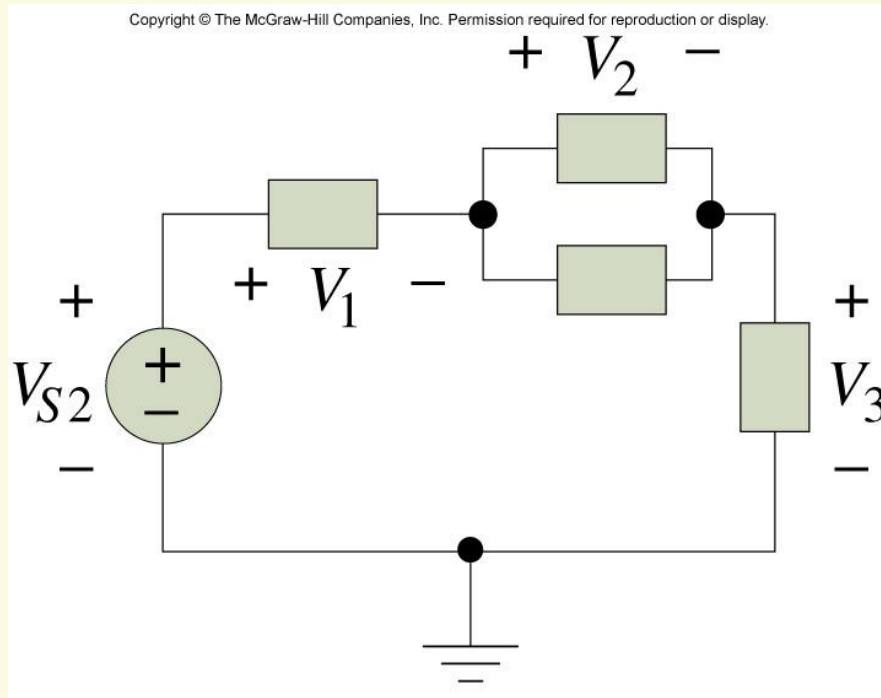


$$V_{S2} = 12 \text{ V}, V_1 = 6 \text{ V}, V_3 = 1 \text{ V}$$


Find V_2 .

Some Useful Facts

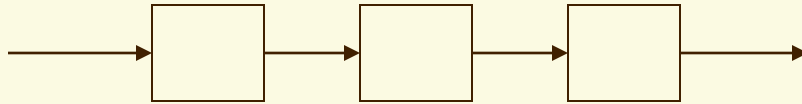- 📄 The branch currents passing through series-connected elements must be the same.




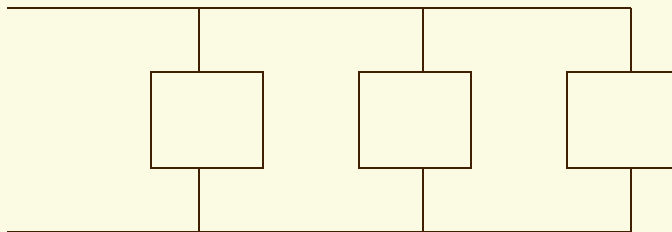- 📄 The voltages across parallel-connected elements must be the same.



Independent Equations

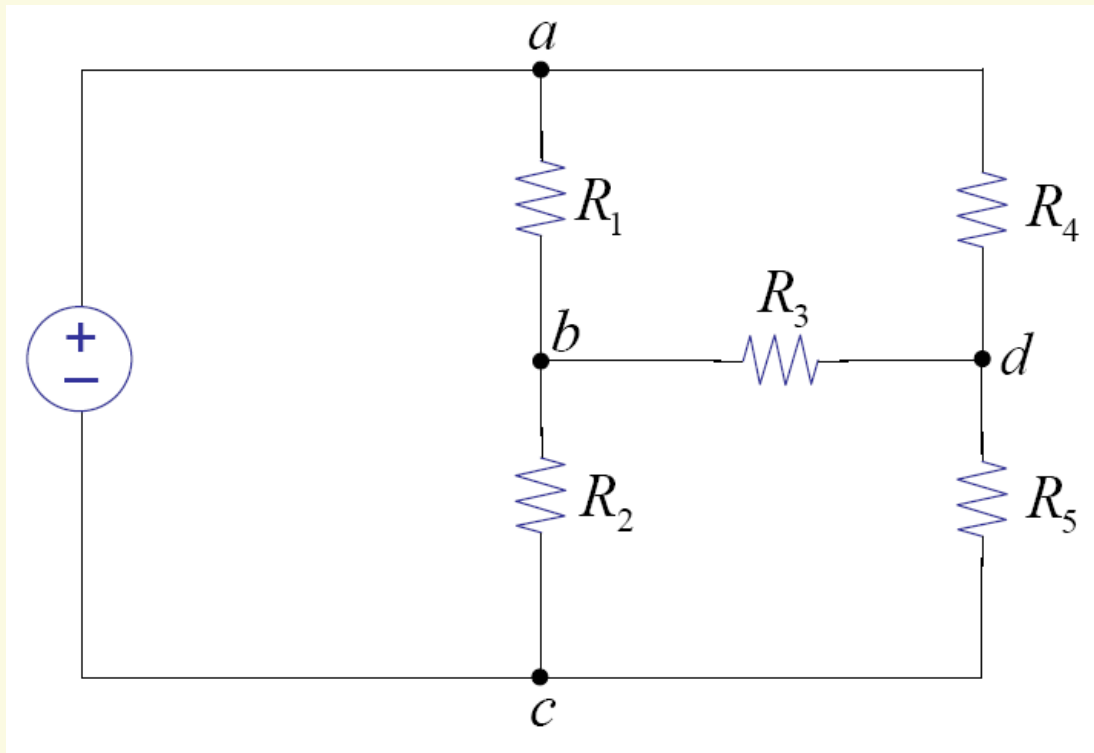- How many independent KCL equations can be made?
- How many independent KVL equations can be made?




Circuit Analysis: Basic Method

 Goal: find all V and I s for all elements

- Write element's V – I relationships
- Write KCL for all nodes
- Write KVL for all loops

Example

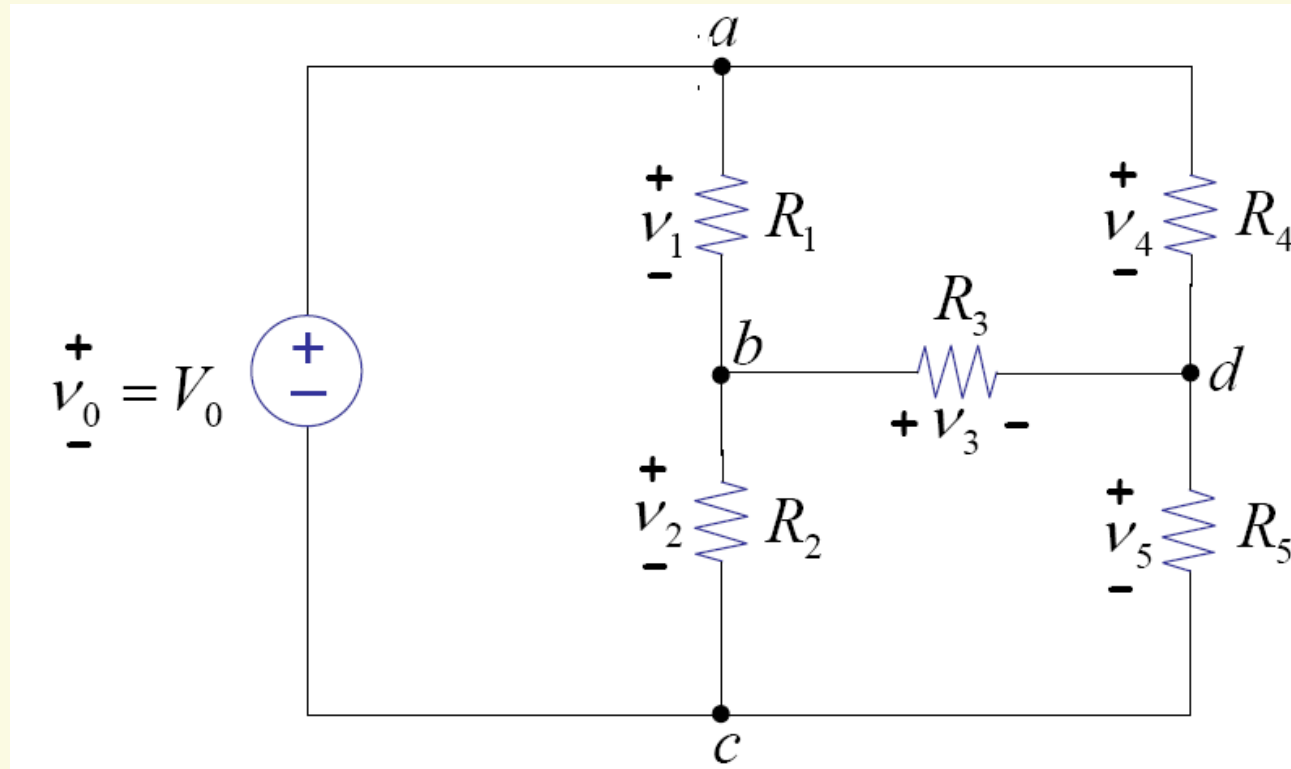


Element's equations


KCL

KVL

Voltage Divider and Series Resistors

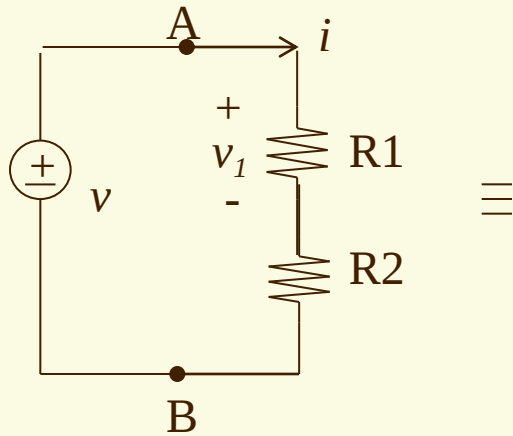


(a) Voltage divider

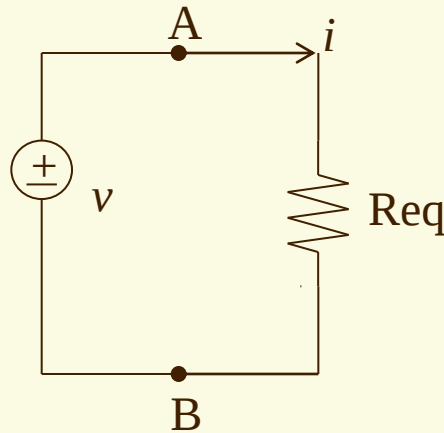


(b) Equivalent resistance

$$v_1 = \frac{R_1}{R_1 + R_2} v$$

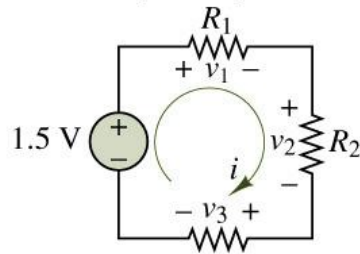

The current i flows through each of the four series elements. Thus, by KVL,

$$1.5 = v_1 + v_2 + v_3$$

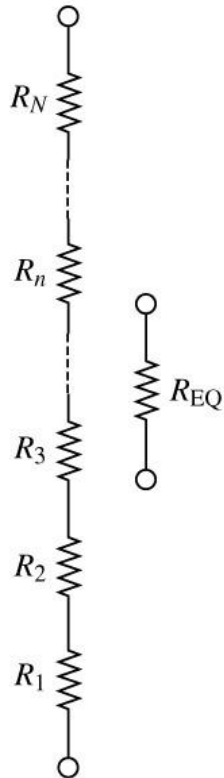


N series resistors are equivalent to a single resistor equal to the sum of the individual resistances.


$$R_1 = 10 \text{ k}\Omega, R_2 = 6 \text{ k}\Omega, R_3 = 8 \text{ k}\Omega$$

Find V_3 .

Current Divider and Parallel Resistors

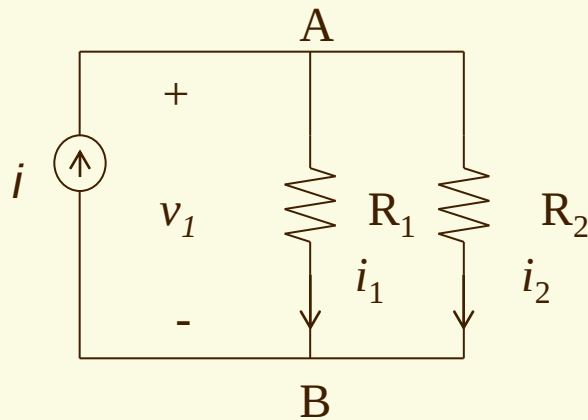

(a) Current divider

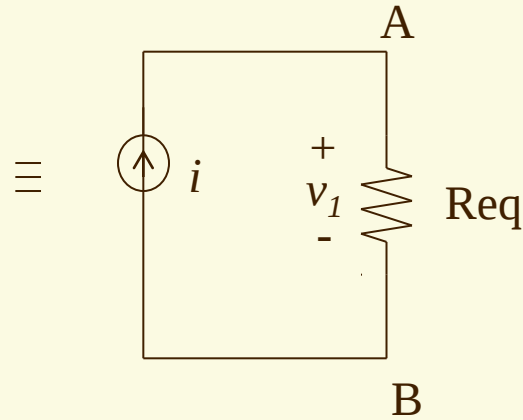


(b) Equivalent resistance


$$i_1 = \frac{G_1}{G_1 + G_2} i = \frac{R_2}{R_1 + R_2} i$$

Parallel circuits

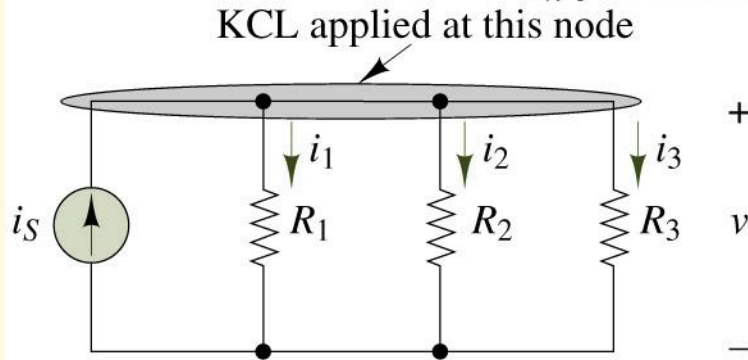Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




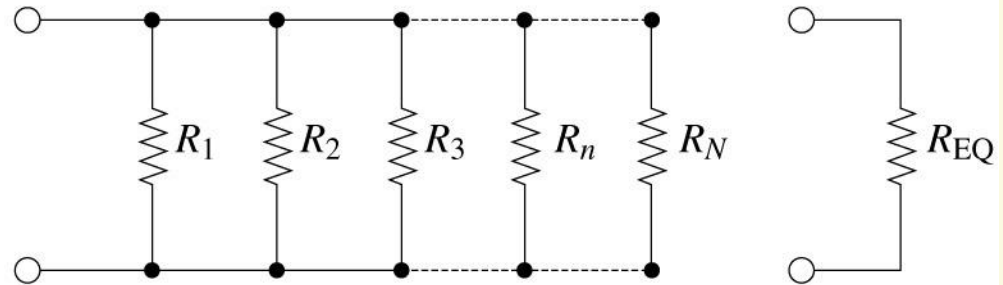The voltage v appears across each parallel element; by KCL, $i_S = i_1 + i_2 + i_3$



N resistors in parallel are equivalent to a single equivalent resistor with resistance equal to the inverse of the sum of the inverse resistances.


Example 1

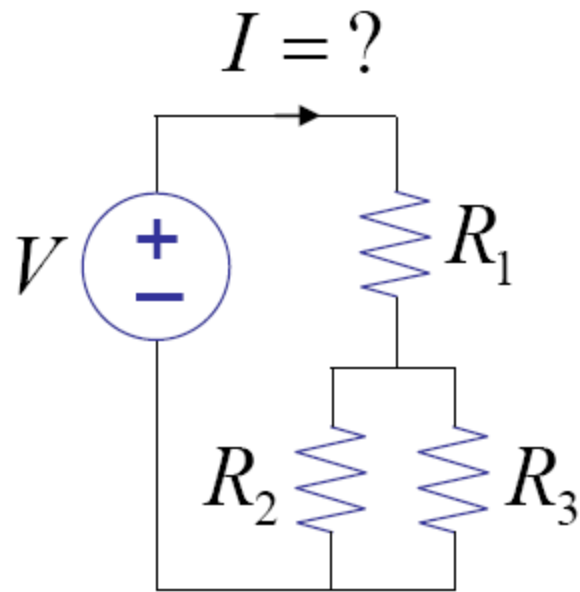

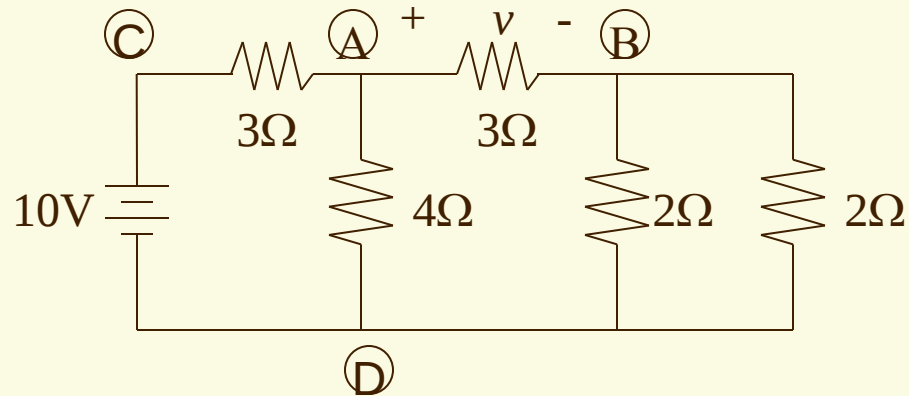Example 2




Find the voltage (v) between nodes A and B.




Wheatstone bridge circuits

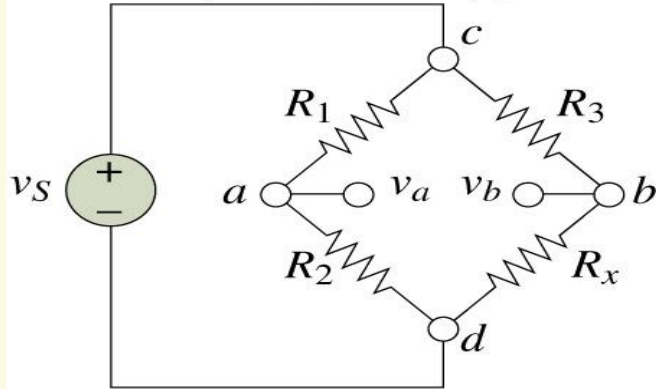Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.



(a)

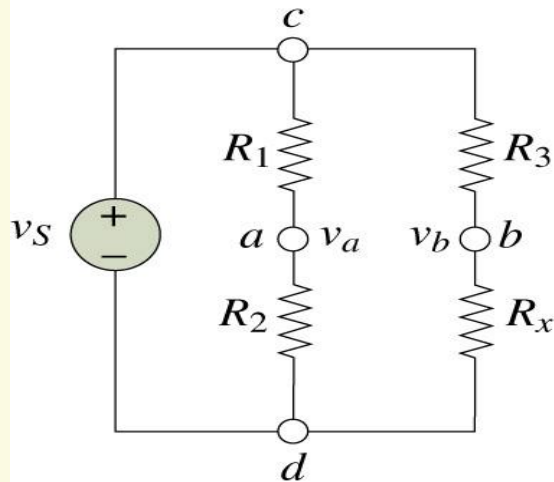

(b)


R_1 , R_2 , R_3 are known

Find R_x by measuring V_{ab}


Symbols for dependent sources

Figure 2.4

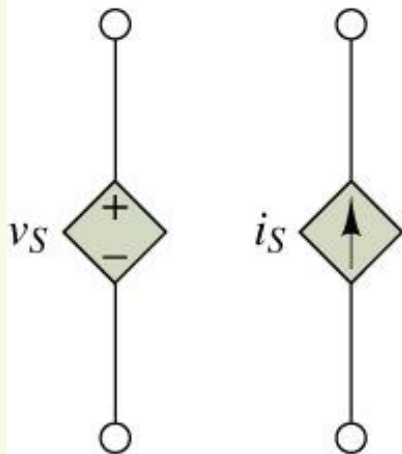
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Source type	Relationship
Voltage controlled voltage source (VCVS)	$v_S = \mu v_x$
Current controlled voltage source (CCVS)	$v_S = r i_x$
Voltage controlled current source (VCCS)	$i_S = g v_x$
Current controlled current source (CCCS)	$i_S = \beta i_x$

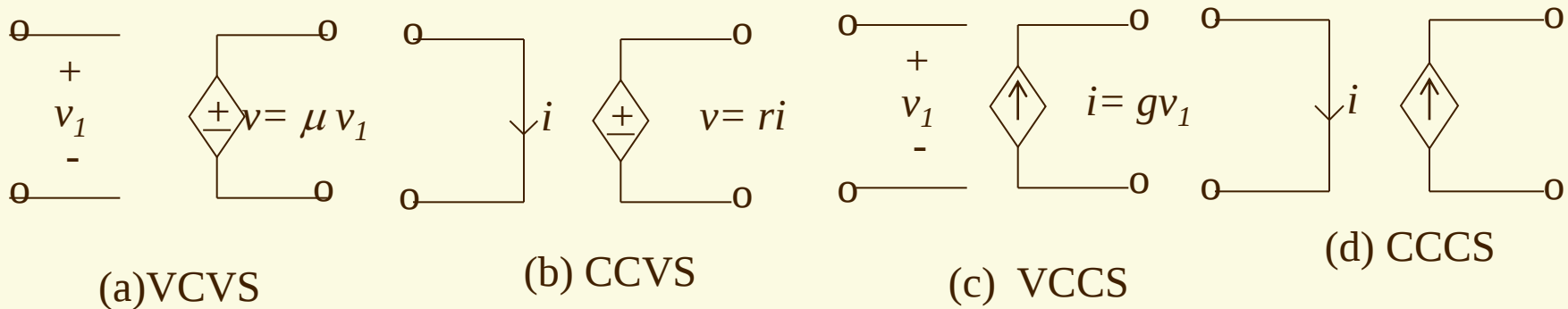

Example 3

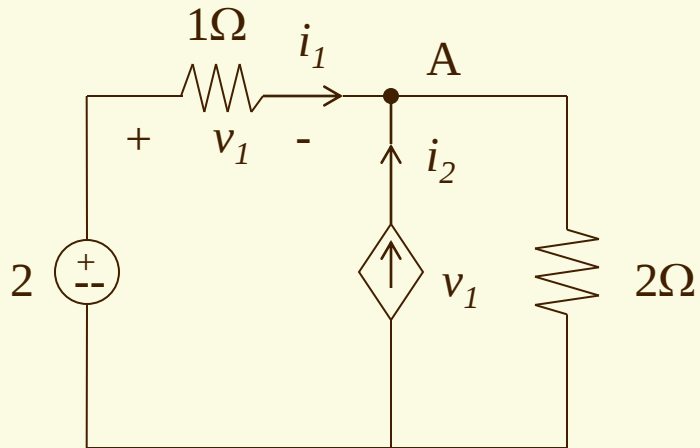


What is the current on 2 Ω resistor?

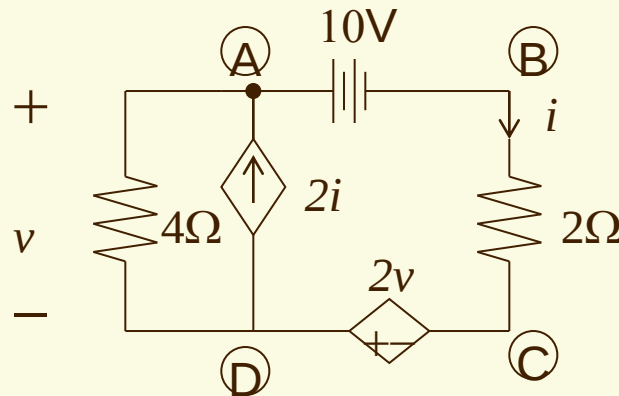Example 4



Find v . How much power does 4 ohm resistor consume?



Now, the voltage source is changed from 10V to 5V. How much power does 4 ohm resistor consume?

Conclusion

-  Kirchhoff's current and voltage laws
-  Basic Circuit Analysis Method
-  Series-parallel circuits
-  Dependent Sources

Chap. 3 Network Theorems

Node (voltage) analysis

Mesh (current) analysis

Superposition principle


Thevenin/Norton equivalent circuits

Branch current in Node Analysis

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

In the node voltage method, we assign the node voltages v_a and v_b ; the branch current flowing from a to b is then expressed in terms of these node voltages.

$$i = \frac{v_a - v_b}{R}$$

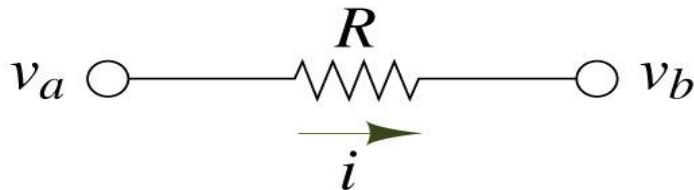

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

By KCL: $i_1 - i_2 - i_3 = 0$. In the node voltage method, we express KCL by

$$\frac{v_a - v_b}{R_1} - \frac{v_b - v_c}{R_2} - \frac{v_b - v_d}{R_3} = 0$$


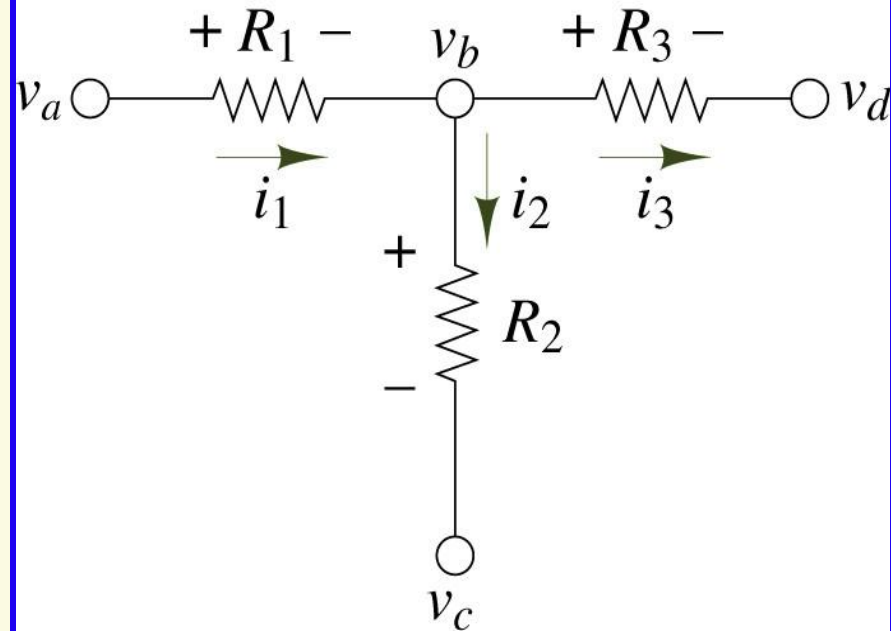


Illustration of Node Analysis

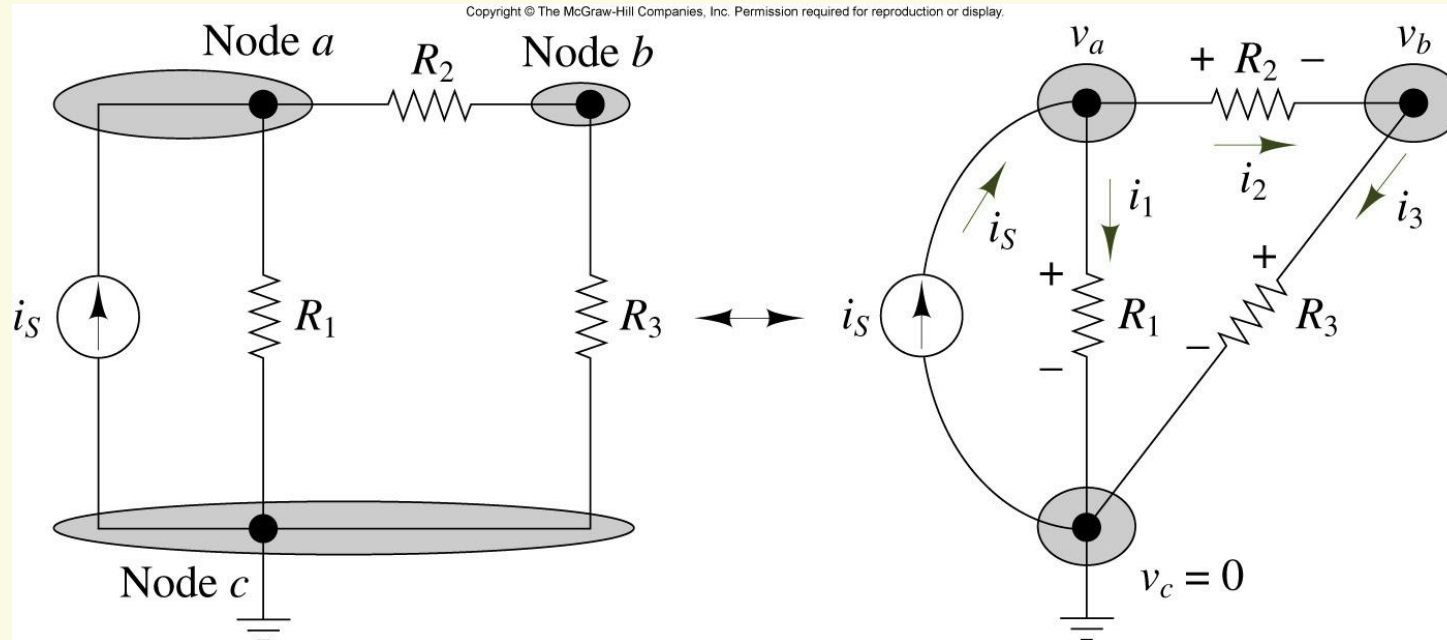


Example


$I_1 = 10\text{mA}$, $I_2 = 50\text{mA}$, $R_1 = 1\text{k}$, $R_2 = 2\text{k}$

$R_3 = 10\text{k}$, $R_4 = 2\text{k}$

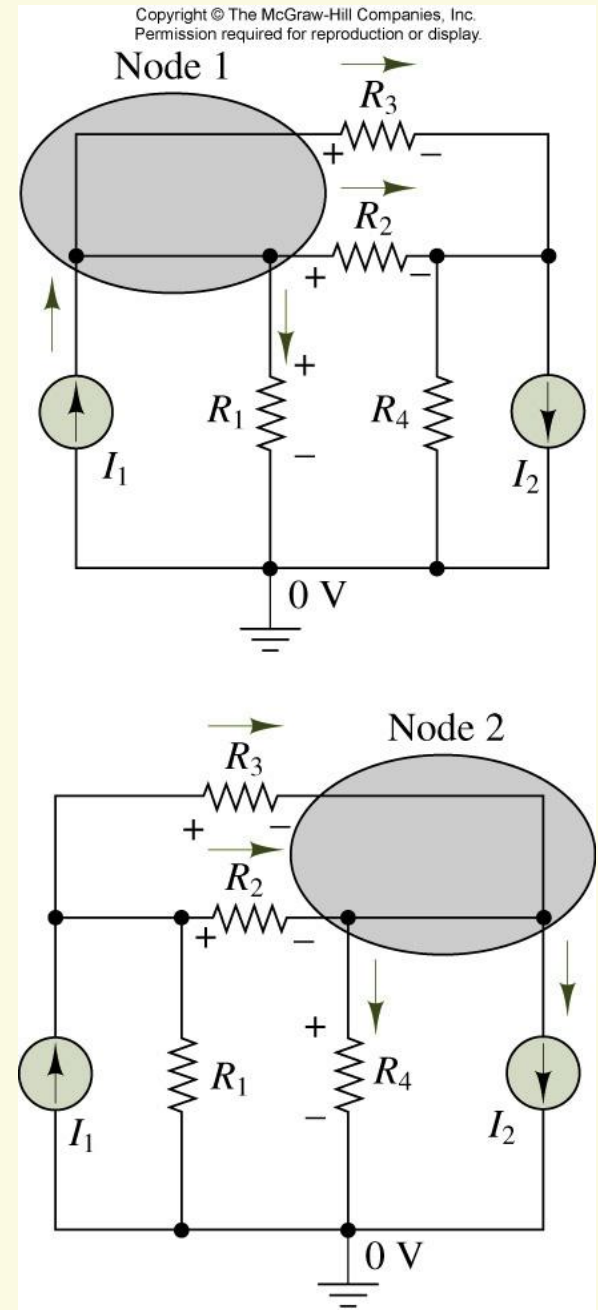
Find all node voltages and branch currents



Matrix Formulation

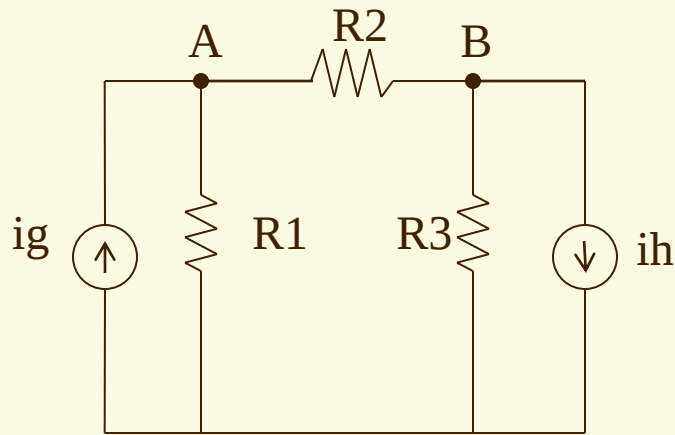


(a)

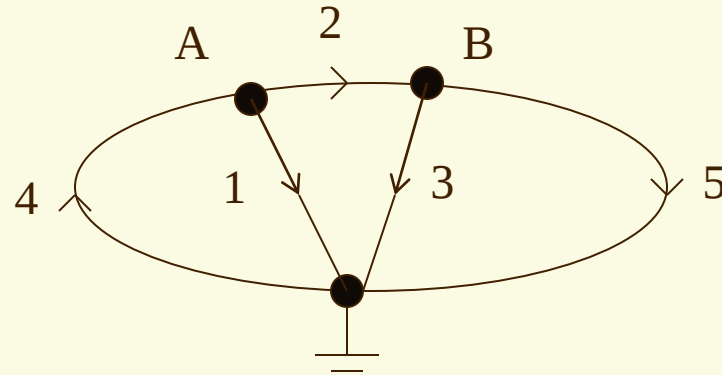


(b)

$$\begin{aligned}
 G_1 e_A + G_2 (e_A - e_B) &= i_g \\
 G_2 (e_B - e_A) + G_3 e_B &= -i_h
 \end{aligned}
 \Rightarrow
 \begin{pmatrix} G_1 + G_2 & -G_2 \\ -G_2 & G_2 + G_3 \end{pmatrix}
 \begin{pmatrix} e_A \\ e_B \end{pmatrix}
 =
 \begin{pmatrix} i_g \\ -i_h \end{pmatrix}$$

Node Analysis with Voltage Source

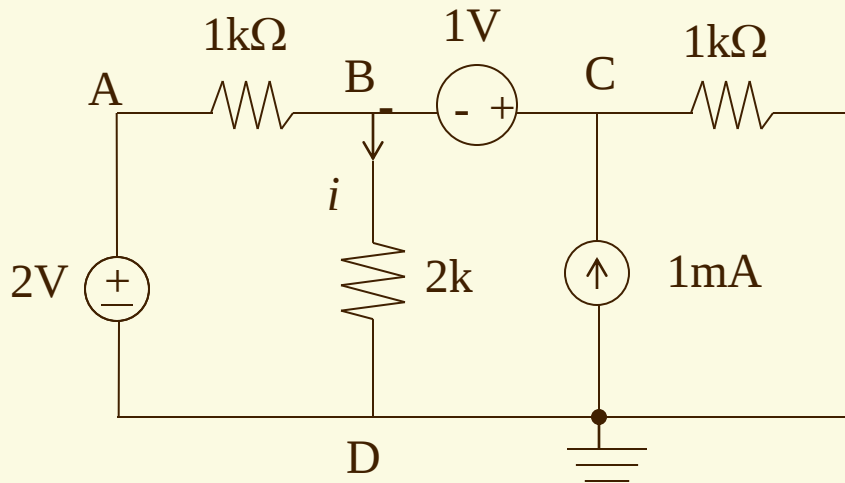

(a)

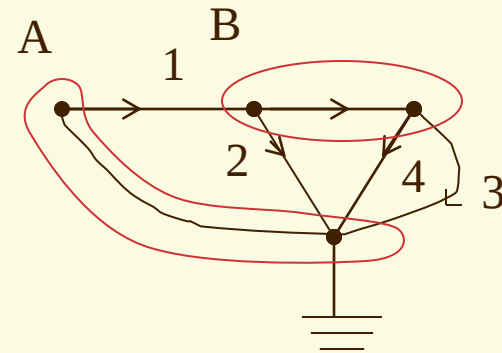

(b)

$$\frac{e_B - e_A}{1} + \frac{e_B}{2} + \frac{e_C}{1} = 1 \Rightarrow \frac{e_B - 2}{1} + \frac{e_B}{2} + \frac{e_B + 1}{1} = 1$$


$$e_B = 0.8, \quad i = 0.4(mA)$$

Circuit for Example

$I = 1\text{A}$, $V = 3\text{V}$, $R_1 = 2$, $R_2 = 2$

$R_3 = 4$, $R_4 = 3$


Find i

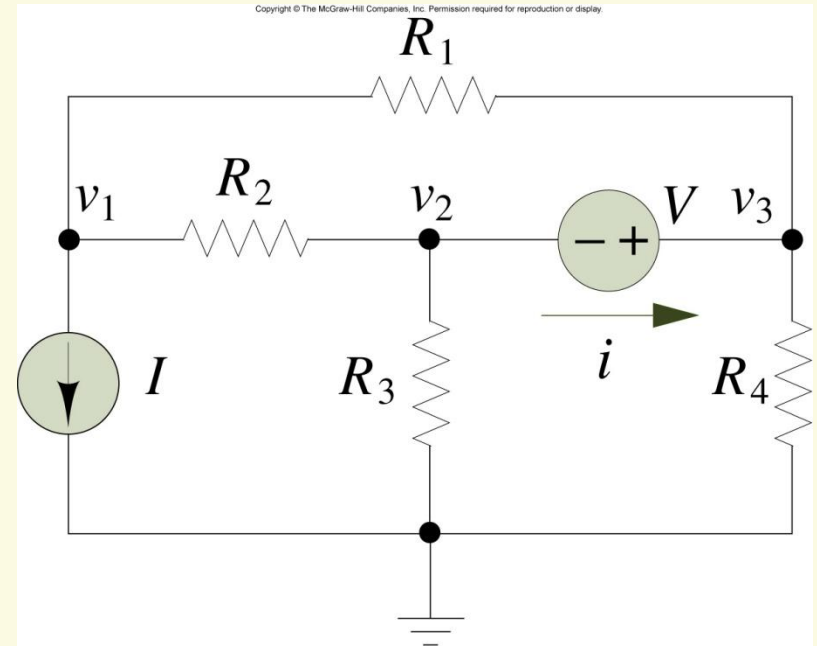

Basic principle of Mesh(Loop) Analysis


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

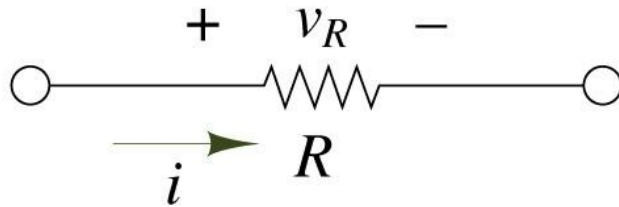The current i , defined as flowing from left to right, establishes the polarity of the voltage across R .



Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

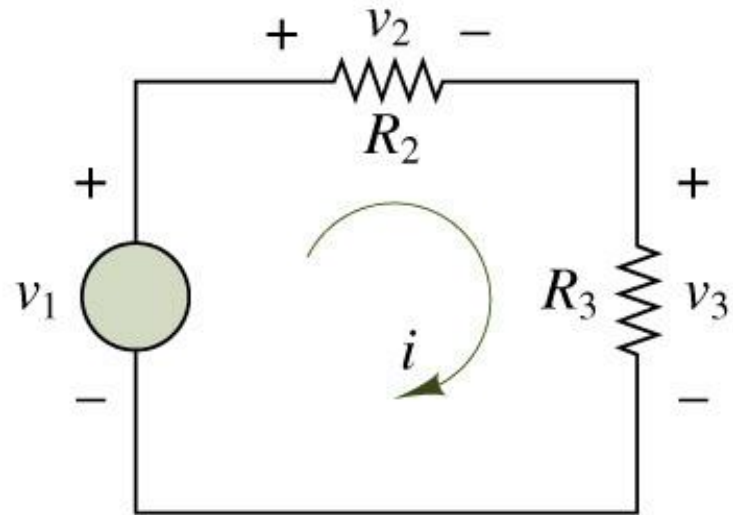Once the direction of current flow has been selected, KVL requires that $v_1 - v_2 - v_3 = 0$.




A mesh

A two-mesh circuit

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Mesh 1: KVL requires that
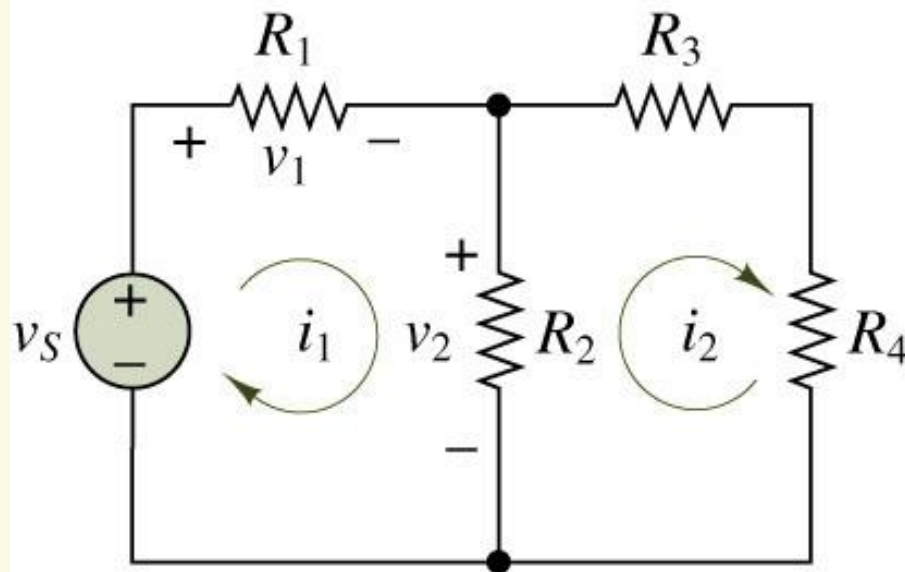
$$v_S - v_1 - v_2 = 0, \text{ where } v_1 = i_1 R_1, \\ v_2 = (i_1 - i_2) R_2.$$




Example


$V_1 = 10V$, $V_2 = 9V$, $V_3 = 1V$,

$R_1 = 5k$, $R_2 = 10k$, $R_3 = 5k$, $R_4 = 5k$


Find i

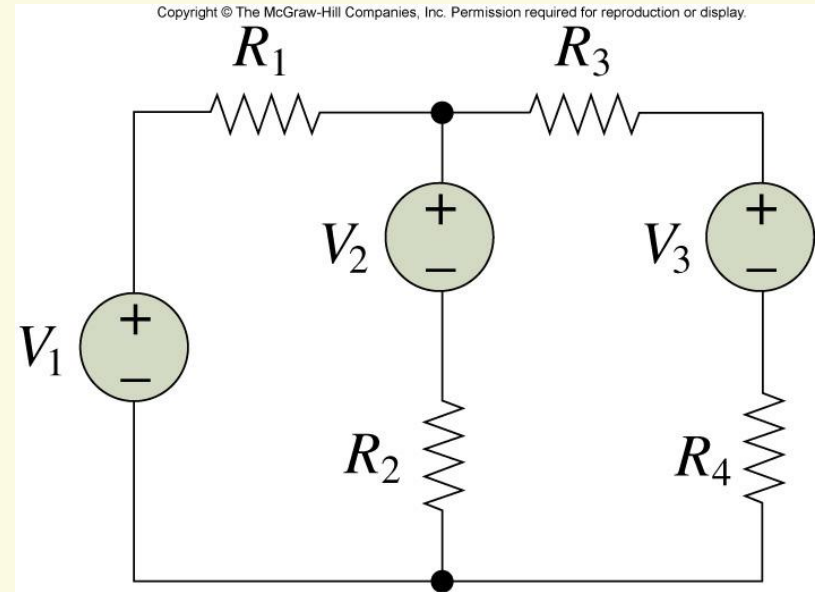

Mesh Analysis with Current Sources

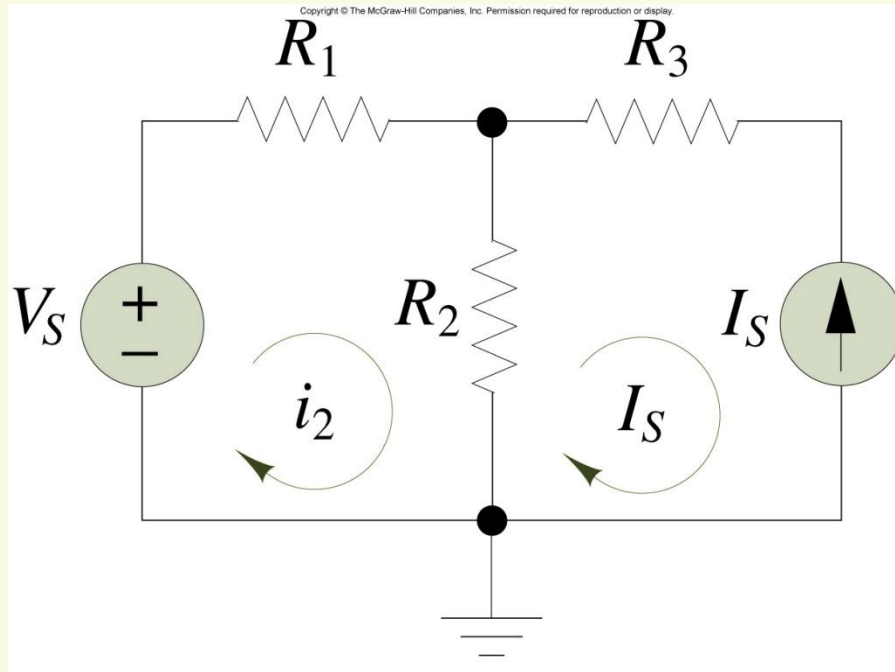


Matrix Formulation

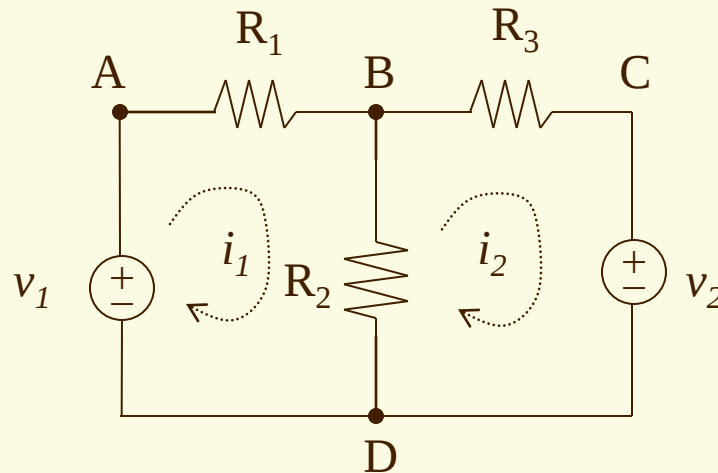

$$\begin{aligned} R_1 i_1 + R_2 (i_1 - i_2) &= v_1 \\ R_2 (i_2 - i_1) + R_3 i_2 &= -v_2 \end{aligned} \quad \Rightarrow \quad \begin{pmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} v_1 \\ -v_2 \end{pmatrix}$$

Node Analysis with Controlled Sources

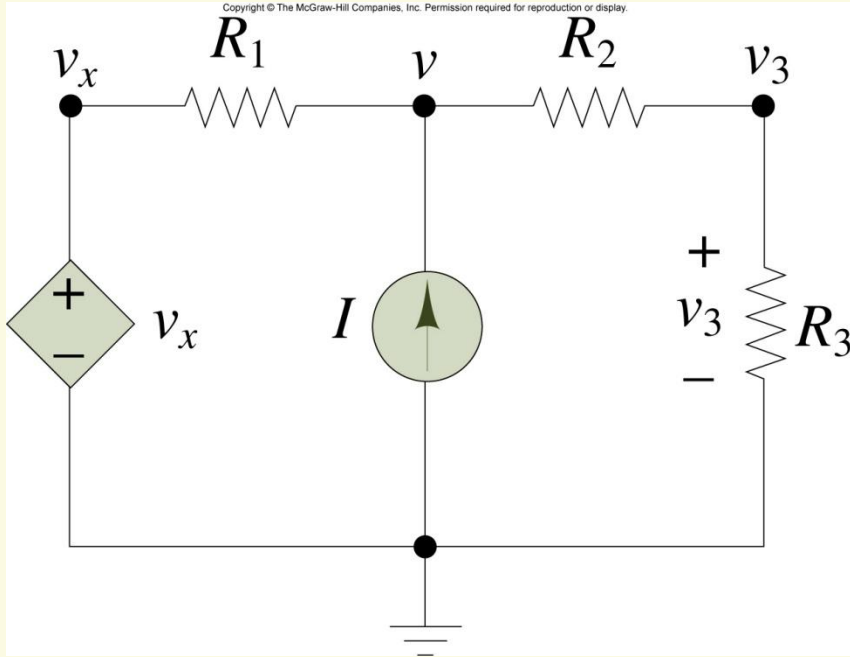

$$I = 0.5\text{mA}, V_x = 2 \times v_3$$


$$R_1 = 5\text{k}, R_2 = 2\text{k}, R_3 = 4\text{k}$$

Find v


Exercise



Find i using the node analysis technique

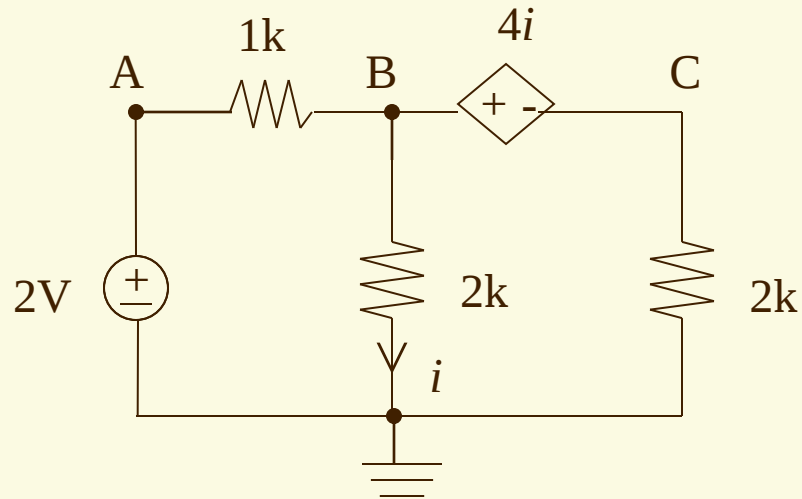

Loop Analysis

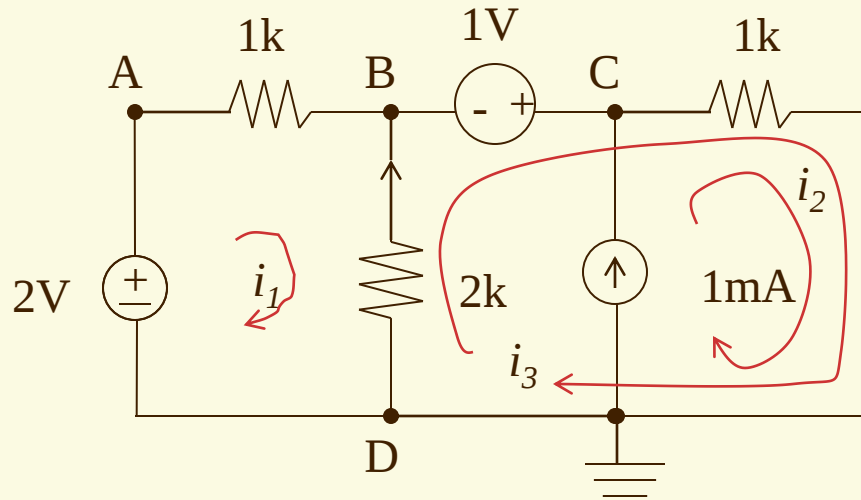


$$\{A, B, D, A\} \quad i_1 + 2(i_1 - i_3) = 2$$

$$\{B, C, D, B\} \quad (i_3 + i_2) + 2(i_3 - i_1) = 1, \quad i_2 = 1$$

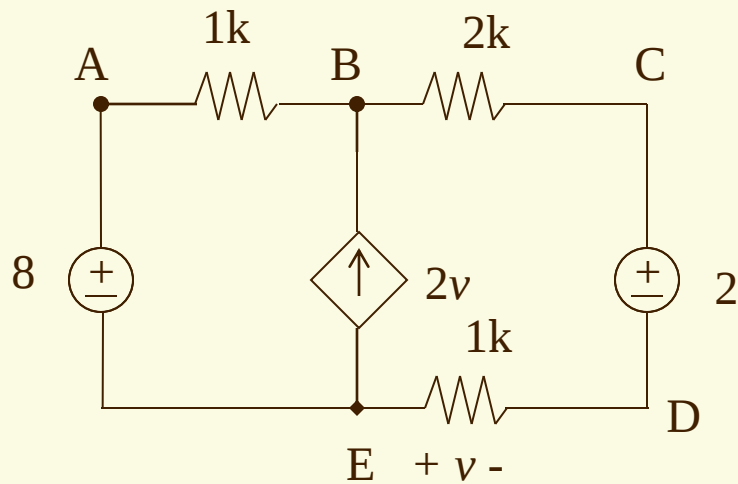Exercise



Find v using the loop analysis technique.




Linearity

Write node equations


$$e = f_1(R_1, R_2)V + f_2(R_1, R_2)I$$

Linear in V and I

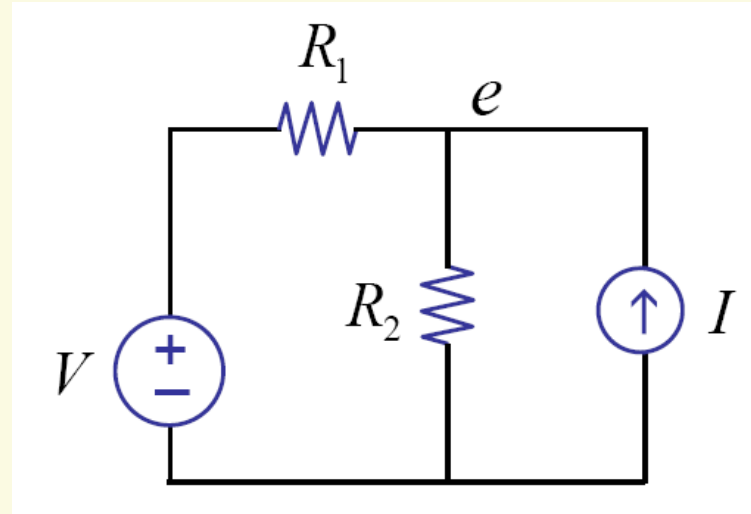


Linearity

Homogeneity

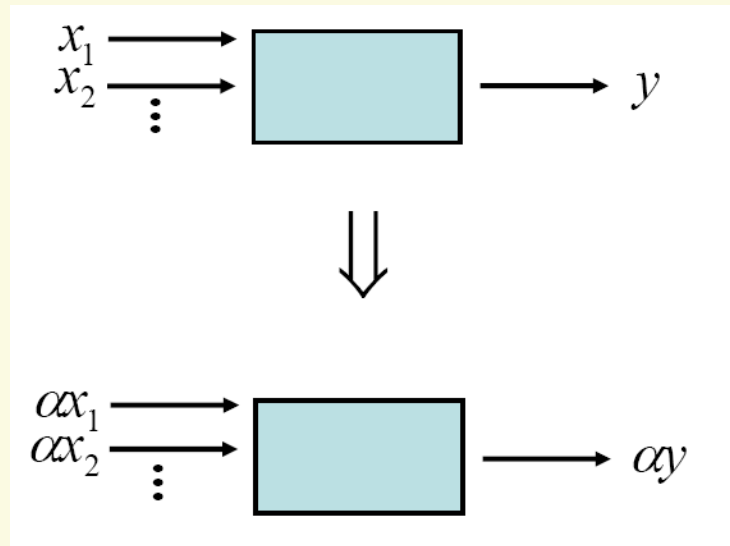


Superposition

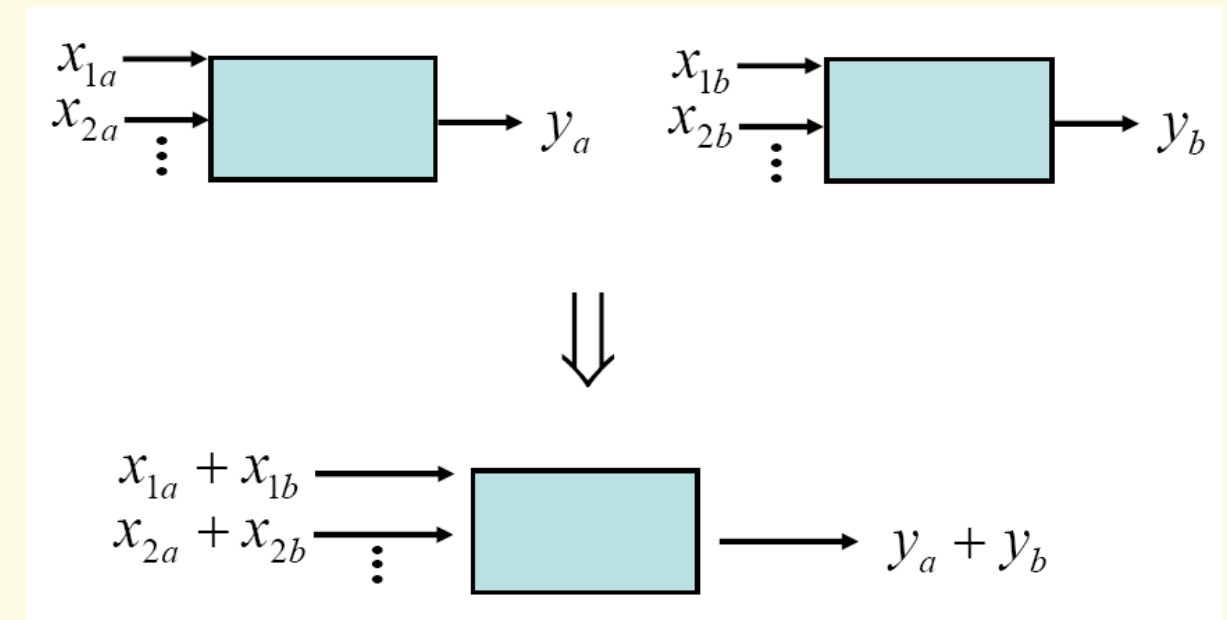

Superposition Principle

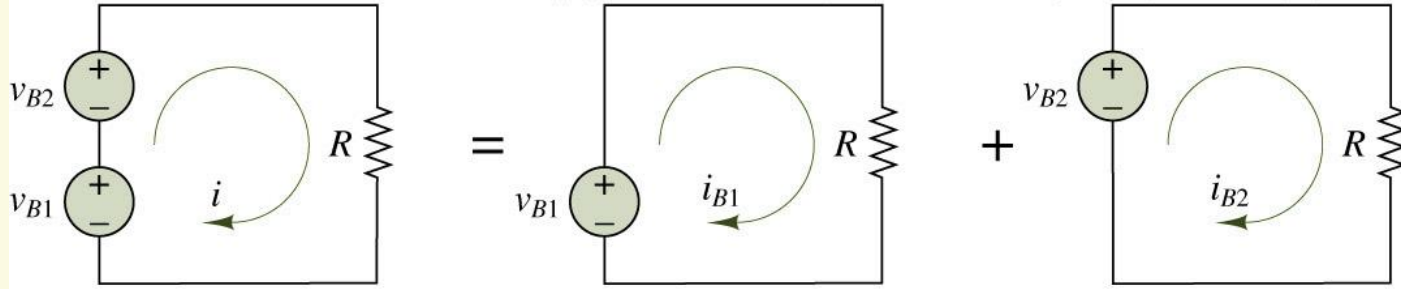Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




The net current through R is the sum of the individual source currents:
 $i = i_{B1} + i_{B2}$.


Zeroing Voltage and Current Sources

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

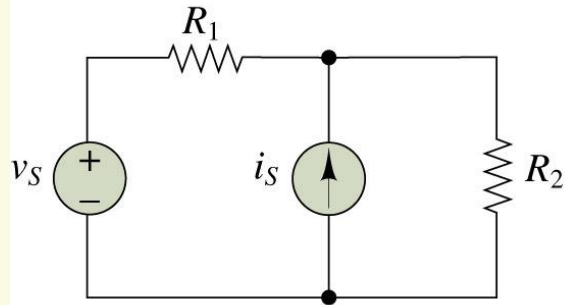1. In order to set a voltage source equal to zero, we replace it with a short circuit.




A circuit

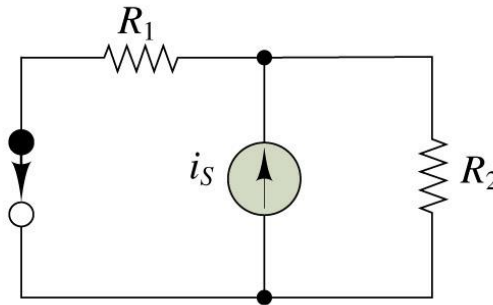


The same circuit with $v_S = 0$

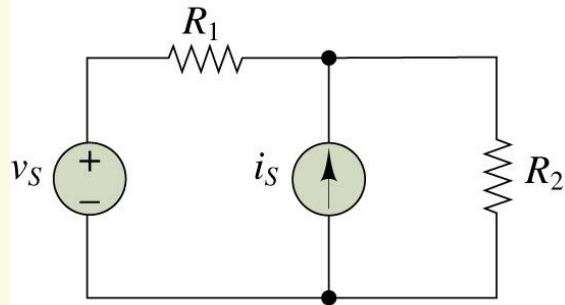2. In order to set a current source equal to zero, we replace it with an open circuit.




A circuit

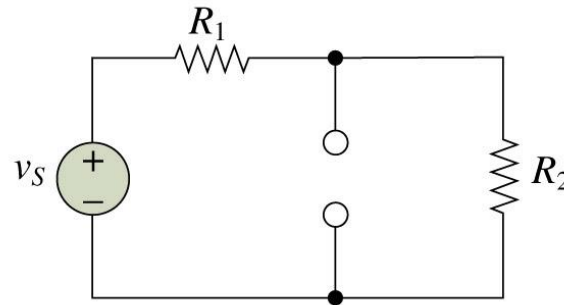


The same circuit with $i_S = 0$


Exercise

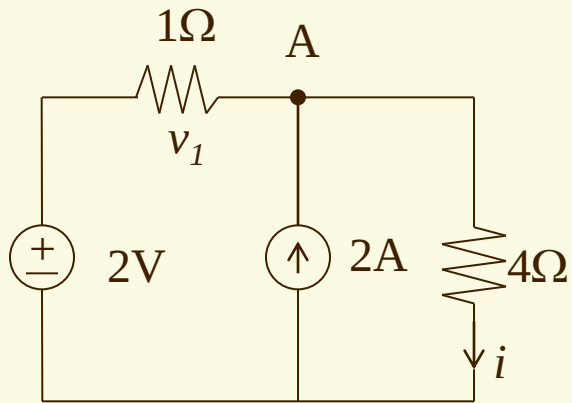

(a)

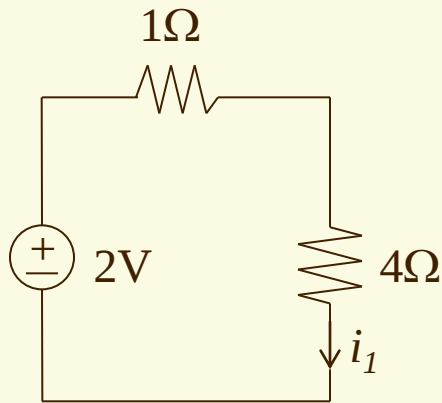


(b)

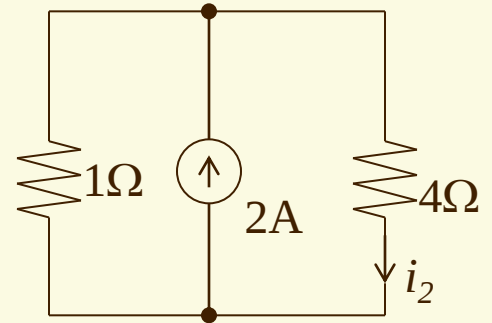


(c)


Superposition with Controlled Sources

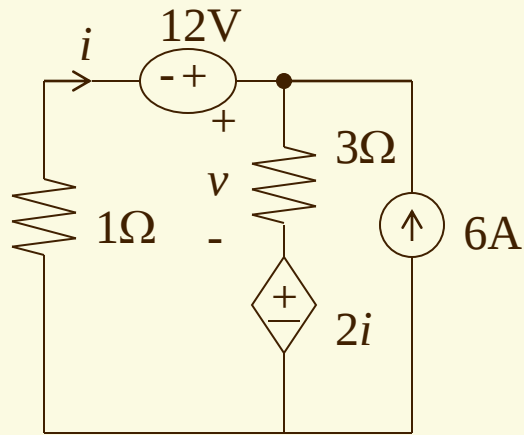

(a)

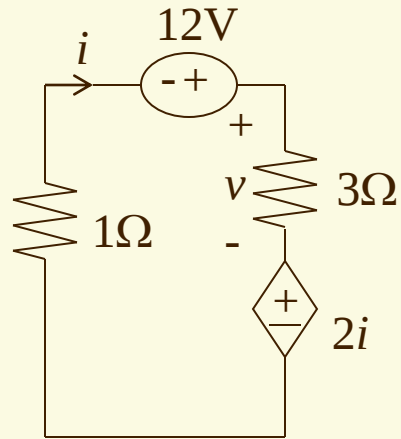

(b)

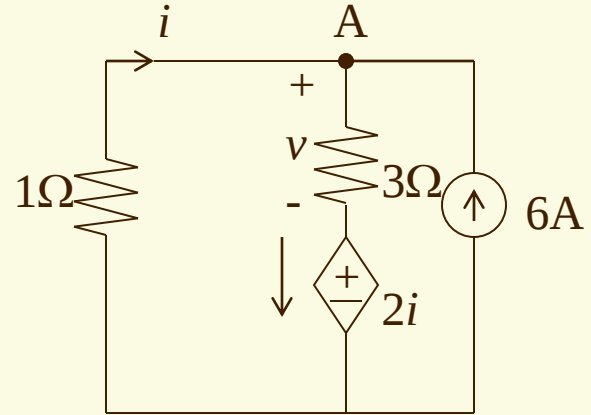

B
(c)


$$v = v_{(b)} + v_{(c)}$$

$$(b): 12 = 3i + 2i + i \rightarrow i = 2, v = 6$$

$$(c): i + 3(i + 6) + 2i = 0 \rightarrow i = -3, v = 9$$

Deviation of the Thevenin's Network

Consider

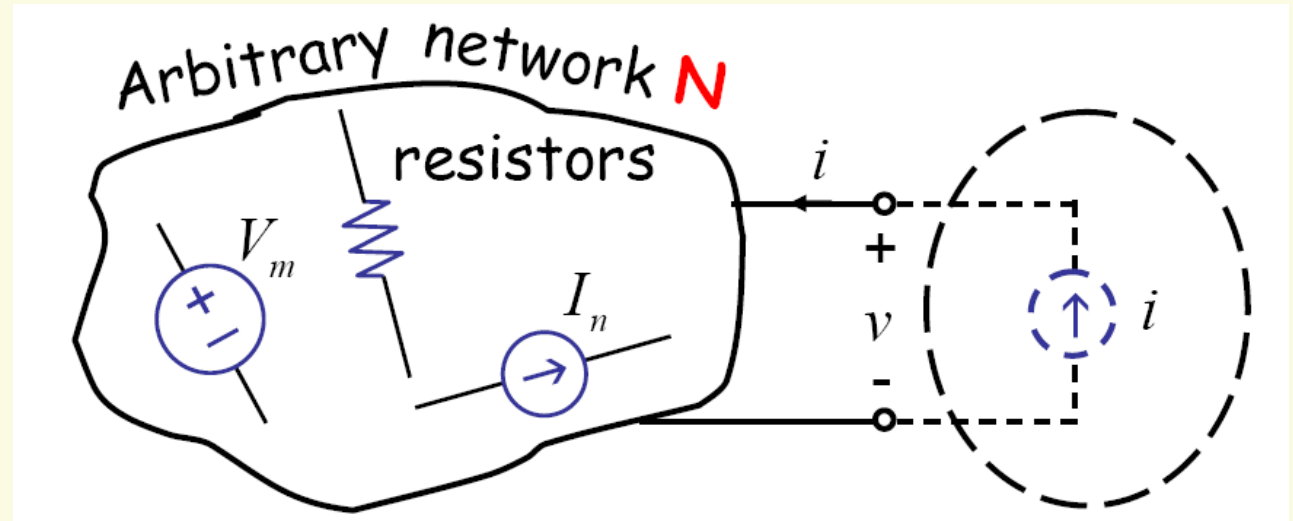

By superposition

$$v = \sum_m \alpha_m V_m + \sum_n \beta_n I_n + Ri$$

↑

no
units

↑

resistance
units

also
independent
of external
excitement &
behaves like
a resistor

By setting

$$\left\{ \begin{array}{l} \forall_n I_n = 0, \\ i = 0 \end{array} \right. \quad \left\{ \begin{array}{l} \forall_m V_m = 0, \\ i = 0 \end{array} \right.$$


All

$$\left\{ \begin{array}{l} \forall_n I_n = 0, \\ \forall_m V_m = 0 \end{array} \right.$$

independent of external
excitation and behaves like a
voltage " v_{TH} "

Thevenin equivalent network

$$v = v_{TH} + R_{TH}i$$

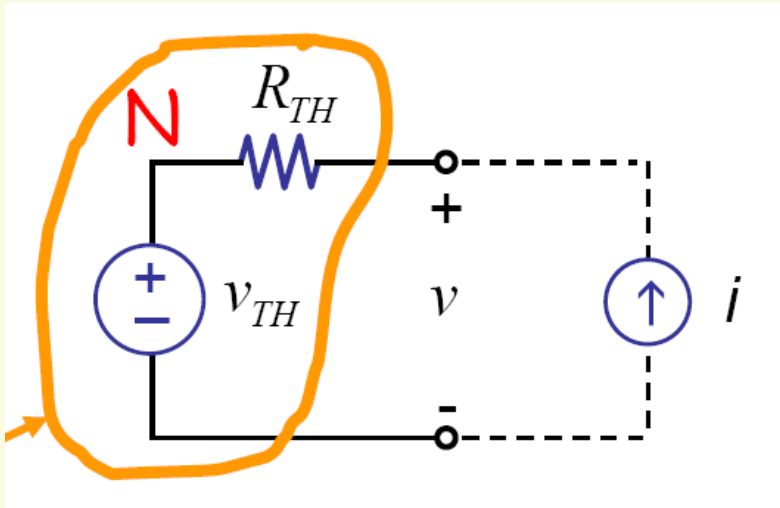

Thevenin equivalent network



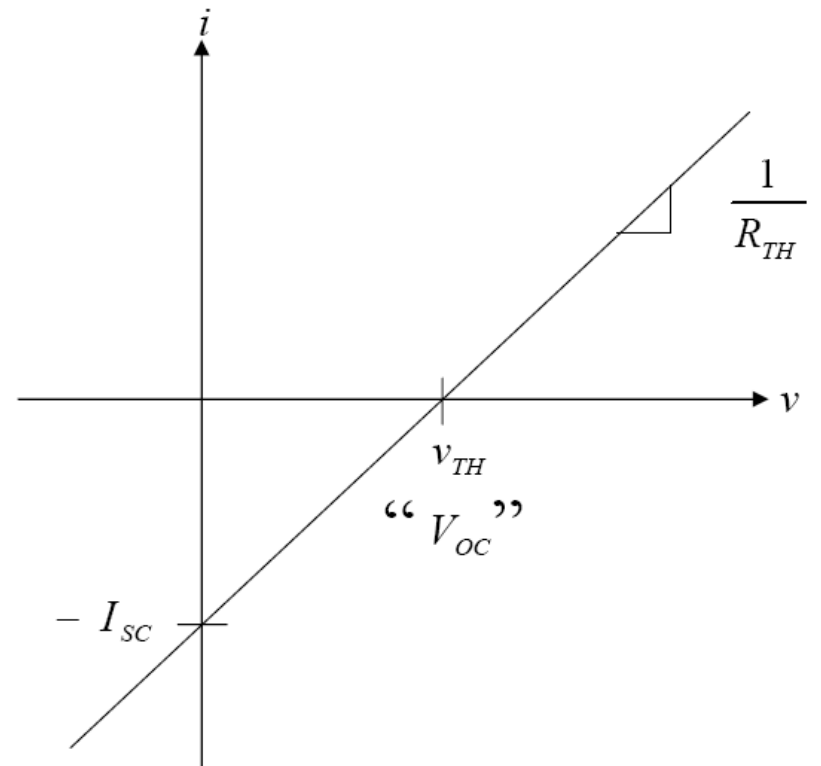


Illustration of Thévenin theorem

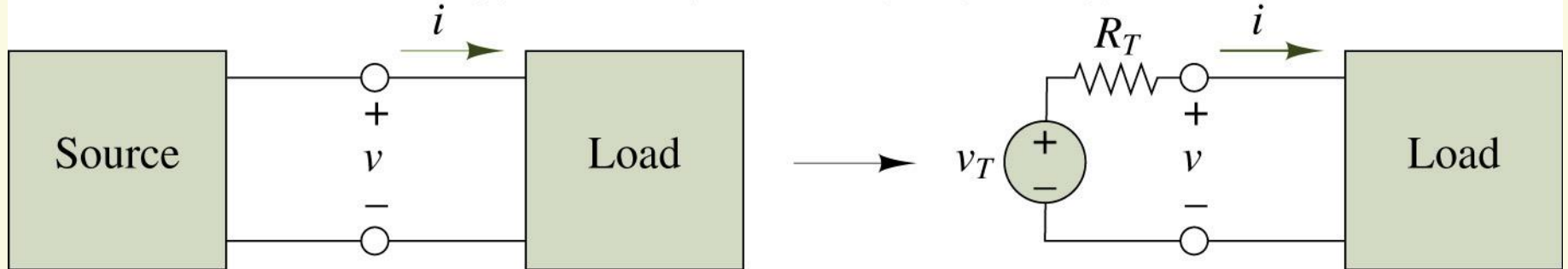Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Open-circuit and Thévenin voltage

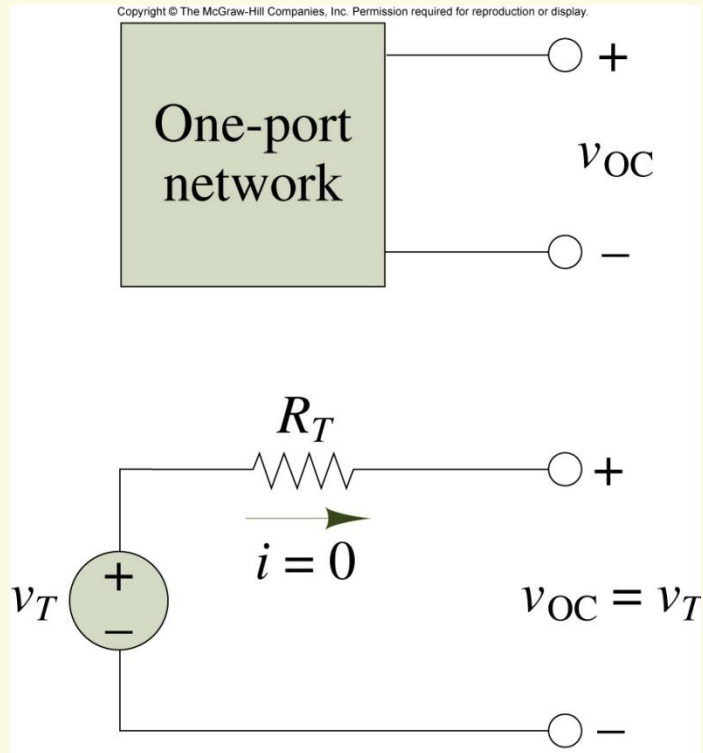


Computation of Thévenin resistance

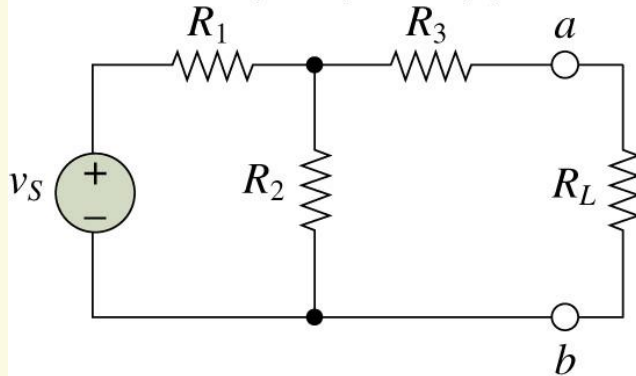Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.




Complete circuit

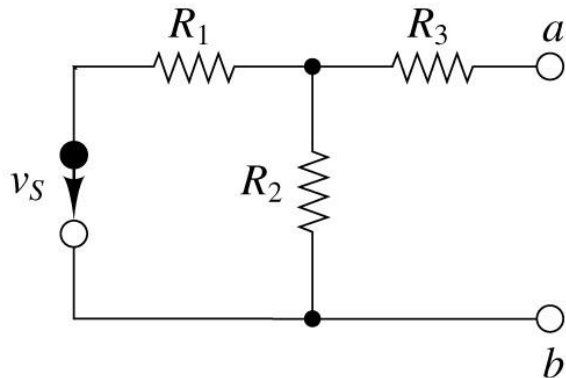


Circuit with load removed
for computation of R_T . The voltage
source is replaced by a short circuit.

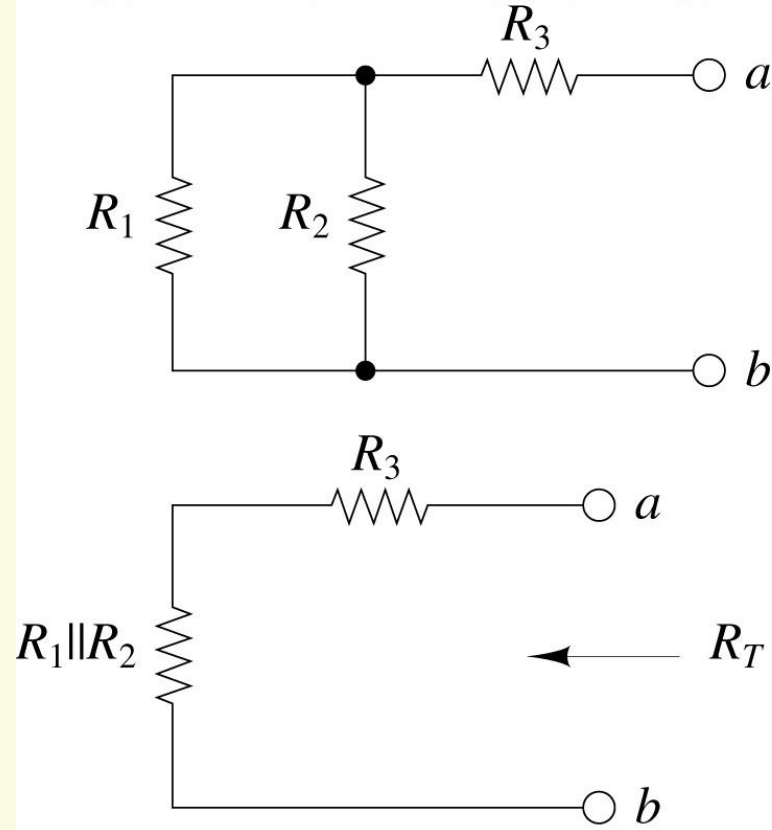Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Example

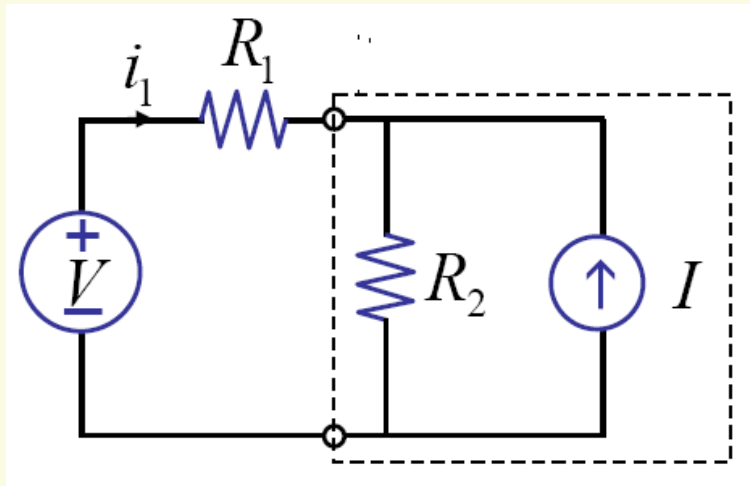


A circuit and its Thévenin equivalent

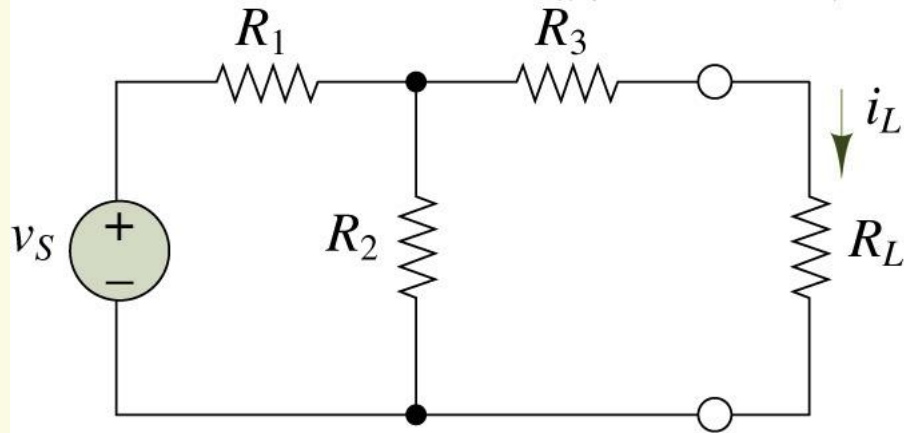Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




A circuit

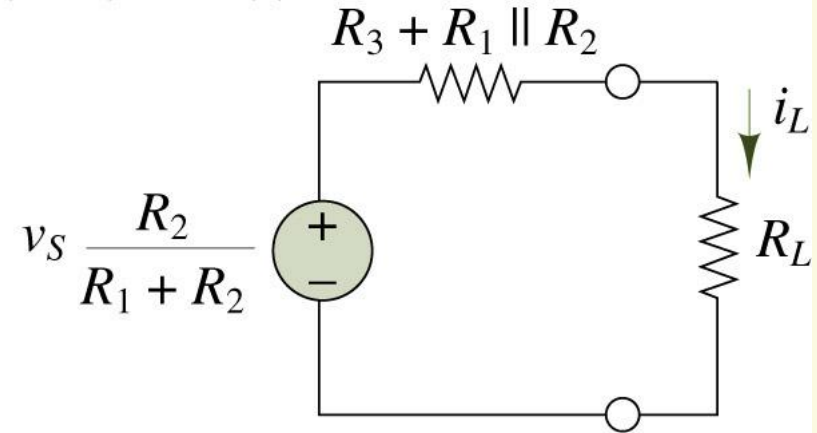

Its Thévenin equivalent

Norton equivalent circuit

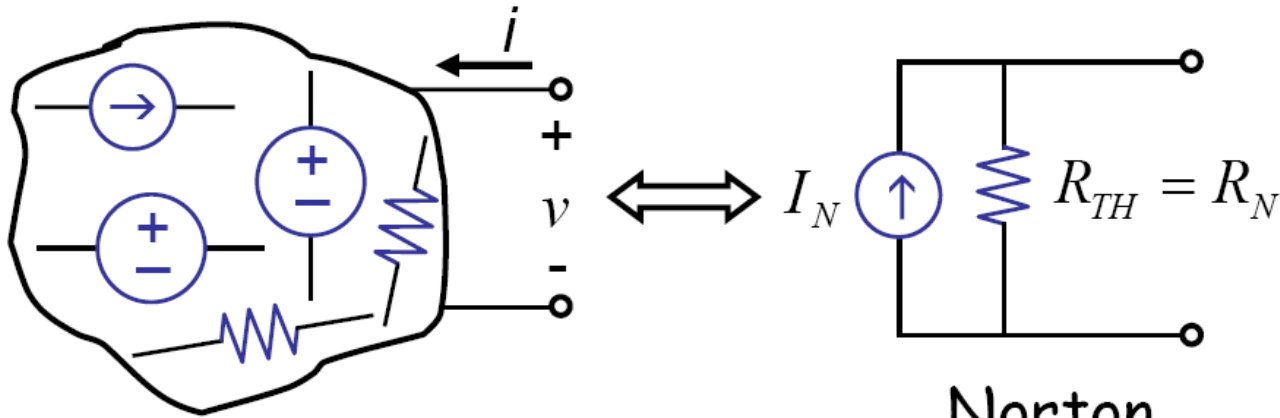


Norton
equivalent


$$I_N = \frac{V_{TH}}{R_{TH}}$$

Illustration of Norton theorem

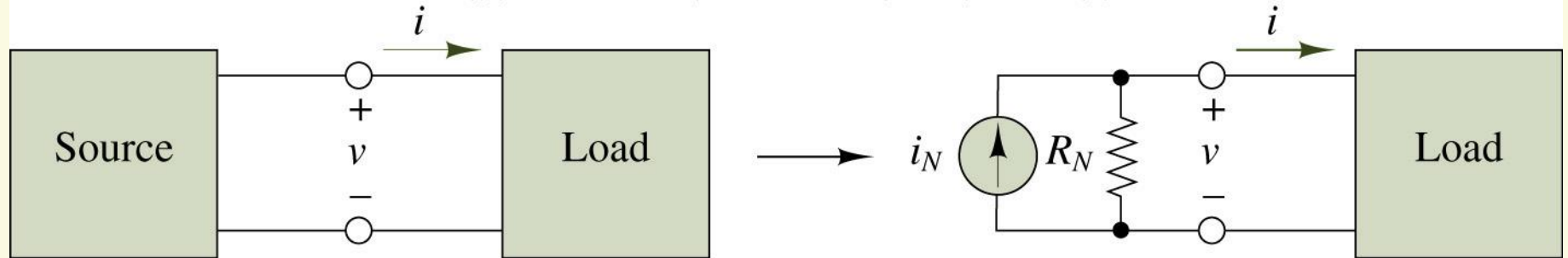
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Computation of Norton current

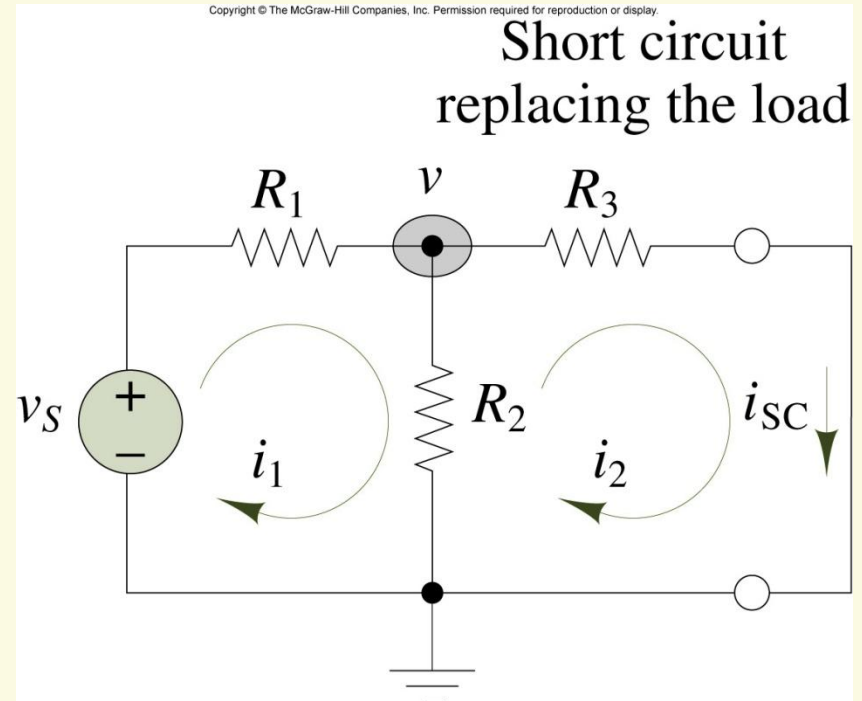



Example

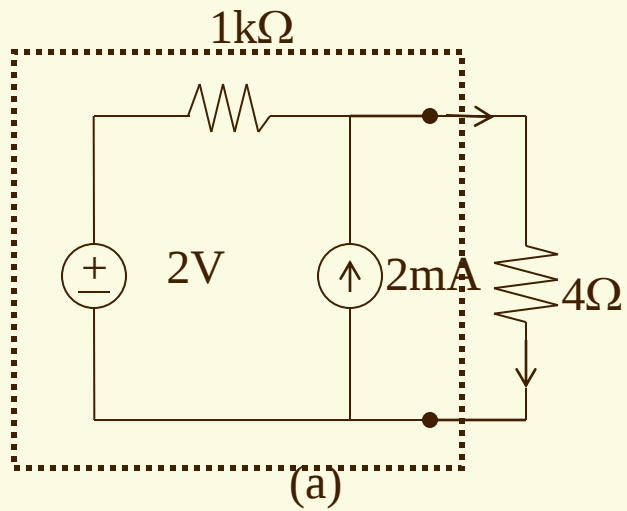

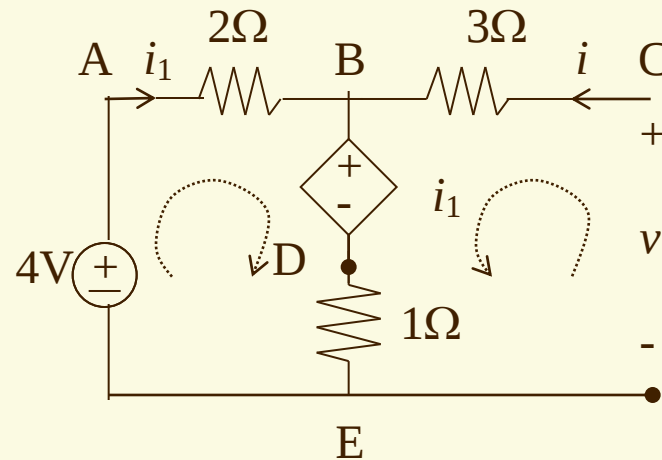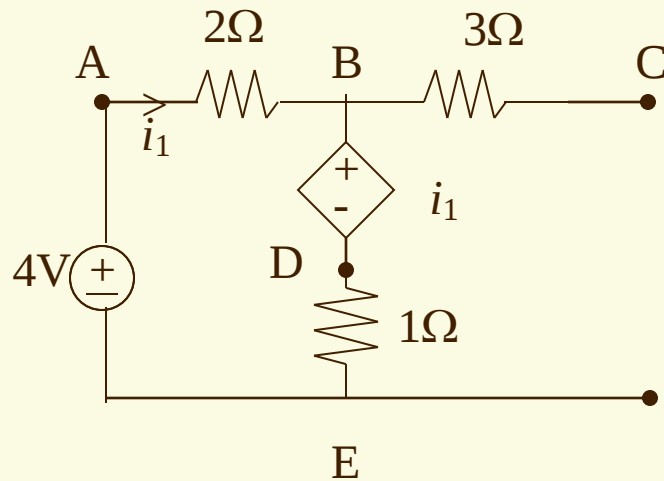
Exercise





Obtain Thevenin and Norton equivalent circuits





Source Transformation

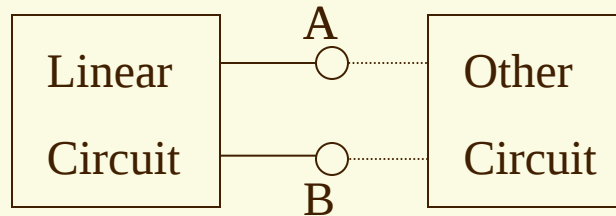

(a)

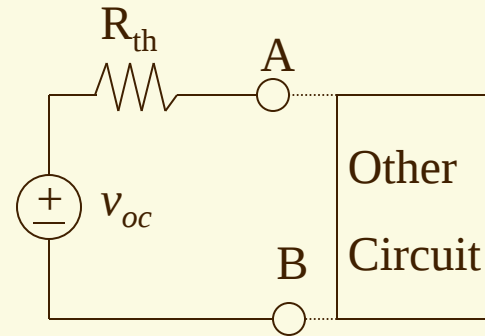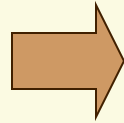


(b) Thevenin

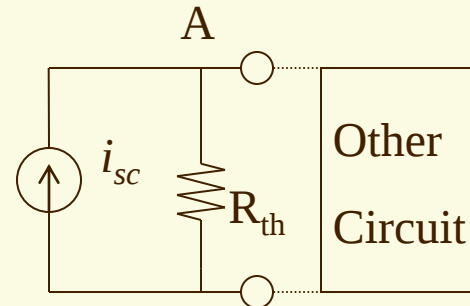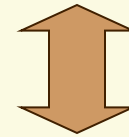

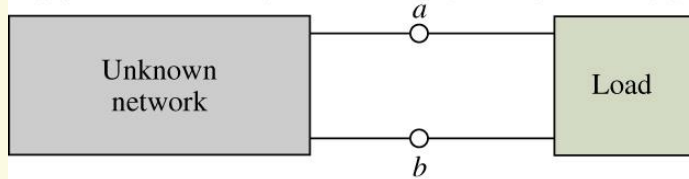
(c) Norton

Measurement of open-circuit voltage and short-circuit current


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



An unknown network connected to a load

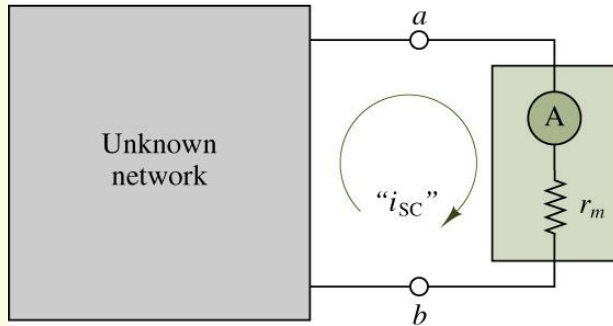

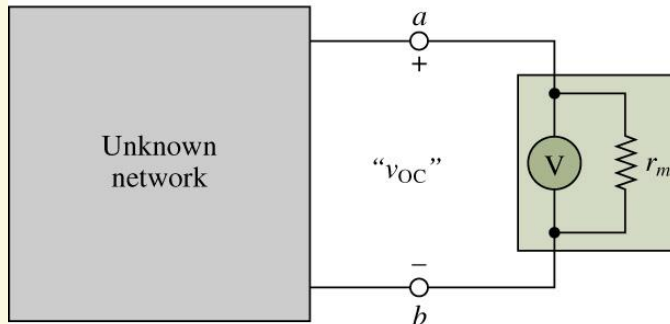Network connected for measurement of short-circuit current



Network connected for measurement of open-circuit voltage

Conclusion

- 📄 Network analysis: node analysis and mesh analysis
- 📄 Superposition principle: linear circuit
- 📄 Thevenin and Norton equivalent circuits