Chap. 11 Energy and Power in Digital Circuits

Average Power in an RC Circuit Power Dissipation in Logic Gates CMOS Logic

RC Circuit with a Switch





During T1





Energy Computation

Total energy provided by the source during T1

$$E = \int_{0}^{T_{1}} V_{S} i \, dt = \int_{0}^{T_{1}} V_{S} \frac{V_{S}}{R_{1}} e^{-\frac{t}{R_{1}C}} \, dt = C V_{S}^{2} (1 - e^{-\frac{T_{1}}{R_{1}C}})$$

$$\approx C V_{S}^{2} \quad if \quad T_{1} >> R_{1}C$$

Intersection Energy stored in the capacitor: $E_C = \frac{1}{2}CV_S^2$

Energy dissipated in the resistor: $E_1 = \frac{1}{2}CV_s^2$ Independent of R

During T2

$$\stackrel{+}{\underset{-}{\overset{-}{\overset{-}}}} \stackrel{C}{\underset{-}{\overset{-}{\overset{-}}}} R_2$$

Initially, $v_C = V_S$ (recall $T_1 >> R_I C$)

If we assume $T_2 >> R_2 C$

Capacitor energy is fully discharged = Energy dissipated by the resister: $E_2 = \frac{1}{2}$

$$E_2 = \frac{1}{2}CV_s^2$$

- independent of R

Putting Together

Energy dissipated in each cycle

$$E = E_1 + E_2 = CV_s^2$$

 assuming that Capacitor is fully charged and discharged during the period.



$$\overline{P} = \frac{E}{T} = CV_s^2 f$$

Power Dissipation of Inverter





During input is low



During input is high



Easy way to solve

Average power = static power + dynamic power

- Static power: independent of the frequency
- Dynamic power: charging-and-discharging of the capacitor

Average Power



Static power: Independent of the switching frequency.
 Dynamic power: related to switching capacitor

$$\frac{P_{static}}{P_{dynamic}} = \frac{R_L + R_{ON}}{R_L} \times \frac{T}{2R_L C_L}$$

Example II.1

Worst static power dissipation $R_L = 100k\Omega, \quad R_{ON} = 10k\Omega$ V_{S} R_L

Some numbers



Power Minimization

Dynamic power

- Reduce the supply voltage (5V -> 1.5V)
 - Change the voltage on need
- Reduce the capacitance
- Reduce the frequency
 - Turn off clock when not in use

Static power

- CMOS logic

CMOS Logic



PMOS



on when $v_{GS} \leq V_{TP}$ off when $v_{GS} > V_{TP}$ e.g. $V_{TP} = -1V$

CMOS Inverter



No static power! - No direct path from the supply to ground

Dynamic Power of CMOS



Static Power of CMOS

- Leakage power
 - Transient current



Some Examples

Example II.6: Processor SA27E

- # of gates = 3M, 25% activity

 $C_L = 30 fF, V_S = 1.5V, f = 425 MHz$

 $P_{dynamic} = (Fraction \ switching) \times (\# \ gates) \times fC_L V_S^2$

Exercise

Estimate the power of the following processor (~ P-IV)

- # of gates = 25M, 25% activity

$$C_L = 1 fF$$
, $V_S = 1.5V$, $f = 3GHz$

Summary

- Total power = static power + dynamic power
- CMOS does not exhibit static loss
- Dynamic power

 $P_{dynamic} = (Fraction \ switching) \times (\# \ gates) \times fC_L V_S^2$

- Reduce the supply voltage
- Reduce the switching activities
- Turn off the logic not in use (clock gating)

Chap. 12 Transients in Secondorder Circuits

LC Circuit RLC Circuits

LC Circuit



Solutions

- Find the particular solution
- Find the form of homogeneous solution
- Use initial condition to obtain the total solution
- < example >



Zero initial condition:

$$v_{C} = 0, i_{L} = 0$$

Homogeneous Solution

General Form: $v_H(t) = Ae^{st}$

$$LCAs^{2}e^{st} + Ae^{st} = 0 \implies s = \pm j\omega_{o}, \quad \omega_{o} = \frac{1}{\sqrt{LC}}$$

Total Solution

Total solution

$$v(t) = v_P(t) + v_H(t)$$
$$v(t) = V_0 + A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t}$$

$$v(t) = V_0 - \frac{V_0}{2} \left(e^{j\omega_0 t} + e^{-j\omega_0 t} \right)$$

$$= V_0 - V_0 \cos \omega_o t$$

Find A1 and A2 from initial conditions

Total Solution: Plot



$$v(t) = V_0 - V_0 \cos \omega_0 t$$

$$\omega_o = \frac{l}{\sqrt{LC}}$$

$$o_{o}t$$
 $i(t) = CV_0\omega_o \sin\omega_o t$

Undriven LC Circuit

$$L \begin{bmatrix} i_{C} + v_{C} \\ - v_{C} \end{bmatrix} = V$$

$$v_C(t) = A_1 e^{j\omega_o t} + A_2 e^{-j\omega_o t}$$





Observations from undriven LC Circuit

1. LC circuits are capable of oscillation

- \bigcirc 2. Important time constant: \sqrt{LC}
- 3. Characteristic impedance $\sqrt{\frac{L}{C}}$

$$W_T = \frac{C}{2} v_{C_{peak}}^2 = \frac{L}{2} i_{L_{peak}}^2 \implies \frac{v_{C_{peak}}}{i_{C_{peak}}} = \sqrt{\frac{L}{C}}$$

Example 12.1

 $C = 1\mu F$, $L = 100\mu H$, $(i_L = 0.5A, v_C = 10V \text{ at some } t)$

RLC Circuits

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Series RLC Circuit: second order circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

R L 000 $+v_L(t)$ $+v_R(t)$ + $v_C(t)$ i(t)C $v_S(t)$ -2

$$\frac{d^2 v_C(t)}{dt^2} + \frac{R}{L} \frac{dv_C(t)}{dt} + \frac{1}{LC} v_C(t) = \frac{1}{LC} v_S(t)$$

Homogeneous Solution

$$v_{C}(t) = K_{1}e^{s_{1}t} + K_{2}e^{s_{2}t} \Longrightarrow$$

$$s^{2} + 2\alpha s + \omega_{o}^{2} = 0, \quad \alpha \equiv \frac{R}{2L}, \quad \omega_{o} = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow s_{1,2} = -\alpha \pm \sqrt{\alpha^{2} - \omega_{o}}$$

Overdamped case: real and distinct roots $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} \quad (\alpha > w_o)$

Critically damped case: real and repeated roots

$$s_{1,2} = -\omega_o \quad (\alpha = \omega_o)$$

Underdamped case: complex conjugate roots

$$s_{1,2} = -\alpha \pm j\omega_{d,} \quad \omega_d = \sqrt{\omega_o^2 - \alpha^2} \quad (\alpha < \omega_o)$$

Natural Response: overdamped case

$$K_1 = K_2 = 1$$
, $\omega_0 = 1$, $\alpha = 1.5$



Natural Response: Critically damped case

$$K_1 = K_2 = 1, \quad \omega_o = 1, \quad \alpha = 1$$



Natural Response: Underdamped case

$$K_1 = K_2 = 1$$
, $\omega_0 = 1$, $\alpha = 0.2$



Response to step input voltage

 $\omega_{o} = 1, \quad \alpha = 0.2 \sim 4 \equiv Zeta$



Exercise: Parallel RLC Circuit



Find i_L(†) assume zero initial state $R = 5k\Omega, C = 1\mu F, L = 1H, V_s = 25V$

Exercise

Find the range of L to make $v_c(t)$ to be overdamped



Exercise



Find the differential equation for capacitor voltage. Find the total response with the following initial condition. $i_{L}(0) = 4 \text{ mA}, v_{C}(0) = 0 \text{ (V)}$



Example 12.4 Ideal Switched Power Supply



(1) S1 on, S2 off

(2) S1 off, S2 on until inductor current becomes zero

(3) S1 off, S2 off



Summary

- LC Circuit
 RLC Circuit
 - Three kinds of transient responses
 - Over-damped
 - Critically damped
 - Under-damped

Chap. 13 Sinusoidal Steady State: Imdepance and Frequency Response

Sinusoidal Steady-state Response Impedance Frequency Response Filter

Sinusoidal Response of RC Circuit





$$v_I(t) = V_i \frac{e^{j\omega t} + e^{-j\omega t}}{2}$$

Find the particular solution to $V_i e^{j\omega t}$

Total solution

$$v_C = v_P + v_H$$

$$v_{C} = \frac{V_{i}}{\sqrt{1 + \omega^{2}R^{2}C^{2}}} \cos(\omega t + \phi) + Ae^{-\frac{t}{RC}}$$

where $\phi = tan^{-1}(-\omega RC)$

Given
$$v_C(0) = 0$$
 for $t = 0$
so,

$$A = -\frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\phi)$$

Sinusoidal Steady State (SSS)

Particular solution for sinusoidal input after transients have died



All information of SSS is contained in the complex amplitude $\frac{V_i}{1 + j\omega RC}$

Magnitude Plot



Phase Plot

$$\phi = tan^{-1} - \omega RC$$



Impedance Model

 $\begin{array}{ccc} + & & & \\ & &$ $\begin{array}{ccc} & & & i_{C} = I_{C}e^{j\omega t} & & i_{C} = C\frac{dv_{C}}{dt} \\ & & & \downarrow \\ & & \downarrow \\ & & \downarrow \\ & & \downarrow \\ & & &$

Impedance Model

Circuit corresponding to a complex exponential input



 $\frac{V_C}{V_I}$

Series RLC Circuit



Exercise 1



Exercise 2



Find *v(t)* at steady state (time unit: *msec*)



What we are doing? The Big Picture





$$\left|\frac{V_r}{V_i}\right| = \frac{\omega RC}{\sqrt{\left(1 - \omega^2 LC\right)^2 + \left(\omega RC\right)^2}}$$

Observe

Low
$$\omega$$
: $\approx \omega RC$
High ω : $\approx \frac{R}{\omega L}$
 $\omega \sqrt{LC} = 1$: ≈ 1

Frequency Response



Frequency Response of Basic Elements



RC and RL Circuits





RLC Circuits



Intuitively:



Resonance

Equivalent impedance = Resistor

$$Z_L + Z_C = 0$$

Circuit response is maximum



Another Example



AM Radio Receiver





Selectivity



Quality Factor: Q

 $\Delta \omega$:

Note that abs magnitude is $\frac{1}{\sqrt{2}}$

when
$$\frac{V_r}{V_i} = \frac{1}{1 + j\left(\omega \frac{L}{R} - \frac{1}{\omega CR}\right)} = \frac{1}{1 \pm j1}$$

i.e. when $\frac{\omega L}{R} - \frac{1}{\omega CR} = \pm 1$

$$\Delta \omega = \omega_1 - \omega_2 = \frac{R}{L}$$

Quality Factor

$$Q = \frac{\omega_o}{\frac{R}{L}} = \frac{\omega_o L}{R}$$

$$\omega_o = \frac{l}{\sqrt{LC}}$$

Lower R, higher QAnother interpretation

$$Q = 2\pi \frac{\text{energy stored}}{\text{energy lost per cycle}}$$
$$= 2\pi \frac{\frac{1}{2}L|I_r|^2}{\frac{1}{2}|I_r|^2 R \frac{2\pi}{\omega_0}}$$
$$Q = \frac{\omega_o L}{R}$$

Exercise



Find the resonance frequency and the equivalent impedance at resonance.



Summary

- Sinusoidal Steady-state Response
- Impedance
- Frequency Response
- Filter