




# **Chap. 15 The Operational Amplifier Abstraction**

Device Properties of OP AMP



OP AMP Circuits

OP AMP RC Circuits

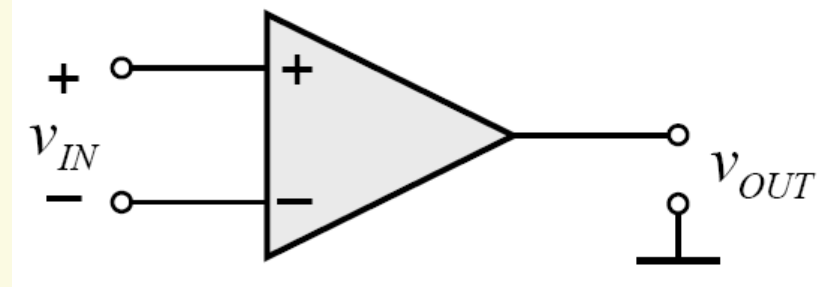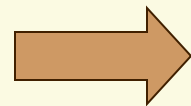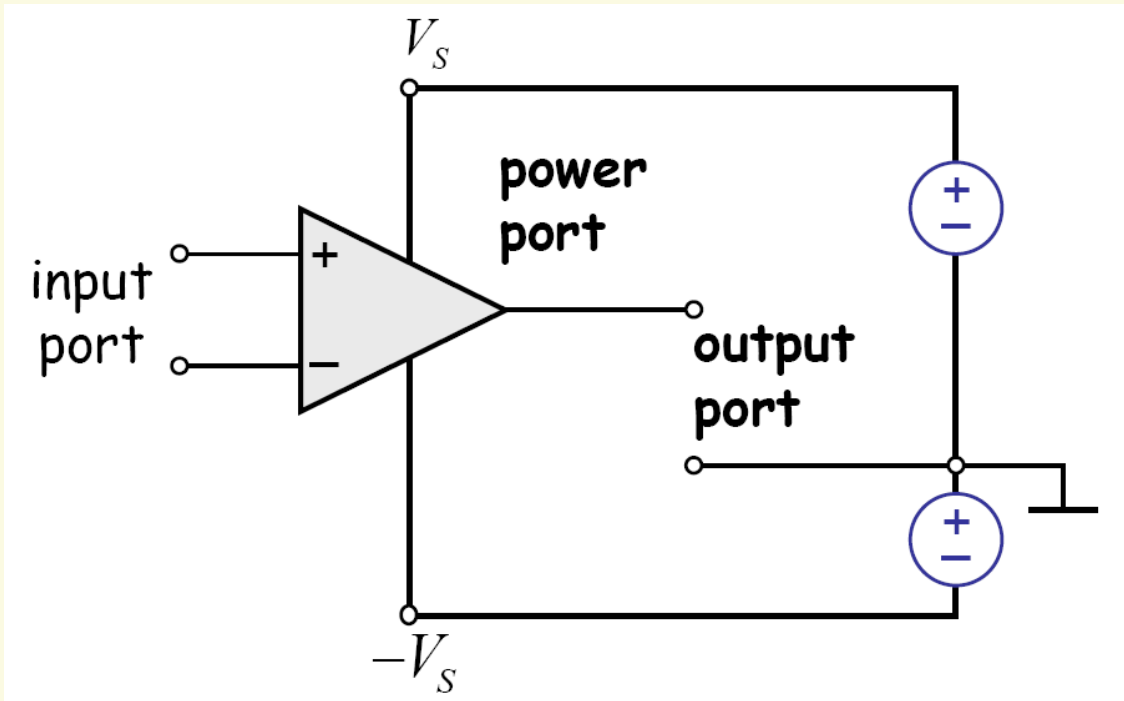
# Operational Amplifier (OP AMP) Abstraction





# Ideal Circuit Model of OP AMP

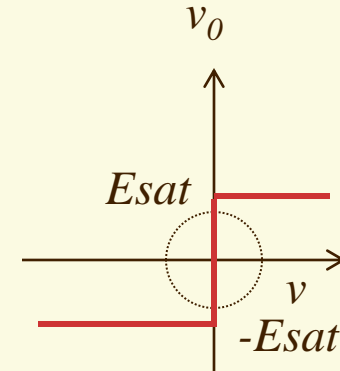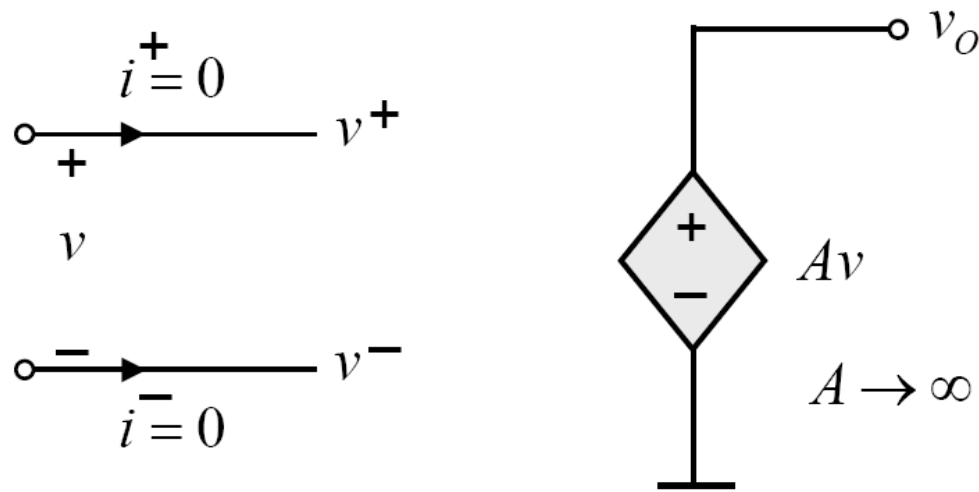


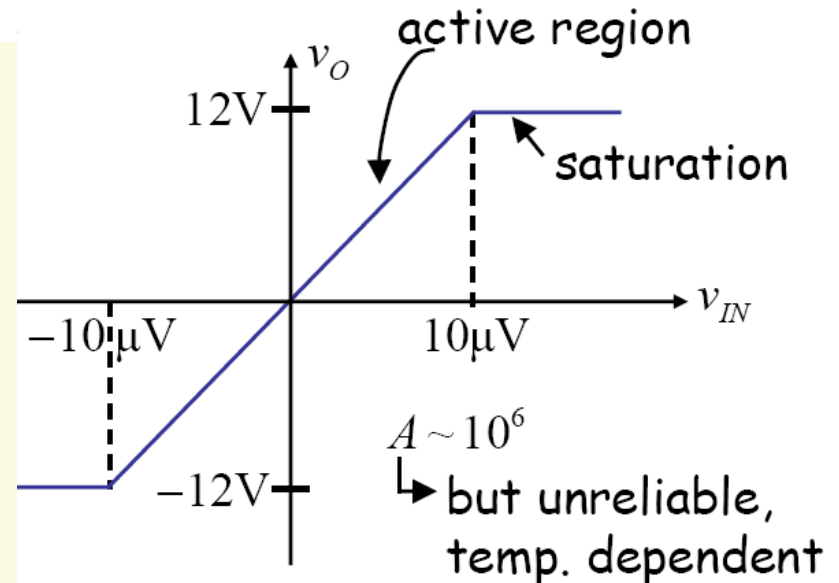
- Input resistance is infinite
- Output resistance is 0
- Infinite gain




# Comparator (OP AMP in Saturation)

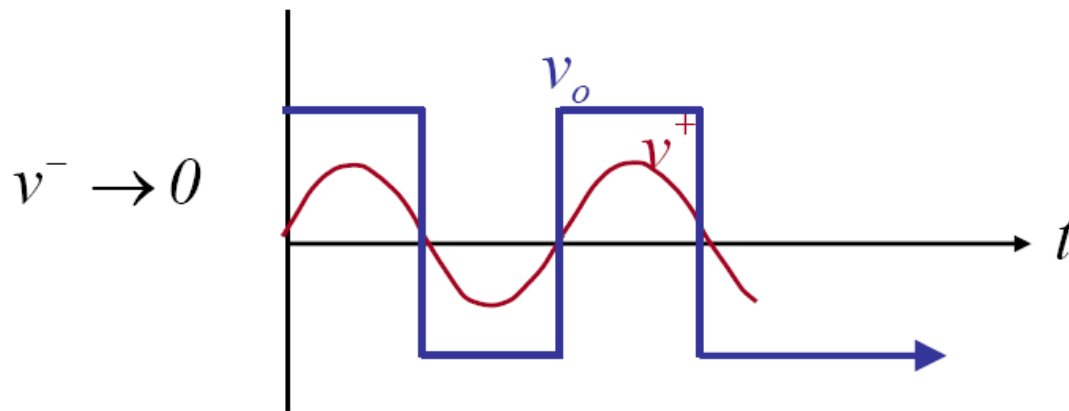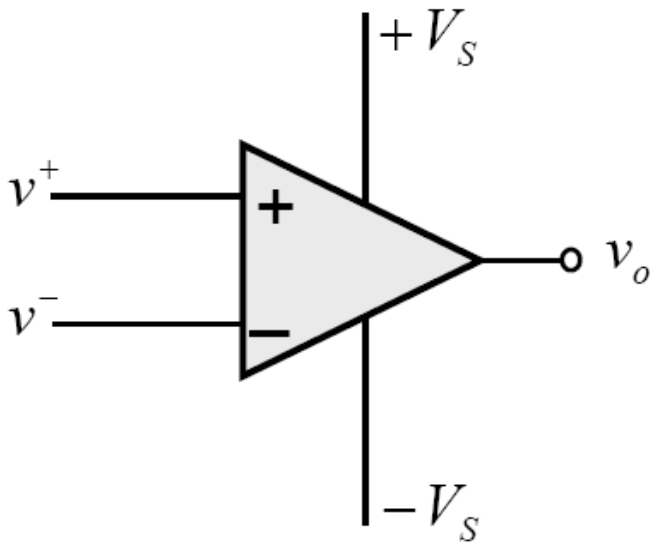

# Non-inverting Amplifier

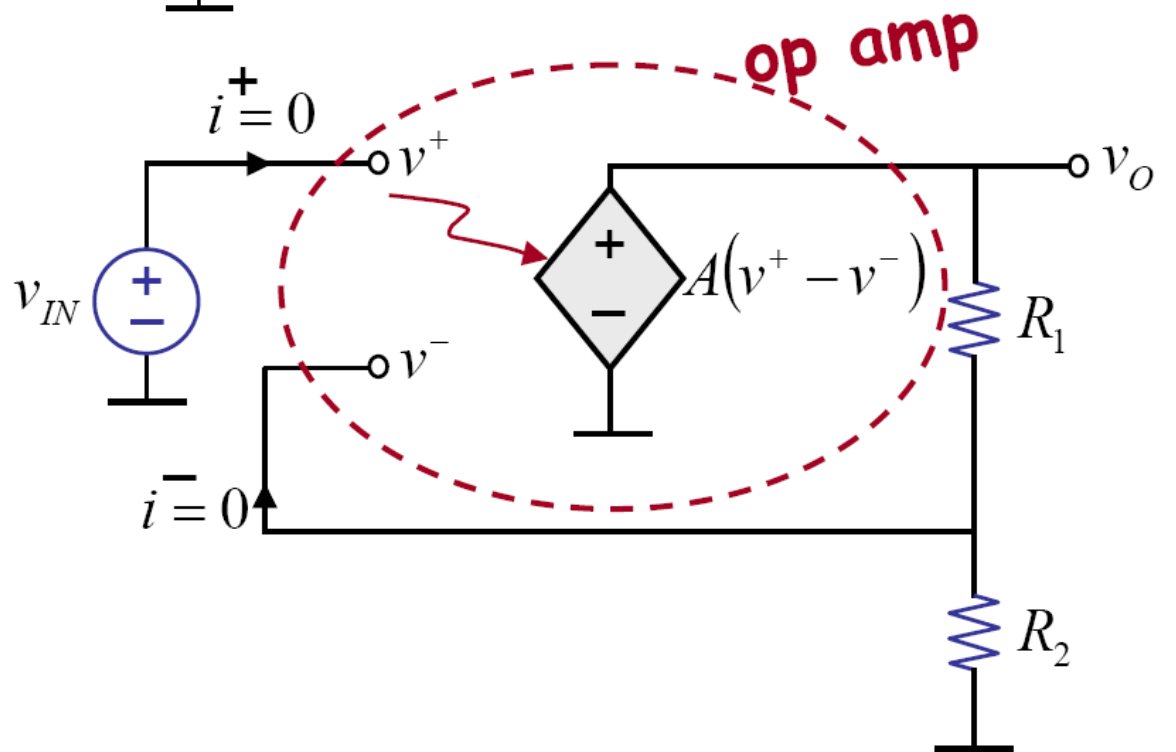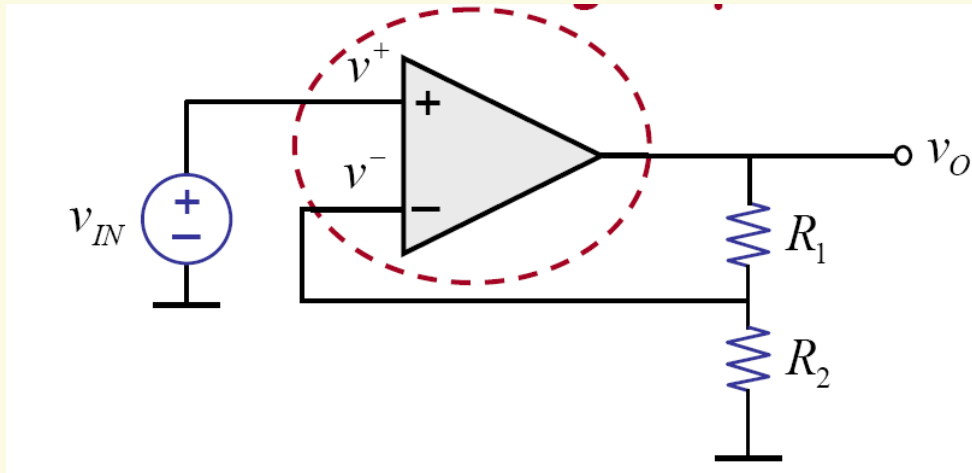


# Non-inverting Amplifier (2)

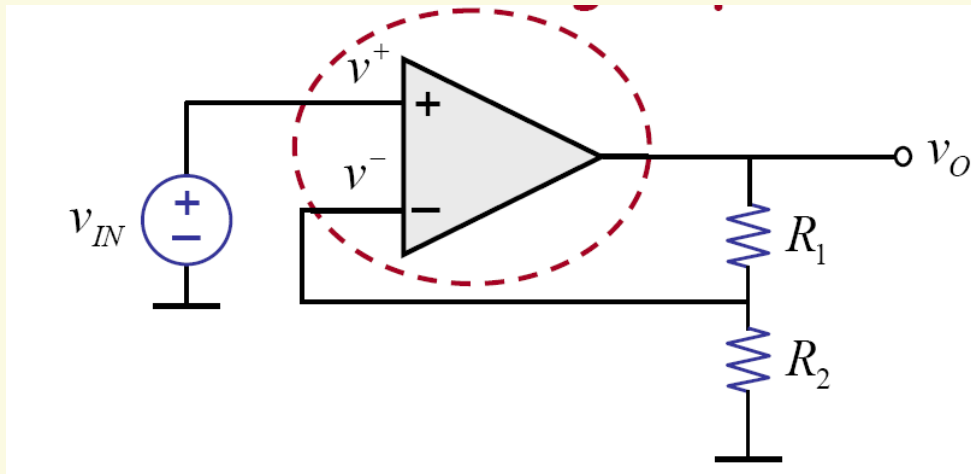

Show

$$v_O = \frac{Av_{IN}}{1 + \frac{AR_2}{R_1 + R_2}} \approx v_{IN} \underbrace{\frac{(R_1 + R_2)}{R_2}}_{\text{gain}}$$


# Negative Feedback

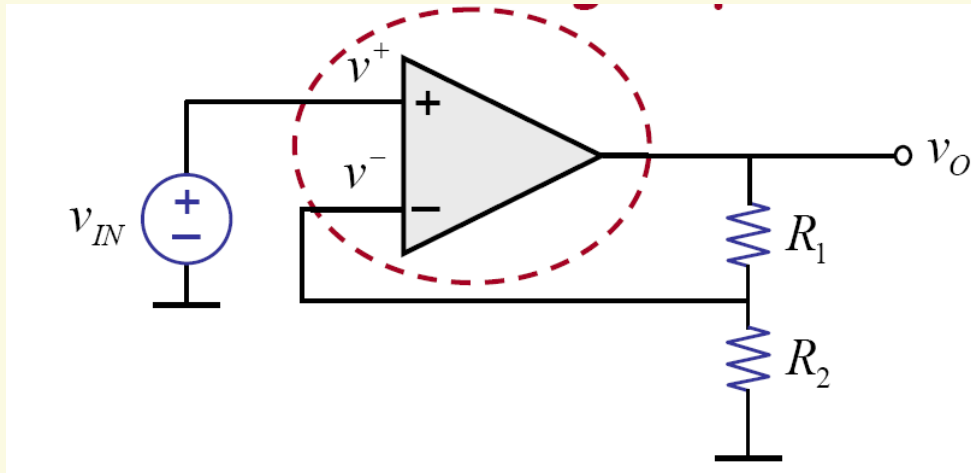

- Portion of output is fed back into the negative input
  - Stable state is reached without saturation
- Output is independent of OP AMP gain and temperature.

$$v^+ - v^- = \frac{v_O}{A} = \frac{\left(\frac{R_1 + R_2}{R_1}\right)v_{IN}}{A} \rightarrow 0 \quad \Rightarrow \quad v^+ \approx v^-$$


# Easy Solution

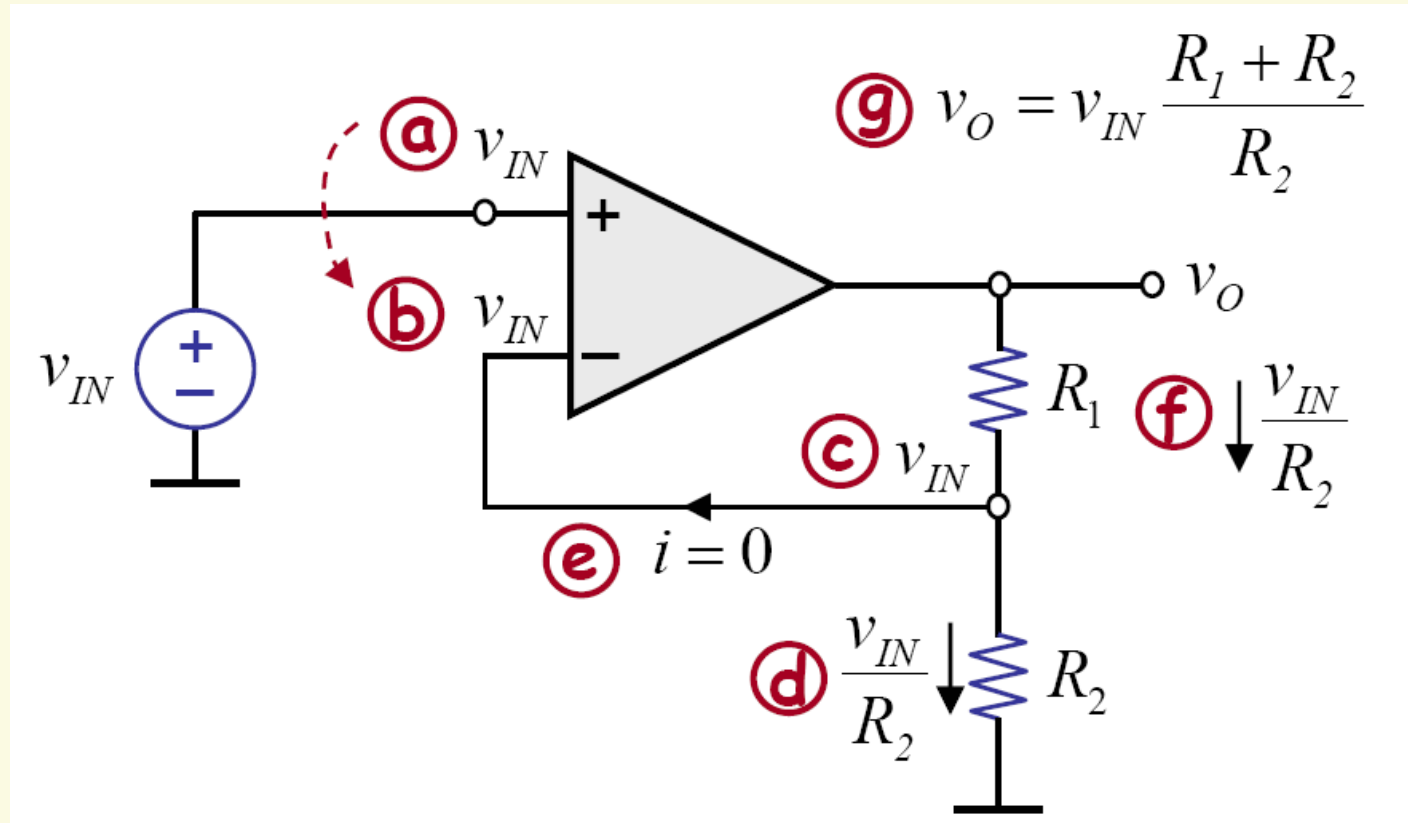

Node equation at the input ports !




# Voltage Follower

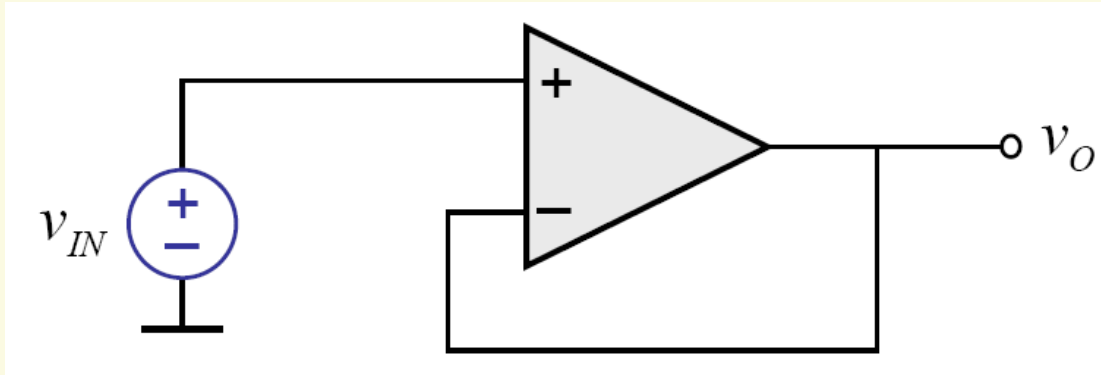


- 📄 Voltage gain = 1, current gain = infinite
- 📄 **Buffer**: isolate the input and the output circuits
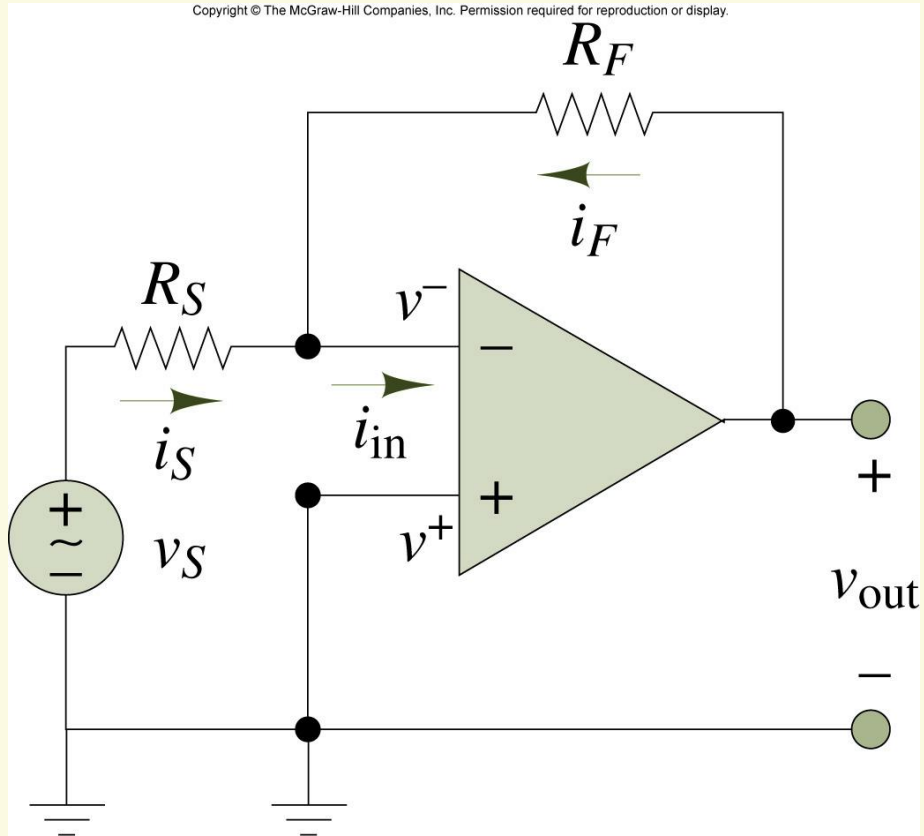
# Inverting OP AMP


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




# Adder

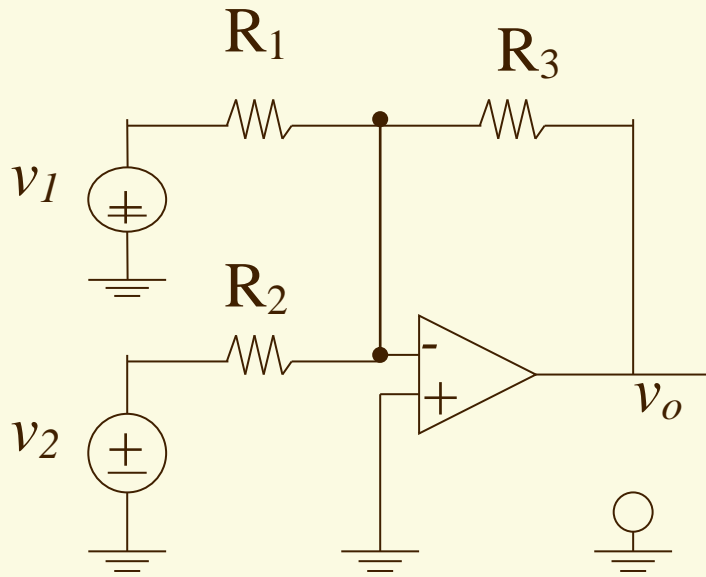


# Subtractor

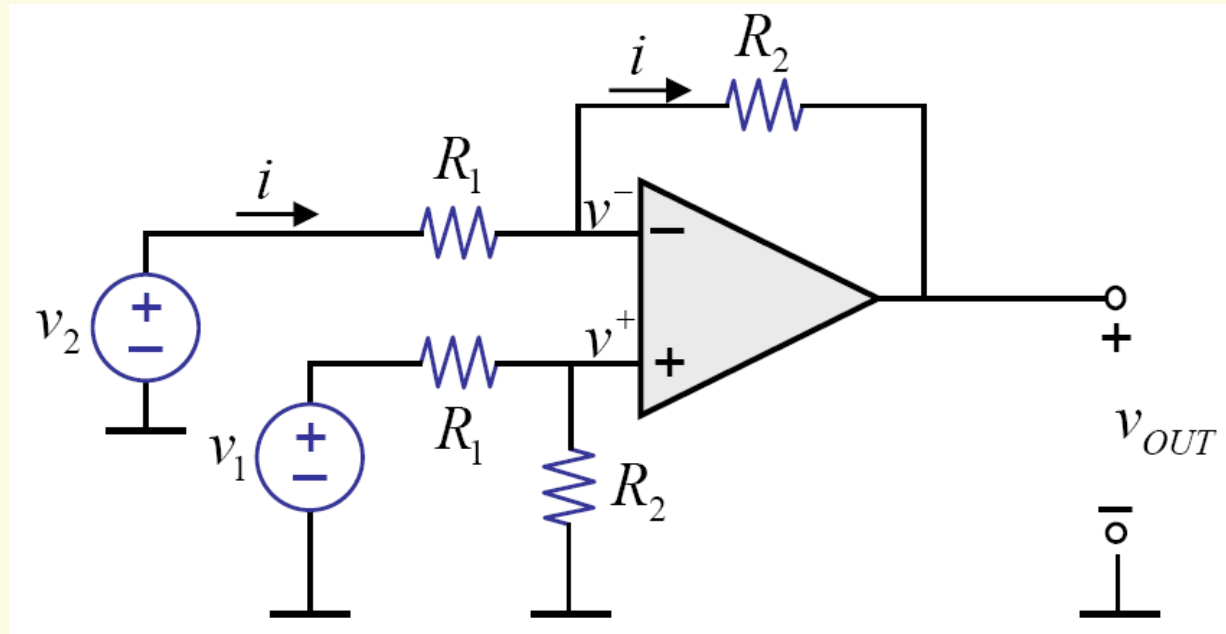


# Exercise

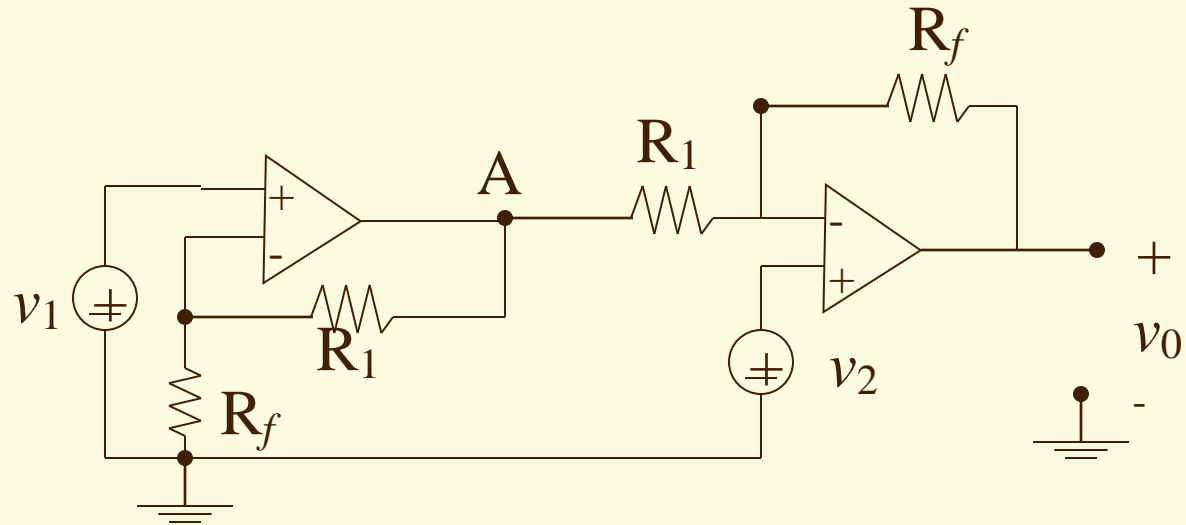


# Current Source from OP AMP

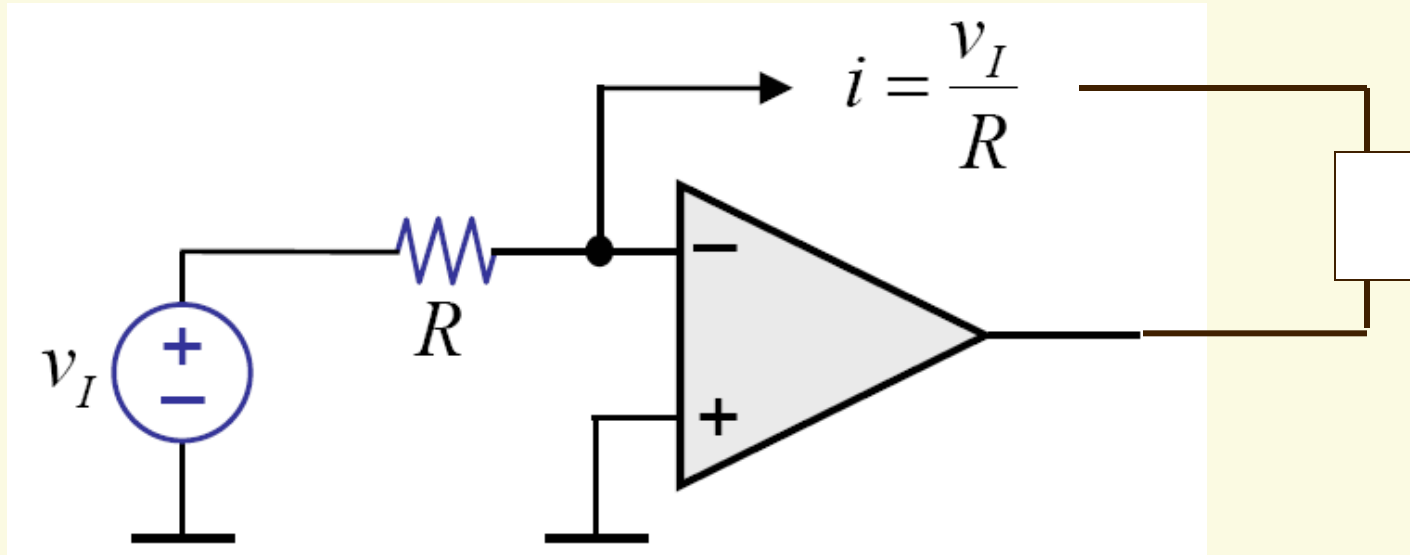

# OP AMP Integrator

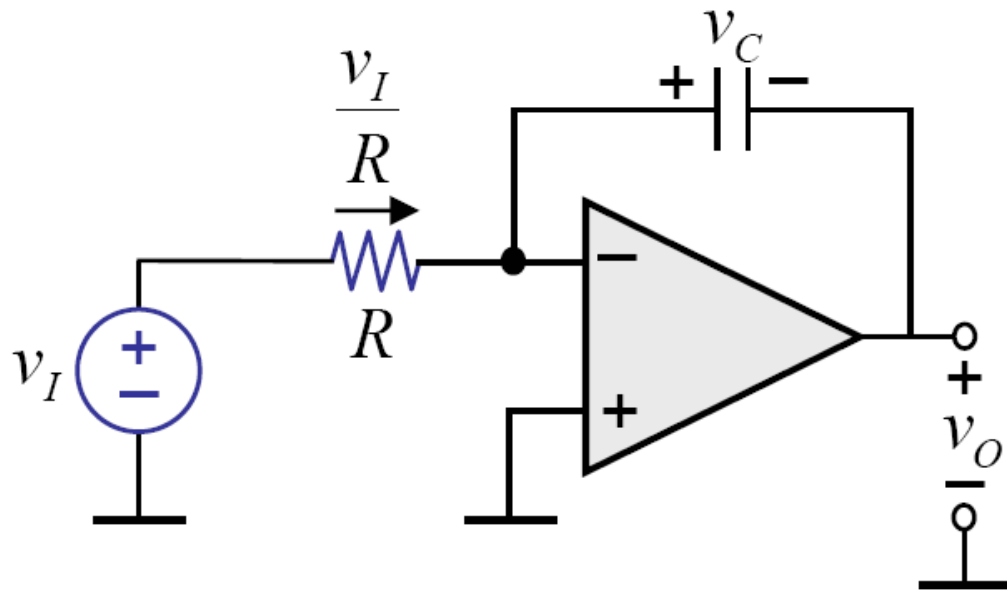


# OP AMP Differentiator

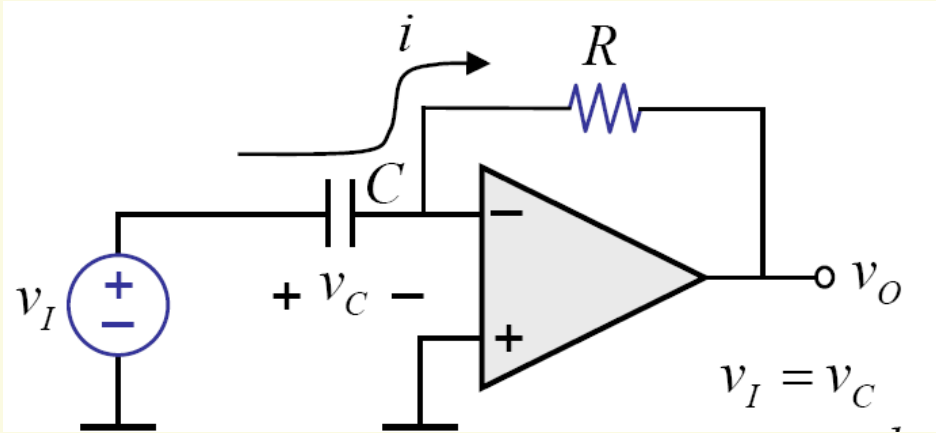



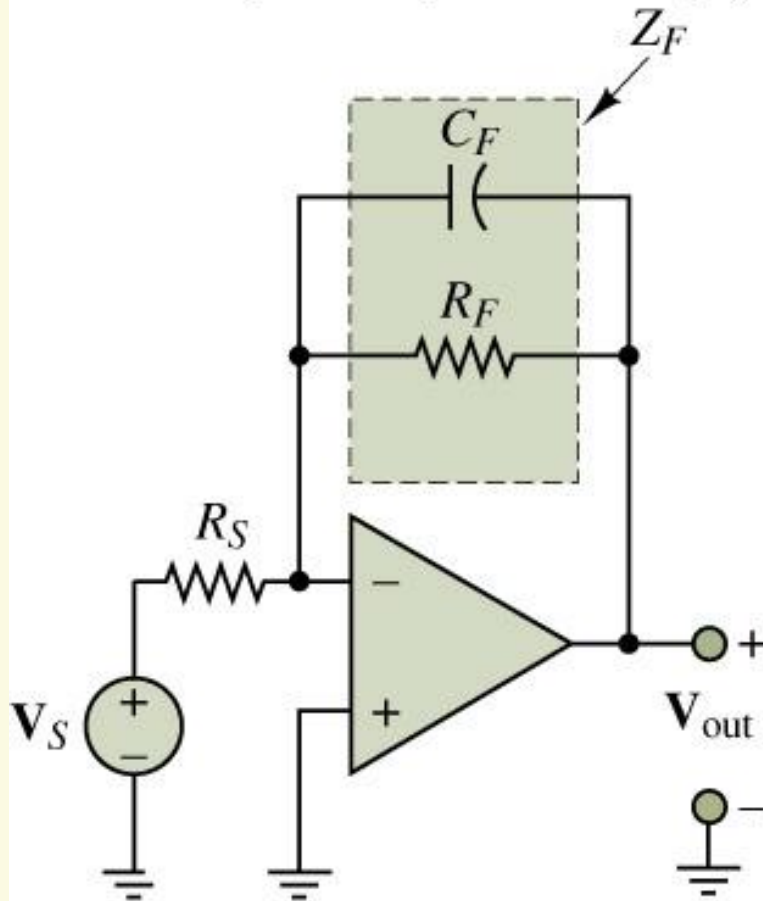
# OP AMP Active Filter

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.




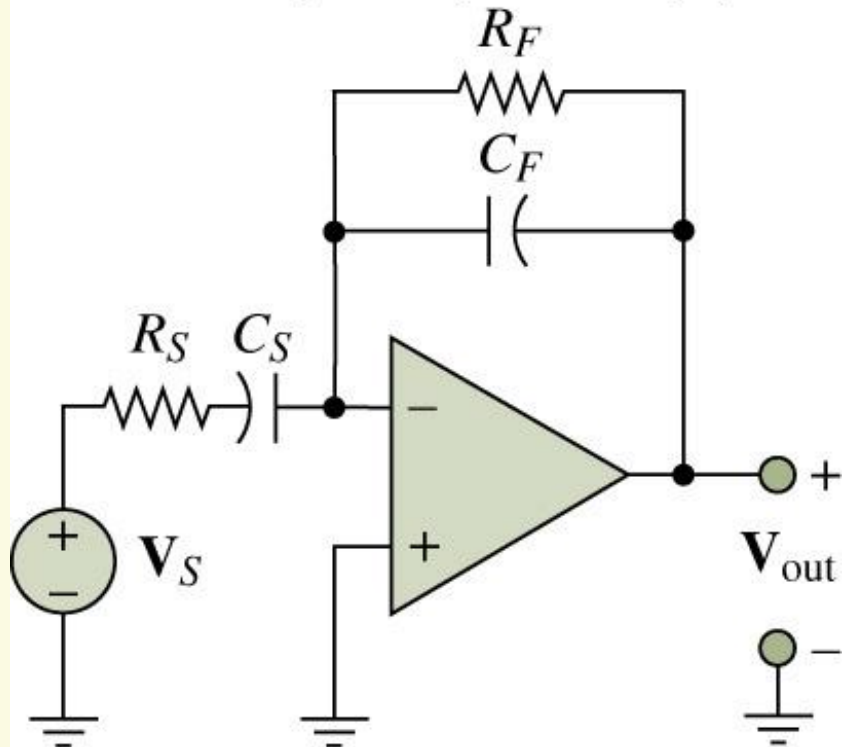
# Exercise



Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.





# Positive Feedback

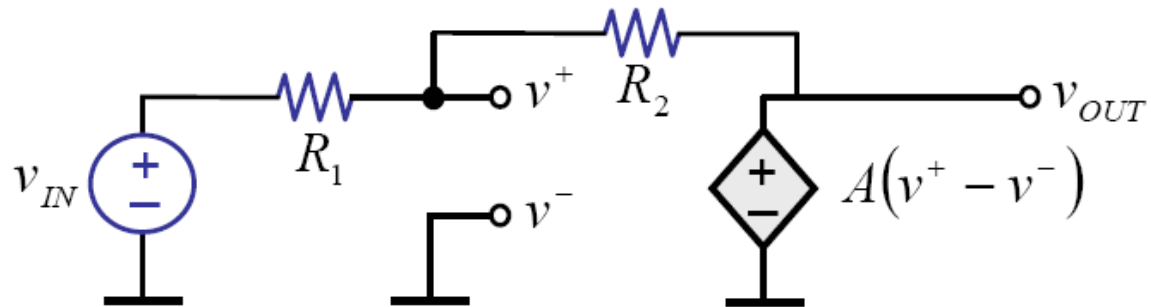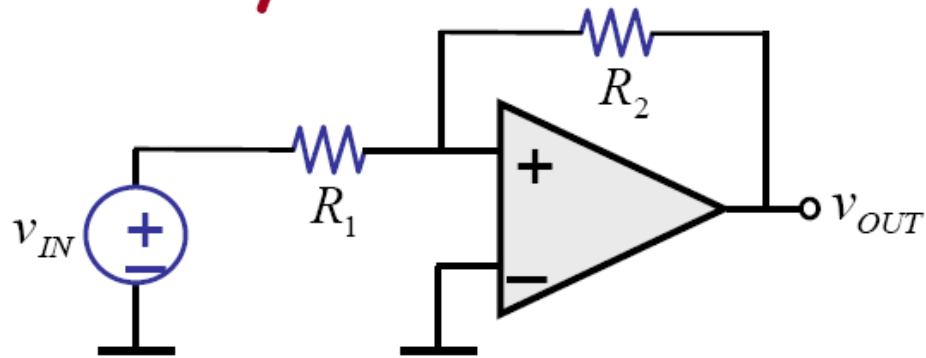

# Voltage Characteristic

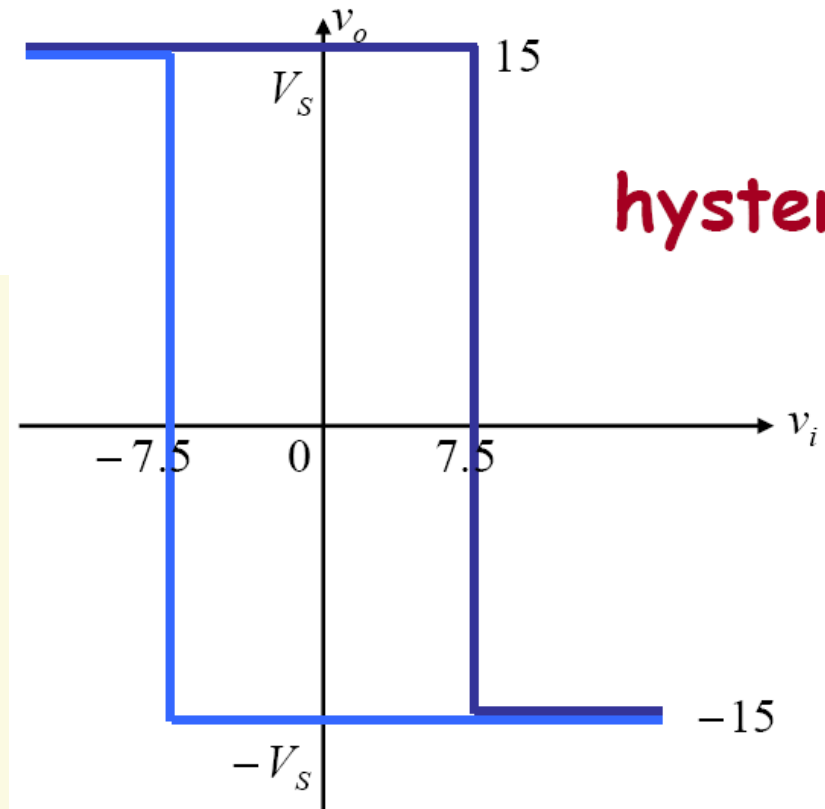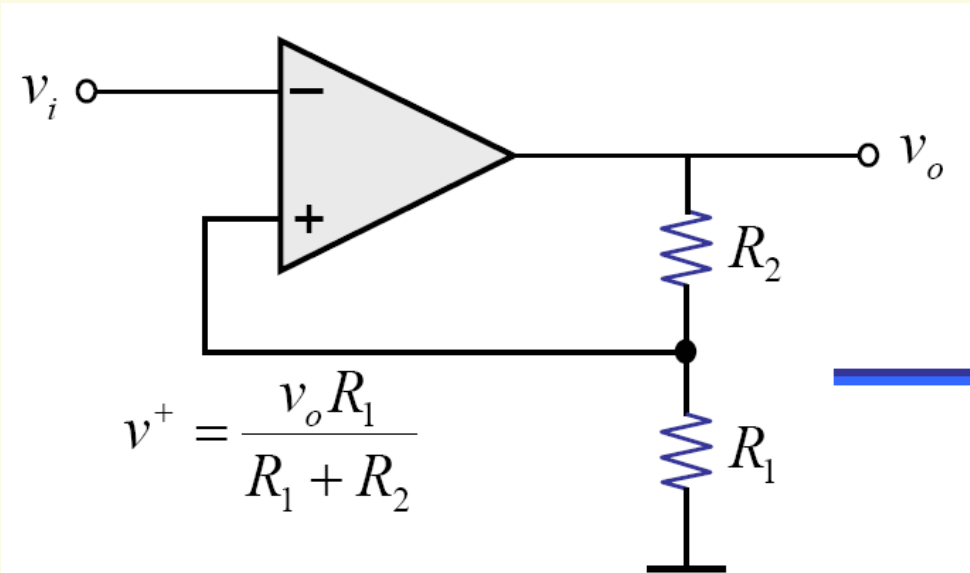

# Oscillator

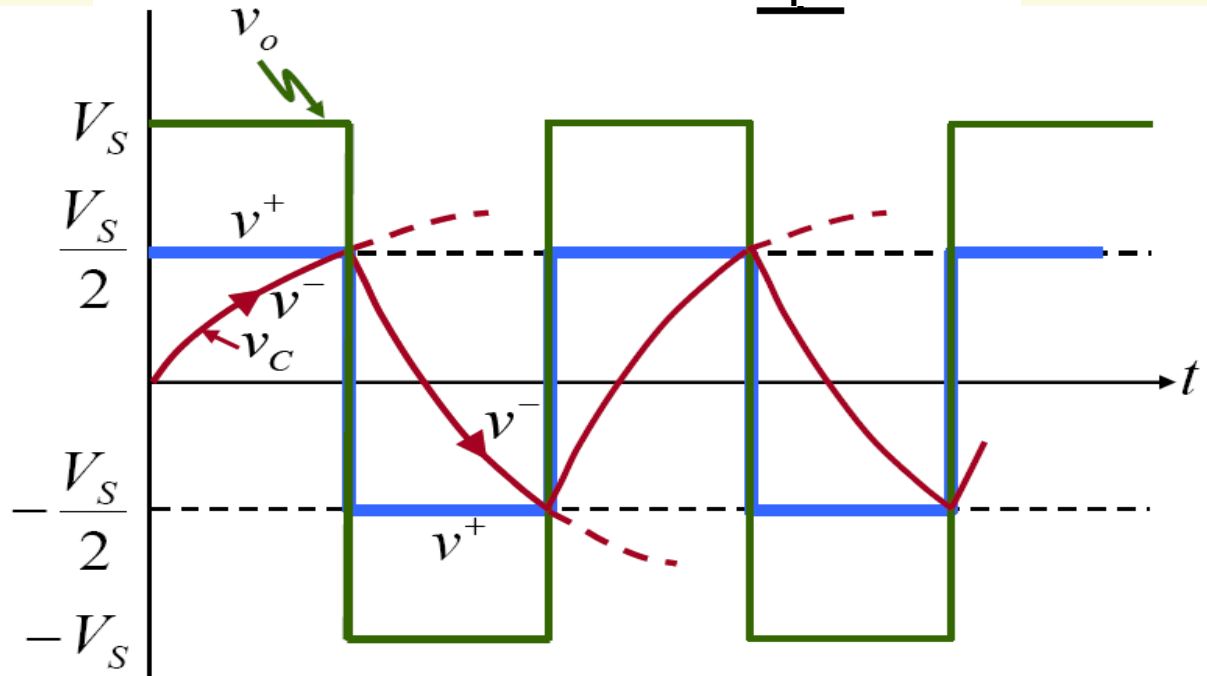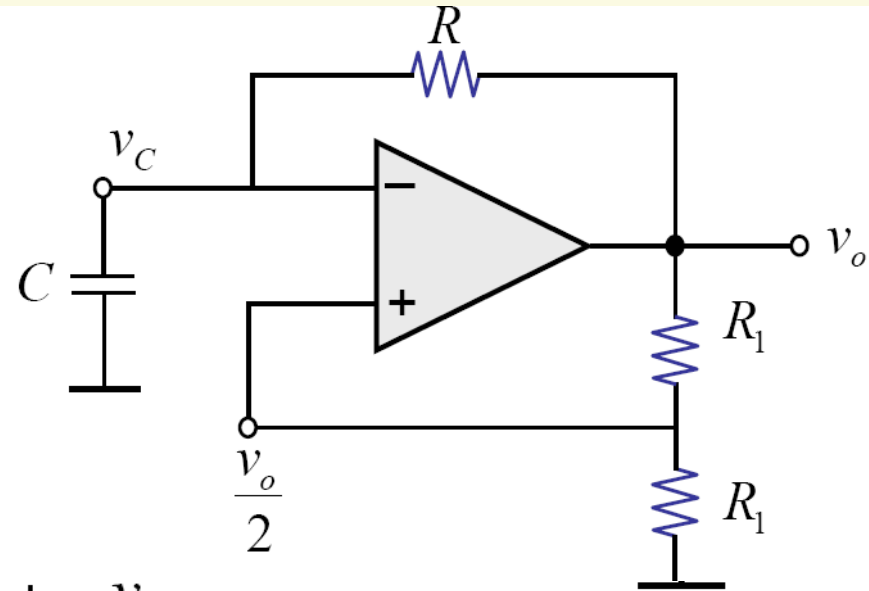



# Summary

- 📄 Ideal OP AMP
- 📄 Comparator: OP AMP in saturation
- 📄 Negative Feedback Circuits
- 📄 Active Filters
- 📄 Positive Feedback - oscillator

# Chap. 16 Diodes


Diode Characteristics

Peak Detector

Clamping Circuit






# Reminder: Diode Characteristics

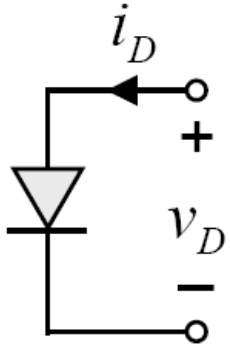

$$i_D = I_S \left( e^{\frac{v_D}{V_T}} - 1 \right)$$



$$I_S = 10^{-12} \text{ A}$$

$$V_T = 0.025 \text{ V}$$

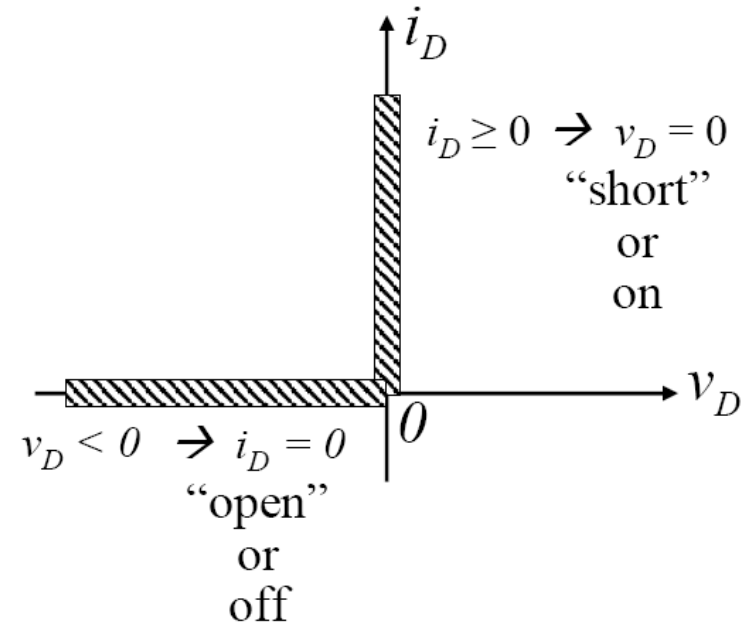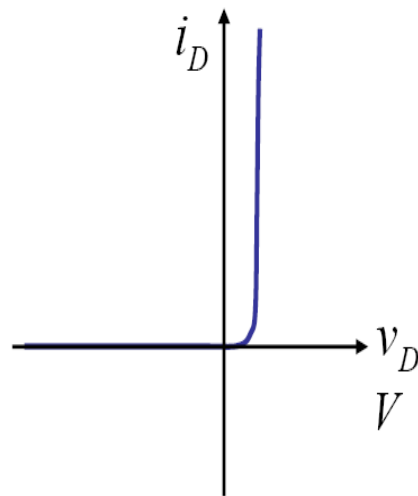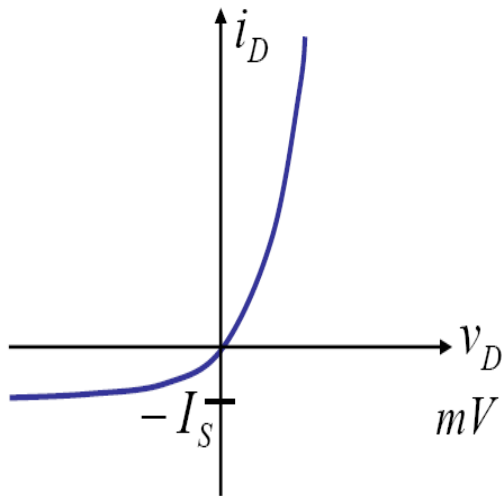

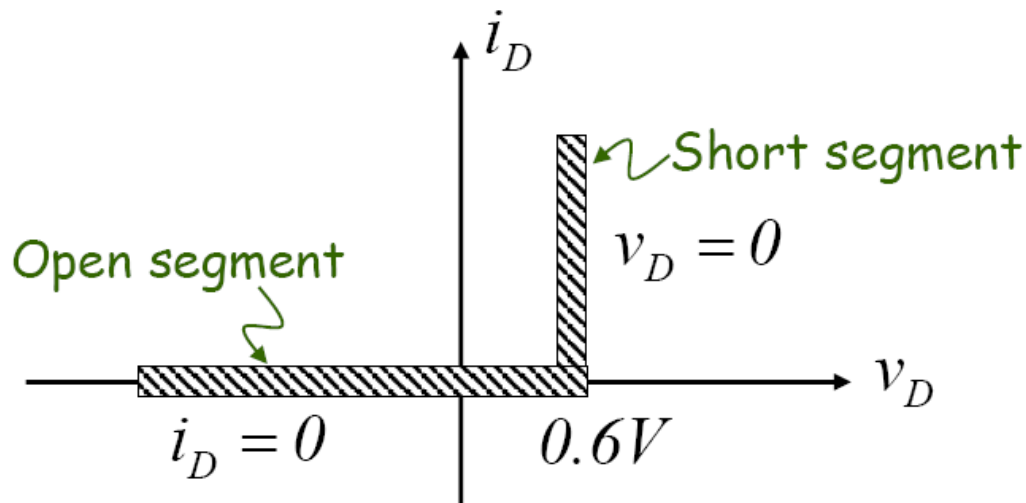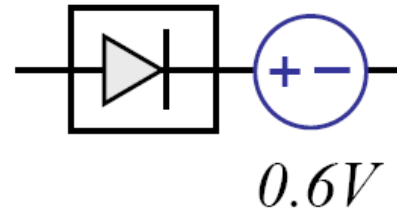
# Ideal Diode and Practical Diode

"Practical" diode model  
ideal with offset



# Half Wave Rectifier

Consider

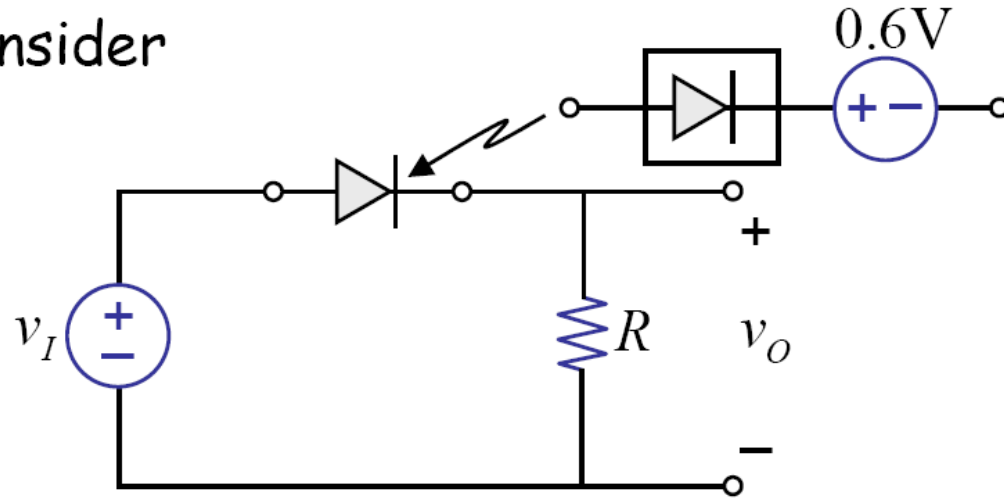


$v_I$  is a sine wave

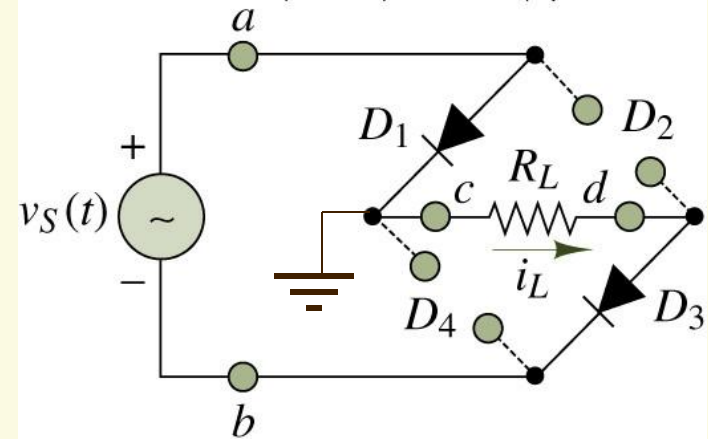
# Bridge Rectifier

- Do not need center-tapped transformer
- Smaller PIV

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.



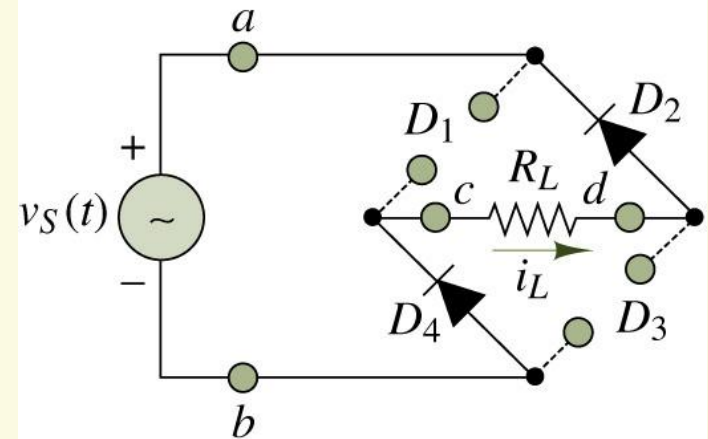
During the positive half-cycle of  $v_S(t)$ ,  $D_1$  and  $D_3$  are forward-biased and  $i_L = v_S(t)/R_L$  (ideal diodes).



During the negative half-cycle of  $v_S(t)$ ,  $D_2$  and  $D_4$  are forward-biased and  $i_L = -v_S(t)/R_L$  (ideal diodes).
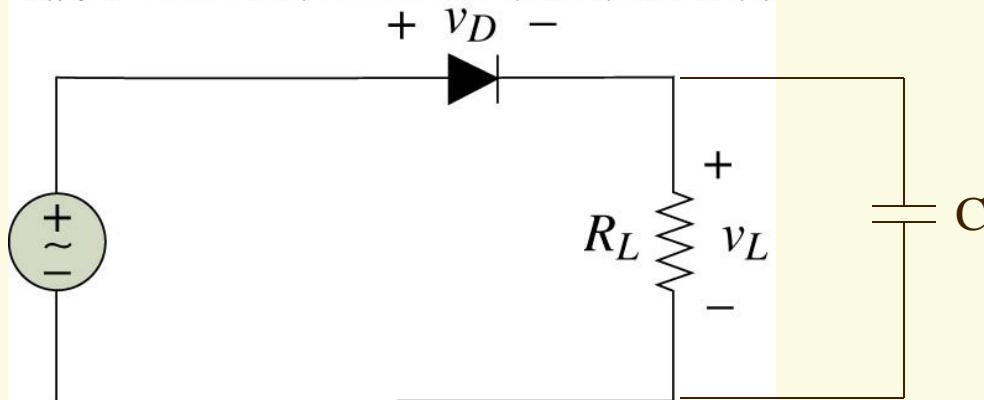
# Peak rectifier

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Ripple voltage 
$$V_r = V_p \left( 1 - e^{-\frac{T-\Delta t}{RC}} \right) \approx V_p \frac{T}{RC}$$

What is the ripple voltage for a Bridge rectifier?


# Exercise: Clipper or Limiter

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


Limiter circuit

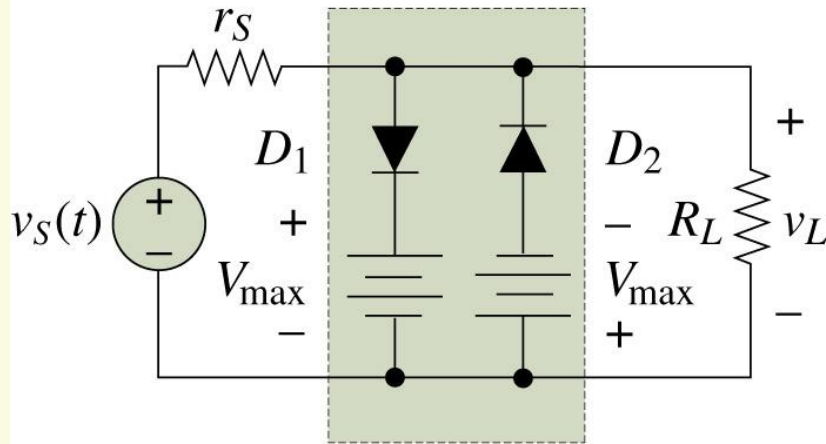


# Diode Clamping Circuit

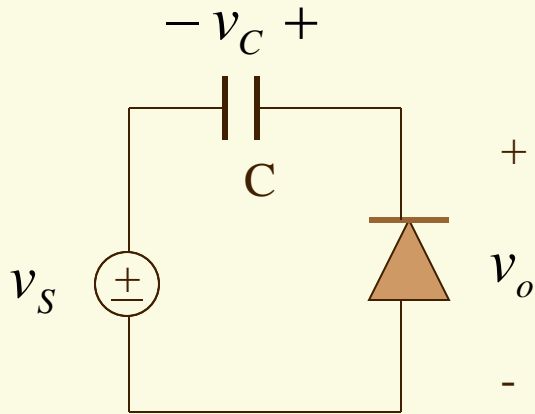




$$v_o = v_C + v_S$$

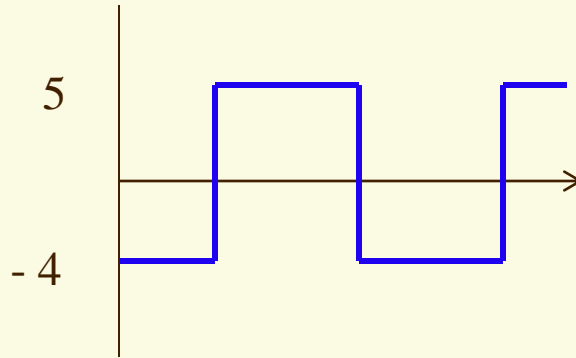

Sinusoidal input

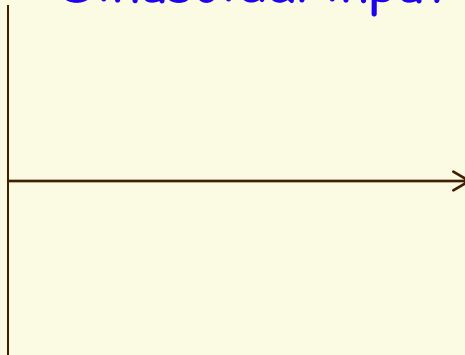


# More Diode Clamping Circuits

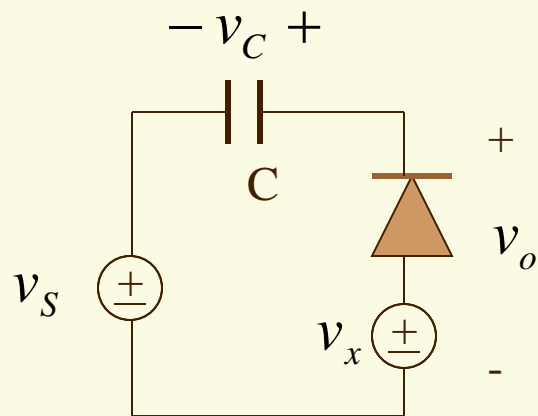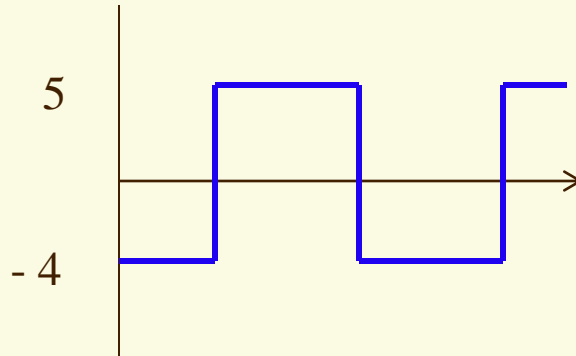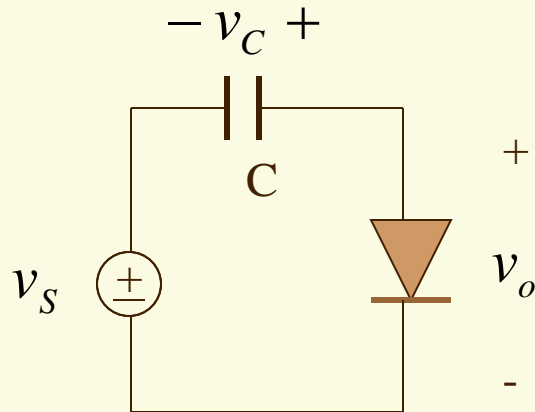




# Diode Clamp with Resistor

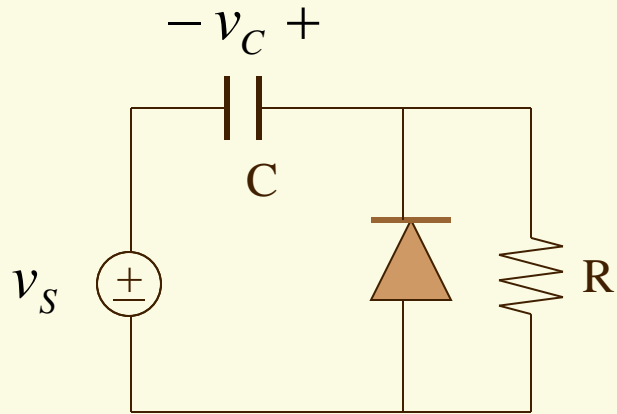

+  
 $v_o$   
-

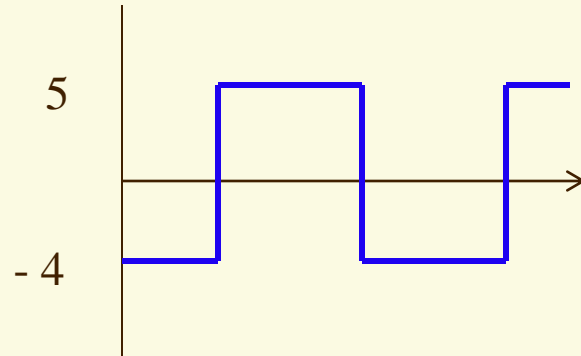

# Summary: Diode Circuits

 Rectifier

 Peak Detector

 Limiter

 Clamping Circuits

A spiral-bound notebook with a textured, light brown cover. The spiral binding is on the left side. The text "THE END..." is printed in the center of the cover.

**THE END...**