

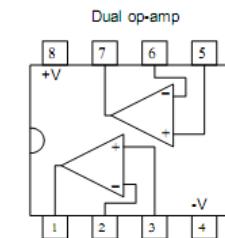
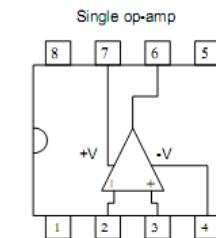


# Electrical Systems II

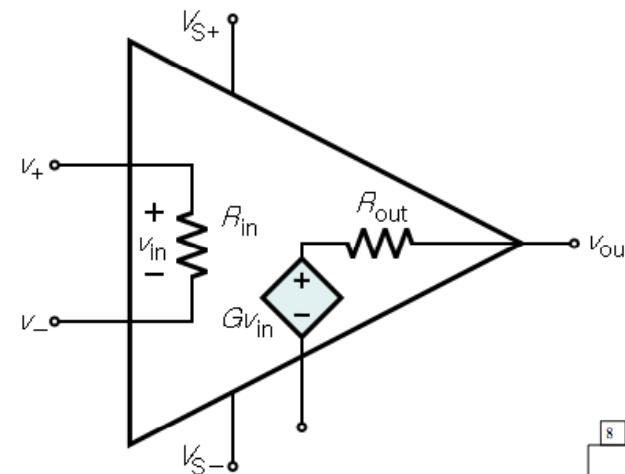

# Operational Amplifiers

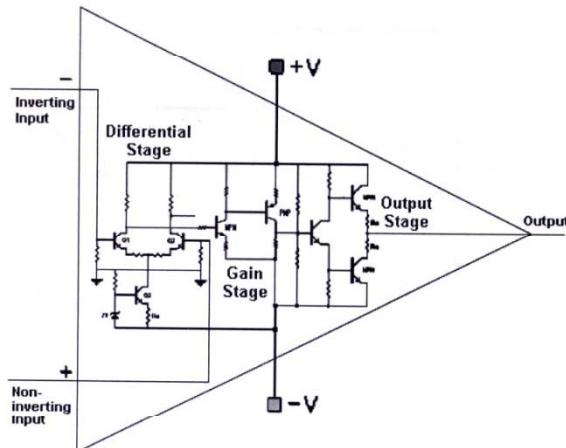


## Golden Rules of OP Amp

1. The voltage difference between  $V_-$  and  $V_+$  is Zero.
2. The inputs draw no current.



# Operational Amplifiers

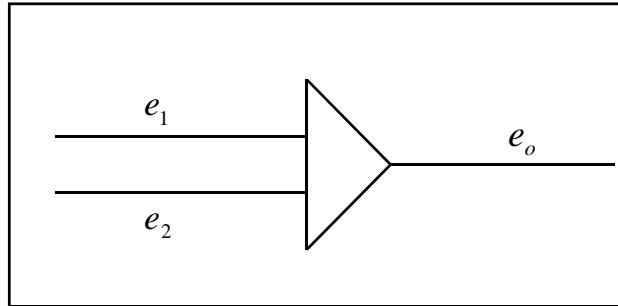


$$e_0 = K (e_2 - e_1)$$


- i)  $K = 10^5 \sim 10^6$  for dc signals and ac of less than 10 Hz frequency.
- ii)  $K = 1$  for ac 1 MHz ~ 50MHz
- iii) Ideal CP amps
  - $K = \infty$
  - no current flow into the input terminals
  - the output voltage is not affected by the load connected to the output terminal



# Inverting Amplifier

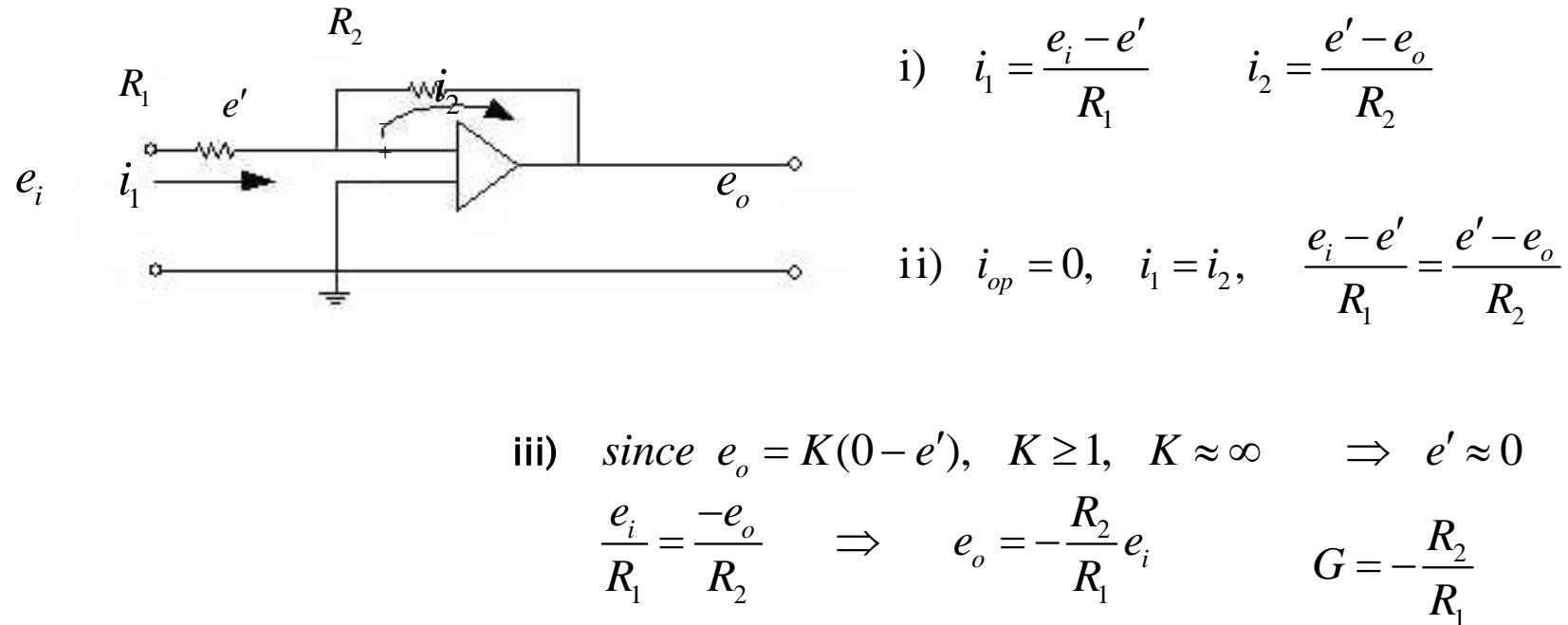

# Non-inverting Amplifier

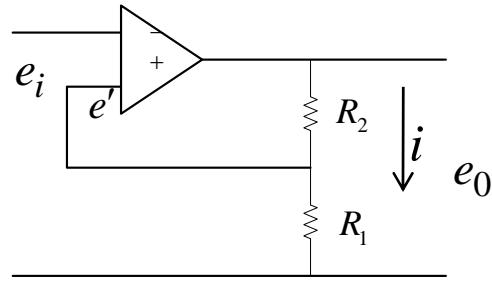

$$e' = e_i \quad (\because K \approx \infty)$$

$$i = \frac{e_o - e_i}{R_2} = \frac{e_i}{R_1}$$


$$G = \left(1 + \frac{R_2}{R_1}\right)$$

$$\Rightarrow e_o = \left(1 + \frac{R_2}{R_1}\right) e_i$$



# Example of Operational Amplifier Circuit

ex)

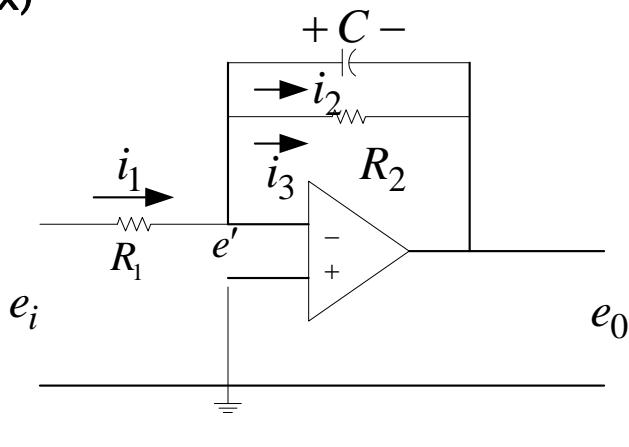

$$e' = 0, \quad i_1 = i_2 + i_3$$

$$i_1 = \frac{e_i}{R_1}, \quad \frac{dv_c}{dt} = \frac{1}{C} i_2 = \left( -\frac{de_o}{dt} \right)$$

$$(v_c = e' - e_o = -e_o)$$

$$i_3 = \frac{e' - e_o}{R_2} = -\frac{e_o}{R_2}$$

$$\Rightarrow \frac{e_i}{R_1} = C \frac{dv_c}{dt} - \frac{1}{R_2} e_o = C \frac{de_o}{dt} - \frac{1}{R_2} e_o$$

$$\Rightarrow \frac{de_o}{dt} = -\frac{1}{CR_2} e_o - \frac{1}{CR_1} e_i$$



# Examples of Operational Amplifiers


**Laplace Transform :**  $E_o(s) \left( s + \frac{1}{CR_2} \right) = -\frac{1}{CR_1} E_i(s)$

$$T.F = \frac{E_o(s)}{E_i(s)} = -\frac{1}{s + \frac{1}{CR_2}} \cdot \frac{1}{CR_1} = -\frac{R_2}{R_1} \cdot \frac{1}{R_2 C s + 1}$$


**Step input response :**  $E_i(s) = \frac{1}{s}$ ,  $e_i(t) = \begin{cases} 1 & t \geq 0 \\ 0 & t < 0 \end{cases}$

$$\begin{aligned} E_o(s) &= -\frac{R_2}{R_1} \frac{1}{R_2 C s + 1} \cdot E_i(s) \\ &= -\frac{R_2}{R_1} \frac{1}{R_2 C s + 1} \cdot \frac{1}{s} = -\frac{R_2}{R_1} \left( \frac{1}{s} - \frac{1}{s + (1/R_2 C)} \right) \end{aligned}$$
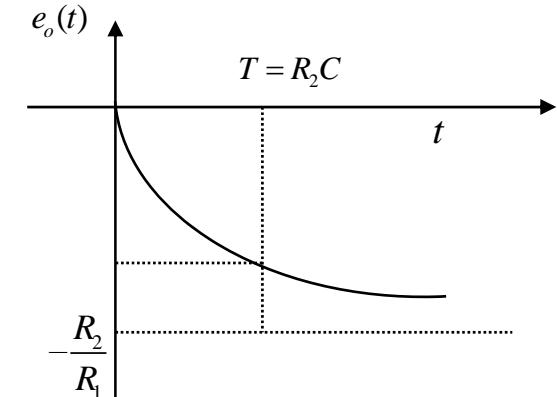
$$e_o(t) = -\frac{R_2}{R_1} \left( 1 - e^{(-1/R_2 C)t} \right)$$



# Examples of Complex Impedance

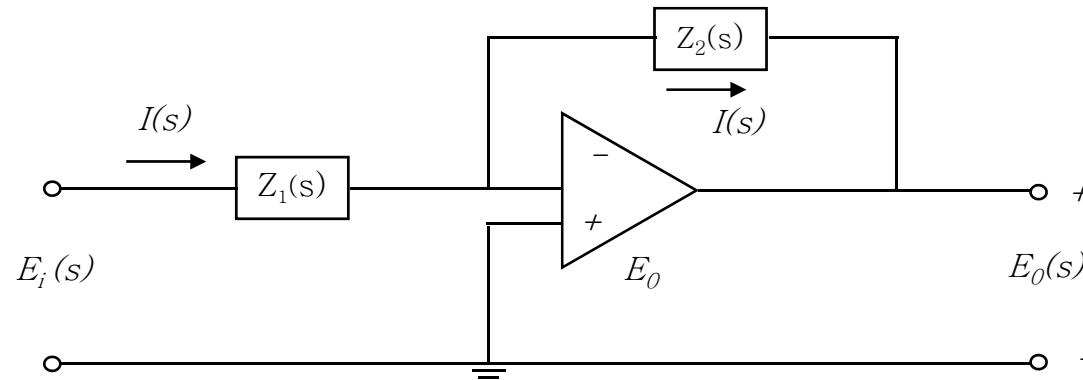


$$E_i(s) = Z_1(s)I(s), \quad E_o(s) = Z_2(s)I(s)$$

$$\frac{E_o(s)}{E_i(s)} = -\frac{Z_2(s)}{Z_1(s)}$$



# Examples of Complex Impedance

ex)

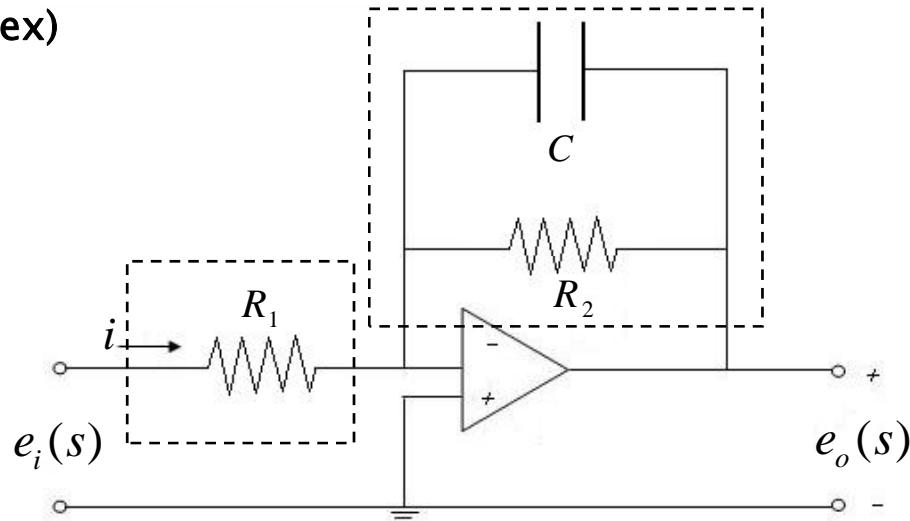

$$Z_1(s) = R_1$$

$$Z_2(s) = \frac{1}{Cs + \frac{1}{R_2}} = \frac{R_2}{R_2 C s + 1}$$


$$I(s) = Cs \cdot E(s) + \frac{1}{R_2} E(s)$$

$$\frac{E_o(s)}{E_i(s)} = -\frac{Z_2(s)}{Z_1(s)} = -\frac{R_2}{R_1} \frac{1}{R_2 C s + 1}$$




# Other Examples

Differentiator/High Pass Filter

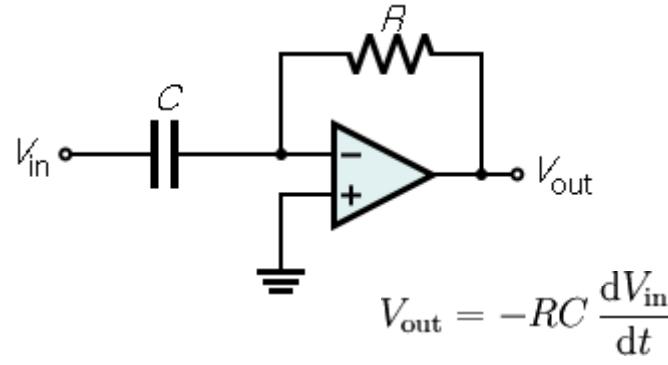


Integrator/Low Pass Filter

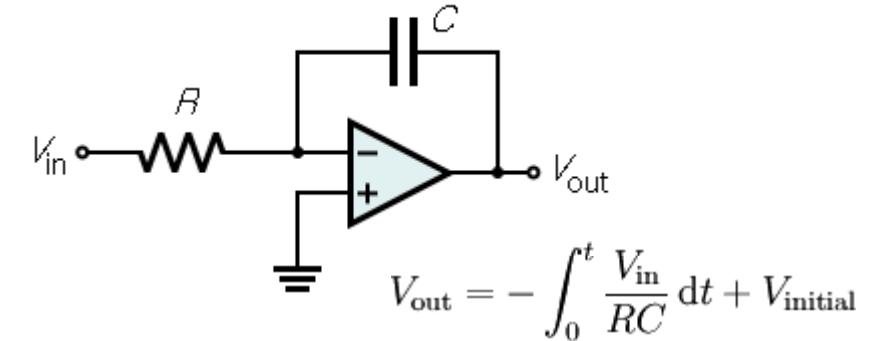


# Other Examples

Summing Amplifier

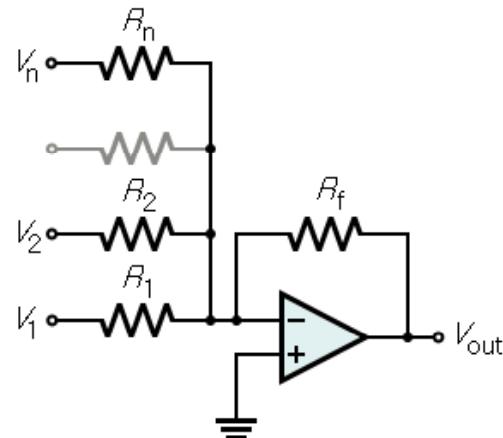

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \cdots + \frac{V_n}{R_n} \right)$$

Instrumentation Amplifier

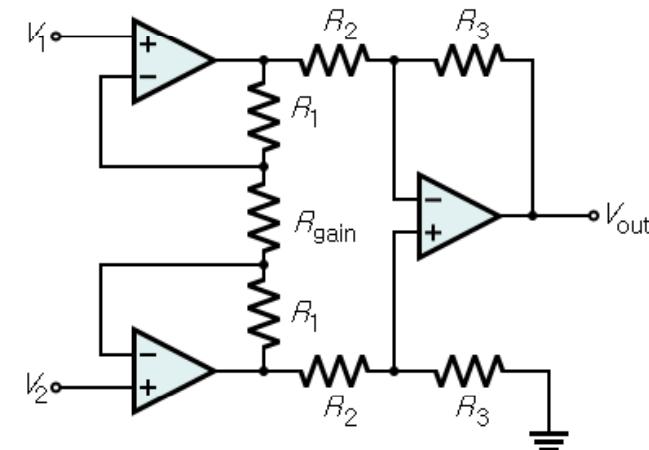

$$\frac{V_{out}}{V_2 - V_1} = \left( 1 + \frac{2R_1}{R_{gain}} \right) \frac{R_3}{R_2}$$

