
Chapter 1

Introduction

Why study logic design?

- it is the implementation basis for all modern computing devices
 - building large things from small components
 - provide a model of how a computer works
- More important reasons
 - the inherent parallelism in hardware is often our first exposure to parallel computation
 - it offers an interesting counterpoint to software design and is therefore useful in furthering our understanding of computation, in general

What will we learn in this class? (1 / 2)

- The basics of logic design
 - Boolean algebra, logic minimization, state, timing, CAD tools
- The concept of state in digital systems
 - analogous to variables and program counters in software systems


What will we learn in this class? (2/2)

- How to specify/simulate/compile/realize our designs
 - hardware description languages (HDLs)
 - tools to simulate the workings of our designs
 - logic compilers to synthesize the hardware blocks of our designs
 - mapping onto programmable hardware
- Contrast with software design
 - sequential and parallel implementations
 - specify algorithm as well as computing/storage resources it will use

Applications of logic design

- Conventional computer design
 - CPUs, busses, peripherals
- Networking and communications
 - phones, modems, routers
- Embedded products
 - in cars, toys, appliances, entertainment devices
- Scientific equipment
 - testing, sensing, reporting
- The world of computing is much bigger than just PCs!

Global processor/controller market

 

Source: WSTS

PC CPUs constitute less than 2% of the market

What is logic design? (1 / 2)

- Digital hardware consists of components
- Components or building blocks
 - Switches built from semiconductor transistors
 - Most basic element
 - Higher level circuits such as logic gates and memories
- A logic designer should choose the right component to solve logic design problems
- Constraints: size, cost, performance, power consumption
 - Cost vs. size


* A circuit is an interconnected collection of switches

What is logic design? (2/2)

- Each component has
 - a set of input wires
 - a set of output wires
 - Each wire is set to some analog voltage value
 - But will be interpreted as either 1 or 0 ([digital abstraction](#))
- Transistors react to the voltage levels on the input wires
 - Switch their state and cause a change in output wires
 - At macro scale, a component that contains transistors reacts to input voltage values
- Depending on the way a circuit reacts to the input voltages
 - Combinational logic circuits
 - Sequential logic circuits

What is digital hardware?

- Collection of devices that sense and/or control wires, which carry a digital value (i.e., a physical quantity that can be interpreted as a “0” or “1”)
 - example: digital logic where voltage $< 0.8\text{v}$ is a “0” and $> 2.0\text{v}$ is a “1”
- Primitive digital hardware devices
 - logic computation devices (sense and drive)
 - are two wires both “1” - make another be “1” (AND)
 - is at least one of two wires “1” - make another be “1” (OR)
 - is a wire “1” - then make another be “0” (NOT)
 - memory devices (store)
 - store a value
 - recall a previously stored value

 


Computation: abstract vs. implementation


- Computation has been a mental exercise (paper, programs)
- This class is about physically implementing computation using physical devices that use voltages to represent logical values
- Basic units of computation are:
 - representation: "0", "1" on a wire
set of wires (e.g., binary integer)
 - assignment: $x = y$
 - data operations: $x + y - 5$
 - control:
 - sequential statements: $A; B; C$
 - conditionals: $\text{if } x == 1 \text{ then } y$
 - loops: $\text{for } (i = 1 ; i == 10, i++)$
 - procedures: $A; \text{proc}(\dots); B;$
- We will study how each of these are implemented in hardware and composed into computational structures

Switches: basic element of physical implementations

- Implementing a simple circuit

 

 close switch (if A is "1" or asserted)
and turn on light bulb (Z)




open switch (if A is "0" or unasserted)
and turn off light bulb (Z)

$$Z \equiv A$$


Z and A are equivalent boolean variables

Switches (cont'd)

 - Compose switches into more complex ones (Boolean functions):



$$Z \equiv A \text{ and } B$$

 


$$Z \equiv A \text{ or } B$$

Switching networks

- Switch settings
 - determine whether or not a conducting path exists to light the light bulb
- To build larger computations
 - use a light bulb (output of the network) to set other switches (inputs to another network).
- Connect together switching networks
 - to construct larger switching networks, i.e., there is a way to connect outputs of one network to the inputs of the next.

A switch?

- A mechanical switch

 

- A semiconductor switch or transistor


Transistor networks

- Modern digital systems are designed in CMOS technology
 - MOS stands for Metal-Oxide on Semiconductor
 - C is for complementary because there are both normally-open and normally-closed switches: nMOS and pMOS
- MOS transistors act as voltage-controlled switches

* CMOS: complementary metal-oxide semiconductor

n-channel (or n-type) MOS (nMOS) circuit

 - Three terminals: source-gate-drain (or S-G-D for short)
- three layers: polysilicon (used to be metal) – SiO₂ - substrate




- If G is at positive voltage, electrons in the substrate will move toward G terminal, which sets up a channel between S and D
 - And D is at high voltage, current will flow from drain to source
- Metal is replaced by polysilicon which is more adhesive

* n+: heavily doped n-type semiconductor

p-channel (or p-type) MOS (pMOS) circuit

 
- Three terminals: source-gate-drain (or S-G-D for short)
- Same principle, but reverse doping and voltage
 - Source (V_{ss}) is positive with regard to drain (V_{dd})
- Bubble indicates the inverted behavior



- If G is at positive voltage, the current does not flow
- If G is at ground level, the current flows


MOS transistors

 - MOS transistors have three terminals: drain, gate, and source
 - they act as switches in the following way:
if the voltage on the gate terminal is (some amount) higher/lower than the source terminal, then a conducting path will be established between the drain and source terminals



n-channel

 
open when voltage at G is low
closed when voltage at G is high



p-channel

closed when voltage at G is low
open when voltage at G is high

MOS networks


 


what is the relationship between x and y?

x	y
0 volts	
3 volts	

- A simple component is made up of two transistors
 - X: input
 - Y: output
 - What is this function?
- In CMOS circuits, pMos and nMOS are used in pair

Two input networks

  


what is the relationship between x, y and z1/z2?

x	y	z1	z2
0 volts	0 volts		
0 volts	3 volts		
3 volts	0 volts		
3 volts	3 volts		

Three input NAND gate

 - Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0



- In general, the more inputs, the more transistors (TRs)
- In CMOS, a variable requires a pair of TRs

Digital vs. analog

- Convenient to think of digital systems as having only discrete, digital, input/output values
- In reality, real electronic components exhibit continuous, analog behavior
- Why do we make the digital abstraction anyway?
 - switches operate this way
 - easier to think about a small number of discrete values
 - Quantization error, though
- Why does it work?
 - does not propagate small errors in values
 - always resets to 0 or 1

P.14


Combinational logic symbols

- Common combinational logic systems have standard symbols called logic gates


- Buffer,




- NOT

 


- AND,

 


- NAND

 

- OR,

 


- NOR

 

easy to implement
with CMOS transistors
(the switches we have
available and use most)


Combinational vs. sequential digital circuits

 - A simple model of a digital system is a unit with inputs and outputs:




- Combinational means "memory-less"
 - a digital circuit is combinational if its output values only depend on its (current) input values

 Combinational vs. sequential digital circuits



(a) Combinational

$$\text{Output} = f(\text{In})$$

 

(b) Sequential

$$\text{Output} = f(\text{In}, \text{Previous In})$$

Sequential logic

- Sequential systems
 - exhibit behaviors (output values) that depend not only on the current input values, but also on previous input values


Example of combinational and sequential logic

■ Combinational:

- ❑ input A, B
- ❑ wait for clock edge
- ❑ observe C
- ❑ wait for another clock edge
- ❑ observe C again: will stay the same

■ Sequential:

 - ❑ input A, B
- ❑ wait for clock edge
- ❑ observe C
- ❑ wait for another clock edge
- ❑ observe C again: may be different



Abstractions

- Some we've seen already
 - digital interpretation of analog values
 - transistors as switches
 - switches as logic gates
 - use of a clock to realize a synchronous sequential circuit
- Some others we will see
 - truth tables and Boolean algebra to represent combinational logic
 - encoding of signals with more than two logical values into binary form
 - state diagrams to represent sequential logic
 - hardware description languages to represent digital logic
 - waveforms to represent temporal behavior

An example

- Calendar subsystem: number of days in a month (to control watch display)
 - Combinational logic
 - used in controlling the display of a wrist-watch LCD screen
 - inputs: month, leap year flag
 - outputs: number of days


Implementation in software

```
integer number_of_days ( month, leap_year_flag)
{
    switch (month) {
        case 1: return (31);
        case 2: if (leap_year_flag == 1) then return (29)
                else return (28);
        case 3: return (31);
        ...
        case 12: return (31);
        default: return (0);
    }
}
```

P.16

Implementation as a combinational digital system

 - Encoding:
 - how many bits for each input/output?
 - binary number for month
 - four wires for 28, 29, 30, and 31
- Behavior:
 - combinational
 - truth table specification



month	leap	d28	d29	d30	d31
0000	-	-	-	-	-
0001	-	0	0	0	1
0010	0	1	0	0	0
0011	1	0	1	0	0
0011	-	0	0	0	1
0100	-	0	0	1	0
0101	-	0	0	0	1
0110	-	0	0	1	0
0111	-	0	0	0	1
1000	-	0	0	0	1
1001	-	0	0	1	0
1010	-	0	0	0	1
1011	-	0	0	1	0
1100	-	0	0	0	1
1101	-	-	-	-	-
111-	-	-	-	-	-

Don't care

Combinational example (cont'd)

- Truth-table to logic to switches to gates
 - $d_{28} = 1$ when month=0010 and leap=0
 - $d_{28} = m_8' \cdot m_4' \cdot m_2 \cdot m_1' \cdot \text{leap}'$
 - $d_{31} = 1$ when month=0001 or month=0011 or ... month=1100
 - $d_{31} = (m_8' \cdot m_4' \cdot m_2' \cdot m_1) + (m_8' \cdot m_4' \cdot m_2 \cdot m_1) + \dots$
 $(m_8 \cdot m_4 \cdot m_2' \cdot m_1')$
 - $d_{31} =$ can we simplify more?

symbol for and

symbol for or

symbol for not

month	leap	d28	d29	d30	d31
0001	-	0	0	0	1
0010	0	1	0	0	0
0010	1	0	1	0	0
0011	-	0	0	0	1
0100	-	0	0	1	0
...					
1100	-	0	0	0	1
1101	-	-	-	-	-
111-	-	-	-	-	-
0000	-	-	-	-	-



Combinational example (cont'd)

- $d_{28} = m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_{1'} \cdot \text{leap}'$
- $d_{29} = m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_{1'} \cdot \text{leap}$
- $d_{30} = (m_{8'} \cdot m_{4'} \cdot m_{2'} \cdot m_{1'}) + (m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_{1'}) + (m_{8'} \cdot m_{4'} \cdot m_{2'} \cdot m_1) + (m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_1)$
 $= (m_{8'} \cdot m_{4'} \cdot m_{1'}) + (m_{8'} \cdot m_{4'} \cdot m_1)$
- $d_{31} = (m_{8'} \cdot m_{4'} \cdot m_{2'} \cdot m_1) + (m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_1) + (m_{8'} \cdot m_{4'} \cdot m_{2'} \cdot m_{1'}) + (m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_{1'}) + (m_{8'} \cdot m_{4'} \cdot m_{2'} \cdot m_1) + (m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_{1'})$



Combinational example (cont'd)

- $d_{28} = m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_{1'} \cdot \text{leap}'$
- $d_{29} = m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_{1'} \cdot \text{leap}$
- $d_{30} = (m_{8'} \cdot m_{4'} \cdot m_{2'} \cdot m_{1'}) + (m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_{1'}) + (m_{8'} \cdot m_{4'} \cdot m_{2'} \cdot m_1) + (m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_1)$
- $d_{31} = (m_{8'} \cdot m_{4'} \cdot m_{2'} \cdot m_1) + (m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_1) + (m_{8'} \cdot m_{4'} \cdot m_{2'} \cdot m_{1'}) + (m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_{1'}) + (m_{8'} \cdot m_{4'} \cdot m_{2'} \cdot m_1) + (m_{8'} \cdot m_{4'} \cdot m_2 \cdot m_{1'})$

  

Another example (Door combination lock)

- punch in 3 values in sequence and the door opens; if there is an error the lock must be reset; once the door opens the lock must be reset
 - Sequential logic
 - inputs: sequence of input values, reset
 - Numeric number: 4 wires
 - outputs: door open/close
 - memory: must remember combination
 - or always have it available as an input

Implementation in software

```
integer combination_lock ( ) {
    integer v1, v2, v3;
    integer error = 0;
    static integer c[3] = 3, 4, 2;

    while (!new_value( ));
    v1 = read_value( );
    if (v1 != c[1]) then error = 1;

    while (!new_value( ));
    v2 = read_value( );
    if (v2 != c[2]) then error = 1;

    while (!new_value( ));
    v3 = read_value( );
    if (v2 != c[3]) then error = 1;


    if (error == 1) then return(0); else return (1);
}
```

Array index starts from 1

P.19, 20


Implementation as a sequential digital system

- Encoding:
 - ❑ how many bits per input value?
 - ❑ how many values in sequence?
 - ❑ how do we know a new input value is entered?
 - ❑ how do we represent the states of the system?
- Behavior:
 - ❑ clock wire tells us when it's ok to look at inputs (i.e., they have settled after change)
 - ❑ sequential: sequence of values must be entered
 - ❑ sequential: remember if an error occurred
 - ❑ finite-state specification

 

Sequential example (cont'd): abstract control

 - Finite-state diagram
 - states: 5 states
 - represent point in execution of machine
 - each state has inputs and outputs
 - transitions: 6 from state to state, 5 self transitions, 1 global
 - changes of state occur when clock says it's ok
 - based on value of inputs
 - inputs: reset, new, results of comparisons
 - output: open/closed



Sequential example (cont'd): data-path vs. control


- Internal structure

- data-path

- storage for combination
 - comparators

- control

 
- finite-state machine controller
 - control for data-path
 - state changes controlled by clock



* Multiplexer (MUX)


Sequential example (cont'd): FSM

 - Finite-state machine (FSM)
 - refine state diagram to include internal structure



Sequential example (cont'd): FSM

 - Finite-state machine
 - generate state table (much like a truth-table)



reset	new	equal	state	next state	mux	open/closed
1	-	-	-	S1	C1	closed
0	0	-	S1	S1	C1	closed
0	1	0	S1	ERR	-	closed
0	1	1	S1	S2	C2	closed
0	0	-	S2	S2	C2	closed
0	1	0	S2	ERR	-	closed
0	1	1	S2	S3	C3	closed
0	0	-	S3	S3	C3	closed
0	1	0	S3	ERR	-	closed
0	1	1	S3	OPEN	-	open
0	-	-	OPEN	OPEN	-	open
0	-	-	ERR	ERR	-	closed

* state is not input, but internal variable

Sequential example (cont'd): encoding

■ Encode state table

- state can be: S1, S2, S3, OPEN, or ERR
 - needs at least 3 bits to encode: 000, 001, 010, 011, 100
 - and as many as 5: 00001, 00010, 00100, 01000, 10000
 - choose 4 bits: 0001, 0010, 0100, 1000, 0000
- output mux can be: C1, C2, or C3
 - needs 2 to 3 bits to encode
 - choose 3 bits: 001, 010, 100
- output open/closed can be: open or closed
 - needs 1 or 2 bits to encode
 - choose 1 bits: 1, 0

Sequential example (cont'd): encoding

- Encode state table

- state can be: S1, S2, S3, OPEN, or ERR
 - choose 4 bits: 0001, 0010, 0100, 1000, 0000
- output mux can be: C1, C2, or C3
 - choose 3 bits: 001, 010, 100
- output open/closed can be: open or closed
 - choose 1 bits: 1, 0

Internal input

Internal output

system's or external output

external input

	reset	new	equal	state	next state	mux	open/closed
	1	-	-	-	0001	001	0
	0	0	-	0001	0001	001	0
	0	1	0	0001	0000	-	0
	0	1	1	0001	0010	010	0
	0	0	-	0010	0010	010	0
	0	1	0	0010	0000	-	0
	0	1	1	0010	0100	100	0
	0	0	-	0100	0100	100	0
	0	1	0	0100	0000	-	0
	0	1	1	0100	1000	-	1
	0	-	-	1000	1000	-	1
	0	-	-	0000	0000	-	0


good choice of encoding!

mux is identical to last 3 bits of next state


open/closed is identical to first bit of state

Sequential example (cont'd): controller implementation


- Implementation of the controller

 

 
special circuit element, called a register, for remembering inputs when told to by clock



Design hierarchy

 

terminologies

 

Summary

- That was what the entire course is about
 - converting solutions to problems into combinational and sequential networks effectively organizing the design hierarchically
 - doing so with a modern set of design tools that lets us handle large designs effectively
 - taking advantage of optimization opportunities