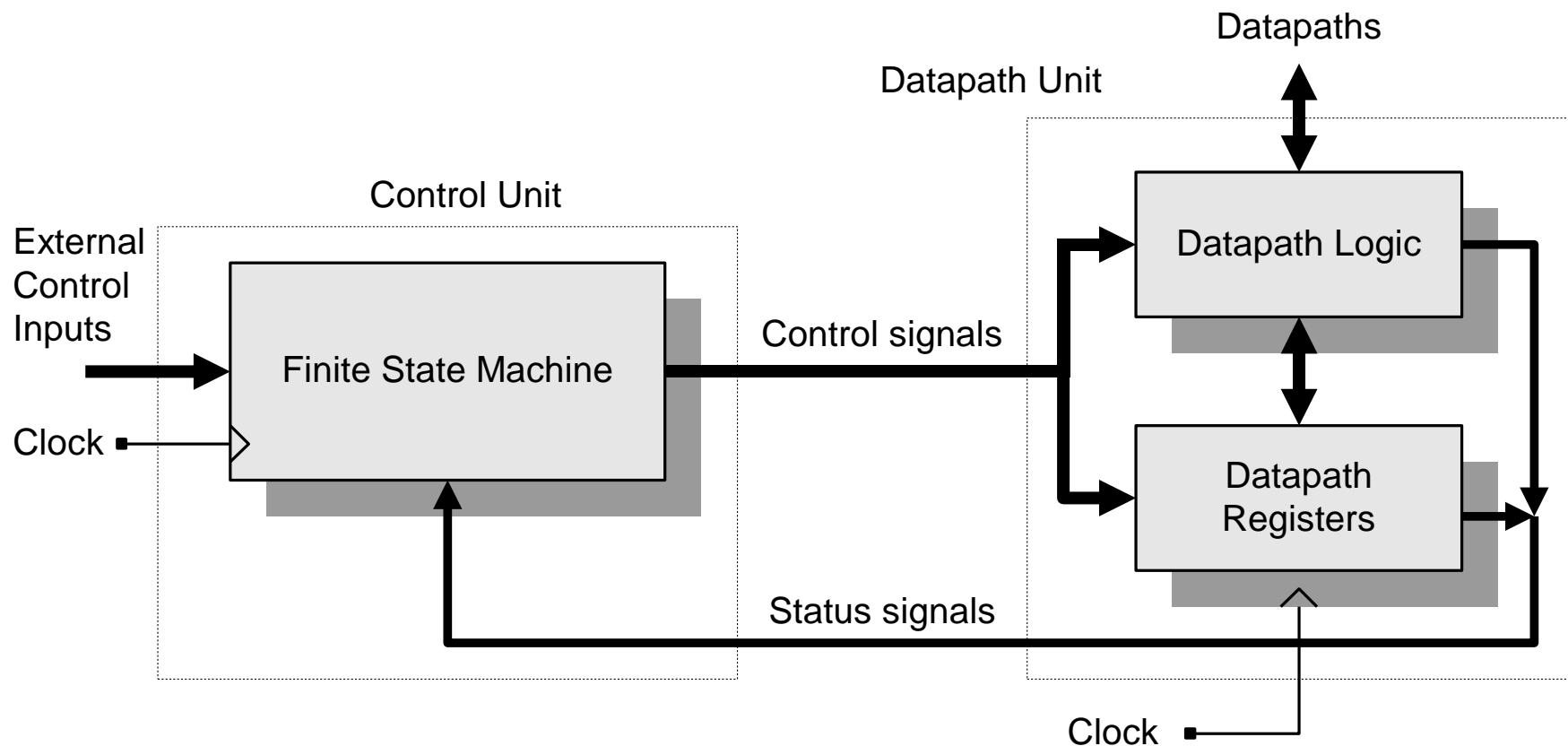



# CPU Design Example

Prof. Soo-Ik Chae

# Partitioned Sequential Machine



# Application-Driven Architecture

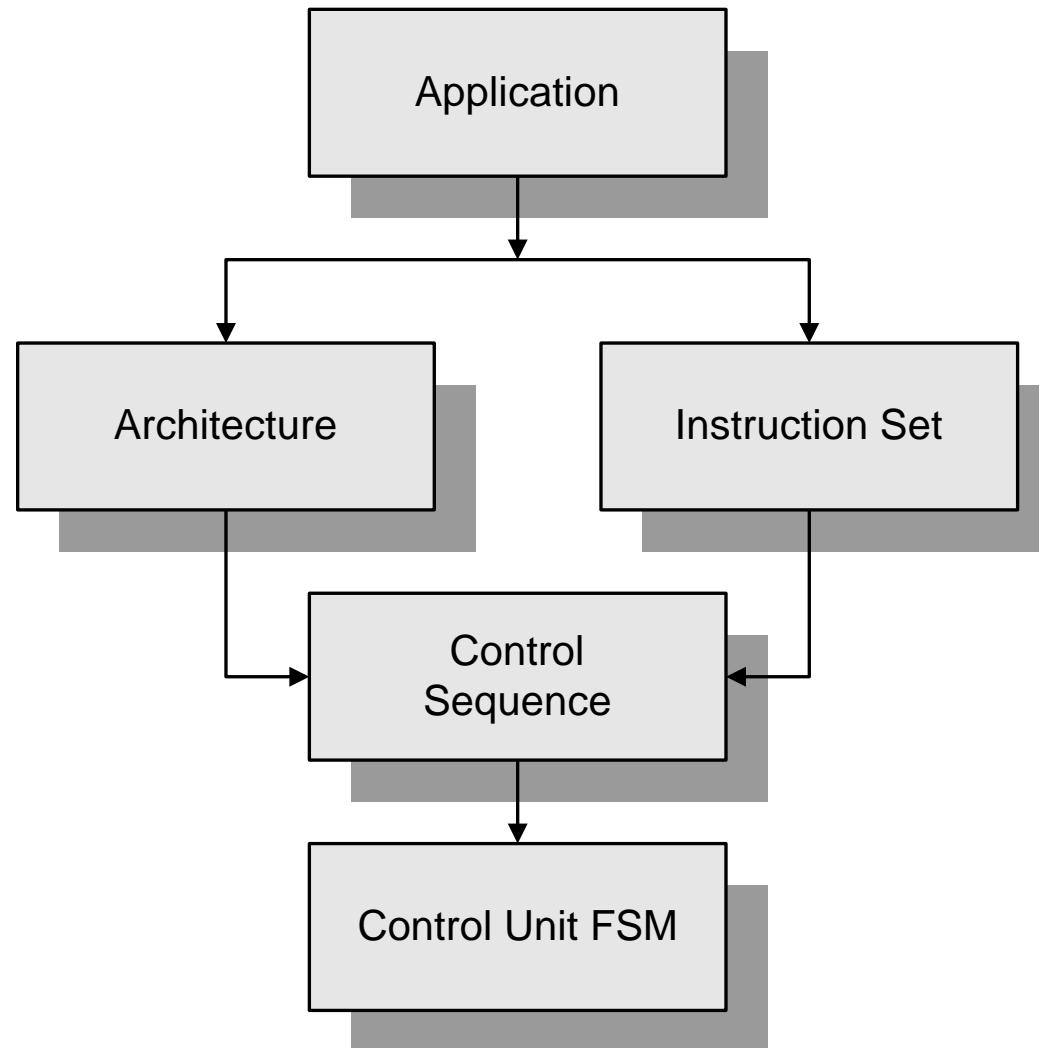

## RISC ALU

- ❖ Digital circuits are designed to perform arithmetic and/or logic operations, or in general a mixture of them
  - Arithmetic operations : ADD, SUB, MUL, DIV etc.
  - Logic operations : NOT, AND, OR etc.
- ❖ A mathematical problem usually can be decomposed into a number of arithmetic and/or logic operations which may be executed serially or in parallel. However, to save the cost of hardware circuits, usually only one copy of circuit is built for each specific arithmetic or logic function. As a result, the mathematical problem is rearranged into a sequential order of the combinations of these operations.
  - E.g. : partition  $D = A + B + C$  into  $D \leftarrow A + B$  followed by  $D \leftarrow D + C$
- ❖ These arithmetic or logic circuits are collected together to form an arithmetic and logic unit (ALU), and a set of systematic methods are created for this ALU to invoke the functions built in the ALU
- ❖ These methods are collectively referred to as the instruction set, which may also involve memory access and/or data movement


## RISC vs CISC

- ❖ To support the functions of ALU, a number of data elements such as registers and counters are also necessary to help bring data from memory/register to the inputs of ALU and store the output of ALU to memory or registers
- ❖ The entire set of supporting elements plus the ALU as well as its accompanying instruction set is referred to as the central processing unit (CPU)
- ❖ Central processing unit (CPU)
  - As it is suggested by its name, all arithmetic operations are executed by this unit one instruction at a time.
  - There are two types of design methodologies for the instruction sets of CPU
    - Reduced instruction-set computers (RISC), which features
      - A small number of instructions that execute in short cycles
      - A small number of cycles per instruction
    - Complex instruction-set computers (CISC)

## RISC Stored Program Machine (SPM)

- ❖ A RISC store-program machine (SPM) consists of three functional units : a processor, a controller and memory
- ❖ Program instructions and data are stored in memory
- ❖ Instructions are fetched from memory synchronously, decoded and executed to
  - Operate on data with ALU
  - Change the contents of storage registers
  - Change the content of the program counter (PC), instruction register (IR) and the address register (ADD\_R)
  - Change the content of memory
  - Retrieve data and instructions from memory
  - Control the movement of data on the system busses

# RISC Stored Program Machine (SPM)

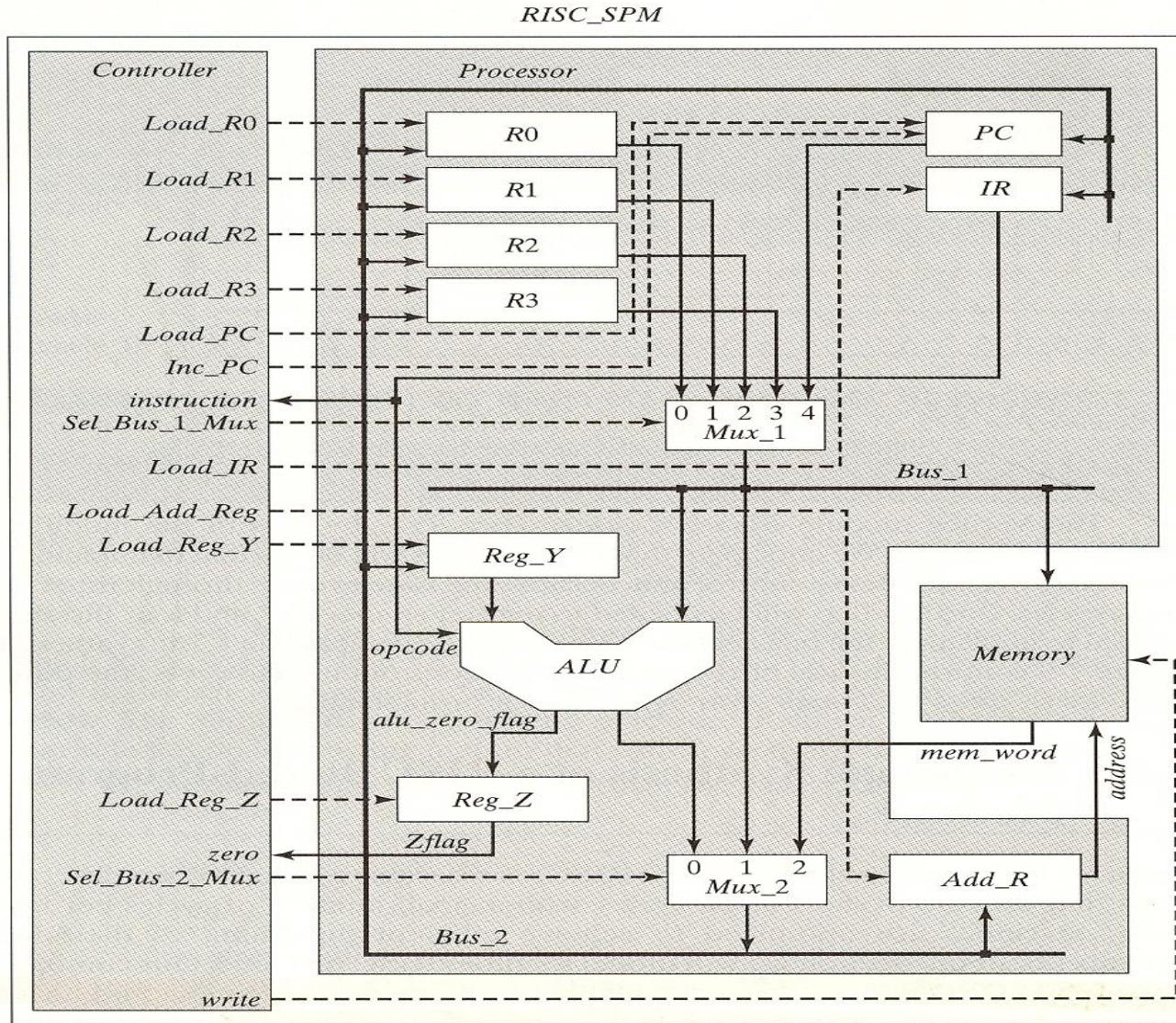

## Control Functions

- ❖ Functions of the control unit:
  - Determine when to load registers
  - Select the path of data through the multiplexers
  - Determine when data should be written to memory
  - Control the three-state busses in the architecture.

# Control Signals

## Control Signal

*Load\_Add\_Reg*

## Action

Loads the address register

*Load\_PC*

Loads *Bus\_2* to the program counter

*Load\_IR*

Loads *Bus\_2* to the instruction register

*Inc\_PC*

Increments the program counter

*Sel\_Bus\_1\_Mux*

Selects among the *Program Counter*, *R0*, *R1*, *R2*, and *R3* to drive *Bus\_1*

*Sel\_Bus\_2\_Mux*

Selects among *Alu\_out*, *Bus\_1*, and memory to drive *Bus\_2*

*Load\_R0*

Loads general purpose register *R0*

*Load\_R1*

Loads general purpose register *R1*

*Load\_R2*

Loads general purpose register *R2*

*Load\_R3*

Loads general purpose register *R3*

*Load\_Reg\_Y*


Loads *Bus\_2* to the register *Reg\_Y*

*Load Reg\_Z*

Stores output of *ALU* in register *Reg\_Z*

*write*

Loads *Bus\_1* into the *SRAM* memory

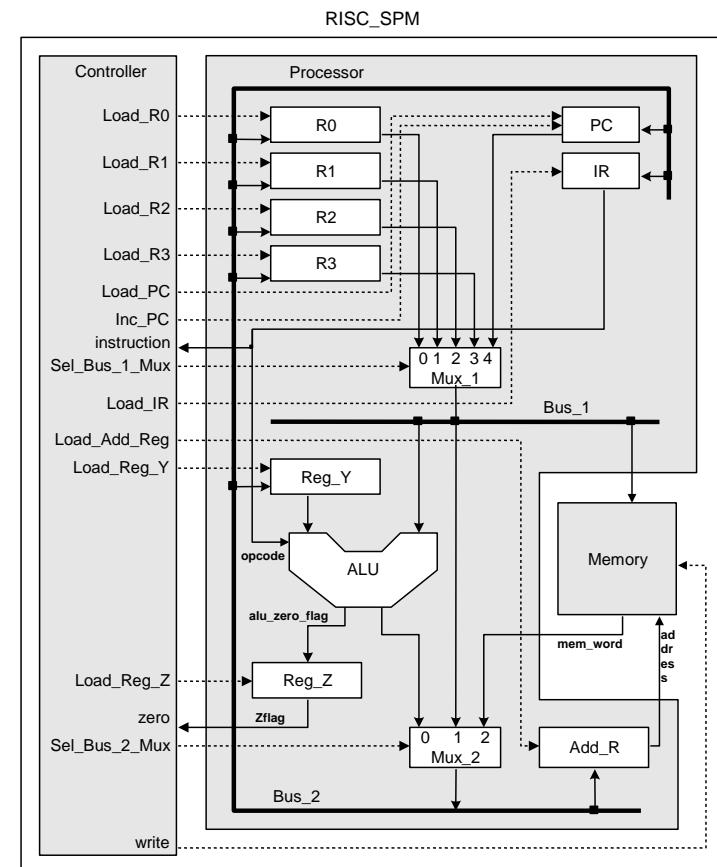

## RISC SPM: Instruction Set [1]

- ❖ The design of the controller depends on the processor's instruction set.
- ❖ RISC SPM has two types of instructions.
- ❖ Short Instruction – 8 bits (basic arithmetic)

opcode				source		destination	
0	0	1	0	0	1	1	0

- ❖ Long Instruction – 16 bits (accessing memory)

opcode				source		destination	
0	1	1	0	1	0	don't care	don't care
address							
0	0	0	1	1	1	0	1

# RISC SPM: Instruction Set [2]

## ❖ Instruction Set

- Single-Byte instruction
  - NOP
  - ADD : Dest  $\leftarrow$  Source + Des
  - AND : Dest  $\leftarrow$  Source & Des.
  - NOT : Dest  $\leftarrow$  Source
  - SUB : Dest  $\leftarrow$  Source - Des
- Two-Byte instruction
  - RD : Dest  $\leftarrow$  Memory
  - WR : Memory  $\leftarrow$  Source
  - BR : PC  $\leftarrow$  Address
  - BRZ : PC  $\leftarrow$  Address if zero flag == 0

<b>Opcode</b>				<b>Source</b>	<b>Dest.</b>

<b>Opcode</b>				<b>Source</b>	<b>Dest.</b>	
<b>Address</b>						
					X	X

# RISC SPM: Instruction Set [3]

Instr	Instruction Word			Action
	opcode	src	dest	
NOP	0000	??	??	none
ADD	0001	src	dest	dest <= src + dest
SUB	0010	src	dest	dest <= dest - src
AND	0011	src	dest	dest <= src && dest
NOT	0100	src	dest	dest <= ~src
RD*	0101	??	dest	dest <= memory[Add_R]
WR*	0110	src	??	memory[Add_R] <= src
BR*	0111	??	??	PC <= memory[Add_R]
BRZ*	1000	??	??	PC <= memory[Add_R]
HALT	1111	??	??	Halts execution until reset

\* Requires a second word of data; ? denotes a don't care.

## Controller Design

- ❖ Three phases of operation: *fetch*, *decode*, and *execute*.
  - Fetching: Retrieves an instruction from memory (2 clock cycles)
  - Decoding: Decodes the instruction, manipulates datapaths, and loads registers (1 cycle)
  - Execution: Generates the results of the instruction (0, 1, or 2 cycles)

## Controller States [1]

*S\_idle* State entered after reset is asserted. No action.

---

*S\_fet1* Load the Add\_R with the contents of the PC

*S\_fet2* Load the IR with the word addressed by the Add\_R,  
Increment the PC

---

*S\_dec* Decode the IR

Assert signals to control datapaths and register transfers.

---

*S\_ex1* Execute the *ALU* operation for a single-byte instruction,

Conditionally assert the zero flag, Load the destination register

## Controller States [2]

*S\_rd1* Load Add\_R with the second byte of an RD instruction  
Increment the PC.

*S\_rd2* Load the destination register with memory[Add\_R]

---

*S\_wr1* Load Add\_R with the second byte of a WR instruction,  
Increment the PC.

*S\_wr2* Write memory[Add\_R] with the source register

---

*S\_br1* Load Add\_R with the second byte of a BR instruction  
Increment the PC.

*S\_br2* Load the PC with the memory[Add\_R]

---

*S\_halt* Default state to trap failure to decode a valid instruction



Which states are similar?

- ❖ RISC-SPM controller : The machine has three phases of operation: fetch, decode and execute
  - A total 11 states
    - S\_idle: initial state
    - S\_fet1: addr reg  $\Leftarrow$  PC, S\_fet2: load instruction  $\Leftarrow$  mem[addr]
    - S\_dec: decode the instr and assert control signals to datapath
    - S\_ex1: execute the ALU for single-byte instr and load dest reg
    - S\_rd1: addr reg  $\Leftarrow$  2nd byte of a RD instruction and PC ++
    - S\_rd2: dest  $\Leftarrow$  mem [S\_rd1]
    - S\_wr1: addr reg  $\Leftarrow$  2nd byte of a WR instruction and PC ++
    - S\_wr2: mem [S\_wr1]  $\Leftarrow$  source
    - S\_br1: addr reg  $\Leftarrow$  2nd byte of a BR instruction and PC++
    - S\_br2: PC  $\Leftarrow$  mem [S\_br1]
    - S\_halt : trap failure to decode a valid instruction



## Instruction Sequence

- ❖ Fetch instruction from memory
- ❖ Decode instruction and fetch operands
- ❖ Execute instruction
  - ALU operations
  - Update storage registers
  - Update program counter (PC)
  - Update the instruction register (IR)
  - Update the address register (ADD\_R)
  - Update memory
  - Control datapaths



# Controller ASM: NOP/ADD/SUB/AND

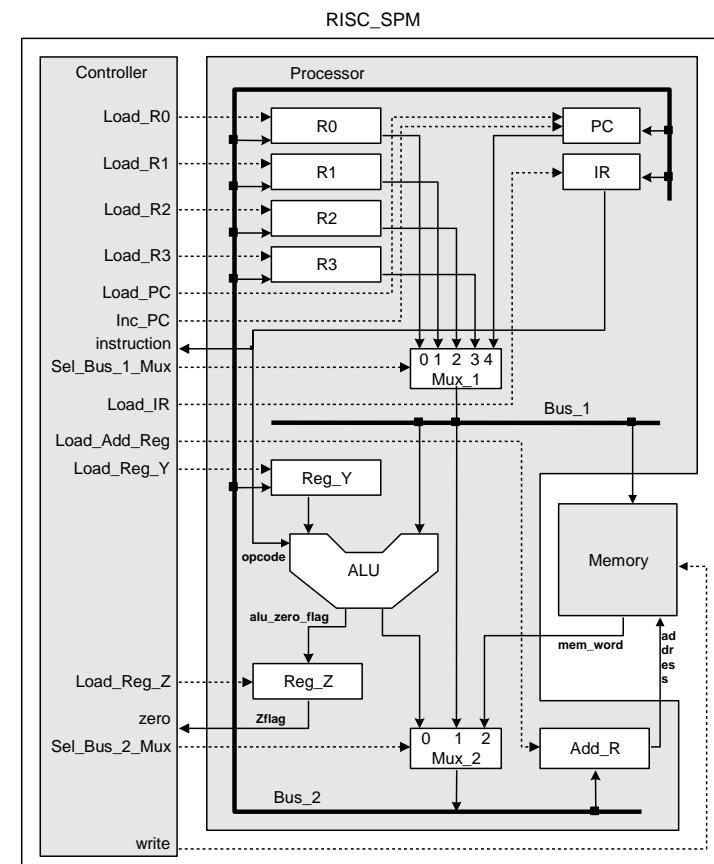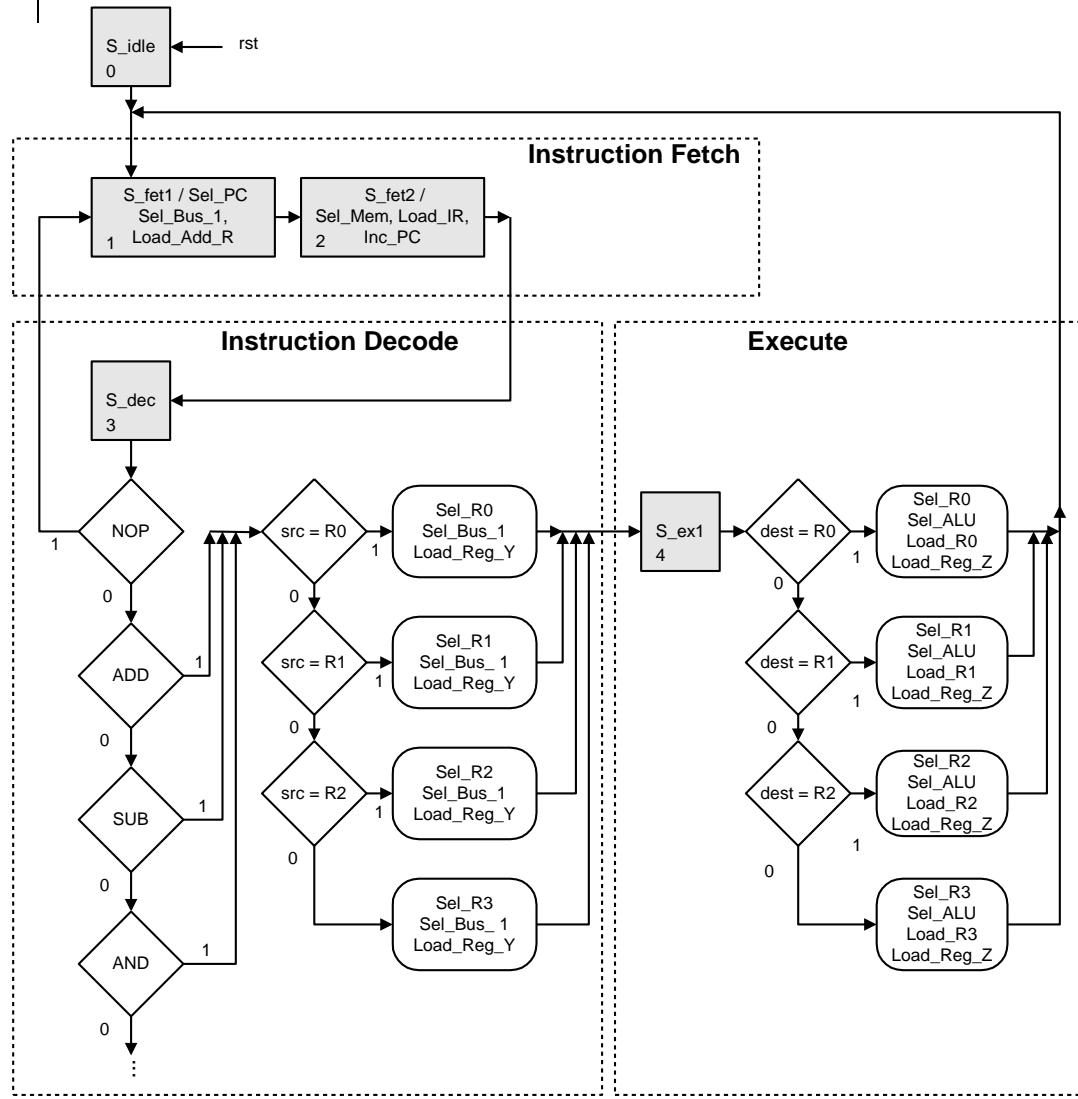



# Controller ASM: NOT

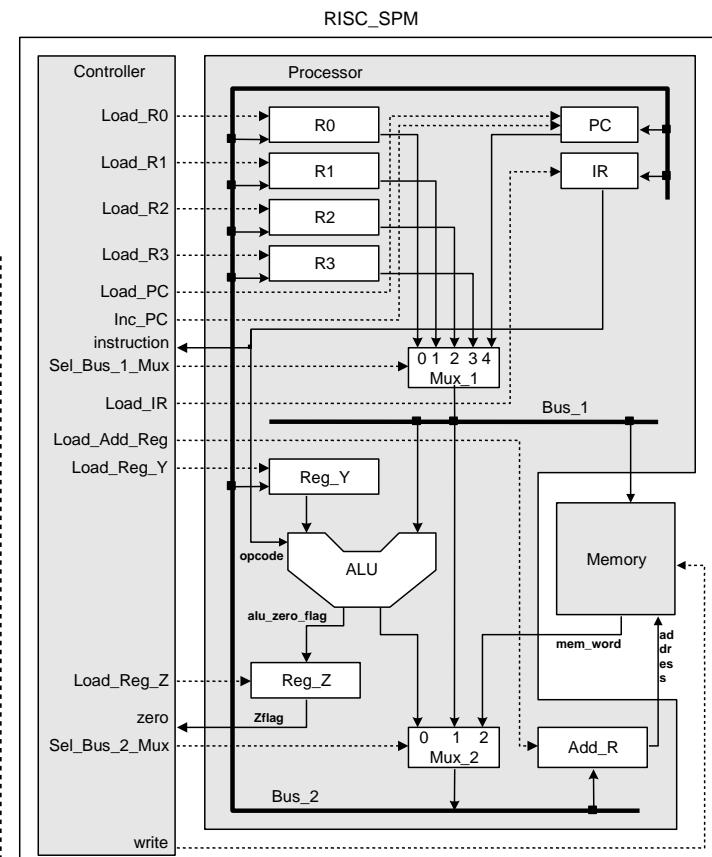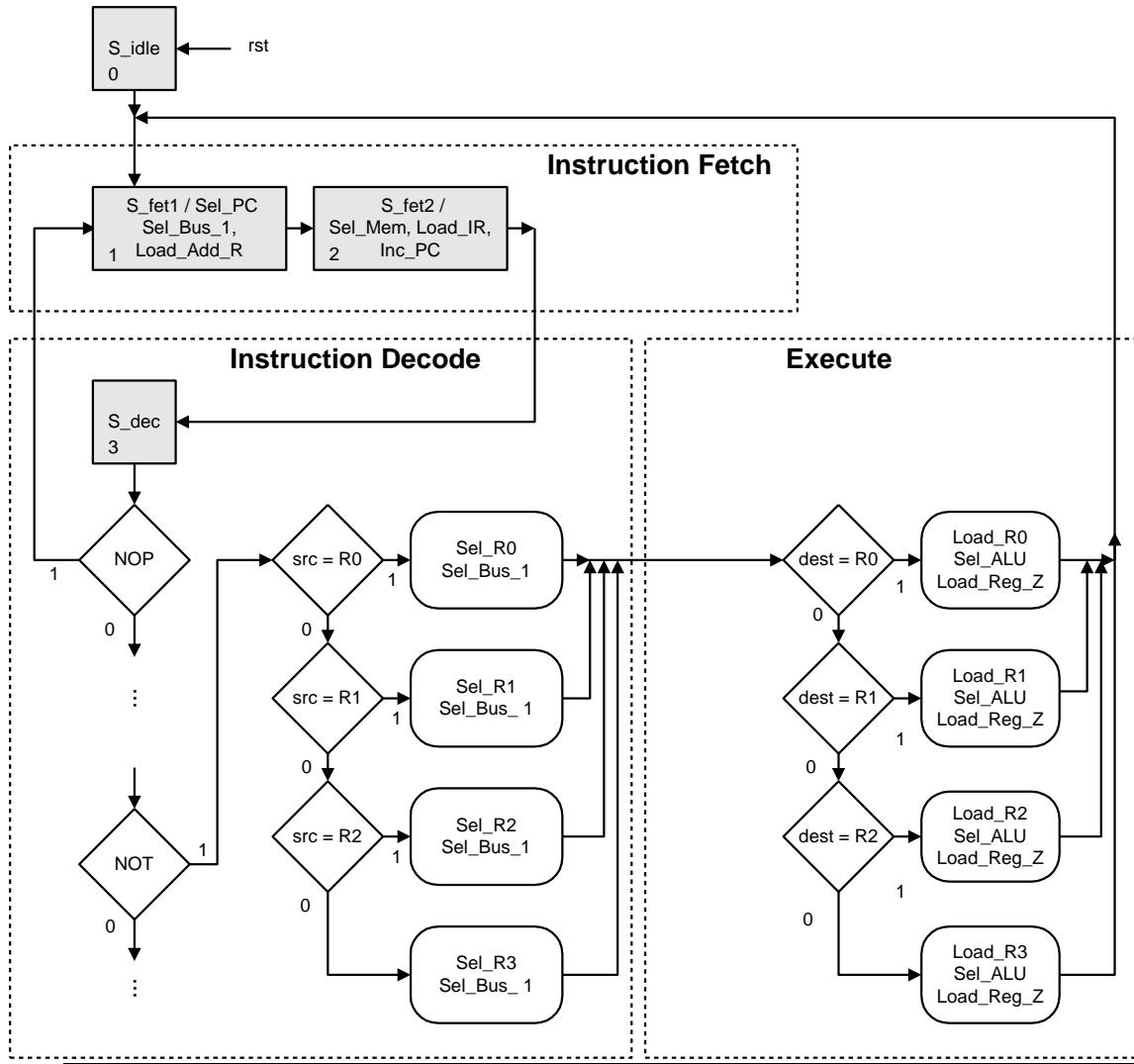



## Controller ASM: RD

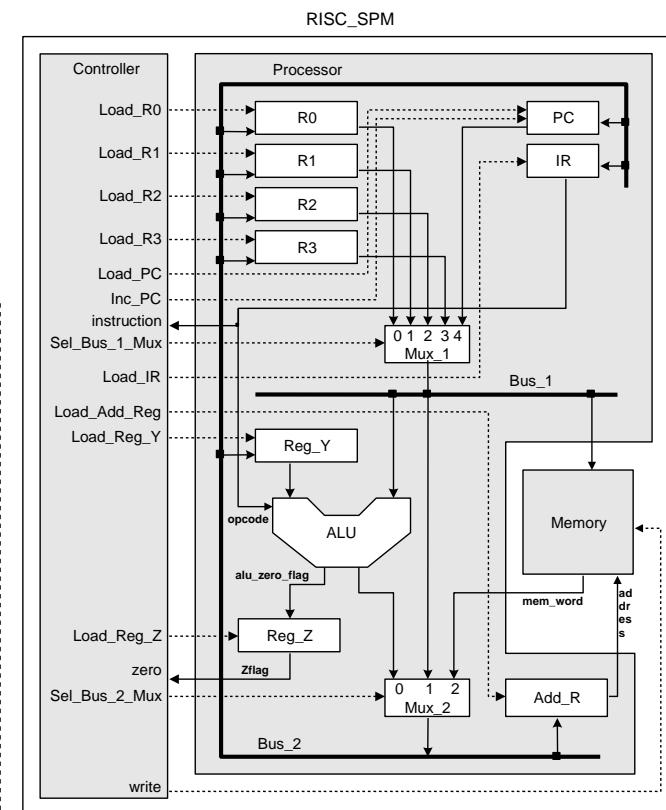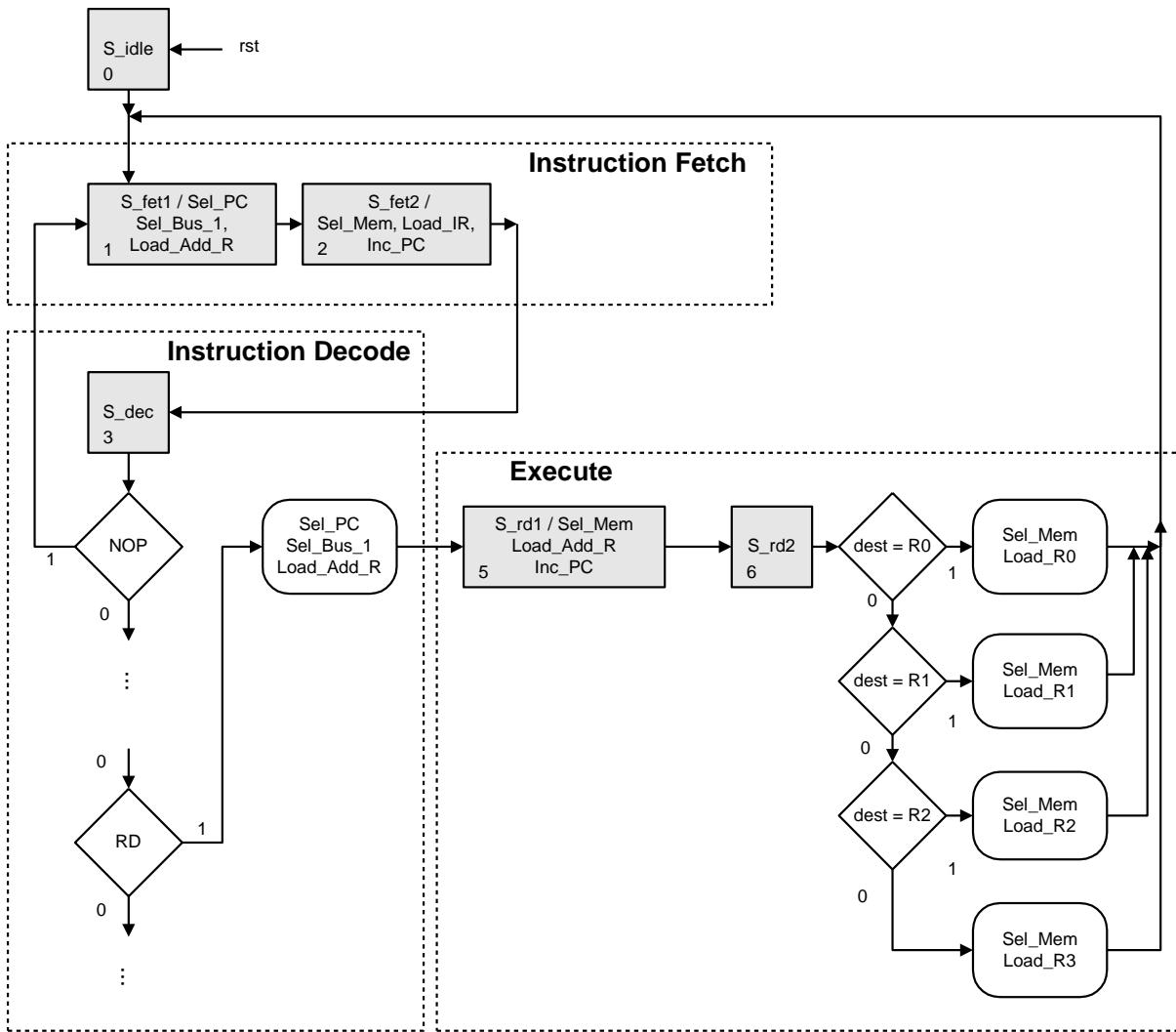


## Controller ASM: WR

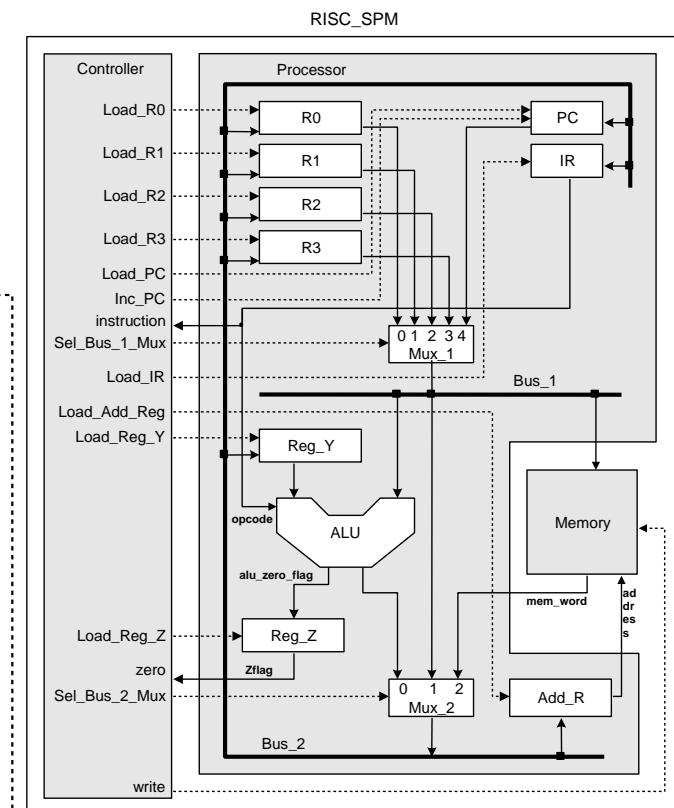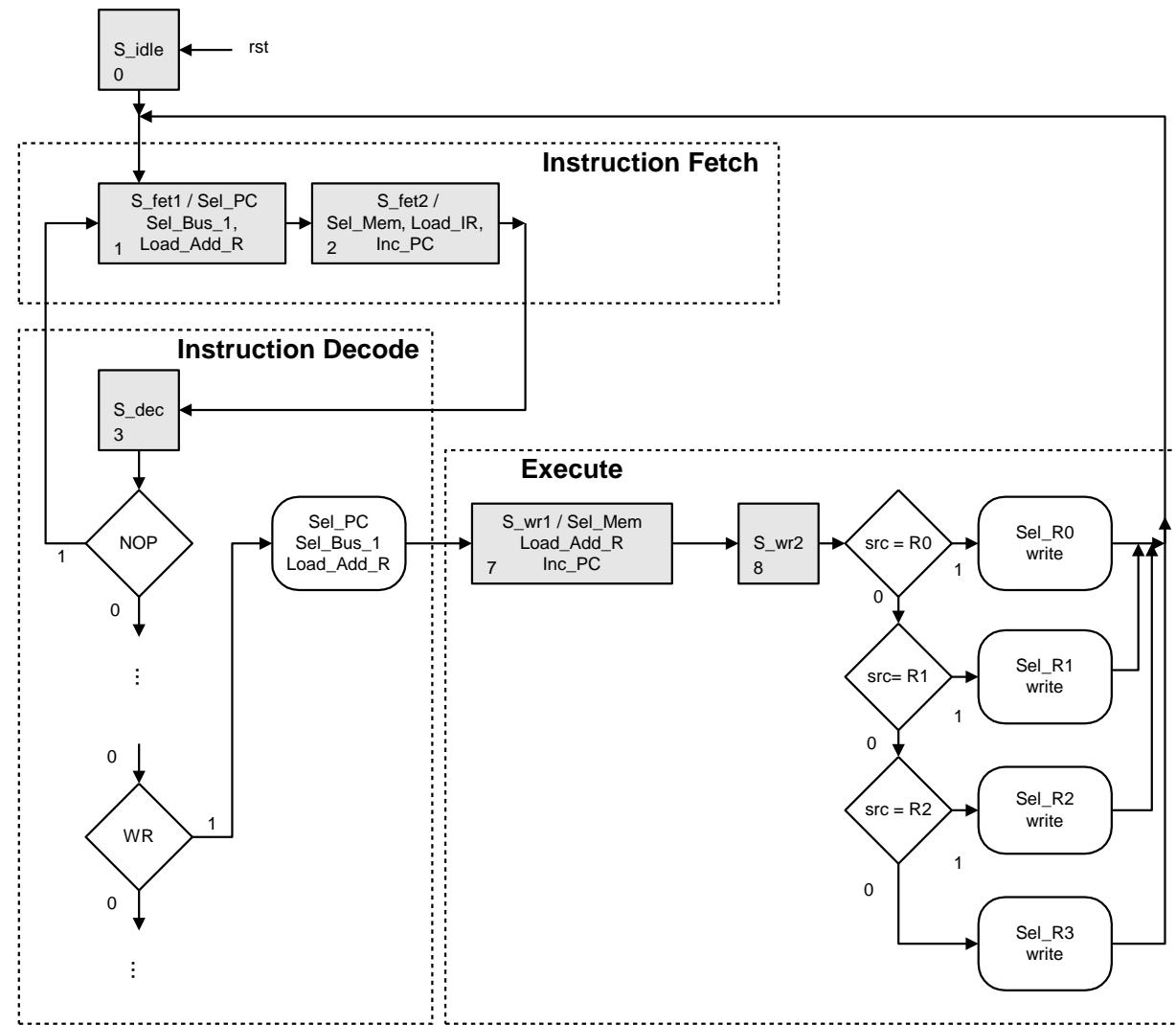

# Controller ASM: BR/BRZ

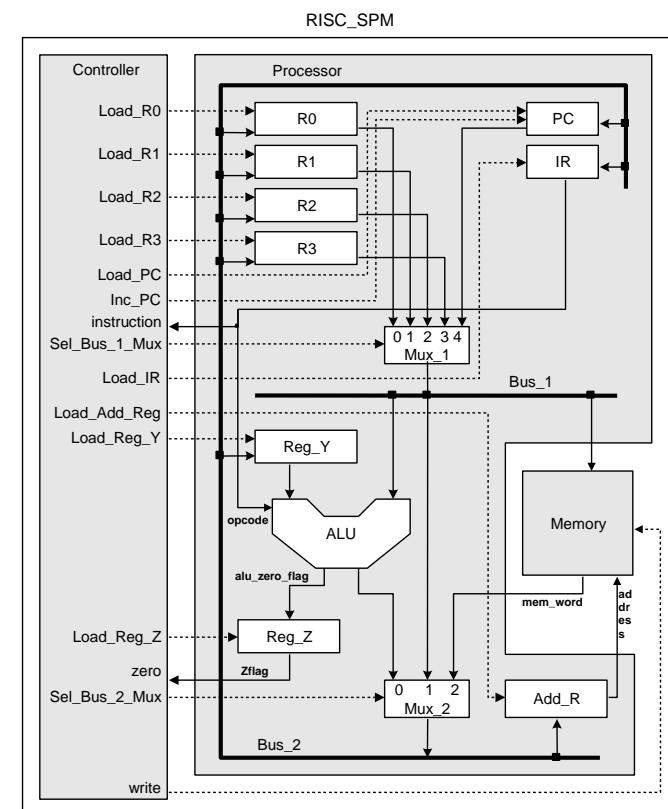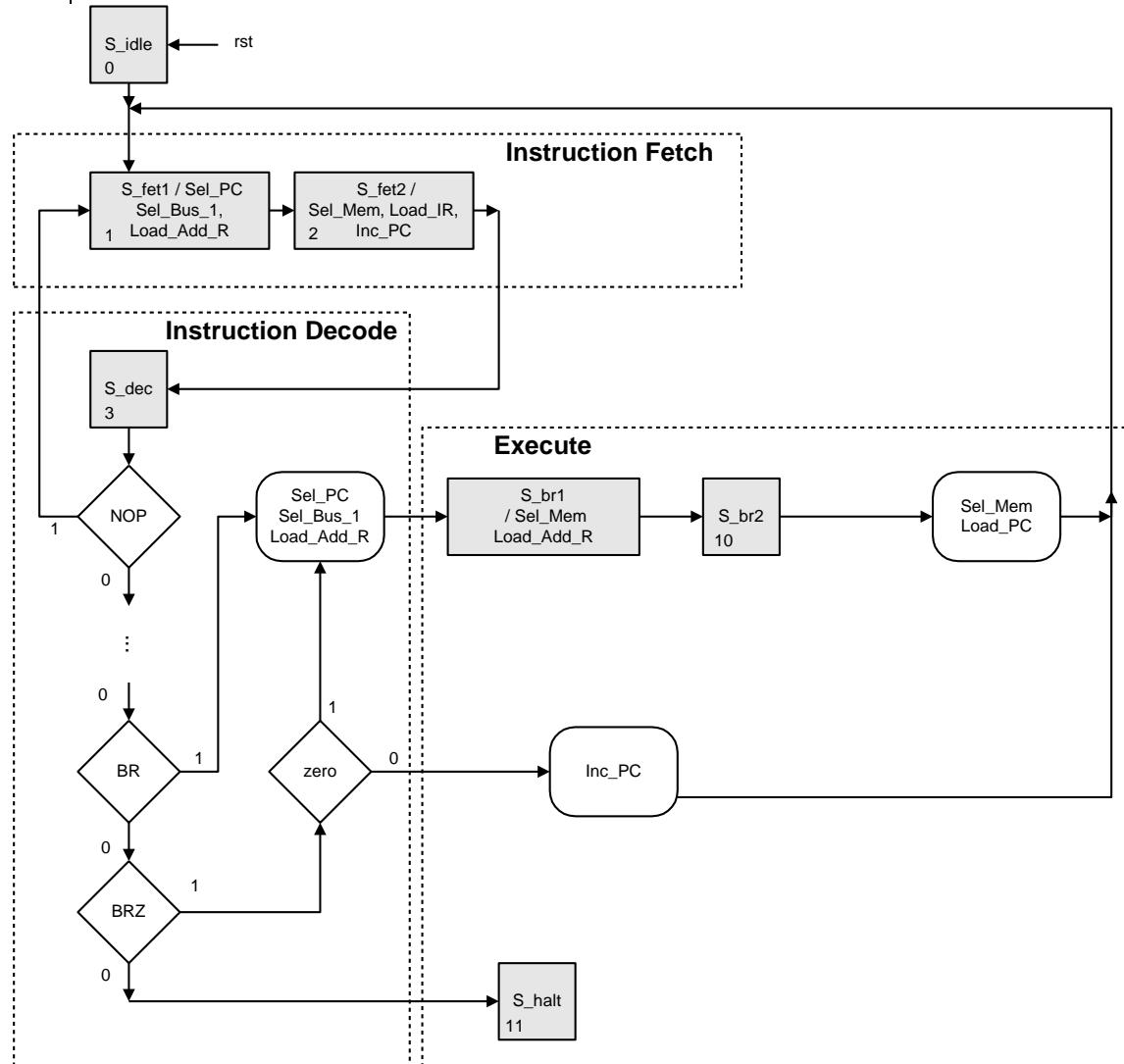

# RISC Stored Program Machine (SPM)

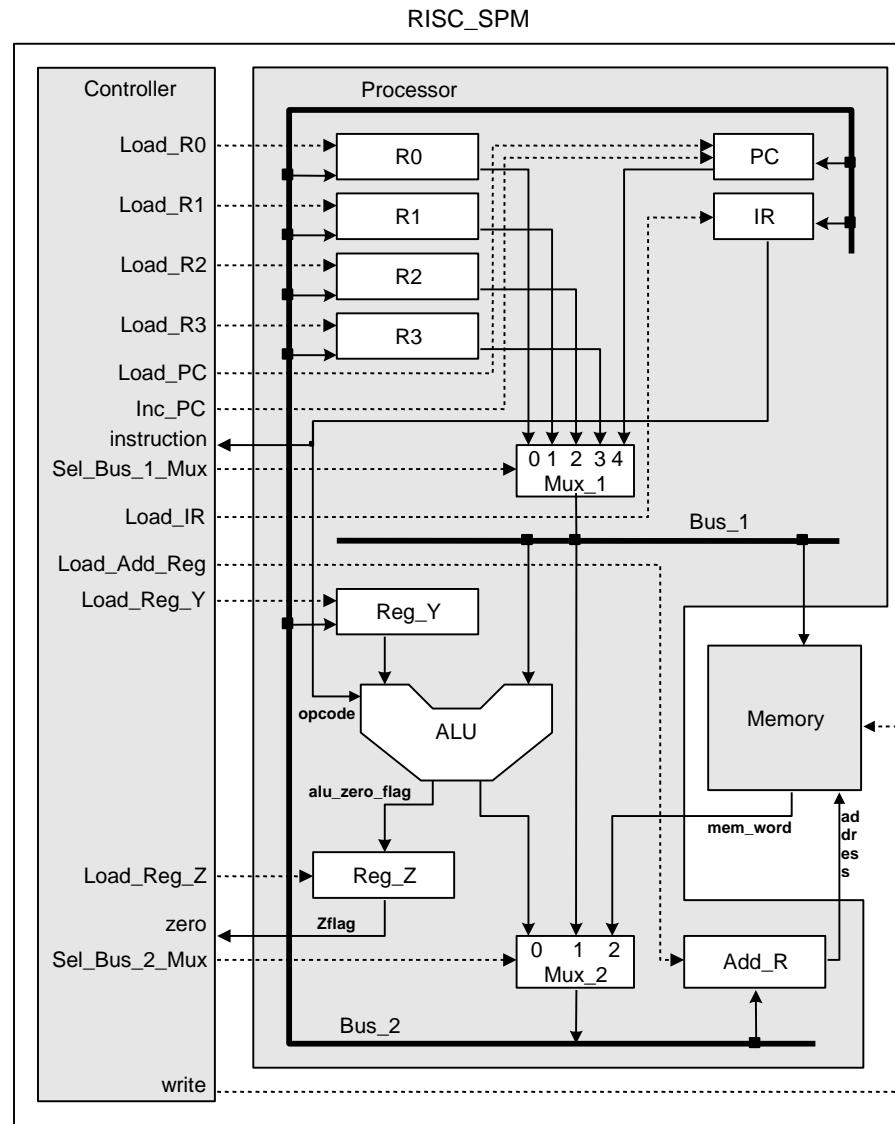

# RISC-SPM [1]

```
module RISC_SPM (clk, rst);
    parameter word_size = 8;
    parameter Sel1_size = 3;
    parameter Sel2_size = 2;
    wire [Sel1_size-1: 0] Sel_Bus_1_Mux;
    wire [Sel2_size-1: 0] Sel_Bus_2_Mux;
    input clk, rst;
    // Data Nets
    wire zero;
    wire [word_size-1: 0] instruction, address, Bus_1, mem_word;
    // Control Nets
    wire Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC, Load_IR;
    wire Load_Add_R, Load_Reg_Y, Load_Reg_Z;
    wire write;
```

## RISC-SPM [2]

```
Processing_Unit M0_Processor (instruction, zero, address, Bus_1, mem_word, Load_R0,  
Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC, Sel_Bus_1_Mux, Load_IR,  
Load_Add_R, Load_Reg_Y, Load_Reg_Z, Sel_Bus_2_Mux, clk, rst);
```

```
Control_Unit M1_Controller (Load_R0, Load_R1, Load_R2, Load_R3,  
Load_PC, Inc_PC, Sel_Bus_1_Mux, Sel_Bus_2_Mux , Load_IR,  
Load_Add_R, Load_Reg_Y, Load_Reg_Z, write, instruction, zero,  
clk, rst);
```

```
Memory_Unit M2_MEMORY
```

```
    (.data_out(mem_word), .data_in(Bus_1), .address(address), .clk(clk), .write(write) );
```

```
endmodule
```

```
/* For parameters that occur in multiple modules, include them in a separate file (e.g., definitions.v)  
and then use `include definitions.v */
```

```
module RISC_SPM (clk, rst);
    parameter word_size = 8;
    parameter Sel1_size = 3;
    parameter Sel2_size = 2;
    wire [Sel1_size-1: 0] Sel_Bus_1_Mux;
    wire [Sel2_size-1: 0] Sel_Bus_2_Mux;
    input clk, rst;

    // Data Nets
    wire zero;
    wire [word_size-1: 0] instruction, address, Bus_1, mem_word;


    // Control Nets
    wire Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC, Load_IR;
    wire Load_Add_R, Load_Reg_Y, Load_Reg_Z;
    wire write;

    Processing_Unit M0_Processor
        (instruction, zero, address, Bus_1, mem_word, Load_R0, Load_R1,
        Load_R2, Load_R3, Load_PC, Inc_PC, Sel_Bus_1_Mux, Load_IR,
        Load_Add_R, Load_Reg_Y, Load_Reg_Z, Sel_Bus_2_Mux, clk, rst);

    Control_Unit M1_Controller (Load_R0, Load_R1, Load_R2, Load_R3, Load_PC,
        Inc_PC, Sel_Bus_1_Mux, Sel_Bus_2_Mux , Load_IR, Load_Add_R,
        Load_Reg_Y, Load_Reg_Z, write, instruction, zero, clk, rst);

    Memory_Unit M2_SRAM (
        .data_out(mem_word),
        .data_in(Bus_1),
        .address(address),
        .clk(clk),
        .write(write) );
endmodule
```

# Processing unit of the RISC SPM

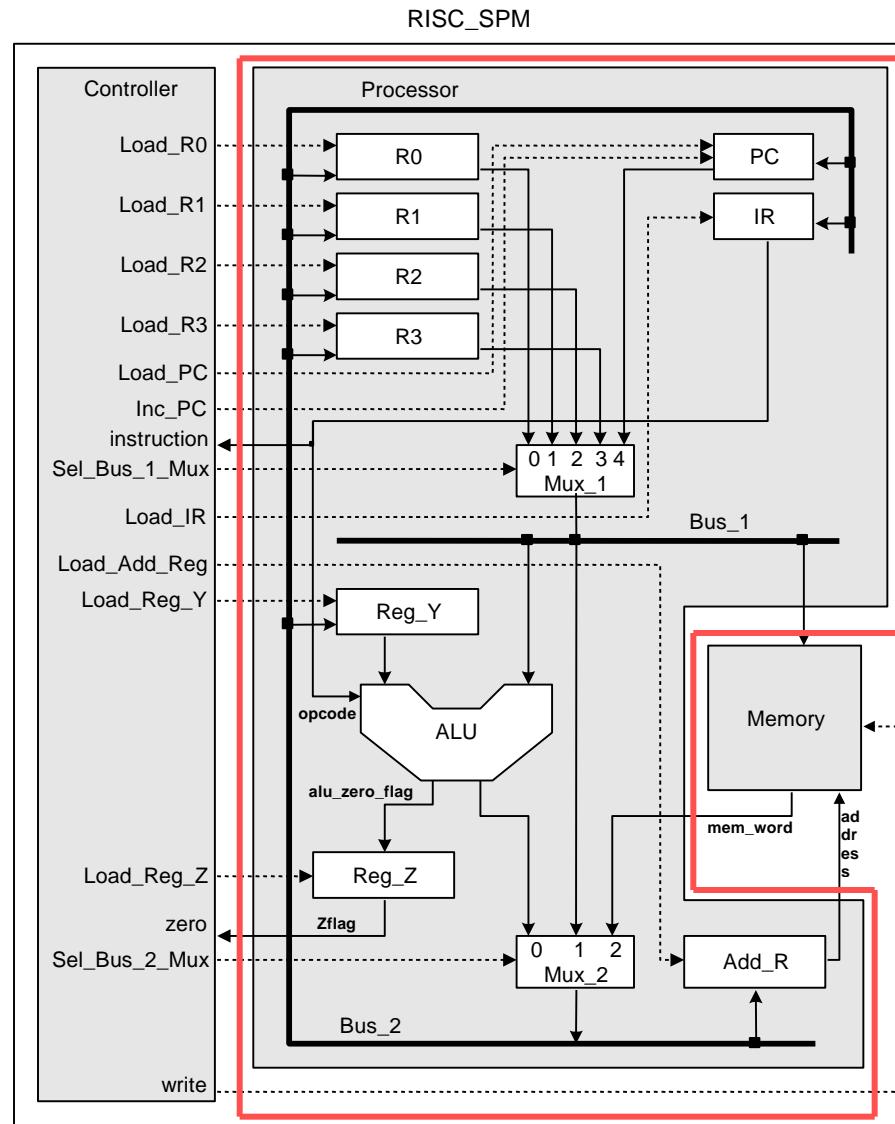

17 signals except  
rst and clk

# Processing Unit [1]

```
module Processing_Unit (instruction, Zflag, address, Bus_1, mem_word, Load_R0, Load_R1,
Load_R2, Load_R3, Load_PC, Inc_PC, Sel_Bus_1_Mux, Load_IR, Load_Add_R,
Load_Reg_Y, Load_Reg_Z, Sel_Bus_2_Mux, clk, rst);

parameter word_size = 8;
parameter op_size = 4;
parameter Sel1_size = 3;
parameter Sel2_size = 2;
output [word_size-1: 0] instruction, address, Bus_1;
output Zflag;
input [word_size-1: 0] mem_word;
input Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC;
input Sel_Bus_1_Mux;
input Sel_Bus_2_Mux;
input Load_IR, Load_Add_R, Load_Reg_Y, Load_Reg_Z;
input clk, rst;
```

## Processing Unit [2]

```
wire Load_R0, Load_R1, Load_R2, Load_R3;  
wire [word_size-1: 0] Bus_2;  
wire [word_size-1: 0] R0_out, R1_out, R2_out, R3_out;  
wire [word_size-1: 0] PC_count, Y_value, alu_out;  
wire alu_zero_flag;  
  
wire [op_size-1 : 0]  
opcode = instruction [word_size-1: word_size-op_size];  
  
Register_Unit    R0      (R0_out, Bus_2, Load_R0, clk, rst);  
Register_Unit    R1      (R1_out, Bus_2, Load_R1, clk, rst);  
Register_Unit    R2      (R2_out, Bus_2, Load_R2, clk, rst);  
Register_Unit    R3      (R3_out, Bus_2, Load_R3, clk, rst);  
Register_Unit    Reg_Y   (Y_value, Bus_2, Load_Reg_Y, clk, rst);
```

## Processing Unit [3]

```
D_flop           Reg_Z    (Zflag, alu_zero_flag, Load_Reg_Z, clk, rst);  
Address_Register Add_R    (address, Bus_2, Load_Add_R, clk, rst);  
Instruction_Register IR      (instruction, Bus_2, Load_IR, clk, rst);  
Program_Counter PC       (PC_count, Bus_2, Load_PC, Inc_PC, clk, rst);  
Multiplexer_5ch Mux_1    (Bus_1, R0_out, R1_out, R2_out, R3_out,  
                           PC_count, Sel_Bus_1_Mux);  
Multiplexer_3ch Mux_2    (Bus_2, alu_out, Bus_1, mem_word,  
                           Sel_Bus_2_Mux);  
Alu_RISC          ALU      (alu_zero_flag, alu_out, Y_value, Bus_1, opcode);  
endmodule
```

# Register unit, D\_flop, and address register

```
module Register_Unit (data_out, data_in, load, clk, rst);
    parameter word_size = 8;
    output [word_size-1: 0] data_out;
    input [word_size-1: 0] data_in;
    input load;
    input clk, rst;
    reg [word_size-1: 0] data_out;

    always @ (posedge clk or negedge rst)
        if (rst == 0) data_out <= 0; else if (load) data_out <= data_in;
endmodule

module D_flop (data_out, data_in, load, clk, rst);
    output data_out;
    input data_in;
    input load;
    input clk, rst;
    reg data_out;
```

## Register unit, D\_flop, and address register

```
always @ (posedge clk or negedge rst)
  if (rst == 0) data_out <= 0; else if (load == 1) data_out <= data_in;
endmodule

module Address_Register (data_out, data_in, load, clk, rst);
  parameter word_size = 8;
  output [word_size-1: 0] data_out;
  input  [word_size-1: 0] data_in;
  input                  load, clk, rst;
  reg      [word_size-1: 0] data_out;
  always @ (posedge clk or negedge rst)
    if (rst == 0) data_out <= 0; else if (load) data_out <= data_in;
endmodule
```

## Instruction register

```
module Instruction_Register (data_out, data_in, load, clk, rst);
parameter word_size = 8;
output [word_size-1: 0] data_out;
input [word_size-1: 0] data_in;
input load;
input clk, rst;
reg [word_size-1: 0] data_out;
always @ (posedge clk or negedge rst)
if (rst == 0) data_out <= 0; else if (load) data_out <= data_in;
endmodule
```

# Program Counter

```
module Program_Counter (count, data_in, Load_PC, Inc_PC, clk, rst);
    parameter word_size = 8;
    output [word_size-1: 0]      count;
    input   [word_size-1: 0]      data_in;
    input                      Load_PC, Inc_PC;
    input                      clk, rst;
    reg                         count;
    always @ (posedge clk or negedge rst)
        if (rst == 0) count <= 0;
        else if (Load_PC) count <= data_in;
        else if (Inc_PC) count <= count +1;
    endmodule
```

## 5-Input Multiplexor

```
module Multiplexer_5ch (mux_out, data_a, data_b, data_c, data_d, data_e, sel);
    parameter word_size = 8;
    output [word_size-1: 0]         mux_out;
    input   [word_size-1: 0]        data_a, data_b, data_c, data_d, data_e;
    input   [2: 0] sel;

    assign mux_out =  (sel == 0) ? data_a:
                      (sel == 1) ? data_b :
                      (sel == 2) ? data_c:
                      (sel == 3) ? data_d :
                      (sel == 4) ? data_e : 'bx;
endmodule
```


/\* Implementation for Multiplexer\_3ch is similar \*/

What would happen if we left out 'bx' ?

# ALU

```
module Alu_RISC (alu_zero_flag, alu_out, data_1, data_2, sel);
    parameter word_size = 8, op_size = 4;
    // Opcodes
    parameter NOP = 4'b0000, ADD = 4'b0001, SUB = 4'b0010, AND = 4'b0011,
        NOT = 4'b0100, RD = 4'b0101, WR = 4'b0110, BR = 4'b0111, BRZ = 4'b1000;
    output alu_zero_flag;
    output [word_size-1: 0] alu_out;
    input [word_size-1: 0] data_1, data_2;
    input [op_size-1: 0] sel;
    reg alu_out;
    assign alu_zero_flag = ~|alu_out;
    always @ (sel or data_1 or data_2)
        case (sel)
            NOP: alu_out = 0;
            ADD: alu_out = data_1 + data_2;
            SUB: alu_out = data_2 - data_1;
            AND: alu_out = data_1 & data_2;
            NOT: alu_out = ~ data_2;
            default: alu_out = 0;
        endcase
    endmodule
```

# Control unit of the RISC SPM

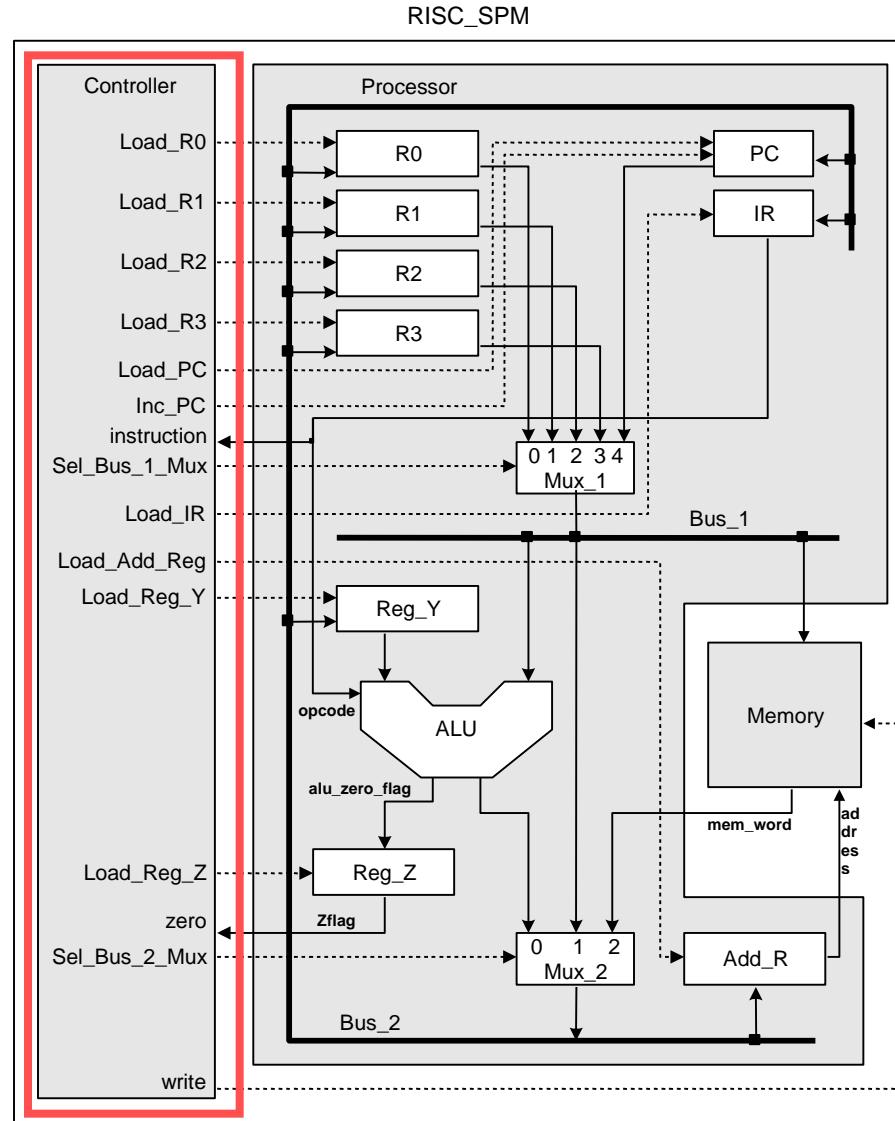

# Control Unit [1]

```
module Control_Unit (Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC,
    Sel_Bus_1_Mux, Sel_Bus_2_Mux, Load_IR, Load_Add_R, Load_Reg_Y, Load_Reg_Z,
    write, instruction, zero, clk, rst);

parameter word_size = 8, op_size = 4, state_size = 4;
parameter src_size = 2, dest_size = 2, Sel1_size = 3, Sel2_size = 2;
// State Codes
parameter S_idle = 0, S_fet1 = 1, S_fet2 = 2, S_dec = 3;
parameter S_ex1 = 4, S_rd1 = 5, S_rd2 = 6;
parameter S_wr1 = 7, S_wr2 = 8, S_br1 = 9, S_br2 = 10, S_halt = 11;
// Opcodes
parameter NOP = 0, ADD = 1, SUB = 2, AND = 3, NOT = 4;
parameter RD = 5, WR = 6, BR = 7, BRZ = 8;
// Source and Destination Register Codes
parameter R0 = 0, R1 = 1, R2 = 2, R3 = 3;
// See textbook for output, input, and reg declarations
```

## Control Unit [2]

```
output Load_R0, Load_R1, Load_R2, Load_R3;
output Load_PC, Inc_PC;
output [Sel1_size-1: 0] Sel_Bus_1_Mux;
output Load_IR, Load_Add_R;
output Load_Reg_Y, Load_Reg_Z;
output [Sel2_size-1: 0] Sel_Bus_2_Mux;
output write;
input [word_size-1: 0] instruction;
input zero;
input clk, rst;

reg [state_size-1: 0] state, next_state;
reg Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC;
reg Load_IR, Load_Add_R, Load_Reg_Y;
reg Sel_ALU, Sel_Bus_1, Sel_Mem;
reg Sel_R0, Sel_R1, Sel_R2, Sel_R3, Sel_PC;
reg Load_Reg_Z, write;
reg err_flag;

wire [op_size-1: 0] opcode = instruction [word_size-1: word_size - op_size];
wire [src_size-1: 0] src = instruction [src_size + dest_size -1: dest_size];
wire [dest_size-1: 0] dest = instruction [dest_size -1: 0];
```

## Control Unit [3]

```
// Mux selectors
assign Sel_Bus_1_Mux[Sel1_size-1: 0] = Sel_R0 ? 0:
                                              Sel_R1 ? 1:
                                              Sel_R2 ? 2:
                                              Sel_R3 ? 3:
                                              Sel_PC ? 4: 3'bx;

assign Sel_Bus_2_Mux[Sel2_size-1: 0] = Sel_ALU ? 0:
                                              Sel_Bus_1 ? 1:
                                              Sel_Mem ? 2: 2'bx;

always @ (posedge clk or negedge rst) begin: State_transitions
  if (rst == 0) state <= S_idle; else state <= next_state; end
always @ (state or opcode or src or dest or zero)
begin: Output_and_next_state
  // set default values for control signals
  Sel_R0 = 0; Sel_R1 = 0; Sel_R2 = 0; Sel_R3 = 0; Sel_PC = 0;
  Load_R0 = 0; Load_R1 = 0; Load_R2 = 0; Load_R3 = 0; Load_PC = 0;
  Load_IR = 0;      Load_Add_R = 0;      Load_Reg_Y = 0;      Load_Reg_Z = 0;
  Inc_PC = 0; Sel_Bus_1 = 0; Sel_ALU = 0; Sel_Mem = 0; write = 0;
  err_flag = 0;      // Used for de-bug in simulation
  next_state = state;
```

## Control Unit [4]

```
case (state)
    S_idle: next_state = S_fet1;
    S_fet1: begin next_state = S_fet2; Sel_PC = 1; Sel_Bus_1 = 1;
              Load_Add_R = 1; end // S_fet1
    S_fet2: begin next_state = S_dec; Sel_Mem = 1; Load_IR = 1;
              Inc_PC = 1; end // S_fet2
    S_dec: case (opcode)
        NOP: next_state = S_fet1;
        ADD, SUB, AND: begin next_state = S_ex1; Sel_Bus_1 = 1; Load_Reg_Y = 1;
                         case (src)
                             R0: Sel_R0 = 1;
                             R1: Sel_R1 = 1;
                             R2: Sel_R2 = 1;
                             R3: Sel_R3 = 1;
                         default : err_flag = 1;
                         endcase
                     end // ADD, SUB, AND
```

## Control Unit [5]

**NOT:** **begin** next\_state = S\_fet1; Load\_Reg\_Z = 1; Sel\_Bus\_1 = 1;  
Sel\_ALU = 1;

**case** (src)

R0: Sel\_R0 = 1;

R1: Sel\_R1 = 1;

R2: Sel\_R2 = 1;

R3: Sel\_R3 = 1;

**default** : err\_flag = 1;

**endcase**

**case** (dest)

R0: Load\_R0 = 1;

R1: Load\_R1 = 1;

R2: Load\_R2 = 1;

R3: Load\_R3 = 1;

**default**: err\_flag = 1;

**endcase**

**end** // NOT

## Control Unit [6]

```
RD: begin next_state = S_rd1; Sel_PC = 1; Sel_Bus_1 = 1;  
      Load_Add_R = 1; end // RD  
WR: begin next_state = S_wr1; Sel_PC = 1; Sel_Bus_1 = 1;  
      Load_Add_R = 1; end // WR  
BR: begin next_state = S_br1; Sel_PC = 1; Sel_Bus_1 = 1;  
      Load_Add_R = 1; end // BR  
BRZ: if (zero == 1) begin next_state = S_br1; Sel_PC = 1;  
      Sel_Bus_1 = 1; Load_Add_R = 1; end  
      else begin next_state = S_fet1; Inc PC = 1; end // BRZ  
      default : next_state = S_halt;  
endcase // (opcode)  
S_ex1: begin next_state = S_fet1; Load_Reg_Z = 1 Sel_ALU = 1;  
      case (dest)  
          R0: begin Sel_R0 = 1; Load_R0 = 1; end  
          R1: begin Sel_R1 = 1; Load_R1 = 1; end  
          R2: begin Sel_R2 = 1; Load_R2 = 1; end  
          R3: begin Sel_R3 = 1; Load_R3 = 1; end  
          default : err_flag = 1;  
      endcase  
end // S_ex1
```

## Control Unit [7]

```
S_rd1: begin next_state = S_rd2; Sel_Mem = 1; Load_Add_R = 1;  
           Inc_PC = 1; end // S_rd1  
S_wr1: begin next_state = S_wr2; Sel_Mem = 1; Load_Add_R = 1;  
           Inc_PC = 1; end // S_wr1  
S_rd2: begin next_state = S_fet1; Sel_Mem = 1;  
           case (dest) R0: Load_R0 = 1; R1: Load_R1 = 1; R2: Load_R2 = 1;  
                  R3: Load_R3 = 1; default : err_flag = 1; endcase end // S_rd2  
S_wr2: begin next_state = S_fet1; write = 1;  
           case (src) R0:      Sel_R0 = 1; R1: Sel_R1 = 1; R2: Sel_R2 = 1;  
                  R3: Sel_R3 = 1; default : err_flag = 1; endcase end // S_wr2  
S_br1: begin next_state = S_br2; Sel_Mem = 1; Load_Add_R = 1; end  
S_br2: begin next_state = S_fet1; Sel_Mem = 1; Load_PC = 1; end  
S_halt: next_state = S_halt;  
default: next_state = S_idle;  
endcase end //state case and always block  
endmodule
```

# Memory Unit

```
module Memory_Unit (data_out, data_in, address, clk, write);
    parameter word_size = 8;
    parameter memory_size = 256;
    output [word_size-1: 0] data_out;
    input [word_size-1: 0] data_in;
    input [word_size-1: 0] address;
    input clk, write;
    reg [word_size-1: 0] memory [memory_size-1: 0];
    assign data_out = memory[address];
    always @ (posedge clk)
        if (write) memory[address] = data_in;
endmodule
```

/\* How would a more realistic memory differ? \*/

## Questions on RISC SPM

- ❖ Why not include memory as part of the processing unit?
- ❖ How could the design be simplified?

## Testing RISC SPM

- ❖ Clear the memory
- ❖ Load the memory with a simple program and data
- ❖ Execute simple program
  - Reads values from memory into registers
  - Perform subtraction to decrement a loop counter
  - Add register contents while executing the loop
  - Branch to a halt when the loop index is 0
- ❖ Probe memory locations and control signals to ensure correct execution

# Testing RISC SPM Verilog [1]

```
module test_RISC_SPM ();
    reg rst;
    wire clk;
    parameter word_size = 8;
    reg [8: 0] k;
    Clock_Unit M1 (clk);
    RISC_SPM M2 (clk, rst);
    // define probes
    wire [word_size-1: 0] word0, word1, ..., word14;          // instructions
    wire [word_size-1: 0] word128, word129, ..., word140;      // data
    assign word0 = M2.M2_SRAM.memory[0];                      // words 1 to 13
    assign word14 = M2.M2_SRAM.memory[14];
    assign word128 = M2.M2_SRAM.memory[128];                 // words 129 to 139
    assign word140 = M2.M2_SRAM.memory[140];
```

## Testing RISC SPM Verilog [2]

```
initial #2800 $finish;           // set end point for simulation
initial begin: Flush_Memory
#2 rst = 0; for (k=0; k<=255; k=k+1) M2.M2_SRAM.memory[k] = 0; #10 rst = 1; end //
    Flush_Memory
initial begin: Load_program #5
                                // opcode_src_dest
M2.M2_SRAM.memory[0] = 8'b0000_00_00;      // NOP
M2.M2_SRAM.memory[1] = 8'b0101_00_10;      // Read Mem[130] to R2
M2.M2_SRAM.memory[2] = 130;                // R2 = 2
M2.M2_SRAM.memory[3] = 8'b0101_00_11;      // Read Mem[131] to R3
M2.M2_SRAM.memory[4] = 131;                // R3 = 0
M2.M2_SRAM.memory[5] = 8'b0101_00_01;      // Read Mem[128] to R1
M2.M2_SRAM.memory[6] = 128;                // R1 = 6
M2.M2_SRAM.memory[7] = 8'b0101_00_00;      // Read Mem[129] to R0
M2.M2_SRAM.memory[8] = 129;                // R0 = 1
```

## Testing RISC SPM Verilog [3]

```
M2.M2_SRAM.memory[9] = 8'b0010_00_01; // Sub R1-R0 to R1
M2.M2_SRAM.memory[10] = 8'b1000_00_00; // BRZ
M2.M2_SRAM.memory[11] = 134;           // Holds address for BRZ (139)
M2.M2_SRAM.memory[12] = 8'b0001_10_11; // Add R2+R3 to R3
M2.M2_SRAM.memory[13] = 8'b0111_00_11; // BR
M2.M2_SRAM.memory[14] = 140;           // Holds address for BR (9)
// Load data
M2.M2_SRAM.memory[128] = 6; M2.M2_SRAM.memory[129] = 1;
M2.M2_SRAM.memory[130] = 2; M2.M2_SRAM.memory[131] = 0;
M2.M2_SRAM.memory[134] = 139; M2.M2_SRAM.memory[135] = 0;
M2.M2_SRAM.memory[139] = 8'b1111_00_00; // HALT
M2.M2_SRAM.memory[140] = 9;           // Repeat Loop
end
endmodule
```