

2007 Fall: Electronic Circuits 2

## CHAPTER 12

# Filters and Tuned Amplifiers

Deog-Kyoon Jeong

[dkjeong@snu.ac.kr](mailto:dkjeong@snu.ac.kr)

School of Electrical Engineering  
Seoul National University

# Introduction

## ◆ Passive LC Filters

## ◆ Electronic Filter – Active Filter


- Active RC Filters
- Switched capacitor circuits

→ Advantages : **No inductors**

Inductors are large and physically bulky for low frequency applications

## 12.1.1 Filter Transmission

◆ Filter – a two port device

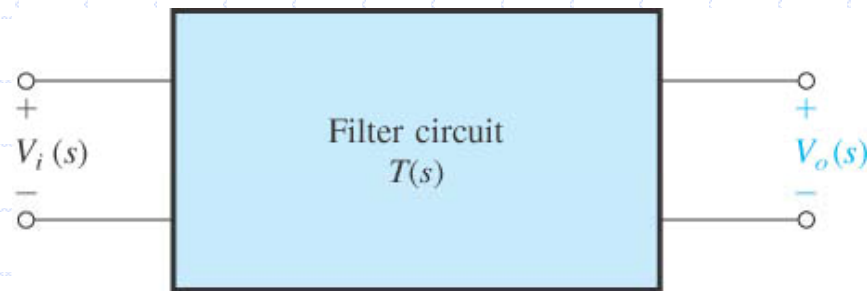


- Transfer function:  $T(s) \equiv \frac{V_o(s)}{V_i(s)}$
- The filter transmission:  $T(j\omega) = |T(j\omega)| e^{j\phi(\omega)}$  ( $s = j\omega$ )  
magnititude phase
- Gain function:  $G(\omega) \equiv 20 \log |T(j\omega)|$  dB
- Attenuation function:  $A(\omega) \equiv -20 \log |T(j\omega)|$  dB
- Input Output relation:  $|V_o(j\omega)| = |T(j\omega)| |V_i(j\omega)|$

# 12.1.2 Filter Types


## ◆ Frequency-selection Function

- Passing : Passband,  $|T|=1$
- Stopping : Stopband,  $|T|=0$


## ◆ Brick-Wall response

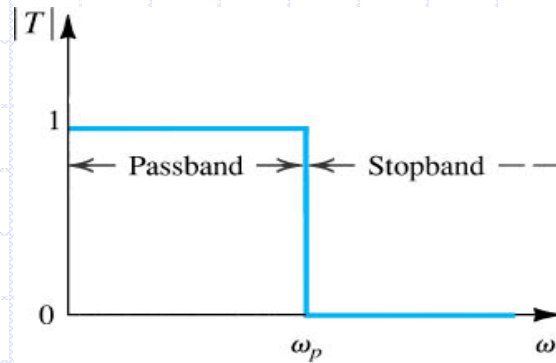


(a) Low-pass (LP)

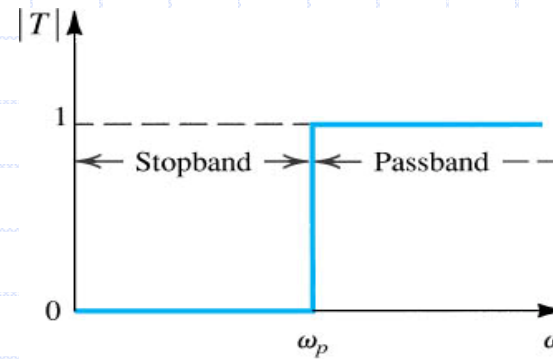

(b) High-pass (HP)

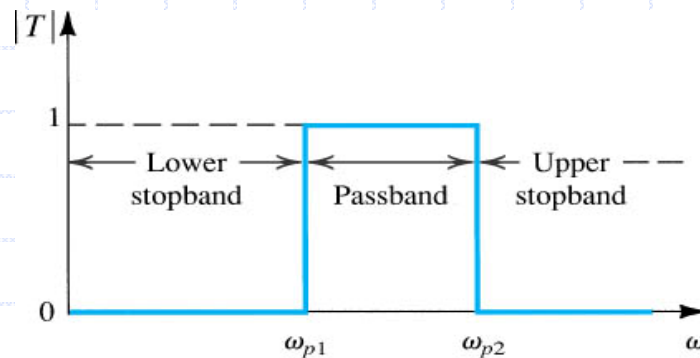

(c) Bandpass (BP)

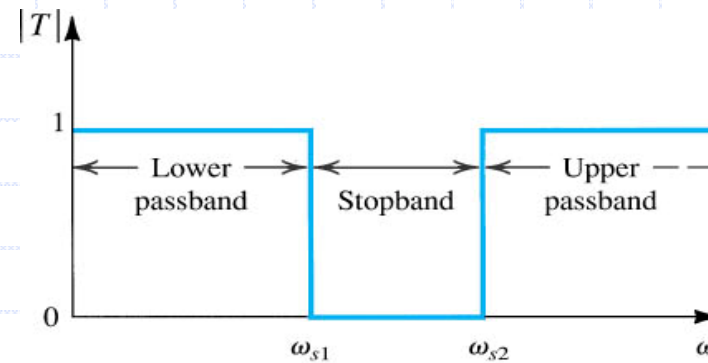


(d) Bandstop (BS)
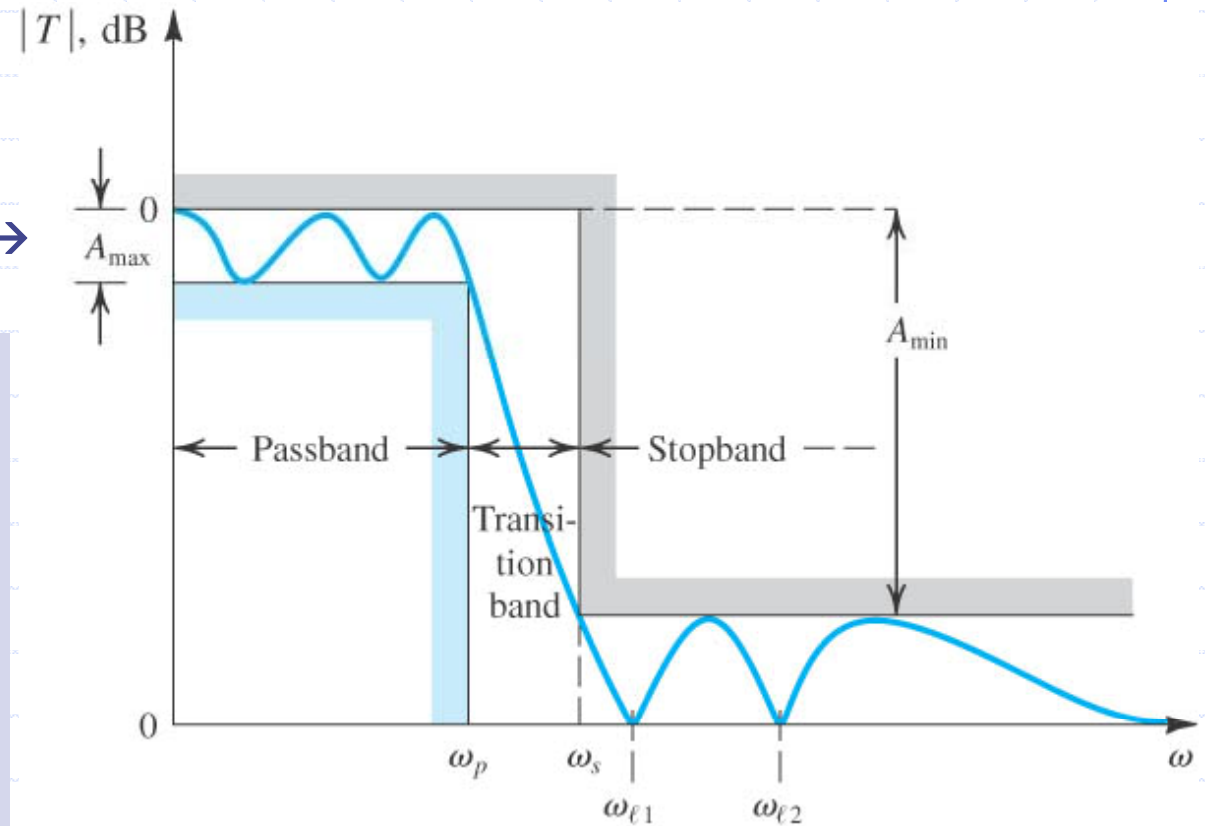
## 12.1.3 Filter Specification

Passband Ripple →  
range: 0.05 dB ~ 3 dB


- $\omega_p$  : Passband edge
- $A_{\max}$  : Maximum allowed variation in passband transmission
- $\omega_s$  : Stopband edge
- $A_{\min}$  : Minimum required stopband attenuation
- $\omega_s/\omega_p$  : Selectivity factor



## 12.1.3 Filter Specification
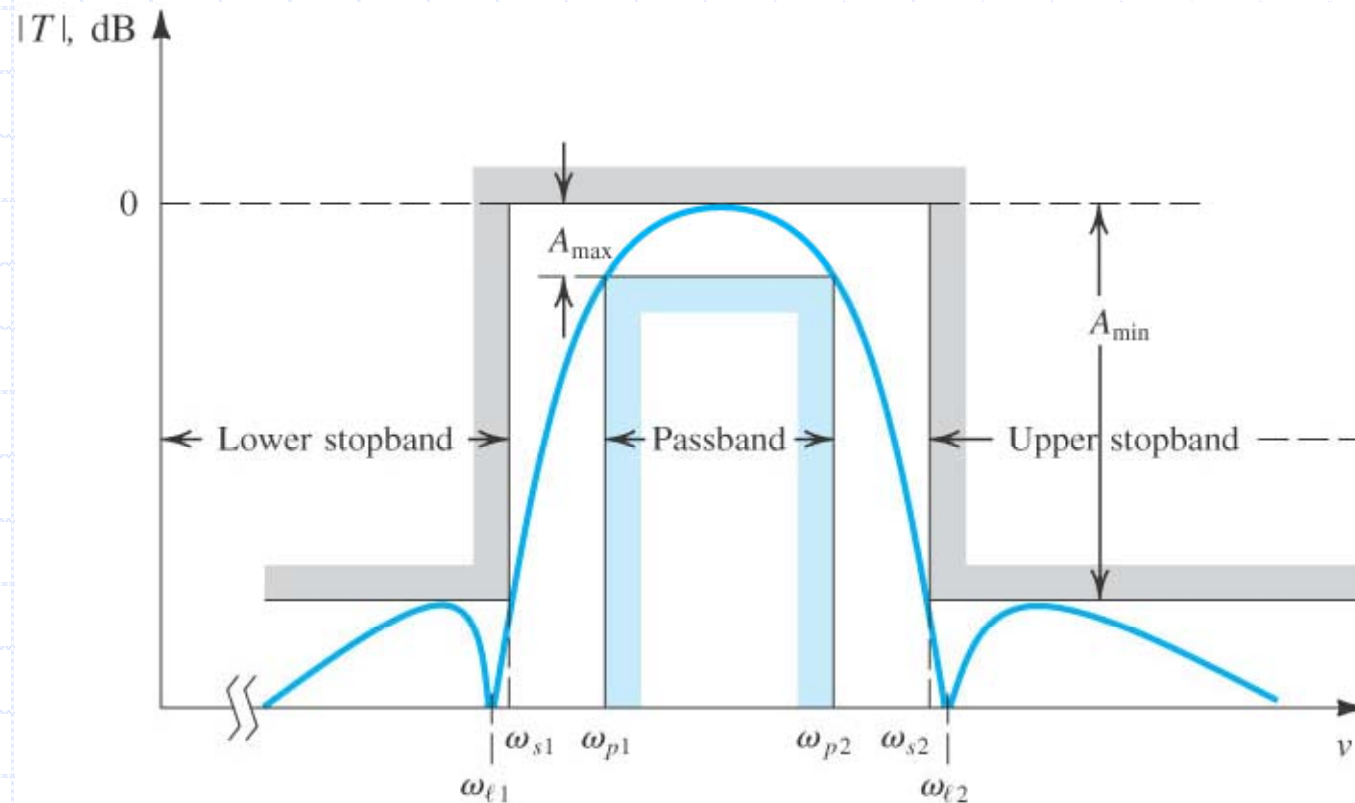
### ◆ Filter Approximation

- The process of obtaining a transfer function that meets given specifications
- Performed using computer programs(Snelgrove, 1982;Ouslis and Sedra, 1995), filter design table(Zverev, 1967) or closed-form expressions(Section 12.3)



## 12.2 The Filter Transfer Function

### ◆ Filter Transfer Function $T(s)$

- $$T(s) = \frac{a_M s^M + a_{M-1} s^{M-1} + \cdots + a_0}{s^N + b_{N-1} s^{N-1} + \cdots + b_0}$$

- N: filter order
- if  $N \geq M$ , stable
- $a_0, \dots, a_M$  &  $b_0, \dots, b_{N-1}$ : real numbers

- $$T(s) = \frac{a_M (s - z_1)(s - z_2) \cdots (s - z_M)}{(s - p_1)(s - p_2) \cdots (s - p_N)}$$

- $z_1, \dots, z_M$ : transfer function zeros = transmission zeros
- $p_1, \dots, p_N$ : transfer function poles = natural modes
- real or complex number (conjugate pair)



## 12.2 The Filter Transfer Function

### ◆ Filter Transfer Function $T(s)$

- Since in the stopband the transmission is zero or small
  - the zeros are usually, placed on the  $j\omega$  axis at stopband frequencies

- Infinite attenuation at  $\omega_{l1}$  and  $\omega_{l2}$ 
  - zeros at  $s = +j\omega_{l1}$  &  $+j\omega_{l2}$   
also at  $s = -j\omega_{l1}$  &  $-j\omega_{l2}$

Numerator polynomial

$$(s + j\omega_{l1})(s - j\omega_{l1})(s + j\omega_{l2})(s - j\omega_{l2}) \\ = (s^2 + \omega_{l1}^2)(s^2 + \omega_{l2}^2)$$


→ for  $s = j\omega$ ,

$$(s^2 + \omega_{l1}^2)(s^2 + \omega_{l2}^2) \\ = (-\omega^2 + \omega_{l1}^2)(-\omega^2 + \omega_{l2}^2)$$

which is zero at  $\omega = \omega_{l1}$  and  $\omega = \omega_{l2}$

- zeros at  $s = \infty$   
the numbers of zeros at  $s = \infty = N - M$
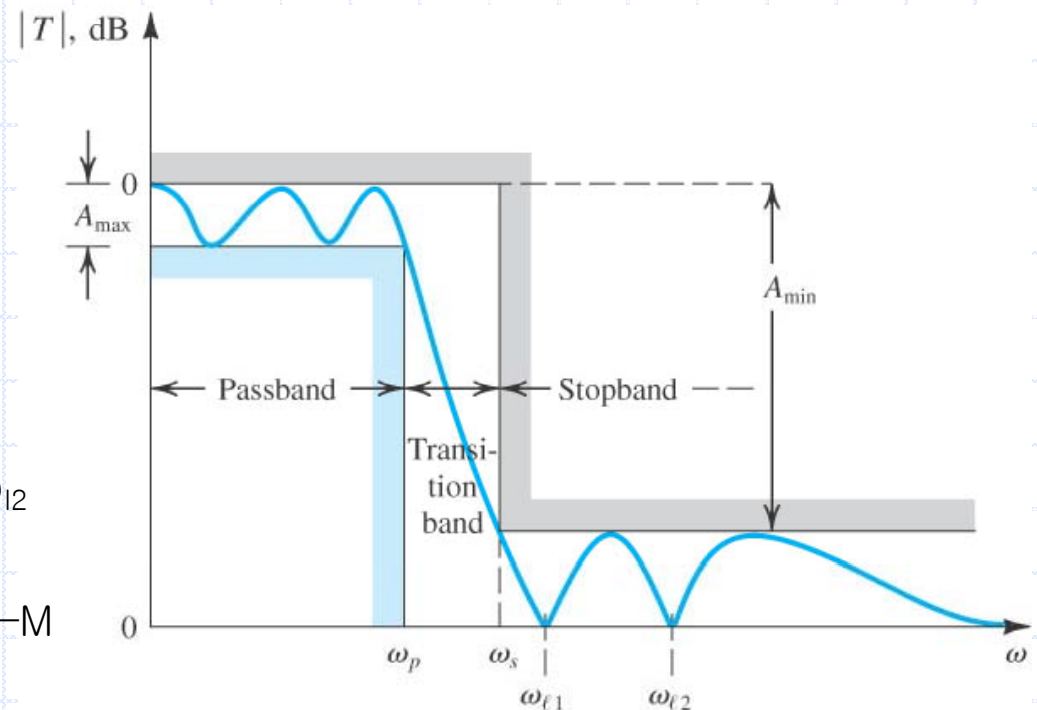
$$\therefore \text{as } s \rightarrow \infty, \quad T(s) \rightarrow \frac{a_M}{s^{N-M}}$$






## 12.2 The Filter Transfer Function

### ◆ Pole-zero pattern for a 5<sup>th</sup>-order LPF (N=5)

- Two pairs of complex-conjugate poles and real-axis pole  
→ all the poles lie in the vicinity of passband  
→ high transmission at passband frequencies

- $s = \pm j\omega_{l1} \ \& \ \pm j\omega_{l2} \ \& \ \infty$

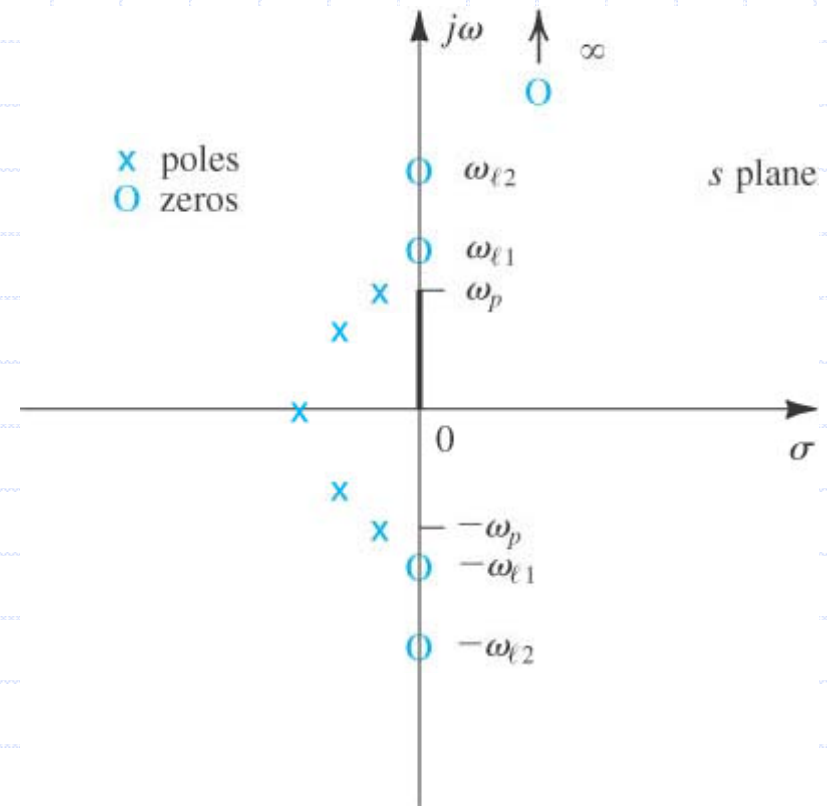- $$T(s) = \frac{a_4(s^2 + \omega_{l1}^2)(s^2 + \omega_{l2}^2)}{s^5 + b_4s^4 + b_3s^3 + b_2s^2 + b_1s + b_0}$$





# 12.2 The Filter Transfer Function

- It has one or more zeros at  $s = 0$  and one or more zeros at  $s = \infty$
- Assuming that only one zero exists at  $s = 0$  &  $s = \infty$


■  $N=6$

■  $s = \pm j\omega_{l1}, s = \pm j\omega_{l2}, s = 0, s = \infty$

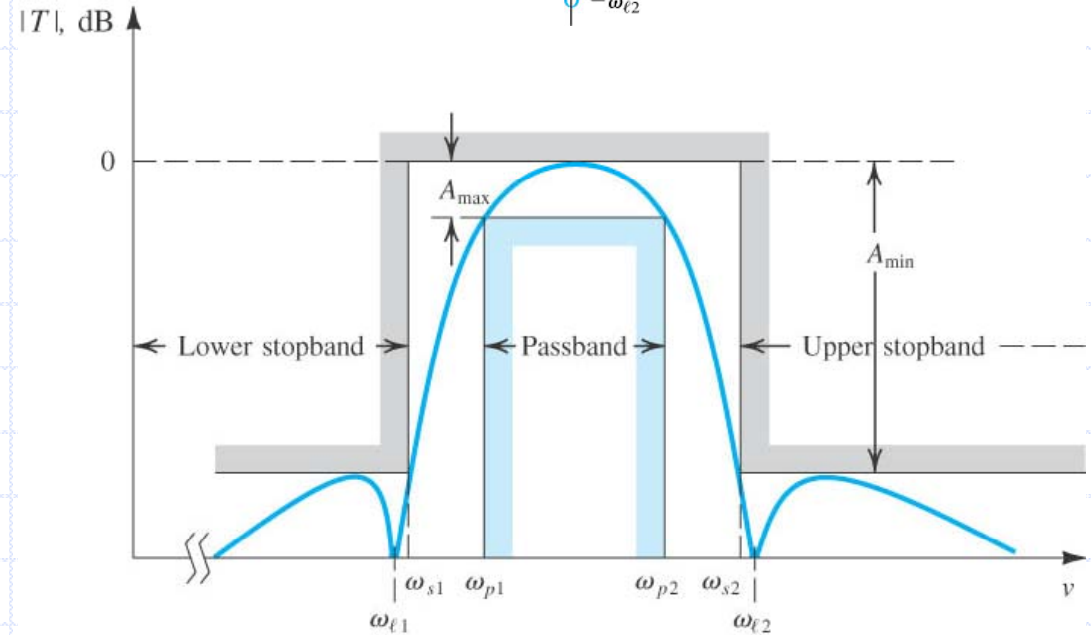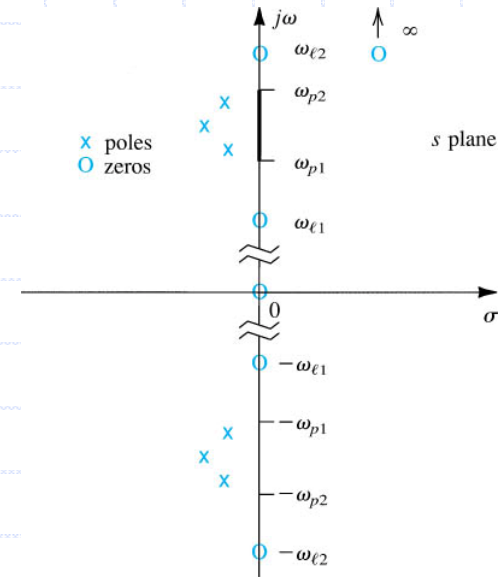■ 
$$T(s) = \frac{a_5 s (s^2 + \omega_{l1}^2)(s^2 + \omega_{l2}^2)}{s^6 + b_5 s^5 + \dots + b_0}$$



## 12.2 The Filter Transfer Function

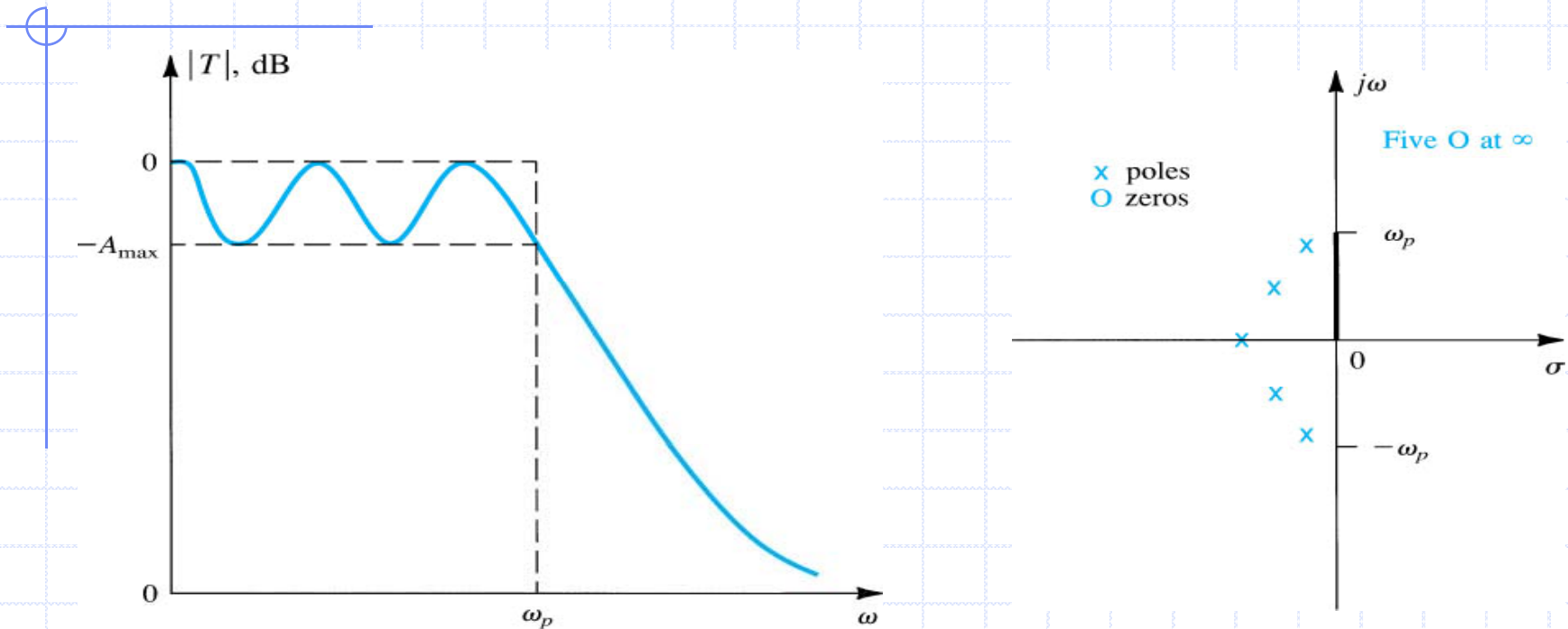

- It is possible that all zeros are at  $s = \infty$
- The more selective the required filter response is, the higher its order must be, and the closer its natural modes are to the  $j\omega$  axis

## 12.2 The Filter Transfer Functions

### ◆ Problem 12.9

A third-order low-pass filter has transmission zeros at  $\omega=2\text{rad/s}$  and  $\omega=\infty$ . Its natural modes are at  $s=-1$  and  $s=-0.5\pm j0.8$ . The dc gain is unity. Find  $T(s)$

- Poles at  $-1$  and  $-0.5\pm j0.8$  : denominator  $D(s)=(s+1)(s^2+s+0.89)$
- Zeros at  $\infty$  and  $\pm j2$  : numerator  $N(s)=k(s+j2)(s-j2)=k(s^2+4)$
- There is one zero at  $\infty$  because  $\text{Degree}(D(s)) - \text{Degree}(N(s)) = 1$ . Thus,

$$T(s) = \frac{k(s^2 + 4)}{(s + 1)(s^2 + s + 0.89)}$$

- DC gain = 1 :  $T(j0) = 4k/0.89 = 1 \rightarrow k = 0.2225$
- $T(s)$  is,

$$T(s) = \frac{0.2225(s^2 + 4)}{(s + 1)(s^2 + s + 0.89)}$$


## 12.3 Butterworth and Chebyshev Filters

◆ In this section, we present two functions that are frequently used in **approximating the transmission characteristics** of low-pass filters.

: Closed-form expressions

## 12.3.1 The Butterworth Filter

### ◆ Filter Transfer Function $T(s)$

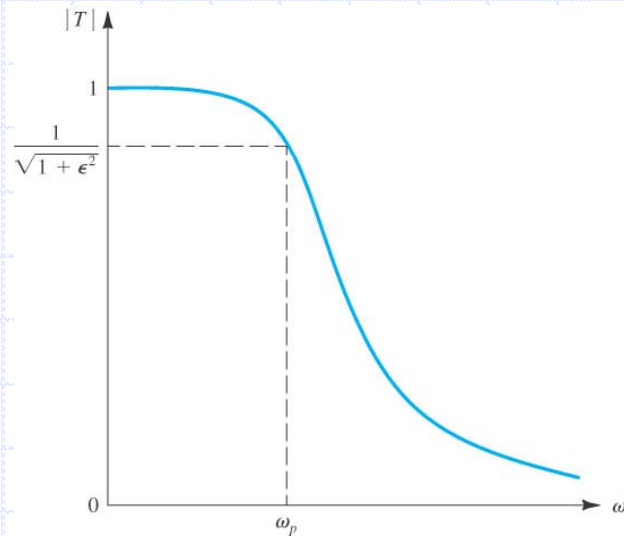

- Monotonically decreasing transmission
- All the transmission zero at  $\omega = \infty$
- The magnitude function for an  $N^{\text{th}}$ -order Butterworth filter with a passband edge  $\omega_p$  is

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 \left(\frac{\omega}{\omega_p}\right)^{2N}}}$$

at  $\omega = \omega_p$ ,

$$|T(j\omega_p)| = \frac{1}{\sqrt{1 + \epsilon^2}}$$

- Thus, the parameter  $\epsilon$  determines the maximum variation in passband transmission,


$$A_{\max} = 20 \log \sqrt{1 + \epsilon^2}$$

- Conversely, given  $A_{\max}$ ,

$$\epsilon = \sqrt{10^{A_{\max}/10} - 1}$$

## 12.3.1 The Butterworth Filter
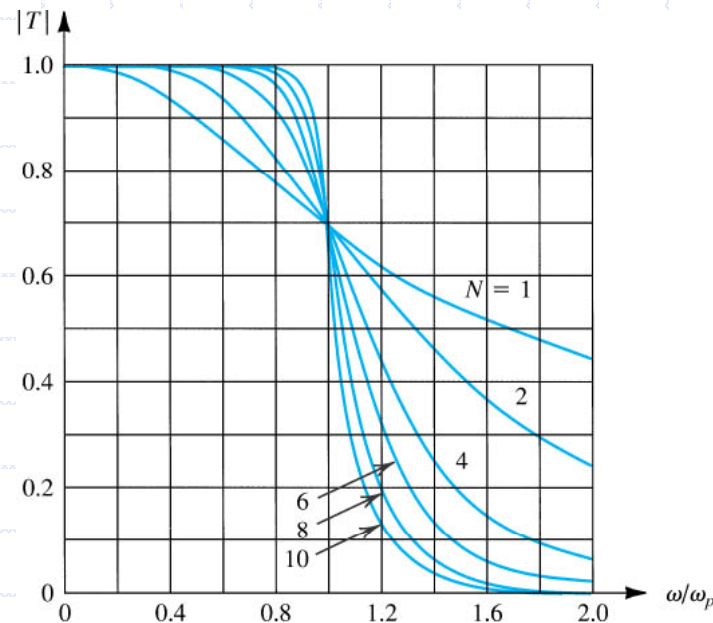
### ◆ Filter Transfer Function $T(s)$ (cont.)




- In the Butterworth response the maximum deviation in passband transmission occurs at the passband edge,  $\omega_p$ , only
- The first  $2N-1$  derivatives of  $|T|$  relative to  $\omega$  are zero at  $\omega = 0$   
→ very flat near  $\omega = 0$  (maximally flat response)
- The degree of passband flatness increases as the order  $N$  is increased  
→ as the order  $N$  is increased the filter response approaches the ideal brick-wall type of response
- The edge of the stopband,  $\omega = \omega_s$ , attenuation is
$$A(\omega_s) = -20 \log \left[ \frac{1}{\sqrt{1 + \varepsilon^2 (\omega_s / \omega_p)^{2N}}} \right] = 10 \log \left[ 1 + \varepsilon^2 (\omega_s / \omega_p)^{2N} \right]$$
- This equation can be used to determine the filter order required, which is the lowest integer value of  $N$  that yields  $A(\omega_s) \geq A_{\min}$



## 12.3.1 The Butterworth Filter
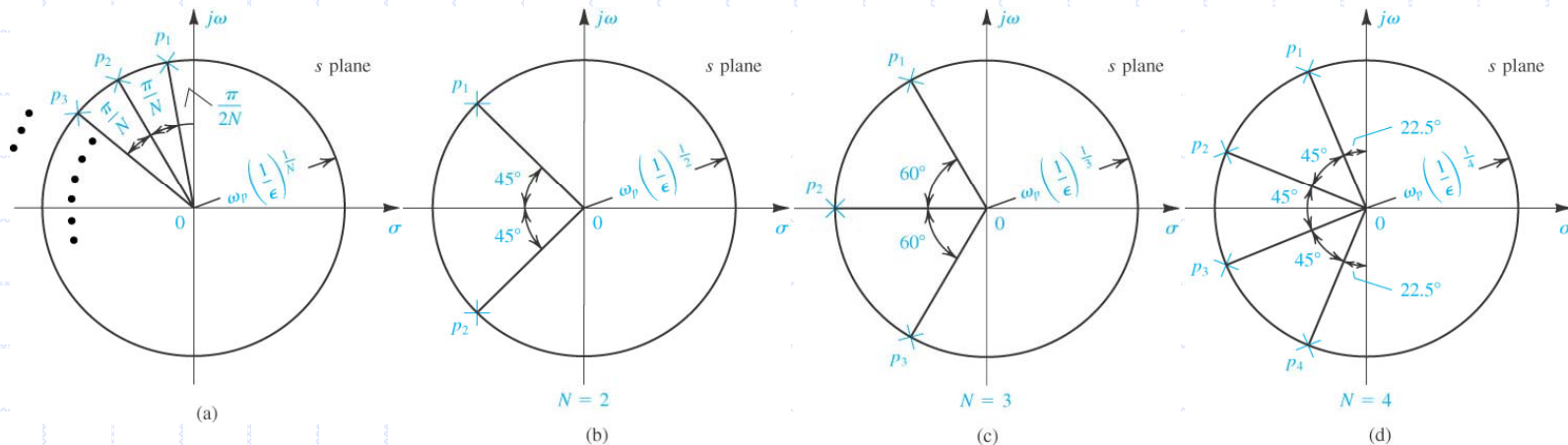
### Filter Transfer Function $T(s)$ (cont.)



- The natural modes of an  $N^{\text{th}}$ -order Butterworth filter can be determined from the graphical construction above.
- Natural modes lies on a circle of radius  $\omega_p(1/\epsilon)^{1/N}$   
 → **same frequency of  $\omega_0 = \omega_p(1/\epsilon)^{1/N}$**
- Space by equal angles of  $\pi/N$ , with the first mode at an angle  $\pi/2N$  from the  $+jw$  axis.
- Transfer function is

$$T(s) = \frac{K\omega_0^N}{(s-p_1)(s-p_2)\cdots(s-p_N)} \rightarrow K \text{ is a constant dc gain of the filter}$$

## 12.3.1 The Butterworth Filter

### ◆ How to find a Butterworth transfer function


- Determine  $\varepsilon$ .

$$\varepsilon = \sqrt{10^{A_{\max}/10} - 1}$$

- Determine the required filter order as the lowest integer value of  $N$  that results in  $A(\omega_S) \geq A_{\min}$ .

$$A(\omega_S) = -20 \log \left[ 1 / \sqrt{1 + \varepsilon^2 (\omega_S / \omega_P)^{2N}} \right] = 10 \log \left[ 1 + \varepsilon^2 (\omega_S / \omega_P)^{2N} \right]$$

- Determine the  $N$  natural modes

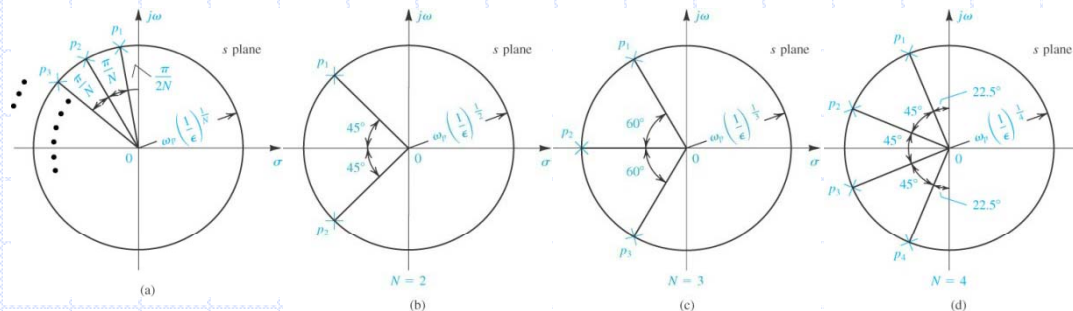

- Determine  $T(s)$

$$T(s) = \frac{K \omega_0^N}{(s - p_1)(s - p_2) \cdots (s - p_N)}$$

## 12.3.1 The Butterworth Filter

### Example 12.1

Find the Butterworth transfer function that meets the following low-pass filter specifications:  $f_p=10\text{kHz}$ ,  $A_{\max}=1\text{dB}$ ,  $f_s=15\text{kHz}$ ,  $A_{\min}=25\text{dB}$ , dc gain=1


- $\epsilon = \sqrt{10^{A_{\max}/10} - 1} = 0.5088$
- $A(\omega_s) = 10 \log[1 + \epsilon^2 (\omega_s/\omega_p)^{2N}]$   
 $= 22.3\text{dB}$  (when  $N=8$ )  
 $= 25.3\text{dB}$  (when  $N=9$ )

$$\omega_0 = \omega_p (1/\epsilon)^{1/N} = 6.773 \times 10^4 \text{ rad/s}$$

$$p_1 = \omega_0 (-\cos 80^\circ + j \sin 80^\circ) = \omega_0 (-0.1736 + j0.9848)$$



Combining  $\omega_0, \omega_9 \rightarrow s^2 + s0.3472\omega_0 + \omega_0^2$
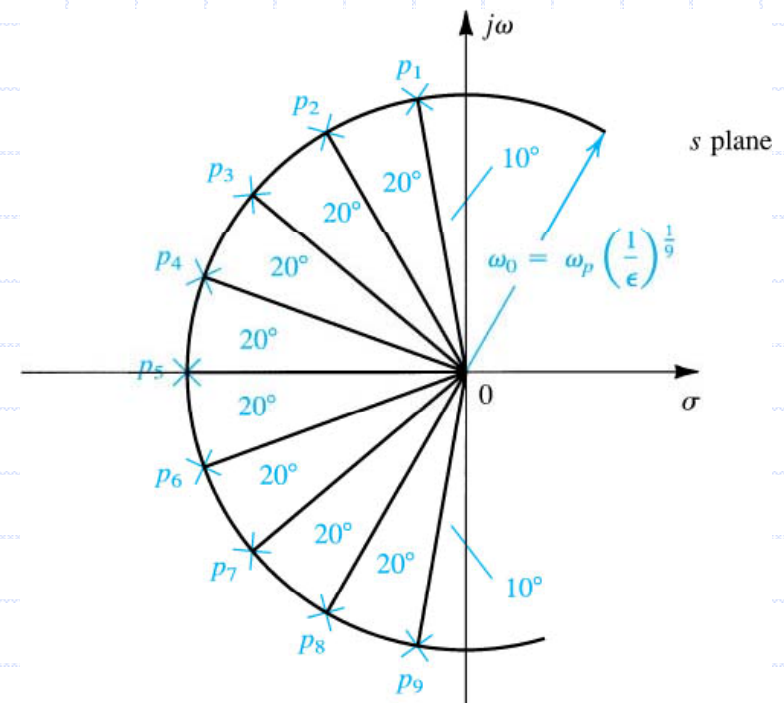
$$T(s) = \frac{K \omega_0^9}{(s + \omega_0)(s^2 + s1.8792\omega_0 + \omega_0^2)(s^2 + s1.5321\omega_0 + \omega_0^2)(s^2 + s\omega_0 + \omega_0^2)(s^2 + s0.3472\omega_0 + \omega_0^2)}$$



## 12.3.2 The Chebyshev Filter


### ◆ The Chebyshev Filter

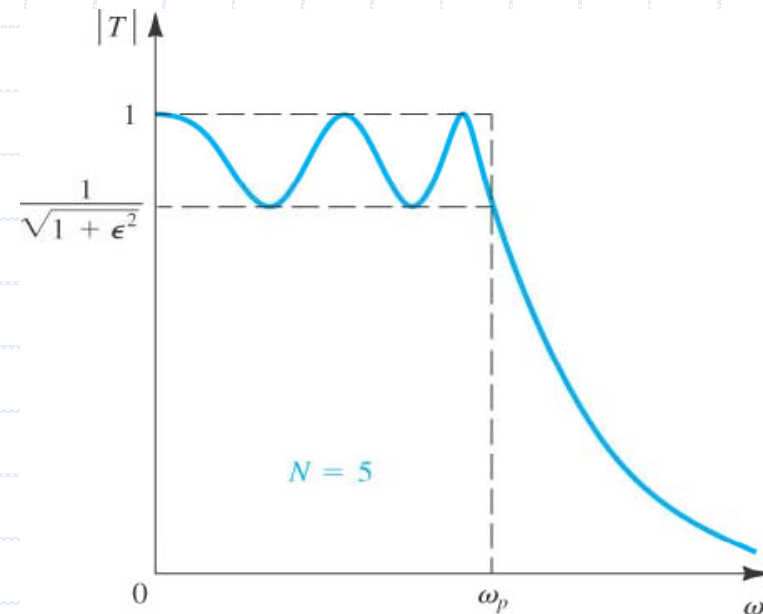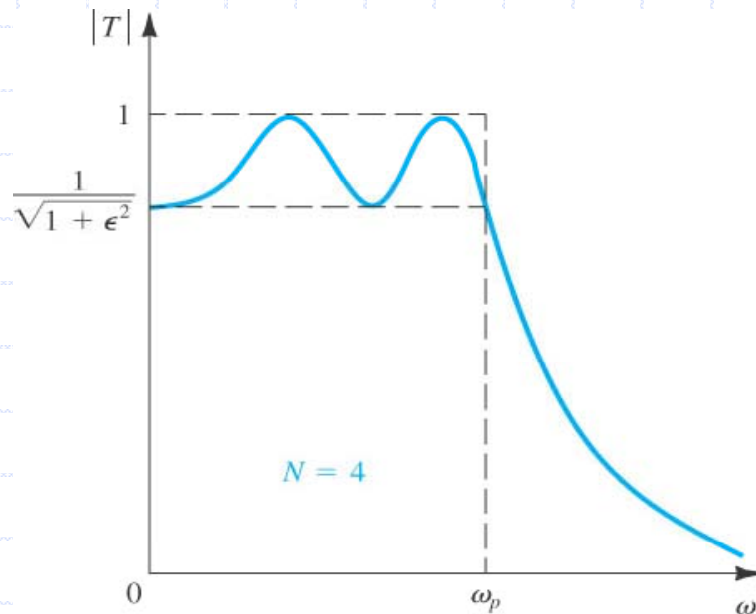

- **Equiripple response** ( $A_{\max}$  = the peak ripple) in the passband and a monotonically decreasing transmission in the stopband.
- The odd-order filter,  $|T(0)|=1$   
The even-order filter exhibits its maximum magnitude deviation at  $w = 0$ .
- Total number of passband maxima and minima equals the order of the filter,  $N$ .
- All the zeros are at  $w = \infty$ .

## 12.3.2 The Chebyshev Filter

### ◆ The Chebyshev Filter (cont.)

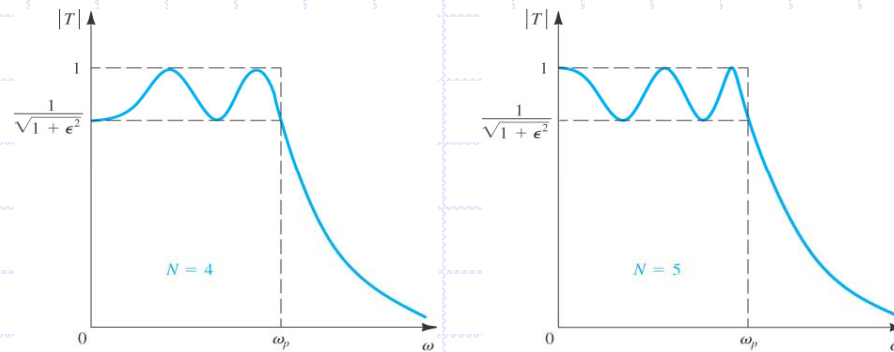

- The magnitude of the transfer function with a passband edge  $\omega_p$  is

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \varepsilon^2 \cos^2[N \cos^{-1}(\omega/\omega_p)]}} \quad \text{for } \omega \leq \omega_p$$

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \varepsilon^2 \cosh^2[N \cosh^{-1}(\omega/\omega_p)]}} \quad \text{for } \omega \geq \omega_p$$

$$|T(j\omega_p)| = \frac{1}{\sqrt{1 + \varepsilon^2}} \quad \text{for } \omega = \omega_p$$

- Thus, the parameter  $\varepsilon$  determines the passband ripple according to


$$A_{\max} = 10 \log(1 + \varepsilon^2)$$

conversely,

$$\varepsilon = \sqrt{10^{A_{\max}/10} - 1}$$

## 12.3.2 The Chebyshev Filter

### ◆ The Chebyshev Filter (cont.)

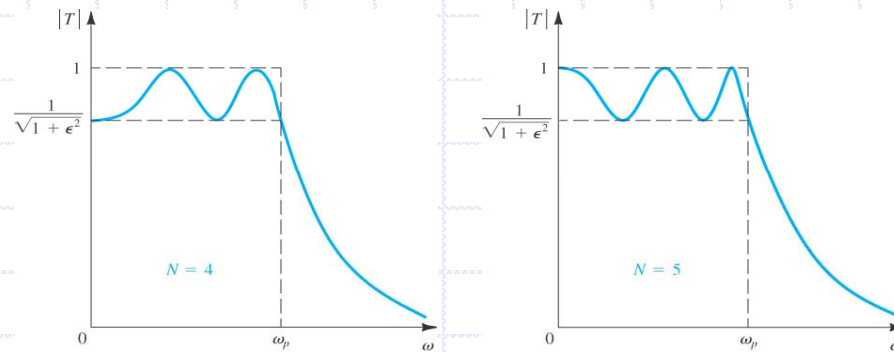

- The attenuation at the stopband edge ( $\omega = \omega_s$ ) is

$$A(\omega_s) = 10 \log[1 + \epsilon^2 \cosh^2(N \cosh^{-1}(\omega_s/\omega_p))]$$


→ this equation can be used to determine the order  $N$  required to obtain a specified  $A_{\min}$  by finding the lowest integer value of  $N$  that yields  $A(\omega_s) \geq A_{\min}$ .

- Increasing the order  $N$  of the Chebyshev filter causes its magnitude function to approach the ideal brick-wall low-pass response.



## 12.3.2 The Chebyshev Filter

### ◆ The Chebyshev Filter (cont.)

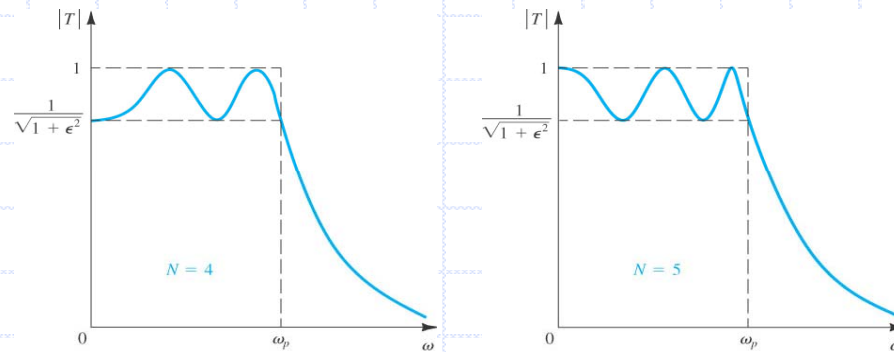

- The poles are

$$p_k = -\omega_p \sin\left(\frac{2k-1}{N} \frac{\pi}{2}\right) \sinh\left(\frac{1}{N} \sinh^{-1} \frac{1}{\epsilon}\right) + j\omega_p \cos\left(\frac{2k-1}{N} \frac{\pi}{2}\right) \cosh\left(\frac{1}{N} \sinh^{-1} \frac{1}{\epsilon}\right) \quad k = 1, 2, \dots, N$$

- The transfer function is

$$T(s) = \frac{K\omega_p^N}{\epsilon 2^{N-1} (s-p_1)(s-p_2)\cdots(s-p_N)}$$



## 12.3.2 The Chebyshev Filter

### ◆ How to find the transfer function

1. Determine  $\varepsilon$

$$\varepsilon = \sqrt{10^{A_{\max}/10} - 1}$$

2. Determine the order required,  $A(\omega_S)$

$$A(\omega_S) = 10 \log[1 + \varepsilon^2 \cosh^2(N \cosh^{-1}(\omega_S/\omega_P))]$$

3. Determine the poles,  $p_k$

$$p_k = -\omega_P \sin\left(\frac{2k-1}{N} \frac{\pi}{2}\right) \sinh\left(\frac{1}{N} \sinh^{-1} \frac{1}{\varepsilon}\right) + j\omega_P \cos\left(\frac{2k-1}{N} \frac{\pi}{2}\right) \cosh\left(\frac{1}{N} \sinh^{-1} \frac{1}{\varepsilon}\right) \quad k = 1, 2, \dots, N$$

4. Determine the transfer function,  $T(s)$

$$T(s) = \frac{K\omega_P^N}{\varepsilon 2^{N-1} (s-p_1)(s-p_2)\cdots(s-p_N)}$$

## 12.3.2 The Chebyshev Filter

### Example 12.2

Find the Chebyshev transfer function that meets the following low-pass filter specifications:  $f_p=10\text{kHz}$ ,  $A_{\max}=1\text{dB}$ ,  $f_s=15\text{kHz}$ ,  $A_{\min}=25\text{dB}$ , dc gain=1

- $\varepsilon = \sqrt{10^{A_{\max}/10} - 1} = 0.5088$
- $A(\omega_s) = 10 \log[1 + \varepsilon^2 \cosh^2(N \cosh^{-1}(\omega_s/\omega_p))]$   
= 21.6dB (when N=4)  
= 29.9dB (when N=5)
- $p_k = -\omega_p \sin\left(\frac{2k-1}{N} \frac{\pi}{2}\right) \sinh\left(\frac{1}{N} \sinh^{-1} \frac{1}{\varepsilon}\right) + j\omega_p \cos\left(\frac{2k-1}{N} \frac{\pi}{2}\right) \cosh\left(\frac{1}{N} \sinh^{-1} \frac{1}{\varepsilon}\right) \quad k=1,2,\dots,N$   
 $p_1, p_5 = \omega_p(-0.0895 \pm j0.9901)$ ,  $p_2, p_4 = \omega_p(-0.2342 \pm j0.6119)$ ,  $p_3 = \omega_p(-j0.2895)$

$$T(s) = \frac{\omega_p^5}{8.1408(s + 0.2895\omega_p)(s^2 + s0.4684\omega_p + 0.4293\omega_p^2)(s^2 + s0.1789\omega_p + 0.9883\omega_p^2)}$$

## 12.4 First-Order and Second-Order Filter Functions

- ◆ Study the simplest filter transfer functions
  - first and second order
- ◆ Cascade design
  - realize a high-order filter.  
→ design of active filters (utilizing op amps and RC circuits)
- ◆ Filter poles occur in complex-conjugate pairs
  - a high-order transfer function  $T(s)$  is factored into the product of second-order functions.
- ◆ If  $T(s)$  is odd there will also be a first-order function in the factorization.
- ◆ Overall transfer function of the cascade
  - simply the product of the transfer functions of the individual blocks.

## 12.4 First-Order and Second-Order Filter Functions

### ◆ General First-Order Transfer Function

$$T(s) = \frac{a_1 s + a_0}{s + \omega_0} \rightarrow \text{bilinear transfer function}$$

- A natural mode at  $s = -\omega_0$
- A transmission zero at  $s = -a_0/a_1$
- High frequency gain  $\rightarrow a_1$
- The numerator coefficients,  $a_0$  and  $a_1$ , determine the type of filter (e.g., low pass, high pass, etc.)
- Active circuit  
Low output impedance  
Limits the high-frequency operation ( $\rightarrow$  op amp)

# 12.4 First-Order and Second-Order Filter Functions

## ◆ First-Order Filters

Filter Type and $T(s)$	s-Plane Singularities	Bode Plot for $ T $	Passive Realization	Op Amp-RC Realization
<p>(a) Low pass (LP)</p> $T(s) = \frac{a_0}{s + \omega_0}$			<p><math>CR = \frac{1}{\omega_0}</math> DC gain = 1</p>	<p><math>CR_2 = \frac{1}{\omega_0}</math> DC gain = <math>-\frac{R_2}{R_1}</math></p>
<p>(b) High pass (HP)</p> $T(s) = \frac{a_1 s}{s + \omega_0}$			<p><math>CR = \frac{1}{\omega_0}</math> High-frequency gain = 1</p>	<p><math>CR_1 = \frac{1}{\omega_0}</math> High-frequency gain = <math>-\frac{R_2}{R_1}</math></p>
<p>(c) General</p> $T(s) = \frac{a_1 s + a_0}{s + \omega_0}$			<p><math>(C_1 + C_2)(R_1 // R_2) = \frac{1}{\omega_0}</math> <math>C_1 R_1 = \frac{a_1}{a_0}</math> DC gain = <math>\frac{R_2}{R_1 + R_2}</math> HF gain = <math>\frac{C_1}{C_1 + C_2}</math></p>	<p><math>C_2 R_2 = \frac{1}{\omega_0}</math> <math>C_1 R_1 = \frac{a_1}{a_0}</math> DC gain = <math>-\frac{R_2}{R_1}</math> HF gain = <math>-\frac{C_1}{C_2}</math></p>

# 12.4 First-Order and Second-Order Filter Functions

## ◆ First-Order Filters (cont.)

$T(s)$	Singularities	$ T $ and $\phi$	Passive Realization	Op Amp-RC Realization
<p>All pass (AP)</p> $T(s) = -a_1 \frac{s - \omega_0}{s + \omega_0}$ <p><math>a_1 &gt; 0</math></p>			<p><math>CR = 1/\omega_0</math> Flat gain (<math>a_1</math>) = 0.5</p>	<p><math>CR = 1/\omega_0</math> Flat gain (<math>a_1</math>) = 1</p>

- Although the transmission is constant, its phase shows frequency selectivity
- All-pass filters are used as phase shifters and in systems that require phase shaping

## 12.4 First-Order and Second-Order Filter Functions

### ◆ Second-Order Filter Functions

- The general second order (or biquadratic) filter transfer function

$$T(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + (\omega_0 / Q)s + \omega_0^2}$$

- $\omega_0$  and  $Q$  determine the natural modes (poles) according to

$$p_1, p_2 = -\frac{\omega_0}{2Q} \pm j\omega_0 \sqrt{1 - (1/4Q^2)}$$


- $Q > 0.5$  : complex-conjugate natural modes.



## 12.4 First-Order and Second-Order Filter Functions

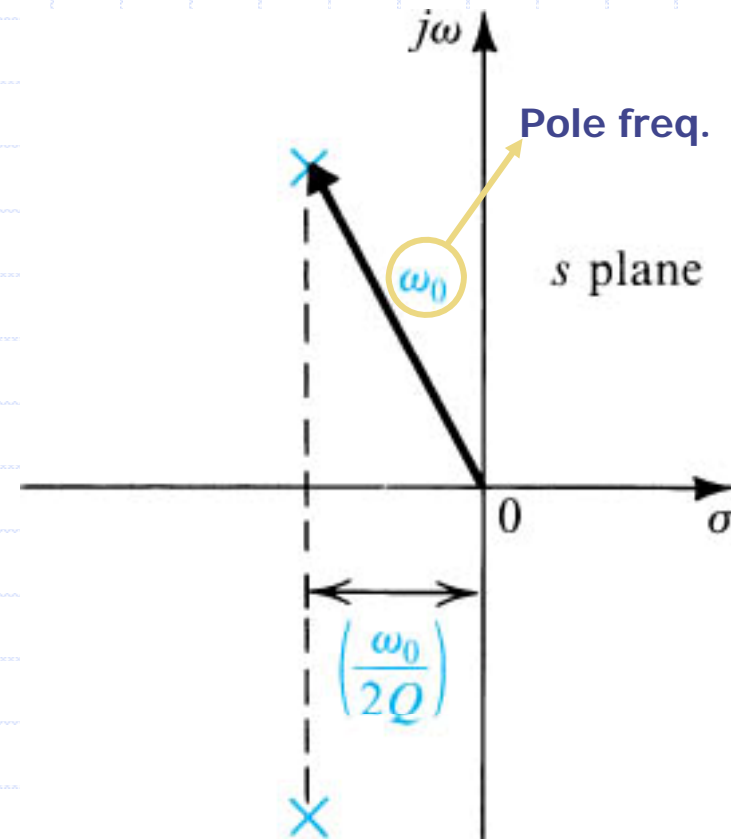
### ◆ Second-Order Filter Functions (cont.)

- $Q$  determines the distance of the poles from the  $j\omega$  axis  
: the higher the value of  $Q$ , the closer the poles are to the  $j\omega$  axis  
→ more selective
- $Q < 0$  → poles are in the RHP  
→ oscillation
- $Q = \text{pole quality factor} = \text{pole } Q$



# 12.4 First-Order and Second-Order Filter Functions

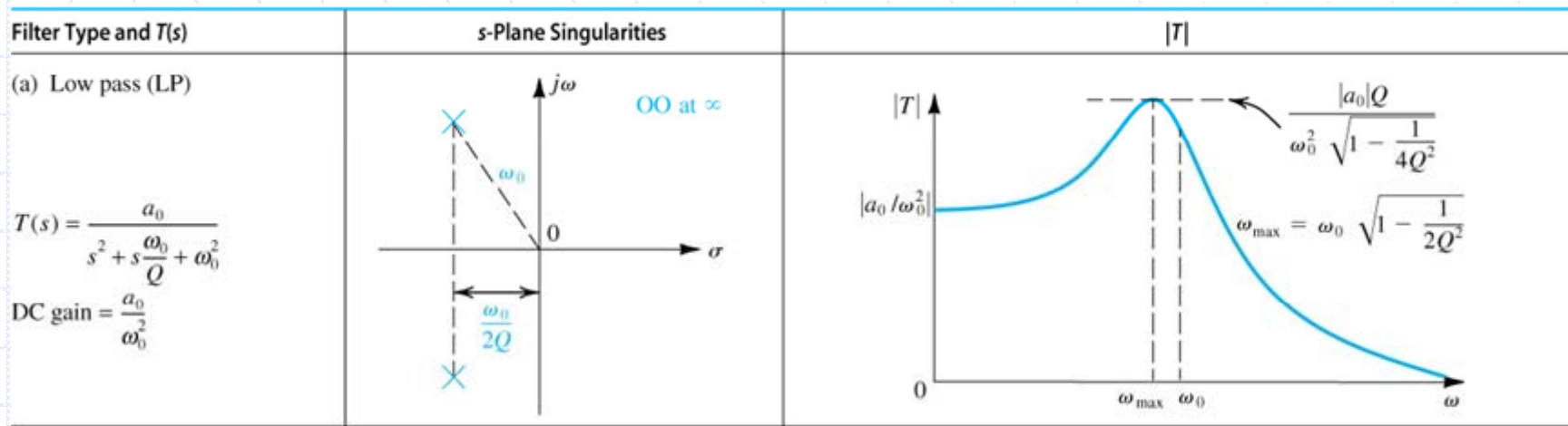
## ◆ Second-Order Filter Functions – LP case



- Lowpass Filter : The peak occurs only for  $Q > \frac{1}{\sqrt{2}}$   
 $Q = \frac{1}{\sqrt{2}} \rightarrow$  Butterworth, or maximally flat

# 12.4 First-Order and Second-Order Filter Functions
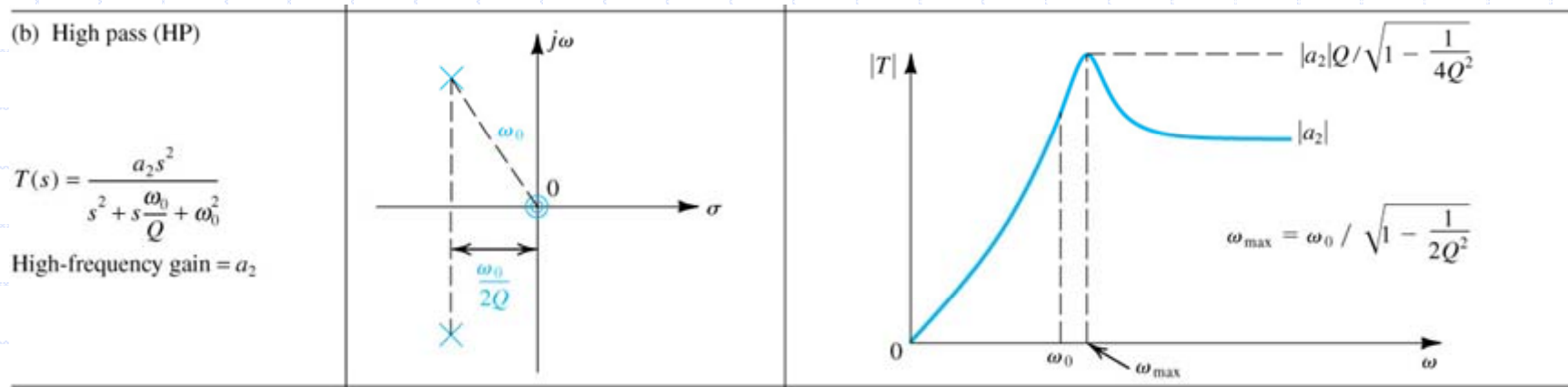
## ◆ Second-Order Filter Functions – HP case



- Highpass Filter : Transmission zeros at  $s=0$

Peak for  $Q > \frac{1}{\sqrt{2}}$



# 12.4 First-Order and Second-Order Filter Functions

## ◆ Second-Order Filter Functions – BP case

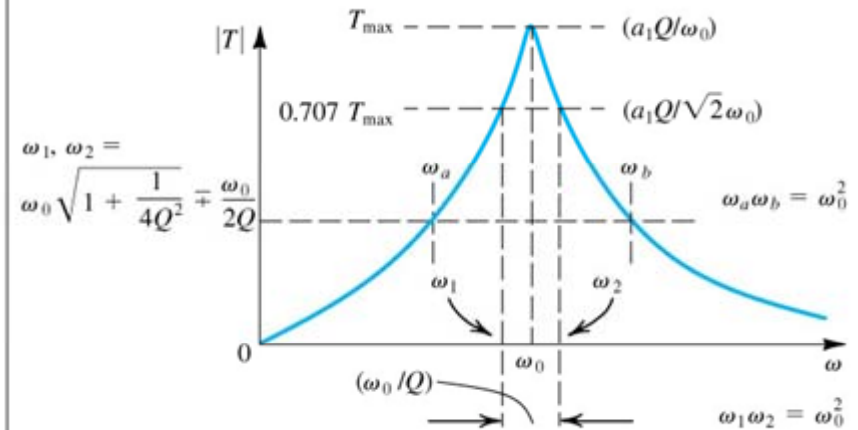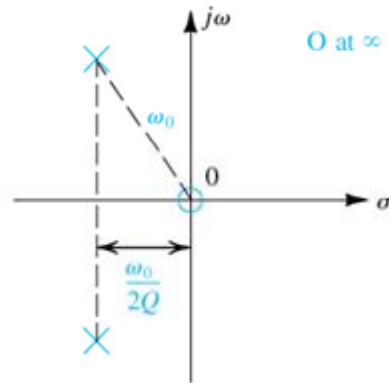(c) Bandpass (BP)

$$T(s) = \frac{a_1 s}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\text{Center-frequency gain} = \frac{a_1 Q}{\omega_0}$$



- Bandpass Filter : Transmission zeros at  $s=0$  and  $s=\infty$   
Magnitude response peaks at  $\omega = \omega_0 = \text{center frequency}$

$$\text{3dB: } \omega_1, \omega_2 = \omega_0 \sqrt{1 + \frac{1}{4Q^2}} \pm \frac{\omega_0}{2Q}$$

$$\text{BW} = \omega_2 - \omega_1 = \frac{\omega_0}{Q} : \text{as } Q \uparrow, \text{ BW } \downarrow \text{ (more selective)}$$

# 12.4 First-Order and Second-Order Filter Functions

## ◆ Second-Order Filter Functions – Notch case

Filter Type and $T(s)$	s-Plane Singularities	$ T $
(d) Notch  $T(s) = a_2 \frac{s^2 + \omega_0^2}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$ DC gain = High-frequency gain = $a_2$		

- Notch Filter : Transmission zeros are located on the  $j\omega$  axis, at the complex-conjugate locations  $\pm j\omega_n$ , then the magnitude response exhibits zero transmission at  $\omega = \omega_n$ .

(notch in the magnitude response occurs at  $\omega = \omega_n$ , notch frequency)

# 12.4 First-Order and Second-Order Filter Functions

## ◆ Second-Order Filter Functions – LPN, HPN



(e) Low-pass notch (LPN)

$$T(s) = a_2 \frac{s^2 + \omega_n^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\omega_n \geq \omega_0$$

DC gain =  $a_2 \frac{\omega_n^2}{\omega_0^2}$

High-frequency gain =  $a_2$

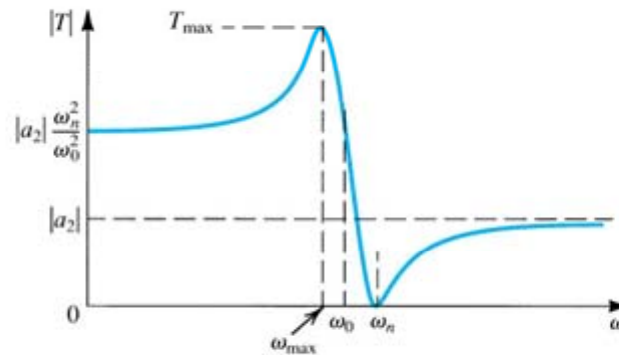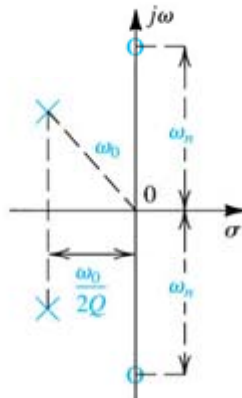

$$\omega_{\max} = \omega_0 \sqrt{\frac{\left(\frac{\omega_n^2}{\omega_0^2}\right) \left(1 - \frac{1}{2Q^2}\right) - 1}{\frac{\omega_n^2}{\omega_0^2} + \frac{1}{2Q^2} - 1}}$$



(f) High-pass notch (HPN)

$$T(s) = a_2 \frac{s^2 + \omega_n^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\omega_n \leq \omega_0$$

DC gain =  $a_2 \frac{\omega_n^2}{\omega_0^2}$

High-frequency gain =  $a_2$

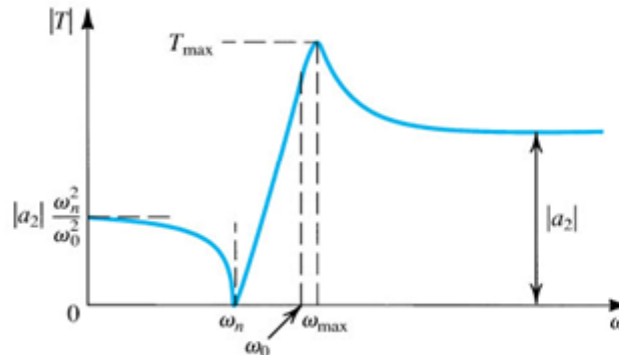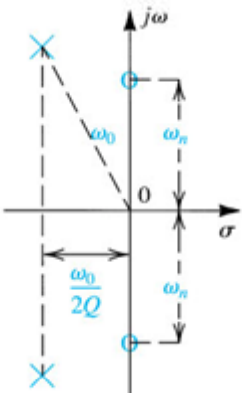

$$T_{\max} = \frac{|a_2| |\omega_n^2 - \omega_{\max}^2|}{\sqrt{(\omega_0^2 - \omega_{\max}^2)^2 + \left(\frac{\omega_0}{Q}\right)^2 \omega_{\max}^2}}$$




# 12.4 First-Order and Second-Order Filter Functions

## ◆ Second-Order Filter Functions – All-pass case

(g) All pass (AP)

$$T(s) = a_2 \frac{s^2 - s\frac{\omega_0}{Q} + \omega_0^2}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$$

Flat gain =  $a_2$

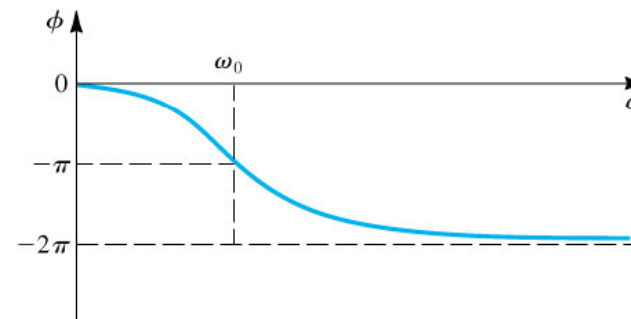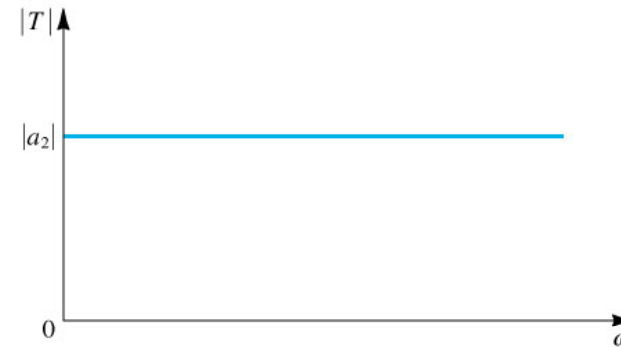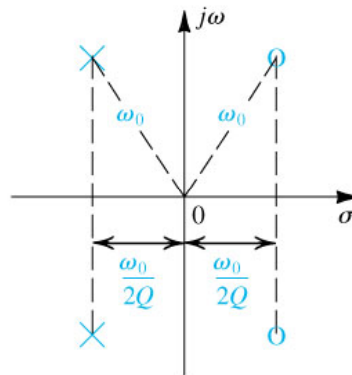

- Allpass Filter : Two transmission zeros are in the right half of the s plane, at the mirror image locations of the poles



# 12.4 First-Order and Second-Order Filter Functions

## Problem 12.19

Use the information displayed in below figure to design a first-order op amp-RC low-pass filter having a 3-dB frequency of 10 kHz, a dc gain magnitude of 10, and an input resistance of 10kΩ

Filter Type and $T(s)$	s-Plane Singularities	Bode Plot for $ T $	Passive Realization	Op Amp-RC Realization
(a) Low pass (LP)  $T(s) = \frac{a_0}{s + \omega_0}$			$CR = \frac{1}{\omega_0}$ $\text{DC gain} = 1$	$CR_2 = \frac{1}{\omega_0}$ $\text{DC gain} = -\frac{R_2}{R_1}$

# 12.4 First-Order and Second-Order Filter Functions

## Problem 12.19 (cont.)


Filter Type and $T(s)$	$s$ -Plane Singularities	Bode Plot for $ T $	Passive Realization	Op Amp-RC Realization
(a) Low pass (LP)  $T(s) = \frac{a_0}{s + \omega_0}$			<p> <math>CR = \frac{1}{\omega_0}</math>            DC gain = 1         </p>	<p> <math>CR_2 = \frac{1}{\omega_0}</math>            DC gain = <math>-\frac{R_2}{R_1}</math> </p>

- $R_{in} = R_1 = 10\text{k}\Omega$
- DC gain =  $-R_2/R_1 = -10$   
 $\rightarrow R_2 = 10R_1 = 100\text{k}\Omega$
- $R_2C = 1/\omega_0$   
 $\rightarrow C = 1/\omega_0 R_2 = 0.159\text{nF}$

# 12.4 First-Order and Second-Order Filter Functions
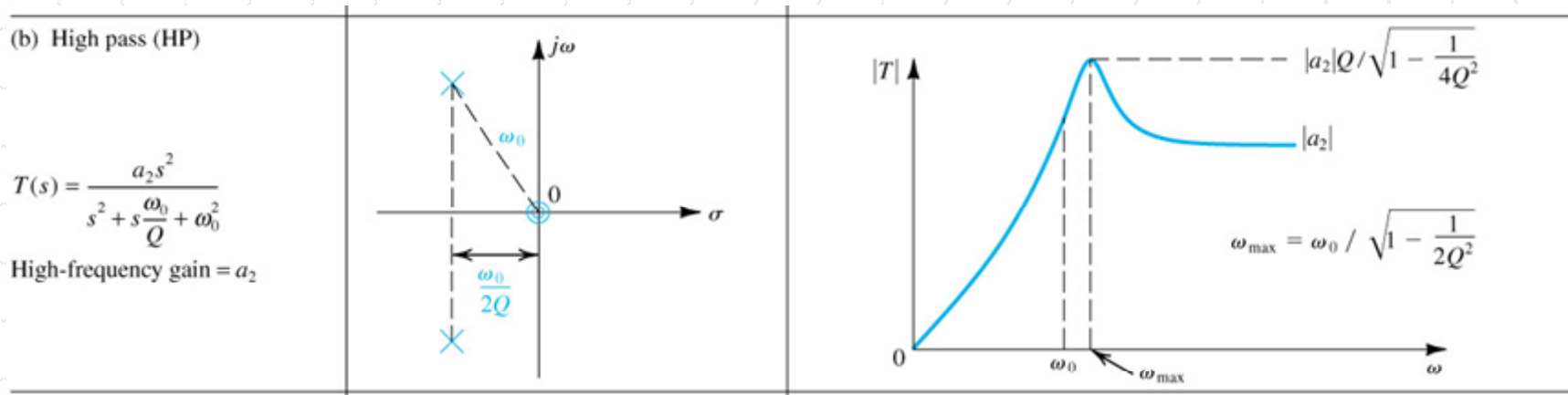
## Problem 12.28

Use the information given in below figure to find the transfer function of a second-order high-pass filter with natural modes at  $-0.5 \pm j\sqrt{3}/2$  and a high frequency gain of unity.





# 12.4 First-Order and Second-Order Filter Functions

## Problem 12.28 (cont.)

(b) High pass (HP)

$$T(s) = \frac{a_2 s^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

High-frequency gain =  $a_2$

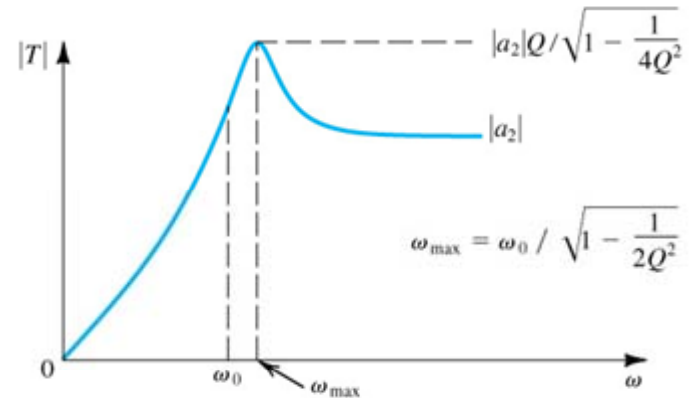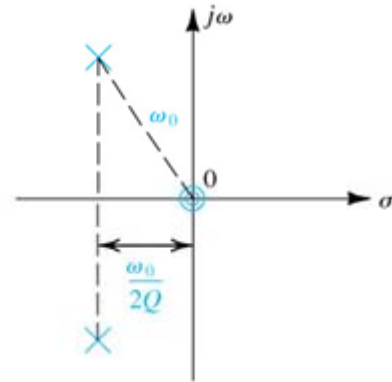

- $\omega_0 = \sqrt{(1/2)^2 - (\sqrt{3}/2)^2} = 1, \quad \omega_0 / 2Q = 1/2$


$$\rightarrow T(s) = \frac{a_2 s^2}{(s^2 + s \omega_0 / Q + \omega_0^2)} = \frac{a_2 s^2}{(s^2 + s + 1)}$$

- $|T(j\infty)| = a_2 = 1. \text{ Thus,}$


$$T(s) = \frac{s^2}{(s^2 + s + 1)}$$

## 12.5 The Second-Order LCR Resonator


### ◆ The Resonator Natural Modes

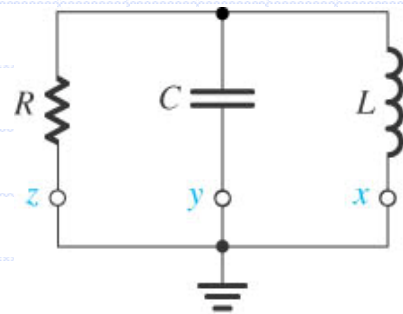

(a)

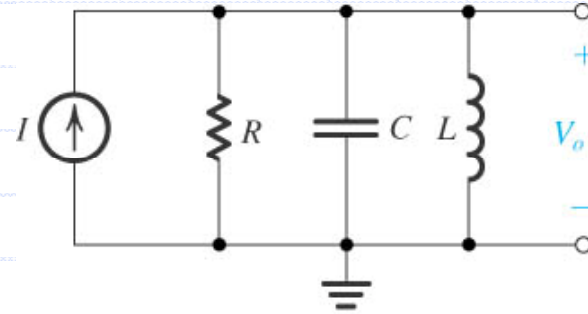

(b)

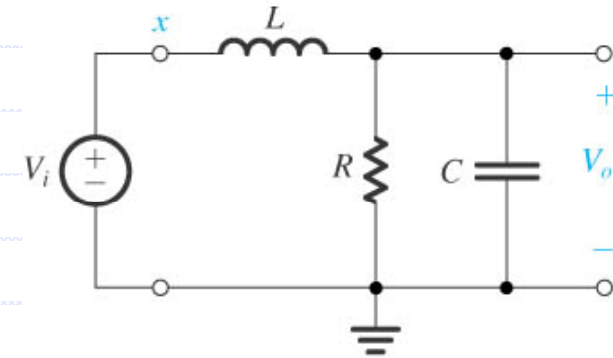

(c)

- The natural modes can be determined by applying an excitation that does not change the natural structure of the circuit
- In fig(b) the resonator is excited with a current source  $I$ .  
: An independent ideal current source is equivalent to an open circuit  $\rightarrow$  does not alter the natural structure of the resonator

## 12.5 The Second-Order LCR Resonator

### The Resonator Natural Modes


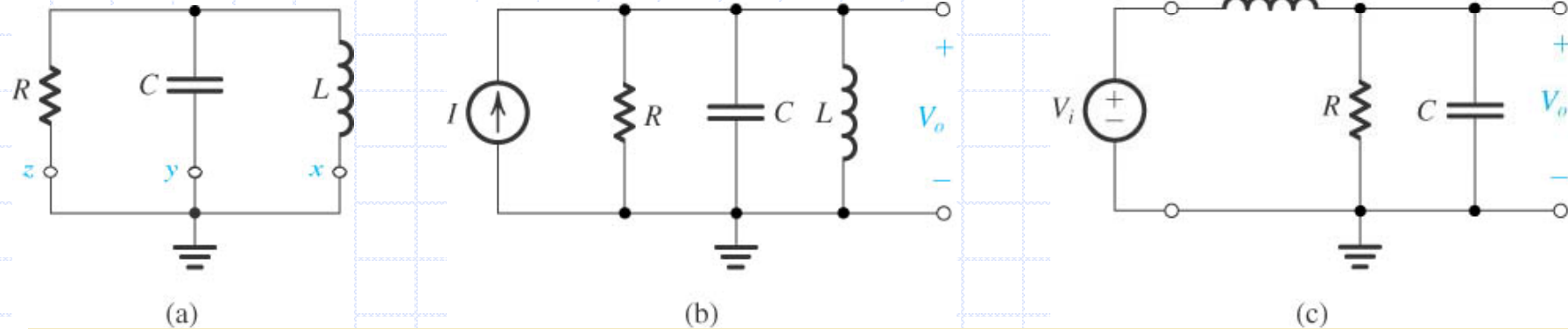


Figure 12.17 (a) The second-order parallel LCR resonator. (b, c) Two ways of exciting the resonator of (a) without changing its *natural structure*: resonator poles are those poles of  $V_o/I$  and  $V_o/V_i$ .


- The natural modes can be determined by applying an excitation that does not change the natural structure of the circuit
- In fig(b) the resonator is excited with a current source  $I$ .  
: An independent ideal current source is equivalent to an open circuit → does not alter the natural structure of the resonator
- An alternative way of exciting the parallel LCR resonator is shown in Fig. (c)

## 12.5 The Second-Order LCR Resonator

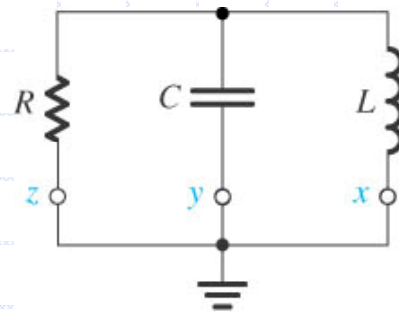
### ◆ The Resonator Natural Modes (cont.)



(a)

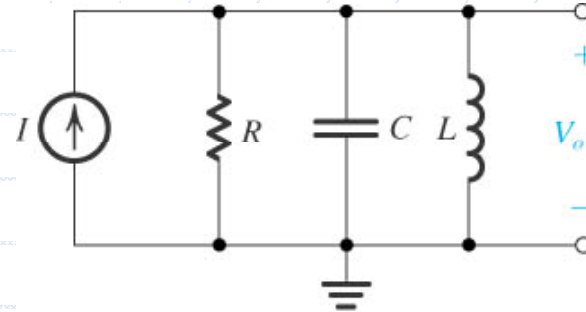

(b)

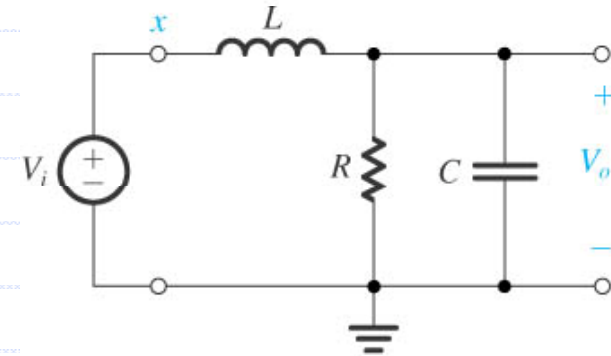

(c)

$$\frac{V_o}{I} = \frac{1}{Y} = \frac{1}{\frac{1}{sL} + sC + \frac{1}{R}} = \frac{\frac{s}{C}}{s^2 + s\left(\frac{1}{CR}\right) + \frac{1}{LC}}$$

- Equating the denominator to the standard form  $[s^2 + s(\omega_0/Q) + \omega_0^2]$


$$\omega_o^2 = \frac{1}{LC} \quad ; \quad \frac{\omega_o}{Q} = \frac{1}{CR} \quad ; \quad \omega_o = \frac{1}{\sqrt{LC}} \quad ; \quad Q = \omega_o CR$$




## 12.5 The Second-Order LCR Resonator
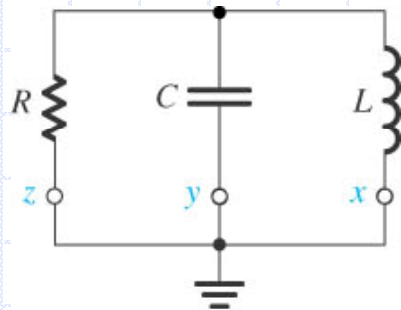
### ◆ Realization of Transmission Zeros

- Find out where to inject the input voltage signal  $V_i$  so that the transfer function  $V_o/V_i$  is the desired one



(a)

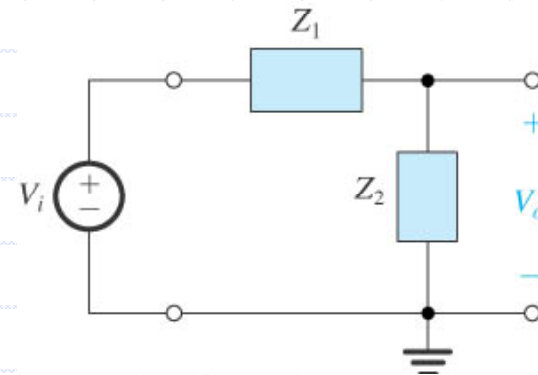


(a) General structure

- Any of the nodes labeled  $x$ ,  $y$ , or  $z$  can be disconnected from ground and connected to  $V_i$  forming of a voltage divider.


$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$

## 12.5 The Second-Order LCR Resonator
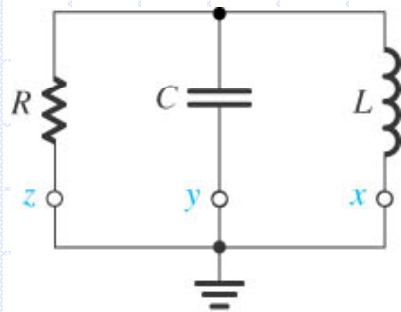
### ◆ Realization of Transmission Zeros (cont.)



(a)

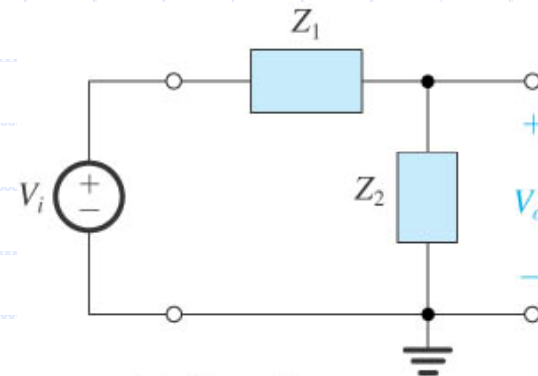


(a) General structure

- The transmission zeros :  $Z_2(s) = \text{zero}$  &  $Z_1(s) \neq \text{zero}$   
or  $Z_1(s) \rightarrow \text{infinite}$  &  $Z_2(s) \rightarrow \text{not infinite}$
- The output will be zero either when  $Z_2(s)$  behaves as a short circuit  
of  $Z_1(s)$  behaves as an open circuit.
- If there is a value of  $s$  at which both  $Z_1$  and  $Z_2$  are zero, then  $V_o/V_i$   
will be finite and no transmission zero is obtained

## 12.5 The Second-Order LCR Resonator
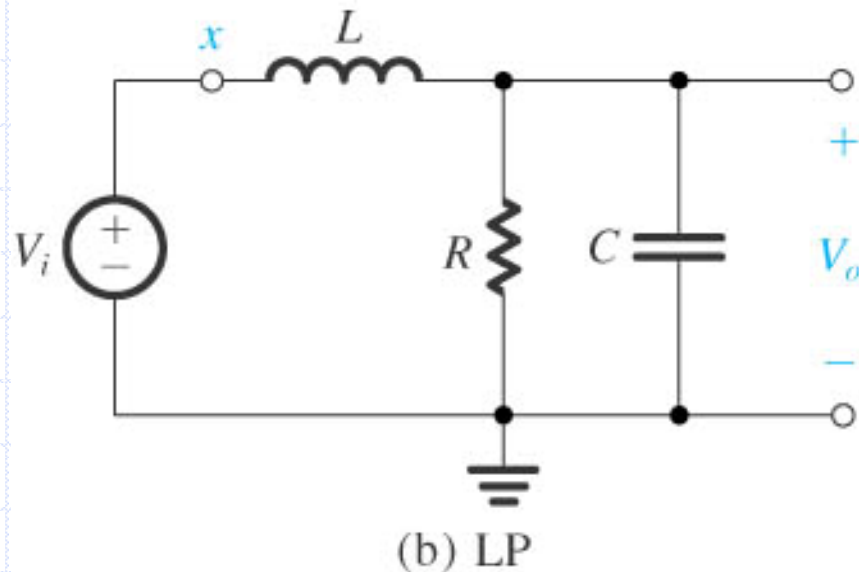
### ◆ Realization of the Low-Pass Function



zeros  $sL = \infty$


$$\frac{1}{sC + \frac{1}{R}} = 0$$

$\Rightarrow$  two zeros at  $s = \infty$

$$T(s) \equiv \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{Y_1}{Y_1 + Y_2} = \frac{\frac{1}{sL}}{\frac{1}{sL} + sC + \frac{1}{R}}$$
$$= \frac{1/LC}{s^2 + s(1/CR) + 1/LC}$$

## 12.5 The Second-Order LCR Resonator
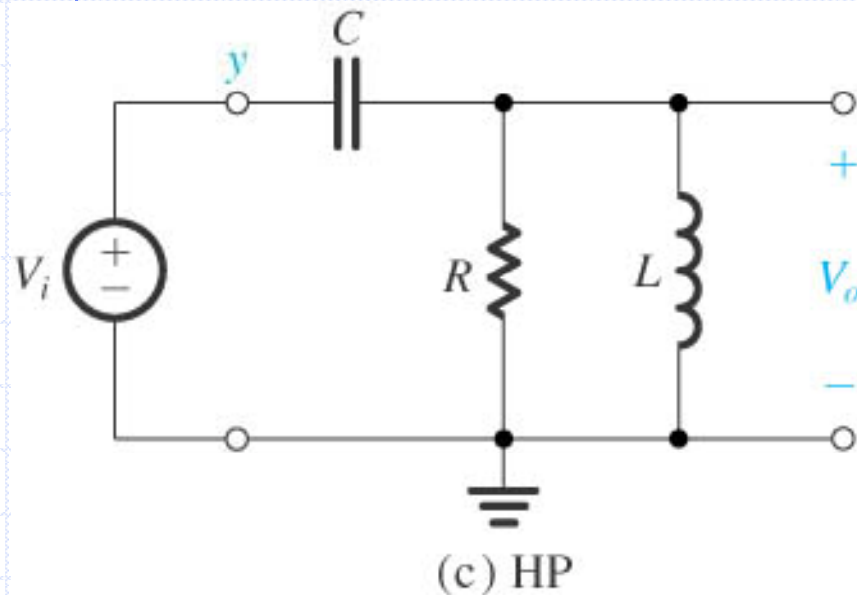
### ◆ Realization of the High-Pass Function




zeros  $\begin{cases} s = 0 : \text{Capacitor} \\ s = 0 : \text{Inductor} \end{cases}$

$$T(s) \equiv \frac{V_o}{V_i} = \frac{a_2 s^2}{s^2 + s\left(\frac{\omega_o}{Q}\right) + \omega_o^2}$$

$$a_2 = 1$$

## 12.5 The Second-Order LCR Resonator
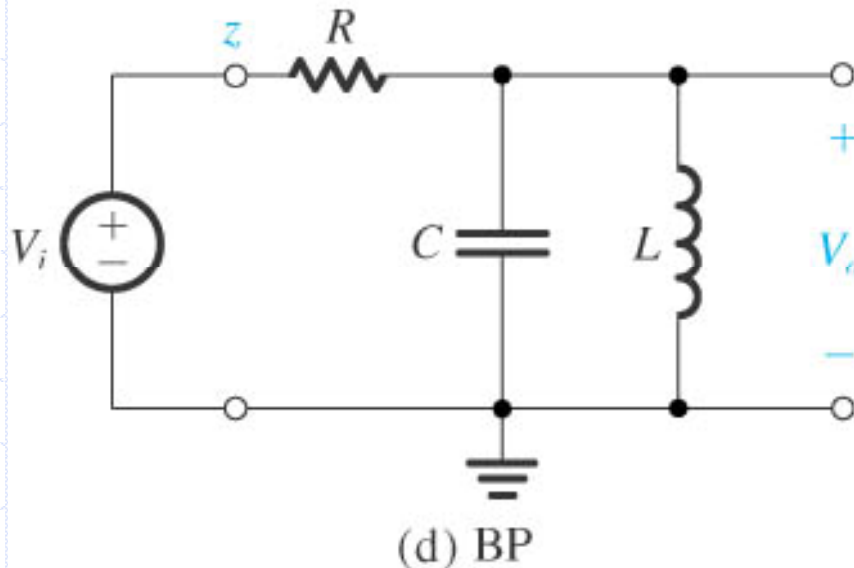
### ◆ Realization of the Band-Pass Function




zeros  $\begin{cases} s = 0 : \text{Inductor} \\ s = \infty : \text{Capacitor} \end{cases}$

- at  $\omega_0$ , LC-tuned circuit exhibits an infinite impedance  
→ no current flows
- the center freq. gain is unity

$$T(s) = \frac{Y_R}{Y_R + Y_L + Y_C} = \frac{\frac{1}{R}}{\frac{1}{R} + \frac{1}{sL} + sC}$$
$$= \frac{s\left(\frac{1}{CR}\right)}{s^2 + s\left(\frac{1}{CR}\right) + \left(\frac{1}{LC}\right)}$$

## 12.5 The Second-Order LCR Resonator

### ◆ Realization of the Notch Function

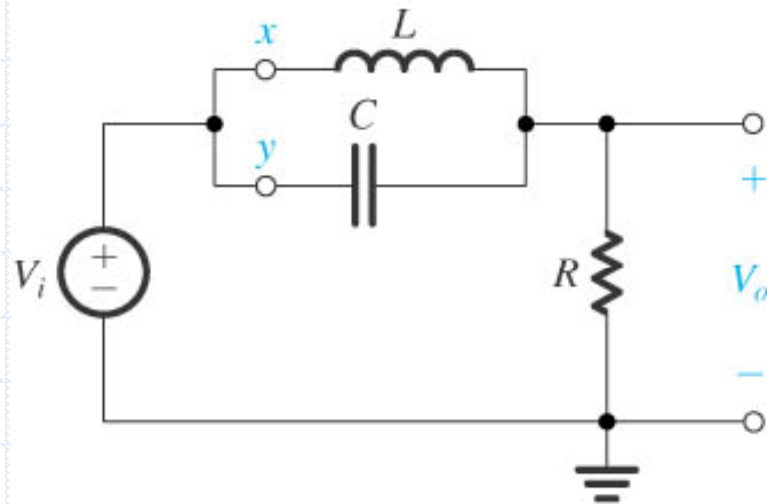

(e) Notch at  $\omega_0$


- The impedance of the LC circuit becomes infinite at  $\omega_0 = 1/\sqrt{LC}$   
→ zero transmission
- The resistor does not introduce zeros.

$$T(s) = a_2 \frac{s^2 + \omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$


- The high-frequency gain  $a_2$  can be found from the circuit to be unity

# 12.5 The Second-Order LCR Resonator
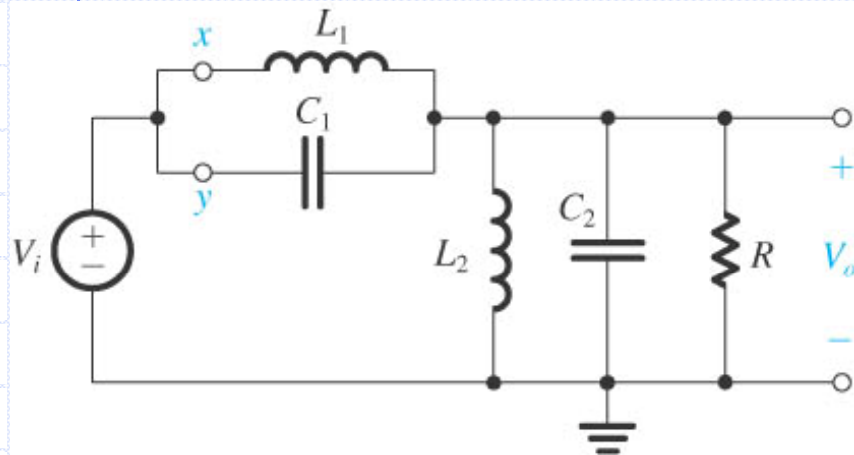
## Realization of the Notch Function (cont.)



(f) General notch

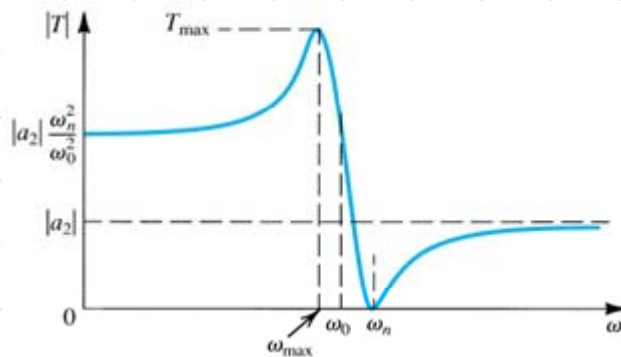

- To place the notch frequency  $\omega_n$  arbitrarily relative to  $\omega_0$ ,

$$L_1 C_1 = 1/\omega_n^2$$

- Thus the  $L_1 C_1$  tank circuit introduces a pair of zeros at  $\pm j\omega_n$



- Not to alter the natural modes,

$$C_1 + C_2 = C \quad \& \quad L_1 || L_2 = L$$



# 12.5 The Second-Order LCR Resonator
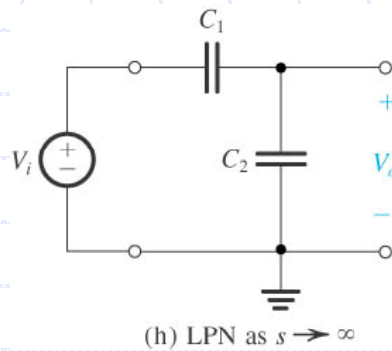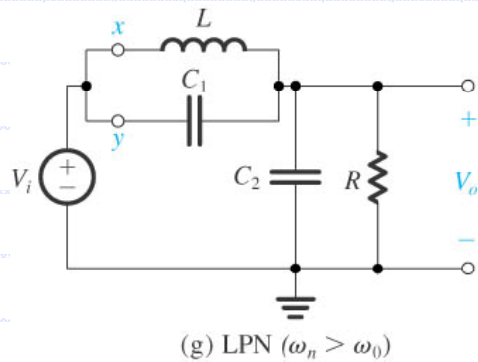
## ◆ Realization of the Notch Function - LPN



- For the LPN,  $\omega_n > \omega_0$   
 $\rightarrow L_1 C_1 < (L_1 || L_2)(C_1 + C_2)$   
*This condition can be satisfied with  $L_2$  eliminated (i.e.,  $L_2 = \infty$  and  $L_1 = L$ )*

- Transfer function

$$T(s) = \frac{s^2 + (1/LC_1)}{s^2 + s(1/CR) + 1/L(C_1 + C_2)}$$

- As  $s \rightarrow \infty$


$$V_o/V_i = C_1/(C_1 + C_2)$$

Thus,

$$a_2 = C_1/(C_1 + C_2)$$

## 12.5 The Second-Order LCR Resonator
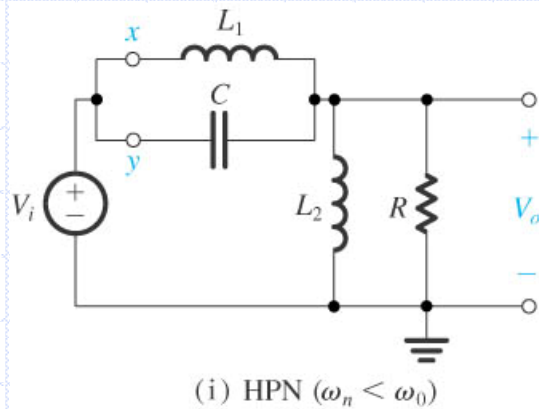
### ◆ Realization of the Notch Function - HPN



- For the HPN,  $\omega_n < \omega_0$

$$\rightarrow L_1 C_1 > (L_1 \parallel L_2)(C_1 + C_2)$$

Which can be satisfied by selecting  $C_2 = 0$


- Transfer function

$$T(s) = \frac{s^2 + (1/L_1 C)}{s^2 + s(1/CR) + [1/(L_1 \parallel L_2)C]}$$

- As  $s \rightarrow \infty$   $V_o$  approaches  $V_i$ , thus the high frequency gain,  $a_2$ , is unity.

## 12.5 The Second-Order LCR Resonator
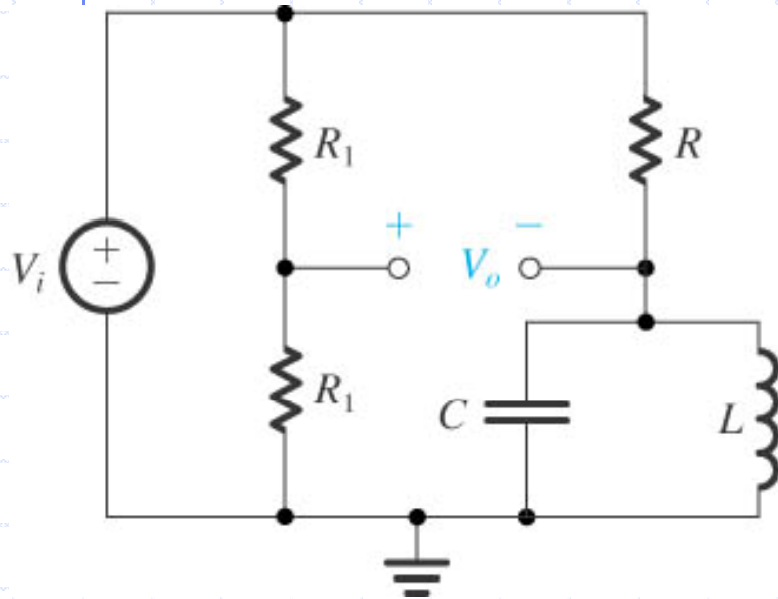
### ◆ Realization of the All-pass Function



- The all-pass transfer function

$$T(s) = \frac{s^2 - s(\omega_0 / Q) + \omega_0^2}{s^2 + s(\omega_0 / Q) + \omega_0^2} = 1 - \frac{s2(\omega_0 / Q)}{s^2 + s(\omega_0 / Q) + \omega_0^2}$$

- The second term is a bandpass function with a center-frequency gain of 2
- All pass realization with a flat gain of 0.5

$$T(s) = 0.5 - \frac{s(\omega_0 / Q)}{s^2 + s(\omega_0 / Q) + \omega_0^2}$$


## 12.5 The Second-Order LCR Resonator

### ◆ Problem 12.36

Use the circuit of below figure, design a lowpass filter with  $\omega_0 = 10^5$  rad/s and  $Q = 1/\sqrt{2}$ . Utilize a 0.1 $\mu$ F capacitor

$$T(s) = \frac{1/LC}{s^2 + s(1/CR) + 1/LC} = \frac{a_0}{(s^2 + s\omega_0/Q + \omega_0^2)}$$

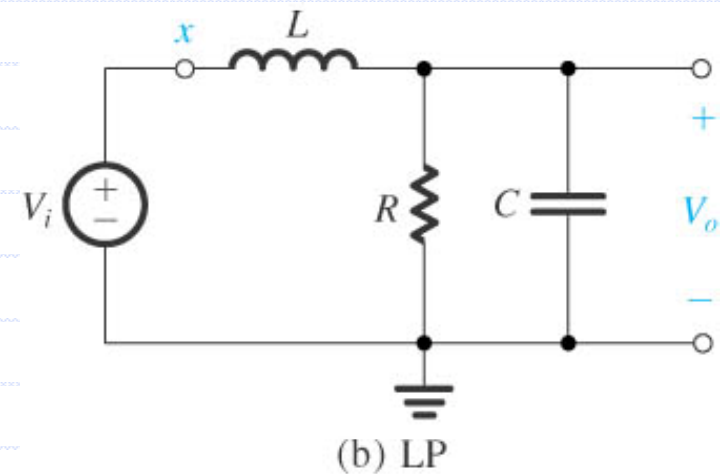- $\omega_0 = 1/\sqrt{LC} \rightarrow L = 1\text{mH}$
- $Q = \omega_0 CR$   
 $\rightarrow R = Q/\omega_0 C = 70.7\Omega$




## 12.6 Second-Order Active Filters Based on Inductor Replacement

- ◆ Study a family of op amp-RC circuits (various second-order filters)
- ◆ Based on an op amp-RC resonator
- ◆ Obtained by replacing the inductor  $L$ , in the LCR resonator with an op amp-RC circuit that has an inductive input impedance

## 12.6 Second-Order Active Filters Based on Inductor Replacement
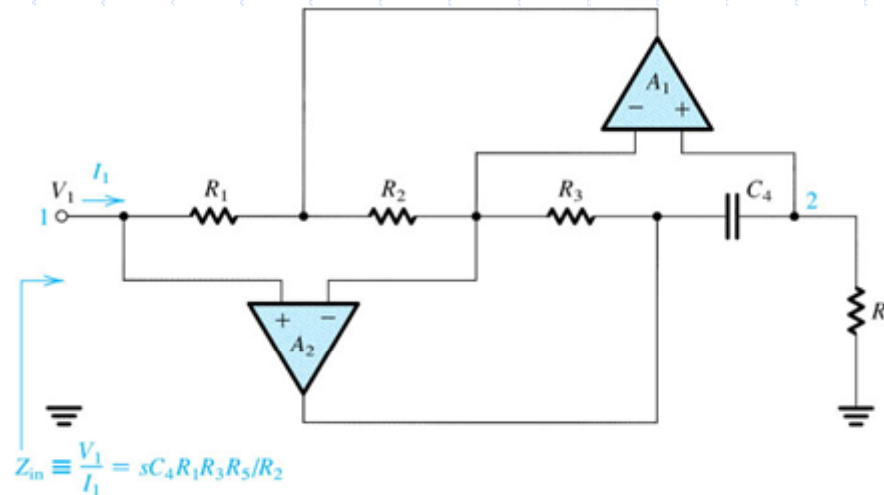
### ◆ The Antoniou Inductance-Simulation Circuit




- Invented by A. Antoniou
- If the circuit is fed at its input (node 1) with a voltage source  $V_1$  and the input current is denoted  $I_1$ , (for ideal op amps)

$$Z_{in} = V_1 / I_1 = sC_4 R_1 R_3 R_5 / R_2$$

$$L = C_4 R_1 R_3 R_5 / R_2$$

## 12.6 Second-Order Active Filters Based on Inductor Replacement
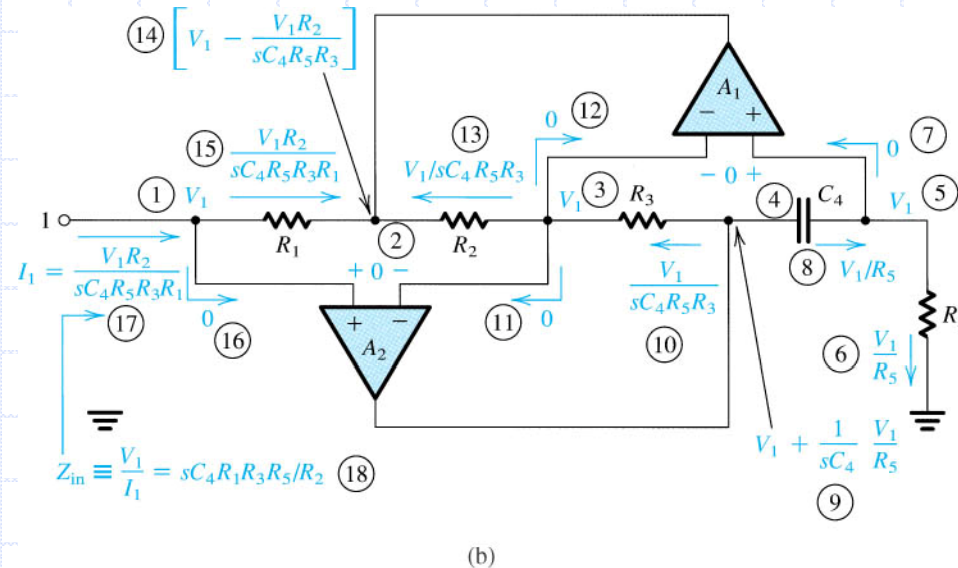
### ◆ The Antoniou Inductance-Simulation Circuit (cont.)



- Assuming ideal op amps.
- The design of this circuit is usually based on selecting
 
$$R_1 = R_2 = R_3 = R_5 = R \quad L = CR^2$$
- Convenient values are selected for C and R to yield the desired inductance value L



# 12.4 First-Order and Second-Order Filter Functions

## Problem 12.40

Design the Antoniou inductance-simulation circuit to realize an inductance of 0.1H


- $$L = C_4 R_1 R_3 R_5 / R_2$$

choose  $R_1 = R_2 = R_3 = R_5 = 10K \Omega$

$\rightarrow L = 10^8 C_4 H$

- $$L = 0.1H$$

$\rightarrow C_4 = 1nF$

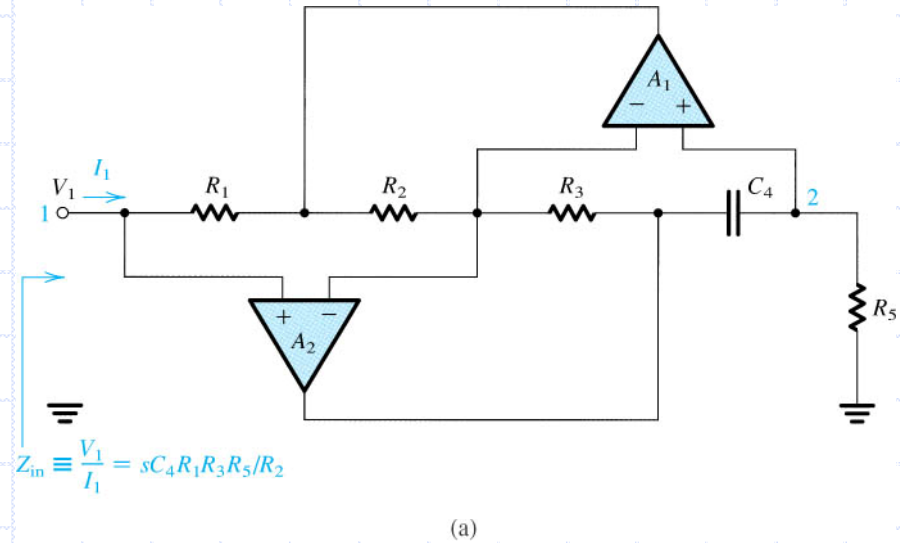

# 12.6 Second-Order Active Filters Based on Inductor Replacement

## ◆ The Op Amp-RC Resonator


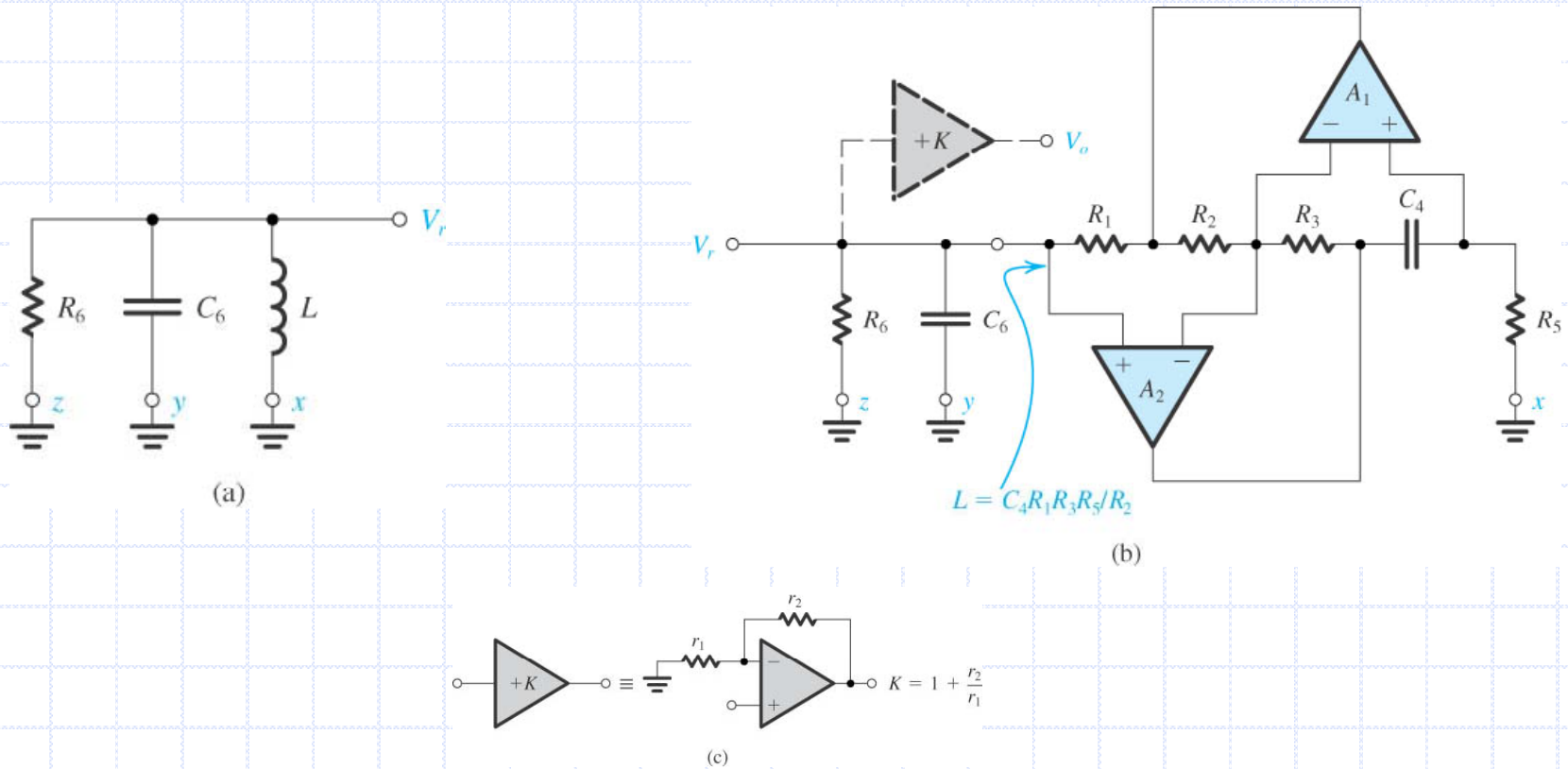


Figure 12.21 (a) An LCR resonator. (b) An op amp-RC resonator obtained by replacing the inductor  $L$  in the LCR resonator of (a) with a simulated inductance realized by the Antoniou circuit of Fig. 12.20(a). (c) Implementation of the buffer amplifier  $K$ .

## 12.6 Second-Order Active Filters Based on Inductor Replacement

### ◆ The Op Amp-RC Resonator (cont.)

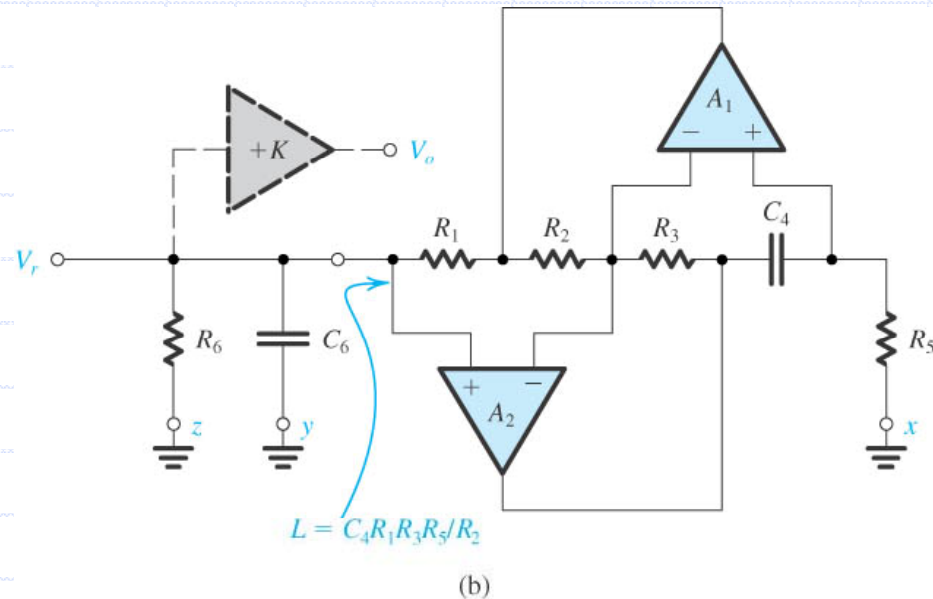


- Replacing the inductor  $L$  with a simulated inductance realized by the Antoniou circuit  $\rightarrow$  second-order resonator.
- Pole frequency

$$\omega_0 = 1/\sqrt{LC} = 1/\sqrt{C_4C_6R_1R_3R_5/R_6}$$

## 12.6 Second-Order Active Filters Based on Inductor Replacement

### ◆ The Op Amp-RC Resonator (cont.)

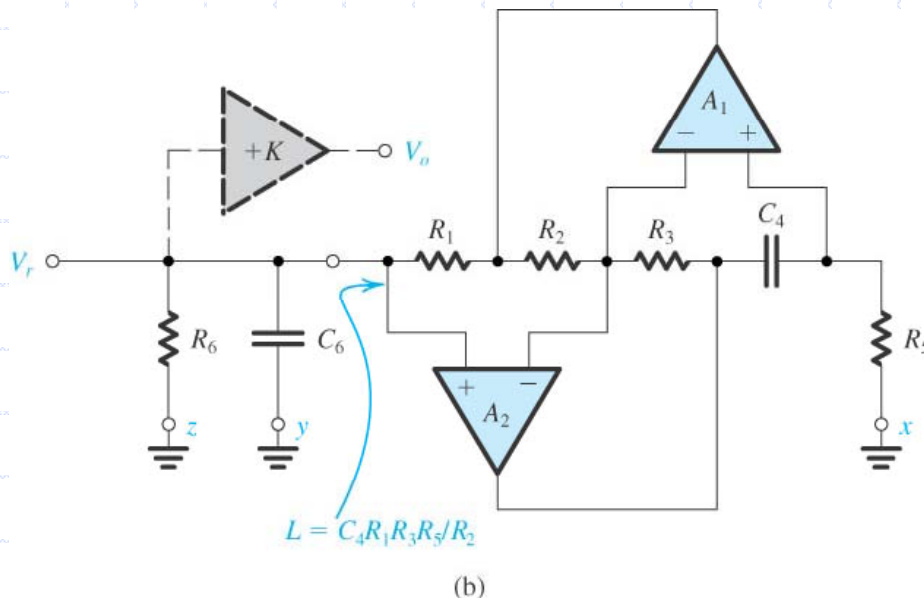

- Pole Q factor

$$Q = \omega_0 C_6 R_6 = R_6 \sqrt{C_6 R_2 / C_4 R_1 R_3 R_5}$$

- Usually selects

$C_4 = C_6 = C$  and  $R_1 = R_2 = R_3 = R_5 = R$ ,  
which results in




$$\omega_0 = 1 / CR$$

$$Q = R_6 / R$$

- Select a practically convenient value for  $C \rightarrow$  determine the value of  $R$  to realize a given  $\omega_0 \rightarrow$  determine the value of  $R_6$  to realize a given  $Q$

# 12.6 Second-Order Active Filters Based on Inductor Replacement

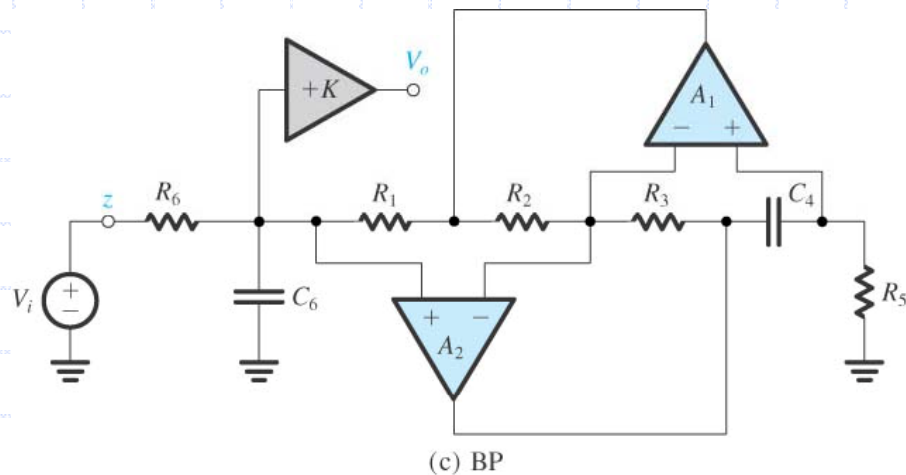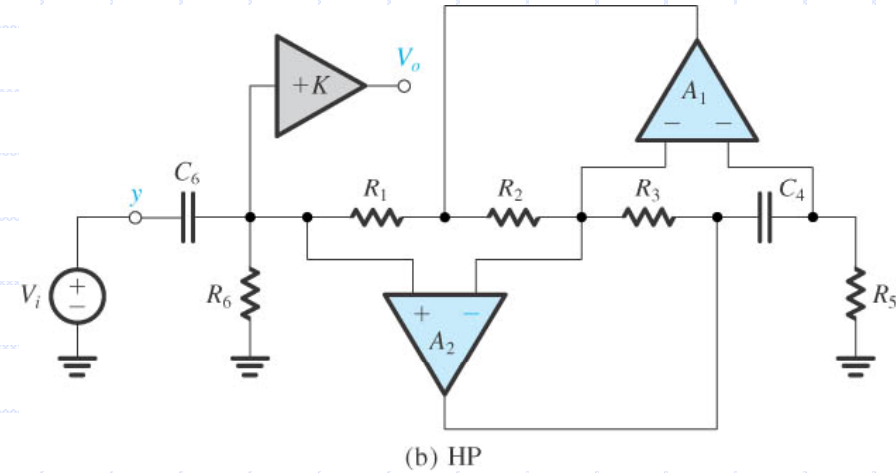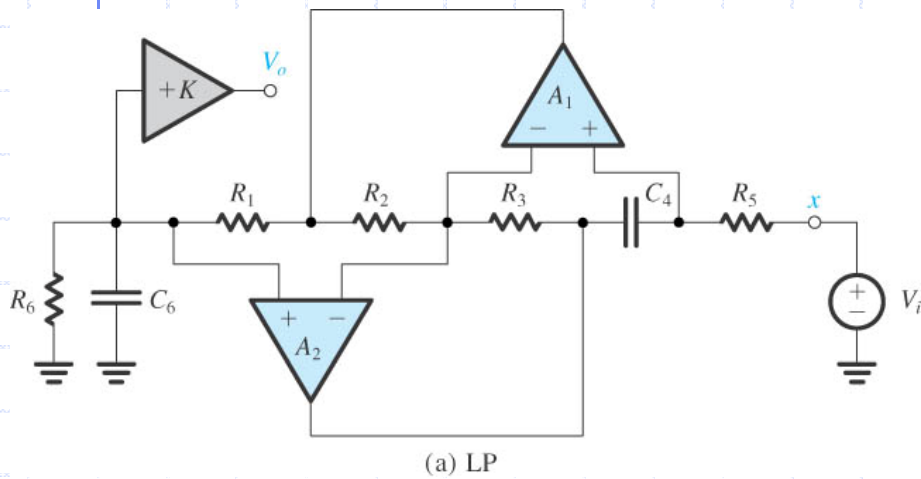
## Realization of the Various Filter types




- Low-pass function : inject  $V_i$  to node  $y$
- High-pass function : inject  $V_i$  to node  $z$
- disconnect node  $z$  from ground and connect it to the signal source  $V_i$

# 12.6 Second-Order Active Filters Based on Inductor Replacement

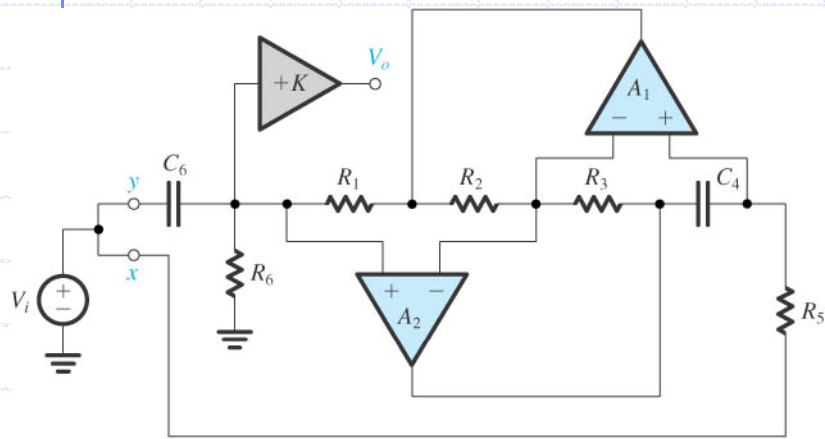
## Realization of the Various Filter types (cont.)




(d) Notch at  $\omega_0$

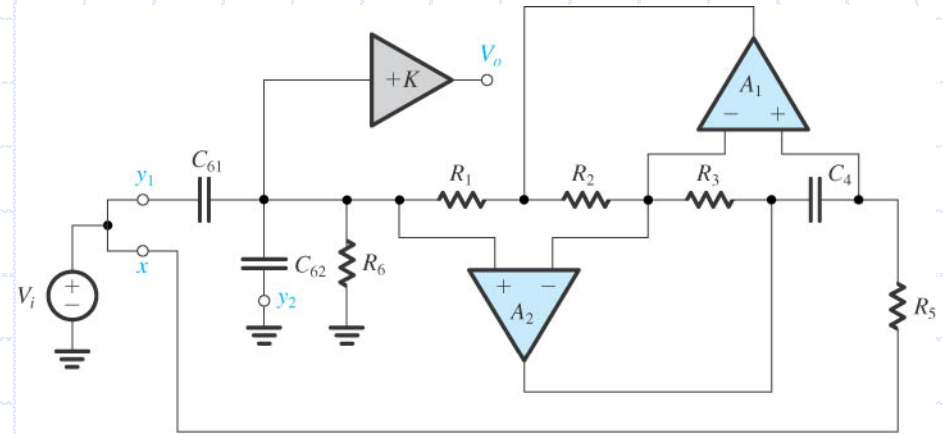

(e) LPN,  $\omega_n \geq \omega_0$

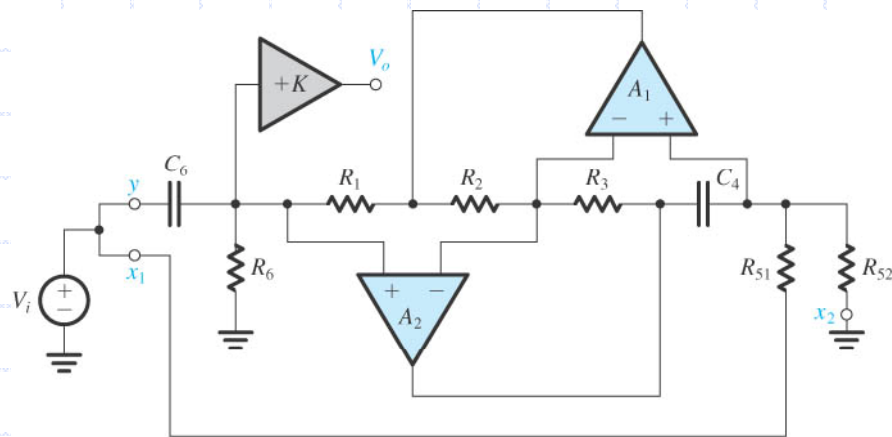



(f) HPN,  $\omega_n \leq \omega_0$

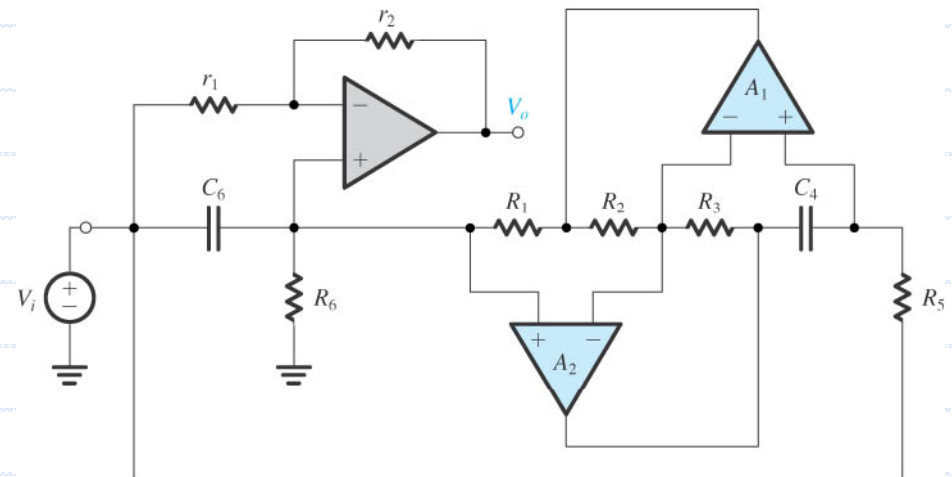

(g) All-pass

# 12.6 Second-Order Active Filters Based on Inductor Replacement
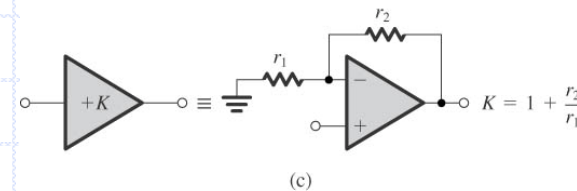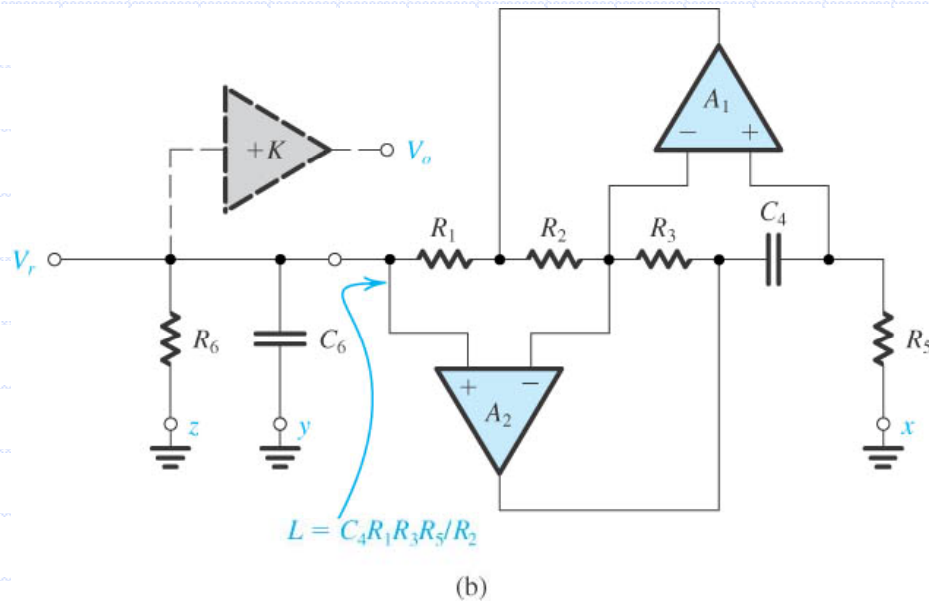
## ◆ Realization of the Various Filter types (cont.)



- In all cases the output can be taken as the voltage across the resonance circuit,  $V_r$ .
- Connecting a load there would change the filter characteristics.  
→ The problem can be solved by utilizing a buffer amplifier.



## 12.6 Second-Order Active Filters Based on Inductor Replacement

### ◆ The All- Pass circuit

- An all-pass function with a flat gain of unity


$AP = 1 - (BP \text{ with a center frequency gain of } 2) \rightarrow \text{complementary}$

- All-pass circuit with unity flat gain is the complement of the bandpass circuit a center-frequency of 2.
- A simple procedure for obtaining the complement of a given linear circuit : Interchanging input and ground in a linear circuit generates a circuit whose transfer function is the complement of that of the original circuit.

# 12.6 Second-Order Active Filters Based on Inductor Replacement
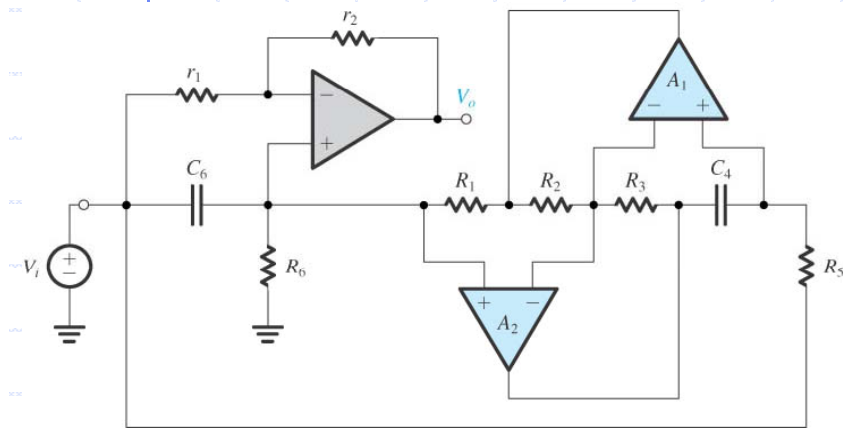
## Problem 12.44

Design the all-pass circuit of below figure to provide a phase shift of 180(degree) at  $f=1$  KHz and to have  $Q=1$ . Use 1-nF capacitors.





(g) All-pass

(g) All pass (AP)

$$T(s) = a_2 \frac{s^2 - s\frac{\omega_0}{Q} + \omega_0^2}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$$

Flat gain =  $a_2$

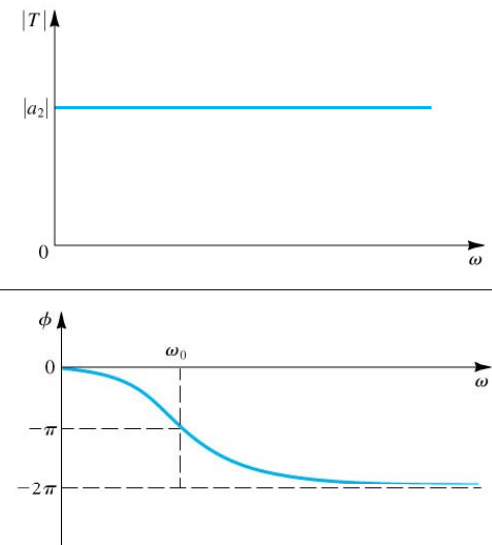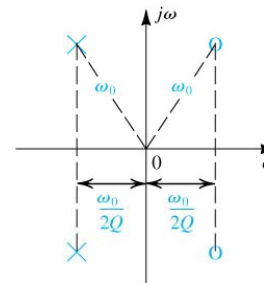

# 12.6 Second-Order Active Filters Based on Inductor Replacement

## Problem 12.44 (cont.)

- Phase shift = 180° at  $f = f_0$

$$\rightarrow f_0 = 1\text{kHz} = R_2 / (2\pi C_4 C_6 R_1 R_3 R_5)$$


Let  $R_1 = R_2 = R_3 = R_5 = R$ ,  $C_4 = C_6 = C = 1\text{nF}$ , then

$$f_0 = 2\pi / (CR)^2$$

- $R = 1 / (2\pi f_0 C) = 159.16\text{k}\Omega = R_1 = R_2 = R_3 = R_5$

- $\omega_0 / Q = 1 / R_6 C_6$
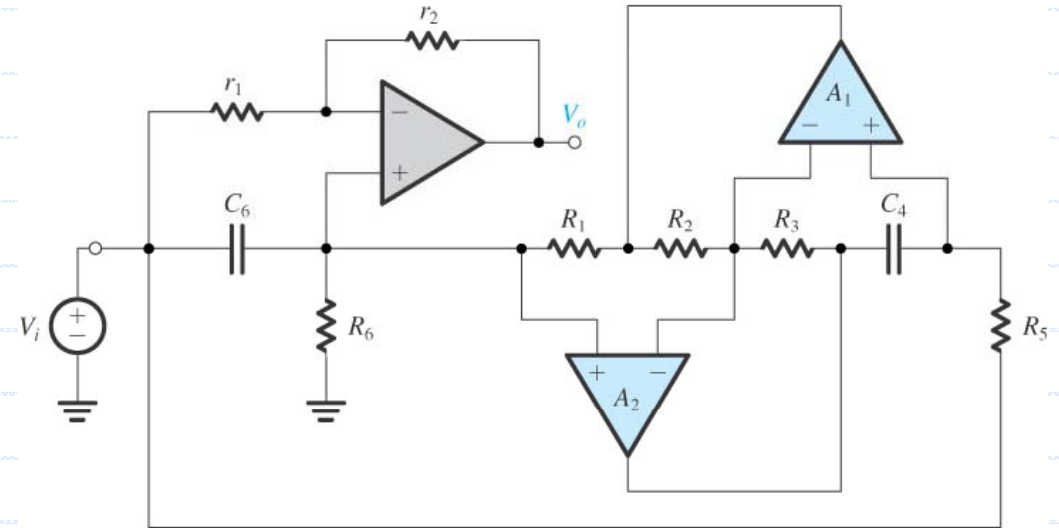
$$\rightarrow R_6 = Q / (C_6 \omega_0) = 159.16\text{k}\Omega$$



(g) All-pass

$$T(s) = a_2 \frac{s^2 - s \frac{\omega_0}{Q} + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

Flat gain =  $a_2$

# 12.7 Second-Order Active Filters Based on the Two-Integrator-Loop Topology


## ◆ Derivation of the Two-Integrator-Loop Biquad

- To derive the two-integrator-loop biquadratic circuit, start from the second-order high-pass transfer function


$$\frac{V_{hp}}{V_i} = \frac{Ks^2}{s^2 + s(\omega_0 / Q) + \omega_0^2}$$

- Cross-multiplying the equation and dividing both sides by  $s^2$ ,
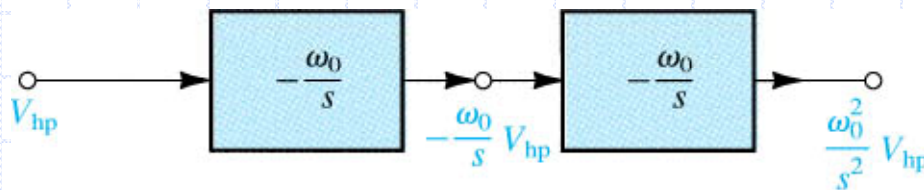
$$V_{hp} + \frac{1}{Q} \left( \frac{\omega_0}{s} V_{hp} \right) + \left( \frac{\omega_0^2}{s^2} V_{hp} \right) = KV_i$$



(a)

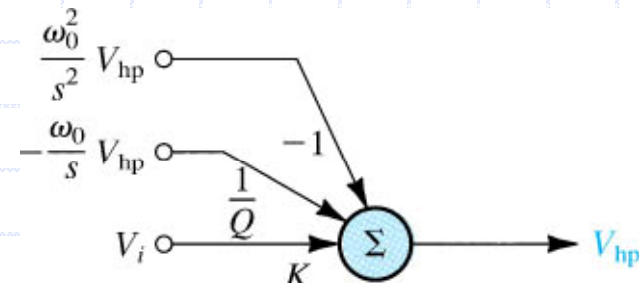


(b)

## 12.7 Second-Order Active Filters Based on the Two-Integrator-Loop Topology

### ◆ Derivation of the Two-Integrator-Loop Biquad(cont)

- A complete block diagram realization

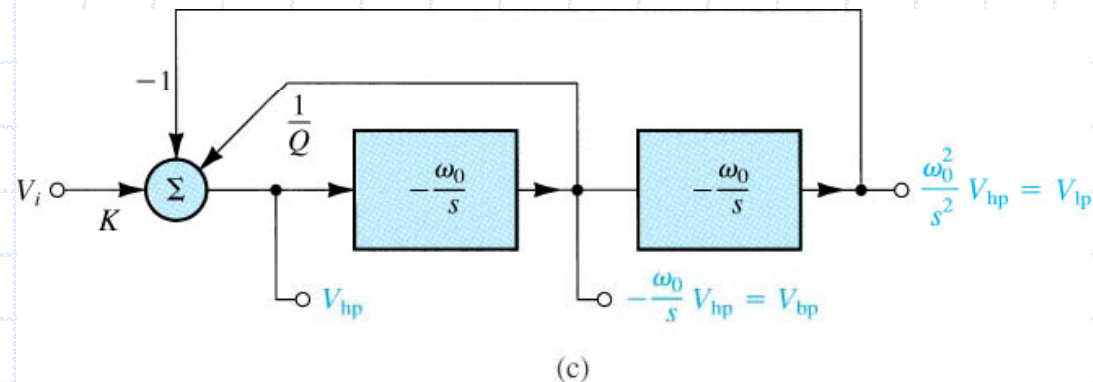

- From the output of the summer, obtained high-pass transfer function

$$T_{hp} = \frac{V_{hp}}{V_i}$$

- From the output of the first integrator, obtained bandpass function

$$T_{bp}(s) = \frac{(-\omega_0/s)V_{hp}}{V_i} = \frac{K\omega_0 s}{s^2 + s(\omega_0/Q) + \omega_0^2}$$


- From the output of the second integrator, obtained lowpass function

$$T_{lp}(s) = \frac{(-\omega_0^2/s^2)V_{hp}}{V_i} = \frac{K\omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

## 12.7 Second-Order Active Filters Based on the Two-Integrator-Loop Topology
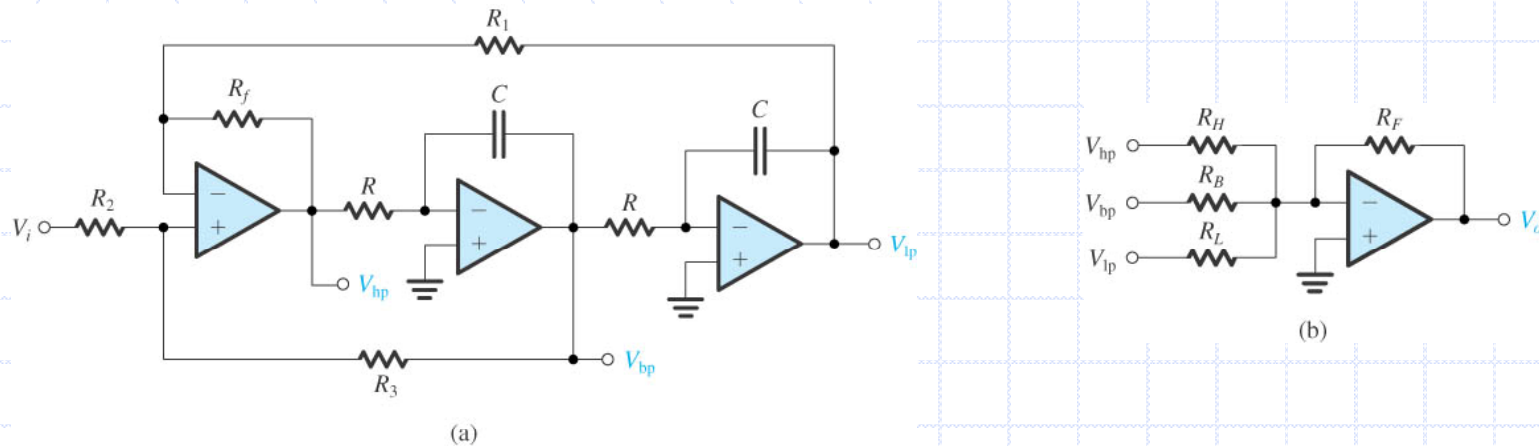
### ◆ Circuit Implementation – KHN biquad

- The Kerwin-Huelsman-Newcomb circuit(KHN biquad)



- Integrator : Miller integrator circuit having  $CR=1/w_0$
- Summer : Op-amp summing circuit

# 12.7 Second-Order Active Filters Based on the Two-Integrator-Loop Topology

## ◆ Circuit Implementation – KHN biquad

- Design procedure

- 1) Select suitable C and R for  $CR=1/\omega_0$

- 2) Determine the values of the resistors associated with the summer from

$$V_{hp} = \frac{R_3}{R_2 + R_3} \left(1 + \frac{R_f}{R_1}\right) V_i + \frac{R_3}{R_2 + R_3} \left(1 + \frac{R_f}{R_1}\right) \left(-\frac{\omega_o}{s} V_{hp}\right) - \frac{R_f}{R_1} \left(\frac{\omega_o^2}{s^2} V_{hp}\right)$$



$$V_{hp} = K V_i - \frac{1}{Q} \left(\frac{\omega_o}{s} V_{hp}\right) - \left(\frac{\omega_o^2}{s^2} V_{hp}\right)$$

$$\frac{R_f}{R_1} = 1$$



$$\frac{R_3}{R_2} = 2Q - 1 \quad (\because R_f = R_1)$$

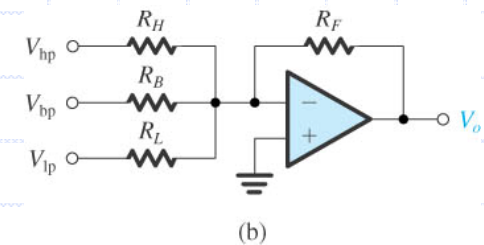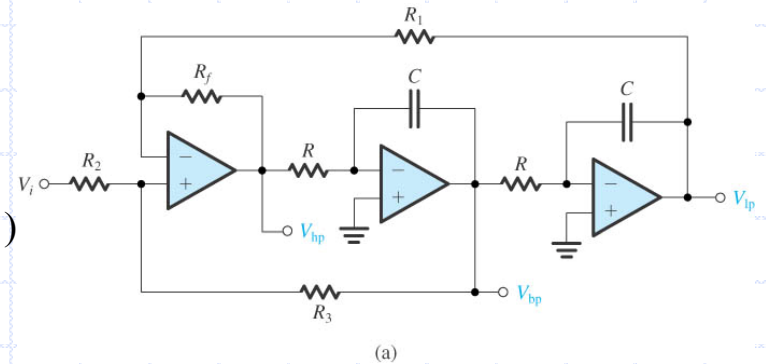
$$K = 2 - (1/Q) \quad (\because R_f = R_1, \frac{R_3}{R_2} = 2Q - 1)$$





## 12.7 Second-Order Active Filters Based on the Two-Integrator-Loop Topology

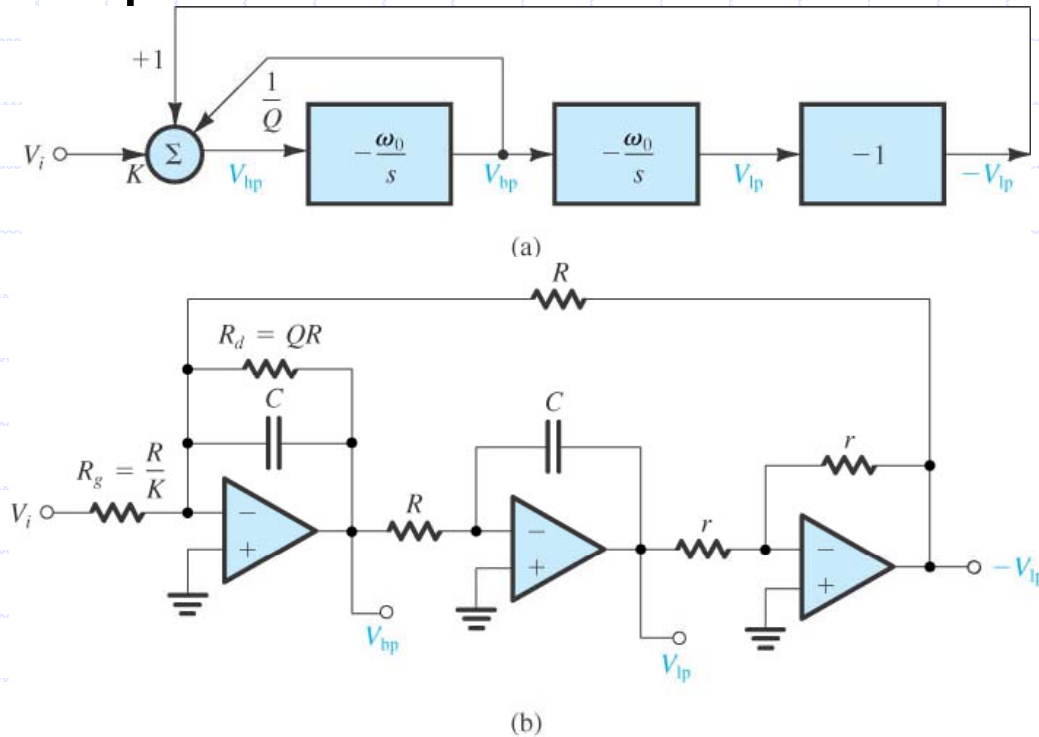
### ◆ Circuit Implementation – Tow-Thomas Biquad



- All three op amp are used in a single-ended mode.
- All the coefficients of the summer have the same sign.
- High-pass function is no longer available.

## 12.7 Second-Order Active Filters Based on the Two-Integrator-Loop Topology
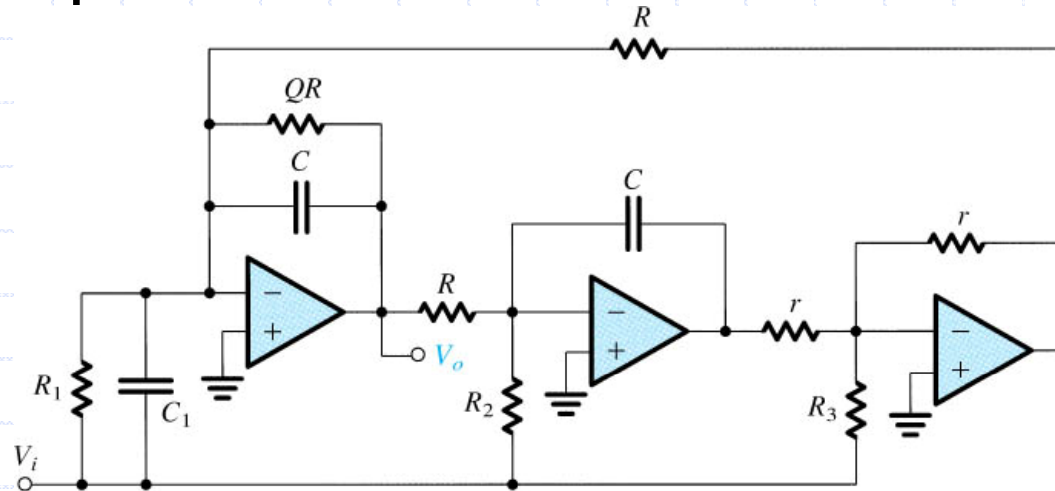
### ◆ Circuit Implementation – Tow-Thomas Biquad




- Feedforward scheme is employed to realize the finite transmission zeros required for the notch and all-pass functions
- The virtual ground at the input of each of the three op amps permits the input signal to be fed to all three op amps.
- Transfer functions is

$$\frac{V_o}{V_i} = \frac{s^2(C_1/C) + s(1/C)(1/R_1 - r/RR_3) + 1/(C^2RR_2)}{s^2 + s(1/QCR) + 1/(CR)^2}$$

# 12.6 Second-Order Active Filters Based on Inductor Replacement
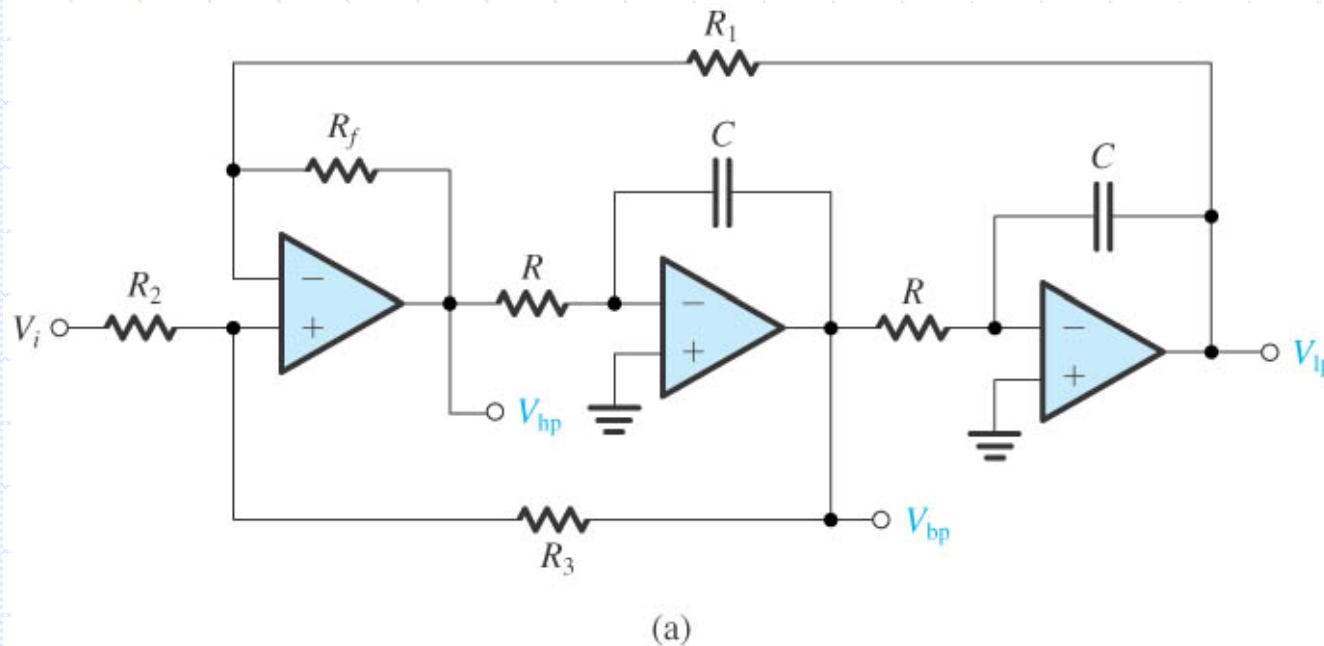
## Problem 12.49


Design the KHN circuit to realize a bandpass filter with a center frequency of 1kHz and a 3-dB bandwidth of 50Hz. Use 10-nF capacitors.



# 12.6 Second-Order Active Filters Based on Inductor Replacement
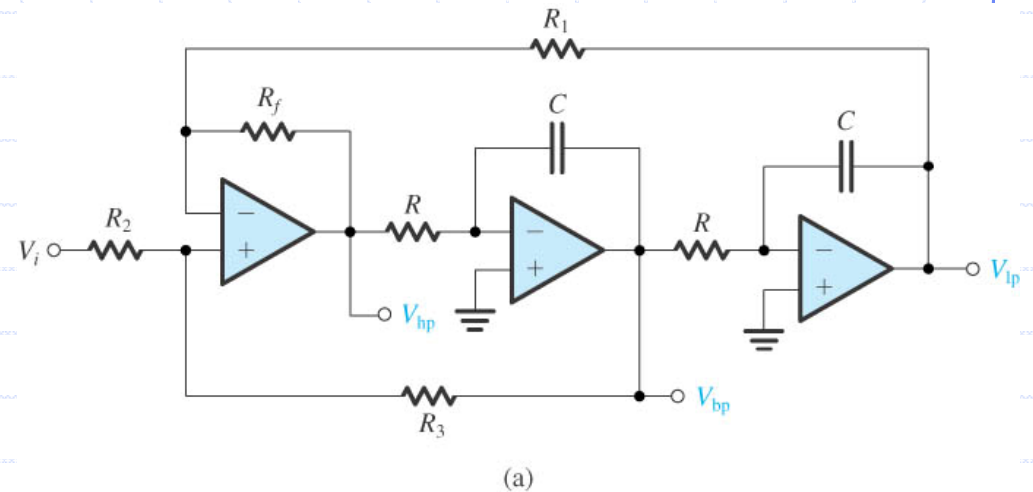
## Problem 12.49 (cont.)

- $B = \omega_0 / Q$   
 $\rightarrow Q = (2\pi 10^3) / (2\pi 50) = 50$
- Choose  $C = 10\text{nF}$   
 $\rightarrow R = 1 / \omega_0 C = 15.92\text{k}\Omega$
- Use  $R_1 = R_f = 10\text{k}\Omega$ ,  
 $R_3 / R_2 = 2Q - 1 = 39$
- Choose  $R_2 = 10\text{k}\Omega \rightarrow R_3 = 390\text{k}\Omega$




$$\frac{R_f}{R_1} = 1$$

$$\frac{R_3}{R_2} = 2Q - 1 \quad (\because R_f = R_1)$$

$$K = 2 - (1/Q) \quad (\because R_f = R_1, \frac{R_3}{R_2} = 2Q - 1)$$

## 12.8 Single-Amplifier Biquadratic Active Filters

◆ the Sallen-and-Key circuits (p. 1132)

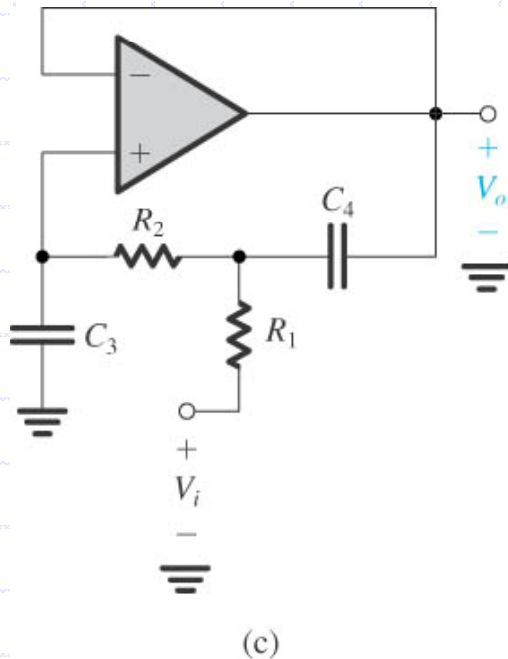

$$\frac{V_o}{V_i} = \frac{1/(C_3 C_4 R_1 R_2)}{s^2 + s \frac{1}{C_4 R_2} \left(1 + \frac{R_2}{R_1}\right) + \frac{1}{C_3 C_4 R_1 R_2}}$$

$$\omega_0 = \frac{1}{\sqrt{C_3 C_4 R_1 R_2}}$$

$$Q = \frac{1}{\sqrt{C_3 C_4 R_1 R_2}} \frac{C_4}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$DC \text{ gain} = 1$$