
 


CPLD, FPGA

Modern Design Method

- Using CAD tools (like Xilinx) and programmable logic devices
 - Along with RAMs and ROMs
 - Complex Programmable Logic Devices (CPLDs)
 - Field Programmable Logic Devices (FPGAs)
- Xilinx XC9500 CPLD and XC4000 FPGA family
 - Can program wide range of combinational circuits
 - Can program wide range of sequential circuits
 - CAD tool automatically do (fitting/place-and-route) from our high level specification

PLD (Programmable Logic Device)

 


$$D_1 = Q_1 X + Q_2 \bar{Q}_1 Y$$

$$D_2 = Q_1 \bar{X} + \bar{Q}_2 Q_1$$


$$Z = Q_1 Q_2$$

General CPLD Architecture

 


- PLD
- Programmable Interconnect
- I/O block


Xilinx 9500-family architecture

 


Function Block

 

I/O Block

 

Switch Matrix

 


Programmable elements

- Many elements should be correctly programmed
 - FBs
 - Programmable AND array
 - Product term allocator
 - Programmable Mux in macrocells
 - I/O Blocks
 - Output enable selection for three-state driver output buffer
 - Switch matrix
 - Programmable connection between switch inputs (macrocell outputs and external inputs) to switch outputs (inputs to FB AND array)
- Fortunately, once we give a high-level design description (using schematic form and VHDL, etc), CAD's fitting software automatically find the solution


View of Fitted Design

- XC9536-5-PC44 -

(elevator system controller)

 


General FPGA chip architecture

 


- Larger number of small blocks (compare with CPLD)
- 3 basic components
 - Configurable Logic Block (CLB) – programmable logic
 - Input/Output Block (IOB) – around chip, associated with I/O pins of the package
 - Programmable interconnects – interconnect CLBs and IOBs for implementing larger functions

Configurable Logic Block (CLB)

 

3 Look Up Tables (G, F, H)

 
- Configured to implement any function of 4 (3 for H) inputs
- Universal Function Generator
 - How to build?
 - With SRAM



- 16x1 SRAM
- Store truth table of the Function (2^4 rows)
- SRAM loaded at config time – to make it work as a specific function

 Example Function using F, G, H

- Parity of 9 inputs: $H = 1$ if odd, $H=0$ if even



Power of F, G, H

$$G = G(G1, G2, G3, G4)$$

$$F = F(F1, F2, F3, F4)$$

$$H = H((F, H2), (G, H0), H1)$$

- Any function of 4 inputs (F) + Any function of 4 inputs (G) + Any function of 3 inputs (H)
- Any function of 5 inputs (F+G+H) – how?
- Any function of 4 inputs (F) + Some function of 6 inputs
- Some function of 9 inputs (F+G+H)

2 D f/fs


- D: F or G or H or DIN/H2 (D_x, D_y configured by M12, M7)
- CLK: K or K- (CLK_x, CLK_y configured by M14, M9)
- EN: 1 or EC (EN_x, EN_y configured by M15, M10)
- S/R control
 - set or reset at configuration
 - Respond to global set/reset signal (not shown) or S/R line

Outputs

- $X = F \text{ or } H$
- $XQ = M4 \text{ or } Qx \text{ (} Dx = F \text{ or } G \text{ or } H \text{ or DIN)}$
- $Y = G \text{ or } H$
- $YQ = M6 \text{ or } Qy \text{ (} Dy = F \text{ or } G \text{ or } H \text{ or DIN)}$

 Example Configuration of CLBs

- Implementing 74x166 (8-bit parallel-in, serial-out shift register)



$$D_A = \overline{EN} \cdot Q_A + EN \cdot \overline{LD} \cdot SER + EN \cdot LD \cdot A$$

$$D_B = \overline{EN} \cdot Q_B + EN \cdot \overline{LD} \cdot Q_A + EN \cdot LD \cdot B$$

⋮

$$D_H = \overline{EN} \cdot Q_H + EN \cdot \overline{LD} \cdot Q_G + EN \cdot LD \cdot H$$

Can implement any 5 variable functions?

$$D_A = \overline{EN} \cdot Q_A + EN \cdot \overline{LD} \cdot SER + EN \cdot LD \cdot A$$



$$H1 = Q_A$$

$$G = D_A \text{ (when } H1 = 0) = EN \cdot \overline{LD} \cdot SER + EN \cdot LD \cdot A$$

$$F = D_A \text{ (when } H1 = 1) = \overline{EN} + EN \cdot \overline{LD} \cdot SER + EN \cdot LD \cdot A$$


$$H = \overline{H1} \cdot G + H1 \cdot F$$

How many CLBs for implementing 8-bit shift register x166?

- only 8 f/fs → 4 CLBs?


- But, all G, F, H in a CLB should be used for each D equation.

I/O Block (IOB)

 


- 1 per I/O pin
- 2 f/fs
- Open collector, tri-state output, registered or not
- Direct Input or Input through f/f (Synchronizer)

Programmable Interconnect



 


Detail Look

 

Programmable Switch Matrix (PSM)

   - PSM make possible variety of difficult interconnections
 - Can lengthen segments
 - Can turn corners



Pretty Complex Interconnect


- Implement huge combination of Interconnects using
 - Direct wires – direct connect to adjacent CLB
 - Single wires – one hop connect to adjacent CLB through a PSM
 - Double wires – travel past 2 CLBs before hitting a switch
 - Long wires – travel length of chip
 - Programmable connections
 - Programmable switch matrix (PSM)

Place and Routing

- Place (On which CLB, a specific function need to be implemented)
- Routing (How to interconnect CLBs?)
 - Avoid use of PSM as much as possible to reduce the delay
- Place and Routing is an inter-dependent complex problem
- Fortunately, CAD tool will do for us

Example

- Find Place and Routing for 74x194

 


$$DA = \overline{S1} \overline{S0} QA + \overline{S1} S0 RIN + S1 \overline{S0} QB + S1 S0 A$$

$$DB = \overline{S1} \overline{S0} QB + \overline{S1} S0 QA + S1 \overline{S0} QC + S1 S0 B$$


$$DC = \overline{S1} \overline{S0} QC + \overline{S1} S0 QB + S1 \overline{S0} QD + S1 S0 C$$

$$DD = \overline{S1} \overline{S0} QD + \overline{S1} S0 QC + S1 \overline{S0} LIN + S1 S0 D$$


QA

 


QB

 


QC

 


QD

 

 


Routing from inputs is not shown

IOB for S1

 

IOB for QA

 

View of Placed Design

- XC2VP2-7-FG256 –

(elevator system controller)

