

2007 Fall: Electronic Circuits 2

---

CHAPTER 11

# Memory and Advanced Digital Circuits

Y. Kwon

---

# Introduction

- ◆ **Combinational circuits** : depends on the present values of the input
- ◆ **Sequential circuits** : memory included.
  - output depends not only on the present inputs but also on the previous inputs.
  - timing generator (clock) required.
- ◆ **Two approaches for providing memory**
  - Static : positive feedback (bistable circuit)
  - Dynamic : charge on a capacitor → need refresh

# 11.1.1 The Latch

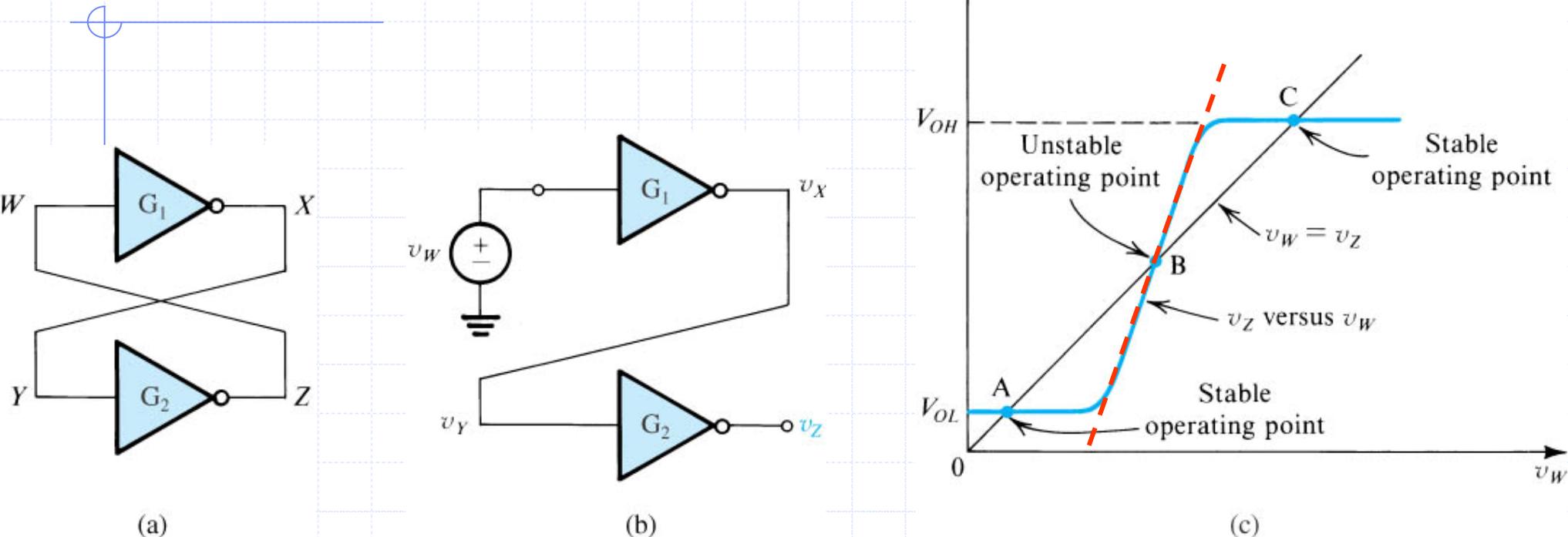


Figure 11.1 (a) Basic latch. (b) The latch with the feedback loop opened. (c) Determining the operating point(s) of the latch.

- ◆ Latch can store one bit of information
  - $v_X$  is high &  $v_Z$  is low = 1
- ◆ two stable operating points  $A$  &  $C$ .  $\rightarrow$  regenerative (loop gain  $> 1$ )
- ◆ unstable operating point  $B$

## 11.1.2 The SR Flip-Flop

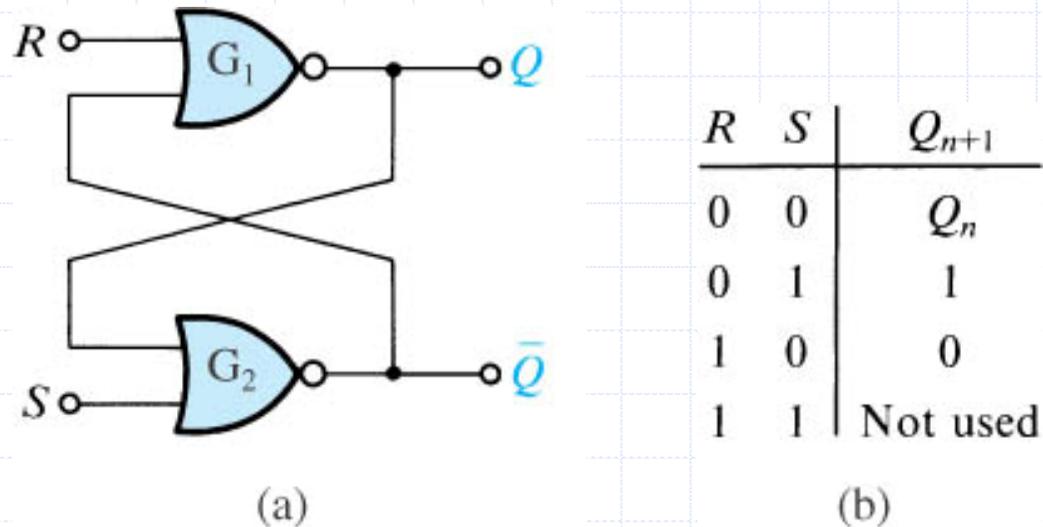


Figure 11.2 (a) The set/reset (SR) flip-flop and (b) its truth table.

- ◆ Flip-flop = latch + triggering circuit
- ◆  $S=R=0 \rightarrow$  memory (or rest) state  $\rightarrow$  retains the value
- ◆  $S=1, R=0 \rightarrow \bar{Q}=0, Q=1$  (set)  $\rightarrow$  retained after  $S$  returns to 0
- ◆  $S=1, R=1 \rightarrow \bar{Q}=0, Q=0 \rightarrow$  undefined, but depends on which one returns to zero first.

## 11.1.3 CMOS Implementation of SR Flip-Flops

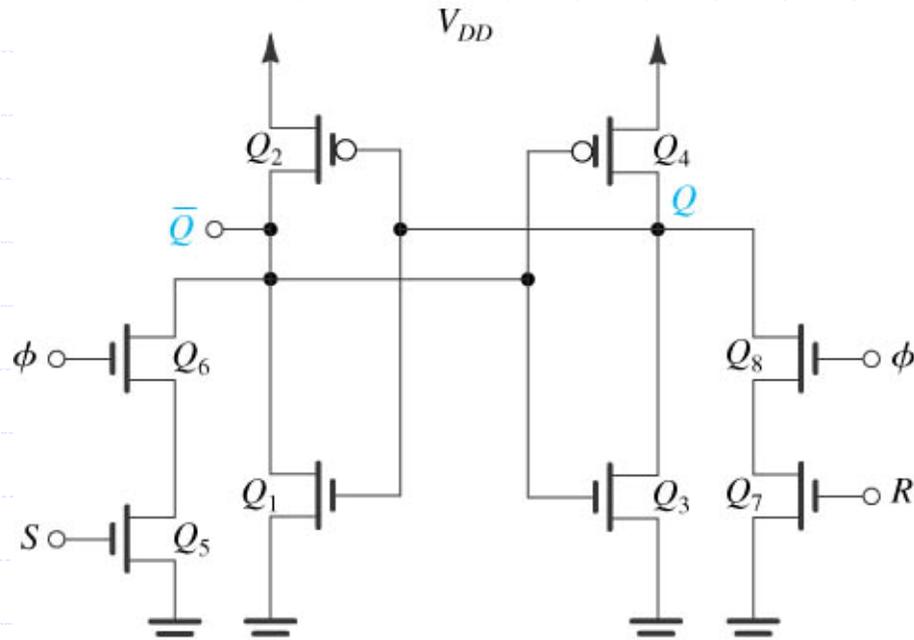


Figure 11.3 CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by  $\phi$ .

- ◆ Clock signal( $\Phi$ ) is high  $\rightarrow$  set or reset action performed.
- ◆  $S=1 \rightarrow \bar{Q} \downarrow \rightarrow V_{Q3} \downarrow \rightarrow Q \uparrow \rightarrow V_{Q1} \uparrow \rightarrow \bar{Q} \downarrow$  (regenerative)

## 11.1.4 A Simpler CMOS Implementation of the Clocked SR Flip-Flop

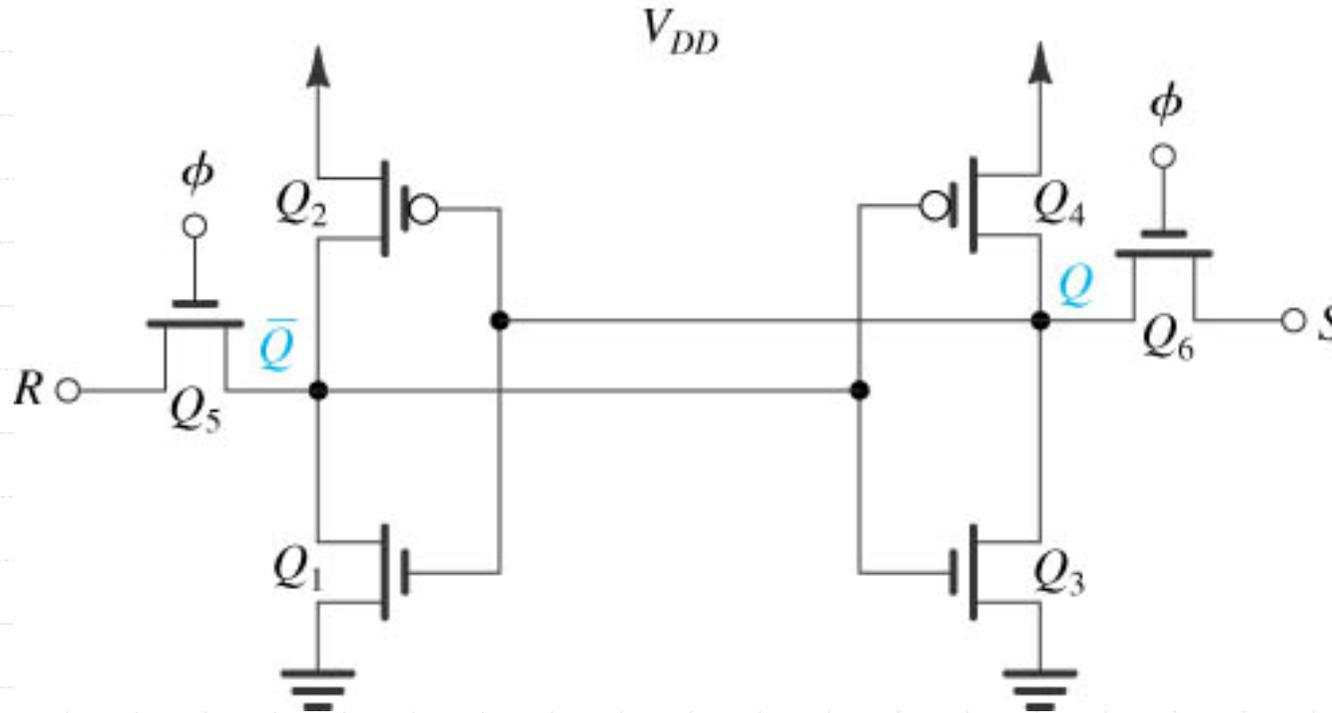


Figure 11.5 A simpler CMOS implementation of the clocked SR flip-flop.

- ◆ Pass-transistor logic is employed
- ◆ Very popular in the design of static random-access memory (SRAM)

## 11.1.5 D Flip-Flop Circuits


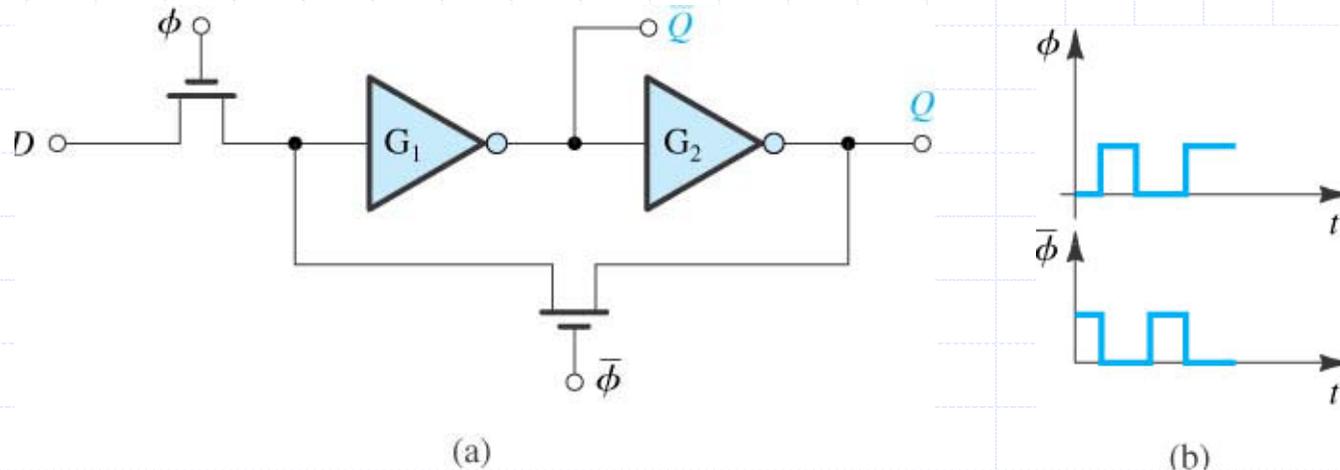


Figure 11.7 A simple implementation of the D flip-flop.

### ◆ Simple implementation of the D flip-flop:

- $\Phi = 1$  and  $\bar{\Phi} = 0$ : the loop is open and  $Q$  is determined by  $D$ .
- $\Phi = 0$  and  $\bar{\Phi} = 1$ : the loop is closed and the flip-flop is in latch mode.  
→ latch stores the value of  $D$  right before the clock went down.
- two-phase non-overlapping clock is required for D flip-flop operation.
- Major drawback: the output simply follows the signal on the D input line during  $\Phi$ .


## 11.1.5 D Flip-Flop Circuits (cont.)

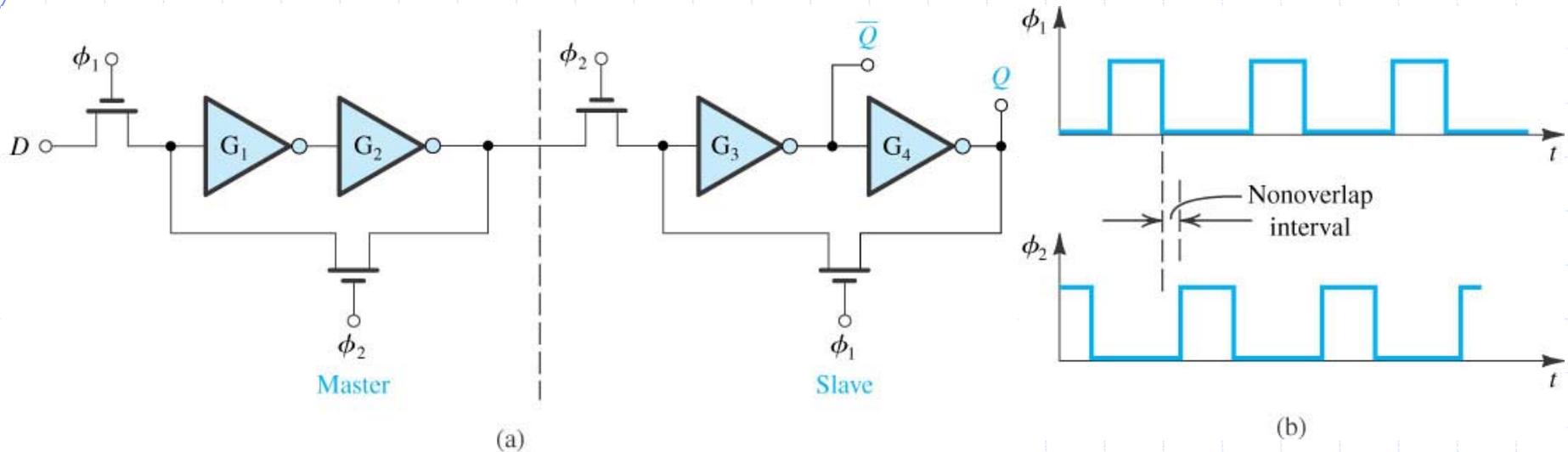

**Figure 11.8** (a) A master–slave D flip-flop. The switches can be, and usually are, implemented with CMOS transmission gates. (b) Waveforms of the two-phase nonoverlapping clock required.

- ◆ Two clock phases,  $\Phi_1$  &  $\Phi_2$ , must be nonoverlapping.
- ◆ Positive transition of clock  $\Phi_2$  the output  $Q$  adopts the value of  $D$ .
- ◆ During the nonoverlap interval, feedback loops open  
→ capacitances maintain most of their charge.
- ◆ Nonoverlap interval should be kept reasonably short (one-tenth or less of the clock period, and of the order of 1ns or so in current practice)


## 11.2 MULTIVIBRATOR CIRCUITS

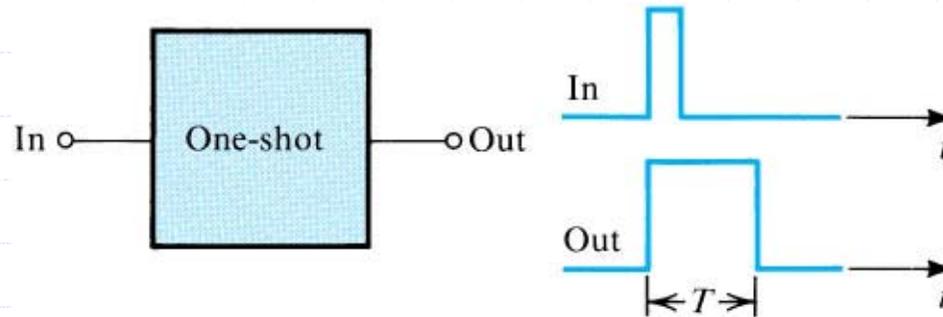

**Figure 11.9** The monostable multivibrator (one-shot) as a functional block, shown to be triggered by a positive pulse. In addition, there are one shots that are triggered by a negative pulse.

- ◆ Bistable multivibrator (two stable states, e.g. flip-flop).
- ◆ Monostable multivibrator (one stable state + quasi-stable state, e.g. pulse stretcher or pulse standardizer).
- ◆ Astable multivibrator (no stable states + two quasi-stable states, e.g. periodic pulse generator).

## 11.2.1 A CMOS Monostable Circuit

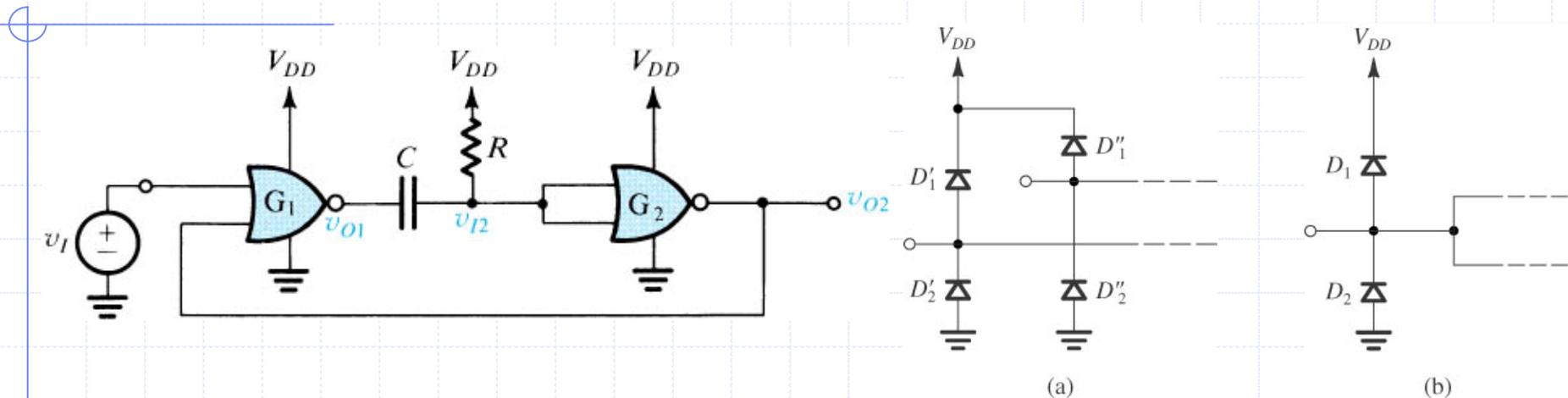

- ◆ Commercially available CMOS gates have a special arrangement of diodes connected at their input terminals
- ◆ Prevent the input voltage signal from rising above the supply voltage  $V_{DD}$  and from falling below ground voltage.
- ◆ Effect on the operation of the inverter-connected gate  $G_2$ .
  - The diodes provide a low-resistance path to the power supply for voltages exceeding the power supply limits, the input current for intermediate voltages is essentially zero.

## 11.2.1 A CMOS Monostable Circuit (cont.)


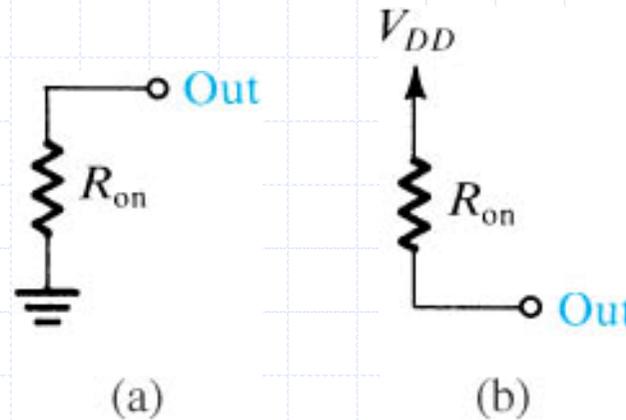


Figure 11.12 Output equivalent circuit of CMOS gate when the output is (a) low and (b) high.

### ◆ Approximate output equivalent circuits of the gate.


- Fig.11.12(a) : when the gate output is low. In this state, current can flow from the external circuit into the output terminal of the gate; the gate is said to be sinking current.
- Fig.11.12(b) : when the gate output is high. In this state, current can flow from  $V^{DD}$  through the output terminal of the gate into the external circuit; the gate is said to be sourcing current.
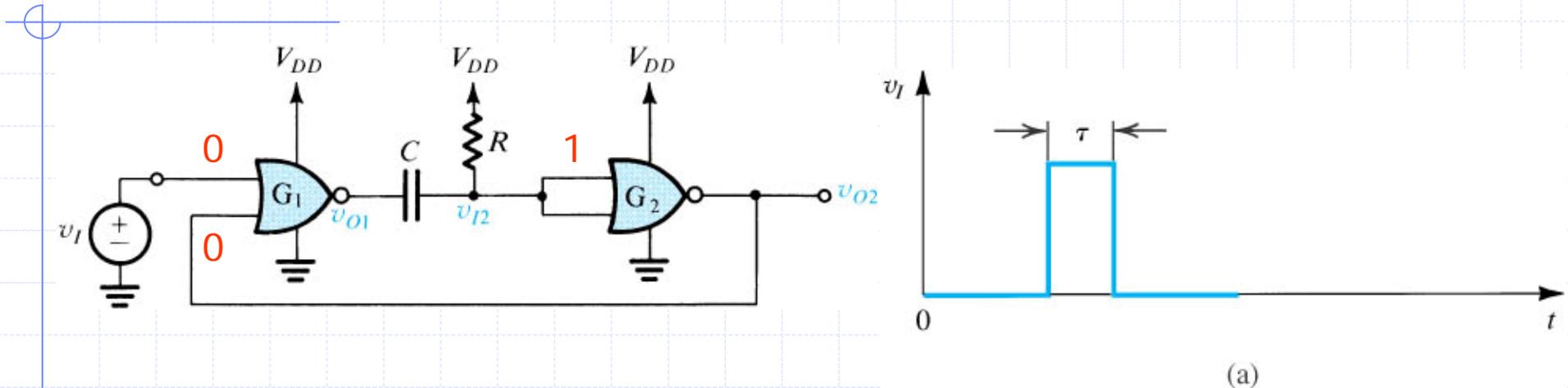
## 11.2.1 A CMOS Monostable Circuit (cont.)




1. Stable state of the monostable circuit (the state of the circuit before the trigger pulse is applied): The output of  $G_1$  is high at  $V_{DD}$ , the capacitor is discharged, and the input voltage to  $G_2$  is high at  $V_{DD}$ .
  - The output of  $G_2$  is low, at ground voltage.
  - Low voltage is fed back to  $G_1$ ; since  $v_I$  also is low, the output of  $G_1$  is high, as initially assumed.
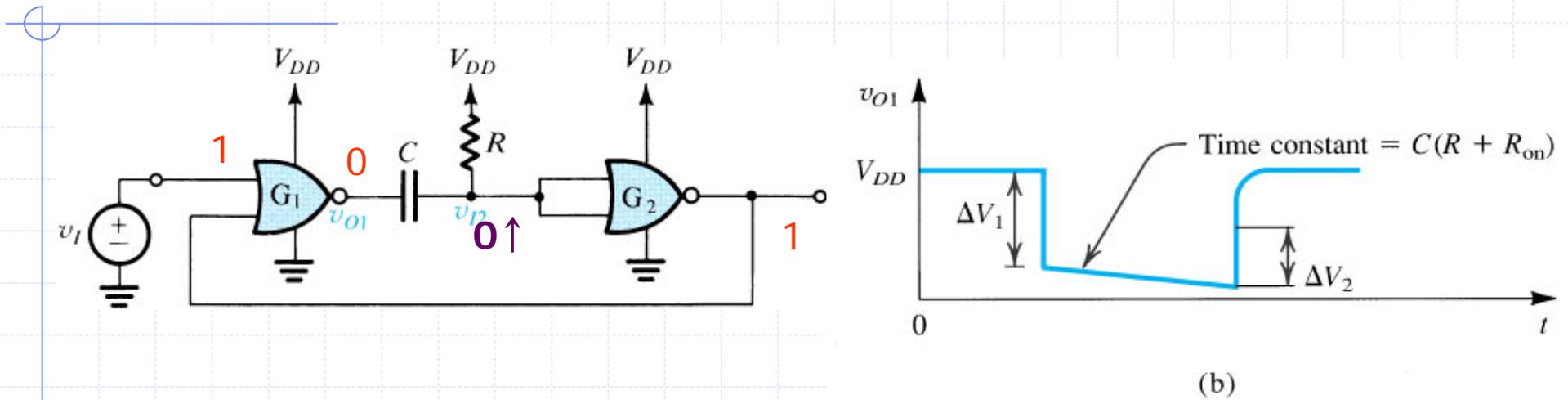
## 11.2.1 A CMOS Monostable Circuit (cont.)




2. Trigger pulse is applied: The output of  $G_1$  will go low (but its output will not go all the way to 0V). The output of  $G_1$  drops by a value  $\Delta V_1$ .
  - $G_2 \rightarrow$  the drop of voltage at its input causes its output to go high (to  $V_{DD}$ ).
  - Keeps the output of  $G_1$  low even after the triggering pulse has disappeared.
  - The Circuit is now in the quasi-stable state.
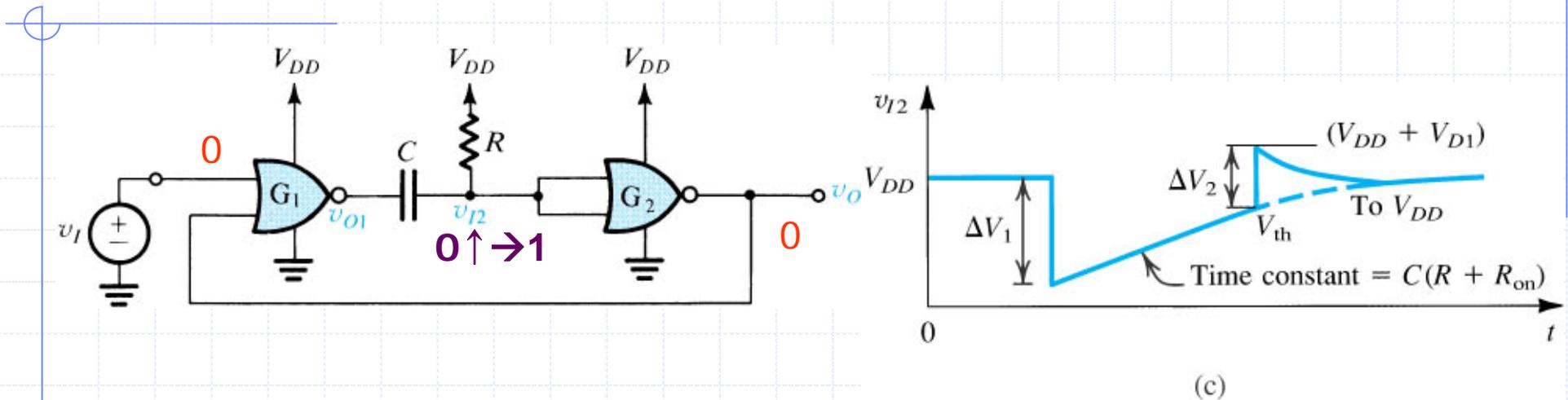
## 11.2.1 A CMOS Monostable Circuit (cont.)



3. Operation in the quasi-stable state : The current through  $R$ ,  $C$ , and  $R_{on}$  causes  $C$  to charge, and the voltage  $V_{I2}$  rises exponentially toward  $V_{DD}$  with a time constant  $C(R + R_{on})$ .
- $V_{I2}$  continue to rise until it reaches  $V_{th}$  of inverter  $G_2$
  - $G_2$  will switch and its output  $v_{O2}$  will go to  $0V$ , which will in turn cause  $G_1$  to switch on toward  $V_{DD}$ .

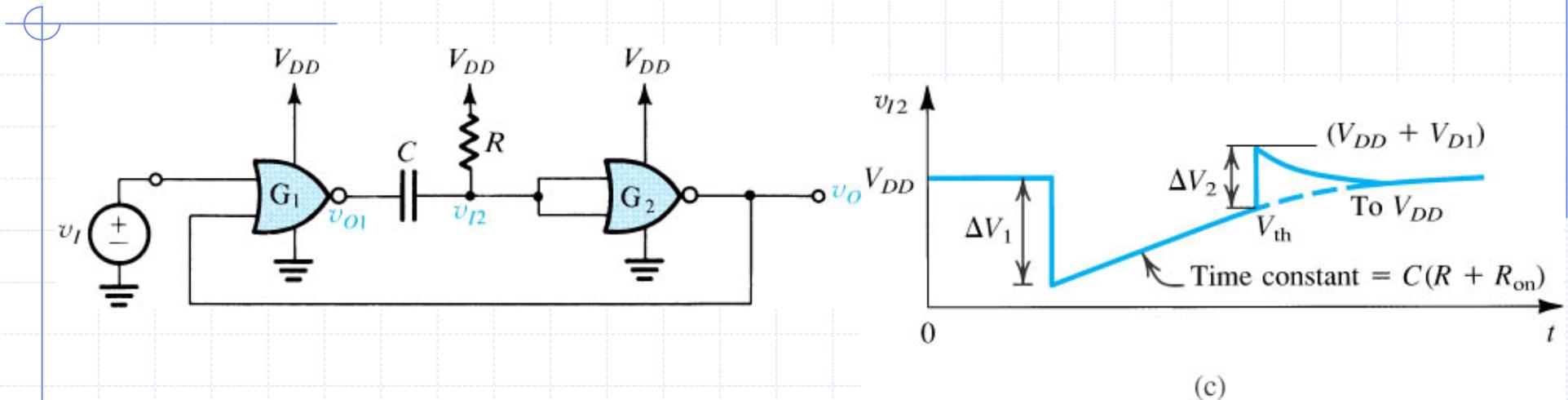
## 11.2.1 A CMOS Monostable Circuit (cont.)




- The output of  $G_1$  will attempt to rise to  $V_{DD}$  (instantaneous rise). Limited to an amount  $\Delta V_2$  by the limiting action of diode.  

$$\Delta V_2 = V_{DD} + V_{D1} - V_{th}$$
- $V_{O1}$  rise. And the input of  $G_2$  will rise by an equal amount  $\Delta V_2$ .
- Now  $V_{I2} > V_{DD}$ , current will flow from the output of  $G_1$  through  $C$  and then through the parallel combination of  $R$  and  $D_1$ .
- This current discharges  $C$  until  $V_{I2}$  drops to  $V_{DD}$  and  $v_{O1}$  rises to  $V_{DD}$ .
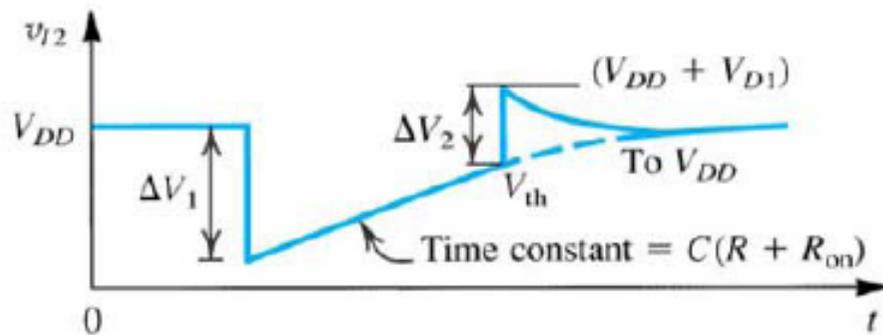
## 11.2.1 A CMOS Monostable Circuit (cont.)



(c)

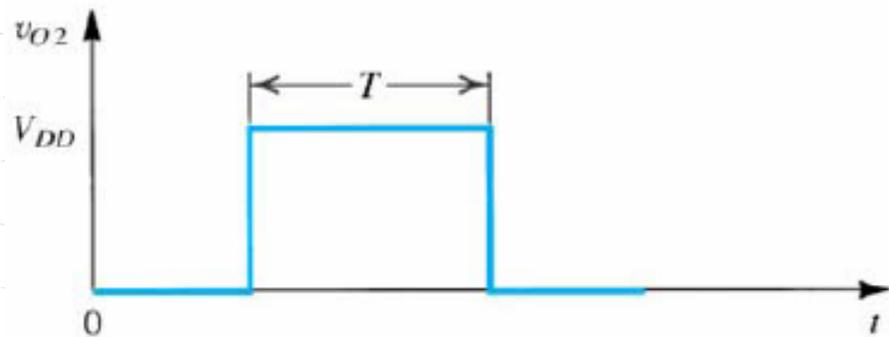

(d)

✳ The monostable circuit should not be retriggered until the capacitor has been discharged (recovery time: the capacitor discharge interval).

$$v_{I2}(t) = V_{DD} - \Delta V_1 e^{-t/\tau_1}$$


$$\tau_1 = C(R + R_{on})$$

Substituting for  $t = T$  and  $v_{I2}(T) = V_{th}$ .

$$T = C(R + R_{on}) \ln\left(\frac{R}{R + R_{on}} \frac{V_{DD}}{V_{DD} - V_{th}}\right)$$


Figure 11.13 Timing diagram for the monostable circuit in Fig. 11.10.

## 11.2.2 An Astable Circuit

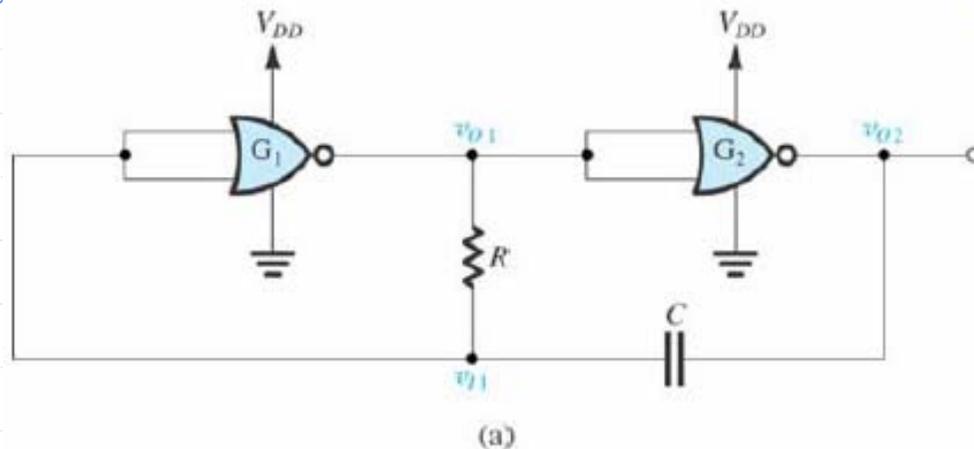


**Figure 11.15** (a) A simple astable multivibrator circuit using CMOS gates. (b) Waveforms for the astable circuit in (a). The diodes at the gate input are assumed to be ideal and thus to limit the voltage  $v_{I1}$  to 0 and  $V_{DD}$ .

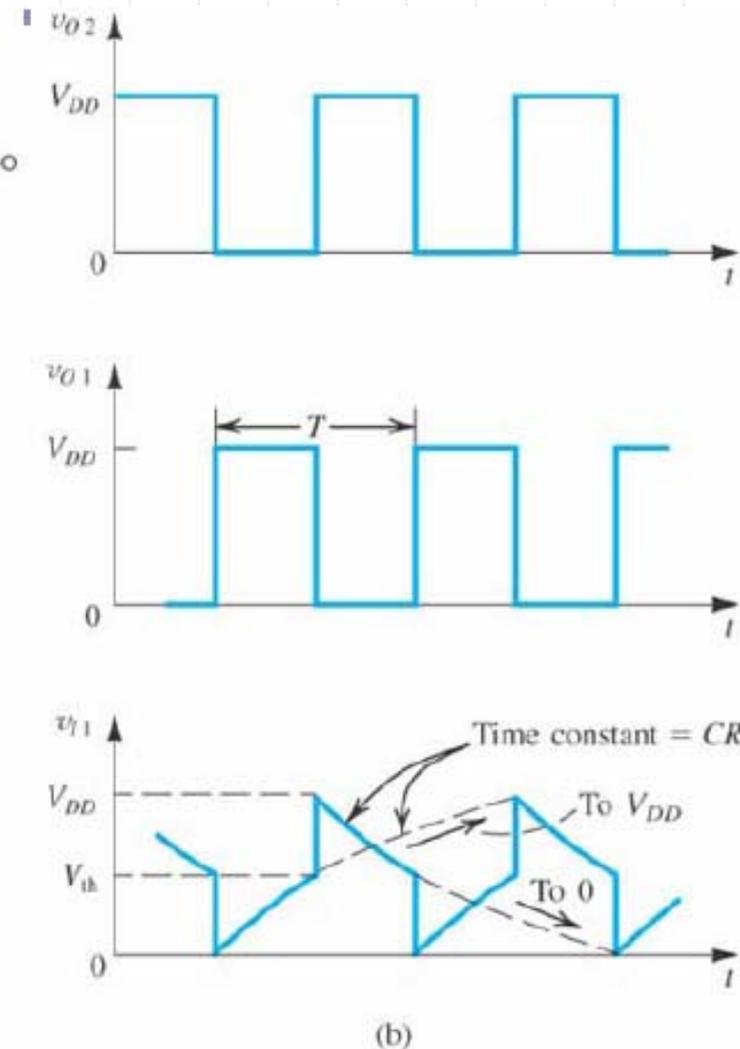- Assume that the NOR gates are of the CMOS family.
- Neglect the finite output resistance of the CMOS gate.
- Assume that the clamping diodes are ideal.  
→ The waveforms of Fig. 11.15(b) are obtained.



## 11.2.3 The Ring Oscillator

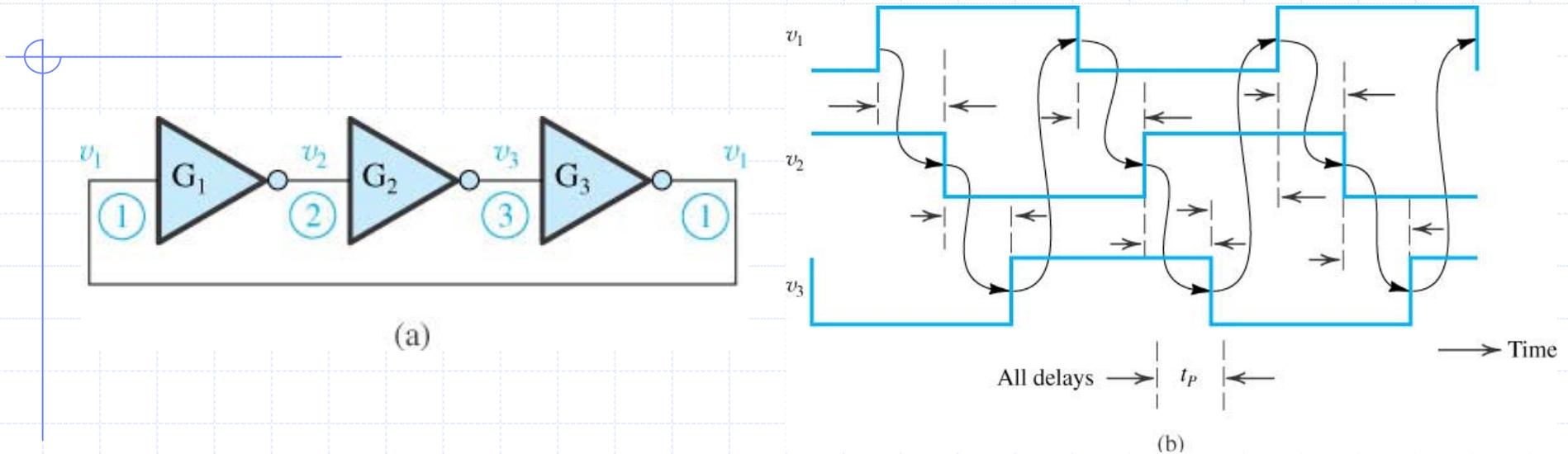

**Figure 11.16** (a) A ring oscillator formed by connecting three inverters in cascade. (Normally at least five inverters are used.)

(b) The resulting waveform. Observe that the circuit oscillates with frequency  $1/6t_p$ .

- ◆ The ring oscillator is formed by connecting an odd number of inverters in a loop.
- ◆ Usually at least five inverters are used.
- ◆ A ring with  $N$  inverters will oscillate with period of  $2Nt_p$  and frequency  $1/2Nt_p$ .
- ◆ Ring oscillator provides a relatively simple means for measuring the inverter propagation delay.