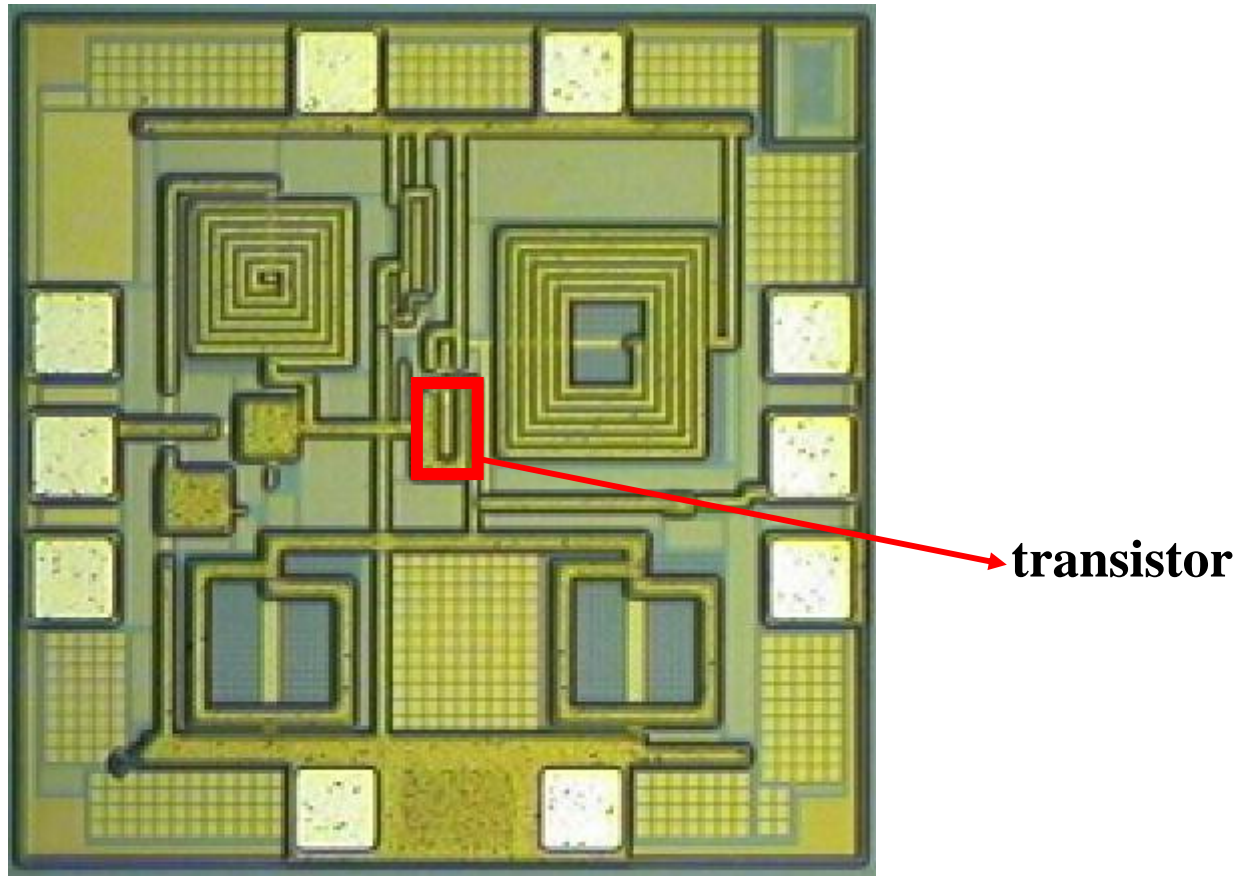


# Second-Order Active Filters Based on Inductor Replacement


---

- Obtained by replacing the inductor  $L$  in the  $LCR$  resonator with an op amp- $RC$  circuit that has an inductive input impedance.



2GHz LNA

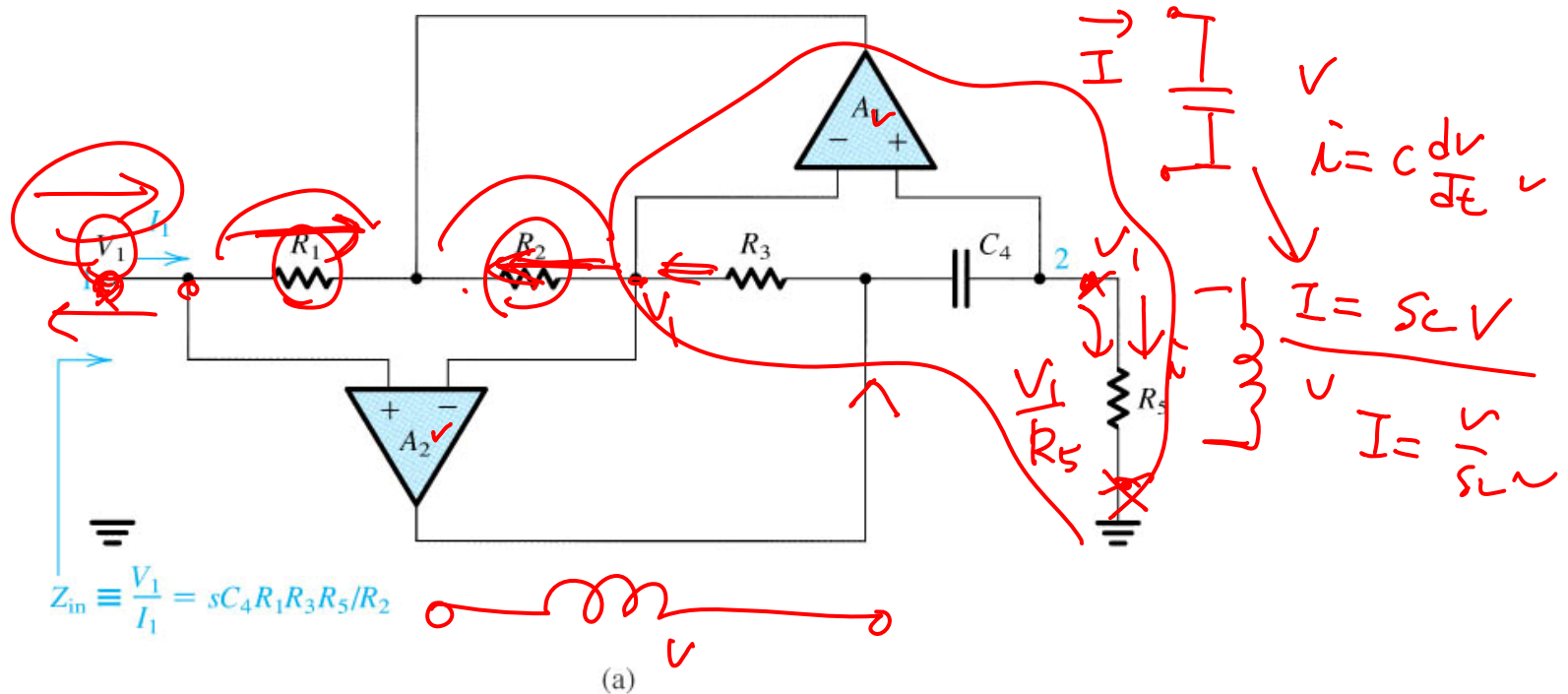
# The Antoniou Inductance-Simulation Circuit




- Invented by A. Antoniou.
- If the circuit is fed at its input (node 1) with a voltage source  $V_1$  and the input current is denoted  $I_1$ , (for ideal op amps)

$$Z_{in} \equiv \frac{V_1}{I_1} = \frac{sC_4 R_1 R_3 R_5}{R_2} \qquad L = \frac{C_4 R_1 R_3 R_5}{R_2}$$

$$i = v / sa \parallel$$

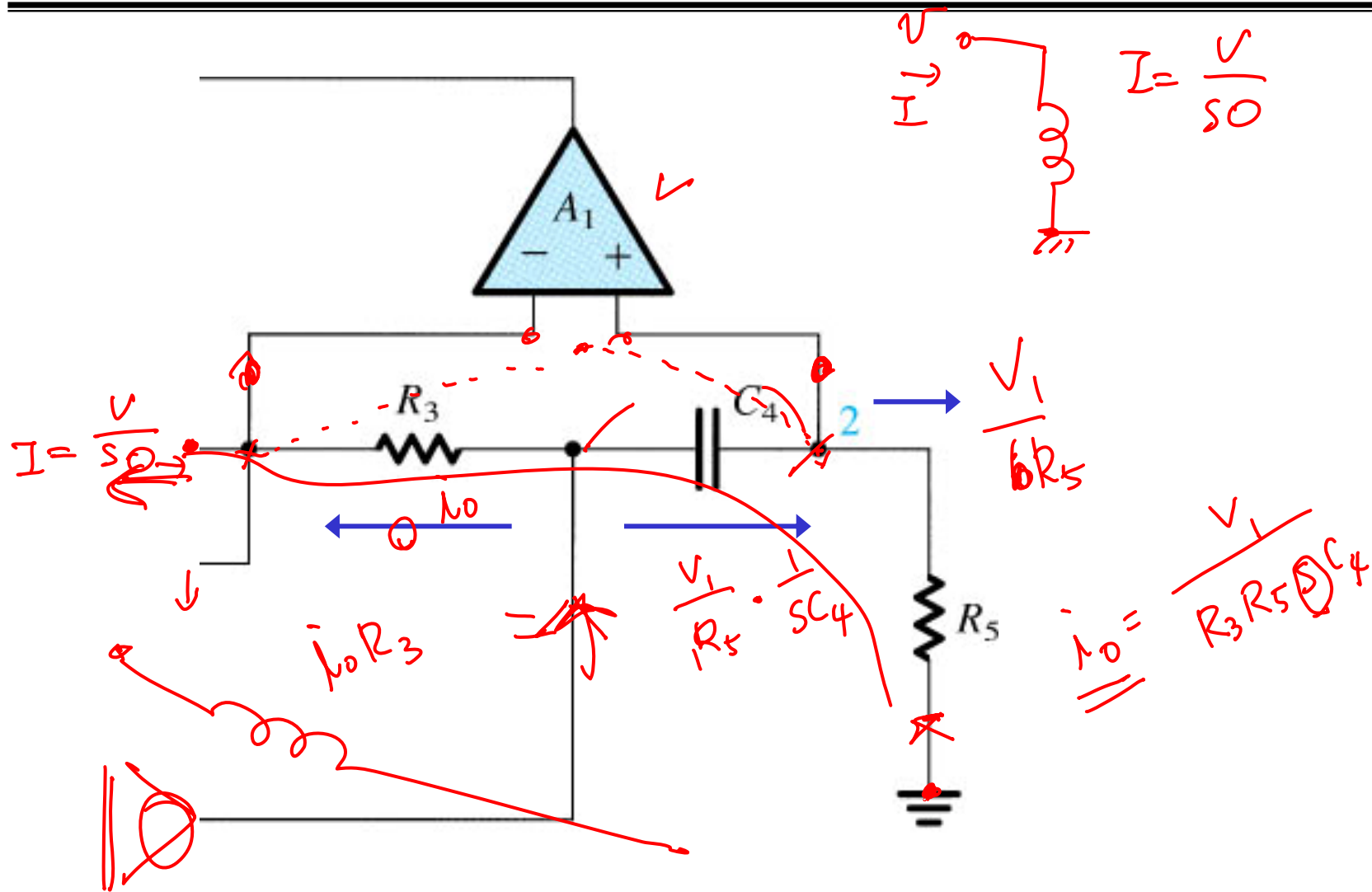
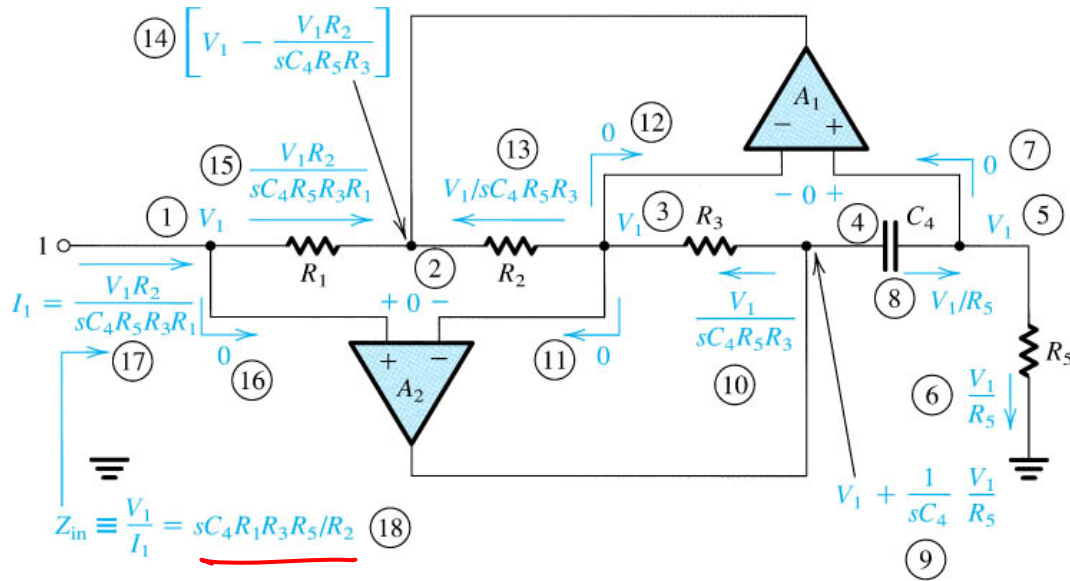
# The Antoniou Inductance-Simulation Circuit



① Assuming ideal op amps.

② Analysis begins at node 1, which is assumed to be fed by a voltage source  $V_1$ .


③ Analysis proceeds step by step, with the order of the steps indicated by the circled numbers.

- The design of this circuit is usually based on selecting

$$\underline{R_1=R_2=R_3=R_5=R} \text{ and } \underline{C_4=C} \rightarrow \underline{L=CR^2}$$

- Convenient values are selected for  $C$  and  $R$  to yield the desired inductance value  $L$ .

# The Op Amp-RC Resonator

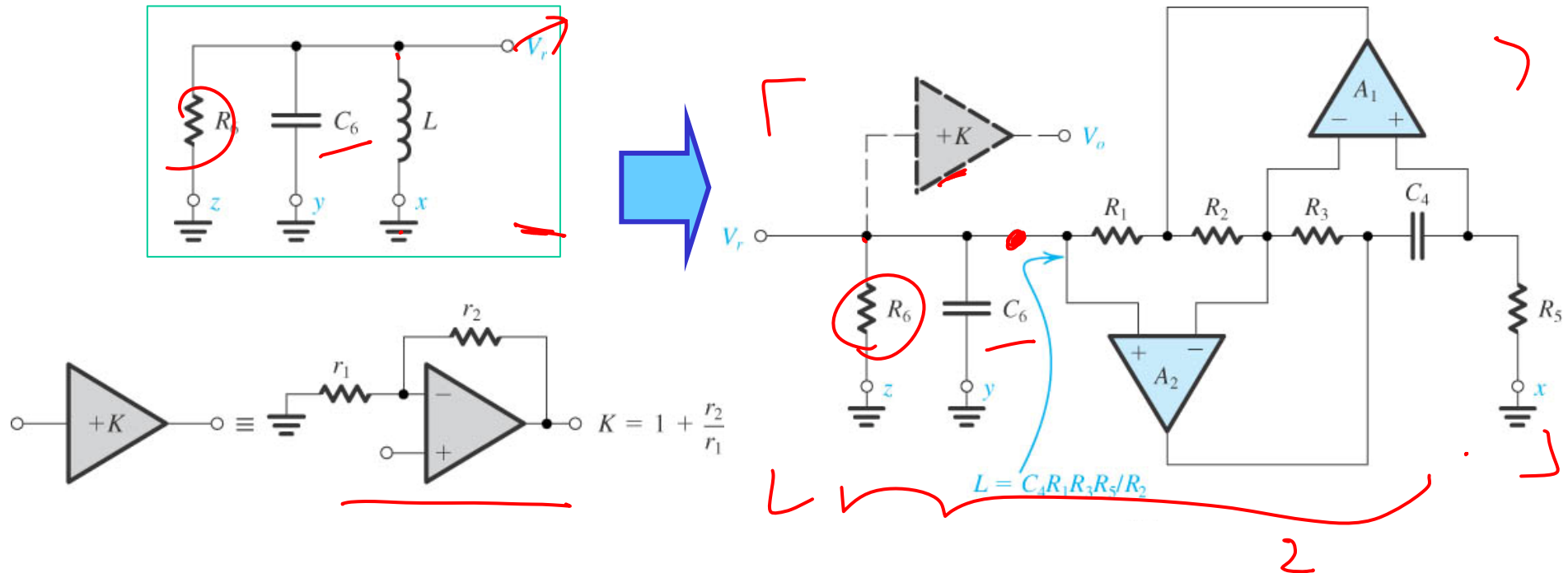

- Replacing the inductor  $L$  with a simulated inductance realized by the Antoniou circuit  $\rightarrow$  Second-order resonator.
- Pole frequency

$$\omega_o = \frac{1}{\sqrt{LC_6}} = \frac{1}{\sqrt{C_4 C_6 R_1 R_3 R_5 / R_2}}$$

# The Op Amp-RC Resonator



- Pole Q factor

$$Q = \omega_o C_6 R_6 = R_6 \sqrt{\frac{C_6}{C_4} \frac{R_2}{R_1 R_3 R_5}}$$

- Usually selects  $C_4 = C_6 = C$   
and  $R_1 = R_2 = R_3 = R_5 = R$ ,  
which results in

$$\omega_o = \frac{1}{CR}$$

$$Q = \frac{R_6}{R}$$


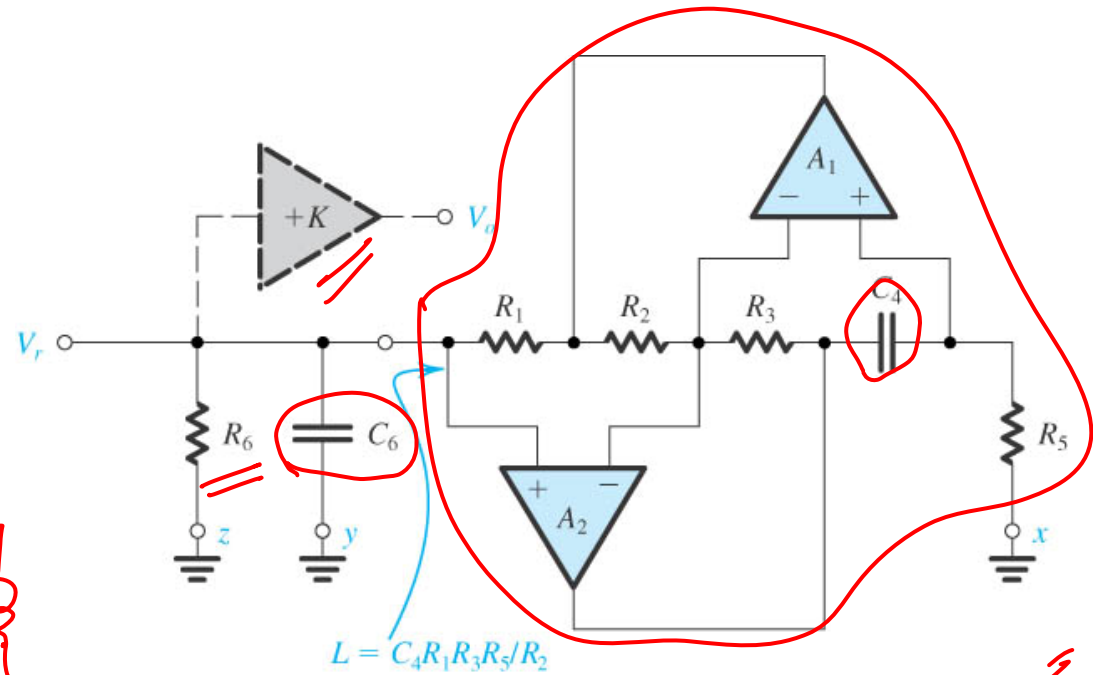
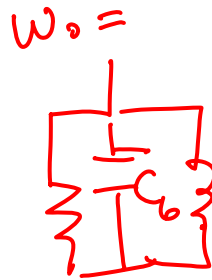


- Select a practically convenient value for  $C$ 
  - Determine the value of  $R$  to realize a given  $\omega_o$
  - Determine the value of  $R_6$  to realize a given  $Q$
- Op-amp buffer amplifier is used at the output to eliminate loading effect.
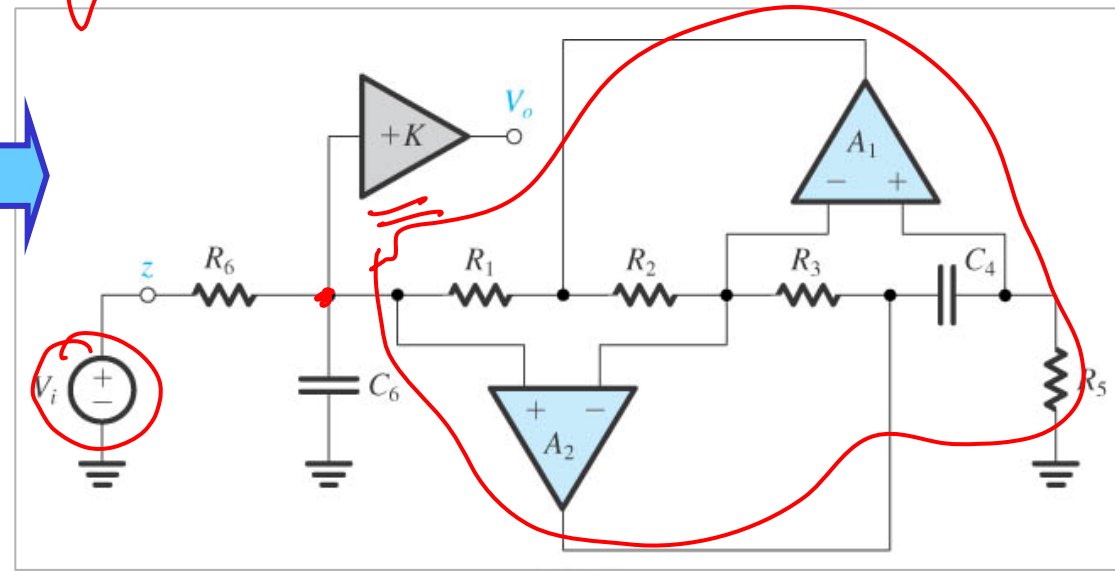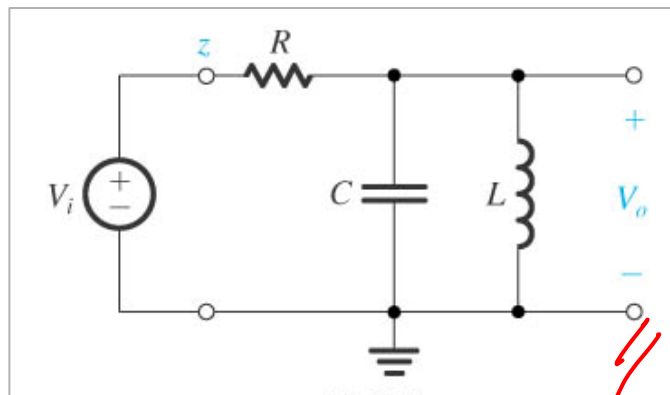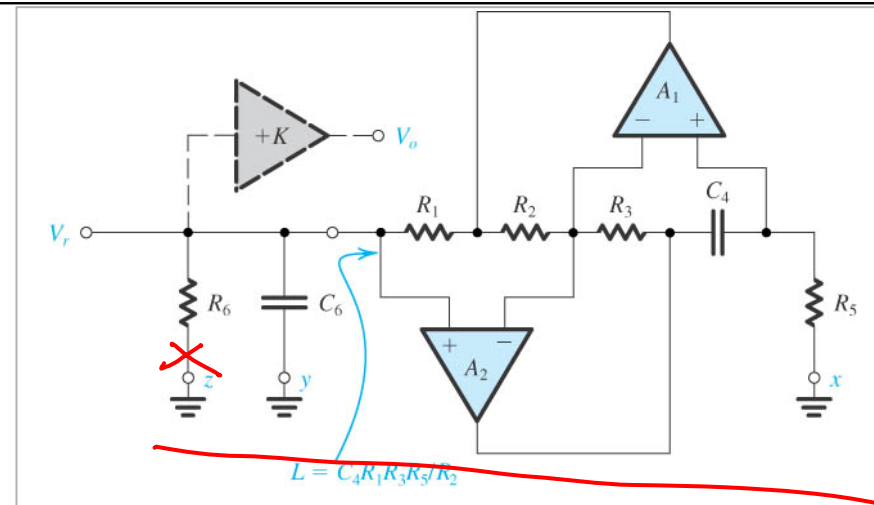
# Realization of the Various Filter Types




□ Bandpass function.

→ disconnect node  $z$  from ground and connect it to the signal source  $V_i$


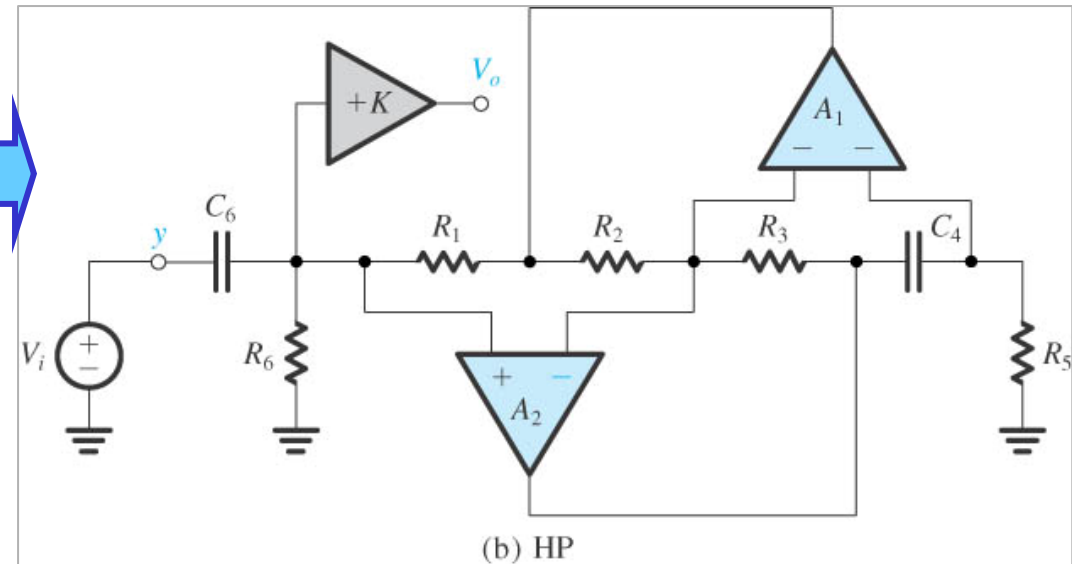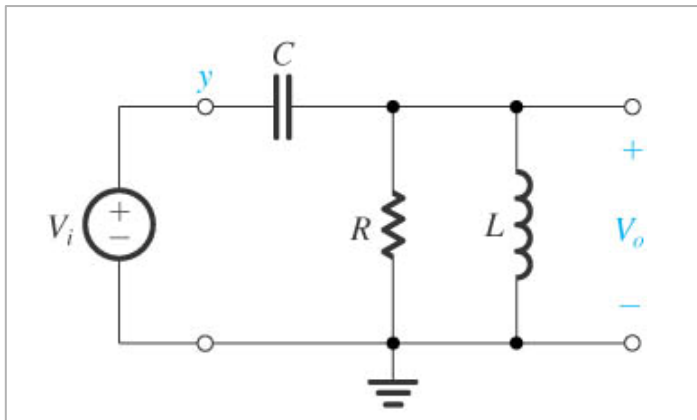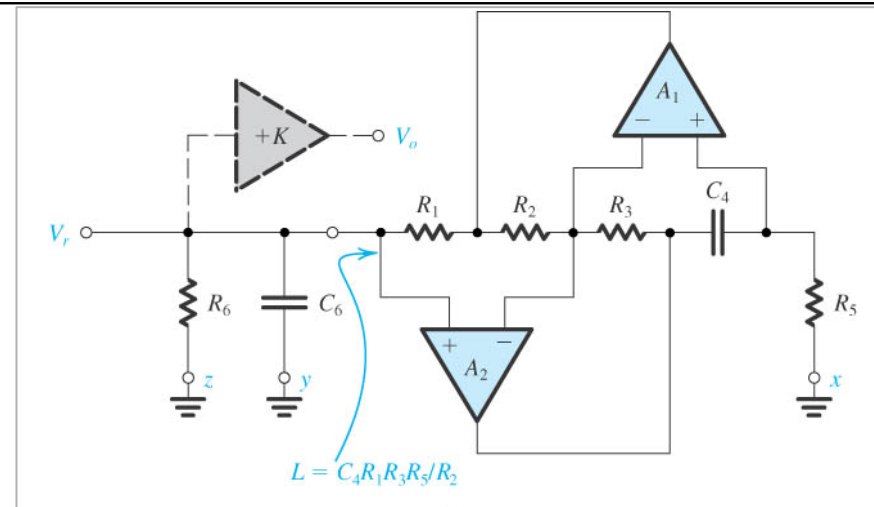
# Realization of the Various Filter Types




- High-pass function
  - inject  $V_i$  to node  $y$





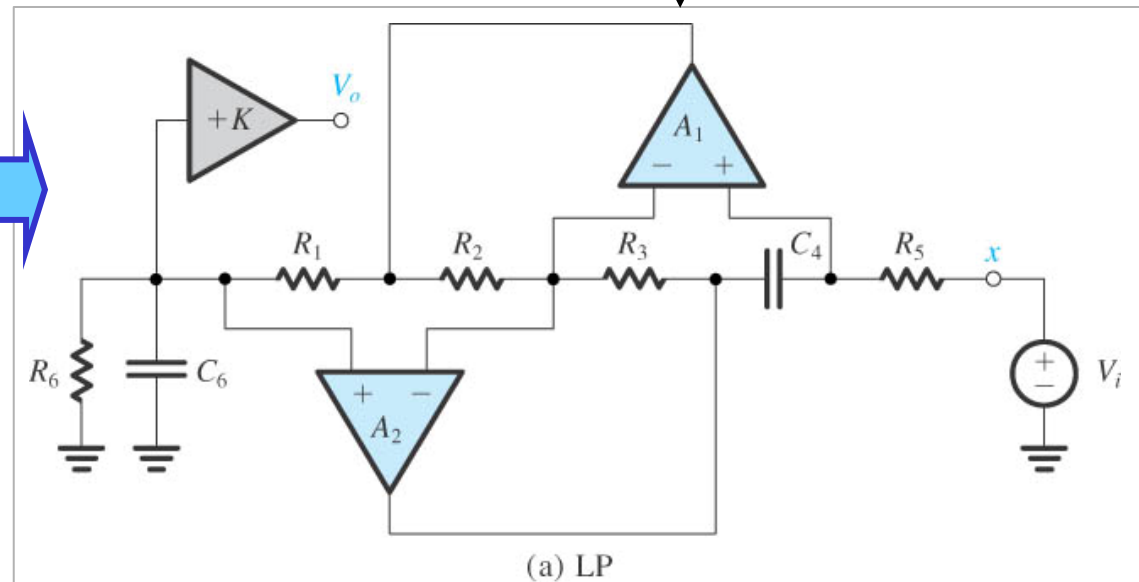
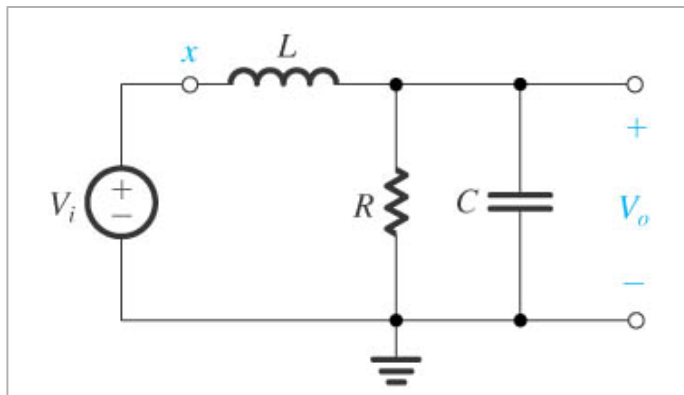
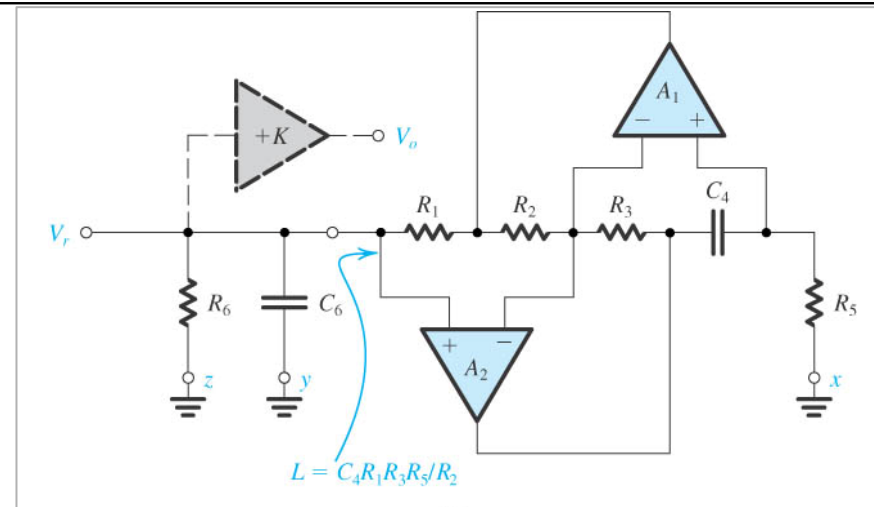
# Realization of the Various Filter Types

- Low-pass function
  - inject  $V_i$  to node  $x$


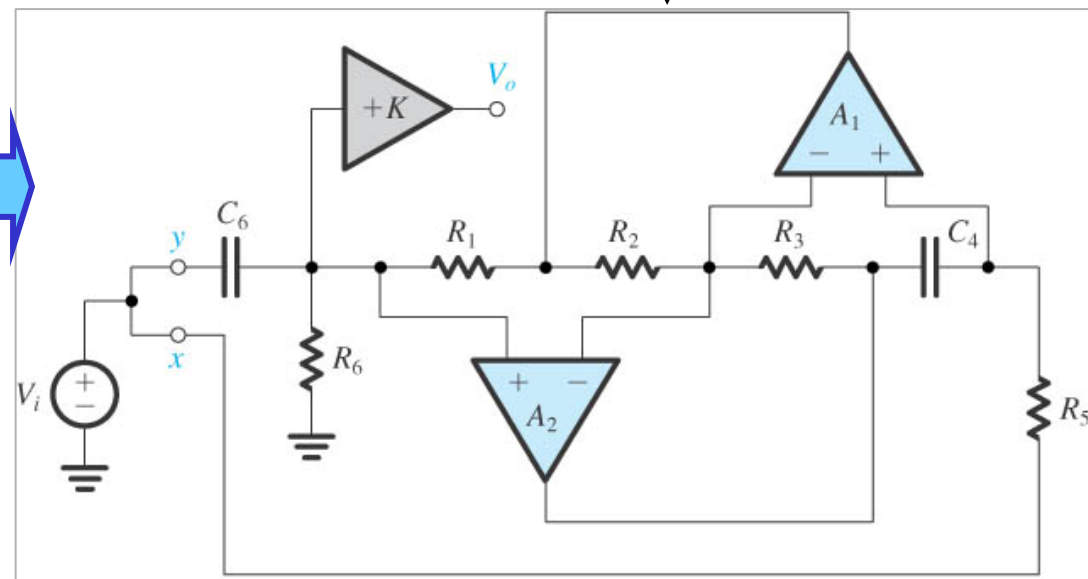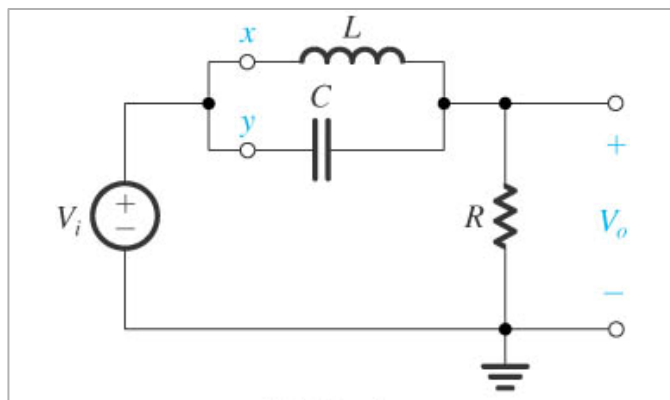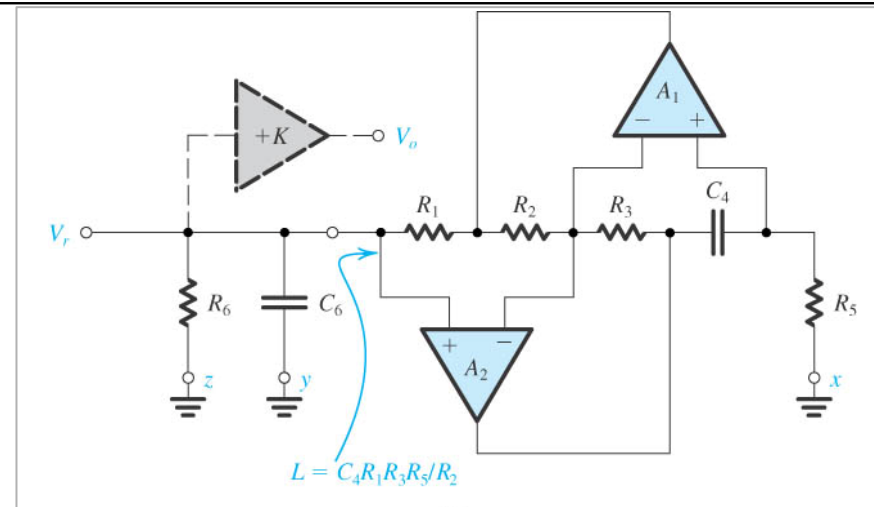
# Realization of the Various Filter Types

- Regular Notch function ( $\omega_n = \omega_o$ ).
- Feed  $V_i$  to node  $x$  and  $y$



# The All – Pass Circuit

- An all-pass function with a flat gain of unity


$$AP = 1 - (\text{BP with a center-frequency gain of } 2) \rightarrow \text{complementary}$$

$$T' = 1 - T$$

- All-pass circuit with unity flat gain is the **complement** of the bandpass circuit with a center-frequency gain of 2.

- A simple procedure for obtaining the complement of a given linear circuit.

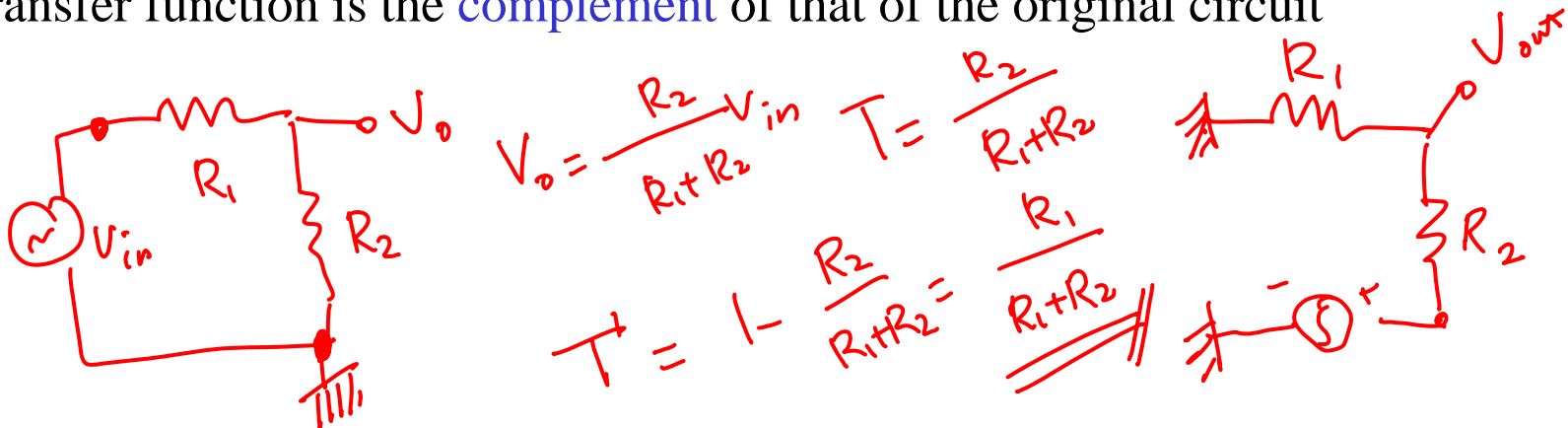: **Interchanging input and ground** in a linear circuit generates a circuit whose transfer function is the **complement** of that of the original circuit



# The All – Pass Circuit

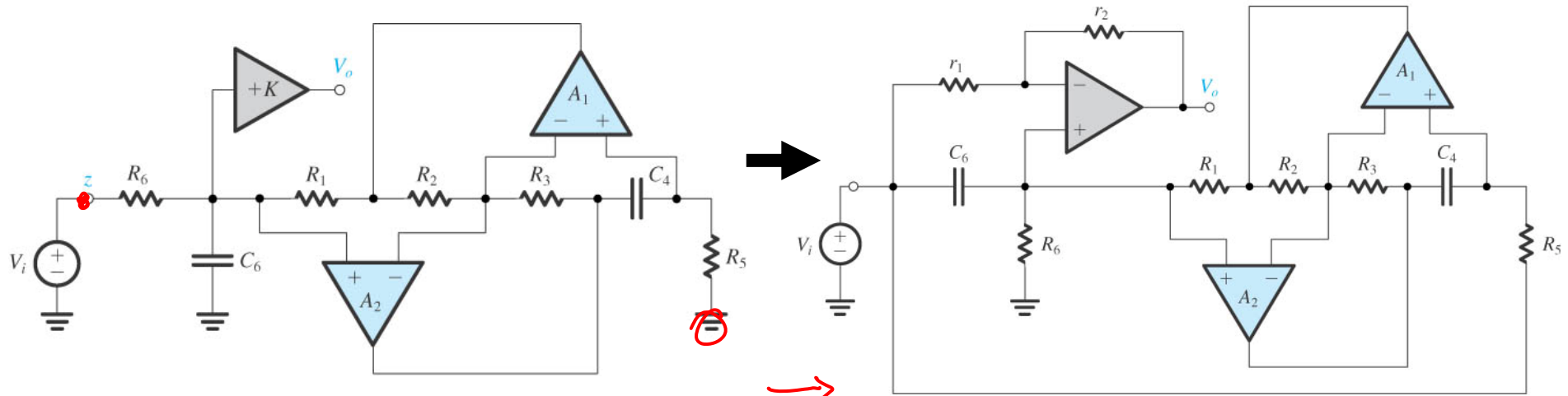


Fig. 12.22(c) Band-Pass 2

Fig. 12.22(g) All-Pass

- All pass filter implementation.

- ① Use the circuit of Fig. 12.22(c) to realize a BP with a gain of 2 by simply selecting  $K = 2$  and implementing the buffer amplifier with the circuit of Fig.12.21(c) with  $r_1 = r_2$ .
- ② Then interchange input and ground and thus obtain the all-pass circuit of Fig.12.22(g)


# Derivation of the Two-Integrator-Loop Biquad

- To derive the two-integrator-loop biquadratic circuit, start from the second-order high-pass transfer function HP

$$\frac{V_{hp}}{V_i} = \frac{Ks^2}{s^2 + s(\omega_o/Q) + \omega_o^2}$$


,  $K$  is the high-frequency gain
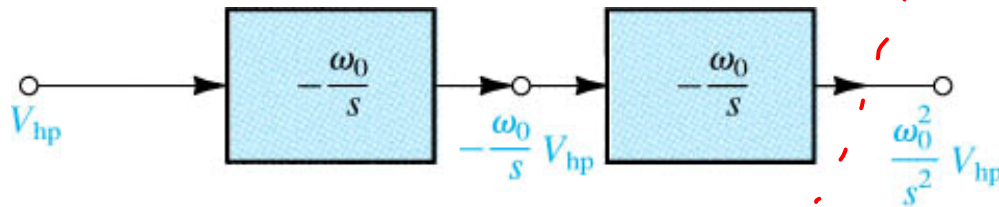
$$V_{hp} + \frac{1}{Q} \left( \frac{\omega_o}{s} V_{hp} \right) + \left( \frac{\omega_o^2}{s^2} V_{hp} \right) = KV_i$$




- To express  $V_{hp}$ ,
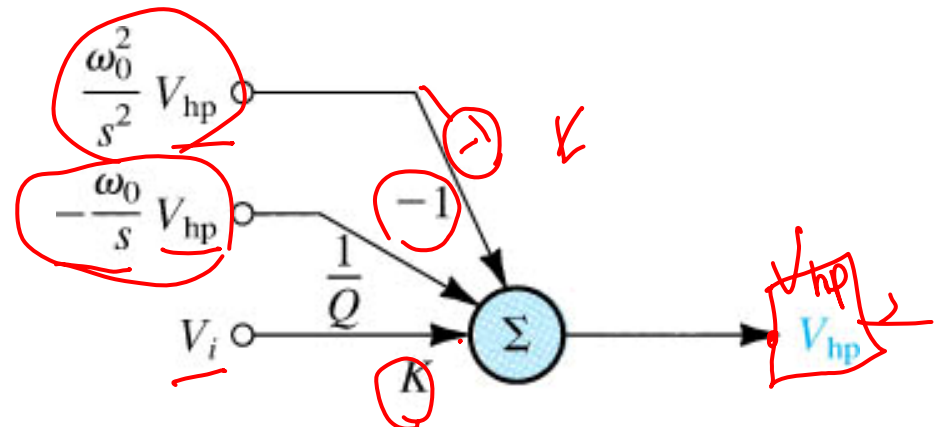
$$V_{hp} = KV_i - \frac{1}{Q} \frac{\omega_o}{s} V_{hp} - \frac{\omega_o^2}{s^2} V_{hp}$$



# Derivation of the Two-Integrator-Loop Biquad

- A complete block diagram realization

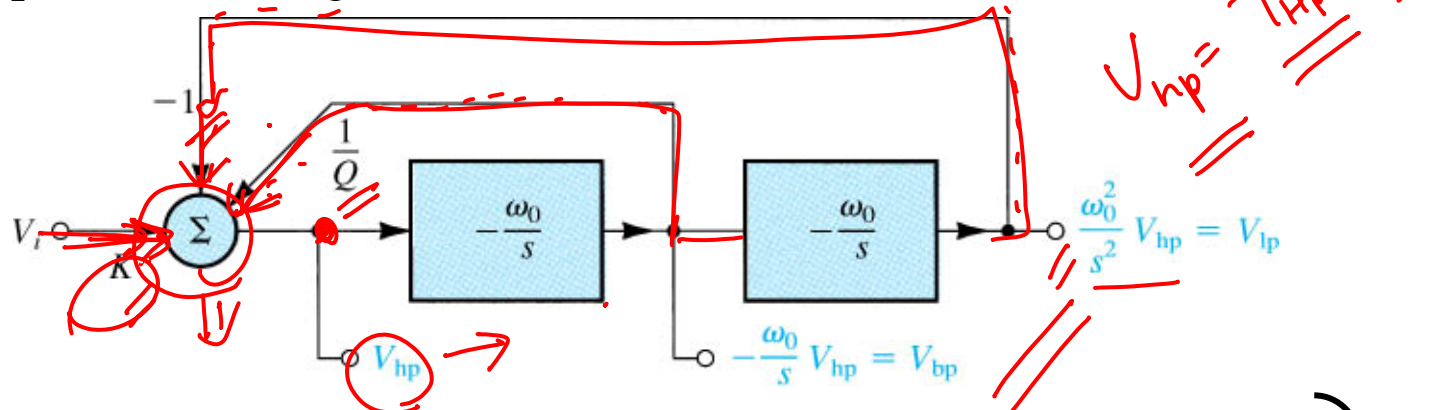

- From the output of the **summer**, obtained **high-pass** transfer function

$$T_{hp} \equiv \frac{V_{hp}}{V_i}$$

$\frac{Cs^2}{s^2 + as + b} \leftarrow \text{HP} \times -\frac{\omega_0}{s} =$

- From the output of the **first integrator**, obtained **bandpass** function

$$T_{bp}(s) \equiv \frac{(-\omega_0/s)V_{hp}}{V_i} = \frac{K\omega_0 s}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

$\left( \left( -\frac{\omega_0}{s} \right) \leftarrow \text{BP} \right)$


Simultaneously  
→ Universal  
active filter

- From the output of the **second integrator**, obtained **lowpass** function


$$T_{lp}(s) \equiv \frac{(\omega_0^2/s^2)V_{hp}}{V_i} = \frac{K\omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

$\rightarrow \text{LP}$
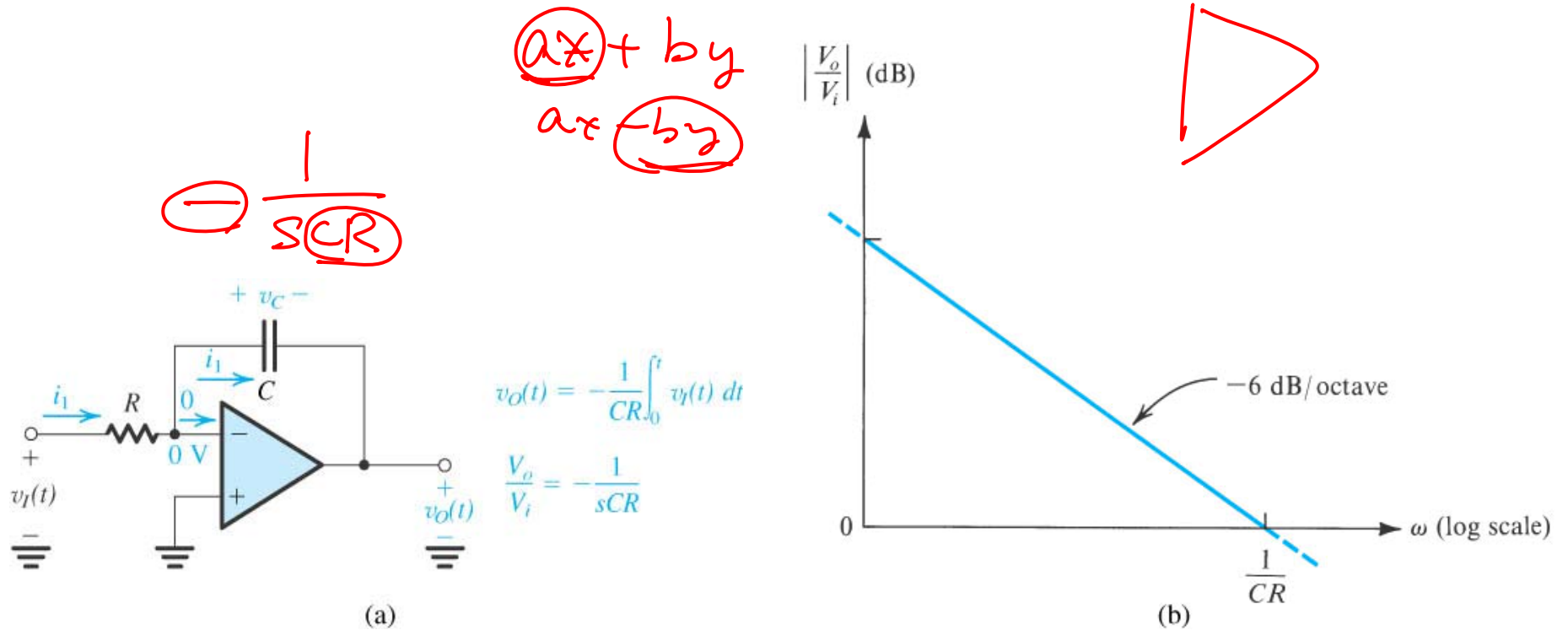
# Circuit Implementation using OP-AMP (Miller Integrator)



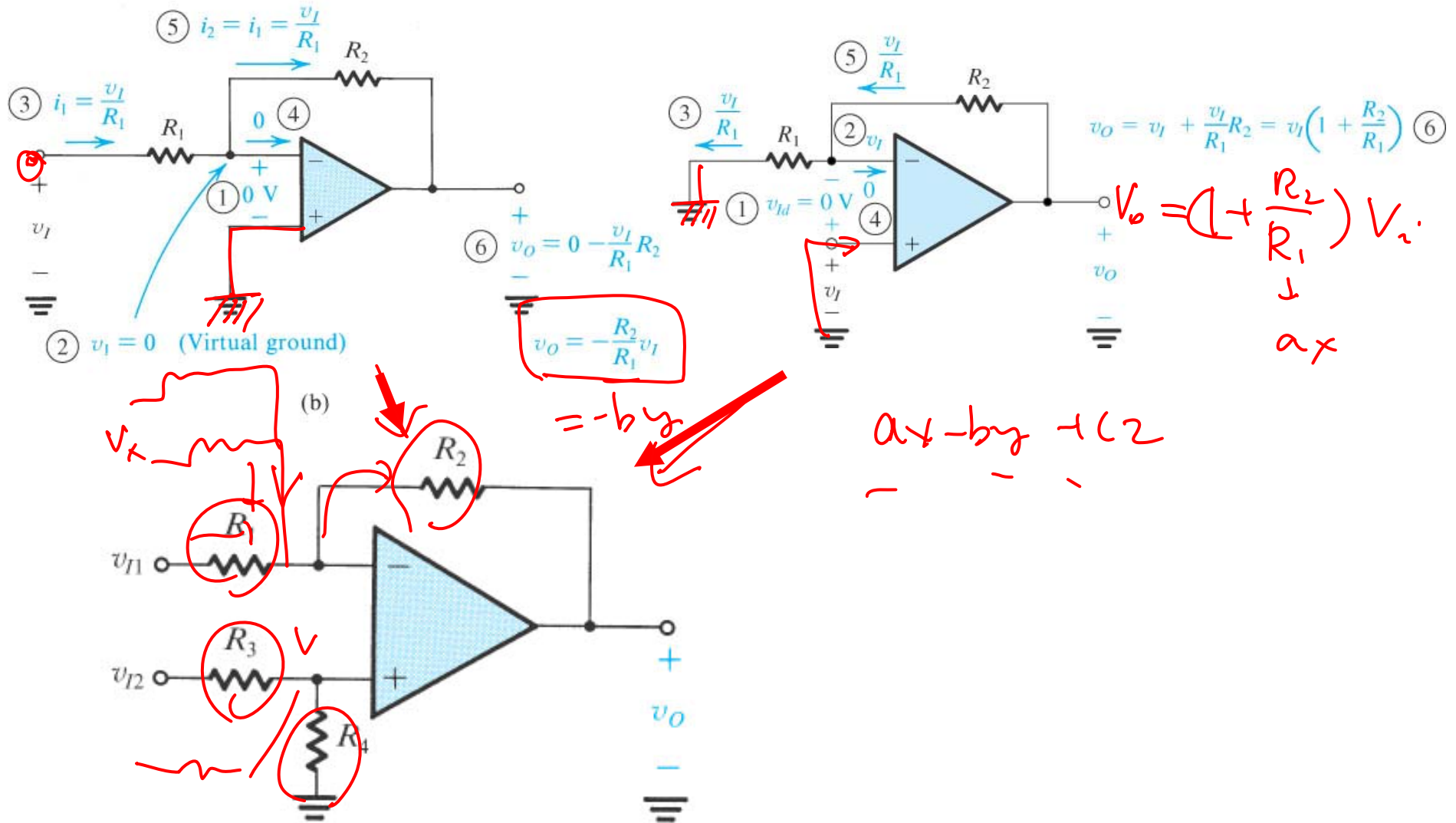
# Circuit Implementation using OP-AMP (Basic)





# Circuit Implementation

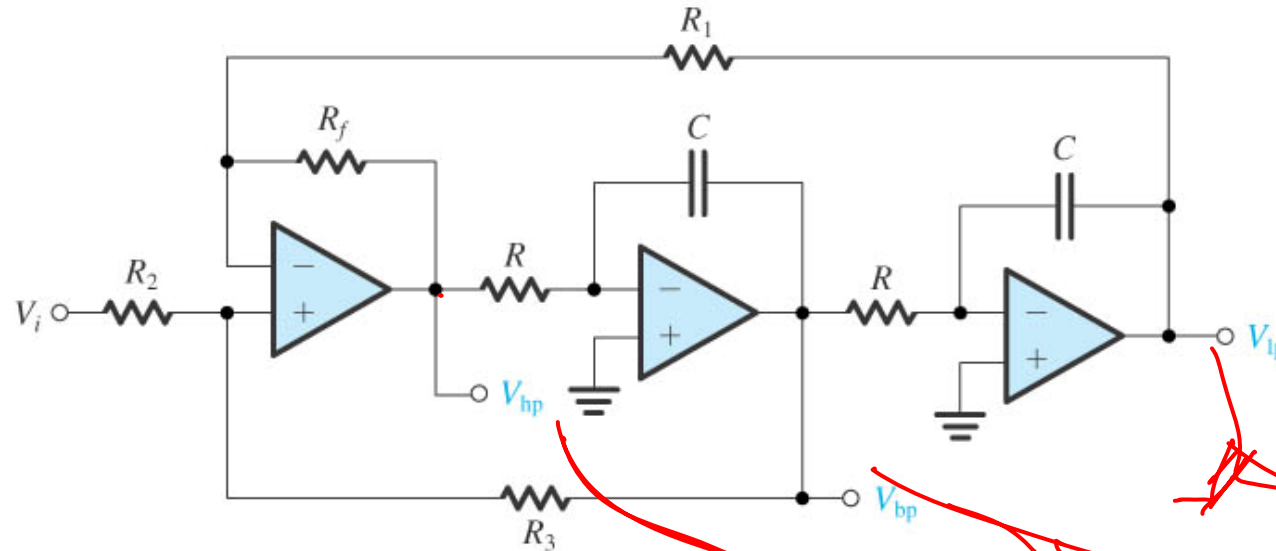

❑ The Kerwin-Huelsman-Newcomb circuit (KHN biquad)

– integrator → Miller integrator circuit having  $CR=1/\omega_0$ .

– summer → op-amp summing circuit

❑ Design the circuit

① Select suitable  $C$  and  $R$  for  $CR=1/\omega_0$ .

② Determine the values of the resistors associated with the summer

$$V_{hp} = \frac{R_3}{R_2 + R_3} \left( 1 + \frac{R_f}{R_1} \right) V_i + \frac{R_2}{R_2 + R_3} \left( 1 + \frac{R_f}{R_1} \right) \left( -\frac{\omega_o}{s} V_{hp} \right) - \frac{R_f}{R_1} \left( \frac{\omega_o^2}{s^2} V_{hp} \right)$$

# Circuit Implementation - Coefficients

- $$V_{hp} = \frac{R_3}{R_2 + R_3} \left( 1 + \frac{R_f}{R_1} \right) V_i + \frac{R_2}{R_2 + R_3} \left( 1 + \frac{R_f}{R_1} \right) \left( -\frac{\omega_o}{s} V_{hp} \right) - \frac{R_f}{R_1} \left( \frac{\omega_o^2}{s^2} V_{hp} \right)$$

→  $\frac{R_f}{R_1} = 1$

→  $\frac{R_3}{R_2} = 2Q - 1$  ( $\because R_f = R_1$ )


→  $K = 2 - \frac{1}{Q}$  ( $\because R_f = R_1, \frac{R_3}{R_2} = 2Q - 1$ )

→ the gain is fixed to this value

$$V_{hp} = KV_i - \frac{1}{Q} \frac{\omega_o}{s} V_{hp} - \frac{\omega_o^2}{s^2} V_{hp}$$

*Handwritten notes:  $\omega_o$  in a box,  $R_1, R_2, R_3$  with arrows pointing to the original equation.*

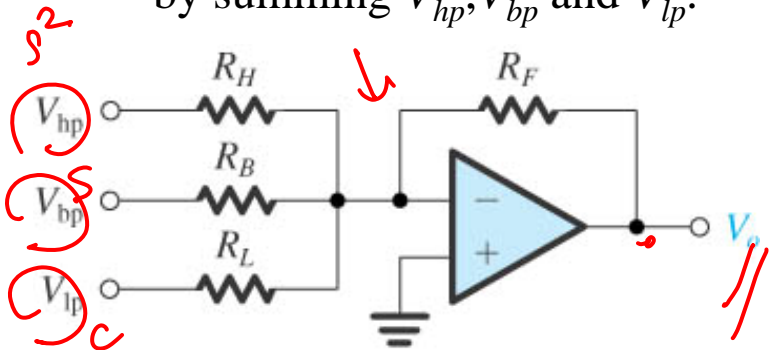- Realizing notch and all-pass functions by summing  $V_{hp}, V_{bp}$  and  $V_{lp}$ .





$$V_o = - \left( \frac{R_F}{R_H} V_{hp} + \frac{R_F}{R_B} V_{bp} + \frac{R_F}{R_L} V_{lp} \right)$$

$$= -V_i \left( \frac{R_F}{R_H} T_{hp} + \frac{R_F}{R_B} T_{bp} + \frac{R_F}{R_L} T_{lp} \right)$$

$$\frac{V_o}{V_i} = -K \frac{(R_F/R_H)s^2 - s(R_F/R_B)\omega_o + (R_F/R_L)\omega_o^2}{s^2 + s(\omega_o/Q) + \omega_o^2}$$

- Different zeros can be obtained by the appropriate selection of the values of the summing resistors
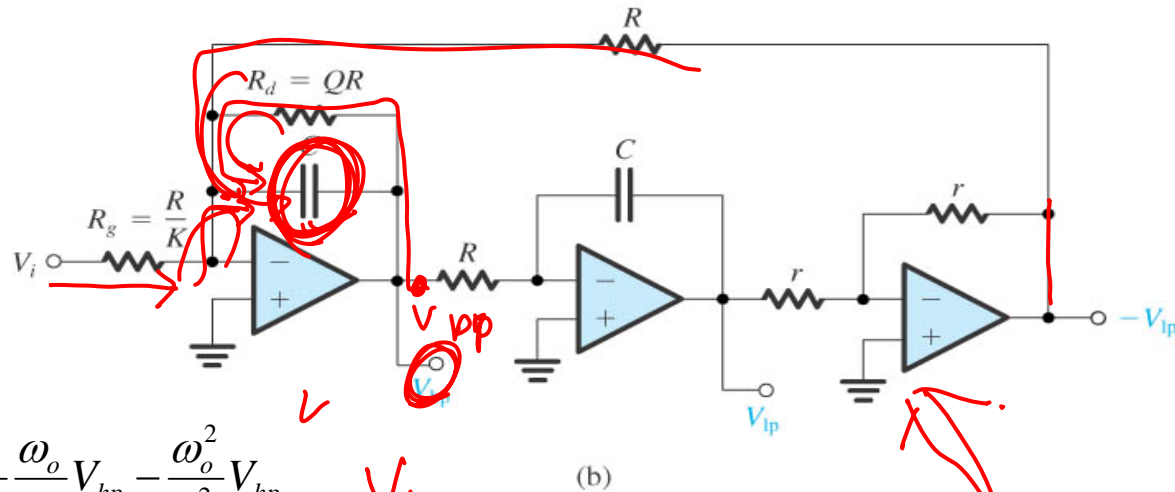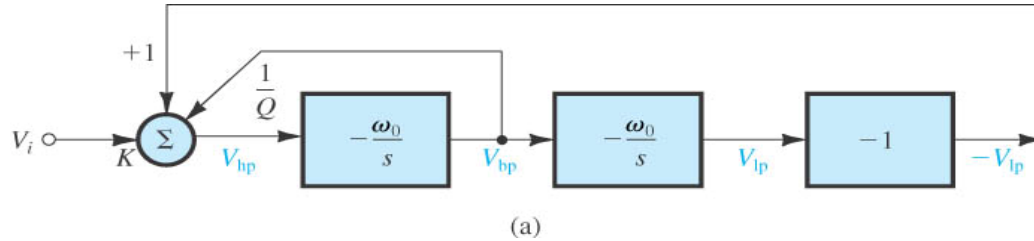
# An Alternative Two-Integrator-Loop Biquad Circuit




$$V_{hp} = KV_i - \frac{1}{Q} \frac{\omega_o}{s} V_{hp} - \frac{\omega_o^2}{s^2} V_{hp}$$

$$-\frac{\omega_o}{s} V_{hp} = -\frac{\omega_o}{s} KV_i - \frac{\omega_o}{s} \frac{1}{Q} V_{bp} + \frac{\omega_o}{s} V_{lp}$$

$$V_{bp} = -\frac{\omega_o}{s} KV_i - \frac{\omega_o}{s} \frac{1}{Q} V_{bp} - \left(-\frac{\omega_o}{s} V_{lp}\right) = -\frac{\omega_o}{s} \left\{ KV_i + \frac{1}{Q} V_{bp} + (-V_{lp}) \right\}$$

- **Tow-Thomas Biquad Circuit** : all in single-ended mode with the same sign  $\rightarrow$  no HP
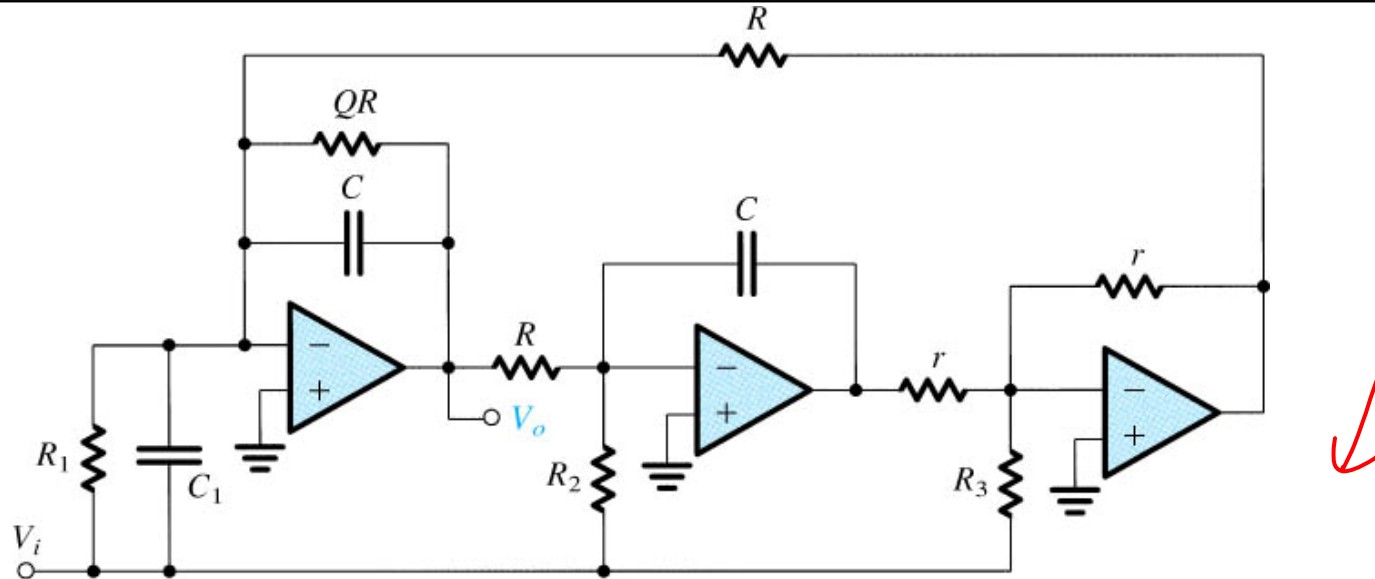
# An Alternative Two-Integrator-Loop Biquad Circuit




- Feedforward scheme is employed to realize the finite transmission zeros required for the notch and all-pass functions.
- The virtual grounds at the input of each of three amps permits the input signal to be fed to all the op functions.
- Transfer function is (Derive it)

$$\frac{V_o}{V_i} = - \frac{s^2 \left( \frac{C_1}{C} \right) + s \frac{1}{C} \left( \frac{1}{R} - \frac{r}{RR_3} \right) + \frac{1}{C^2 RR_2}}{s^2 + s \frac{1}{QCR} + \frac{1}{C^2 R^2}}$$

---

# **Additional Slides**

# Realization of the Notch Functions

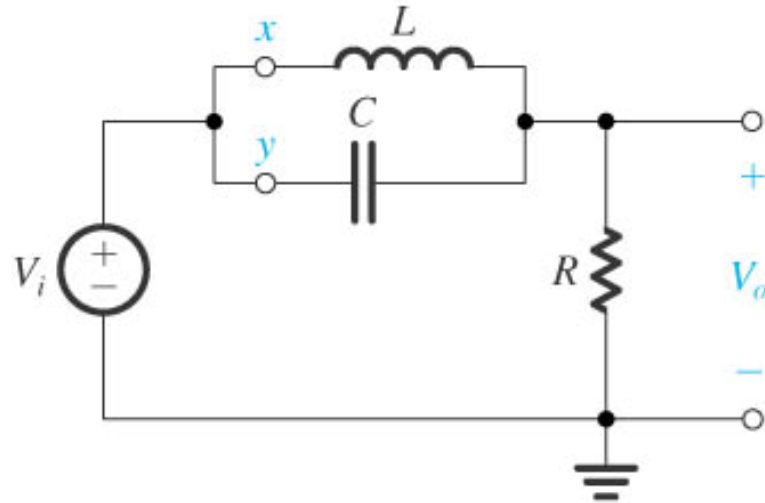

(e) Notch at  $\omega_0$


- The impedance of the LC circuit becomes infinite at  $\omega_0 = 1/\sqrt{LC}$   
 $\rightarrow$  zero transmission

- The resistor does not introduce zeros.

$$T(s) = a_2 \frac{s^2 + \omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

- To obtain arbitrary  $\omega_n$

$$L_1 C_1 = \frac{1}{\omega_n^2}$$

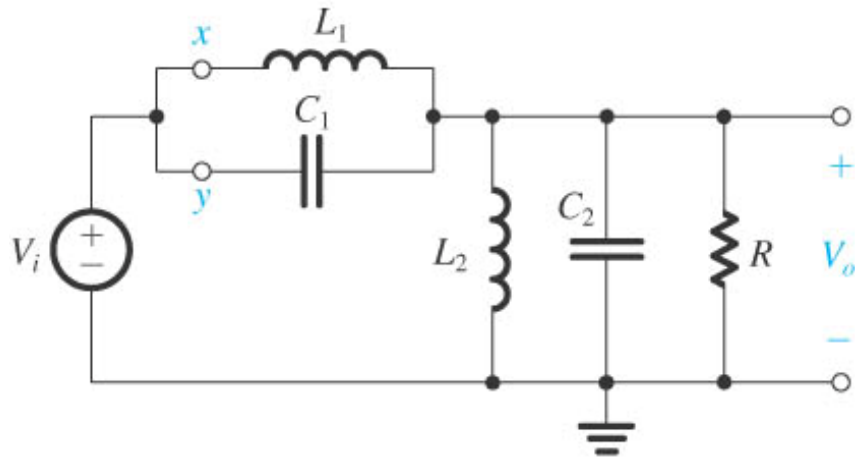

(f) General notch

- $L_1 C_1$  tank will introduce a pair of zeros at  $\pm j\omega_n$ , provided the  $L_2 C_2$  tank is not resonant at  $\omega_n$ .


- The natural modes have not been altered,  
 $C_1 + C_2 = C$  ;  $L_1 \parallel L_2 = L$

- It is obtained from the original LCR resonator by lifting part of L and part of C off ground


# Switched-Capacitor Filters
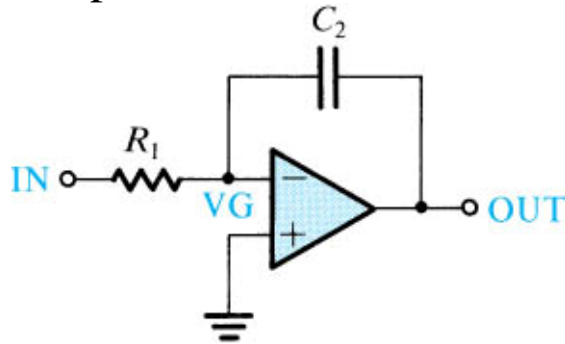
## □ The Basic Principle

- A capacitor switched between two circuit nodes is equivalent to a resistor




(a)

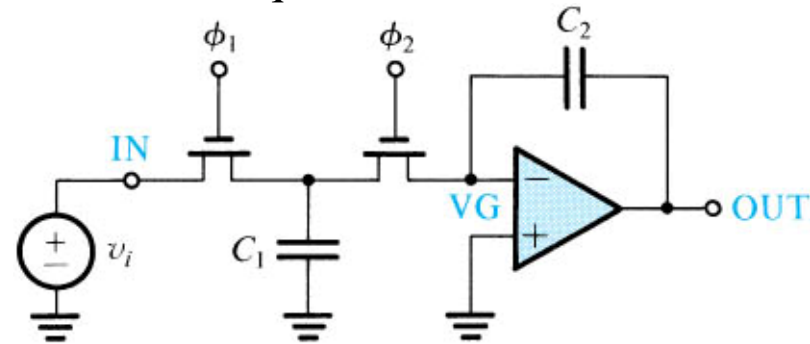

(b)

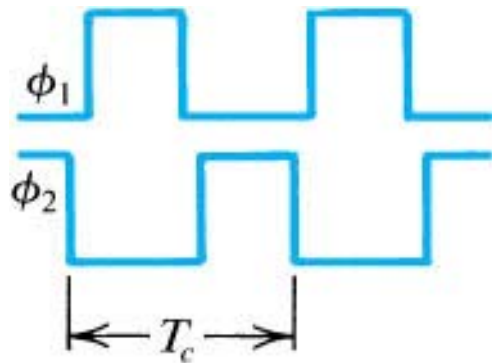- The two MOS switches are driven by a non-overlapping two-phase clock




(c)

- During  $\phi_1$ ,  $C_1$  charges up to  $v_i$

$$q_{C1} = C_1 v_i$$

- During  $\phi_2$ ,  $C_1$  is connected to the input of the op amp

# Switched-Capacitor Filters

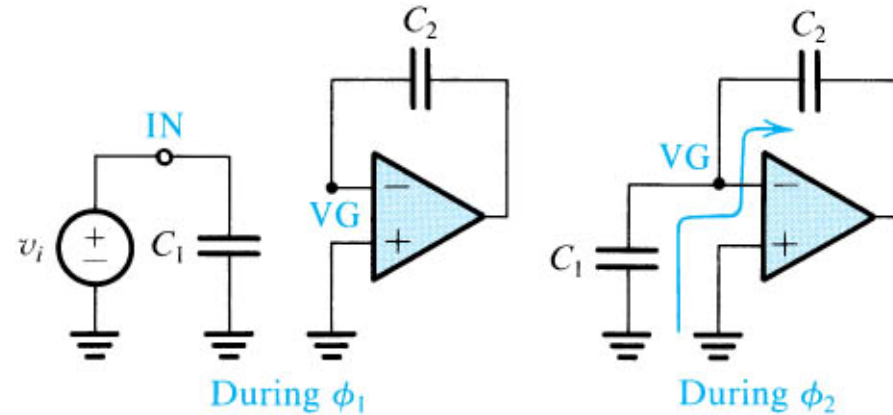

(d)

- During each  $T_c$ ,  $q_{C_1} = C_1 v_i$  is extracted from the input source and supplied to  $C_2$


$$i_{av} = \frac{C_1 v_i}{T_c}$$

$$R_{eq} \equiv \frac{v_i}{i_{av}} = \frac{T_c}{C_1}$$

$$\text{Time constant} = C_2 R_{eq} = T_c \frac{C_2}{C_1}$$



# Tuned Amplifiers

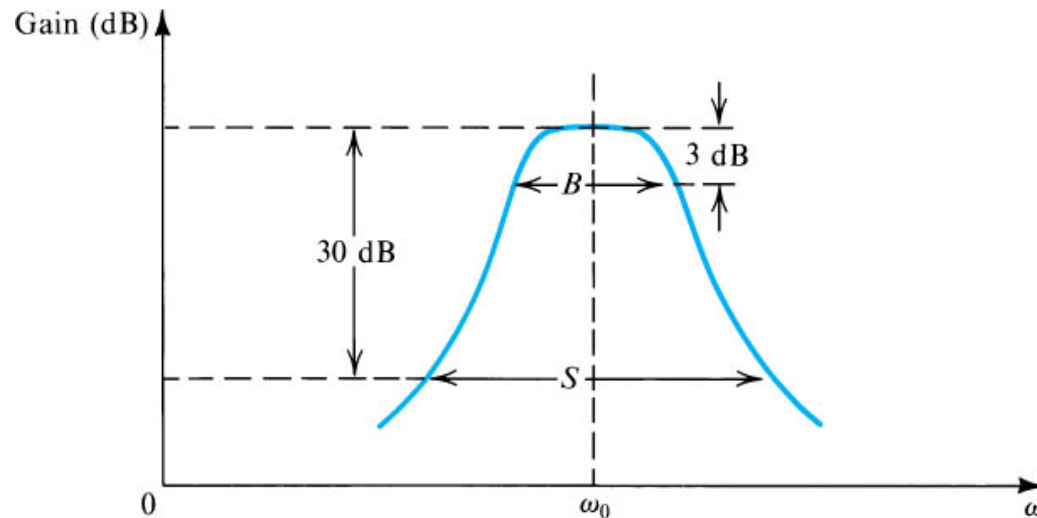

- $\omega_o$ =center frequency
- $B$ =3-dB bandwidth
- Skirt selectivity= $S/B$
- In many applications,  $B < 5\%$  of  $\omega_o \rightarrow$  narrow-band  
 $\rightarrow$  certain approximations

# Tuned Amplifiers

## □ The Basic Principle

- The use of a parallel LCR circuit as the load or at the input
- Single-tuned amplifier
- $R = R_L \parallel r_o$
- $C = C_L + \text{FET output capacitance}$  (usually very small)

$$\square V_o = -\frac{g_m V_i}{Y_L} = -\frac{g_m V_i}{sC + 1/R + 1/sL}$$


$$\frac{V_o}{V_i} = -\frac{g_m}{C} \frac{s}{s^2 + s(1/CR) + 1/LC}$$

$$\omega_o = 1/\sqrt{LC}, \quad B = 1/CR$$


$$Q \equiv \frac{\omega_o}{B} = \omega_o CR$$

$$\frac{V_o(j\omega_o)}{V_i(j\omega_o)} = -g_m R$$

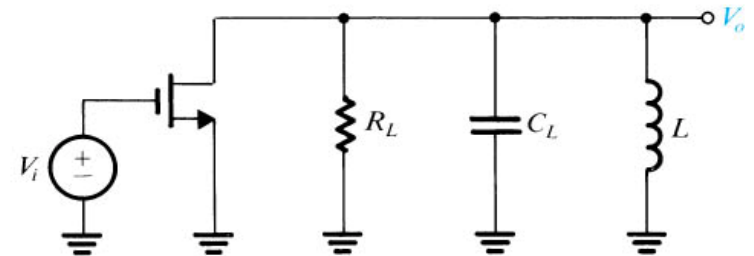- At resonance the reactance of  $L$  &  $C$  cancel out and the impedance of the parallel LCR circuit reduces to  $R$



(a)

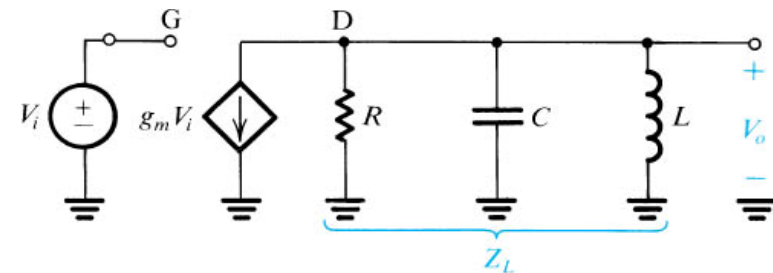

(b)

# Tuned Amplifiers

## □ Inductor Losses

$$Q_o \equiv \frac{\omega_o L}{r_s} : 50 \sim 200$$

- The analysis of a tuned amplifier is greatly simplified by representing the inductor loss by a parallel resistance  $R_p$

$$Y(j\omega_o) = 1/(r_s + j\omega_o L)$$

$$= \frac{1}{j\omega_o L} \frac{1}{1 - j(1/Q_o)} = \frac{1}{j\omega_o L} \frac{1 + j(1/Q_o)}{1 + (1/Q_o)^2}$$


$$Q_o \gg 1$$

$$Y(j\omega_o) \cong (1/j\omega_o L)(1 + j(1/Q_o))$$


$$Q_o = \frac{R_p}{\omega_o L}$$

$$R_p = \omega_o L Q_o = r_s Q_o^2$$

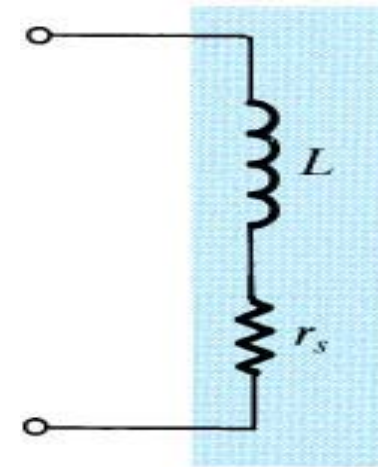- The coil Q factor poses an upper limit on the value of Q achieved by the tuned circuit




(a)

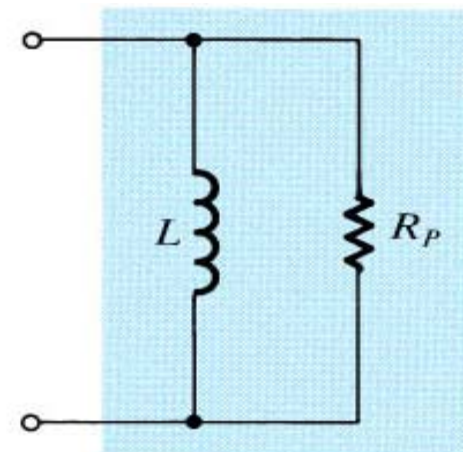

(b)

# Tuned Amplifiers

## □ Use of Transformers

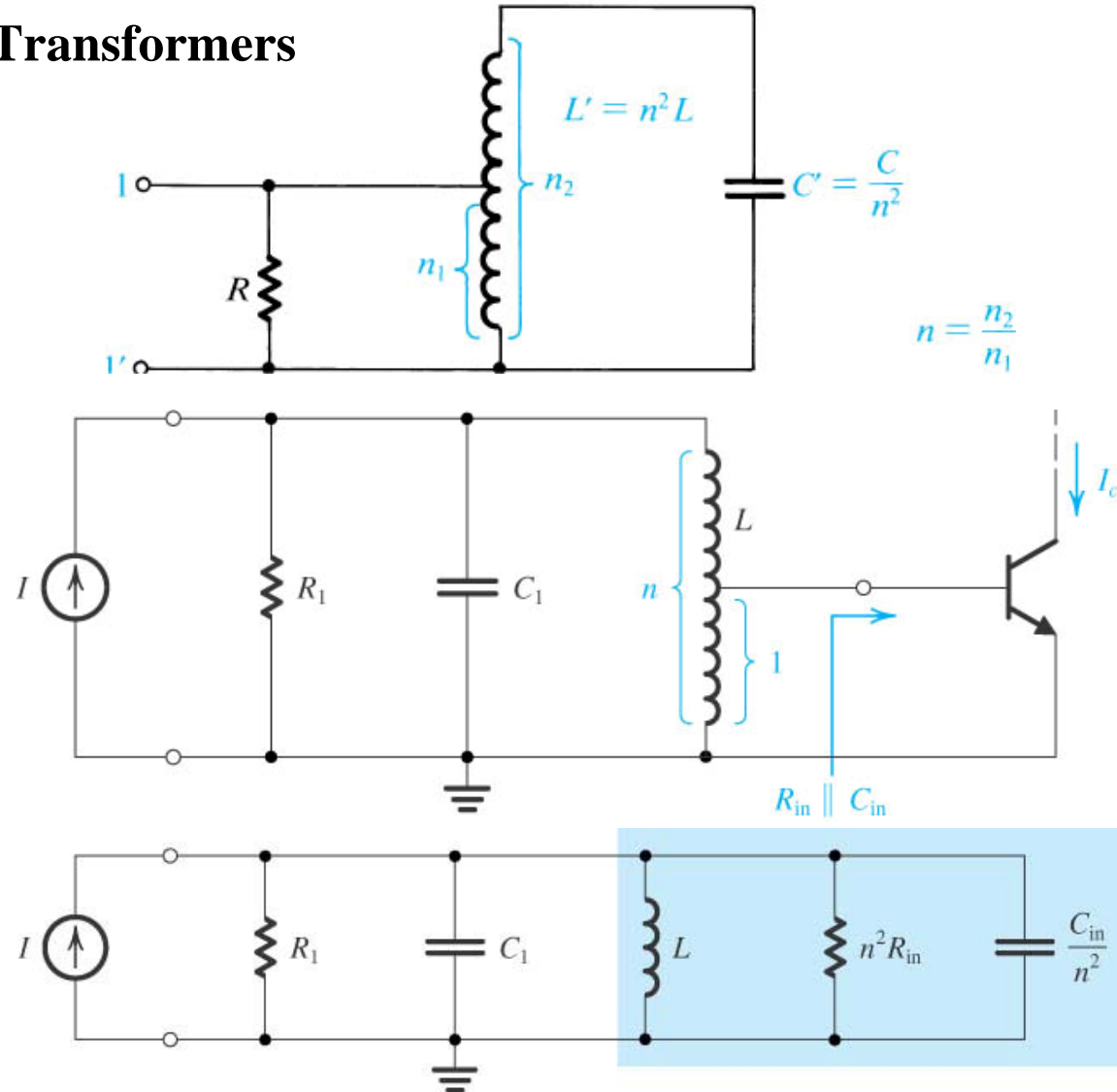


# Tuned Amplifiers
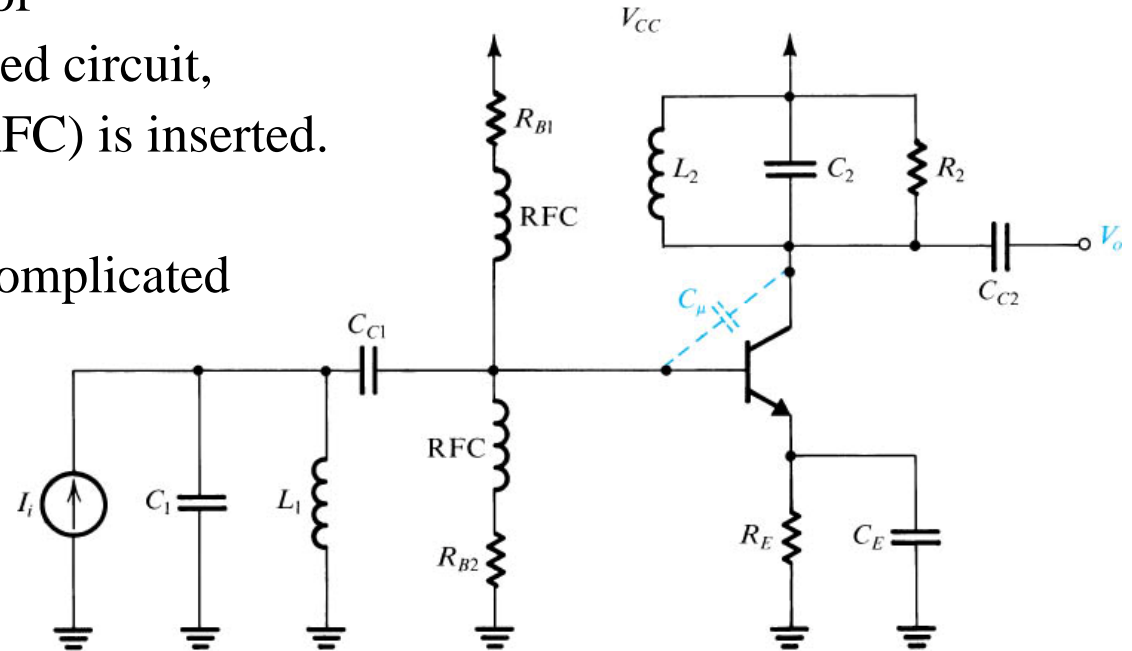
## ❑ Amplifiers with Multiple Tuned Circuits

- To avoid the loading effect of  $R_{B1}$  and  $R_{B2}$  on the input tuned circuit, a radio-frequency choke (RFC) is inserted.

- The analysis and design is complicated by the Miller effect due to  $C_{\mu}$ . The reflected impedance will cause detuning response of the input circuit.




- Method1: Neutralizing by using additional circuits arranged to feed back a current equal and opposite to that through  $C_{\mu}$ .
- Method2: Using circuits that do not suffer from Miller effect.

# Tuned Amplifiers
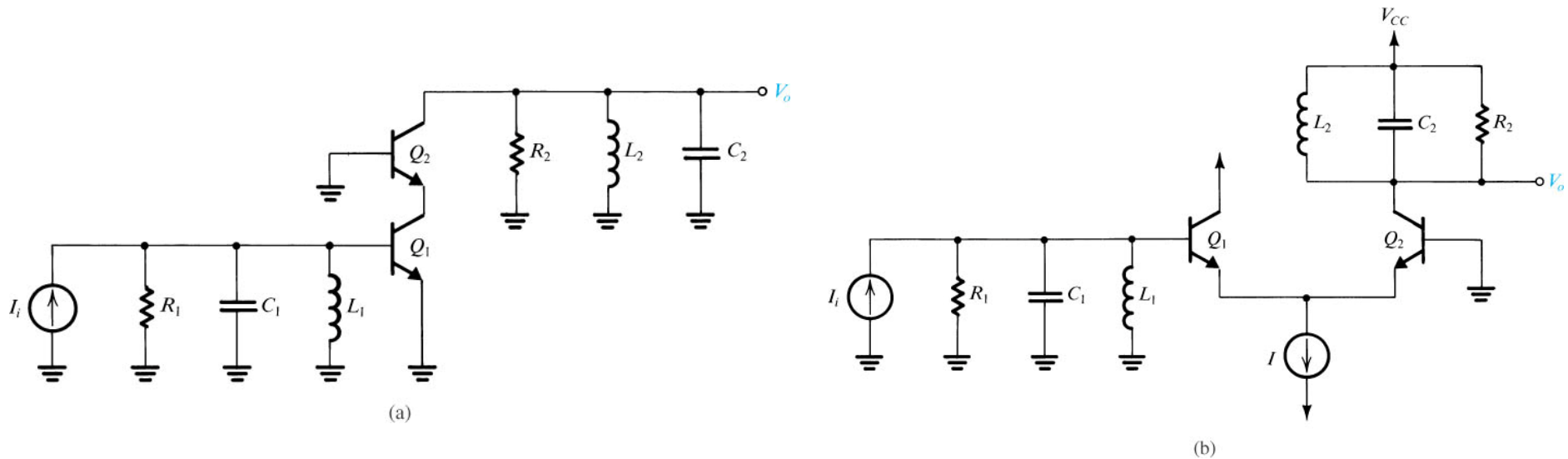
## □ The Cascode and the CC-CB Cascade


- No Miller effect: cascode and the common-collector, common-base cascade



# Tuned Amplifiers
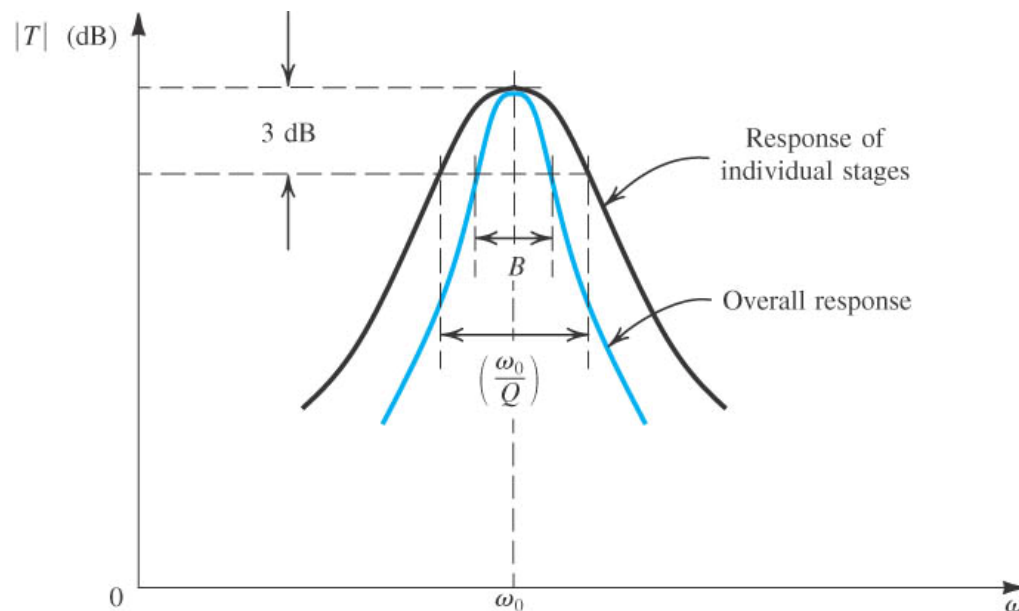
## □ Synchronous Tuning

- A tuned amplifier with multiple tuned circuits
- Assuming the overall response is the product of the individual responses
- N identical resonant circuits : synchronously tuned case



$$B = \frac{\omega_0}{Q} \sqrt{2^{1/N} - 1}$$

Bandwidth-shrinkage factor