

2007 Fall: Electronic Circuits 2

CHAPTER 14

Output Stages and Power Amplifiers



Introduction

- ◆ In this chapter, we will be covering...
 - Classification of Output Stages
 - Class A Output Stage
 - Class B Output Stage
 - Class AB Output Stage
 - Biasing the Class AB Circuit

14.1 Classification of Output Stages

- ◆ Output stages are classified according to the collector current waveform when an input signal is applied.
- ◆ When a sinusoidal input signal is applied,
 - Class A : biased at a current greater than the amplitude of signal current.
 - Class B : biased at zero dc current.
 - Class AB : an intermediate class between A and B.
biased at a nonzero dc current much smaller than the peak current of the sine-wave signal.

Thermal Issues

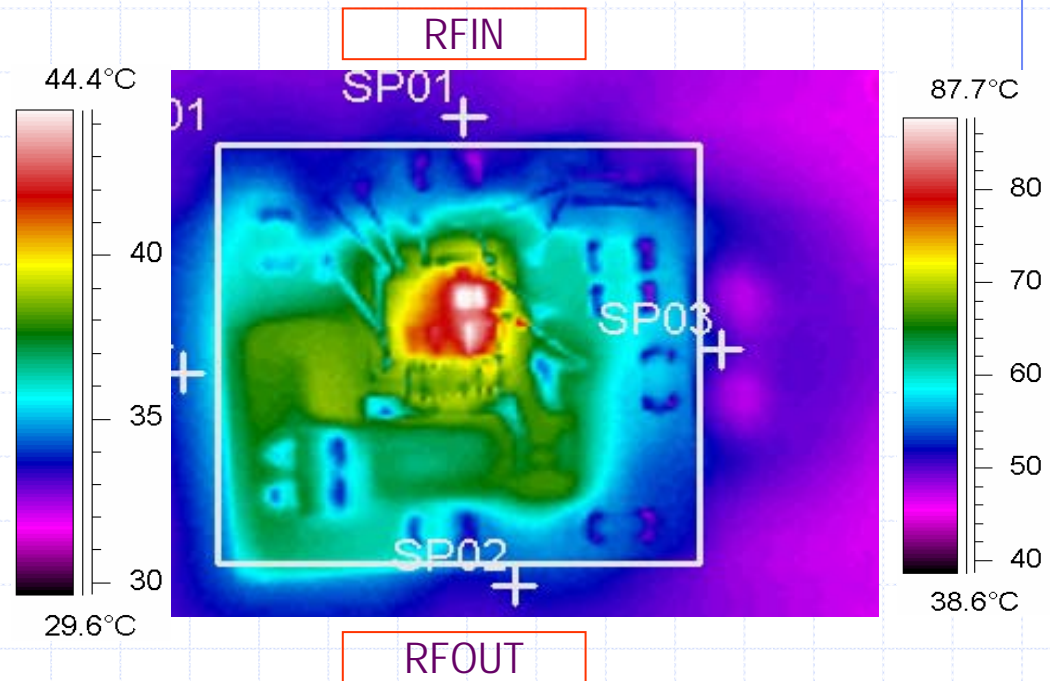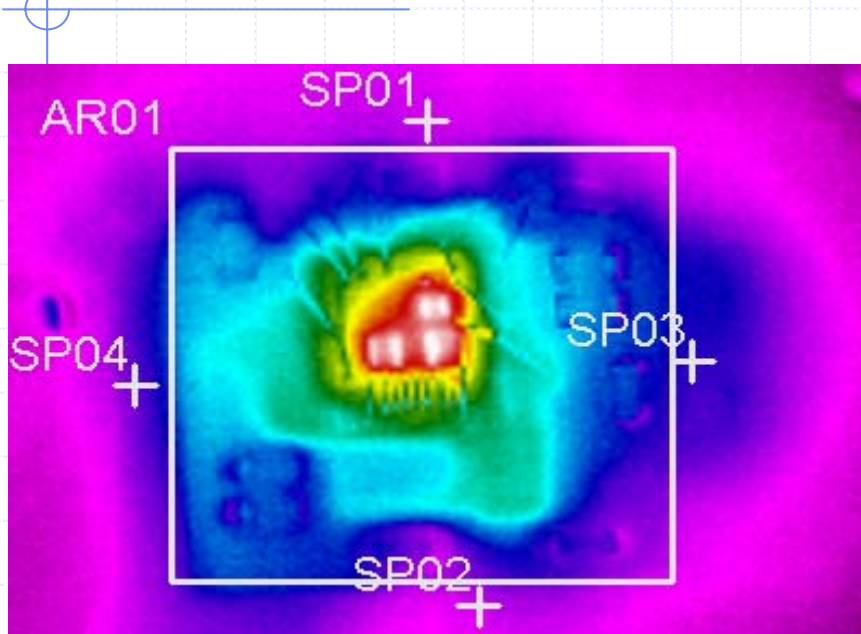


Dissipated Power (W)	T-junction (°C)	T-case (°C)
0.369	45.3	33.4

Dissipated Power (W)	T-junction (°C)	T-case (°C)
1.113	91.9	51.1

- ◆ Junction temperature
- ◆ Dissipated power = $P_{\text{supply}} - P_{\text{output}} \rightarrow$ Need to minimize P_d

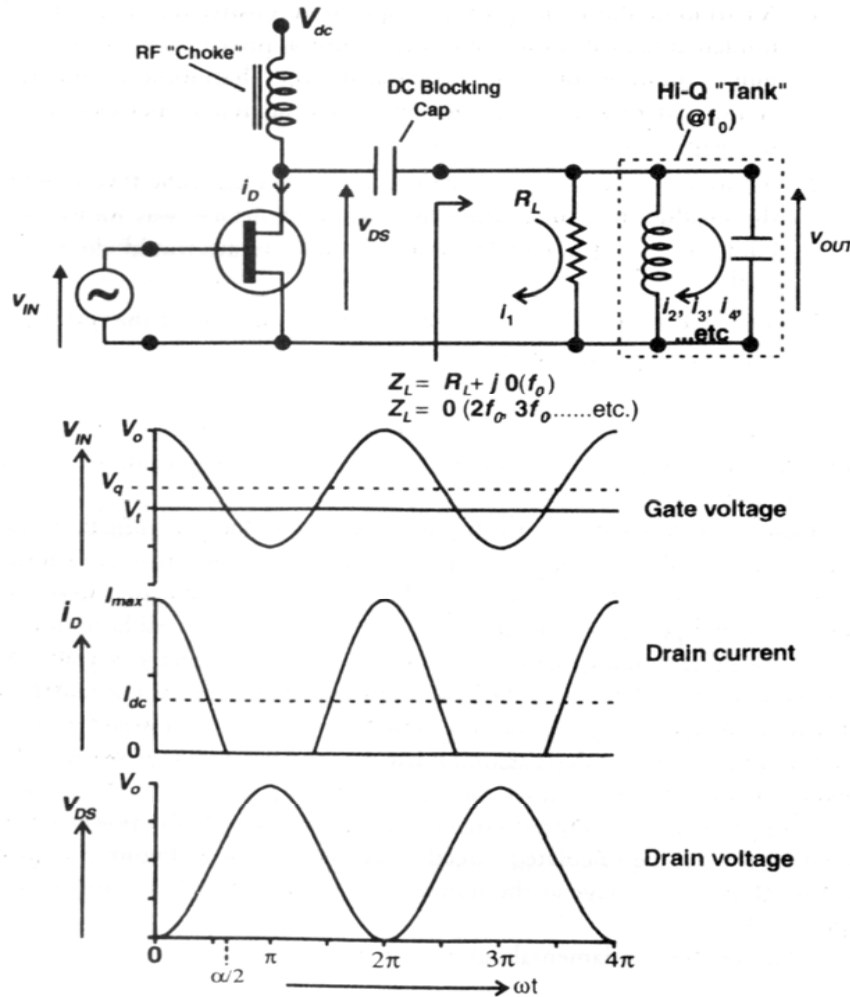Conduction Angle Dependence under Harmonic Short Termination



- ◆ Harmonic short termination
 - No harmonic voltage
 - Load resistance

$$\textcircled{1} \quad R_{opt} = \frac{V_{DC}}{I_1}$$

$$\textcircled{2} \quad R_{opt, class-A} = R_{opt, class-B}$$

$$\textcircled{3} \quad R_{opt, class-AB} < R_{opt, class-A}$$


R_L determines voltage swing


Class and Efficiency

- ◆ Output Efficiency (Drain/Collector Efficiency)

$$\eta \triangleq \frac{P_1}{P_{dc}}$$


- ◆ $\eta \uparrow$ rapidly as class-C

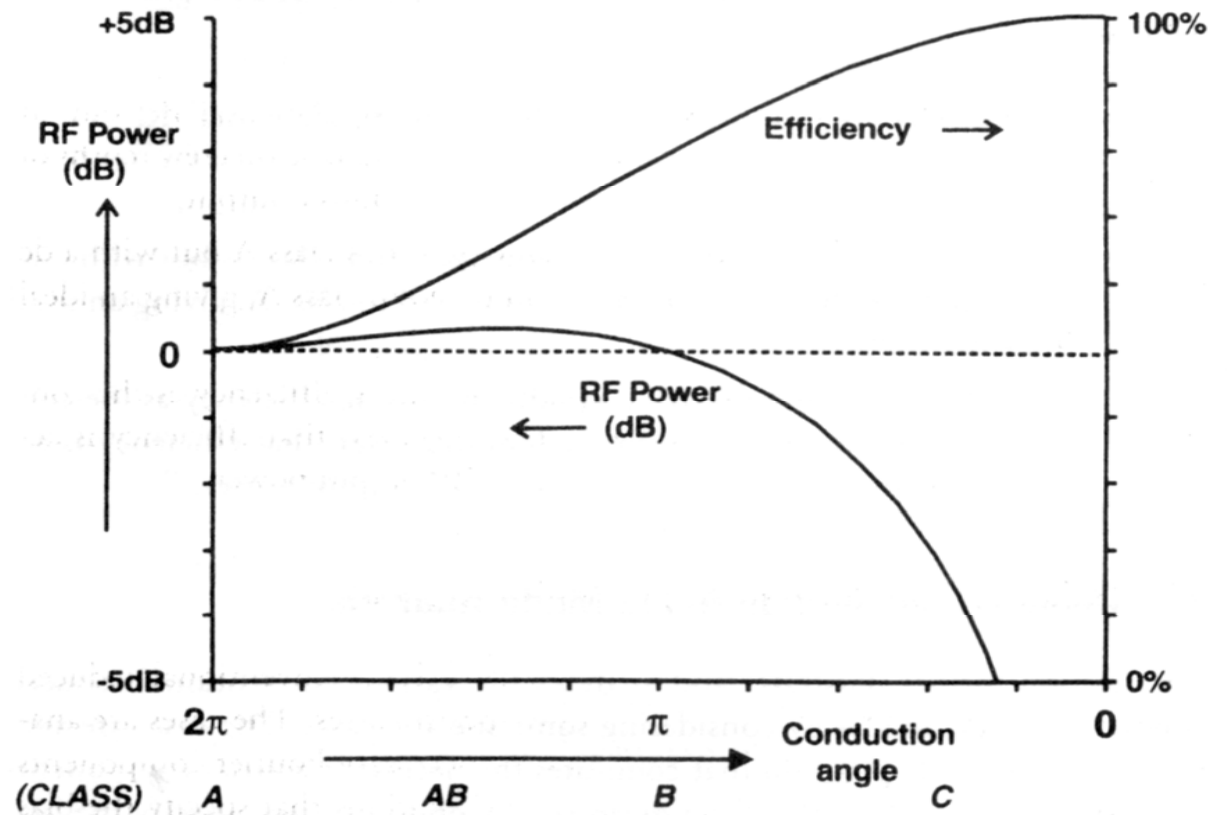

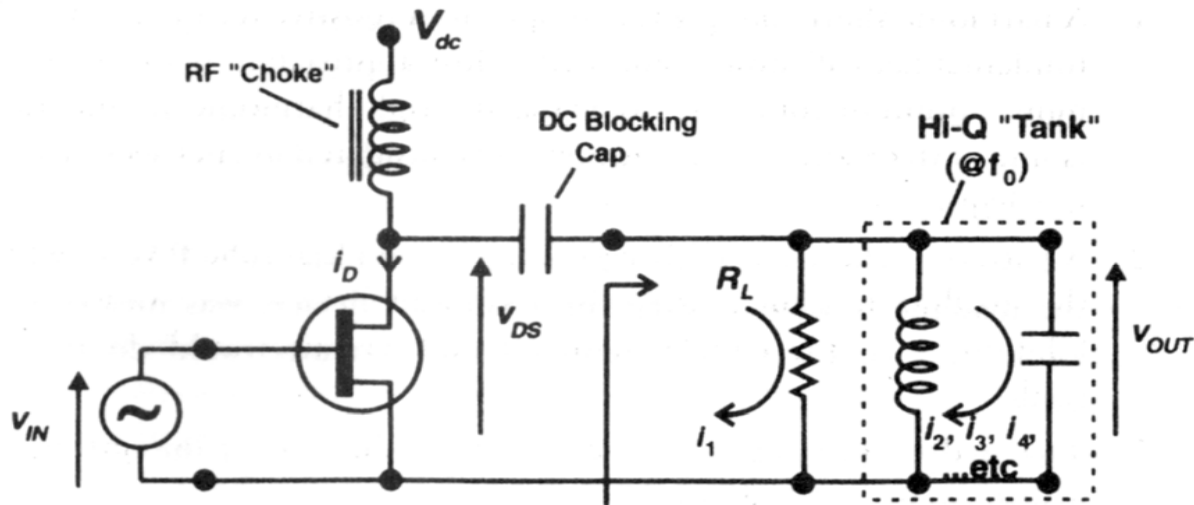

$$Z_L = R_L + j0(f_0)$$
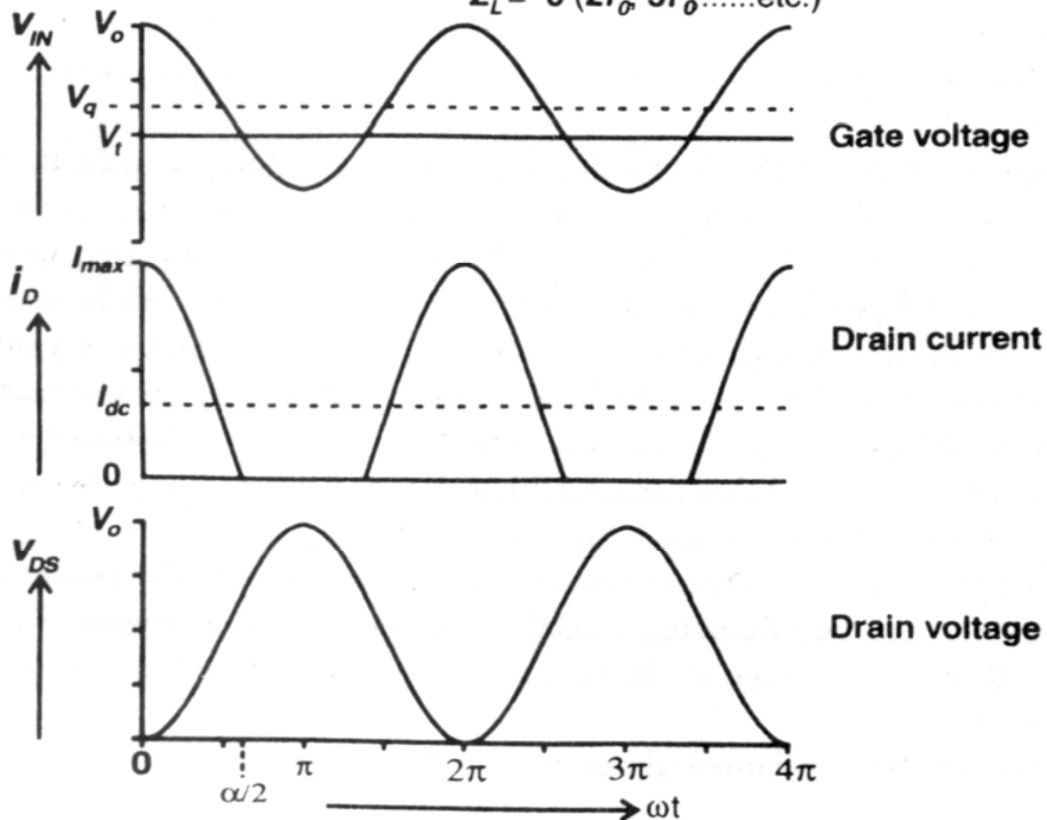
$$Z_L = 0 (2f_0, 3f_0, \dots \text{etc.})$$




Ideal Case

- All harmonics short-circuited → No distortion
- R_L determines voltage swing
- R_L also determines DC power consumption

14.1 Classification of Output Stages


◆ Collector current waveforms for transistors operating in

(a) class A

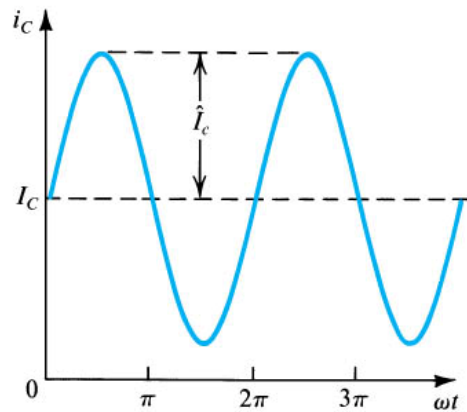


(a)

(b) class B

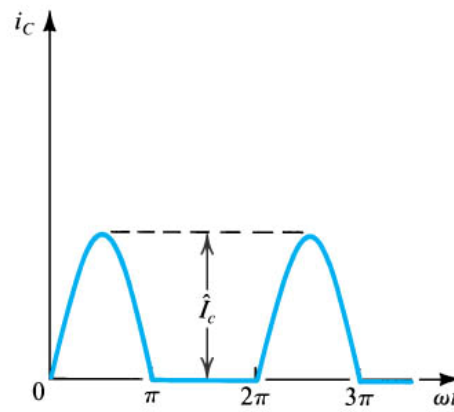

(b)



(c) class AB

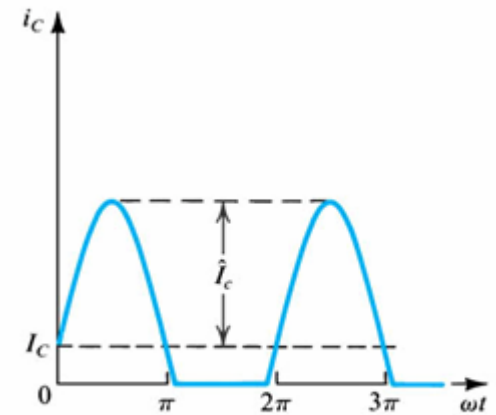

(c)

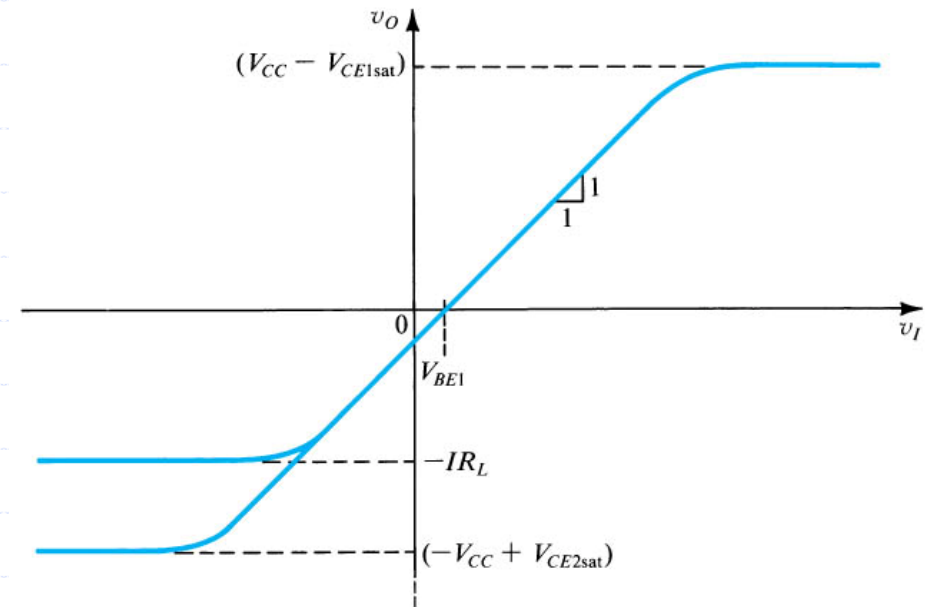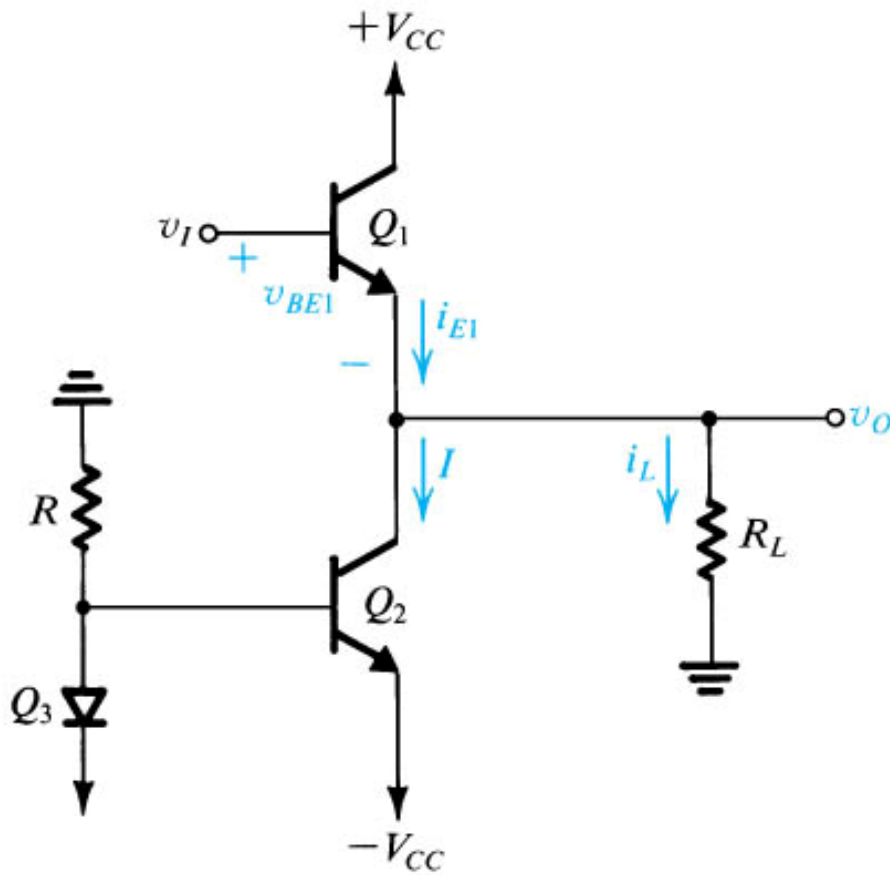14.2.1 Transfer Characteristic

◆ The emitter follower – the most popular class A ckt.



14.2.1 Transfer Characteristic (cont.)

- The bias current must be greater than the largest negative load current.

- The transfer characteristic is



$$v_o = v_i - v_{BE1}$$

- The positive limit of the linear region is given by

$$v_{Omax} = V_{CC} - V_{CE1sat}$$




- In the negative direction, the limit of the linear region is
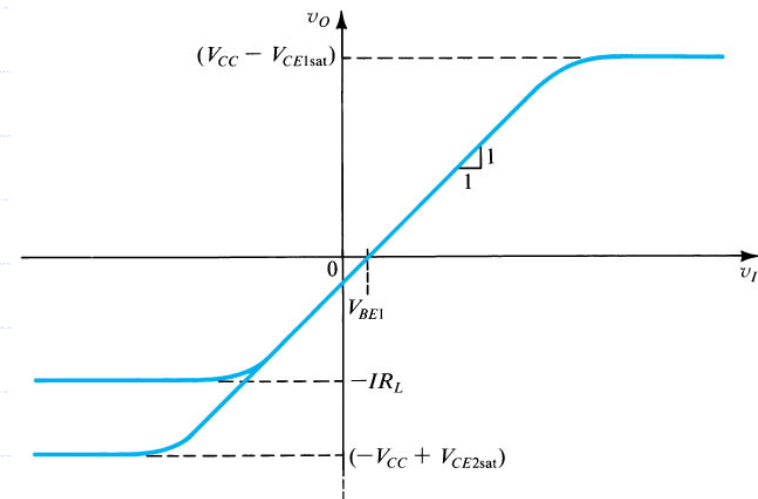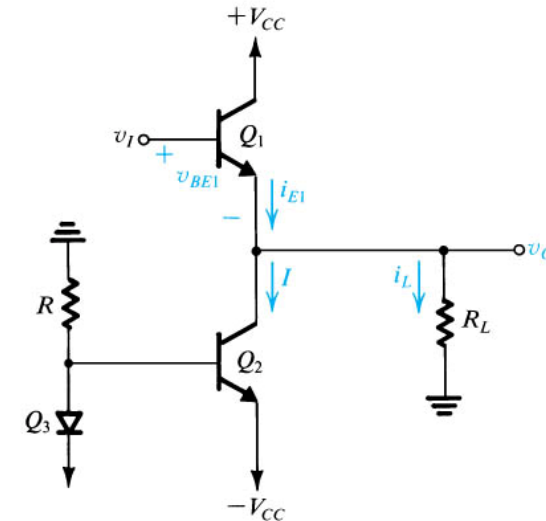
$$v_{Omin} = -IR_L \quad \text{or} \quad -V_{CC} + V_{CE2sat}$$



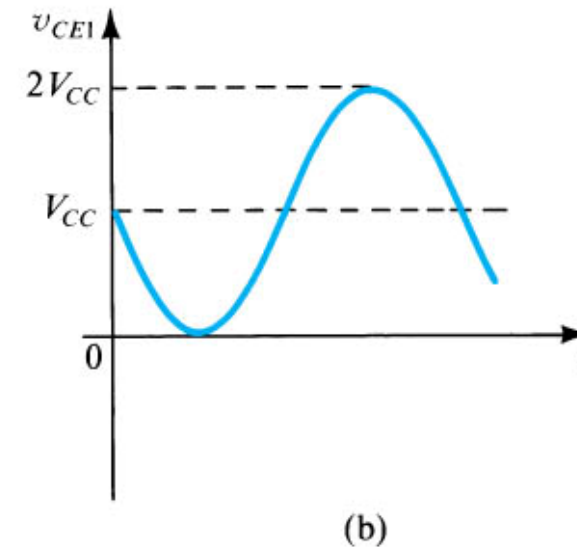
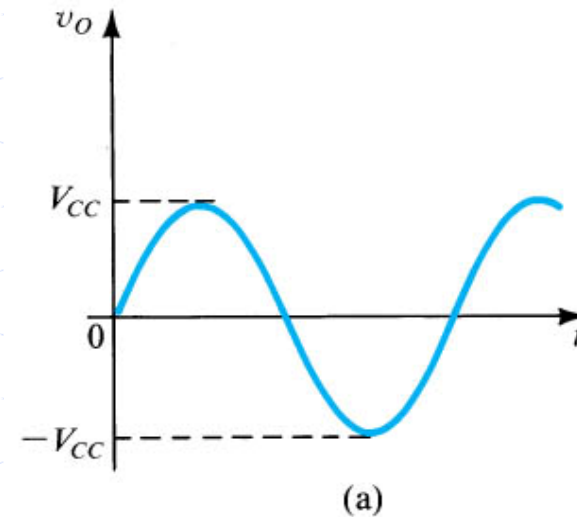
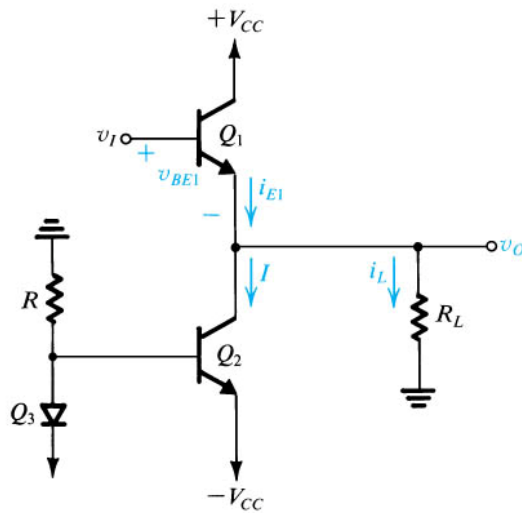
14.2.2 Signal Waveforms

- For sine-wave input, neglecting V_{CEsat} , the output voltage can swing from $-V_{CC}$ to $+V_{CC}$ with the quiescent value being zero.
- Since $v_{CE1} = V_{CC} - v_o$,



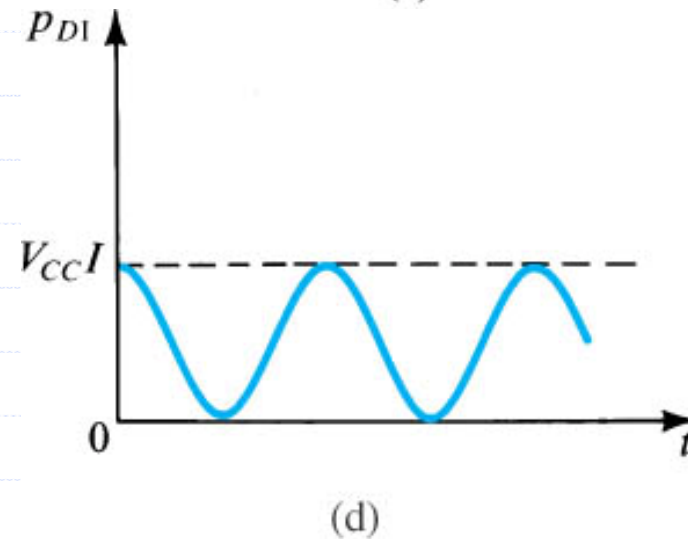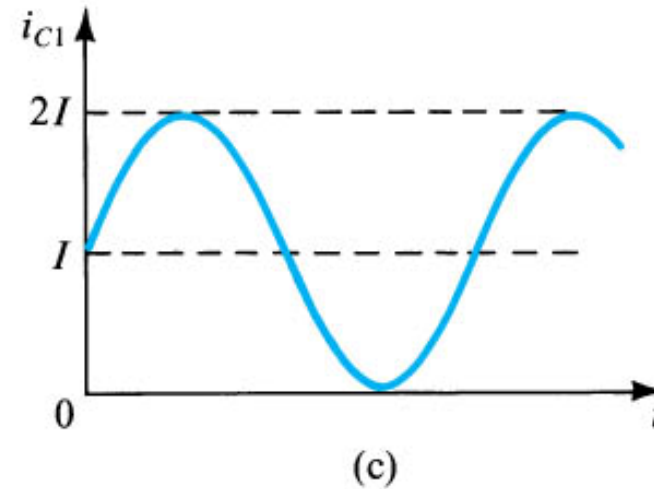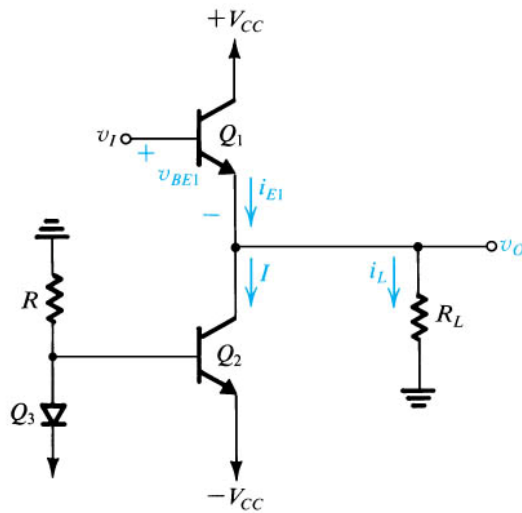14.2.2 Signal Waveforms (cont.)

- Assuming that the bias current is selected to allow a maximum negative load current of V_{CC}/R_L ,
- The instantaneous power dissipation in Q_1 , $p_{D1} = v_{CE1} \cdot i_{C1}$



14.2.3 Power Dissipation

- ◆ The maximum instantaneous power dissipation in Q_1
= $V_{CC} \cdot I$
= The quiescent power dissipation in Q_1 .
 - The emitter follower transistor dissipates the largest amount of power when $v_o=0$: The transistor Q_1 must be able to withstand a continuous power dissipation of $V_{CC} \cdot I$.
 - The power dissipation in Q_1 depends on the value of R_L : When $R_L=0$, a very large current may flow through Q_1 : short circuit protection is needed.

- ◆ The maximum instantaneous power dissipation in Q_2
= $2 \cdot V_{CC} \cdot I$

14.2.4 Power-Conversion Efficiency

- ◆ Power-Conversion Efficiency of an output stage is defined as

$$\eta = \frac{\text{Load power}(P_L)}{\text{Supply power}(P_S)}$$

- For the emitter follower, the average load power will be

$$P_L = \frac{(\hat{V}_o / \sqrt{2})^2}{R_L} = \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$$

- The average (positive + negative) supply power is,

$$P_S = 2V_{CC}I$$

- Thus, the PCE is,

$$\eta = \frac{1}{4} \frac{\hat{V}_o^2}{I R_L V_{CC}} = \frac{1}{4} \frac{\hat{V}_o}{I R_L} \frac{\hat{V}_o}{V_{CC}}$$

14.2.4 Power-Conversion Efficiency (cont.)

- ◆ The maximum efficiency is 25%, obtained when

$$\hat{V}_o = V_{CC} = IR_L$$

- ◆ Because 25% is a rather low figure, the class A output stage is rarely used in high-power applications (>1W).
- ◆ In practice the output voltage swing is limited to lower values to avoid transistors saturation and associated nonlinear distortion. Thus the efficiency achieved is usually in the 10% to 20% range.

14.3 Class B Output Stage

- ◆ The class B output stage consists of a complementary pair of transistors connected in such a way that both cannot conduct simultaneously.

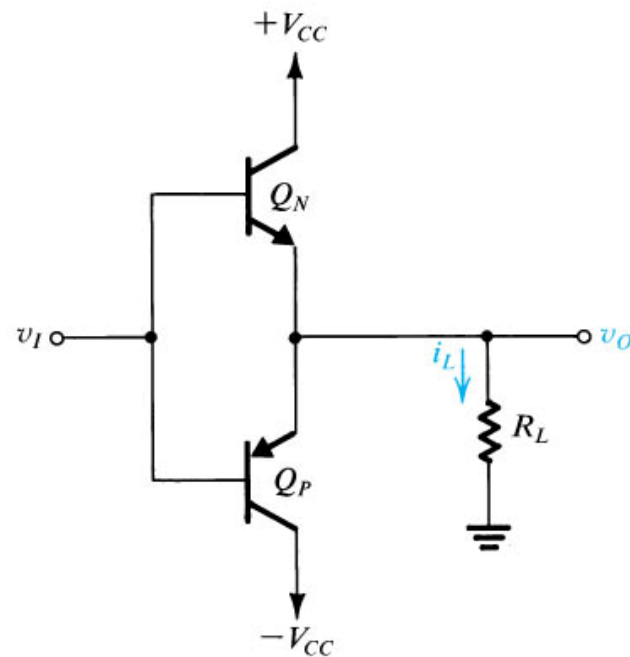


Figure 14.5 A class B output stage.