

# Fundamentals of Microelectronics

- **CH1 Why Microelectronics?**
- **CH2 Basic Physics of Semiconductors**
- **CH3 Diode Circuits**
- **CH4 Physics of Bipolar Transistors**
- **CH5 Bipolar Amplifiers**
- **CH6 Physics of MOS Transistors**
- **CH7 CMOS Amplifiers**
- **CH8 Operational Amplifier As A Black Box**
- **CH16 Digital CMOS Circuits**

# Chapter 7 CMOS Amplifiers

- **7.1 General Considerations**
- **7.2 Common-Source Stage**
- **7.3 Common-Gate Stage**
- **7.4 Source Follower**
- **7.5 Summary and Additional Examples**

# Chapter Outline

## General Concepts

---


- **Biasing of MOS Stages**
- **Realization of Current Sources**

## MOS Amplifiers

---

- **Common-Source Stage**
- **Common-Gate Stage**
- **Source Follower**

# MOS Biasing

 


$$\frac{R_2 V_{DD}}{R_1 + R_2} = V_{GS} + I_D R_S \quad \& \quad I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$V_{GS} = -(V_1 - V_{TH}) + \sqrt{V_1^2 + 2V_1 \left( \frac{R_2 V_{DD}}{R_1 + R_2} - V_{TH} \right)}$$

$$V_1 = \frac{1}{\mu_n C_{ox} \frac{W}{L} R_S}$$

- Voltage at  $X$  is determined by  $V_{DD}$ ,  $R_1$ , and  $R_2$ .
- $V_{GS}$  can be found using the equation above, and  $I_D$  can be found by using the NMOS current equation.


## Self-Biased MOS Stage

 


$$I_D R_D + V_{GS} + R_S I_D = V_{DD}$$

- The circuit above is analyzed by noting  $M_1$  is in saturation and no potential drop appears across  $R_G$ .


# Current Sources

 


(a)

 

(b)

 



(c)

 

(d)

- When in saturation region, a MOSFET behaves as a current source.
- NMOS draws current from a point to ground (sinks current), whereas PMOS draws current from  $V_{DD}$  to a point (sources current).

# Common-Source Stage

  


$$\lambda = 0$$

$$A_v = -g_m R_D$$

$$A_v = -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D R_D}$$

# Operation in Saturation

 

$$V_{in} - V_{out} < V_{TH}$$

$$V_{GS} - (V_{DD} - R_D I_D) < V_{TH}$$

$$R_D I_D < V_{DD} - (V_{GS} - V_{TH})$$

- In order to maintain operation in saturation,  $V_{out}$  cannot fall below  $V_{in}$  by more than one threshold voltage.
- The condition above ensures operation in saturation.



## Example 7.4

**Example  
7.4**

Calculate the small-signal voltage gain of the CS stage shown in Fig. 7.6 if  $I_D = 1 \text{ mA}$ ,  $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$ ,  $V_{TH} = 0.5 \text{ V}$ , and  $\lambda = 0$ . Verify that  $M_1$  operates in saturation.

**Solution** We have


$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$

$$= \frac{1}{300 \Omega}$$

Thus,

$$A_v = -g_m R_D$$

$$= 3.33.$$

 

**Figure 7.6** Example of CS stage.


To check the operation region, we first determine the gate-source voltage:

$$V_{GS} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} \quad (7.42)$$

$$= 1.1 \text{ V}. \quad (7.43)$$

The drain voltage is equal to  $V_{DD} - R_D I_D = 0.8 \text{ V}$ . Since  $V_{GS} - V_{TH} = 0.6 \text{ V}$ , the device indeed operates in saturation and has a margin of  $0.2 \text{ V}$  with respect to the triode region. For example, if  $R_D$  is doubled with the intention of doubling  $A_v$ , then  $M_1$  enters the triode region and its transconductance drops.

## CS Stage with $\lambda=0$

 


$$A_v = -g_m R_L$$

$$R_{in} = \infty$$

$$R_{out} = R_L$$

## CS Stage with $\lambda \neq 0$

 


$$A_v = -g_m (R_L \parallel r_o)$$

$$R_{in} = \infty$$

$$R_{out} = R_L \parallel r_o$$

➤ However, Early effect and channel length modulation affect CE and CS stages in a similar manner.


# CS Gain Variation with Channel Length

 

$$|A_v| = \frac{\sqrt{2\mu_n C_{ox} \frac{W}{L}}}{\lambda \sqrt{I_D}} \propto \sqrt{\frac{2\mu_n C_{ox} WL}{I_D}}$$

- Since  $\lambda$  is inversely proportional to  $L$ , the voltage gain actually becomes proportional to the square root of  $L$ .

# CS Stage with Current-Source Load

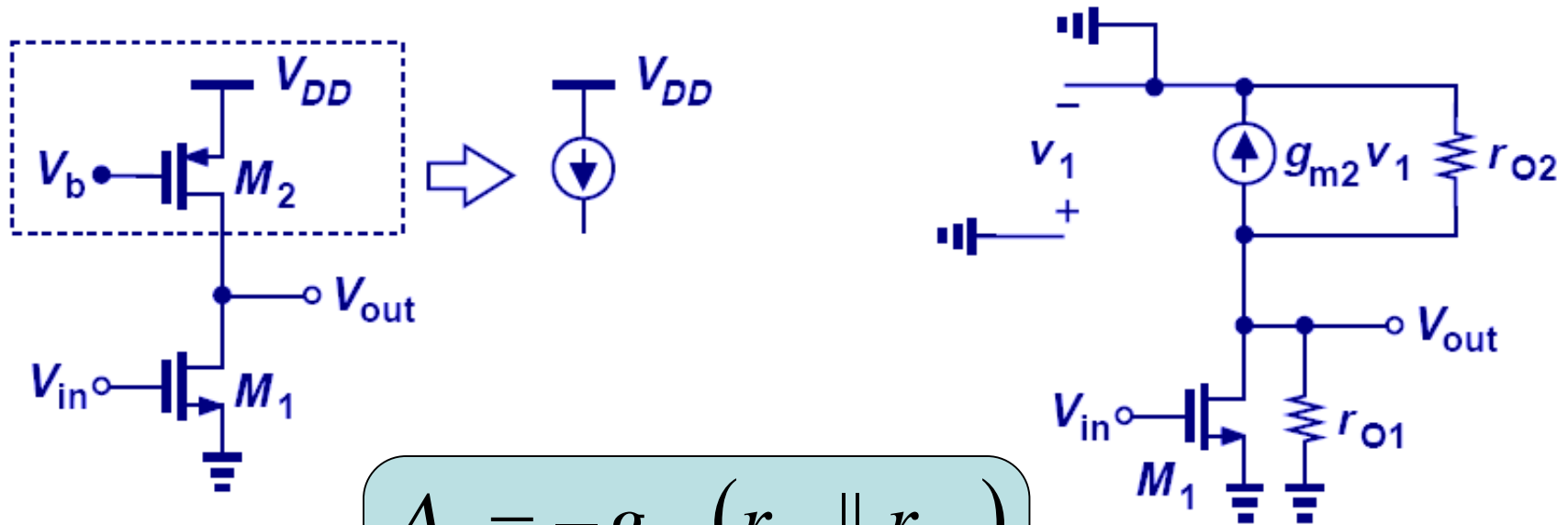


$$A_v = -g_{m1} (r_{O1} \parallel r_{O2})$$

$$R_{out} = r_{O1} \parallel r_{O2}$$

- To alleviate the headroom problem, an active current-source load is used.
- This is advantageous because a current-source has a high output resistance and can tolerate a small voltage drop across it.




## PMOS CS Stage with NMOS as Load

 

$$A_v = -g_{m2} (r_{o1} \parallel r_{o2})$$

➤ Similarly, with PMOS as input stage and NMOS as the load, the voltage gain is the same as before.

# CS Stage with Diode-Connected Load

   


$$A_v = -g_{m1} \cdot \frac{1}{g_{m2}} = -\sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

$$A_v = -g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{O2} \parallel r_{O1} \right)$$

➤ Lower gain, but less dependent on process parameters.
 
## CS Stage with Diode-Connected PMOS Device




$$A_v = -g_{m2} \left( \frac{1}{g_{m1}} \parallel r_{o1} \parallel r_{o2} \right)$$

- Note that PMOS circuit symbol is usually drawn with the source on top of the drain.



# CS Stage with Degeneration

 

$$A_v = - \frac{R_D}{R_S + \frac{1}{g_m} \left( 1 + \frac{R_S + R_D}{r_0} \right)}$$


$$\lambda \neq 0$$

$$A_v = - \frac{R_D}{\frac{1}{g_m} + R_S}$$

$$\lambda = 0$$

- Similar to bipolar counterpart, when a CS stage is degenerated, its gain, I/O impedances, and linearity change.


## Example of CS Stage with Degeneration

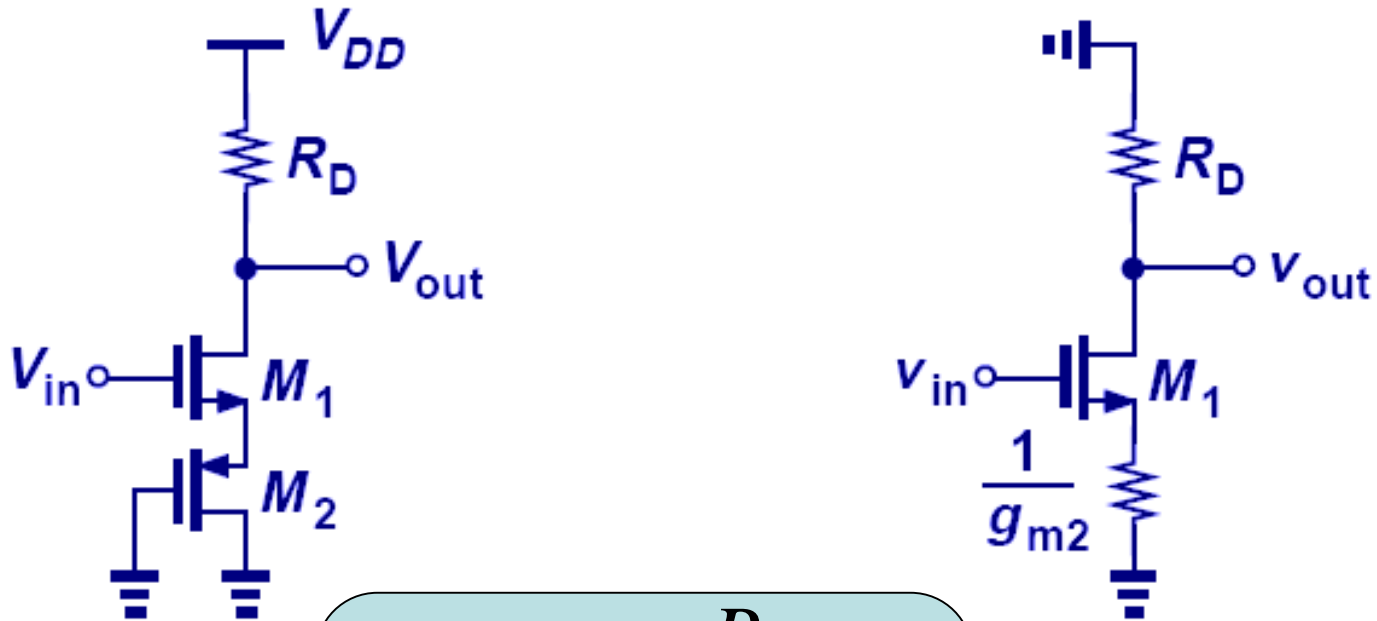

$$A_v = - \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

➤ A diode-connected device degenerates a CS stage.


## CS Stage with Gate Resistance

 

$$V_{R_G} = 0$$

- Since at low frequencies, the gate conducts no current, gate resistance does not affect the gain or I/O impedances.

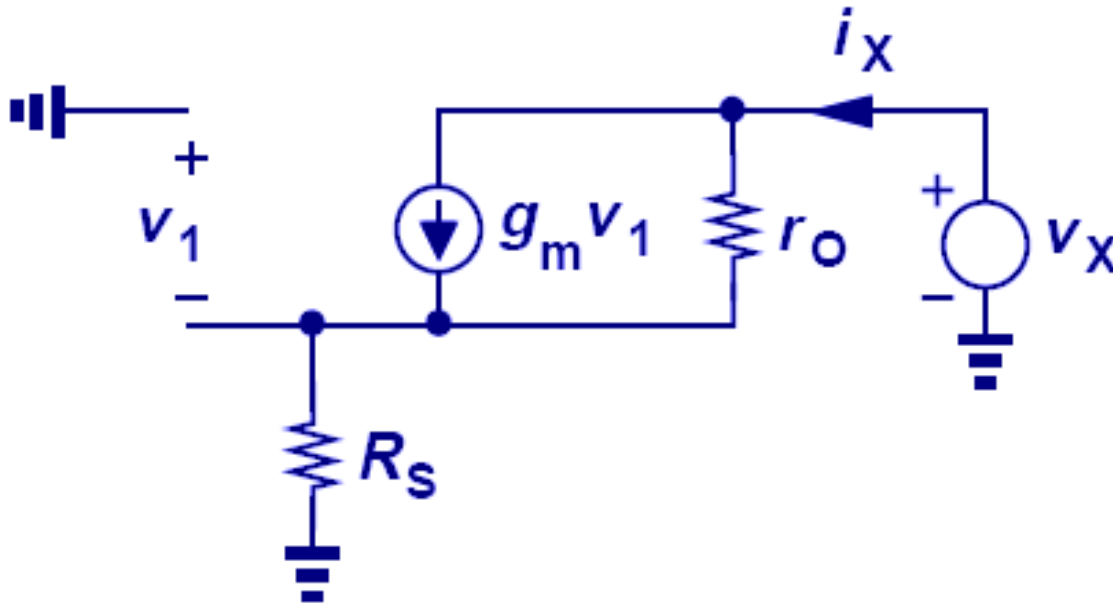
# Output Impedance of CS Stage with Degeneration



$$r_{out} \approx g_m r_o R_S + r_o$$

- Similar to the bipolar counterpart, degeneration boosts output impedance.


## Output Impedance Example (I)

 

$$R_{out} = r_{O1} \left( 1 + g_{m1} \frac{1}{g_{m2}} \right) + \frac{1}{g_{m2}}$$

➤ When  $1/g_m$  is parallel with  $r_{O2}$ , we often just consider  $1/g_m$ .




## Output Impedance Example (II)

 

$$R_{out} \approx g_{m1} r_{O1} r_{O2} + r_{O1}$$

- In this example, the impedance that degenerates the CS stage is  $r_o$ , instead of  $1/g_m$  in the previous example.


# CS Core with Biasing

   

$$A_v = \frac{R_1 \parallel R_2}{R_G + R_1 \parallel R_2} \cdot \frac{-R_D}{\frac{1}{g_m} + R_S}, A_v = -\frac{R_1 \parallel R_2}{R_G + R_1 \parallel R_2} g_m R_D$$

- Degeneration is used to stabilize bias point, and a bypass capacitor can be used to obtain a larger small-signal voltage gain at the frequency of interest.

# Common-Gate Stage

 


$$A_v = g_m R_D$$

- **Common-gate stage is similar to common-base stage: a rise in input causes a rise in output. So the gain is positive.**



## Signal Levels in CG Stage

 

- In order to maintain  $M_1$  in saturation, the signal swing at  $V_{out}$  cannot fall below  $V_b - V_{TH}$ .

## Example 7.12

### Example 7.12

A microphone having a dc level of zero drives a CG stage biased at  $I_D = 0.5 \text{ mA}$ . If  $W/L = 50$ ,  $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$ ,  $V_{TH} = 0.5 \text{ V}$ , and  $V_{DD} = 1.8 \text{ V}$ , determine the maximum allowable value of  $R_D$  and hence the maximum voltage gain. Neglect channel-length modulation.

**Solution** With  $W/L$  known, the gate-source voltage can be determined from

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

as

$$V_{GS} = 0.947 \text{ V}.$$

For  $M_1$  to remain in saturation,

$$V_{DD} - I_D R_D > V_b - V_{TH} \tag{7.98}$$


and hence

$$R_D < 2.71 \text{ k}\Omega. \tag{7.99}$$

Also, the above value of  $W/L$  and  $I_D$  yield  $g_m = (447 \Omega)^{-1}$  and


$$A_v \leq 6.06. \tag{7.100}$$

Figure 7.22 summarizes the allowable signal levels in this design. The gate voltage can be generated using a resistive divider similar to that in Fig. 7.20(a).

 

**Figure 7.22** Signal levels in CG stage.

## I/O Impedances of CG Stage

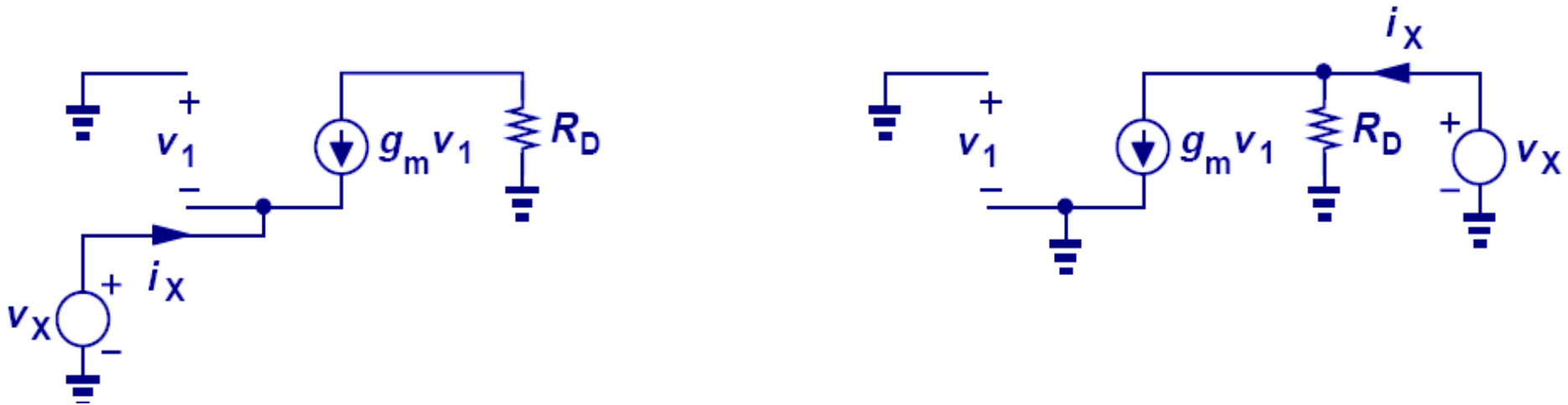


$$R_{in} = \frac{1}{g_m}$$

$$\lambda = 0$$

$$R_{out} = R_D$$

➤ The input and output impedances of CG stage are similar to those of CB stage.


## CG Stage with Source Resistance

 

$$A_v = \frac{R_D}{\frac{1}{g_m} + R_S}$$

➤ When a source resistance is present, the voltage gain is equal to that of a CS stage with degeneration, only positive.


# Generalized CG Behavior

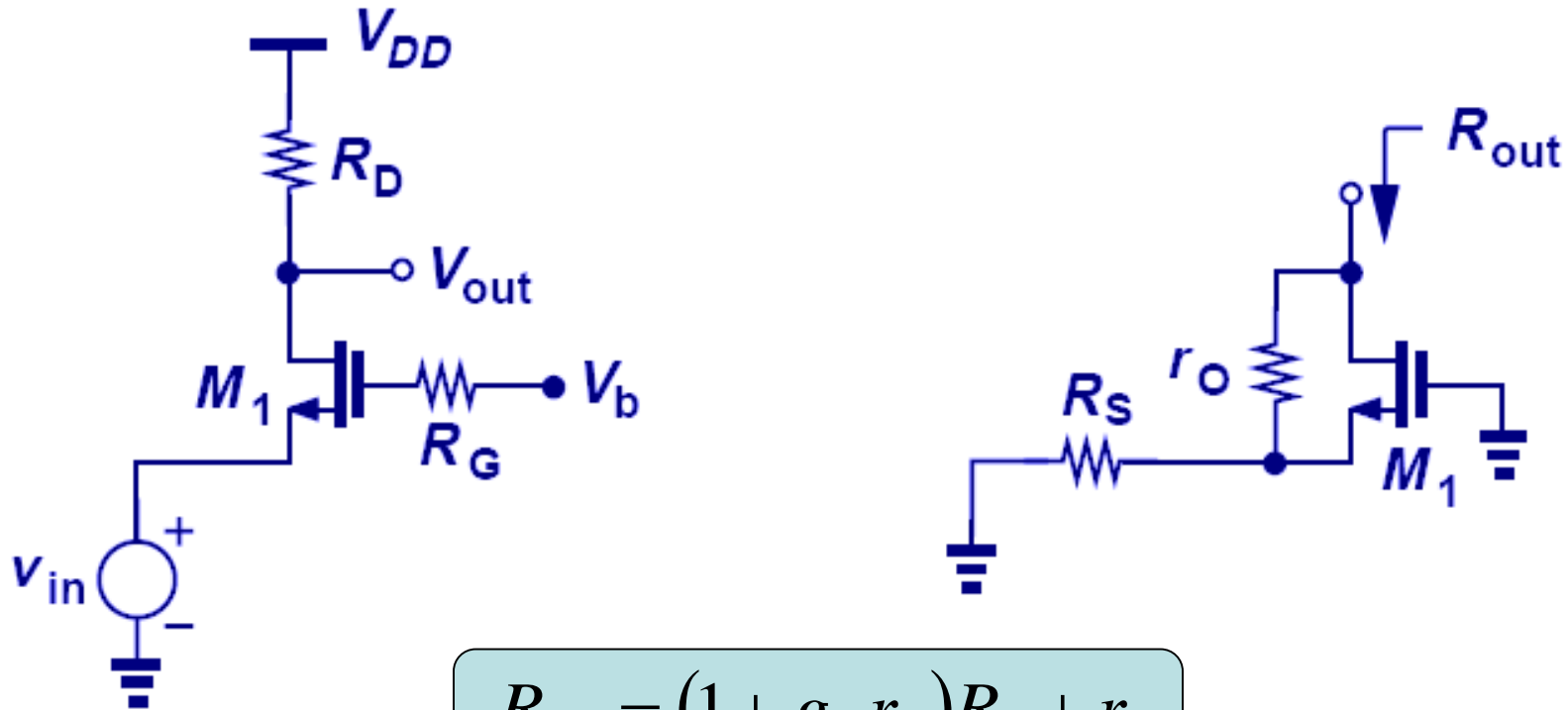

$$R_{out} = (1 + g_m r_o) R_S + r_o$$

- When a gate resistance is present it does not affect the gain and I/O impedances since there is no potential drop across it ( at low frequencies).
- The output impedance of a CG stage with source resistance is identical to that of CS stage with degeneration.


# Example of CG Stage

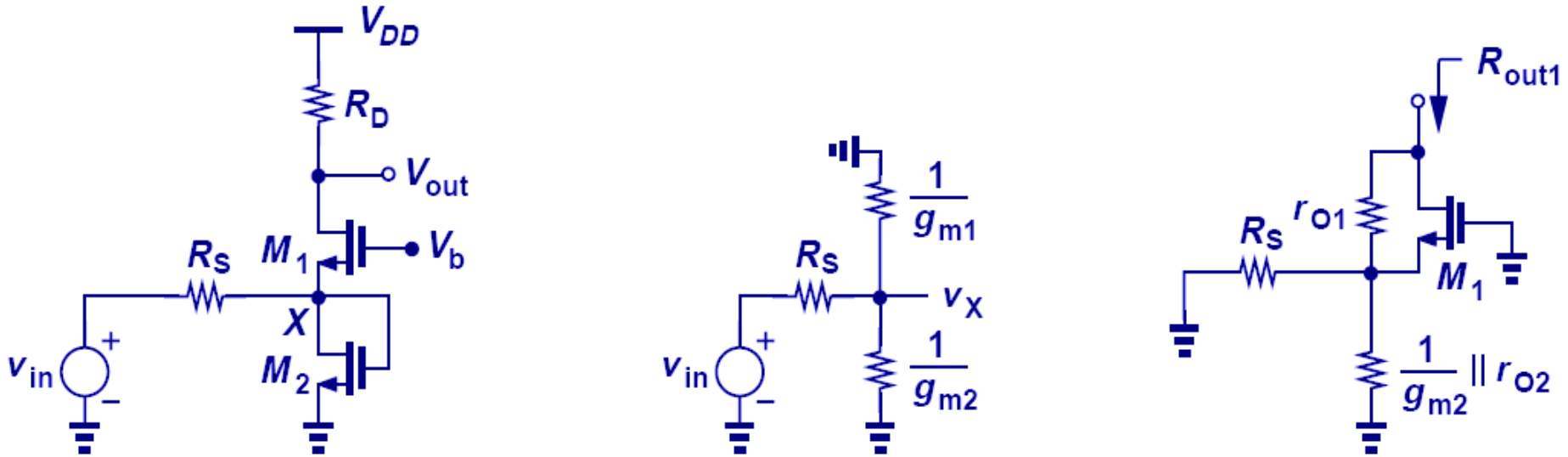

$$\frac{v_{out}}{v_{in}} = \frac{g_{m1} R_D}{1 + (g_{m1} + g_{m2}) R_S} \quad R_{out} \approx \left[ g_{m1} r_{o1} \left( \frac{1}{g_{m2}} \parallel R_S \right) + r_{o1} \right] \parallel R_D$$

➤ **Diode-connected  $M_2$  acts as a resistor to provide the bias current.**


## CG Stage with Biasing

 

$$\frac{v_{out}}{v_{in}} = \frac{R_3 \parallel (1/g_m)}{R_3 \parallel (1/g_m) + R_S} \cdot g_m R_D$$



- $R_1$  and  $R_2$  provide gate bias voltage, and  $R_3$  provides a path for DC bias current of  $M_1$  to flow to ground.

# Source Follower Stage

 



# Source Follower Core

  

$$\frac{v_{out}}{v_{in}} = \frac{r_o \parallel R_L}{\frac{1}{g_m} + r_o \parallel R_L}$$

➤ **Similar to the emitter follower, the source follower can be analyzed as a resistor divider.**

## Example 7.17

### Example 7.17

Design a source follower to drive a  $50\text{-}\Omega$  load with a voltage gain of 0.5 and a power budget of 10 mW. Assume  $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$ ,  $V_{TH} = 0.5 \text{ V}$ ,  $\lambda = 0$ , and  $V_{DD} = 1.8 \text{ V}$ .

**Solution** With  $R_L = 50 \Omega$  and  $r_O = \infty$  in Fig. 7.28, we have

$$A_v = \frac{R_L}{\frac{1}{g_m} + R_L}$$

and hence

$$g_m = \frac{1}{50 \Omega}. \quad (7.134)$$

The power budget and supply voltage yield a maximum supply current of 5.56 mA. Using this value for  $I_D$  in  $g_m = \sqrt{2\mu_n C_{ox}(W/L)I_D}$  gives

$$W/L = 360. \quad (7.135)$$


 
 


Figure 7.28 Source follower.


## Source Follower Example

 

$$A_v = \frac{r_{O1} \parallel r_{O2}}{\frac{1}{g_{m1}} + r_{O1} \parallel r_{O2}}$$

➤ In this example,  $M_2$  acts as a current source.

# Output Resistance of Source Follower

 


$$R_{out} = \frac{1}{g_m} \parallel r_o \parallel R_L \approx \frac{1}{g_m} \parallel R_L$$

$$R_o = \frac{1}{g_m} \parallel r_o + \frac{R_D}{1 + g_m r_o} \text{ if } R_D \neq 0$$

- The output impedance of a source follower is relatively low, whereas the input impedance is infinite ( at low frequencies); thus, a good candidate as a buffer.


## Source Follower with Biasing

 

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - I_D R_S - V_{TH})^2$$


- $R_G$  sets the gate voltage to  $V_{DD}$ , whereas  $R_S$  sets the drain current.
- The quadratic equation above can be solved for  $I_D$ .

# Supply-Independent Biasing

 


- If  $R_s$  is replaced by a current source, drain current  $I_D$  becomes independent of supply voltage.

## Example of a CS Stage (I)

 

(a)

 


(b)

$$A_v = -g_{m1} \left( \frac{1}{g_{m3}} \parallel r_{O1} \parallel r_{O2} \parallel r_{O3} \right)$$

$$R_{out} = \frac{1}{g_{m3}} \parallel r_{O1} \parallel r_{O2} \parallel r_{O3}$$

➤  **$M_1$  acts as the input device and  $M_2, M_3$  as the load.**

## Example of a CS Stage (II)

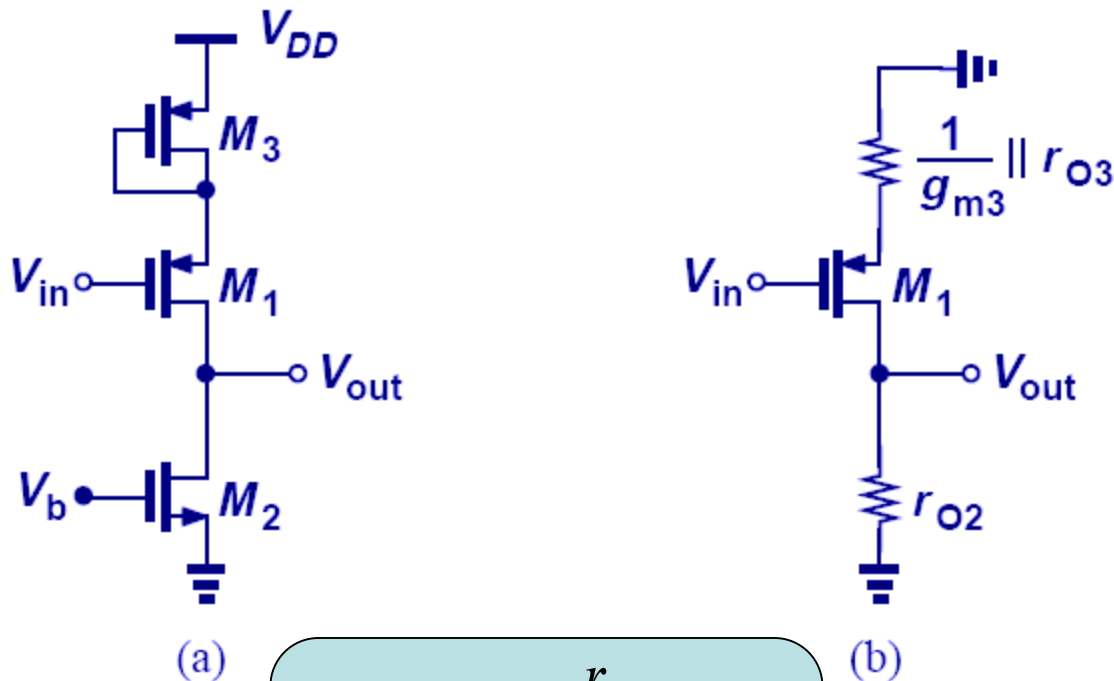


$$A_v = - \frac{r_{O2}}{\frac{1}{g_{m1}} + \frac{1}{g_{m3}} \parallel r_{O3}}$$


➤  $M_1$  acts as the input device,  $M_3$  as the source resistance, and  $M_2$  as the load.



# Examples of CS and CG Stages

 

(a)

 


(b)

$$A_{v\_CS} = -g_{m1} \left[ (1 + g_{m2} r_{O2}) R_S + r_{O2} \right] \parallel r_{O1}$$

$$A_{v\_CG} = \frac{r_{O1}}{\frac{1}{g_{m2}} + R_S}$$


➤ **With the input connected to different locations, the two circuits, although identical in other aspects, behave differently.**

## Example of a Composite Stage (I)

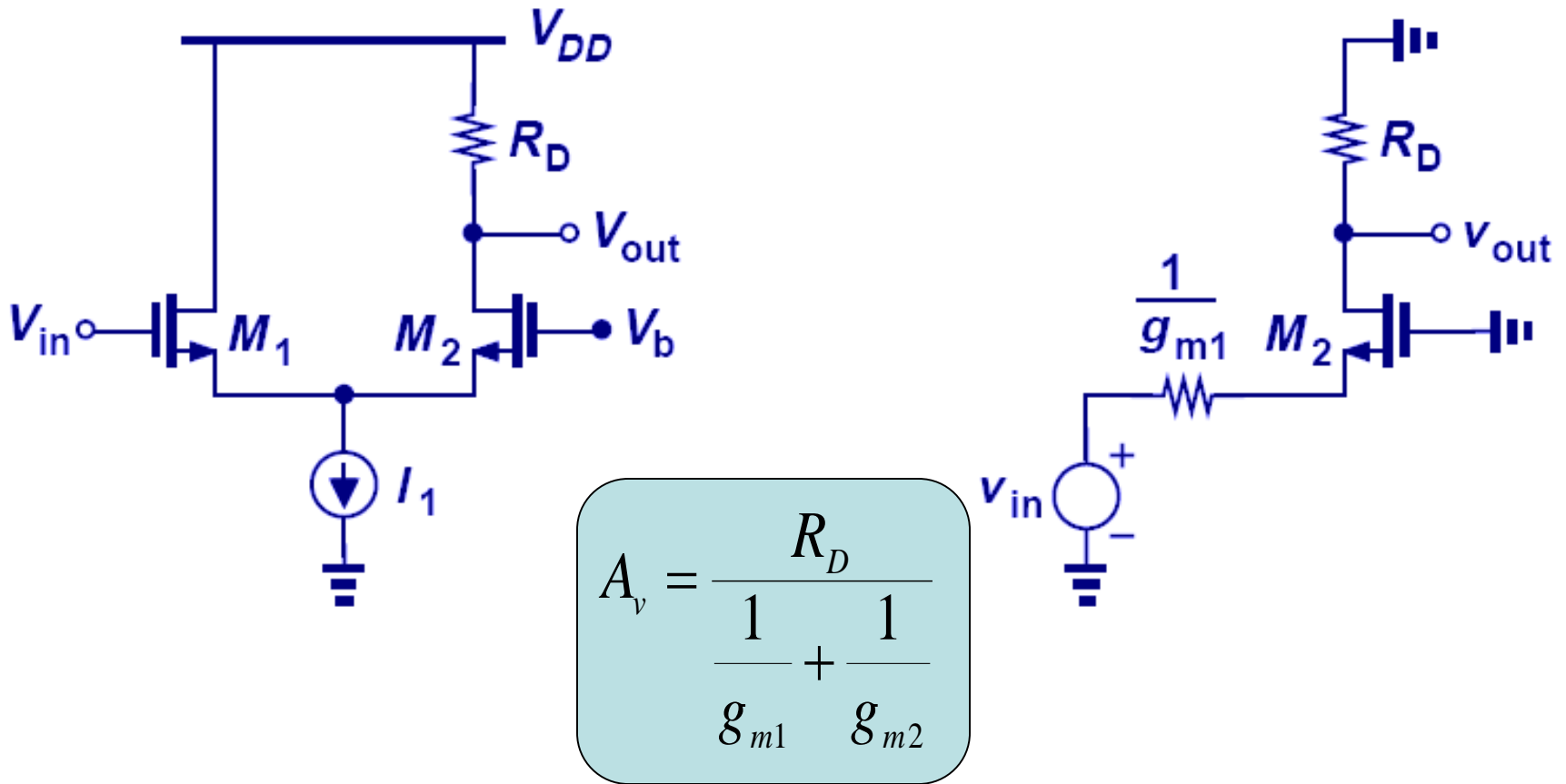

- By replacing the left side with a Thevenin equivalent, and recognizing the right side is actually a CG stage, the voltage gain can be easily obtained.

## Example of a Composite Stage (II)

 

$$\frac{v_{out2}}{v_{in}} = - \frac{\frac{1}{g_{m3}} \parallel r_{O3} \parallel r_{O4}}{\frac{1}{g_{m2}} \parallel r_{O2} + \frac{1}{g_{m1}}}$$

- This example shows that by probing different places in a circuit, different types of output can be obtained.
- $V_{out1}$  is a result of  $M_1$  acting as a source follower whereas  $V_{out2}$  is a result of  $M_1$  acting as a CS stage with degeneration.