

HW#4 - Selected solution

8-5. The following characteristics have been measured on a lossy transmission line at 100 (MHz):

$$Z_0 = 50 + j0 \ (\Omega)$$

$$\alpha = 0.01 \ (\text{dB/m})$$

$$\beta = 0.8\pi \ (\text{rad/m}).$$

Determine R , L , G , and C for the line.

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = R_0 + jX_0, \quad \alpha = 0.01(\text{dB}/m) = 0.01/8.69 = 0.00115(\text{Np}/m)$$

$$\text{Since } Z_0 = R_0 = \text{real} \longrightarrow \text{Im}(Z_0) = X_0 = 0$$

$$\text{This lossy line is distortionless: } R_0 = \sqrt{\frac{L}{C}}, \quad X_0 = 0 \quad \text{i.e., } \frac{R}{L} = \frac{G}{C}$$

In this case,

$$\alpha = R\sqrt{C/L}, \quad \beta = \omega\sqrt{LC}, \quad Z_0 = \sqrt{L/C}$$

$$\therefore R = \frac{\alpha}{\sqrt{C/L}} = \alpha Z_0 = 0.00115 \times 50 = 0.0575(\Omega/m)$$

$$\beta Z_0 = \omega L \longrightarrow L = \frac{\beta Z_0}{\omega} = \frac{0.8\pi \times 50}{2\pi \times 10^8} = 0.2 \times 10^{-6}(\text{H}/m) = 0.2(\mu\text{H}/m)$$

$$G = \frac{RC}{L} = \frac{\alpha}{Z_0} = \frac{0.00115}{50} = 23 \times 10^{-6}(\text{s}/m) = 23(\mu\text{H}/m)$$

$$C = \frac{LG}{R} = \frac{L}{Z_0^2} = \frac{0.2 \times 10^{-6}}{50^2} = 80 \times 10^{-12}(\text{F}/m) = 80(\text{pF}/m)$$

8-11. A 2-(m) lossless air-spaced transmission line having a characteristic impedance $50 \text{ } (\Omega)$ is terminated with an impedance $40 + j30 \text{ } (\Omega)$ at an operating frequency of 200 (MHz). Find the input impedance.

$$(8-79): Z_i = R_0 \frac{Z_L + jR_0 \tan \beta l}{R_0 + jZ_L \tan \beta l}$$

$$\beta l = \frac{2\pi}{\lambda} l = \frac{2\pi l}{c/f} = \frac{2\pi \times 2}{(3 \times 10^8)/(2 \times 10^8)} = \frac{8\pi}{3} = 480^\circ$$

$$\tan \beta l = \tan \frac{8\pi}{3} = \tan \left(3\pi - \frac{\pi}{3} \right) = -\tan \frac{\pi}{3} = -\sqrt{3}$$

$$\begin{aligned} \therefore Z_i &= 50 \frac{(40 + j30) + j50(-\sqrt{3})}{50 + j(40 + j30)(-\sqrt{3})} \\ &\approx 26.3 - j9.87(\Omega) \end{aligned}$$