

Analog Electronic Circuits
Department of Electrical and Computer Engineering
Seoul National University

2014 Fall

D. K. Jeong


Quiz #3

October 22, 2014

Student ID number :

Student name :

1. In the CS stage of Fig.1, we have $R_S=200\Omega$, $C_{GS}=250\text{fF}$, $C_{GD}=80\text{fF}$, $C_{DB}=100\text{fF}$, $g_m=(150\Omega)^{-1}$, $\lambda=0$, $R_L=2\text{k}\Omega$.

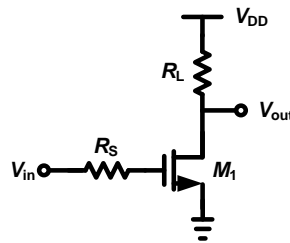

[Fig. 1]

1.1 Find two poles of circuit Fig.1 with the aid of Miller's approximation.

1.2 There is a large error between the frequency response of 1.1 and exact transfer function at high frequencies. Find out the exact locations of the zero(s) and explain why Miller's approximation is not accurate.

※NOTE: Problem 1.2 is changed. Don't calculate poles.

A)