

Analog Electronic Circuits  
Department of Electrical and Computer Engineering  
Seoul National University

2014 Fall

D. K. Jeong

Quiz #6

December 10, 2014

Student ID number :

Student name :

1. Consider the filter shown in Fig below. Compute the sensitivity of the pole and zero frequencies with respect to  $C_1$ ,  $C_2$ , and  $R_1$ .

