

<Solution>

Analog Electronic Circuits

Department of Electrical and Computer Engineering

Seoul National University

2014 Fall

D. K. Jeong


Quiz #6

December 10, 2014

Student ID number :

Student name :

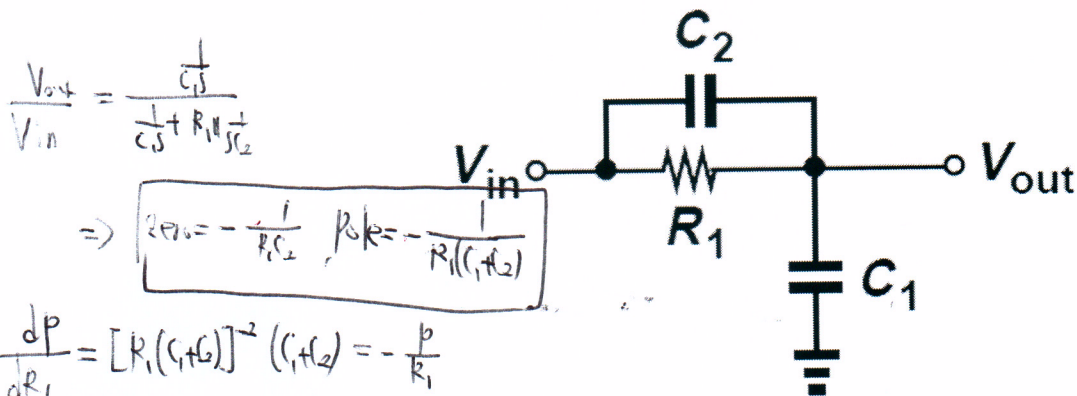1. Consider the filter shown in Fig below. Compute the sensitivity of the pole and zero frequencies with respect to C_1 , C_2 , and R_1 .



$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{C_2}}{\frac{1}{C_2} + R_1 \frac{1}{C_1}}$$

$$\Rightarrow \left[\text{Zero} = -\frac{1}{R_1 C_2}, \text{Pole} = -\frac{1}{R_1 (C_1 + C_2)} \right]$$

$$\frac{dp}{dR_1} = [R_1 (C_1 + C_2)]^{-2} (C_1 + C_2) = -\frac{p}{R_1}$$

$$S_{R_1}^p = \frac{\frac{dp}{p}}{\frac{dR_1}{R_1}} = -1$$

$$S_{C_1}^p = -\frac{C_1}{C_1 + C_2}$$

$$S_{C_2}^p = -\frac{C_2}{C_1 + C_2}$$

$$S_{R_1}^z = S_{C_2}^z = -1$$

$$S_{C_1}^z = 0$$

(8741)

<해답>

$\left\{ \begin{array}{l} \text{다항식 10점} \\ \text{분리도출해 내다 -1점} \end{array} \right\}$