

PSPICE Assignments #4

- Due: 2014/12/03(Wed) 3:30 PM
- Submit a hardcopy report.
- For any questions, send an e-mail to [jhhwang@isd1.snu.ac.kr](mailto:jhhwang@isd1.snu.ac.kr)

1. Use the Model listed below. It is all included in the basic library.  
 The emitter follower of Fig.2 must be designed to drive  $R_L=4\text{ ohms}$  with a voltage gain of 0.8. Use Q2N2222 model for NPN bipolar junction transistor model. Use IDC (Ideal Current Source) for  $I_1$ .  
 $V_{CC}=1.8\text{V}$ ,  $V_{EE}=0\text{V}$ ,  $V_{BE,on}=0.8\text{V}$ ,  $I_S=7.3\times 10^{-15}\text{A}$ ,  $V_A=\infty$ ,  $\beta>100$ .


 


Fig.2

 - a) Assuming  $I_{C1}=I_1$ , find  $I_1$  that make the circuit satisfy the given voltage gain condition.
- b) Assuming  $V_{in}$  is limited by  $V_{CC}$  and  $V_{EE}$  (i.e.  $0\sim 1.8\text{V}$ ), find the followings.
  - 1)  $V_{out}$  range.
  - 2) the most reasonable offset voltage value for  $V_{out}$ . (HINT: When output range is  $0\sim 400\text{mV}$ , the most reasonable offset voltage would be  $200\text{mV}$  to have the maximum swing.)
  - 3) input offset voltage when taking the result from 2) into account.
  - 4) input swing when taking voltage gain and the result from 1) into consideration.
  - 5) Verify 2) and 3) using Bias Voltage/Current Display from the button shown below.



- c) By using VSIN to have sinusoidal voltage input, show that the required conditions from a) and b) are satisfied. You may use 'transient' simulation. You need to set proper VOFF(=offset), VAMPL(=amplitude) and FREQ(=frequency) values for VSIN.

<End of PSPICE Assignments #4>