

Electronic Circuits II
School of Electrical Engineering
Seoul National University

Fall 2007

D.K. Jeong

Homework Assignment #3
Quiz on 10:30am, 10/16/2007

Read Sedra/Smith 8.8 through 9.2.

[1] Do **all Exercises** (8.10-8.18, 9.1-9.8).

[2] **Problems** 8.61, 8.69, 8.71, 8.80, 9.4, 9.12, 9.13, 9.16

<End of Homework Assignment #3>