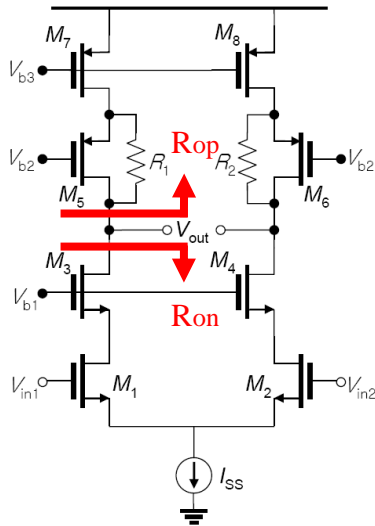


Quiz 2	Subject	Professor	Student ID#	Student Name	Score
Date: 2009.09.16	Microelectronics 2	Jong-Ho Lee			

1. Assume that each odd-numbered MOS transistor on left path of telescopic differential pair in the circuit shown below has the same properties as each even-numbered MOS transistors on the right path. For example, M_1 and M_2 are symmetric, and this relation is valid for other transistor pairs. Resistors R_1 and R_2 are also symmetric. Tail current source is ideal. All transistors have an output resistance r_o due to a finite Early voltage V_A . Answer for the following questions.



(a) Compute the differential gain of the circuit. $R_1 (=R_2)$ can have an arbitrary resistance value.

Answer)

Using half circuit analysis,

$$R_{op} = R_1 // r_{o5} + r_{o7} \{ 1 + g_{m5}(R_1 // r_{o5}) \}$$

$$\approx r_{o7} g_{m5} (R_1 // r_{o5})$$

$$R_{on} = r_{o3} + r_{o1} (1 + g_{m3} r_{o3})$$

$$\approx r_{o1} g_{m3} r_{o3}$$

$$A_v = -g_{m1} (R_{op} // R_{on})$$

$$(g_{m1} = g_{m2}, g_{m3} = g_{m4}, g_{m5} = g_{m6}, g_{m7} = g_{m8})$$

$$(r_{o1} = r_{o2}, r_{o3} = r_{o4}, r_{o5} = r_{o6}, r_{o7} = r_{o8})$$

(b) Repeat (a) when $R_1 (=R_2)$ is infinite.

Answer)

$$R_{op} \approx r_{o7} g_{m5} r_{o5} \quad (R_1 (=R_2) = \infty)$$

$$A_v = -g_{m1} (R_{op} // R_{on}) = -g_{m1} (R_{on} // r_{o7} g_{m5} r_{o5})$$

(c) Calculate the differential gain when $R_1 (=R_2)$ is 0Ω , and pMOSFETs M_7 and M_8 are changed to nMOSFETs. Assume that $r_o \gg 1/g_m$.

Answer)

$R_1 (=R_2) = 0$ means $R_1 (=R_2)$ path will be short and so $M_5 (=M_6)$ will be negligible.

$M_7 (=M_8) \Rightarrow$ nMOSFET means the output impedance in $M_7 (=M_8)$

$$\text{is } \frac{1}{g_{m7}} \left(\frac{1}{g_{m8}} \right) \parallel r_{o7} (r_{o8}) \cdot$$

$$R_{op} = \frac{1}{g_{m7}} (r_o \gg 1/g_m)$$

$$R_{on} \approx r_{o1} g_{m3} r_{o3}$$

$$R_{out} = R_{op} // R_{on} \approx \frac{1}{g_{m7}} \quad (r_o \gg 1/g_m)$$

$$A_v = -g_{m1} \frac{1}{g_{m7}} = -\frac{g_{m1}}{g_{m7}}$$