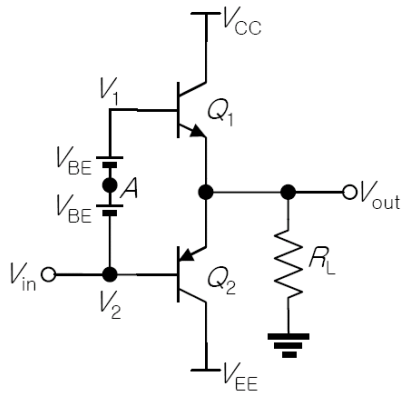


Quiz 8	Subject	Professor	Student ID#	Student Name	Score
Date: 2009.11.04	Microelectronics 2	Jong-Ho Lee			

1. Following figure depicts improved push-pull stage to reduce crossover distortion. Turn-on voltages of Q_1 and Q_2 are V_{BE1} and V_{BE2} , respectively. Answer for the following questions.




(a) Derive input-output relation and plot schematically the relation on given figure below. (3)

Answer)

Assuming $V_{BE1} \cong |V_{BE2}| \cong V_{BE}$,


$$V_{out} = V_{in} + |V_{BE2}| = V_{in} + 2V_{BE} - V_{BE1} \cong V_{in} + V_{BE}$$

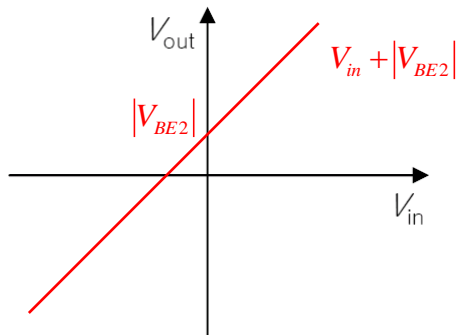

(b) Repeat (a) when V_{in} is applied to node A. (2)

Answer)

$$\begin{aligned} V_{out} &= V_{in} - V_{BE} + |V_{BE2}| \\ &= V_{in} + V_{BE} - V_{BE1} \cong V_{in} \end{aligned}$$

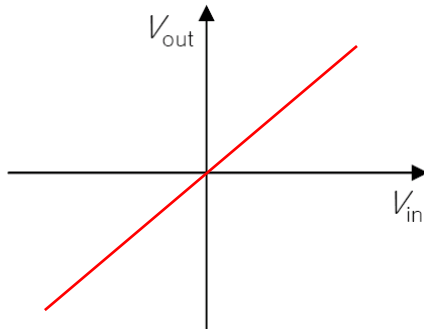

(c) Calculate voltage gain A_v . Assume $r_{\pi} = r_{\pi1} = r_{\pi2}$ and $g_m = g_{m1} = g_{m2}$. Assume $r_{\pi} g_m \gg 1$. (3)

Answer)

$$\begin{aligned} \frac{v_{out}}{R_L} &= \frac{v_{in} - v_{out}}{r_{\pi} \parallel r_{\pi}} + (g_m + g_m)(v_{in} - v_{out}) \\ \frac{v_{out}}{v_{in}} &= \frac{1 + 2g_m \cdot \frac{r_{\pi}}{2}}{\frac{r_{\pi}}{2R_L} + 1 + 2g_m \cdot \frac{r_{\pi}}{2}} = \frac{1 + g_m r_{\pi}}{\frac{r_{\pi}}{2R_L} + 1 + g_m r_{\pi}} \\ &\cong \frac{g_m}{\frac{1}{2R_L} + g_m} = \frac{R_L}{R_L + \frac{1}{2g_m}} \end{aligned}$$

(d) Although the push-pull stage solves the crossover distortion, there is still a non-linearity when V_{out} increases. Explain briefly the reason of the non-linearity. (2)

Answer)

The voltage division relationship from the result of (c) shows an **input-dependant** behavior. As V_{out} becomes more positive, g_{m1} rises and A_v comes closer to unity. As a result, the voltage gain is not constant. Thus, the circuit experiences nonlinearity.