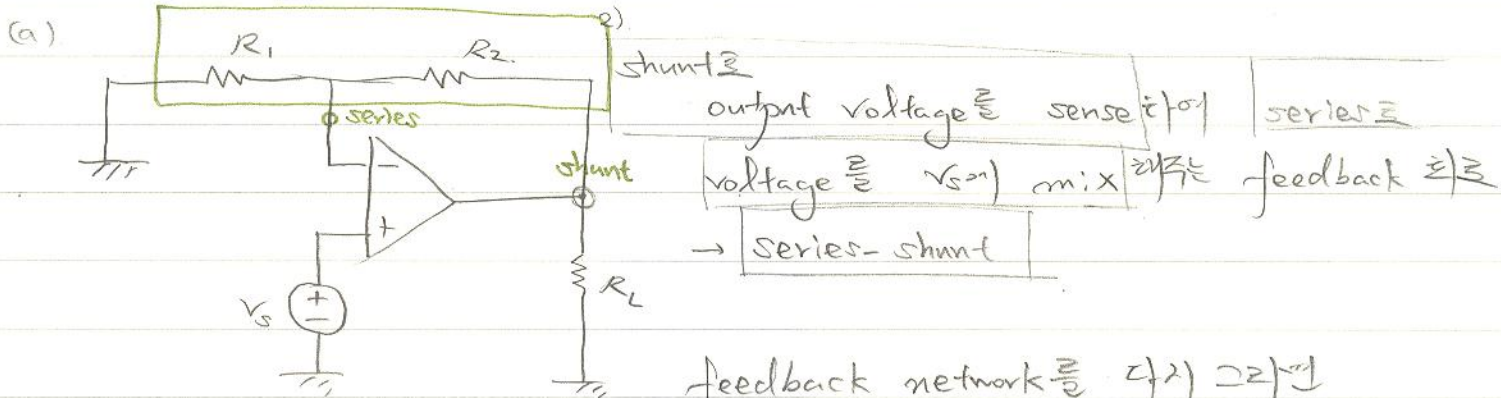





8.26

8

- 1) Identify the feedback topology
- 2) Indicate the output variable being sampled and the feedback sign
- 3) Expression for  $\beta$  and  $A_f$



feedback network를 다시 그리기

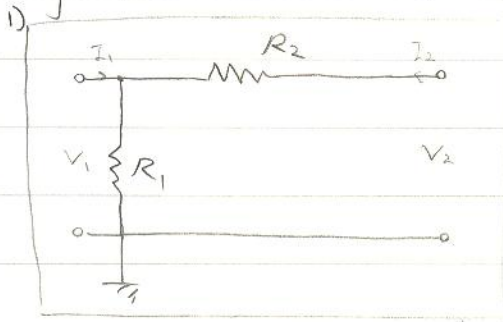


series-shunt 구조이므로 h-parameter two-port network를 이용해 feedforward를 위한 A-circuit과  $\beta$  circuit을 다시 그리는 과정은 아래와 같다

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} \Rightarrow \begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned} \Rightarrow \begin{aligned} h_{11} &= \left. \frac{V_1}{I_1} \right|_{V_2=0} & h_{22} &= \left. \frac{I_2}{V_2} \right|_{I_1=0} & h_{12} &= \left. \frac{V_1}{V_2} \right|_{I_1=0} \end{aligned}$$

이때  $h_{11} = R_1 \parallel R_2$ ,  $h_{22} = \frac{1}{R_1 + R_2}$ ,  $h_{12} = \frac{R_1}{R_1 + R_2}$

A-circuit을 다시 그리기

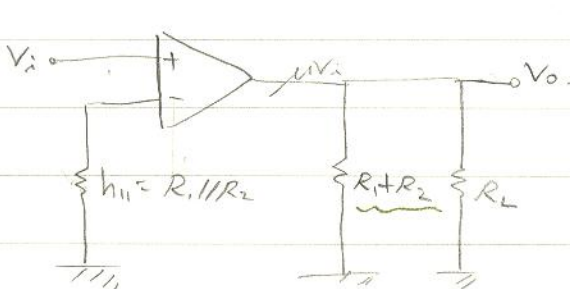

$$A = \frac{V_o}{V_i}$$

한편 op-amp가 gain을  $\mu$ 라 하면

$$A_f = \frac{V_o}{V_i} = \mu$$




$$\beta = h_{12} = \frac{R_1}{R_1 + R_2}$$


$$\Rightarrow A_f = \frac{A}{1 + A\beta} = \frac{\mu}{1 + \frac{\mu R_1}{R_1 + R_2}} = \frac{\mu}{\frac{(1 + \mu)R_1 + R_2}{R_1 + R_2}} = \frac{\mu(R_1 + R_2)}{(1 + \mu)R_1 + R_2}$$

이상) 3) op-amp  $\approx$  ideal ( $\mu = \infty$ )로 가정했을 때
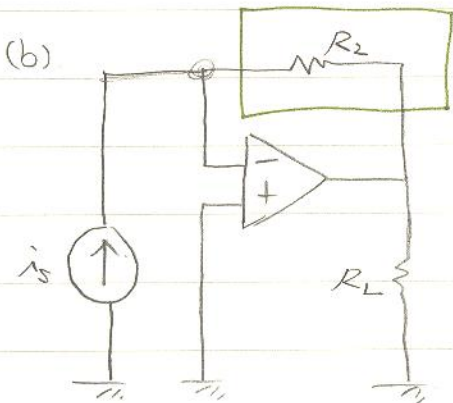
$$\lim_{\mu \rightarrow \infty} A_f = \lim_{\mu \rightarrow \infty} \frac{\mu(R_1 + R_2)}{(1 + \mu)R_1 + R_2} = \frac{R_1 + R_2}{R_1} = \frac{1}{\beta}$$



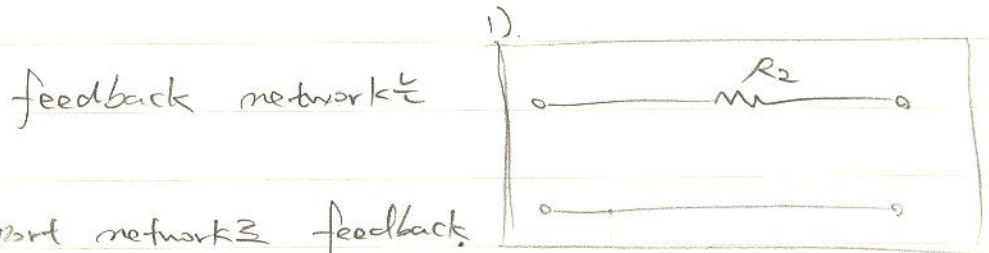output voltage  $\approx$  shunt  $\approx$  sense  $\approx$  signal current  
of shunt  $\approx$  current  $\approx$  mix  $\approx$  있다  
 $\rightarrow$  shunt-shunt  $\approx$




이때 y-parameter two-port network  $\approx$  feedback  
회로를 대체  $\rightarrow$  A-circuit과  $\beta$ -circuit의 구성.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow \begin{aligned} I_1 &= y_{11}V_1 + y_{12}V_2 \\ I_2 &= y_{21}V_1 + y_{22}V_2 \end{aligned} \Rightarrow y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}, y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}, y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$\Rightarrow y_{11} = \frac{1}{R_2}, y_{22} = \frac{1}{R_2}, y_{12} = -\frac{1}{R_2}$$

A-circuit을 다시 그려

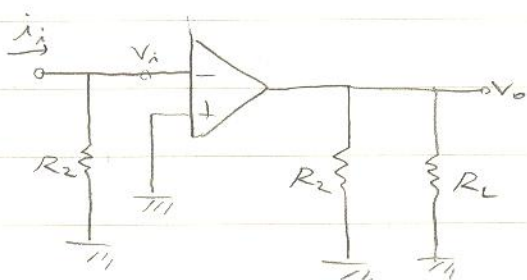

$$A = \frac{V_o}{i_i}$$

$$V_i = i_i R_2 \quad (\because \text{ideal op-amp } \approx \text{가정})$$

$$V_o = -\mu V_i \quad (\because \text{op-amp의 gain을 } \mu \text{로 가정})$$






$$\Rightarrow \boxed{A} = \frac{V_o}{V_i} = \frac{V_i}{I_i} \cdot \frac{V_o}{V_i} = R_2(-\mu) = \boxed{-R_2\mu}$$


$$\boxed{\beta} = \beta_{12} = \boxed{-\frac{1}{R_2}} \Rightarrow A_f = \frac{A}{1+A\beta} = \frac{-R_2\mu}{1+(-R_2\mu) \cdot (-\frac{1}{R_2})} = \frac{-R_2\mu}{1+\mu}$$
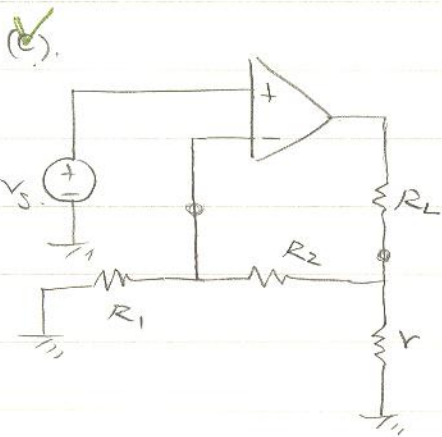
$$3) \lim_{\mu \rightarrow \infty} A_f = \lim_{\mu \rightarrow \infty} \frac{-R_2\mu}{1+\mu} = -R_2 = \boxed{\frac{1}{\beta}}$$



2) output current  $\Xi$  series  $\Xi$  sense  $\Xi$  signal  $\Xi$  voltage  
 $\Xi$  series  $\Xi$  mix  $\Xi$  feedback  $\Xi$   
 $\rightarrow$  series-series  $\Xi$

feedback network

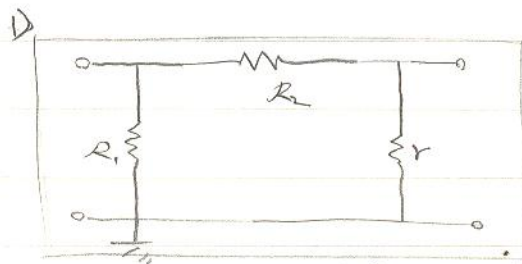


series-series  $\Xi$   $\Rightarrow$  z-parameter 평가  $\Xi$  사용

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \Rightarrow \begin{aligned} V_1 &= Z_{11}I_1 + Z_{12}I_2 \\ V_2 &= Z_{21}I_1 + Z_{22}I_2 \end{aligned} \Rightarrow Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}, Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}, Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{11} = R_1 \parallel (R_2 + r), Z_{22} = r \parallel (R_1 + R_2), Z_{12} = \frac{r}{(R_1 + R_2) + r} R_1$$

A-circuit  $\Xi$   $\Xi$   $\Xi$

$$A = \frac{I_o}{V_i}$$

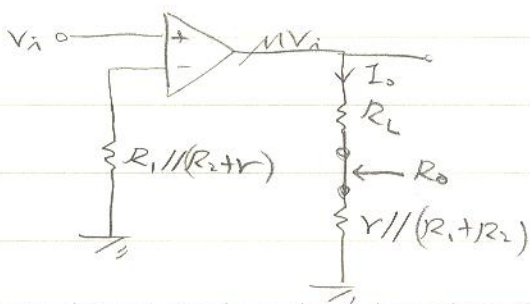

$$\mu V_i = I_o (R_L + r \parallel (R_1 + R_2))$$

$$\Rightarrow \boxed{A} = \frac{I_o}{V_i} = \boxed{\frac{\mu}{R_L + r \parallel (R_1 + R_2)}}$$





$$\Rightarrow [A] = \frac{I_o}{i_i} = \frac{v_i}{i_i} \cdot \frac{I_o}{v_i}$$

$$= (R_2 + r) \left( \frac{-\mu}{R_L + R_2 // r} \right)$$

$$[B] = g_{m2} = \frac{-r}{R_2 + r}$$

$$A_f = \frac{A}{1 + AB} = \frac{-(R_2 + r)\mu / (R_L + R_2 // r)}{1 + (R_2 + r) \left( \frac{-\mu}{R_L + R_2 // r} \right) \left( \frac{-r}{R_2 + r} \right)}$$


$$3) \lim_{\mu \rightarrow \infty} A_f = \frac{(R_2 + r)}{(R_L + R_2 // r) \cdot (R_2 + r)r} = -\frac{R_2 + r}{r} = \frac{1}{\beta}$$

8.33 문제)에 주어진 것은 series-shunt amplifier.

feedback factor  $\beta = 1$ .

$$K_n' = 2k_p' = 120 \mu A / V^2, \quad |V_{th}| = 0.7V, \quad |V_{th}'| = 24V / \mu m.$$

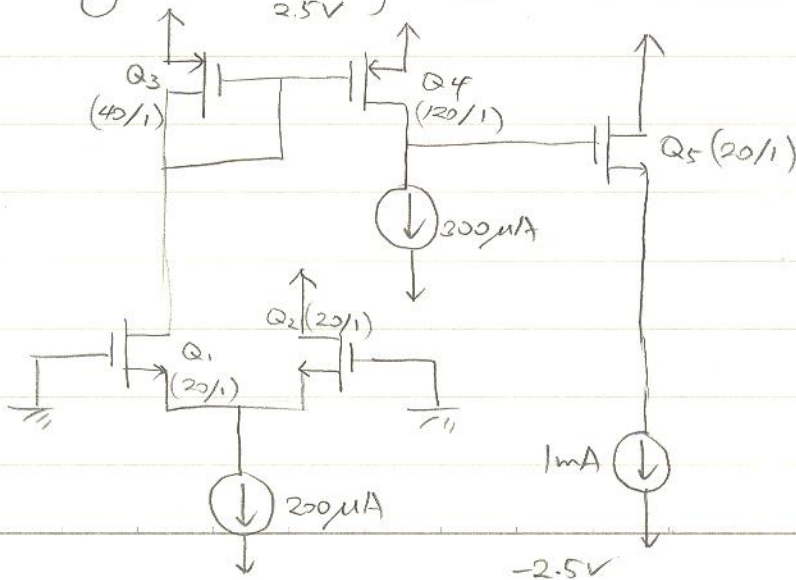(a) with the feedback loop opened and the gate terminals of  $Q_1$  and  $Q_2$  grounded  $\Rightarrow$  find the DC current & the  $V_{ov}$  at each of  $Q_1$  to  $Q_5$







\*  $I_{Q4}$ 는 전류원(이러) 300 $\mu$ A가  
타는것인가? 아닌 전류(이러)  
출력을 전류원으로 그린것인가?

$Q_1$ 과  $Q_2$ 의 bias current를  $I_{Q1}$ ,  $I_{Q2}$ 라 할때

$Q_1$ ,  $Q_2$ 는 동상(은드) 입력이 있고, 완벽히 정합(은)되어 있(은)다(∵ drain voltages의 차이로 인한  $I_D$ 의 mismatch 무시).

$$|I_{Q1}| = |I_{Q2}| = \frac{1}{2}(200\mu A) = 100\mu A$$

이 전류는 이러(은) 입력 트랜지스터  $Q_3$ 를 통해 공급(은)될 것(은)임

$$I_{Q3} = 100\mu A$$

$$\text{이때 } |I_{Q4}| = \frac{(W/L)_4}{(W/L)_3} I_{Q3} = \frac{120}{40} I_{Q3} = 3I_{Q3} = 300\mu A$$

$$|I_{Q5}| = 1\text{mA}$$

은(은)기(은)어(은)기(은)러(은)러(은) Q<sub>1</sub> ~ Q<sub>5</sub>가 은(은)드(은) 동(은)상(은)인(은)다고 가정(은)하면

$$I_{Q1} = \frac{1}{2} k_n' \left(\frac{W}{L}\right) V_{ov1}^2 \Rightarrow 100\mu = \frac{1}{2} \cdot 120\mu \cdot 20 V_{ov1}^2 \Rightarrow V_{ov1} = 0.29V$$

$$\text{이(은)런(은)가(은)리(은)로 } 100\mu = \frac{1}{2} \cdot 120\mu \cdot 20 V_{ov2}^2 \Rightarrow V_{ov2} = 0.29V$$

$$100\mu A = \frac{1}{2} \cdot 60\mu \cdot 40 V_{ov3}^2 \Rightarrow V_{ov3} = 0.29V$$

$$300\mu = \frac{1}{2} \cdot 60\mu \cdot 120 V_{ov4}^2 \Rightarrow V_{ov4} = 0.29V$$

$$1000\mu = \frac{1}{2} \cdot 120\mu \cdot 20 V_{ov5}^2 \Rightarrow V_{ov5} = 0.91V$$

(b). for  $Q_1$

$$|g_{m1}| = \sqrt{2k_n'(W/L)I_{Q1}} = \sqrt{2(120\mu)(20)100\mu} = 692.82\mu = 693\mu A/V$$

$$r_{o1} = \frac{|V_A|}{I_{Q1}} = \frac{24V/\mu m \cdot 1\mu m}{100\mu} = 240k\Omega$$

for  $Q_2$

$$|g_{m2}| = \sqrt{2(120\mu)(20)100\mu} = g_{m1} = 693\mu A/V$$

$$r_{o2} = \frac{|V_A|}{I_{Q2}} = r_{o1} = 240k\Omega$$

for  $Q_3$

$$|g_{m3}| = \sqrt{2(60\mu)(40)100\mu} = 693\mu A/V$$

$$r_{o3} = 240k\Omega$$



for Q4

$$g_{m4} = \sqrt{2(60\mu)(120)(300\mu)} = 2078 \mu A/V$$


$$r_{o4} = 24/300\mu = 80 k\Omega$$

for Q5

$$g_{m5} = \sqrt{2(60\mu)20(100\mu)} = 1550 \mu A/V$$

$$r_{o5} = 24/100\mu = 24 k\Omega$$

(c)

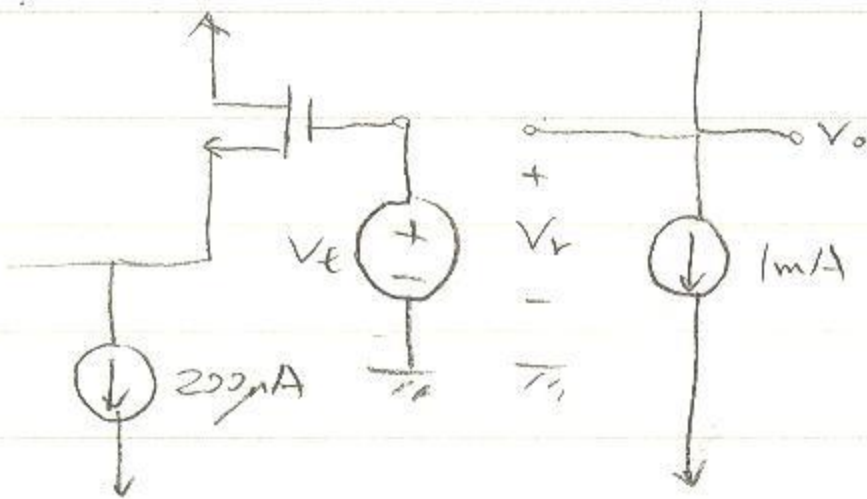

일의 그린치런 가우어 쿠라이

$$-\frac{V_f}{V_r} = A\beta \approx g_{m1}(r_{o1} || r_{o3})$$

$$\beta = 1 \quad |A| = g_{m1}(r_{o1} || r_{o3}) = 84$$

$$(d) A_f = \frac{A}{1+A\beta} = \frac{84}{1+84} = 0.908 V/V$$

$$R_o = r_{o5} = 24 k\Omega$$

$$R_{of} = \frac{R_o}{1+A\beta} = \frac{24 k\Omega}{85} = 280 \Omega$$

(e)  $V_o/V_s = 5$  를 얻기 위하여 feedback connection을 voltage division  $R_1/(R_1+R_2)$  를 통해 이루면  $\beta' = 1/5.3$

$$\Rightarrow A_f = \frac{84}{1+84/5.3} = \frac{84}{16.8} = 5$$

$$\text{이때 } 1+A\beta' = 16.8$$

$$R'_{of} = \frac{R_o}{1+A\beta'} = \frac{24}{16.8} = 1428 \Omega$$



8-39. 이회로는 series-series feedback으로  
 분석 가능하다

$Q_1, Q_2, // Q_3, Q_4$ 가 완전히 정합되었으므로

$$\underline{I_{Q_1} = I_{Q_2} = 0.1 \text{ mA} = I_{Q_3} = I_{Q_4}}$$

$$I_{Q_5} = 0.8 \text{ mA}$$

구한  $I$  값들로  $g_m$ 과  $r_o$ 들의 값을 모두 구할 수 있다

$$\rightarrow g_{m1} = \sqrt{2(20 \mu\text{A/V}) \frac{36}{10}(0.1 \text{ mA})} = 120 \mu\text{A/V}$$

$$\underline{g_{m2} = g_{m1} = 120 \mu\text{A/V} = g_{m3} = g_{m4}}$$


$$g_{m5} = \sqrt{2(20 \mu\text{A/V})(200)(800 \mu\text{A})} = 800 \mu\text{A/V}$$

$$r_{o1} = \frac{|V_A|}{I_{Q_1}} = 1 \text{ M}\Omega$$

$$\underline{r_{o2} = r_{o1} = 1 \text{ M}\Omega = r_{o3} = r_{o4}}$$


$$r_{o5} = \frac{|V_A|}{I_{Q_5}} = \frac{100 \text{ V}}{800 \mu\text{A}} = 125 \text{ k}\Omega$$

이제  $\beta$  값을 구하자

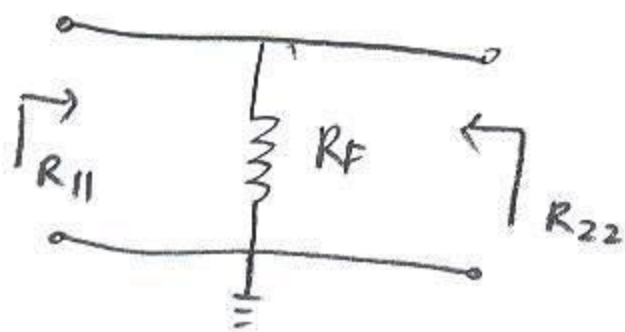


$$R_{11} = R_F = 10 \text{ k}\Omega$$

$$R_{22} = R_F = 10 \text{ k}\Omega$$

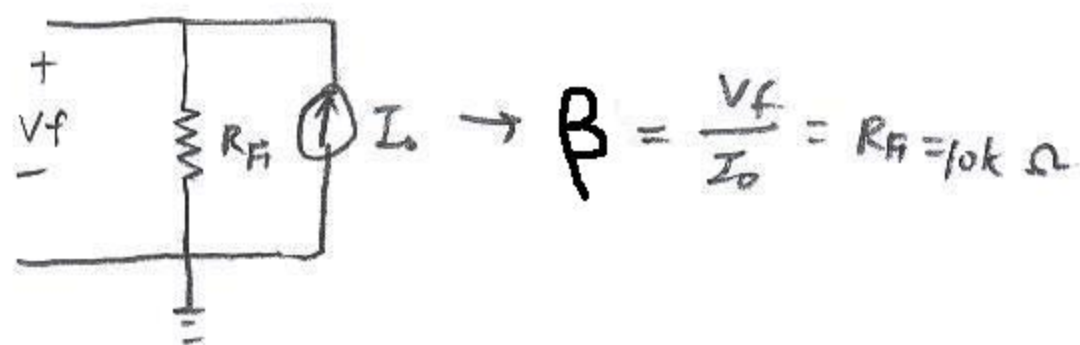




아래 A circuit을 첫번째와 두번째로 나누어 생각  
 첫 번째

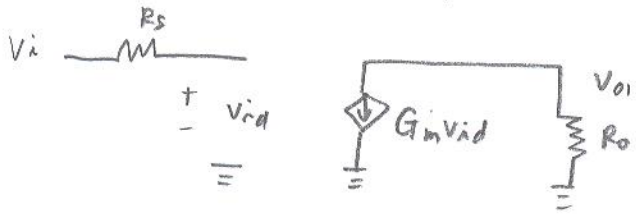

$$R_o = r_{o2} \parallel r_{o4}$$

$$G_m = g_{m2}$$
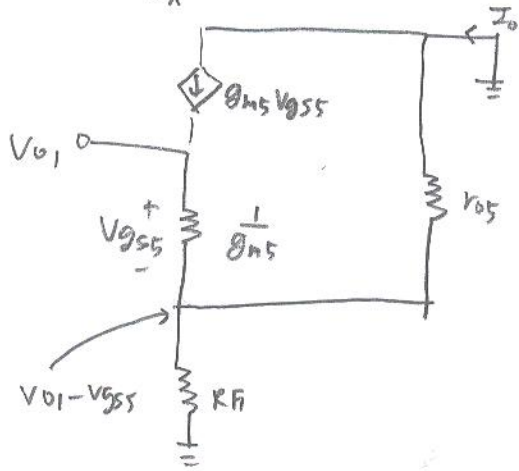
$$\rightarrow \frac{V_o}{V_i} = -G_m R_o = -g_{m2} (r_{o2} \parallel r_{o4}) \quad \text{--- ①}$$



$$\frac{I_o}{V_{o1}} = \frac{I_o}{V_{gs5}} \cdot \frac{V_{gs5}}{V_{o1}} = g_{m5} \frac{\frac{1}{g_{m5}}}{\frac{1}{g_{m5}} + R_F \parallel r_{o5}} \quad \text{--- ②}$$

$$= \frac{1}{g_{m5} + R_F / r_{o5}}$$

①, ②를

$$A = \frac{V_{o1}}{V_i} \cdot \frac{I_o}{V_{o1}} = -g_{m2} (r_{o2} \parallel r_{o4}) \frac{1}{g_{m5} + R_F / r_{o5}}$$

$$= -20 \mu (1M \parallel 1M) \left( \frac{-5.85 \text{ mA/V}}{1.25k + 9.25k} \right)$$

$$= \textcircled{5.85 \text{ mA/V}}$$

$$A_f = \frac{A}{1 + A \beta}$$

$$= \frac{-5.85 \text{ mA/V}}{1 + (-5.85 \text{ mA/V})(10k \Omega)}$$


$$= \textcircled{-98.3 \text{ mA/V}}$$

$$\frac{V_o}{V_s} = \frac{I_o}{V_s} (R_F \parallel r_{o5})$$

$$= (-98.3 \text{ mA/V})(10k \parallel 125k) = \textcircled{-0.909 \text{ V/V}}$$


8-42 shunt-shunt 구조이신 전압 증폭회로

10-

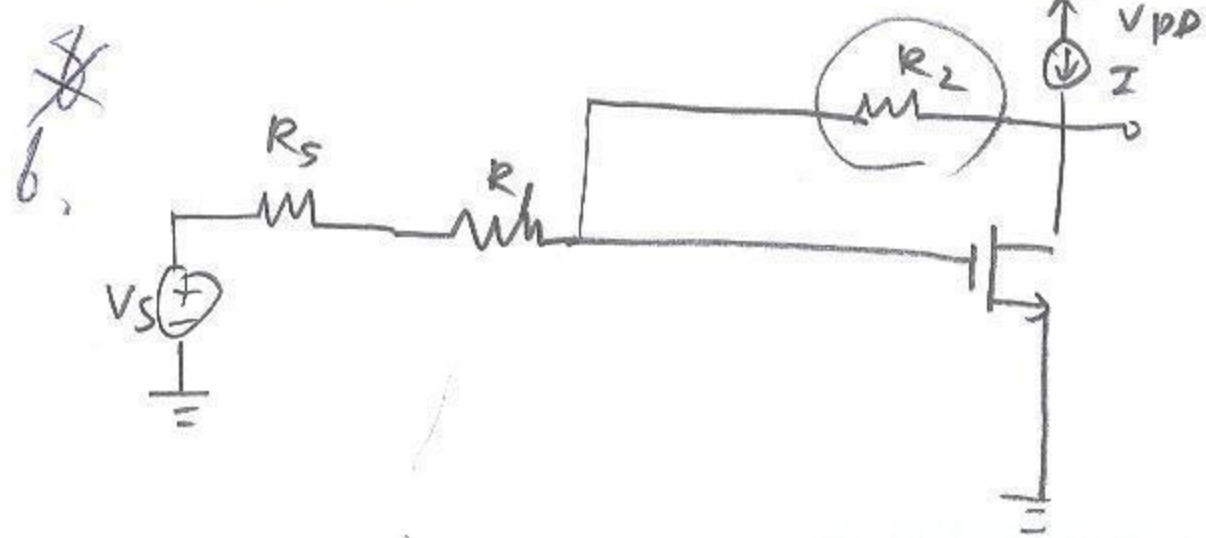

$I_0 = I = 1\text{mA}$  라고

회로를 2개의 y parameter로 분석


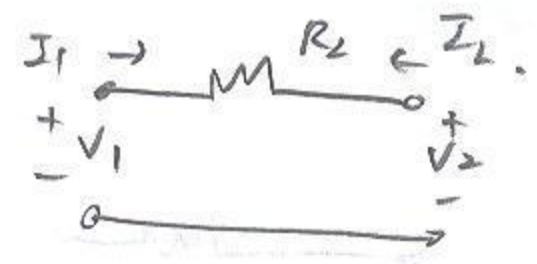


$Y_{11} = \frac{1}{R_2} \rightarrow$  이드미턴스  $R_{11} = R_2 = R_{22}$  ( $\because$  shunt shunt)

$Y_{12} = \beta = \frac{I_1}{V_2} \Big|_{V_1=0} = -\frac{1}{R_2}$

A circuit은 Norton 방식에 따라 등가회로로 바꾸면 ( $\because$  shunt-shunt 이므로

전류  $\rightarrow$  전압이행)

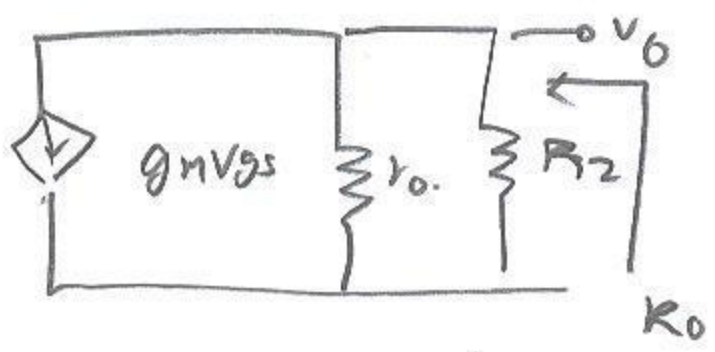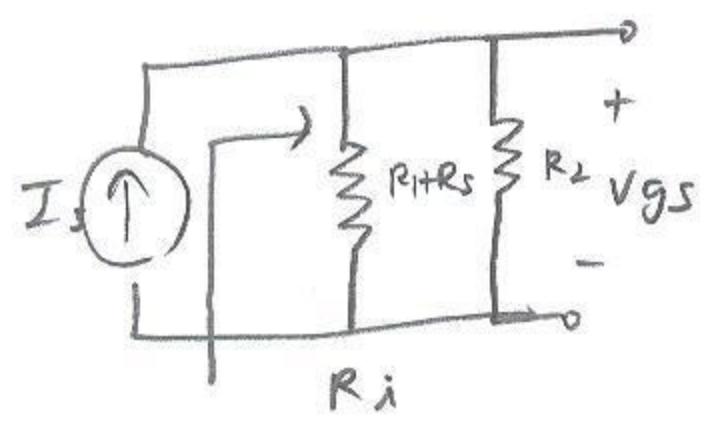

$A = \frac{V_O}{I_S}$

$\frac{V_O}{V_{GS}} = -g_m (r_o \parallel R_2) \quad \text{--- ①}$

$\frac{V_{GS}}{I_S} = (R_1 + R_S) \parallel R_2 \quad \text{--- ②}$

$\therefore \textcircled{1} \times \textcircled{2} = A = (-10\text{m}) (30\text{k} \parallel 4.7\text{M}) [ (1\text{M} + 10\text{k}\Omega) \parallel 4.7\text{M} ]$   
 $= (-10\text{m}) (29.9\text{k}) (831\text{k})$   
 $= -248469 \text{ MV/A}$



$$11 \beta = y_k = -\frac{1}{R_2} = -\frac{1}{4.7 \text{ M}}$$

12

$$A_f = \frac{A}{1 + A\beta} = \frac{-248469 \text{ k}}{1 + (248469 \text{ k}) \left(\frac{1}{4.7 \text{ M}}\right)}$$

$$= -4.6127 \times 10^6 \text{ V/A}$$

$$\begin{aligned} \Rightarrow \frac{V_o}{V_s} &= \frac{V_o}{I_s} \cdot \frac{I}{R_2 + R_1} = A_f \frac{1}{1.01 \text{ M}} \\ &= -4.6127 \text{ M} \cdot \frac{1}{1.01 \text{ M}} \\ &= -4.567 \text{ V/V} \end{aligned}$$

$$\begin{aligned} R_i &= (R_1 + R_5) \parallel R_2 \\ &= (1.01 \text{ M}) \parallel (4.7 \text{ M}) = 831 \text{ k}\Omega \end{aligned}$$

$$R_{if} = \frac{R_i}{1 + A\beta} \quad (\because \text{shunt})$$

$$= \frac{831 \text{ k}\Omega}{53.866} = 15.427 \text{ k}\Omega$$

$$\begin{aligned} R_{in} &= R_{if} - R_s = 15.427 \text{ k}\Omega - 10 \text{ k}\Omega \\ &= 5.427 \text{ k}\Omega \end{aligned}$$

$$R_o = r_o \parallel R_2 = 30 \text{ k}\Omega \parallel 4.7 \text{ M}\Omega = 29.9 \text{ k}\Omega$$

$$R_{of} = \frac{R_o}{1 + A\beta} = \frac{29.9 \text{ k}}{53.866} = 0.555 \text{ k}\Omega$$

↑  
(∵ shunt)


There's no  $R_L$  ∴  $R_{of} = R_{out}$   
 $= 0.555 \text{ k}\Omega$



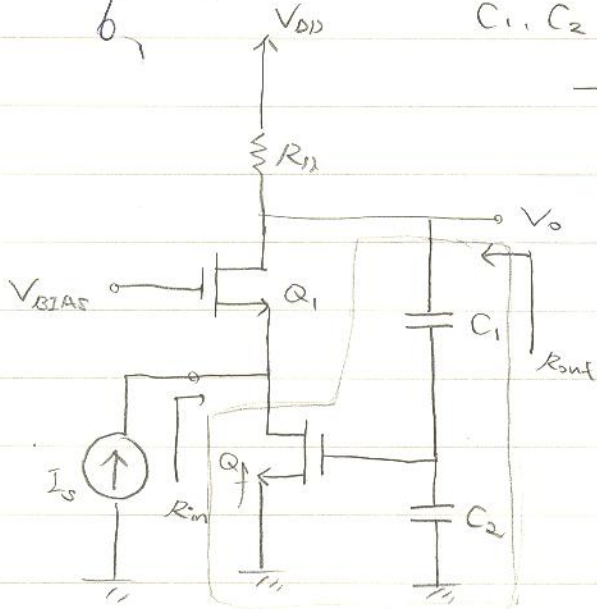8.52

$g_{m1} = 5 \text{ mA/V}$ ,  $R_D = 10 \text{ k}\Omega$ ,  $C_1 = 0.9 \text{ pF}$ ,  $C_2 = 0.1 \text{ pF}$ ,  $g_{mf} = 1 \text{ mA/V}$


$C_1, C_2$  are sufficiently small  
 $\rightarrow$  loading effect can be neglected.



shunt-shunt feedback network

feedback network

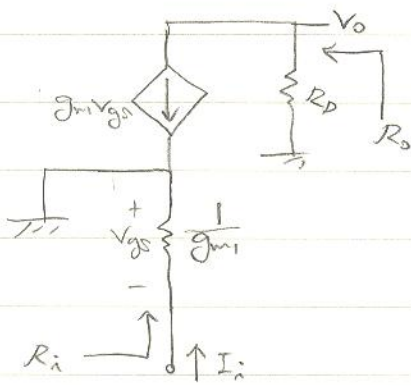수정된 A circuit (loading effect가 없도록 feedback network는 무시된다.)  
 의 회로 분석.






$$A = \frac{V_o}{I_i} = \frac{V_{gs}}{I_i} \cdot \frac{V_o}{V_{gs}}$$

$$= \left(-\frac{1}{g_{m1}}\right) \left(-g_{m1} R_D\right) = R_D$$

$$R_i = 1/g_{m1}, R_o = R_D$$

feedback parameter  $\beta$  (은) 구하기 위하여

$(v_o \rightarrow 0)$

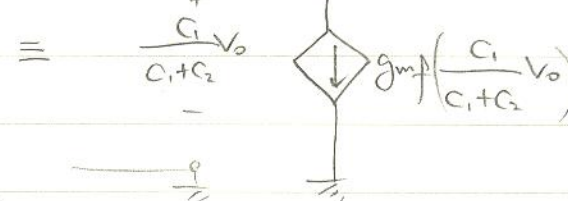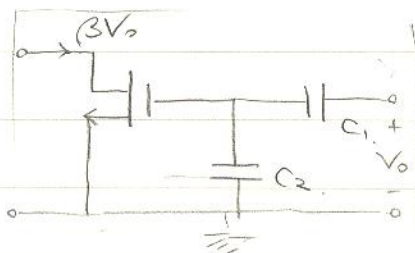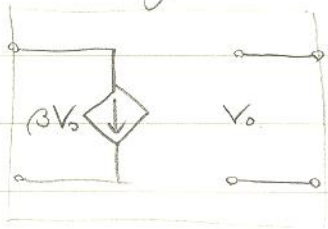

shunt-shunt feedback network의

ideal 회로





$$\beta = \frac{C_1}{C_1 + C_2} g_{mf}$$

$$\Rightarrow \boxed{A_f} = \frac{A}{1 + A\beta} = \frac{R_o}{1 + R_o \left( \frac{C_1}{C_1 + C_2} \right) g_{mf}} = \frac{10k}{1 + 10k(0.1)(1m)} = \boxed{5k\Omega}$$

$$R_{if} = \frac{R_i}{1 + A\beta} = \frac{1}{g_{m1}} \left( \frac{1}{1 + 1} \right) = \frac{1}{2g_{m1}} = \frac{1}{10m} = 0.1k\Omega$$

$$R_{in} = R_{if} = 0.1k\Omega \quad (\because Q_f \text{ 쪽으로 모든 저항은 없다고 생각})$$

$$R_{of} = \frac{R_o}{1 + A\beta} = R_o \left( \frac{1}{2} \right) = \boxed{5k\Omega = R_{out}}$$

8.75 For the amplifier described by Fig 8.37  
with  $f$ -independent feedback,  
Determine the minimum closed-loop voltage gain  
for phase margin of  $90^\circ$  and  $45^\circ$ .

① phase margin :  $90^\circ$

$$\Rightarrow \phi = -90^\circ = - \left| \tan^{-1} \left( \frac{f}{10^5} \right) + \tan^{-1} \left( \frac{f}{10^6} \right) + \tan^{-1} \left( \frac{f}{10^7} \right) \right|$$

$$\Rightarrow \tan^{-1} \left( \frac{f}{10^5} \right) + \tan^{-1} \left( \frac{f}{10^6} \right) + \tan^{-1} \left( \frac{f}{10^7} \right) = 90^\circ$$

$\Rightarrow$  그림으로 부터 대충  $f = 3 \times 10^5 \text{ Hz}$  로 놓고 계산을 해보면

$$\tan^{-1} \left( \frac{f}{10^5} \right) + \tan^{-1} \left( \frac{f}{10^6} \right) + \tan^{-1} \left( \frac{f}{10^7} \right) \Big|_{f=3 \times 10^5 \text{ Hz}} = 89.9^\circ$$

$\therefore 90^\circ$  의 phase margin 을 갖는 frequency 를  $3 \times 10^5 \text{ Hz}$  로 결정..

한편 phase margin 을 결정하는 frequency 는  $20 \log |A(j\omega)|$  라

$20 \log \frac{1}{\beta}$  이 교차하는 frequency 를 이 때,  $20 \log |A\beta| = 0 \quad \therefore |A\beta| = 1$ .



1) req  $|A(f_1)| = \left| \frac{10^5}{(1+jf/10^5)(1+jf/10^6)(1+jf/10^7)} \right|_{f=f_1}$  from (8.79)

$$= \frac{10^5}{\sqrt{1+3^2} \sqrt{1+0.3^2} \sqrt{1+0.03^2}} = 30.28 \times 10^3$$

from  $|A\beta| = 1 \Rightarrow \beta = 33.0 \times 10^{-6}$

$\therefore$  minimum closed-loop voltage gain

$$= |A_f(j\omega)| = \frac{A_{mid}}{1 + A_{mid}\beta} = \frac{10^5}{1 + 10^5(33.0 \times 10^{-6})} = 2.32 \times 10^4$$

2) phase margin:  $45^\circ$

$$45^\circ = \tan^{-1}\left(\frac{f}{10^5}\right) + \tan^{-1}\left(\frac{f}{10^6}\right) + \tan^{-1}\left(\frac{f}{10^7}\right)$$

그림으로부터  $f = 10^6$  Hz. 를 결정.

이 frequency에서  $20 \log |A(j\omega)|$  와  $20 \log \frac{1}{\beta}$  의 차이가 phase margin  $45^\circ$  가 발생하므로,


$|A\beta|_{f=10^6} = 1$  1) req  $|A(f)| = \frac{10^5}{\sqrt{1+1^2} \sqrt{1+1^2} \sqrt{1+0.1^2}} = 7 \times 10^3$

$\Rightarrow \beta = 1.43 \times 10^{-4}$

minimum closed-loop voltage gain

$$A_f(j\omega) = \frac{10^5}{1 + 10^5(1.43 \times 10^{-4})} = 6.54 \times 10^3$$

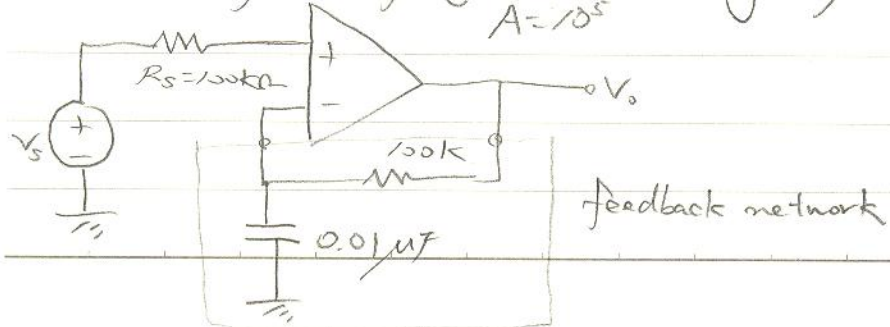8.81 (b) open-loop gain  $10^5$ , single-pole rolloff  $\omega_{3dB} = 10$  rad/s  
 $A = 10^5$










(a) Sketch a Bode plot for the loop gain

- feedback network의 loading effect를 고려하지 않으면 ideal

\* check


series-shunt feedback network  
 이 경우

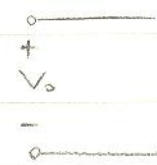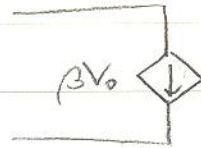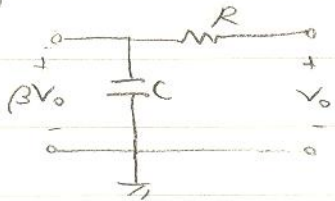

이 경우

$$\Rightarrow \beta(s) = \frac{1/sC}{1/sC + R} = \frac{1}{1 + sCR} = \frac{1}{1 + s/10^3}$$
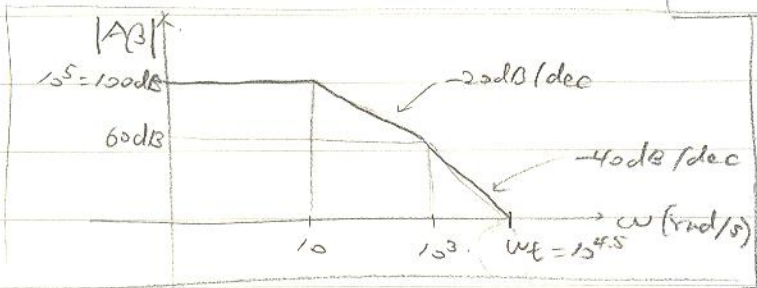
$$A\beta(s) = A(s)\beta(s) = \frac{10^5}{1 + s/10} \cdot \frac{1}{1 + s/10^3}$$



(b) the frequency at which  $|A\beta| = 1$

$$|A\beta| = 1 \Rightarrow 20 \log |A\beta| = 0 \text{ dB}$$

$$\omega_c = 10^{4.5} \text{ (rad/s)} = 31.6 \times 10^3 \text{ rad/s}$$

$$(c) A_f(s) = \frac{10^5}{1 + s/10} \cdot \frac{1}{1 + \frac{10^5}{1 + s/10} \cdot \frac{1}{1 + s/10^3}} = \frac{10^5 (1 + s/10^3)}{(1 + s/10)(1 + s/10^3) + 10^5}$$

$$= \frac{10^6 s + 10^9}{s^2 + 10^3 s + 10^9}$$

Zero at  $\omega = -10^3 \text{ rad/s}$

$$\text{poles at } \omega = \frac{-10^3 \pm \sqrt{10^6 - 4 \times 10^9}}{2} = -500 \pm j 31.6 \times 10^3 \text{ rad/s}$$

$$\omega_0 = 31.6 \text{ krad/s}$$

$$Q = 31.6$$

