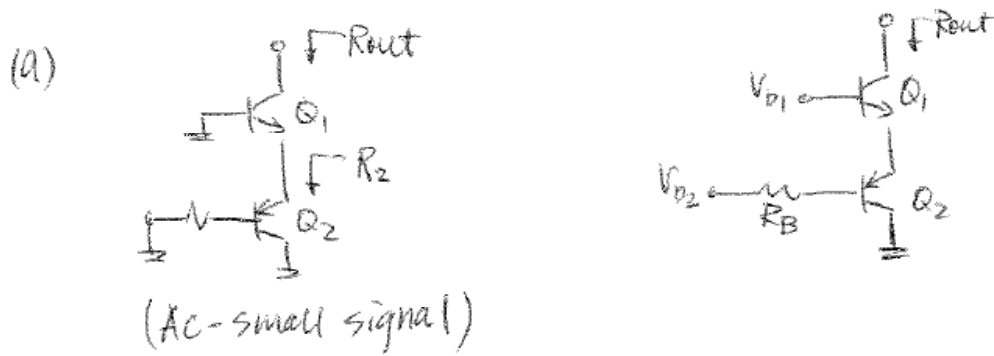


1.

Chapter 9.8




Looking into emitter of Q_2 .

$$R_2 = \frac{1}{\left(\frac{\beta+1}{R_B + r_{\pi 2}} + \frac{1}{r_{o2}}\right)}$$

$$\Rightarrow R_{out} = [1 + g_{m1}(R_2 \parallel r_{\pi 1})] r_{o1} + (R_2 \parallel r_{\pi 1})$$

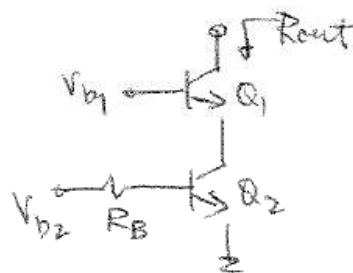(b) R_B does not affect Q_2 in small-signal R_{out} :

$$\therefore R_{out} = [1 + g_{m1}(r_{o2} \parallel r_{\pi 1})] r_{o1} + (r_{o2} \parallel r_{\pi 1})$$




This is a cascode stage.

$$A_v = -g_{m1} r_{o1} g_{m1} (r_{o1} \parallel r_{\pi2})$$

$$= -\frac{I_{c1}}{V_T} \cdot \frac{V_{A1}}{I_{c1}} \cdot \frac{I_{c1}}{V_T} \cdot \frac{1}{\frac{I_{c1}}{V_{A1}} + \frac{I_{c2}}{\beta V_T}}$$

Since $I_{c1} \approx I_{c2}$,
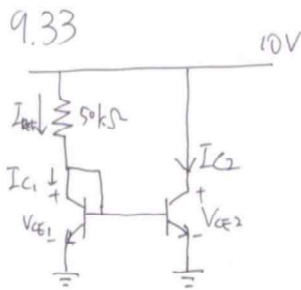
$$A_v \approx -\frac{V_{A1}/V_T^2}{\frac{1}{V_{A1}} + \frac{1}{\beta V_T}} = -\frac{\beta V_A^2}{V_T(V_A + \beta V_T)}$$



$$\beta = 75, \quad I_s = 2 \times 10^{-16} \text{ A}, \quad V_T = 26 \text{ mV}, \quad V_A = 50 \text{ mV}$$

$$I_{C1} = I_s \exp\left(\frac{V_{CE1}}{V_T}\right) \left(1 + \frac{V_{CE1}}{V_A}\right)$$

$$V_T \ln\left[\frac{I_C}{I_s} \frac{V_A}{V_A + V_{CE1}}\right] = V_{CE1} \quad \dots \textcircled{1}$$

$$I_{REF} = I_C \left(1 + \frac{2}{\beta}\right) \quad (\text{Assume two bjts are identical})$$

$$V_{CE1} = 10 - 50 \times 10^3 I_{REF} = 10 - 50 \times 10^3 I_C \times \frac{17}{75} \quad \dots \textcircled{2}$$

$$\text{From } \textcircled{1} \text{ and } \textcircled{2}, \quad V_{CE1} = 115.4 \text{ mV.}$$

$$I_{C2} = I_s \exp\left(\frac{0.1154}{0.026}\right) \times \left(1 + \frac{10}{50}\right)$$

$$= \underline{\underline{0.214 \text{ mA}}}$$

9.40

$$I_{REF} = \frac{V_{DD} - V_{GS1}}{R} = 2 \text{ mA}$$

$$2 \text{ mA} = \frac{1}{2} k_n \frac{W}{L} (V_{GS1} - V_{th})^2$$

$$= \frac{1}{2} \times 20 \mu\text{A} \times \left(\frac{W}{L}\right)_1 \times (1 - 0.4)^2$$

$$\therefore \left(\frac{W}{L}\right)_1 \approx 556$$

—————>>

Given power budget = 2mW
 $V_{BC1} = V_{CB4} = 200\text{ mV}$,
 calculate voltage gain.

$$\alpha_p = \frac{50}{50+1} \approx 0.98$$

$$\alpha_n = \frac{100}{100+1} \approx 0.99$$

\therefore we assume $I_{c,p} \approx I_{e,p}$ & $I_{c,n} \approx I_{e,n}$

This implies that $I_{BIAS} = \frac{\text{Power}}{V_{cc}} = \frac{2\text{mW}}{2.5\text{V}}$
 $\approx 0.8\text{mA}$.

$$\Rightarrow V_{BE1} = V_{in} = V_T \ln\left(\frac{I_{BIAS}}{I_{S1}}\right) = (0.026\text{V}) \cdot \ln\left(\frac{0.8\text{mA}}{6 \cdot 10^{-16}\text{A}}\right) \approx 0.726\text{V}$$


$$V_{C11} = V_{BE1} - V_{BE4} = 0.726\text{V} - 0.2\text{V} = 0.526\text{V}$$

$$\therefore V_{D1} = V_{C1} + V_{BE2} = (0.526\text{V}) + (0.026\text{V}) \ln\left(\frac{0.8\text{mA}}{6 \cdot 10^{-16}\text{A}}\right)$$

$$\approx 1.252\text{V}$$

$$\Rightarrow V_{EB4} = V_{cc} - V_{b3} = V_T \ln\left(\frac{I_{BIAS}}{I_{S4}}\right) = 0.026\text{V} \cdot \ln\left(\frac{0.8\text{mA}}{6 \cdot 10^{-16}\text{A}}\right)$$

$$\approx 0.726\text{V}$$

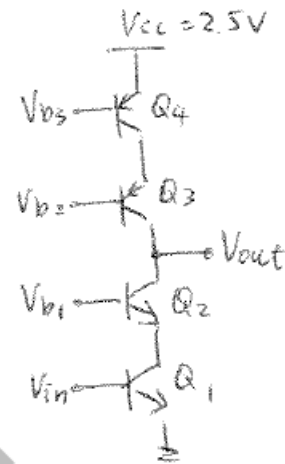

$$V_{b3} = V_{cc} - 0.726V = 1.774V$$

$$V_{c4} = V_{D3} + V_{CEB4} = 1.774V + 0.2V = 1.974V$$

$$\therefore V_{D2} = V_{c4} - V_{EB3} = (1.974V) - (0.026) \ln\left(\frac{0.8mA}{6 \cdot 10^{-16}A}\right)$$

$$\approx 1.248V$$


$$A_v = -g_{m1} \left\{ [g_{m2} r_{o2} (r_{o1} \parallel r_{\pi 2})] \parallel [g_{m3} r_{o3} (r_{o4} \parallel r_{\pi 3})] \right\}$$

After simplifying, A_v is independent of I_{BIAS} :

$$A_v \approx \frac{V_{AN} - V_{AP}}{V_T^2 \left(\frac{V_{AP}}{V_{AN}} + \frac{V_{AP}}{\beta_N V_T} + \frac{V_{AN}}{V_{AP}} + \frac{V_{AN}}{\beta_P V_T} \right)}$$

$$= \frac{5.5}{(0.026V)^2 \left(\frac{5}{5} + \frac{5}{100 \cdot 0.026} + \frac{5}{5} + \frac{5}{50 \cdot 0.026} \right)}$$

$$\approx 4760$$

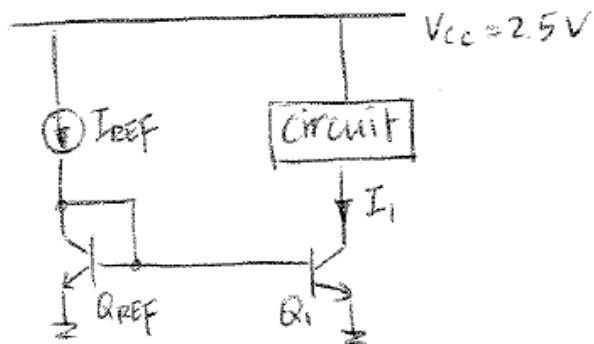

$$I_1 = 0.5 \text{ mA}$$


$$\text{power} = 2 \text{ mW}$$

$$\text{Power} = V_{CC} (I_{REF} + I_1)$$

$$\Rightarrow I_{REF} = \frac{\text{Power}}{V_{CC}} - I_1 = \frac{2 \text{ mW}}{2.5 \text{ V}} - 0.5 \text{ mA} = 0.3 \text{ mA}$$

Therefore, if Q_{REF} has area A_E , then Q_1 has area $\frac{5}{3} A_E$ for the currents specified.
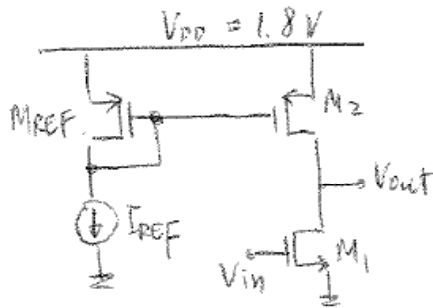
$$\text{i.e. } \frac{A_{REF}}{A_1} = \frac{3}{5}$$



$$A_v = -20$$

$$\text{power} = 2 \text{ mW}$$

$$\left(\frac{W}{L}\right)_1 = \frac{20}{0.18} \quad \lambda_n = 0.1 \text{ V}^{-1}$$

$$\lambda_p = 0.2 \text{ V}^{-1}$$

$$R_{out} = r_{o2} \parallel r_{o1} = \frac{1}{\lambda_n I_{D1} + \lambda_p I_{D1}}$$

$$\Rightarrow A_v = -g_{m1} R_{out} = -\frac{g_{m1}}{\lambda_n I_{D1} + \lambda_p I_{D1}} = -\frac{2 I_{D1} (V_{GS1} - V_{THn})}{I_{D1} (\lambda_n + \lambda_p)}$$

$$\Rightarrow -20 = -\frac{2}{(V_{GS1} - V_{THn}) (\lambda_n + \lambda_p)}$$

$$\Rightarrow V_{GS1} = \frac{1}{10 (\lambda_n + \lambda_p)} + V_{THn}$$

$$= \frac{1}{10 (0.1 + 0.2) \text{ V}^{-1}} + 0.4 \text{ V} \approx 0.73 \text{ V}$$

$$\Rightarrow I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{THn})^2$$

$$= \frac{1}{2} (100 \frac{\mu\text{A}}{\text{V}^2}) \left(\frac{20}{0.18}\right) (0.33 \text{ V})^2 \approx 0.61 \text{ mA}$$

$$\therefore \text{power} = V_{DD} (I_{REF} + I_{D1})$$

$$\Rightarrow I_{REF} = \frac{\text{power}}{V_{DD}} - I_{D1} = \frac{2 \text{ mW}}{1.8 \text{ V}} - 0.61 \text{ mA}$$

$$\approx 0.5 \text{ mA}$$

∴ if M_{REF} has $(\frac{W}{L})_{REF}$, then

$$\frac{(\frac{W}{L})_2}{(\frac{W}{L})_{REF}} = \frac{I_{D2}}{I_{REF}} = \frac{61}{50} \approx 1.2$$

2. a) $V_1 = V_{ov1} + V_{TH}$

$$I_{REF} = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} V_{ov1}^2 = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} V_{ov2}^2, \quad V_{ov1} = V_{ov2}$$

$$\therefore V_2 = V_1 + V_{ov2} + V_{TH} = 2(V_{ov1} + V_{TH})$$

b) $V_{ov1} = V_{ov3} = V_{ov2} = V_{ov4}$

To keep M3 in the saturation region, $V_{DS3} \geq V_1 - V_{TH}$

To keep M4 in the saturation region, $V_{out} \geq V_2 - V_{TH}$

Therefore, $V_{out} \geq 2V_{ov1} + V_{TH}$

c) $V_1 = V_{ov1} + V_{TH}$

$$I_{REF} = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} V_{ov1}^2 = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} V_{ov2}^2, \quad V_{ov1} = V_{ov2}$$

To keep M1 in saturation region, $V_{DS1} \geq V_{ov1}$

$$V_2 = V_{DS1} + V_{ov2} + V_{TH}$$

Therefore, $V_2 \geq 2V_{ov1} + V_{TH}$

d) $V_2 \geq 2V_{ov1} + V_{TH}$, so $V_{out} \geq V_2 - V_{TH} \geq 2V_{ov1}$

$$\therefore V_{out} \geq 2V_{ov1}$$

e) Figure 2 is better because it consumes less voltage headroom than Figure 1.

But Figure 2 need extra biasing circuit. It takes more power and area than Figure 1.

3. $V_{BE1} = V_{BE2} + I_{OUT} \times 1k\Omega$

$$V_{BE1} = V_T \ln\left(\frac{1mA}{I_S}\right), V_{BE2} = V_T \ln\left(\frac{I_{OUT}}{I_S}\right)$$

$$V_{BE1} - V_{BE2} = 26mV \times \ln\left(\frac{1mA}{I_{OUT}}\right) = I_{OUT} \times 1k\Omega$$

$$\therefore I_{OUT} = 0.069mA$$