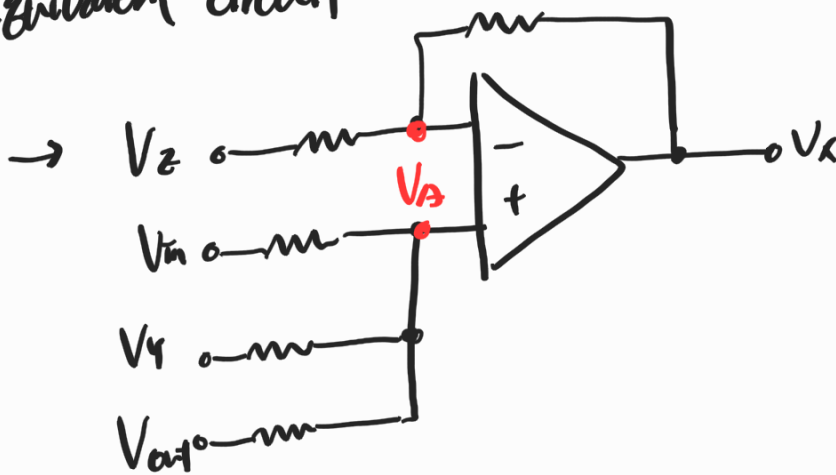


# < Prob 2 >

Equivalent circuit



$$\rightarrow \left\{ \begin{aligned} \frac{V_2 + V_x}{2} = V_A = \frac{V_{in} + V_Y + V_{out}}{3} \quad - (1) \end{aligned} \right.$$

$$V_{out} = -\frac{1}{RC_3S} V_2 \rightarrow V_2 = -RC_3S \cdot V_{out} \quad - (2)$$

$$V_2 = -\frac{1}{RC_2S} V_Y \rightarrow V_Y = R^2 C_2 C_3 S^2 V_{out} \quad - (3)$$

$$V_Y = -\frac{1}{RC_1S} V_x \rightarrow V_x = -R^3 C_1 C_2 C_3 S^3 V_{out} \quad - (4)$$

$$\textcircled{1}, \textcircled{2}, \textcircled{3}, \textcircled{4} \rightarrow H(s) = \frac{-\frac{2}{3} \frac{1}{R^3 C_1 C_2 C_3}}{s^3 + \frac{2}{3} \frac{1}{RC_1} s^2 + \frac{1}{RC_1 C_2} s + \frac{2}{3} \frac{1}{R^3 C_1 C_2 C_3}}$$

Butterworth Response  $\rightarrow H(s) = \frac{k}{(s + \omega_n) (s^2 + \frac{\omega_n}{Q} s + \omega_n^2)}$

$$P_{1,2} = 2\pi \times f_0 \times \left( \cos \frac{2}{3}\pi \pm j \sin \frac{2}{3}\pi \right),$$

$$\rightarrow \frac{\omega_0}{Q} = -(P_1 + P_2) = \omega_0 \rightarrow Q = 1, \omega_n = \sqrt[3]{\frac{2}{3} \frac{1}{R^3 C_1 C_2 C_3}}$$

$$\Rightarrow H(s) = \frac{k}{s^3 + 2\omega_n s^2 + 2\omega_n^2 s + \omega_n^3}$$

WR.

(b)

(d)  $f_0 = 1 \text{ MHz}$  &  $R = 1 \text{ k}\Omega$  &  $\text{mitte}$

$$\begin{aligned} \rightarrow 2\omega_n &= \frac{2}{3} \frac{1}{RC_1} \rightarrow \omega_n = \frac{1}{3} \cdot \frac{1}{RC_1} \rightarrow C_1 = \frac{1}{3} \cdot \frac{1}{R\omega_n} \doteq 53 \text{ pF} \\ 2\omega_n^2 &= \frac{1}{R^2 C_1 C_2} \rightarrow \omega_n = \frac{3}{2} \cdot \frac{1}{RC_2} \\ &\rightarrow C_2 = \frac{3}{2} \cdot \frac{1}{R\omega_n} \doteq 238 \text{ pF} \end{aligned}$$

$$\rightarrow \omega_n^3 = \frac{2}{3} \cdot \frac{1}{R^3 C_1 C_2 C_3} \rightarrow C_3 = \frac{2}{3} \cdot \frac{1}{R^3 \cdot C_1 C_2 \cdot \omega_n^3} \doteq 213 \text{ pF}$$