

Selected Solutions of Mid-term Exam 2

1. 3) X (is proportional \rightarrow is not proportional)
(or dispersive \rightarrow nondispersive)
- 5) X (inductive \rightarrow capacitive)
(or open-circuited \rightarrow short-circuited)
- 7) X ($\lambda/2 \rightarrow \lambda/4$)
(or neighboring... voltage minima \rightarrow successive voltage maxima (minima))
- 9) X ($(1, 0) \rightarrow (-1, 0)$)
(or open-circuit, $P_{oc} \rightarrow$ short-circuit, P_{sc})
(or admittance \rightarrow impedance)
- 14) X (wavelengths \rightarrow half-wavelengths)
- Others) 0

2. a) FIGURE 8-2

b) (8-1) \rightarrow (8-3) for $V(z, t)$, (8-4) \rightarrow (8-5) for $i(z, t)$

c) (8-8), (8-9) \rightarrow (8-10)

$$\text{where } \gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (8-12)$$

d) (8-33): $V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$ (V)

e) (8-35) & (8-38): $Z_0 = \frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = \frac{R + j\omega L}{G + j\omega C} = \frac{\gamma}{G + j\omega C} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$

f) (8-46) \sim (8-51):

$$\frac{R}{L} = \frac{G}{C}; \text{ distortionless condition in c) and e)}$$


$$\gamma = \sqrt{C/L} (R + j\omega L) \Rightarrow \alpha = R\sqrt{C/L}, \beta = \omega\sqrt{LC}$$

$$Z_0 = R_0 + jX_0 = \sqrt{L/C}$$

g) For matched lines, $\Gamma = 0$ and $V_0^- = 0$ (no reflection wave)

$$\therefore \Gamma \equiv \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} = 0 \Rightarrow \underline{Z_L = Z_0}$$

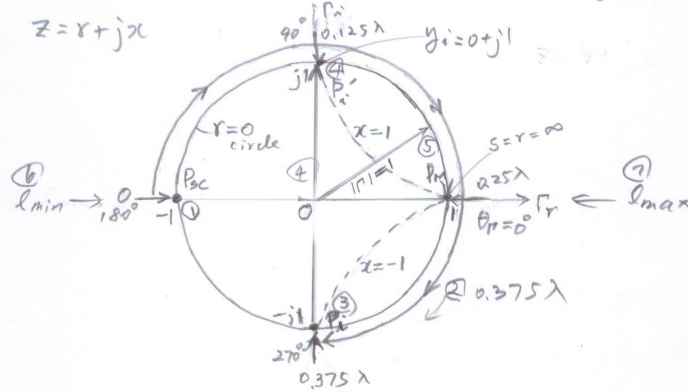3. Given (lossless short-circuited line with $l = 0.1875 \text{ (m)}$ and $Z_0 = R_0 = 5 (\Omega)$)



a) ① Locate P_{sc} , and at P_{sc} $\Gamma = \Gamma_r + j\Gamma_x = -1 + j0$
 $= |\Gamma| e^{j\theta_\Gamma} = 1 e^{j180^\circ}$

b) $f = 600 \text{ (MHz)} = 6 \times 10^8 \text{ Hz} \rightarrow \lambda = \frac{c}{f} = \frac{3 \times 10^8}{6 \times 10^8} = 0.5 \text{ (m)}$

$\therefore l = 0.1875 \text{ (m)} = \frac{0.1875}{0.5} = 0.375 \lambda$

② move P_{sc} along WTA by $\frac{l}{\lambda} = 0.375$ up to P_i at input end.

③ Read z_i at P_i , $z_i = r_i + jx_i = 0 - j1$

$\therefore Z_i = R_0 z_i = 5(0 - j1) = \underline{-j5 (\Omega)}$

c) ④ move to P_i' diametrically opposite to P_i to find y_i

Read $y_i = 0 + j1 \Rightarrow Y_i = \frac{y_i}{Z_0} = \frac{j1}{5} = \underline{j0.2 \text{ (S)}}$

d) ⑤ Draw a circle of radius $\overline{OP_{sc}} : |\Gamma| = 1.0$ and read r at P_m where the $|\Gamma| = 1.0$ circle intersects with the positive-real axis.
 $\Rightarrow \underline{S = r = \infty}$

e) ⑥ At P_{sc} where the voltage is a minimum distance from the s.c. end $\Rightarrow \underline{l_{min} = 0}$

⑦ At P_m where the voltage is a maximum distance from the s.c. end $\Rightarrow \underline{l_{max} = 0.25 \lambda}$
 $= 0.25 \times 0.5$
 $= \underline{0.125 \text{ (m)}}$

4. Given (air-filled $a \times b$ rectang. waveguide
with $\epsilon_0, \mu_0, a = \sqrt{3}b, f = 3.66 \text{ GHz}$, for TM wave
($H_z = 0, E_z = E_z^0(x, y)e^{-\gamma z}$)

a) BVP: (9-53) + (9-61) ~ (9-64)

b) (9-54) ~ (9-60)

c) (9-59)_{TM}, (9-60)_{TM} $\Rightarrow \left\{ \begin{aligned} E_z^0(x, y) &= E_0 \sin\left(\frac{m\pi x}{a}\right) \sin\left(\frac{n\pi y}{b}\right) (V/m) \quad (9-65) \\ h^2 &= \left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2, \text{ for } m, n = 1, 2, 3, \dots \quad (9-66) \end{aligned} \right.$

d) Faraday's law: $(\nabla \times \vec{E} = -j\omega\mu_0 \vec{H})_x \Rightarrow \frac{\partial E_z^0}{\partial y} + \gamma E_y^0 = -j\omega\mu_0 H_x^0$
Ampere's law: $(\nabla \times \vec{H} = j\omega\epsilon_0 \vec{E})_y \Rightarrow -\gamma H_x^0 - \frac{\partial H_z^0}{\partial x} = j\omega\epsilon_0 E_y^0$

\Rightarrow eliminating E_y^0
with $h^2 = \gamma^2 + \omega^2\epsilon_0\mu_0 = \gamma^2 + k^2$
$$H_x^0 = \frac{j\omega\epsilon_0}{h^2} \frac{\partial E_z^0}{\partial y}$$

e) $\gamma^2 = h^2 - k^2 = h^2 - \omega^2\epsilon_0\mu_0 = h^2 - \frac{\omega^2}{c^2} = \left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2 - \frac{\omega^2}{c^2}$

For propagating modes TM_{mn} ($f > f_c$),

$\gamma = j\beta = j\sqrt{\frac{\omega^2}{c^2} - \left(\frac{m\pi}{a}\right)^2 - \left(\frac{n\pi}{b}\right)^2}$

$\therefore \beta^2 = \frac{\omega^2}{c^2} - \left(\frac{m\pi}{a}\right)^2 - \left(\frac{n\pi}{b}\right)^2 = \frac{\omega^2}{c^2} - \frac{\pi^2}{a^2}(m^2 + 3n^2)$: dispersion eqn.

Cutoff at $\gamma = 0$

$\Rightarrow \frac{a^2}{c^2} = \left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2 \Rightarrow \left(\frac{2\pi f_c}{c}\right)^2 = \left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2$

$\Rightarrow (f_c)_{mn} = \frac{c}{2} \sqrt{\left(\frac{m}{a}\right)^2 + \left(\frac{n}{b}\right)^2} = \frac{c}{2a} \sqrt{m^2 + 3n^2}$: cutoff frequency

f) Dominant mode \Rightarrow smallest $(f_c)_{mn} \Rightarrow$ TM₁₁ mode

$(f_c)_{11} = \frac{c}{2a} \sqrt{1^2 + 3 \times 1^2} = \frac{c}{a} = \frac{3 \times 10^8}{a} \text{ (Hz)}$

g) $(\lambda_c)_{11} = \frac{c}{(f_c)_{11}} = \frac{c}{c/a} = a \text{ (m)}$

h) For $f > 1.2(f_c)_{11}$,

$3.6 \times 10^9 > 1.2 \frac{3 \times 10^8}{a} \Rightarrow a > 0.1 \text{ (m)}$