

Analog Electronic Circuits
Department of Electrical and Computer Engineering
Seoul National University

Midterm Exam

October 26, 2020

D.K. Jeong

A sheet of one-sided, A4-size note is allowed.


Roster Number (학번):

Name:


Signature:

Problem	Max Score	Score
1	10	
2	10	
3	10	
4	10	
5	20	
6	20	
7	20	
Total	100	

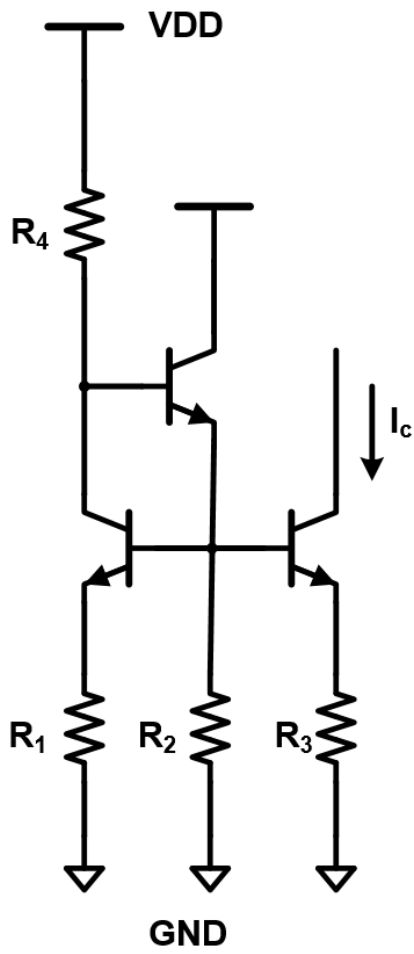[1] Find the values of I_c . Assume that $R_1 = 1\text{k}\Omega$, $R_2 = 10\text{k}\Omega$, $R_3 = 1\text{k}\Omega$, $R_4 = 10\text{k}\Omega$, $V_{BE} = 0.7\text{V}$, $\beta = \infty$, and $V_{DD} = 10\text{V}$.



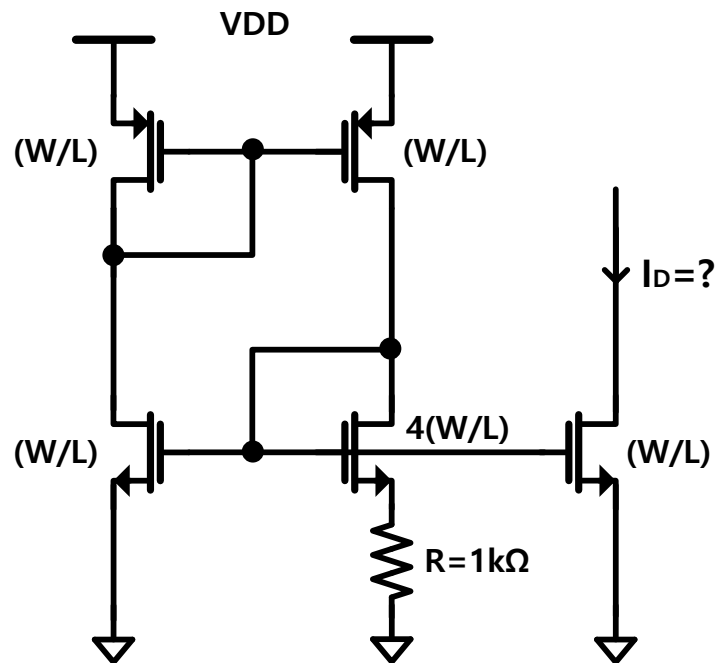[2] Find the value of I_D . Assume that $\left(\frac{W}{L}\right) = 10$, $\mu_n C_{OX} = \mu_p C_{OX} = 200 \mu A/V^2$, $V_{th} = 0.5V$, $\lambda = 0$, and $V_{DD} = 2V$.




[3] For the following circuit, answer the questions.

Assume the circuit is symmetric and all MOS transistors are in the **saturation** region.

(Use $R_1=R_2=5\text{k}\Omega$, $R_c=20\text{k}\Omega$, $R_s=1\text{k}\Omega$, $V_{DD}=5\text{V}$, $I_{SS} = 1\text{mA}$, $V_{thn} = 0.4\text{V}$,

$g_{m1} = g_{m2} = 1\text{ mA/V}$, neglect the channel length modulation. M_1, M_2, M_3 and M_4 are ideally identical.

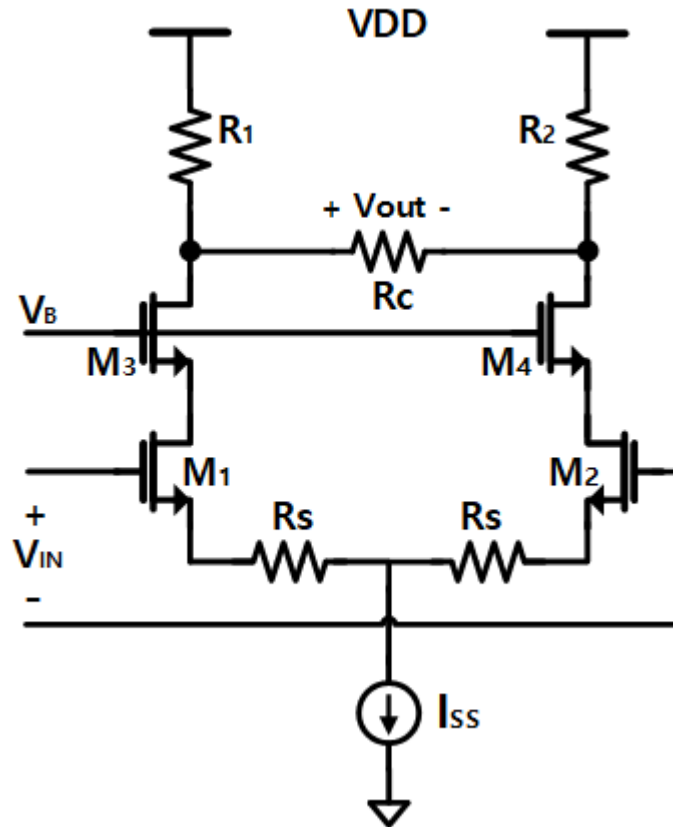
The V_{IN} is the small signal with common mode voltage ($V_{IN,CM}=2\text{V}$.)




A. Find the V_B with the widest dynamic range of output.

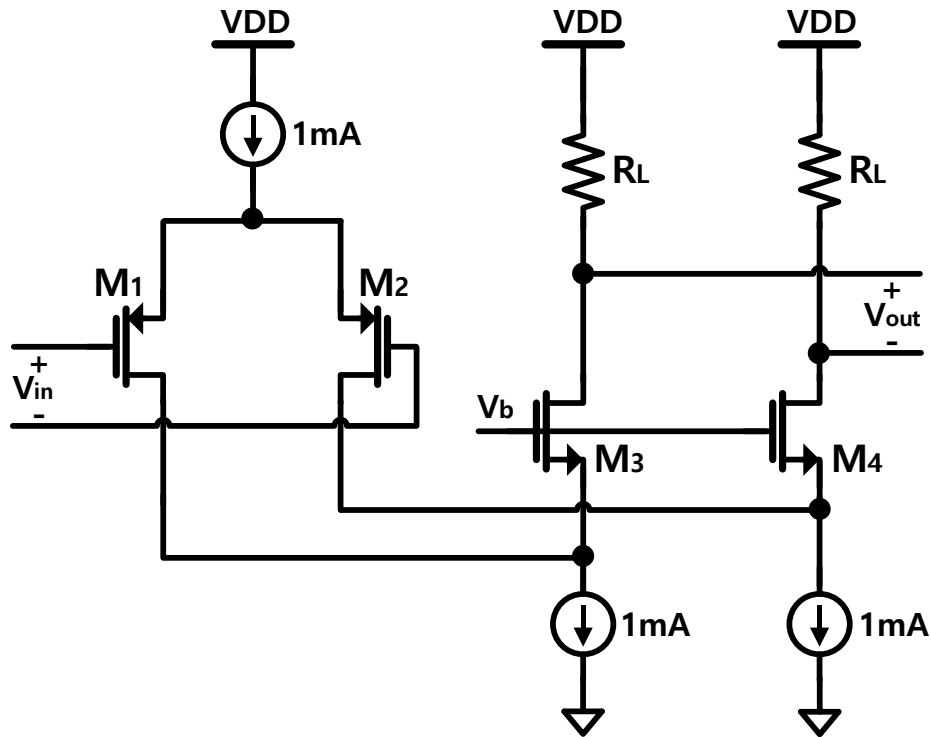B. Derive the expression of small-signal differential voltage gain from V_{in} to V_{out} . Consider the channel length modulation. There is no need to find a value.

[4] Find the small signal gain $A_v (= \frac{V_{out}}{V_{in}})$. Assume that all transistors have the same $(\frac{W}{L})$ of 20, $\mu_n C_{OX} = 200 \mu A/V^2$, $\mu_p C_{OX} = 100 \mu A/V^2$, $V_{th} = 0.5V$, $\lambda_n = 0.01V^{-1}$, $\lambda_p = 0.02V^{-1}$, $R_L = 2k\Omega$, and $V_{DD} = 5V$. Also assume that all MOS transistors are in the **saturation** region.



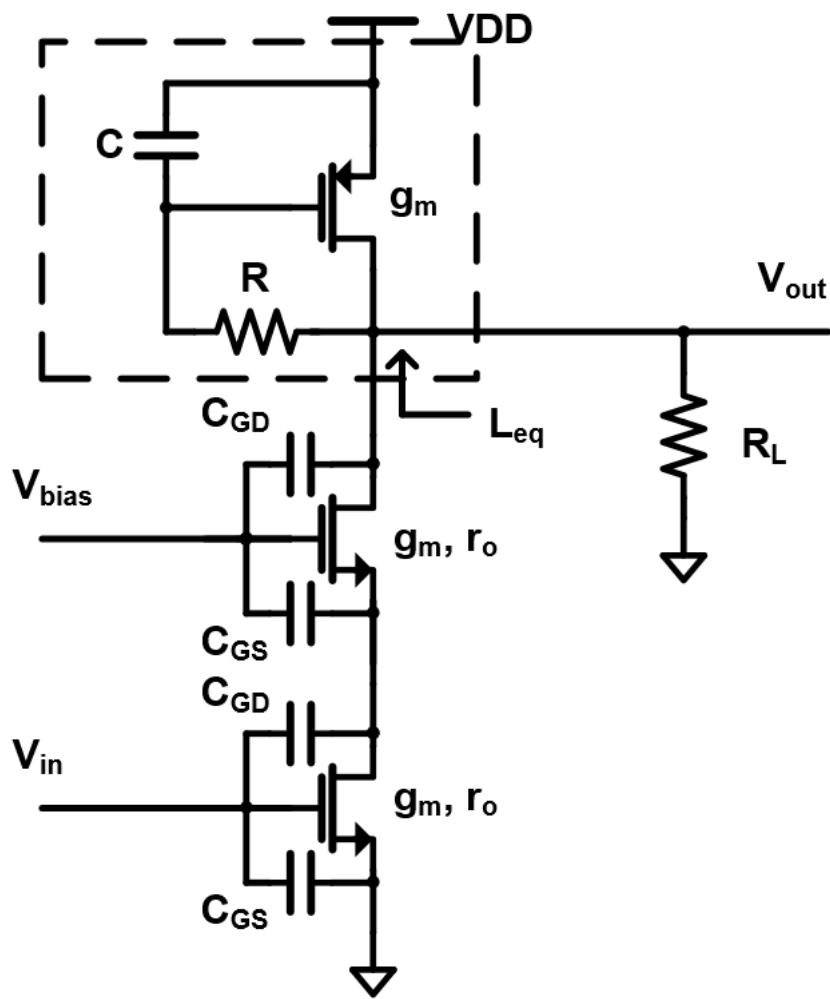[5] For the following active inductor circuit, answer the questions.




A. Find L_{eq} of the active inductor.

B. Find the frequency range where the active inductor becomes purely inductive.

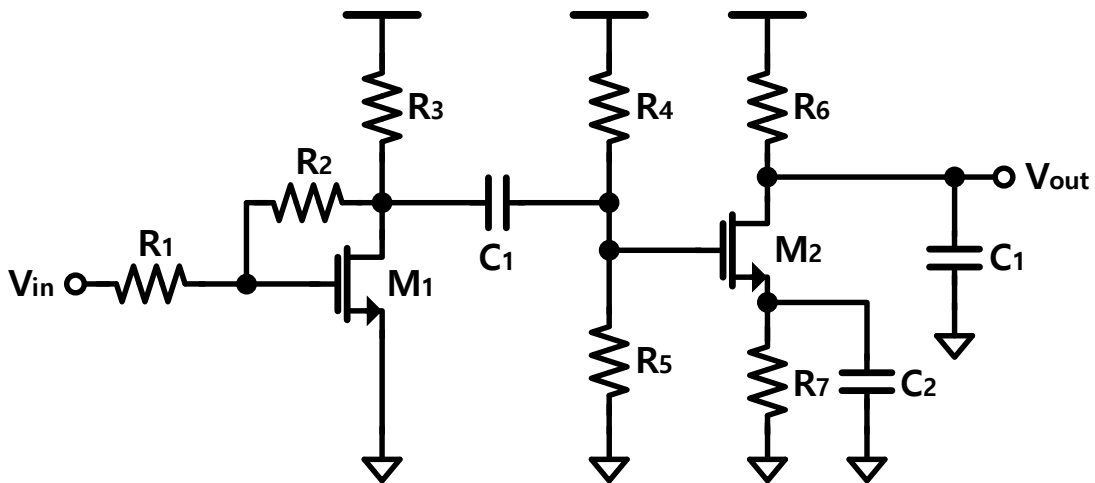C. Find the transfer function of the above circuit.

[6] For the following circuit, find the transfer function $H(s)$ of the circuit and draw a Bode plot of $H(s)$. Assume that $R_1=R_2=R_3=1\text{k}\Omega$, $R_4=R_5=100\text{k}\Omega$, $R_6=2.5\text{k}\Omega$, $R_7=1\text{k}\Omega$, $C_1=2\text{pF}$, $C_2=4\text{pF}$, $C_3=4\text{pF}$, $g_{m1}=2\text{mS}$, $g_{m2}=4\text{mS}$.



[7] Fill in the table. Assume that $g_m = \infty$.

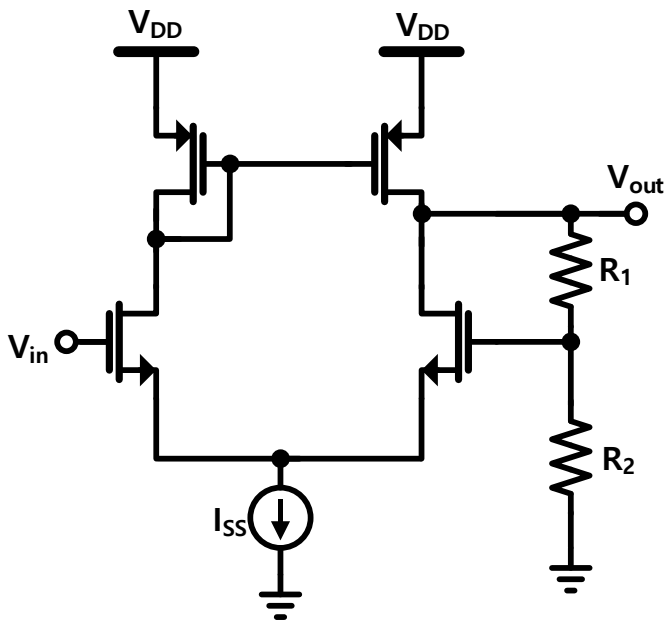


Fig A

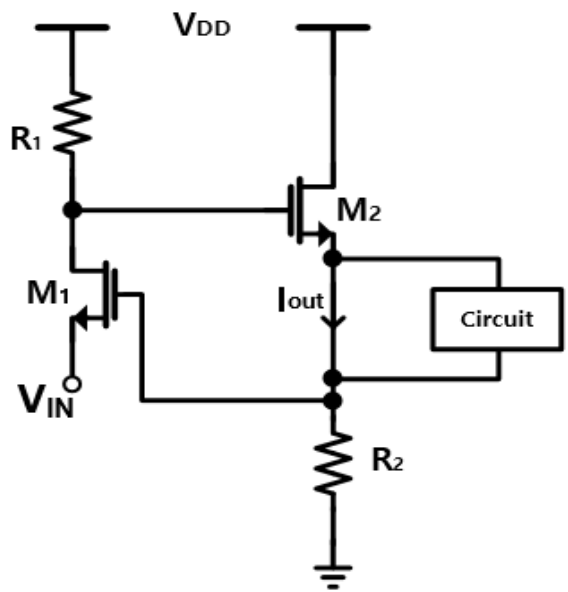


Fig B

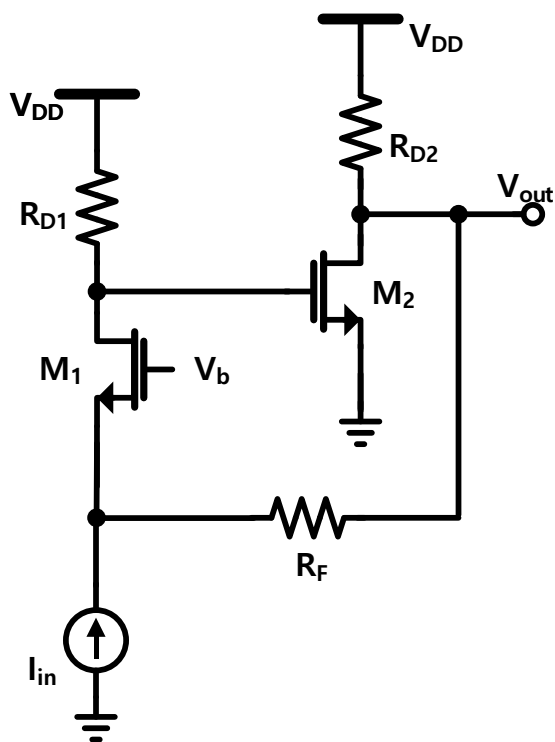


Fig C

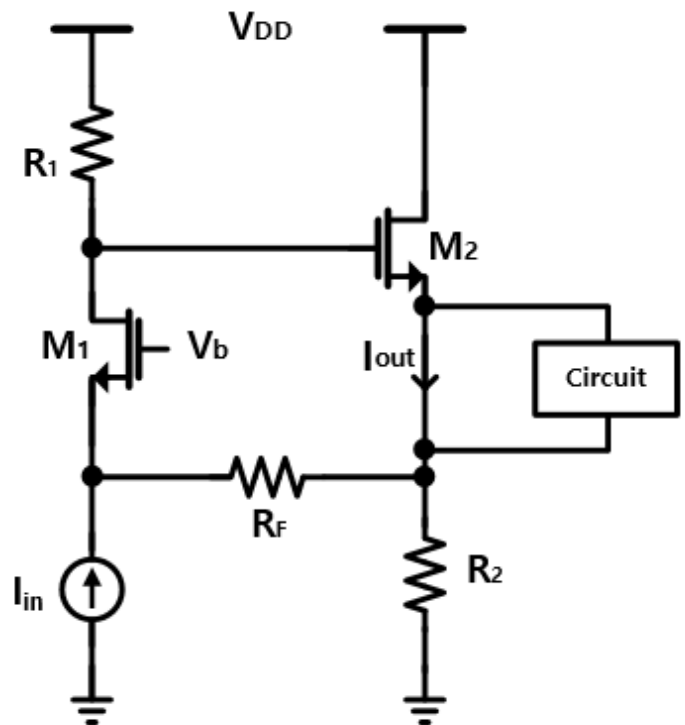


Fig D

	Fig A	Fig B	Fig C	Fig D
Feedback Topology	Voltage to Voltage			
Type of Amplifier				Current Amplifier
Open-loop Gain	∞	∞		
Feedback Factor	$\frac{R_2}{R_1 + R_2}$			
$R_{in-open}$			0	0
$R_{in-closed}$	∞		0	
$R_{out-open}$		R_2		
$R_{out-closed}$	0		0	

{End of Midterm }