
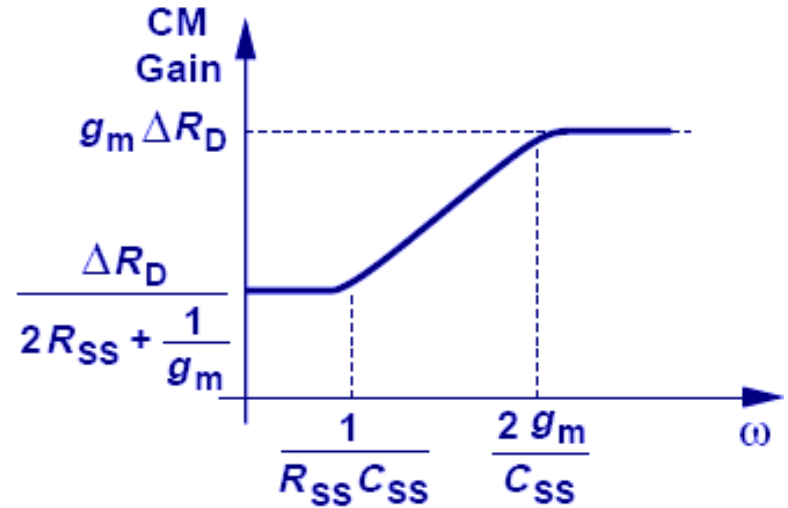


# Common Mode Frequency Response

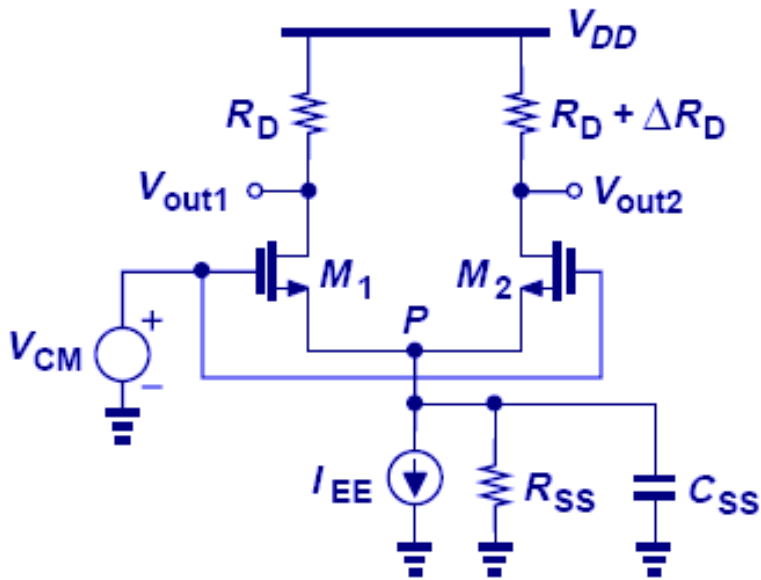

$$\left| \frac{\Delta V_{out}}{\Delta V_{CM}} \right| = \frac{\Delta R_D}{\frac{1}{g_m} + 2 \left( R_{SS} \parallel \frac{1}{C_{SS}s} \right)}$$

$\approx 0$  at high frequency

$\approx g_m \Delta R_D$


$\approx \infty$  at low frequency

$$\left| \frac{\Delta V_{out}}{\Delta V_{CM}} \right| = \frac{\Delta R_D}{\frac{1}{g_m} + 2 \left( R_{SS} \parallel \frac{1}{C_{SS}s} \right)} \approx \frac{\Delta R_D}{\frac{1}{g_m} + 2R_{SS}}$$
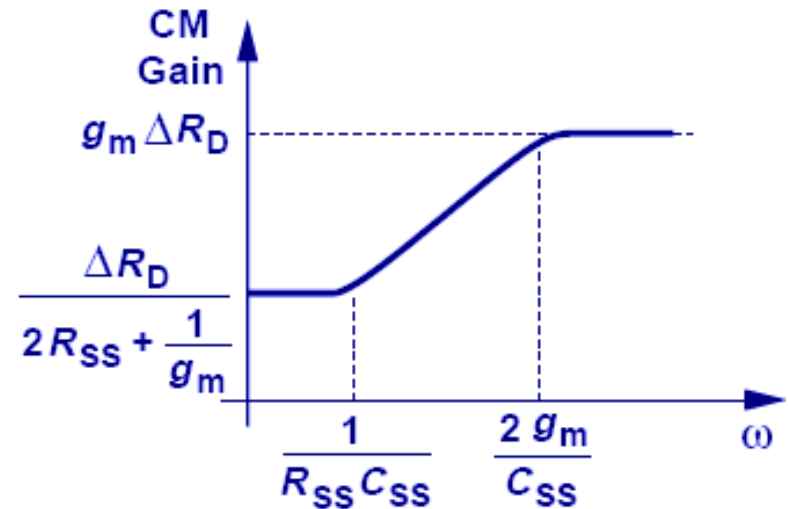
# Common Mode Frequency Response

In page 590 of textbook:

The CM gain indeed rises dramatically at high frequency – by a factor of  $2g_m R_{SS}$  (why?)



$$\left| \frac{A_{CM,high\_f}}{A_{CM,low\_f}} \right| = \frac{\cancel{g_m \Delta R_D}}{\cancel{\Delta R_D} \left( \frac{1}{g_m} + 2R_{SS} \right)} \approx 2g_m R_{SS} \text{ if } 2R_{SS} \gg \frac{1}{g_m}$$

gain at high frequency

gain at low frequency

Usage: If an amount increases by a factor of two, for example, then it becomes two times bigger.