
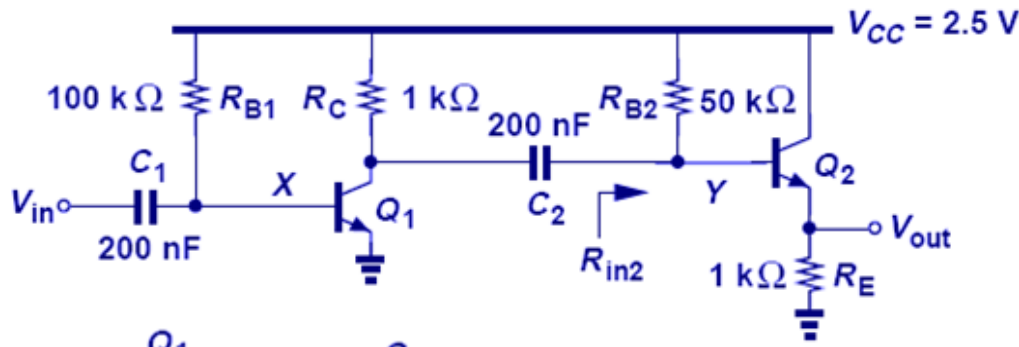


Example: Capacitive Coupling – cont'd

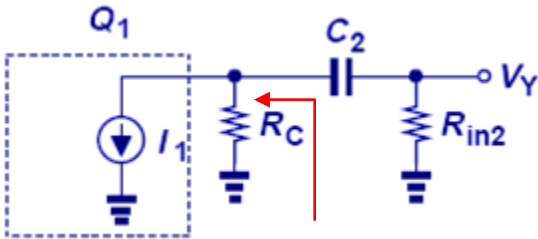


$$\omega_{L1} = \frac{1}{(r_{\pi 1} \parallel R_{B1}) C_1} = 2\pi \times (542 \text{ Hz})$$




$$R_{in2} = R_{B2} \parallel [r_{\pi 2} + (\beta + 1)R_E]$$

$$v_{be1} = \frac{(R_{B1} \parallel r_{\pi 1})}{1/sC_1 + (R_{B1} \parallel r_{\pi 1})} V_{in}$$

$$I_1 = g_{m1} v_{be1}$$

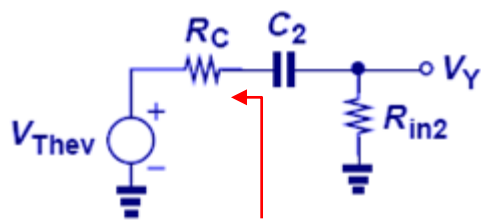




$$V_{Thev} = -I_1 R_C$$

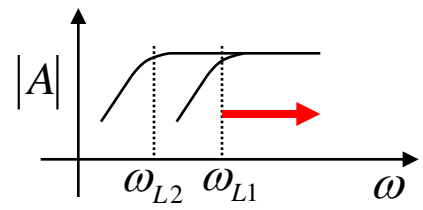

ω_{L1} dominates the low-frequency response

$$\omega_{L2} = \frac{1}{(R_C + R_{in2}) C_2} = \pi \times (22.9 \text{ Hz})$$


Miller Multiplication

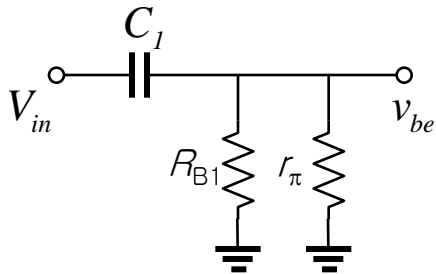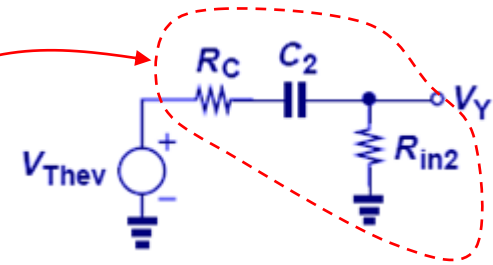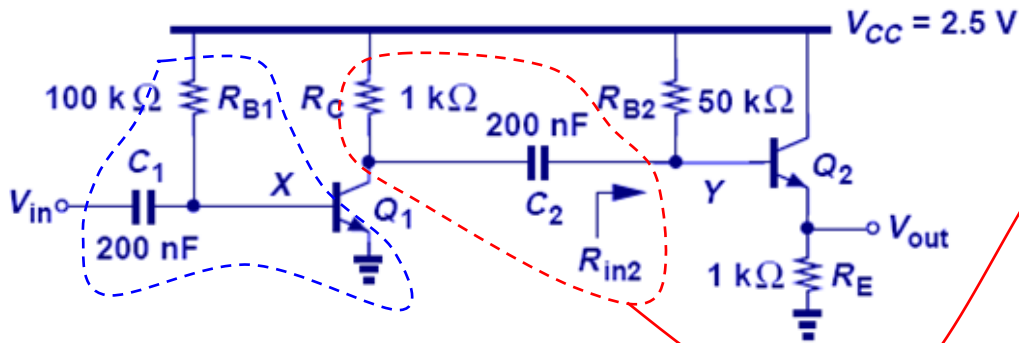

$$\frac{v_{be}}{V_{in}} = \frac{(R_{B1} \parallel r_{\pi})}{(1/sC_1) + (R_{B1} \parallel r_{\pi})}$$

$$= \frac{sC_1 R}{1 + sC_1 R} \quad \because R = R_{B1} \parallel r_{\pi}$$
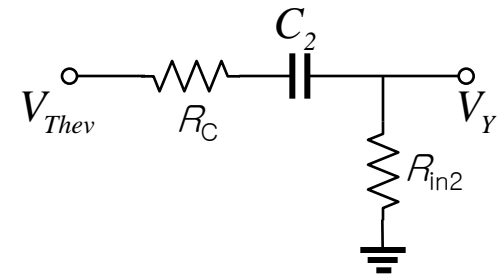
$$\therefore \omega_{L1} = \frac{1}{(r_{\pi 1} \parallel R_{B1}) C_1}$$



$$\frac{V_Y}{V_{Thiv}} = \frac{R_{in2}}{R_C + (1/sC_2) + R_{in2}}$$

$$= \frac{sC_2 R_{in2}}{1 + sC_1 (R_C + R_{in2})}$$

$$\therefore \omega_{L2} = \frac{1}{(R_C + R_{in2}) C_2}$$