

Digital Computer Arithmetic


Part 5 Fast Addition

Soo-Ik Chae
Spring 2009



Conditional Sum Adders

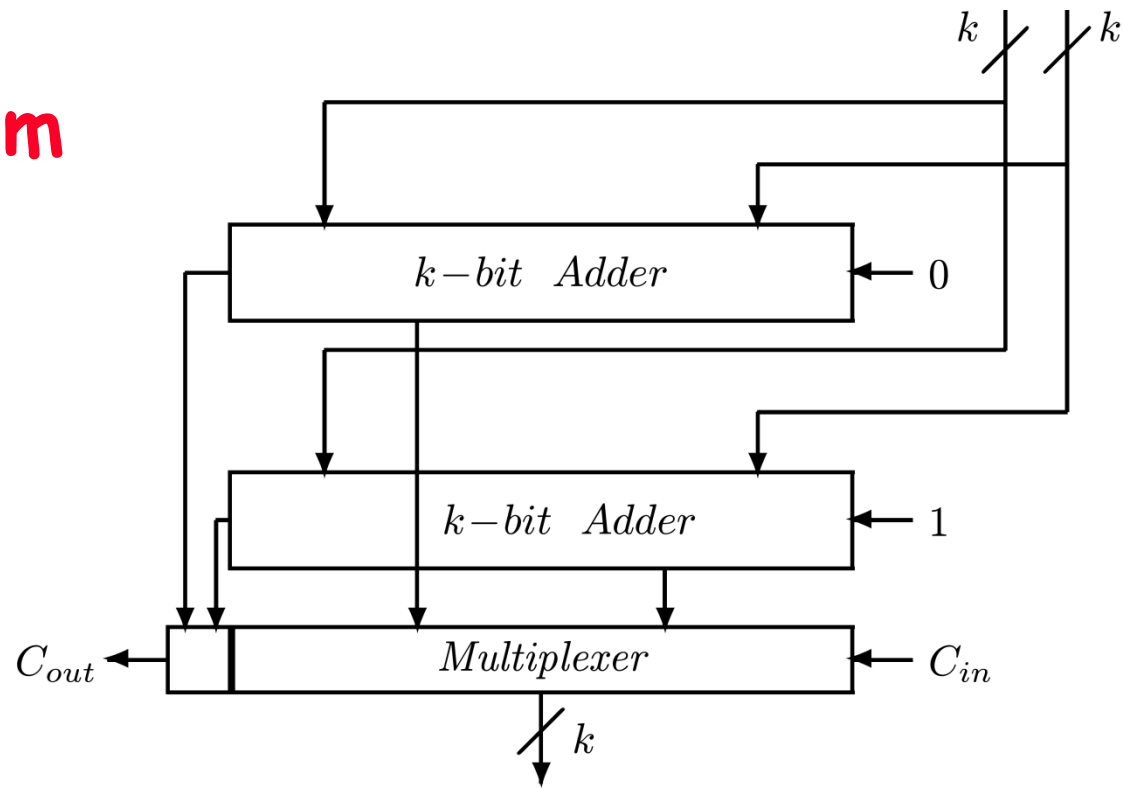- ◆ Logarithmic speed-up of addition
- $O(\log n)$



- ◆ For given k operand bits - generate two outputs - each with k sum bits and an outgoing carry - one for incoming carry 0 and one for 1
- ◆ When incoming carry known - select correct output out of two - no waiting for carry to propagate
- ◆ Should not apply this idea to all n bits at once

Dividing into Groups

- ◆ Divide n bits into smaller groups - apply above to each
- ◆ Serial carry-propagation inside groups done in parallel
- ◆ Groups can be further divided into subgroups
- ◆ Outputs of subgroups combined to generate output of groups
- ◆ Natural division of n - two groups of $n/2$ bits each
- ◆ Each can be divided into two groups of $n/4$, and so on
- ◆ If n power of 2 - last subgroup is of size 1 and $\log_2 n$ steps are needed
- ◆ Division not necessarily into equal-sized subgroups - scheme can be applied even if n not a power of 2

Example - Combining Single Bits into Pairs

◆ s_i^0 / s_i^1 - sum bit at position i under the assumption that incoming carry into currently considered group is $0 / 1$

◆ Similarly - outgoing carries (from group)
 c_{i+1}^0 / c_{i+1}^1

◆ **Step 1** - each bit constitutes a separate group:

i	7	6	
x_i	1	0	
y_i	0	0	
s_i^0	1	0	Assuming incoming carry = 0
c_{i+1}^0	0	0	
s_i^1	0	1	Assuming incoming carry = 1
c_{i+1}^1	1	0	

Example - Step 2

- ◆ **Step 2** - two bit positions combined (using data selectors) into one group of size **2**
- ◆ Carry-out from position **6** becomes internal (to group) carry and appropriate set of outputs for position **7** selected

i	7	6
x_i	1	0
y_i	0	0
s_i^0	1	0
c_{i+1}^0	0	0
s_i^1	0	1
c_{i+1}^1	1	0

$i, i - 1$	7, 6
x_i, x_{i-1}	10
y_i, y_{i-1}	00
s_i^0, s_{i-1}^0	10
c_{i+1}^0	0
s_i^1, s_{i-1}^1	11
c_{i+1}^1	0

Assuming incoming carry = 0

Assuming incoming carry = 1

Example - Addition of Two 8-bit Operands

i		7	6	5	4	3	2	1	0
	x_i	1	0	1	1	0	1	1	0
	y_i	0	0	1	0	1	1	0	1
Step 1	s_i^0	1	0	0	1	1	0	1	1
	c_{i+1}^0	0	0	1	0	0	1	0	0
Step 1	s_i^1	0	1	1	0	0	1	0	
	c_{i+1}^1	1	0	1	1	1	1	1	
Step 2	s_i^0	1	0	0	1	0	0	1	1
	c_{i+1}^0	0		1		1		0	
Step 2	s_i^1	1	1	1	0	0	1		
	c_{i+1}^1	0		1		1			
Step 3	s_i^0	1	1	0	1	0	0	1	1
	c_{i+1}^0	0				1			
Step 3	s_i^1	1	1	1	0				
	c_{i+1}^1	0							
Result		1	1	1	0	0	0	1	1

◆ $\log_2 8 = 3$ steps

◆ Forced carry (=0 here) available at start

◆ Only one set of outputs generated for rightmost group at each step

Carry-Select Adder

- ◆ Variation of conditional sum adder
- ◆ n bits divided into groups - not necessarily equal
- ◆ Each group generates two sets of sum bits and an outgoing carry bit - incoming carry selects one
- ◆ Each group is not further divided into subgroups
- ◆ Comparing Conditional-sum and Carry-look-ahead
 - * Both methods have same speed
 - * Design of conditional sum adder less modular (*why?*)
 - * Carry-look-ahead adder more popular

Optimality of Algorithms and Their Implementations

- ◆ Numerous algorithms for fast addition proposed - technology keeps changing making new algorithms more suitable
- ◆ Performance of algorithm affected by its unique features and number system used to represent operands and results
- ◆ Many studies performed to compare performance of different algorithms - preferably independently of implementation technology
- ◆ Some studies find the limit (bound) on the performance of any algorithm in executing a given arithmetic operation

Optimal Addition Algorithms

- ◆ Execution time reduced by **avoiding (or limiting) carry-propagation**
- ◆ Number systems such as the **residue** number system and the **SD** number system have almost carry-free addition - provide fast addition algorithms
- ◆ These number systems not frequently used - conversions between number systems needed - may be more complex than addition - not always practical

Lower Bound on Addition Speed


- ◆ **Theoretical model** - derives a bound independent of implementation technology
- ◆ **Assumptions:**
 - * Circuit for addition realized using only one type of gate - (f,r) gate - r is radix of number system used and f is fan-in of gate (maximum number of inputs)
 - * All (f,r) gates are capable of computing any r -valued function of f (or less) arguments in exactly the same time
 - * This fixed time period is the unit delay - computation time of adder circuit measured in these units
- ◆ (f,r) gate can compute any function of f arguments - all we need to find out is how many such gates are required and how many circuit levels are needed in order to properly connect the gates

Lower Bound - Cont.

- ◆ A circuit for adding two **radix- r** operands with n digits each - $2n$ inputs and $n+1$ outputs
- ◆ Consider output requiring all $2n$ inputs - can be reduced to a smaller number of arguments by using $\lceil 2n/f \rceil$ such **(f,r)** gates operating in parallel
- ◆ Number of intermediate arguments - $\lceil 2n/f \rceil$ - can be further reduced by a second level of **(f,r)** gates
- ◆ Number of levels in tree - at least $\lceil \log_f 2n \rceil$
- ◆ **Lower bound** - assumes that no argument is needed as input to more than one **(f,r)** gate
- ◆ Lower bound on addition time - measured in units of **(f,r)** gate delay -

$$T_{add} \geq \lceil \log_f 2n \rceil$$

Circuit Implemented with (f, r) Gates

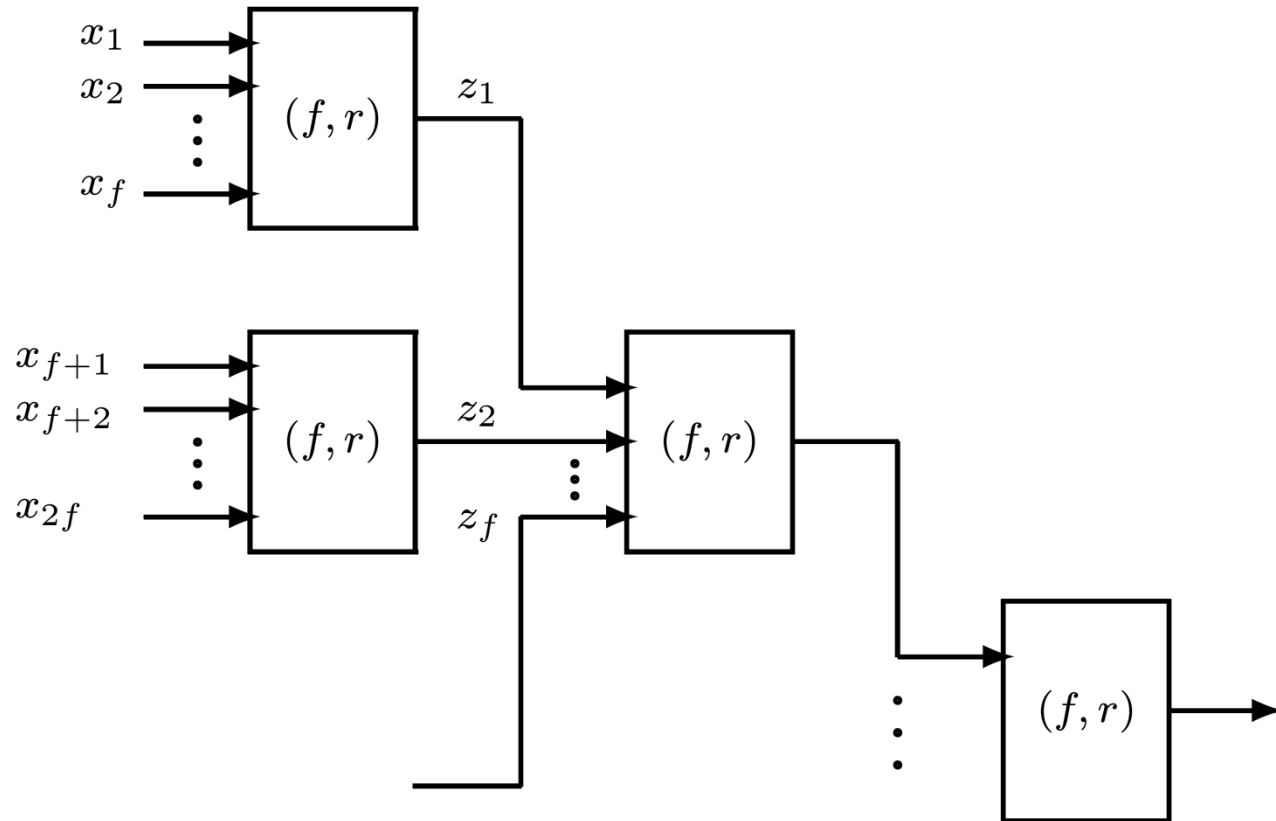

Limitations of Model

- ◆ Only fan-in limitation considered - fan-out ignored
- ◆ Fan-out of gate - ability of its output to drive a number of inputs to similar gates in the next level
- ◆ In practice fan-out is constrained
- ◆ More important - model assumes that any r -valued function of f arguments can be calculated by a single (f,r) gate in one unit delay - not true in practice - $O(f)$
- ◆ Many functions require either a more complex gate (longer delay) or are implemented using several simple gates organized in two or more levels

Improved Bound

- ◆ Previous bound assumes at least one output digit that depends on all $2n$ input digits
- ◆ If not - a better (lower) value for the bound exists - smaller trees (with fewer inputs) can be used
- ◆ This occurs if carry cannot propagate from least-significant to most-significant position
- ◆ **Example** - only $x_i, y_i, x_{i-1}, y_{i-1}$ needed to determine sum digit s_i -
$$T_{add} \geq \lceil \log_f 4 \rceil$$
- ◆ In the binary system - carry can propagate through all n positions -
$$T_{add} \geq \lceil \log_f 2n \rceil$$
- ◆ In the two addition algorithms - carry-look-ahead and conditional sum - execution time proportional to $\log n$ - previous bound approached

Implementation Cost

- ◆ Implementation cost must be considered in addition to execution time
- ◆ Implementation cost measure depends on technology
- ◆ **Example - discrete gates**
 - * Number of gates measures implementation cost
 - * Number of gates along the critical (longest) path (number of circuit levels) determines execution time
- ◆ **Example - full custom VLSI technology**
 - * Number of gates - limited effect on implementation cost
 - * **Regularity** of design and length of interconnections more important - affect both **silicon area** and **design time**
- ◆ **Trade-off between implementation cost and addition speed exists**

Performance - Cost Trade-off

- ◆ If performance more important - carry-look-ahead adder preferable
- ◆ Implementation cost can be reduced - determined by regularity of design and size of required area
- ◆ Taking advantage of the available degree of freedom in design - the blocking factor - bounded by fan-in constraint
- ◆ Additional constraints exist - e.g., number of pins
- ◆ Highest blocking factor - not necessarily best
- ◆ **Example** - blocking factor of **2** results in a very regular layout of binary trees with up to **$\log_2 n$** levels - total area approximately **$n \cdot \log_2 n$**

Manchester Adder

- ◆ If lower cost implementation required, ripple-carry method with speed-up techniques is best


- ◆ Manchester adder uses switches that can be realized using pass transistors

* $P_i = x_i \oplus y_i$ carry-propagate signal


* $G_i = x_i y_i$ carry-generate signal

* $K_i = x_i y_i$ carry-kill signal

 - ◆ Only one of the switches is closed at any time



Manchester Adder

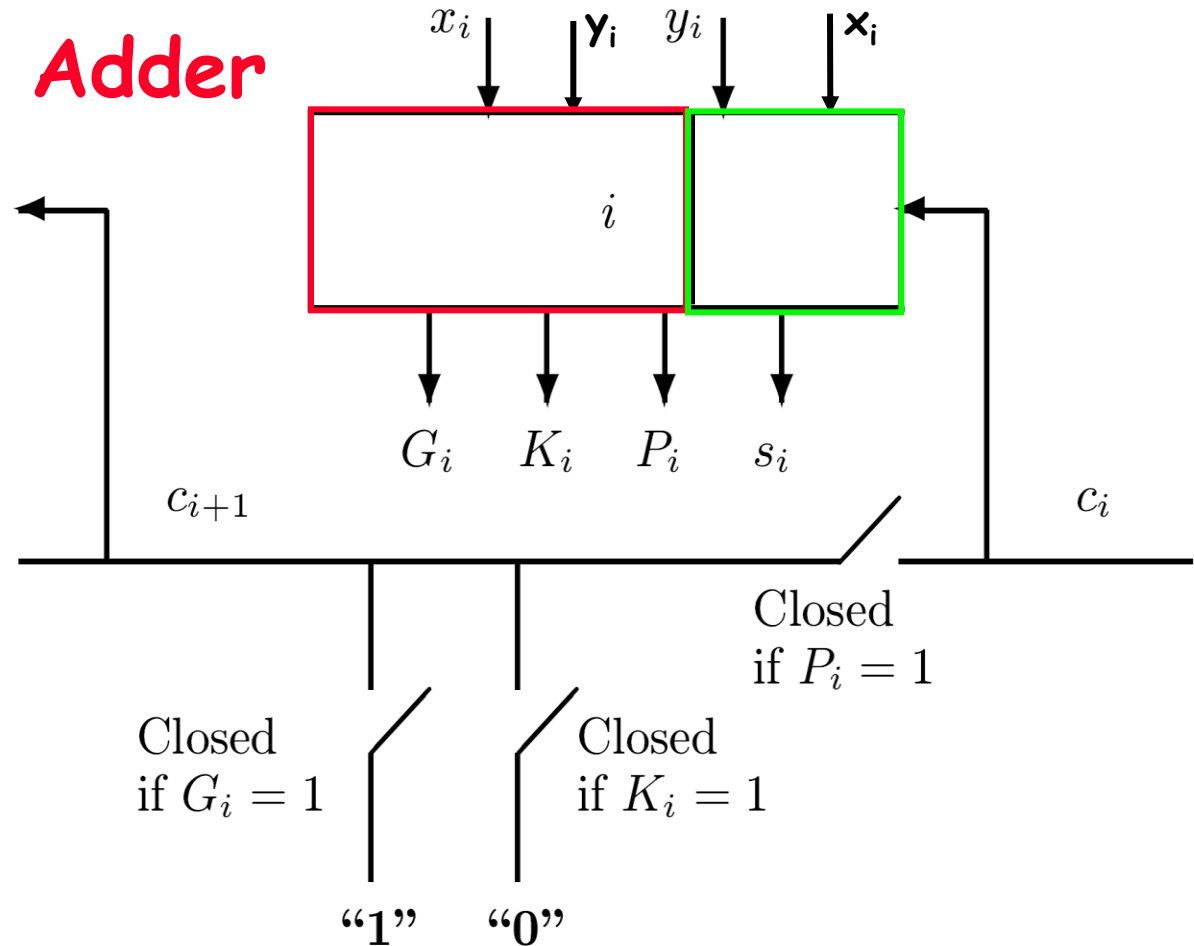

- ◆ $P_i = x_i \oplus y_i$ used instead of $P_i = x_i + y_i$
- ◆ If $G_i = 1$ - an outgoing carry is generated always
- ◆ If $K_i = 1$ - incoming carry not propagated
- ◆ If $P_i = 1$ - incoming carry propagated


Manchester Adder

- ◆ Switches in units 0 through $n-1$ set simultaneously - propagating carry experiences only a single switch delay per stage
- ◆ Number of carry-propagate switches that can be cascaded is limited to k , which depends on technology
 - delay per group - $O(k^2)$
- ◆ n units partitioned into groups with separating devices (**buffers**) between them
- ◆ **In theory** - execution time is still linearly proportional to $O(n)$ although it is faster
- ◆ **In practice** - ratio between execution time and that of another adder (e.g., carry-look-ahead) depends on particular technology
- ◆ Implementation cost - measured in area and/or design regularity - **lower than carry-look-ahead adder**

Carry-Look-Ahead Addition Revisited

- ◆ Generalizing equations for fast adders - carry-look-ahead, carry-select and carry-skip

- ◆ Notation:

 

- * $P_{i:j}$ - group-propagated carry

- * $G_{i:j}$ - group-generated carry

for group of bit positions $i, i-1, \dots, j$ ($i \geq j$)

- ◆ $P_{i:j}=1$ when incoming carry into least significant position j , C_j , is allowed to propagate through all $i-j+1$ positions

- ◆ $G_{i:j}=1$ when carry is generated in at least one of positions j to i and propagates to $i+1$, ($C_{i+1} = 1$)

- * Generalization of previous equations

- * Special case - single bit-position functions P_i and G_i

Group-Carry Functions

◆ Boolean equations


$$P_{i:j} = \begin{cases} P_i & \text{if } i = j \\ P_i \cdot P_{i-1:j} & \text{if } i > j; \end{cases}$$
$$G_{i:j} = \begin{cases} G_i & \text{if } i = j \\ G_i + P_i \cdot G_{i-1:j} & \text{if } i > j. \end{cases}$$

◆ $P_{i:i} \equiv P_i$; $G_{i:i} \equiv G_i$

◆ Recursive equations can be generalized ($i \geq m \geq j+1$)

$$P_{i:j} = P_{i:m} \cdot P_{m-1:j},$$
$$G_{i:j} = G_{i:m} + P_{i:m} \cdot G_{m-1:j}$$

◆ Proof - induction on m

 

Fundamental Carry Operator

- ◆ Boolean operator - fundamental carry operator - ○

$$(P, G) \circ (\tilde{P}, \tilde{G}) = (P \cdot \tilde{P}, G + P \cdot \tilde{G})$$

- ◆ Using the operator ○

- ◆ $(P_{i:j}, G_{i:j}) = (P_{i:m}, G_{i:m}) \circ (P_{m-1:j}, G_{m-1:j})$ ($i \geq m \geq j+1$)

- ◆ Operation is **associative**


$$\begin{aligned} & ((P_{i:m}, G_{i:m}) \circ (P_{m-1:v}, G_{m-1:v})) \circ (P_{v-1:j}, G_{v-1:j}) \\ &= (P_{i:m}, G_{i:m}) \circ ((P_{m-1:v}, G_{m-1:v}) \circ (P_{v-1:j}, G_{v-1:j})) \end{aligned}$$

- ◆ Operation is **idempotent**

$$(P, G) \circ (P, G) = (P \cdot P, G + P \cdot G) = (P, G)$$


- ◆ Therefore
 
$$(P_{i:j}, G_{i:j}) = (P_{i:m}, G_{i:m}) \circ (P_{v:j}, G_{v:j}) \quad \begin{array}{l} i \geq m ; v \geq j ; \\ v \geq m-1 \end{array}$$



Combining two subgroups

- ◆ Group carries $P_{i:j}$ and $G_{i:j}$ calculated from two subgroup carries - subgroups are of arbitrary size and may even overlap
- ◆ Group and subgroup carries used to calculate individual bit carries $C_{i+1}, C_i, \dots, C_{j+1}$, and sum outputs S_i, S_{i-1}, \dots, S_j
- ◆ For the m th bit position, $i \geq m \geq j$
- ◆ $(P_{i:j}, G_{i:j}) = (P_{i:m}, G_{i:m}) \circ (P_{v:j}, G_{v:j})$ $i \geq m ; v \geq j ;$
 $v \geq m-1$

 

Individual Bit Carry & Sum

◆ Must take into account “external” carry c_j

◆ For the m th bit position, $i \geq m \geq j$

$$c_m = G_{m-1:j} + P_{m-1:j} \cdot c_j$$

◆ rewritten as

$$(P_{m-1:j}, G_{m-1:j}) \circ (1, c_j)$$

◆ If $P_m = x_m \oplus y_m$ then $s_m = c_m \oplus P_m$

◆ If $P_m = x_m + y_m$ then $s_m = c_m \oplus (x_m \oplus y_m)$

Various Adder Implementations

- ◆ Equations can be used to derive various implementations of adders - ripple-carry, carry-look-ahead, carry-select, carry-skip, etc.
- ◆ **5-bit ripple-carry adder**: All subgroups consist of a single bit position ; computation starts at position **0**, proceeds to position **1** and so on

$$(P_4, G_4) \circ \{(P_3, G_3) \circ ((P_2, G_2) \circ [(P_1, G_1) \circ \{(P_0, G_0) \circ (1, c_0)\}])\}$$

- ◆ **16-bit carry-look-ahead adder**: **4** groups of size **4**; ripple-carry among groups

$$(P_{15:12}, G_{15:12}) \circ \{(P_{11:8}, G_{11:8}) \circ [(P_{7:4}, G_{7:4}) \circ \{(P_{3:0}, G_{3:0}) \circ (1, c_0)\}]\}$$


Brent-Kung Adder

- ◆ Variant of carry-look-ahead adder - blocking factor of **2** → very regular layout tree with **$\log_2 n$** levels - total area $\approx n \log_2 n$
- ◆ Consider **C_{16}** - incoming carry at stage **16** in a **17**-bit (or more) adder and suppose **$G_0 = x_0 y_0 + P_0 c_0$**
- ◆ The part that generates **$(P_{7:0}, G_{7:0})$** corresponds to

$$\begin{aligned}(P_{7:0}, G_{7:0}) &= (P_{7:4}, G_{7:4}) \circ (P_{3:0}, G_{3:0}) \\ &= \{(P_{7:6}, G_{7:6}) \circ (P_{5:4}, G_{5:4})\} \circ \{(P_{3:2}, G_{3:2}) \circ (P_{1:0}, G_{1:0})\} \\ &= \{[(P_7, G_7) \circ (P_6, G_6)] \circ [(P_5, G_5) \circ (P_4, G_4)]\} \\ &\quad \circ \{[(P_3, G_3) \circ (P_2, G_2)] \circ [(P_1, G_1) \circ (P_0, G_0)]\}\end{aligned}$$

- ◆ Each line, except **c_0** , represents two signals - either **x_m, y_m** or **$P_{v:m}, G_{v:m}$**

Tree Structure for Calculating C_{16}

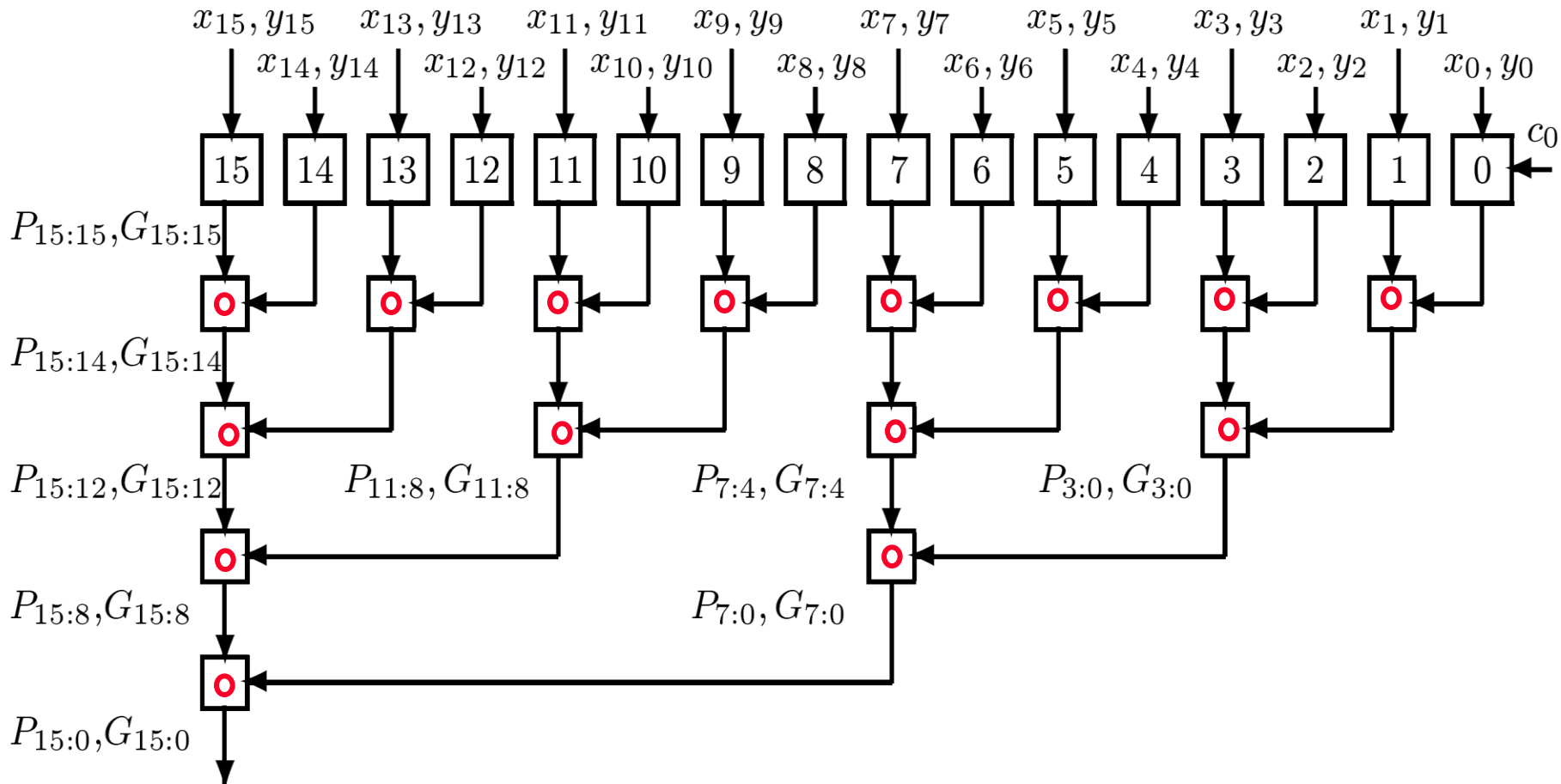


◆ Fundamental carry operator - $\square \circ$

$$(P, G) \circ (\tilde{P}, \tilde{G}) = (P \cdot \tilde{P}, G + P \cdot \tilde{G})$$

Carry Calculation

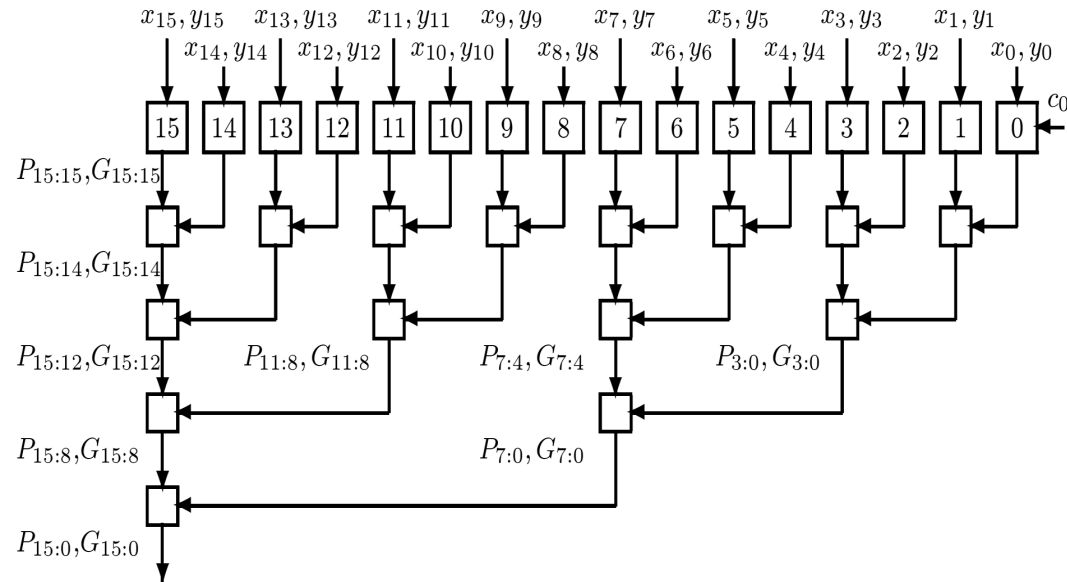- ◆ Circuits in levels 2 to 5 implement fundamental carry op
- ◆ $C_{16} = G_{15:0}$; $P_m = x_m \oplus y_m$
sum: $S_{16} = C_{16} \oplus P_{16}$




- ◆ Tree structure also generates carries C_2 , C_4 and C_8
- ◆ Carry bits for remaining positions can be calculated through extra subtrees that can be added
- ◆ Once all carries are known - corresponding sum bits can be computed
- ◆ Above - blocking factor = 2
 - * Different factors for different levels may lead to more efficient use of space and/or shorter interconnections

Prefix Adders

- ◆ The **BK adder** is a **parallel prefix circuit** - a combinational circuit with $2n$ inputs $(P_1, G_1), (P_2, G_2), \dots, (P_n, G_n)$
- ◆ producing outputs $(P_1, G_1), (P_2, G_2) \circ (P_1, G_1), \dots, (P_n, G_n) \circ (P_{n-1}, G_{n-1}) \circ \dots \circ (P_1, G_1)$, where \circ is an associative binary operation
- ◆ (before the parallel prefix circuit) First stage of adder generates individual P_i and G_i from x_i and y_i
- ◆ Remaining stages constitute the parallel prefix circuit with **fundamental carry operation** serving as the \circ associative binary operation
- ◆ This part of tree can be designed in different ways

 Parallel prefix graph of the 16-bit Brent-Kung Adder




○ : p & g generator ● : fundamental carry operation □ : sum generator

Brent-Kung Parallel Prefix Graph

- ◆ Bullets implement the fundamental carry operation - empty circles generate individual P_i and G_i
- ◆ Number of stages and total delay - can be reduced by modifying structure of parallel prefix graph
- ◆ Minimum # of stages = $\log_2 n$

* 4 for $n=16$


 
* For BK parallel prefix graph = $2\log_2 n - 1$



Prefix Diagram Notation



group generate/propagate

Black cell

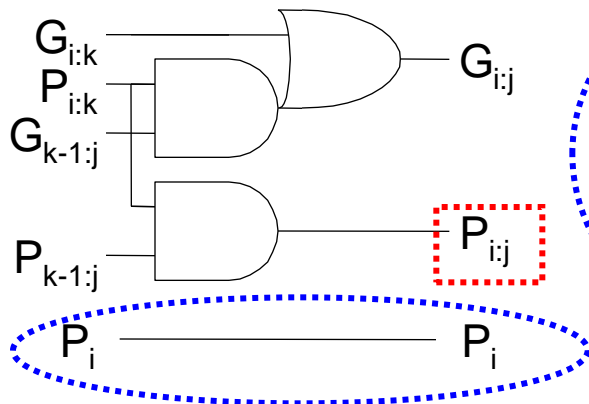
 


group generate

Gray cell

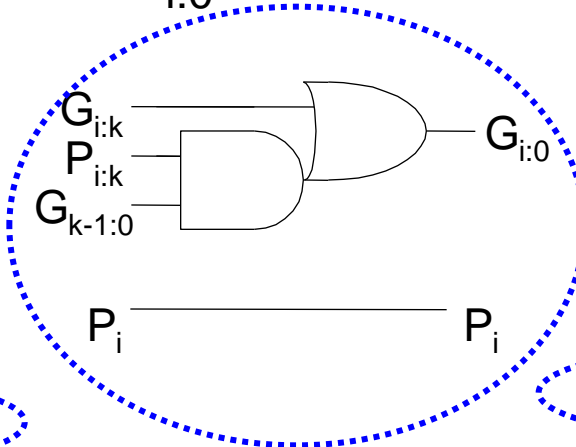 


Buffer

  


Tree Adder Taxonomy

- ◆ **Ideal** N-bit tree adder would have
 - * $L = \log N$ logic levels
 - * Fanout never exceeding 2
 - * No more than one wiring track between levels
- ◆ Describe adder with 3-D taxonomy (l, f, t)
 - * Logic levels: $L + l$
 - * Fanout: $2^f + 1$
 - * Wiring tracks: 2^t
- ◆ **Known tree adders** sit on plane defined by
$$l + f + t = L - 1$$

Tree Adder Taxonomy

 


Tree Adder Taxonomy

 

Brent-Kung Adder


$$(1, f, t) = (3, 0, 0)$$

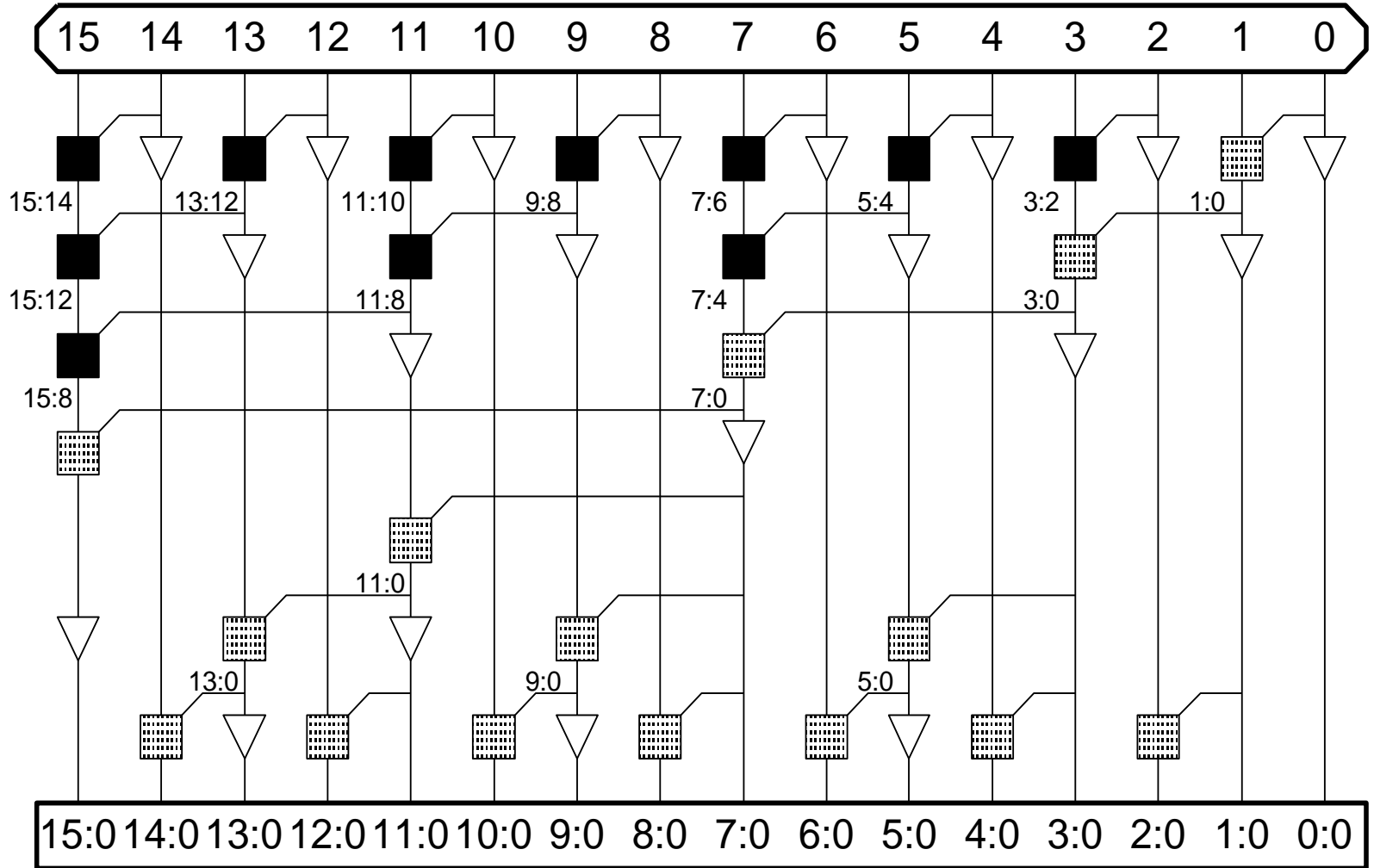

of levels = 7; max fanout = 2; max #of tracks = 1


Sklansky Adder

 - ◆ As a special case of Ladner-Fisher adder
- ◆ Implementing a 4-stage parallel prefix graph
- ◆ Unlike BK, LF adder employs fundamental carry operators with a fan-out ≥ 2 - blocking factor varies from 2 to $n/2$
- ◆ Fan-out $\leq n/2$ requiring buffers : adding to overall delay



Sklansky Adder


$(1,f,t)=(0,3,0)$

 

of levels = 4; fanout (8,4,2,1); max # of tracks = 1


Ladner-Fischer

$$(1, f, t) = (1, 2, 0)$$

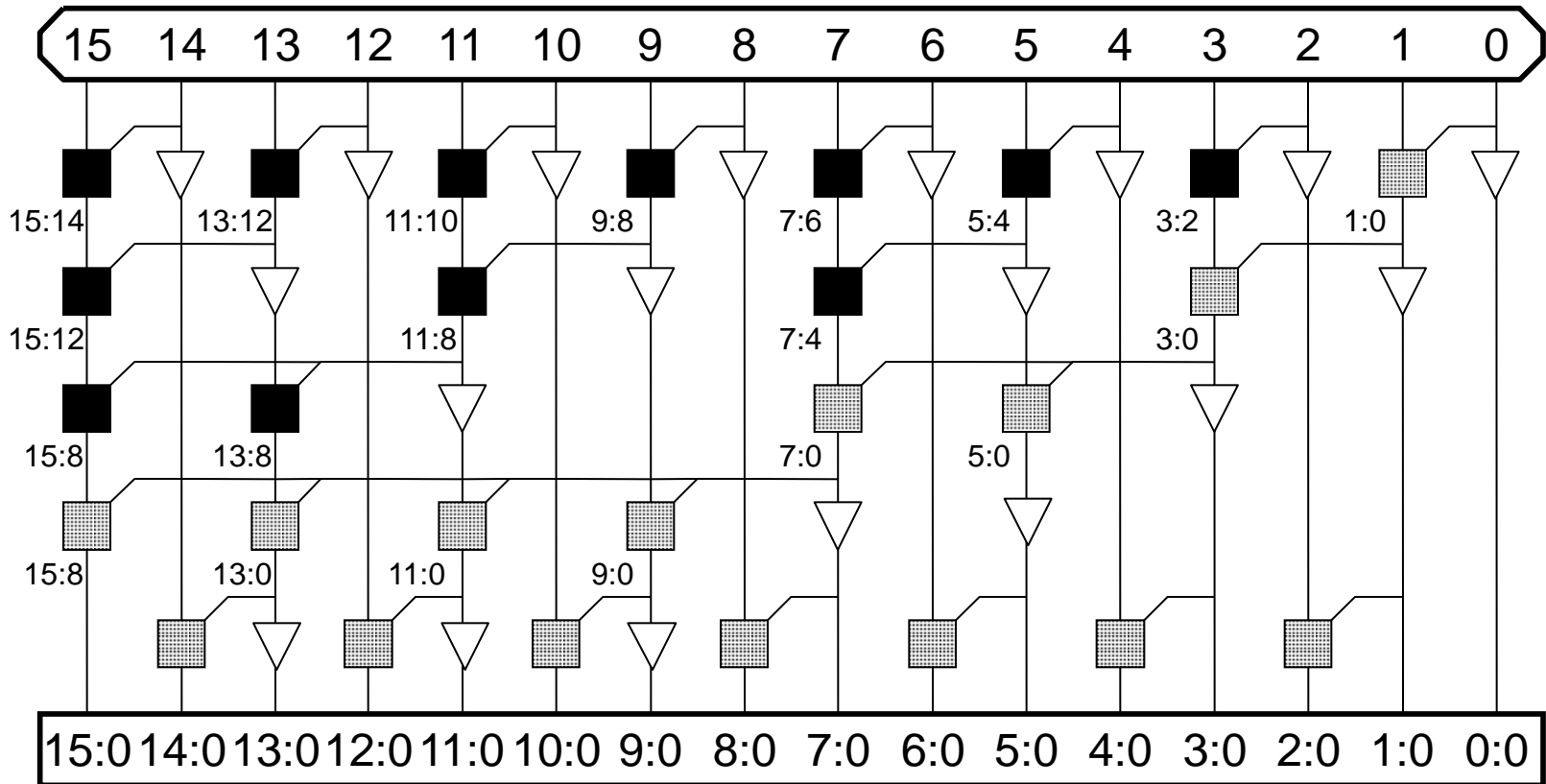


Kogge-Stone Adder

 - ◆ $\log_2 n$ stages - but lower fan-out
- ◆ More lateral wires with long span than BK - requires buffering causing additional delay



Kogge-Stone

$$(1, f, t) = (0, 0, 3)$$

 

fanout (1,1,1,1)


Han-Carlson Adder

◆ Other variants - small delay in exchange for high overall area and/or power

* Compromises between wiring simplicity and overall delay


◆ A hybrid design combining stages from **BK** and **KS**

 * 5 stages - middle 3 resembling **KS** - wires with shorter span than **KS**



Han-Carlson


$$(1, f, t) = (1, 0, 2)$$

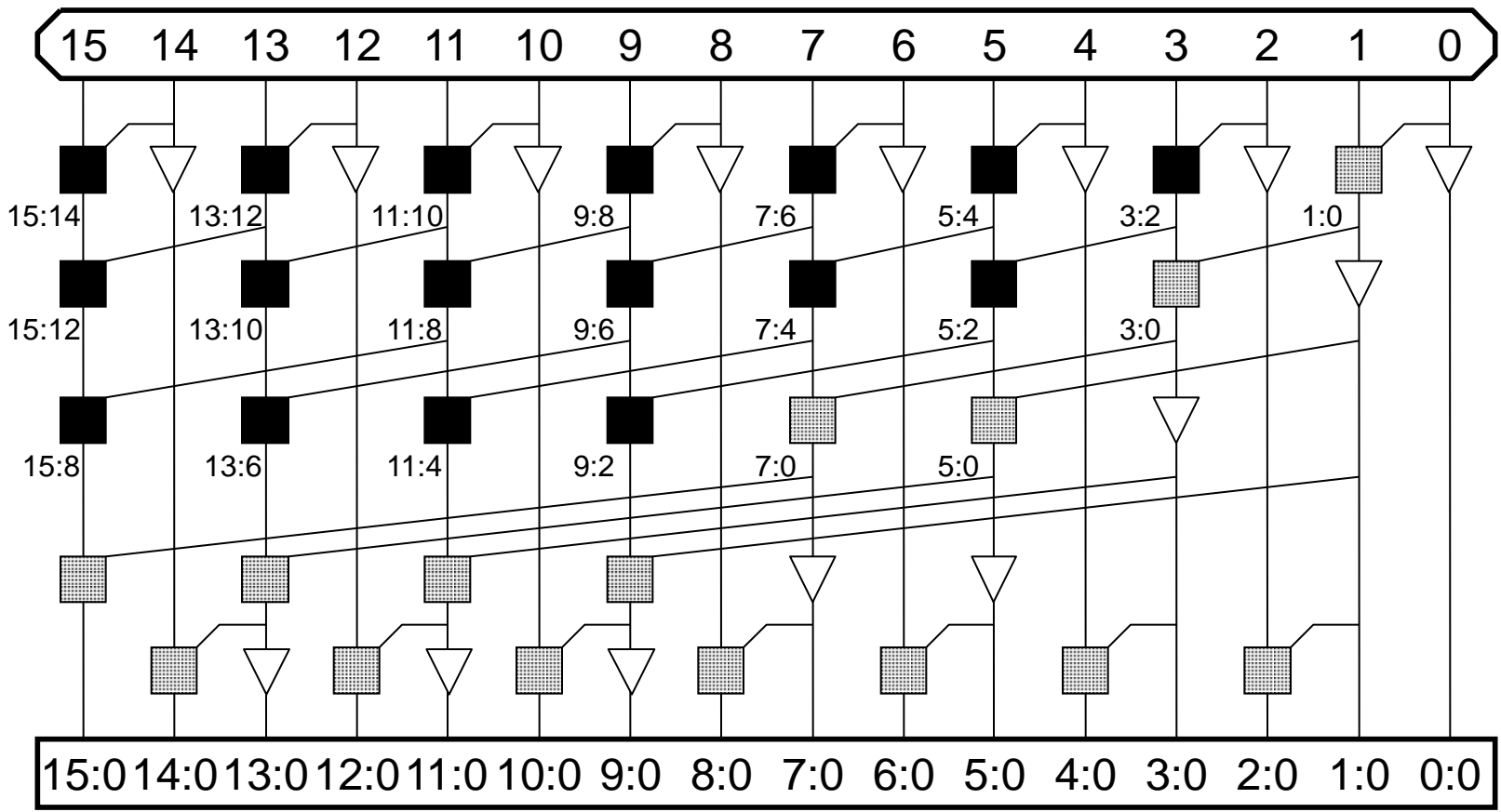

Carry-Select Adders

- ◆ n bits divided into non-overlapping groups of possibly different lengths - similar to conditional-sum adder
- ◆ Each group generates two sets of sum and carry; one assumes incoming carry into group is 0, the other 1
- ◆ the l th group consists of k bit positions starting with j and ending with $i=j+k-1$

Carry-Select Adders

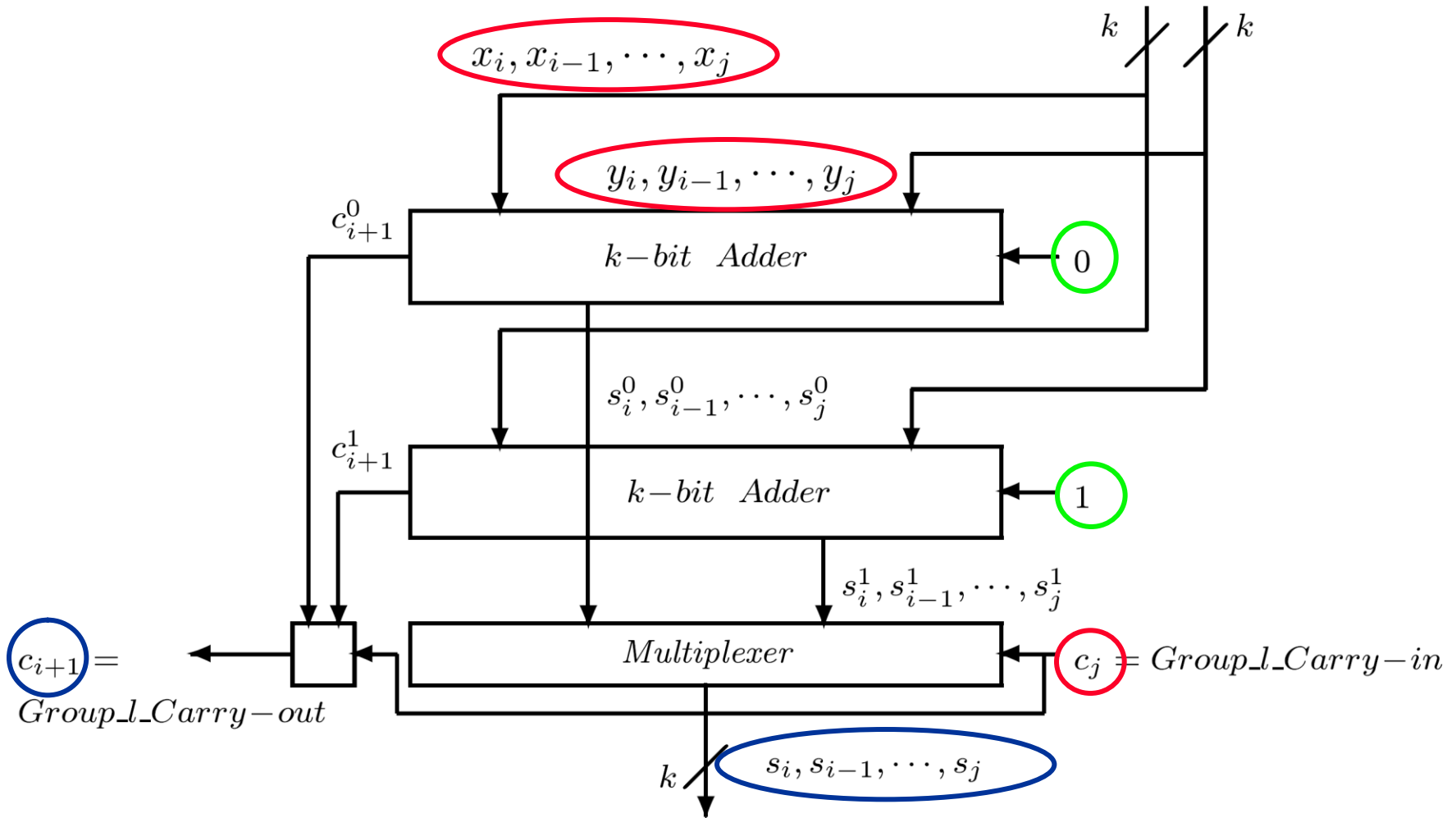

Carry-Select Adder - Equations

- ◆ Outputs of group: sum bits S_i, S_{i-1}, \dots, S_j and group outgoing carry C_{i+1}

$$S_m = S_m^0 \cdot \overline{C_j} + S_m^1 \cdot C_j ; \quad m = j, j + 1, \dots, i$$

$$C_{i+1} = C_{i+1}^0 \cdot \overline{C_j} + C_{i+1}^1 \cdot C_j$$

- ◆ Same notation as for **conditional-sum adder**
- ◆ Two sets of outputs can be calculated in a ripple-carry manner

Detailed Expressions

- ◆ For bit m - calculate carries from $G_{m-1:j}^0$: $G_{m-1:j}^1$

$$(P_{m-1:j}, G_{m-1:j}^0) = (P_{m-1}, G_{m-1}) \circ (P_{m-2}, G_{m-2}) \circ \cdots \circ (P_j, G_j)$$

$$(P_{m-1:j}, G_{m-1:j}^1) = (P_{m-1:j}, G_{m-1:j}^0) \circ (1, 1) = (P_{m-1:j}, G_{m-1:j}^0 + P_{m-1:j})$$

- ◆ $P_{m-1:j}$ has no superscript - independent of incoming carry
 - ◆ Once individual carries are calculated - corresponding sum bits are
- $$s_m^0 = c_m^0 \oplus P_m \quad \text{and} \quad s_m^1 = c_m^1 \oplus P_m$$
- ◆ Since C_{i+1}^0 implies C_{i+1}^1 , $c_{i+1} = c_{i+1}^0 + c_{i+1}^1 \cdot c_j$
 - ◆ Group sizes can be either different

$$c_{i+1} = c_{i+1}^0 \cdot \overline{c_j} + c_{i+1}^1 \cdot c_j \quad \text{and} \quad C_{i+1} \leq C_i$$


Different Group Sizes

◆ Notations:


* Size of group l - k_l

* L - number of groups

* ΔG - delay of a single gate

 

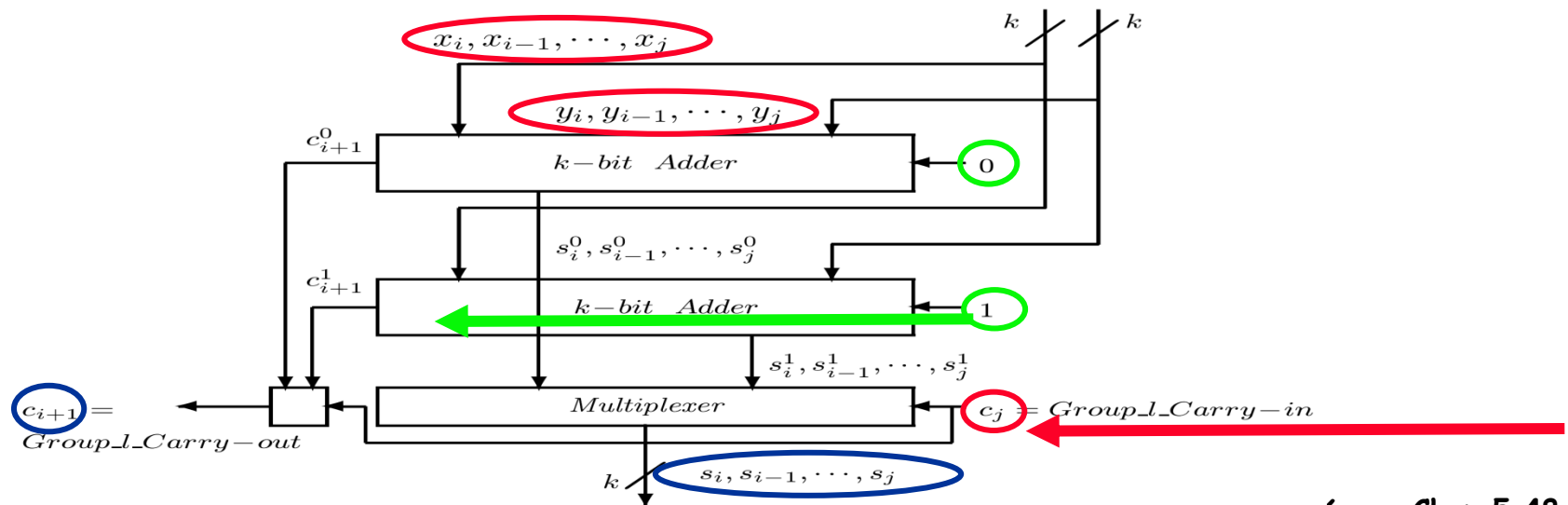- ◆ k_l chosen so that delay of ripple-carry within group is equal to delay of carry-select chain from group 1 to l
- ◆ Actual delays depend on technology and implementation



Different Group Sizes


- ◆ **Example:** Two-level gate implementation of **MUX**
 - * Delay of carry-select chain through preceding $l-1$ groups - $(l-1)2\Delta G$
 - * Delay of ripple-carry in l th group - $k_l 2\Delta G$
- ◆ Equalizing the two - $k_l = l-1$ with $k_l \geq 1 ; l=1,2,\dots,L$

Different Group Sizes - Cont.

- ◆ Resulting group sizes - 1, 1, 2, 3, ...
- ◆ Sum of group sizes $\geq n$
- ◆ $1+L(L-1)/2 \geq n \rightarrow L(L-1) \geq 2(n-1)$
- ◆ **Size of largest group** and execution time of carry-select adder are of the order of \sqrt{n}
- ◆ **Example:** $n=32$, 9 groups required - one possible choice for sizes: 1, 1, 2, 3, 4, 5, 6, 7 & 3
- ◆ Total carry propagation time is $18\Delta G$, instead of $62\Delta G$ for ripple-carry adder

Different Group Sizes - Cont.

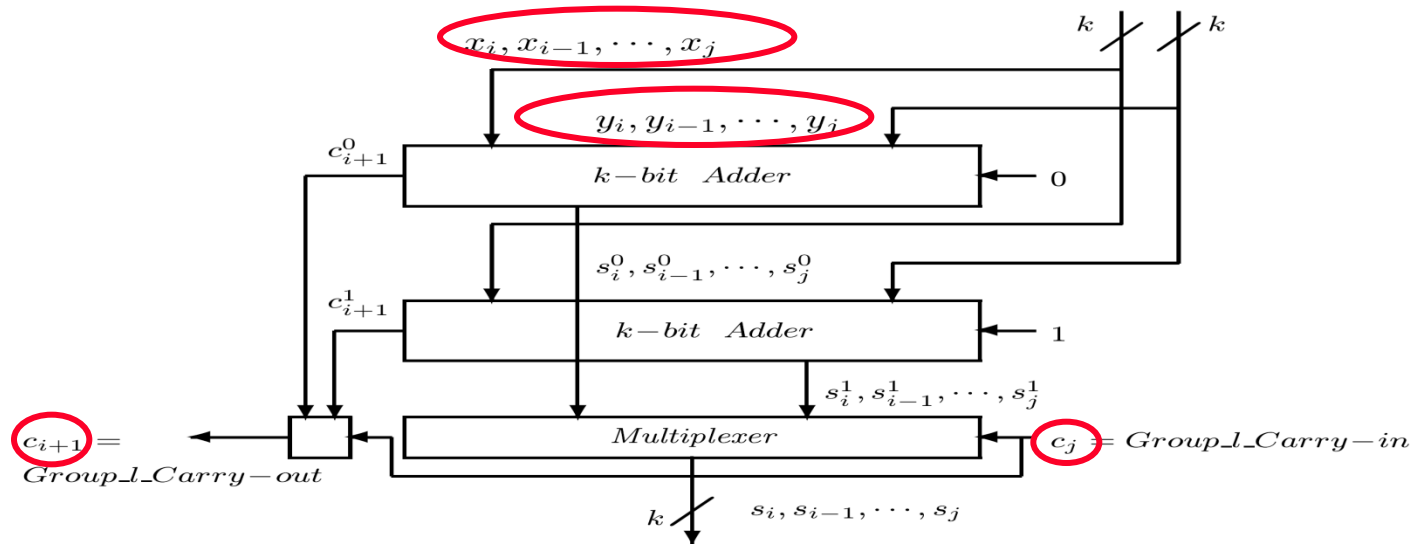- ◆ If sizes of L groups are equal, carry-select chain (i.e., generating Group Carry-Out from Group Carry-In) not necessarily ripple-carry type
- ◆ Single or multiple-level carry-look-ahead can be used




Carry-Skip Adders

- ◆ Reduces time needed to propagate carry by skipping over groups of consecutive adder stages
- ◆ Generalizes idea behind **Manchester Adder**
- ◆ Illustrates dependence of “optimal” algorithm for addition on available technology
 - * Known for many years, only recently became popular
- ◆ In VLSI - speed comparable to carry look-ahead (for commonly used word lengths - not asymptotically)
- ◆ Requires less chip area and consumes less power
- ◆ Based on following observation:
- ◆ Carry propagation process can skip any adder stage for which $x_m \neq y_m$ (or, $P_m = x_m \oplus y_m = 1$)
- ◆ Several consecutive stages can be skipped if all satisfy $x_m \neq y_m$


Carry-Skip Adder - Structure

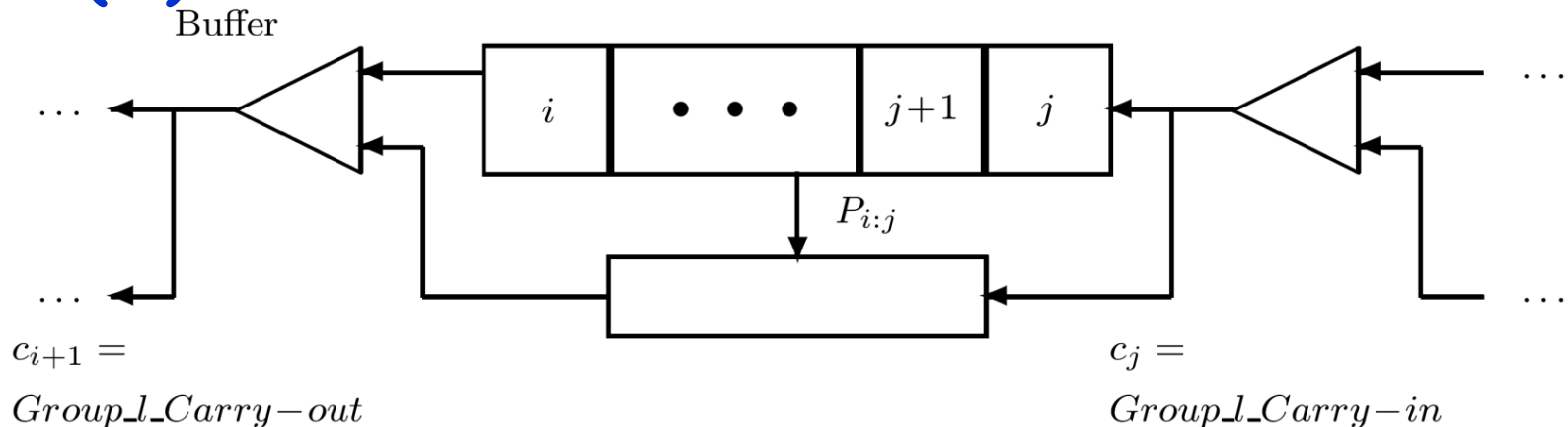- ◆ n stages divided into groups of consecutive stages with simple ripple-carry used in each group
- ◆ Group generates a group-carry-propagate signal that equals 1 if for all internal stages $P_m=1$
- ◆ Signal allows an incoming carry into group to “skip” all stages within group and generate a group-carry-out
- ◆ Group l consists of k bit positions $j, j+1, \dots, j+k-1 (=i)$




Carry Skip Adder - Structure

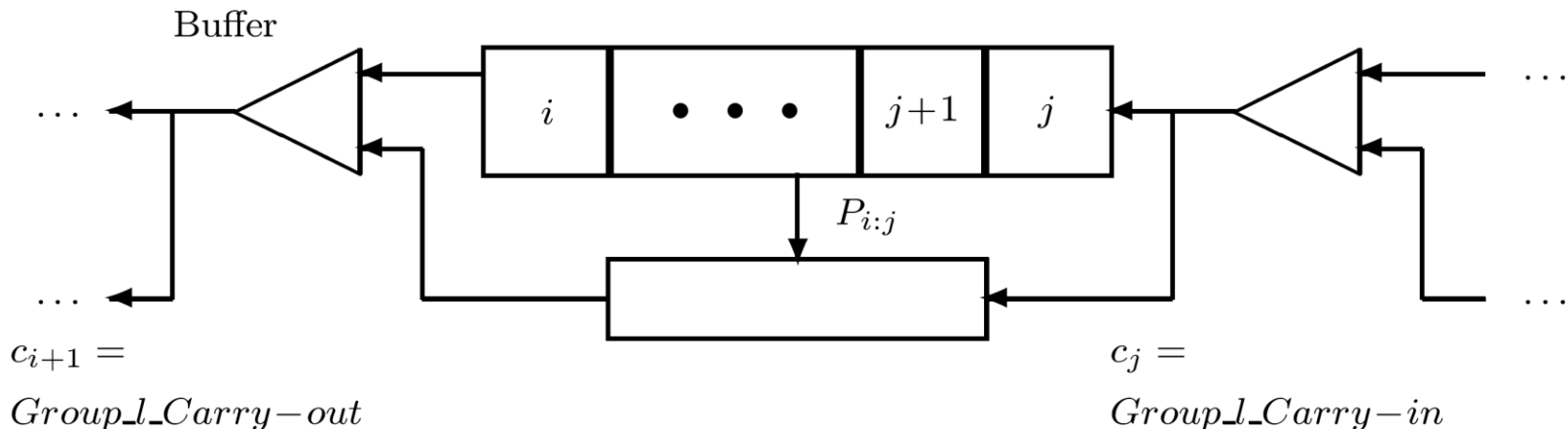- ◆ $Group_I_Carry-out = G_{i:j} + P_{i:j} Group_I_Carry-in$
- ◆ $G_{i:j} = 1$ when a carry is generated internal to group and allowed to propagate through all remaining bit positions including i
- ◆ $P_{i:j} = 1$ when $k=i-j+1$ bit positions allow incoming carry c_j to propagate to next position $i+1$
- ◆ Buffers realize the **OR** operation



 
Example - 15-bit carry-skip adder

- ◆ Consisting of 3 groups of size 5 each
- ◆ $P_{i:j}$ for all groups can be generated simultaneously allowing a fast skip of groups which satisfy $P_{i:j}=1$



Determining Optimal Group Size k

- ◆ **Assumption:** Groups have equal size k - n/k integer
- ◆ k selected to minimize time for longest carry-propagation chain
- ◆ **Notations:**
 - * t_r - carry-ripple time through a single stage
 - * $t_s(k)$ - time to skip a group of size k (for most implementations - independent of k)
 - * t_b - delay of buffer (implements **OR**) between two groups
 - * T_{carry} - overall carry-propagation time - occurs when a carry is generated in stage 0 and propagates to stage $n-1$
- ◆ Carry will ripple through stages $1, 2, \dots, k-1$ within group 1 , skip groups $2, 3, \dots, (n/k-1)$, then ripple through group n/k

 


Determining Optimal k - Cont.

- ◆ $T_{\text{carry}} = (k-1)t_r + t_b + (n/k-2)(t_s + t_b) + (k-1)t_r$
- ◆ **Example** - two-level gate implementation used for ripple-carry and carry-skip circuits

* $t_r = t_s + t_b = 2\Delta G$

 * $T_{\text{carry}} = (4k + 2n/k - 7) \Delta G$




- ◆ Differentiating T_{carry} with respect to k and equating to 0 -

$$k_{\text{opt}} = \sqrt{n/2}$$

- ◆ Group size and carry propagation time proportional to \sqrt{n} - same as for **carry-select adder**
- ◆ **Example**: $n=32$, 8 groups of size $k_{\text{opt}} = 4$ is best
- ◆ $T_{\text{opt}} = 25\Delta G$ instead of $62\Delta G$ for ripple-carry adder

Further Speedup

- ◆ Size of first and last groups smaller than fixed size $k \Rightarrow$ ripple-carry delay through these is reduced
- ◆ Size of center groups increased - since skip time is usually independent of group size
- ◆ Another approach: add second level to allow skipping two or more groups in one step (more levels possible)
- ◆ Algorithms exist for deriving optimal group sizes for different technologies and implementations (i.e., different values of ratio $(t_s+t_b)/t_r$)

 

Variable-Size Groups

- ◆ Unlike equal-sized group case - cannot restrict to analysis of worst case for carry propagation
- ◆ This may lead to trivial conclusion: first and last groups consisting of a single stage - remaining $n-2$ stages constituting a single center group
- ◆ Carry generated at the beginning of center group may ripple through all other $n-3$ stages - becoming the worst case
- ◆ Must consider all possible carry chains starting at arbitrary bit position a (with $x_a=y_a$) and stopping at b ($x_b=y_b$) where a new carry chain (independent of previous) may start

Optimizing Different Size Groups

- ◆ k_1, k_2, \dots, k_L - sizes of L groups $\sum_{i=1}^L k_i = n$
- ◆ **General case**: Chain starts within group u , ends within group v , skips groups $u+1, u+2, \dots, v-1$
- ◆ **Worst case** - carry generated in first position within u and stops in last position within v
- ◆ Overall carry-propagation time is

$$T_{carry}(u, v) = (k_u - 1) \cdot t_r + t_b + \sum_{l=u+1}^{v-1} (t_s(k_l) + t_b) + (k_v - 1) \cdot t_r$$


- ◆ Number of groups L and sizes k_1, k_2, \dots, k_L selected so that longest carry-propagation chain is minimized -

$$\text{minimize} \left[\max_{1 \leq u \leq v \leq L} T_{carry}(u, v) \right]$$

- ◆ Solution algorithms developed - geometrical interpretations or dynamic programming

Optimization - Example

- ◆ 32-bit adder with single level carry-skip
- ◆ $t_s + t_b = t_r$
- ◆ **Optimal organization:** $L=10$ groups with sizes $k_1, k_2, \dots, k_{10} = 1, 2, 3, 4, 5, 6, 5, 3, 2, 1$
- ◆ Resulting in $T_{\text{carry}} \leq 9 t_r$
- ◆ If $t_r = 2 \Delta G$ - $T_{\text{carry}} \leq 18 \Delta G$ instead of $25 \Delta G$ in equal-size group case
- ◆ **Exercise:** Show that any two bit positions in any two groups u and v ($1 \leq u \leq v \leq 10$) satisfy $T_{\text{carry}}(u, v) \leq 9 t_r$

 

Carry-skip vs. Carry-select Adder

- ◆ Strategies behind two schemes sound different
- ◆ Equations relating group-carry-out with group-carry-in are variations of same basic equation
- ◆ Both have execution time proportional to \sqrt{n}
- ◆ Only details of implementation vary, in particular calculation of sum bits
- ◆ Even this difference is reduced when the multiplexing circuitry is merged into summation logic

Hybrid Adders




- ◆ Combination of two or more addition methods
- ◆ **Common approach**: one method **for carry**, another **for sum**
- ◆ Two hybrid adders combining variation of
 - * a carry-select for sum
 - * modified Manchester carry for carry
- ◆ Both divide operands into equal groups - **8** bits each
 - * **First** - uses carry-select for sum for each group of **8** bits separately
 - * **Second** - uses a variant of conditional-sum
- ◆ Group carry-in signal into 8-bit groups, **which selects one out of two sets of sum bits**, is generated by a carry-look-ahead tree
- ◆ **64-bit adder** - carries are **C₈, C₁₆, C₂₄, C₃₂, C₄₀, C₄₈, C₅₆**


Blocking Factor in Carry Tree

- ◆ Structure of carry-look-ahead tree for generating carries similar to those seen before
- ◆ **Differences** - variations in blocking factor at each level and exact implementation of fundamental carry operator
- ◆ Restricting to a fixed blocking factor - natural choices include **2, 4** or **8**
 - * **2** - largest number of levels in tree, vs.
 - * **8** - complex modules for fundamental carry operator with high delay
- ◆ Factor of **4** - a reasonable compromise
- ◆ A **Manchester** carry chain (**MCC**), which generates both carry generate/propagate bits, with a blocking factor of **4**

$$C_m = G_{m-1:0} + P_{m-1:0} \cdot C_0$$

Manchester Carry Module

   

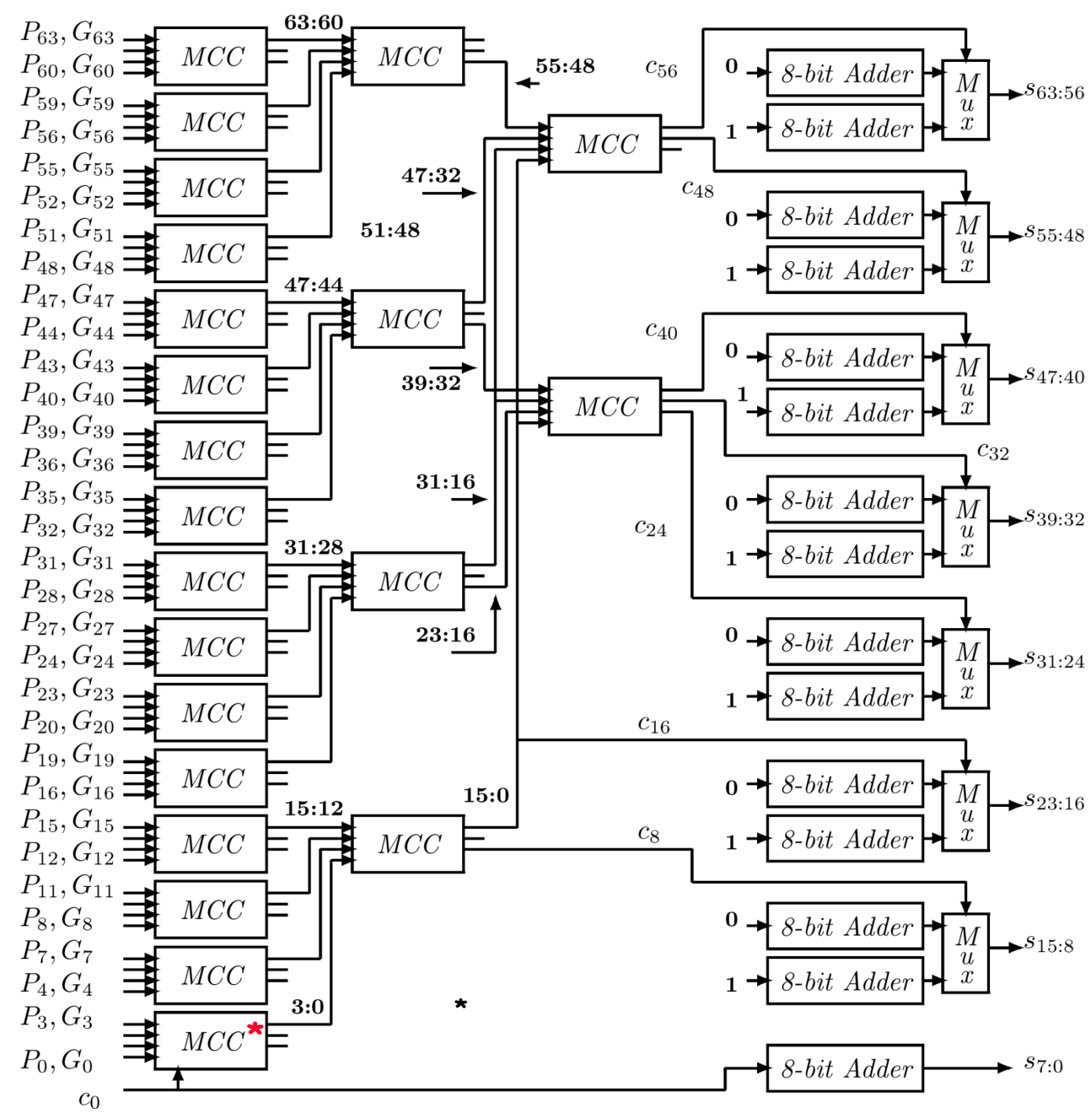

64-bit Hybrid Adder


- 55:48 - 55:0 ⇒ C56**
- 47:32 - 47:0 ⇒ C48**
- 31:16 - 31:0**
- 15:0 - x**

- 38:32 - 39:0 ⇒ C40**
- 31:16 - 31:0 ⇒ C32**
- 23:16 - 23:0 ⇒ C24**
- 15:0 - x**

 - 15:12 - 15:0 ⇒ C16**
- 11:8 - 11:0**
- 7:4 - 7:0 ⇒ C8**
- 3:0 - x**


MCC - General Case

- ◆ **MCC** accepts 4 pairs of inputs:
- ◆ $(P_{i_1:i_0}, G_{i_1:i_0}), (P_{j_1:j_0}, G_{j_1:j_0}), (P_{k_1:k_0}, G_{k_1:k_0}), (P_{l_1:l_0}, G_{l_1:l_0})$
- ◆ where $i_1 \geq i_0, j_1 \geq j_0, k_1 \geq k_0, l_1 \geq l_0$
- ◆ Produces 3 pairs of outputs:
- ◆ $(P_{j_1:i_0}, G_{j_1:i_0}), (P_{k_1:i_0}, G_{k_1:i_0}), (P_{l_1:i_0}, G_{l_1:i_0})$
- ◆ where $i_1 \geq j_0 - 1, j_1 \geq k_0 - 1, k_1 \geq l_0 - 1$
- ◆ Allows overlap among input subgroups




Carry Tree

- ◆ **First level** - 14 **MCCs** calculating $(P_{3:0}, G_{3:0}), \dots, (P_{55:52}, G_{55:52})$
 - * only outputs $P_{3:0}$ and $G_{3:0}$ are utilized
- ◆ **Second level:** each **MCC** generates 2 pairs $(P_{3:0}, G_{3:0}), (P_{1:0}, G_{1:0})$
- ◆ Providing $(P_{7:0}, G_{7:0}), (P_{15:0}, G_{15:0}), (P_{23:16}, G_{23:16}), (P_{31:16}, G_{31:16}), (P_{39:32}, G_{39:32}), (P_{47:32}, G_{47:32}), (P_{55:48}, G_{55:48})$
- ◆ Generates C_8 & C_{16} - $G_{7:0}$ & $G_{15:0}$
- ◆ C_0 is incorporated into **MCC*** for $(P_{3:0}, G_{3:0})$

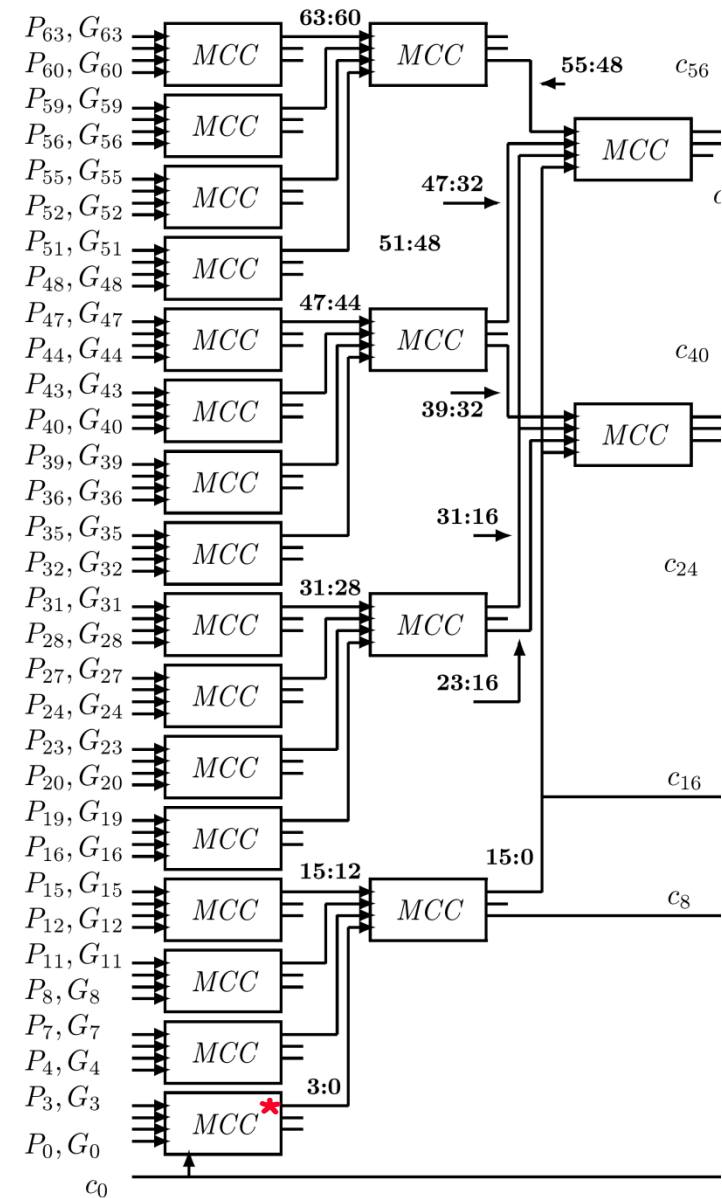

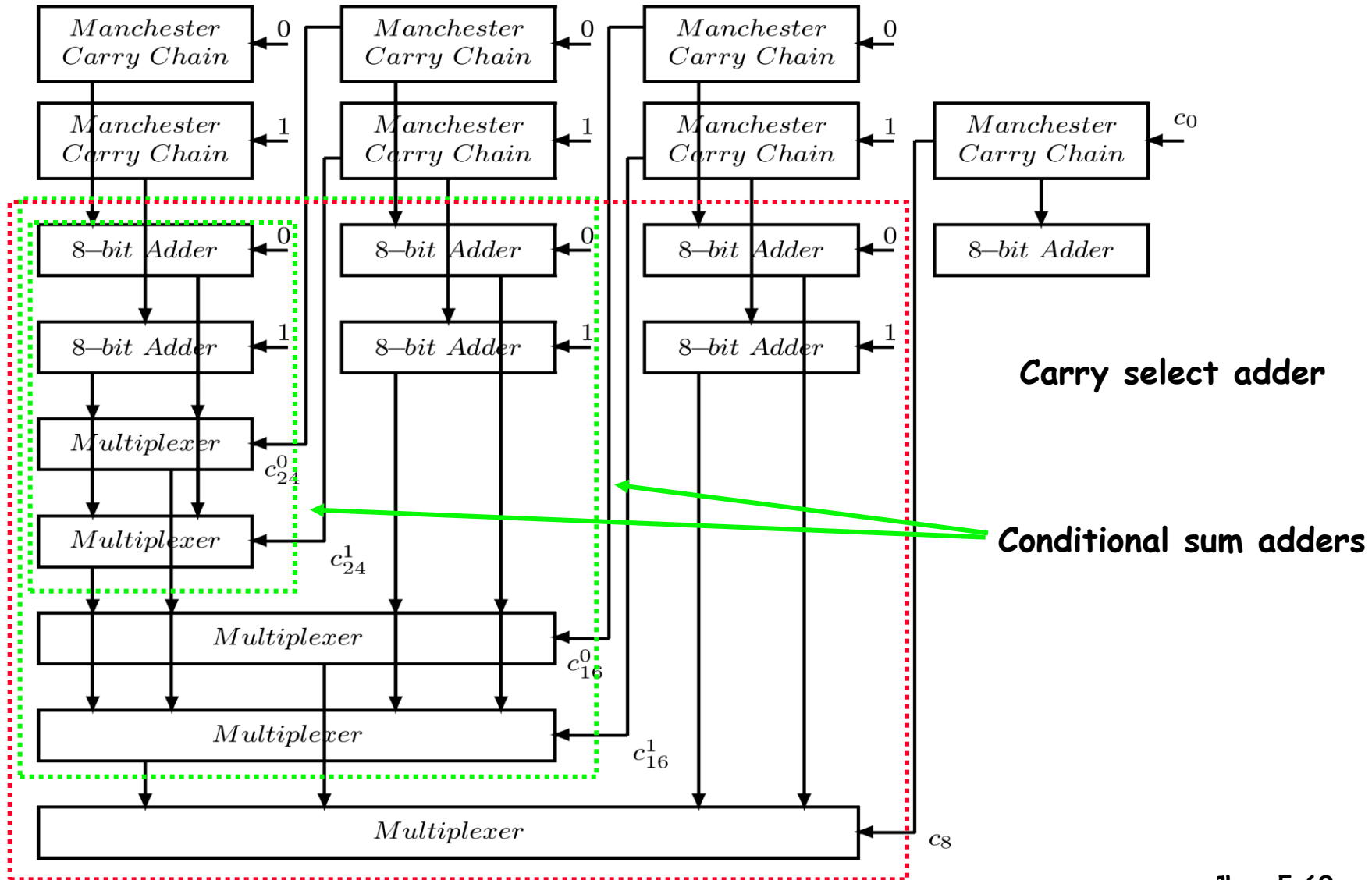A Schematic Diagram of a 32-bit Hybrid Adder




Grouping of Bits in a 64-bit Adder

- ◆ 64 bits divided into two sets of 32 bits, each set further divided into 4 groups of 8 bits
- ◆ For every group of 8 bits - 2 sets of conditional sum outputs generated separately
- ◆ Two most significant groups combined into group of size 16
- ◆ Further combined with next group of 8 to form group of 24 bits and so on
 - * principle of conditional-sum addition
 - * However, the way input carries for basic 8-bit groups are generated is differently with MCC
- ◆ MCC generates P_m , G_m and K_m and C_{out}^0 , C_{out}^1 for assumed incoming carries of 0 and 1
- ◆ Conditional carry-out signals control multiplexers

Dual and Regular Multiplexer

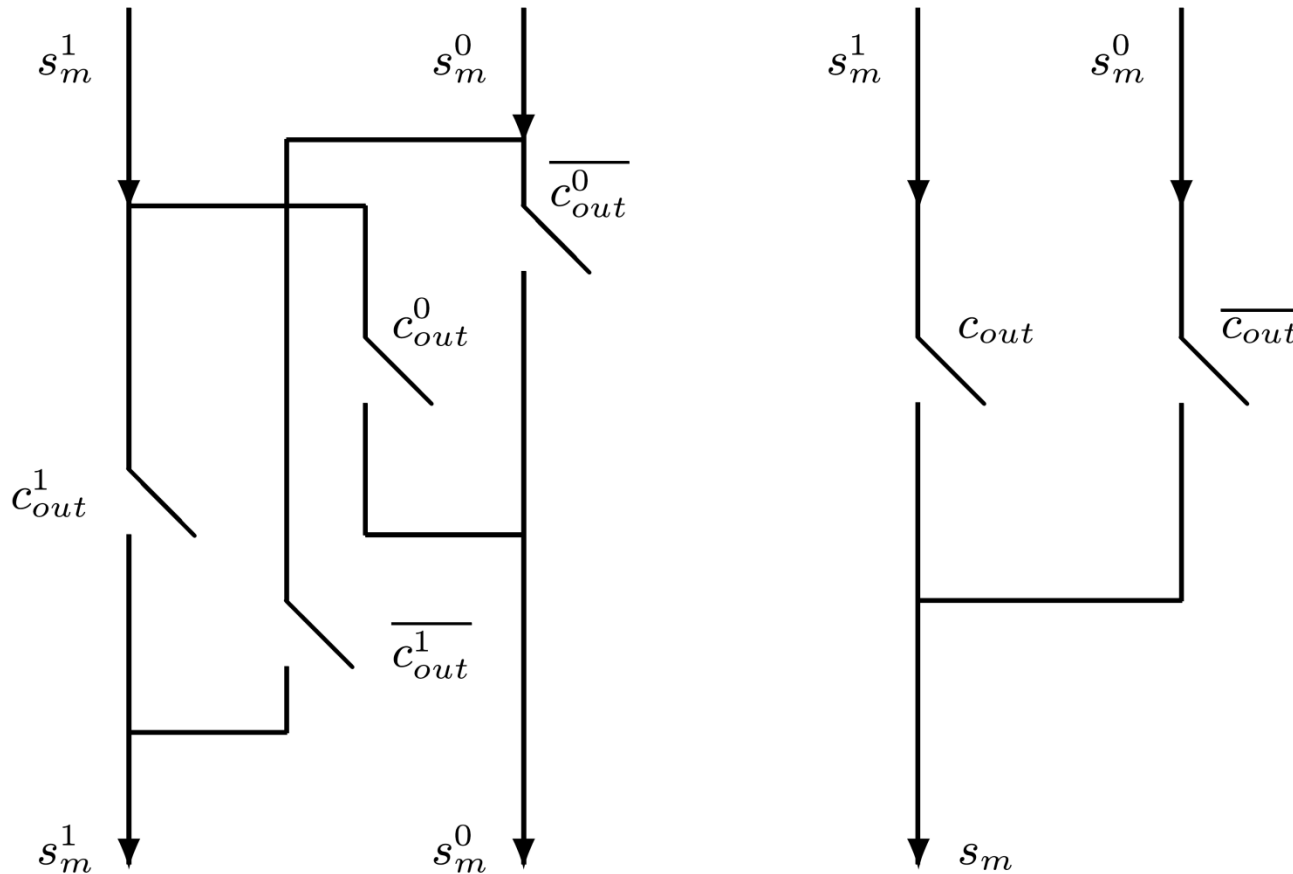- ◆ Two sets of dual multiplexers (of size 8 and 16)
- ◆ Single regular multiplexer of size 24



High-Order Half of 64-bit Adder

- ◆ Similar structure but incoming carry C_{32} calculated by separate carry-look-ahead circuit
- ◆ Inputs are conditional carry-out signals generated by 4 MCCs
- ◆ Allows operation of high-order half to overlap operation of low-order half
- ◆ **Summary**: combines variants of 3 different techniques for fast addition: Manchester carry generation, carry-select, conditional-sum
- ◆ Other designs of hybrid adders exist - e.g., groups with unequal number of bits
- ◆ "Optimality" of hybrid adders depends on technology and delay parameters



Carry-Save Adders (CSAs)


- ◆ 3 or more operands added simultaneously (e.g., in multiplication) using 2-operand adders
- ◆ Time-consuming carry-propagation must be repeated several times: k operands - $k-1$ propagations
- ◆ Techniques for lowering this penalty exist - most commonly used - carry-save addition
- ◆ Carry propagates only in last step - other steps generate partial sum and sequence of carries
- ◆ Basic CSA accepts 3 n -bit operands; generates 2 n -bit results: n -bit partial sum, n -bit carry
- ◆ Second CSA accepts the 2 sequences and another input operand, generates new partial sum and carry
- ◆ CSA reduces number of operands to be added from 3 to 2 without carry propagation

Implementing Carry Save Adders


- ◆ Simplest implementation - **full adder (FA)** with 3 inputs x, y, z
- ◆ $x+y+z=2c+s$ (s, c - sum and carry outputs)

$$s = (x + y + z) \bmod 2 \quad \text{and} \quad c = \frac{(x + y + z) - s}{2}.$$

 - ◆ Outputs - weighted binary representation of number of 1's in inputs
- ◆ **FA** called a **(3,2)** counter
- ◆ **n-bit CSA**: n **(3,2)** counters in parallel with no carry links




Carry-Save Adder for four 4-bit Operands

 

- * Upper 2 levels - 4-bit CSAs
- * 3rd level - 4-bit carry-propagating adder (CPA)
- * Ripple-carry adder - can be replaced by a carry-look-ahead adder or any other fast CPA
- * Partial sum bits and carry bits interconnected to guarantee that only bits having same weight are added by any (3,2) counter



Adding k Operands

 

- ◆ $(k-2)$ CSAs + one CPA
- ◆ If CSAs arranged in cascade - time to add k operands is $(k-2)T_{CSA} + T_{CPA}$
- ◆ T_{CPA} ; T_{CSA} - operation time of CPA ; CSA
- ◆ ΔG ; Δ_{FA} delay of a single gate ; full adder
- ◆ $T_{CSA} = \Delta_{FA} \geq 2 \Delta G$
- ◆ Sum of k operands of size n bits each can be as large as $k(2^n - 1)$
- ◆ Final addition result may reach a length of $n + \lceil \log_2 k \rceil$ bits

Six-operand Wallace Tree

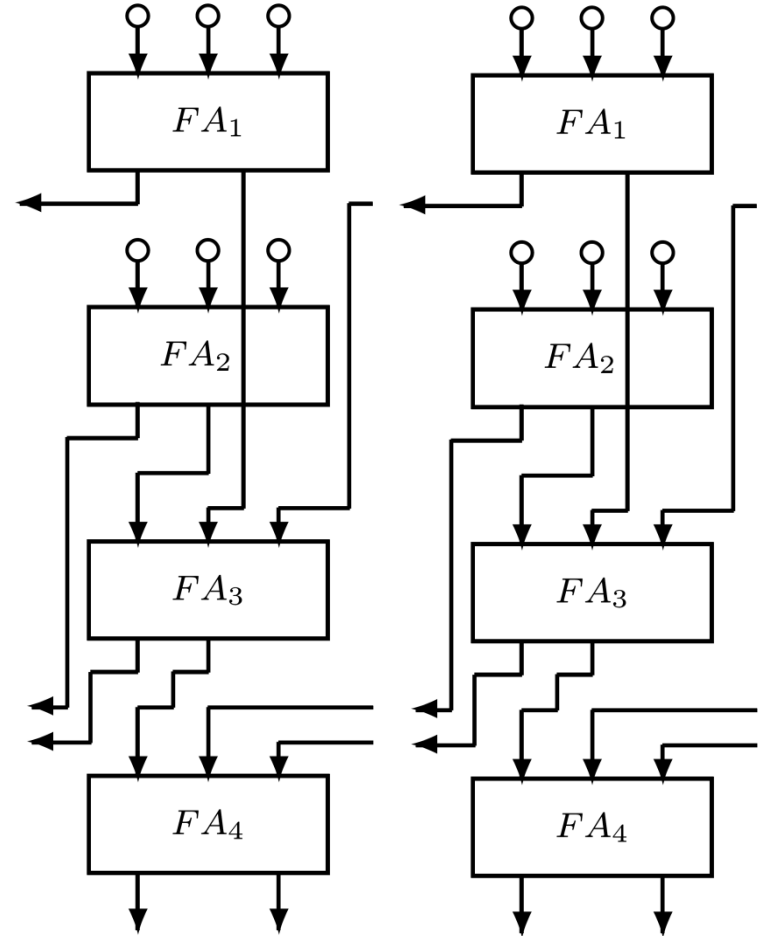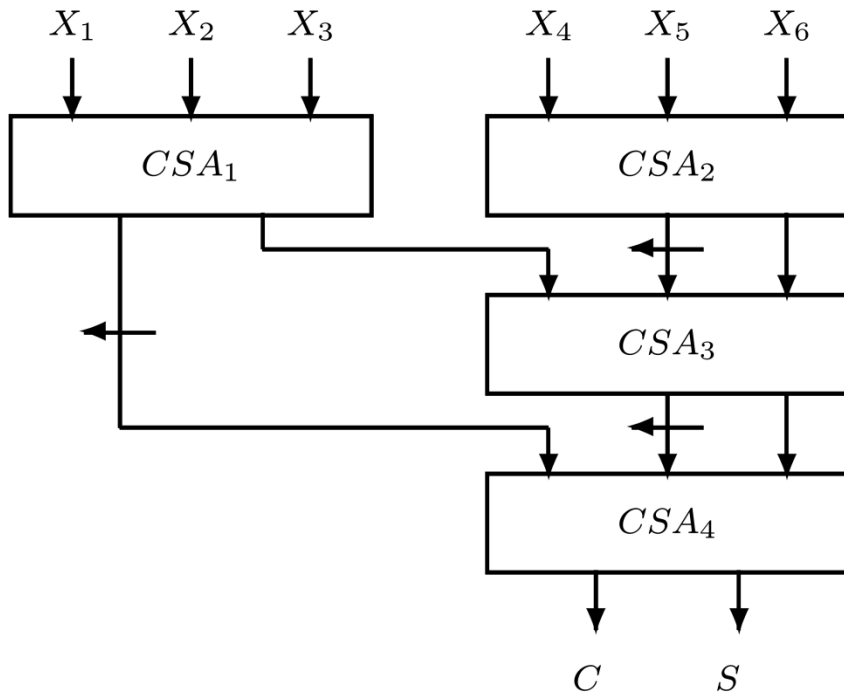- ◆ Better organization for **CSAs** - faster operation time



Number of Levels in Wallace Tree

- ◆ Number of operands reduced by a factor of $2/3$ at each level - $k \cdot \left(\frac{2}{3}\right)^l \leq 2$ (l - number of levels)
- ◆ Consequently, $l = \text{Number of levels} \approx \frac{\log(k/2)}{\log(3/2)}$.
- ◆ Only an estimate of l - number of operands at each level must be an integer
- ◆ N_i - number of operands at level i
- ◆ N_{i+1} - at most $\lfloor 3/2 N_i \rfloor$ ($\lfloor x \rfloor$ - largest integer smaller than or equal to x)
- ◆ Bottom level (0) has 2 - maximum at level 1 is 3 - maximum at level 2 is $\lfloor 9/2 \rfloor = 4$
- ◆ Resulting sequence: 2, 3, 4, 6, 9, 13, 19, 28, ...
- ◆ For 5 operands - still 3 levels

Number of Levels in a CSA Tree for k operands

Number of operands	Number of levels
3	1
4	2
$5 \leq k \leq 6$	3
$7 \leq k \leq 9$	4
$10 \leq k \leq 13$	5
$14 \leq k \leq 19$	6
$20 \leq k \leq 28$	7
$29 \leq k \leq 42$	8
$43 \leq k \leq 63$	9

◆ **Example:** $k=12$ - 5 levels - delay of $5T_{CSA}$ instead of $10T_{CSA}$ in a linear cascade of 10 CSAs


Most Economical Implementation (Fewer CSAs)

- ◆ Achieved when number of operands is element of **3, 4, 6, 9, 13, 19, 28, ...**
- ◆ If given number of operands, **k**, not in sequence - use only enough **CSAs** to reduce **k** to closest (smaller than **k**) element
- ◆ **Example**: **k=27**, use **8 CSAs** (**24** inputs) rather than **9**, in top level - number of operands in next level is **$8 \times 2 + 3 = 19$**
- ◆ Remaining part of tree will follow the series

Number of operands	Number of levels
3	1
4	2
$5 \leq k \leq 6$	3
$7 \leq k \leq 9$	4
$10 \leq k \leq 13$	5
$14 \leq k \leq 19$	6
$20 \leq k \leq 28$	7
$29 \leq k \leq 42$	8
$43 \leq k \leq 63$	9

(7,3) and Other Counters

 - ◆ (7,3) counter: 3 outputs - represent number of 1's in 7 inputs
- ◆ Another example: (15,4) counter
- ◆ In general: (k,m) counter -
k and m satisfy
 $2^m - 1 \geq k$ or
 $m \geq \lfloor \log_2(k+1) \rfloor$
- ◆ (7,3) counter using (3,2) counters:
- ◆ Requires 4 (3,2)'s in 3 levels - no speed-up



(7,3) Counters


- ◆ (7,3) can be implemented as a multilevel circuit - may have smaller delay
- ◆ Number of interconnections affects silicon area - (7,3) preferable to (3,2)
 - * (7,3) has 10 connections and removes 4 bits
 - * (3,2) has 5 connections and removes only 1 bit
- ◆ Another implementation of (7,3) - ROM of size $2^7 \times 3 = 128 \times 3$ bits
- ◆ Access time of ROM unlikely to be small enough
- ◆ Speed-up may be achieved for ROM implementation of (k,m) counter with higher values of k

Avoiding Second Level of Counters


- ◆ Several $(7,3)$ counters (in parallel) are used to add 7 operands - 3 results obtained
- ◆ Second level of $(3,2)$ counters needed to reduce the 3 to 2 results (sum and carry) added by a CPA
- ◆ Similarly - when $(15,4)$ or more complex counters are used - more than two results generated
- ◆ In some cases - additional level of counters can be combined with first level - more convenient implementation
- ◆ When combining a $(7,3)$ counter with a $(3,2)$ counter - combined counter called a $(7:2)$ compressor

(k;m) Compressor

- ◆ Variant of a counter with k primary inputs, all of weight 2^i , and m primary outputs of weights $2^i, 2^{i+1}, \dots, 2^{i+m-1}$
- ◆ Compressor has several incoming carries of weight 2^i from previous compressors, and several outgoing carries of weights 2^{i+1} and up
- ◆ Trivial example of a (6;2) compressor:
- ◆ All outgoing carries have weight 2^{i+1}
- ◆ Number of outgoing carries = number of incoming carries = $k-3$ (in general)

 

Implementation of a (7;2) Compressor

 

* Bottom right (3,2)
 - additional (3,2),
 while remaining four
 - ordinary (7,3)
 counter

- * 7 primary inputs of weight 2^i and 2 carry inputs from columns $i-1$ and $i-2$
- * 2 primary outputs, $S2^i$ and $S2^{i+1}$, and 2 outgoing carries $C2^{i+1}$, $C2^{i+2}$, to columns $i+1$ and $i+2$
- * Input carries do not participate in generation of output carries - avoids slow carry-propagation
- * Not a (9,4) counter - 2 outputs with same weight
- * Above implementation does not offer any speedup
- * Multilevel implementation may yield smaller delay as long as outgoing carries remain independent of incoming carries


multiple-column counters

- ◆ **Generalized parallel counter:** add l input columns and produce m -bit output - $(k_{l-1}, k_{l-2}, \dots, k_0, m)$
- ◆ k_i - number of input bits in i -th column with weight 2^i
- ◆ (k, m) counter - a special case
- ◆ Number of outputs m must satisfy

$$2^m - 1 \geq \sum_{i=0}^{l-1} k_i 2^i$$

- ◆ If all l columns have same height k -
 $(k_0 = k_1 = \dots = k_{l-1} = k)$ -
 $2^m - 1 \geq k(2^l - 1)$

Example - (5,5,4) Counter

 

- ◆ $k=5, l=2, m=4$
- ◆ $2^m - 1 = k(2^l - 1)$ -
all 16 combinations
of output bits are useful



- ◆ (5,5,4) counters can be used to reduce 5 operands (of any length) to 2 results that can then be added with one CPA
- ◆ Length of operands determines number of (5,5,4) counters in parallel
- ◆ Reasonable implementation - using ROMs
- ◆ For (5,5,4) - $2^{5+5} \times 4$ (=1024x4) ROM

Number of Results of General Counters



- ◆ String of (k, k, \dots, k, m) counters may generate more than 2 intermediate results
 - * requiring additional reduction before CPA
- ◆ Number of intermediate results:
- ◆ A set of (k, k, \dots, k, m) counters, with l columns each, produces m -bit outputs at intervals of l bits
- ◆ Any column has at most $\lceil m/l \rceil$ output bits
- ◆ k operands can be reduced to $s = \lceil m/l \rceil$ operands
 - * If $s=2$ - a single CPA can generate final sum
 - * Otherwise, reduction from s to 2 needed

Example

- ◆ Number of bits per column in a 2-column counter (k,k,m) is increased beyond 5 - $m \geq 5$ and $s = \lceil m/2 \rceil > 2$
- ◆ For $k=7$, $2^m - 1 \geq 7 \times 3 = 21 \Rightarrow m=5$
- ◆ $(7,7,5)$ counters generate $s=3$ operands - another set of $(3,2)$ counters is needed to reduce number of operands to 2

Reducing Hardware Complexity of CSA Tree

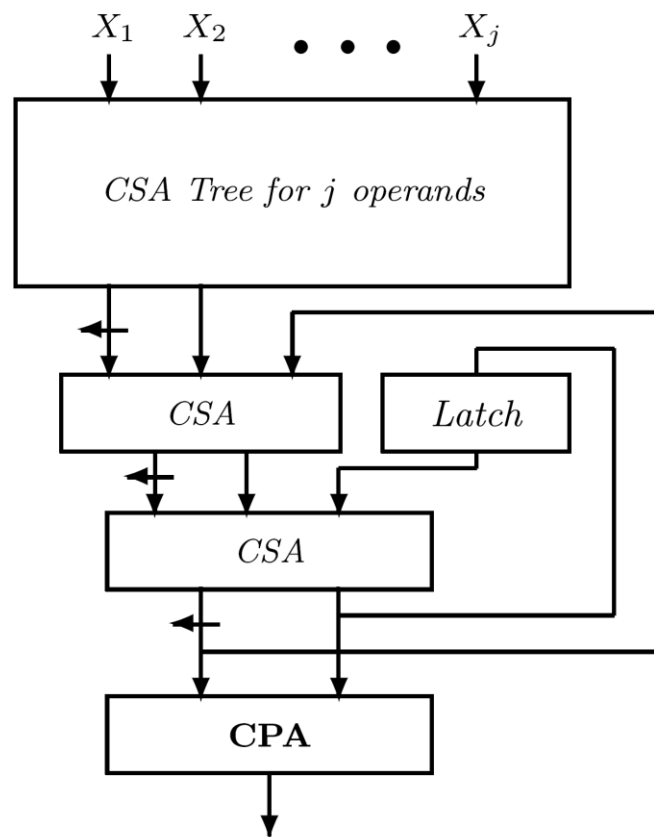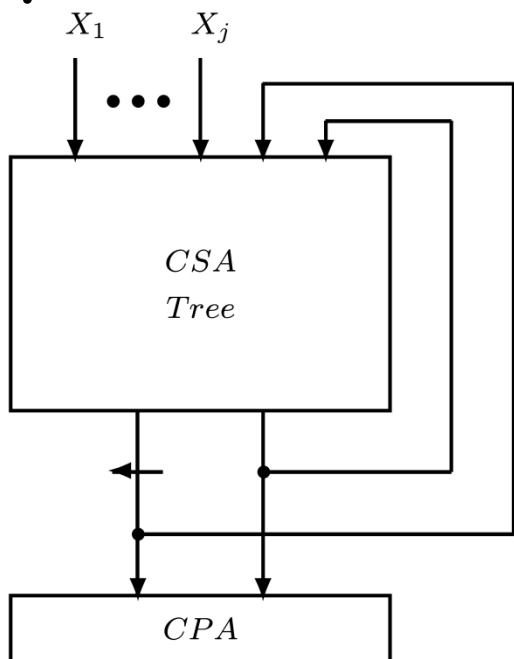- ◆ Design a smaller carry-save tree - use it iteratively
- ◆ n operands divided into $\lceil n/j \rceil$ groups of j operands - design a tree for $j+2$ operands and a CPA




- ◆ Feedback paths - must complete first pass through CSA tree before second set of j operands is applied
- ◆ Execution slowed down - pipelining not possible

Pipelining of Arithmetic Operations

- ◆ **Pipelining** - well known technique for accelerating execution of successive identical operations
- ◆ Circuit partitioned into several subcircuits that can operate independently on consecutive sets of operands
- ◆ Executions of several successive operations overlap - results produced at higher rate
- ◆ Algorithm divided into several steps - a suitable circuit designed for each step
- ◆ **Pipeline stages** operate independently on different sets of operands
- ◆ Storage elements - **latches** - added between adjacent stages - when a stage works on one set of operands, preceding stage can work on next set of operands


Pipelining - Example

 

- ◆ Addition of 2 operands X, Y performed in 3 steps
- ◆ Latches between stages 1 and 2 store intermediate results of step 1
- ◆ Used by stage 2 to execute step 2 of algorithm
- ◆ Stage 1 starts executing step 1 on next set of operands X, Y

Pipelining Timing Diagram

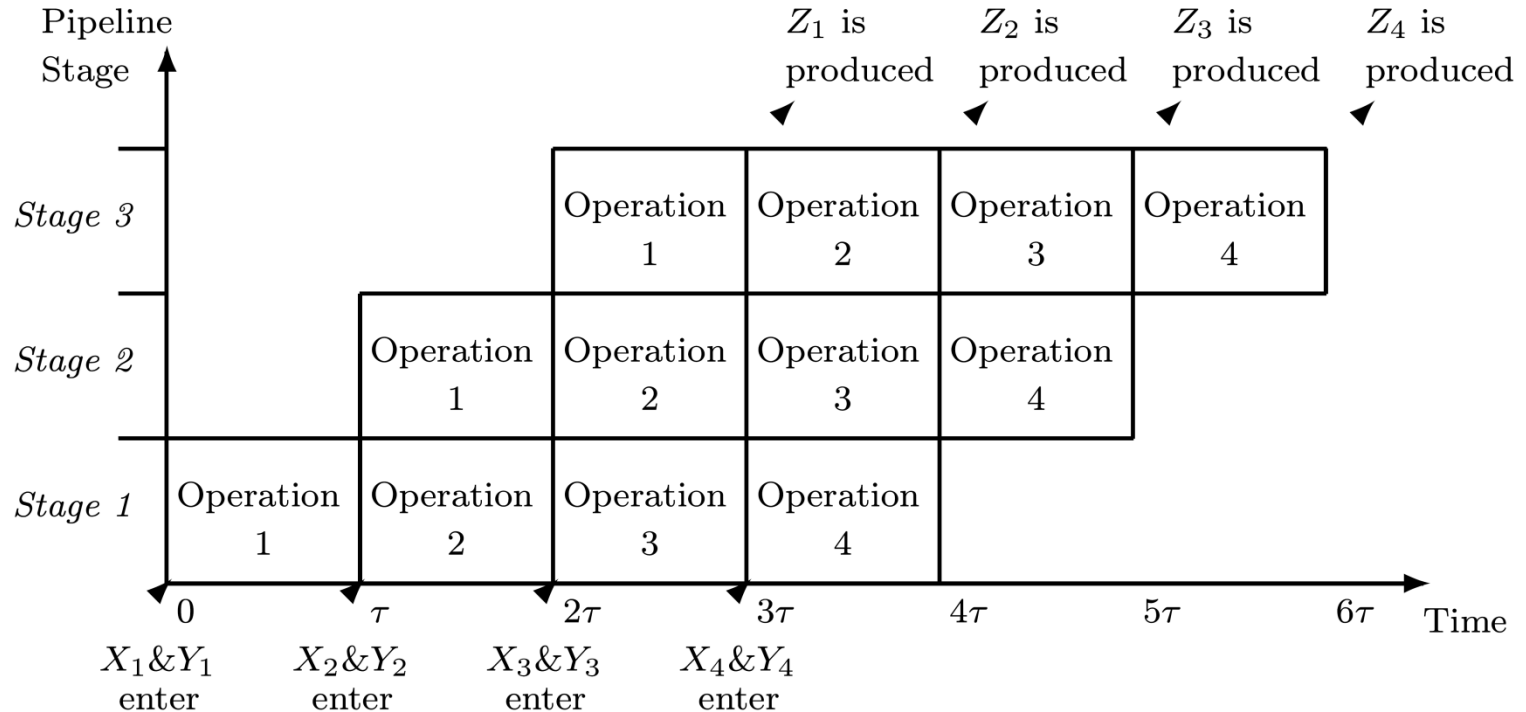- ◆ 4 successive additions with operands X_1 & Y_1 , X_2 & Y_2 , X_3 & Y_3 , X_4 & Y_4 producing results Z_1 , Z_2 , Z_3 , Z_4



Pipeline Rate

- ◆ τ_i - execution time of stage i
- ◆ τ_l - time needed to store new data into latch
- ◆ Delays of different stages not identical - faster stages wait for slowest before switching to next task
- ◆ τ - time interval between two successive results being produced by pipeline:
$$\tau = \max_{1 \leq i \leq k} \{\tau_i\} + \tau_l$$
- ◆ k - number of stages
- ◆ τ - pipeline period ; $1/\tau$ - pipeline rate or bandwidth
- ◆ Clock period $\geq \tau$
- ◆ After latency of 3τ , new results produced at rate $1/\tau$

Design Decisions

- ◆ Partitioning of given algorithm into steps to be executed by separate stages
 - * Steps should have similar execution times - pipeline rate determined by slowest step
- ◆ Number of steps
 - * As this number increases, pipeline period decreases, but number of latches (implementation cost) and latency go up
- ◆ Latency - time elapsed until first result produced
 - * Especially important when only a single pass through pipeline required
- ◆ Tradeoff between latency and implementation cost on one hand and pipeline rate on the other hand
- ◆ Extra delay due to latches, τ_l , can be lowered by using special circuits like Earl latch

Pipelining of Two-Operand Adders

- ◆ Two-operand adders - usually not pipelined
- ◆ Pipelining justified with many successive additions
- ◆ Conditional-sum adder - easily pipelined
- ◆ $\log_2 n$ stages corresponding to $\log_2 n$ steps - execution of up to $\log_2 n$ additions can be overlapped
- ◆ Required number of latches may be excessive
- ◆ Combining several steps to one stage reduces latches' overhead and latency
- ◆ Carry-look-ahead adder cannot be pipelined - some carry signals must propagate backward
- ◆ Different designs can be pipelined - final carries and carry-propagate signals (implemented as $P_i = x_i \oplus y_i$) used to calculate sum bits - no need for feedback connections

Pipelining in Multiple-Operand Adders

- ◆ Pipelining more beneficial in multiple-operand adders like **carry-save adders**
- ◆ Modifying implementation of **CSA** trees to form a pipeline is straightforward - requires only addition of latches
- ◆ Can be added at each level of tree if maximum bandwidth is desired
- ◆ Or - two (or more) levels of tree can be combined to form a single stage, reducing overall number of latches and pipeline latency

Partial Tree

- ◆ Reduced hardware complexity of **CSA** tree - partial tree
- ◆ Two feedback connections prevent pipelining
- ◆ **Modification** - intermediate results of **CSA** tree connected to bottom level of tree
- ◆ Smaller tree with **j** inputs, **2** separate **CSAs**, and a set of latches at the bottom
- ◆ **CSAs** and latches form a pipeline stage
- ◆ Top **CSA** tree for **j** operands can be pipelined too - overall time reduced

