

Digital Logic Design

4190.201.001

2010 Spring Semester


Supplementary Slide for the lab

Naehyuck Chang
Dept. of EECS/CSE
Seoul National University
naehyuck@snu.ac.kr




Logic Tester

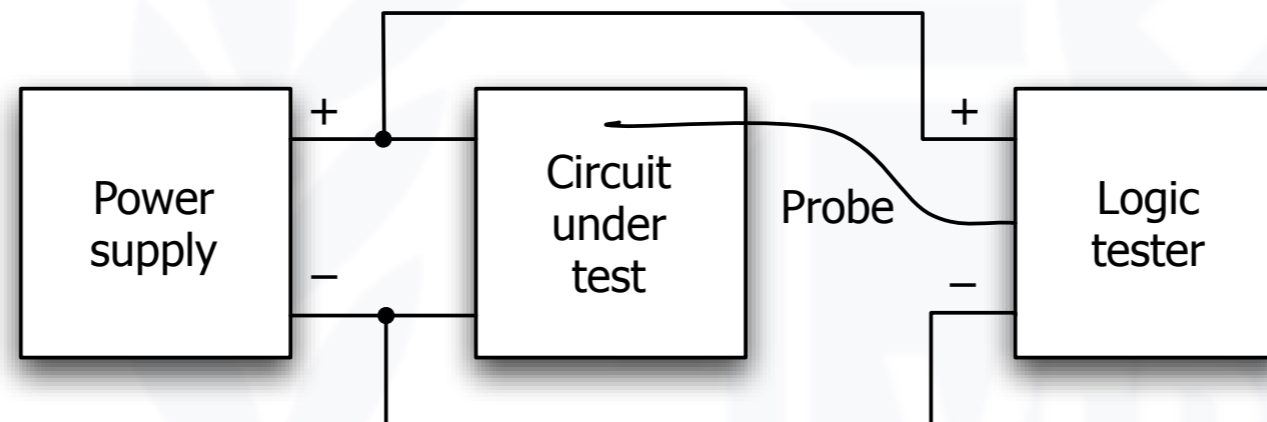- Detect high and low
 - Share the same power supply
 - Share the reference voltage, i.e., GND






CMOS Logic Gates

Threshold voltage of MOSFETs

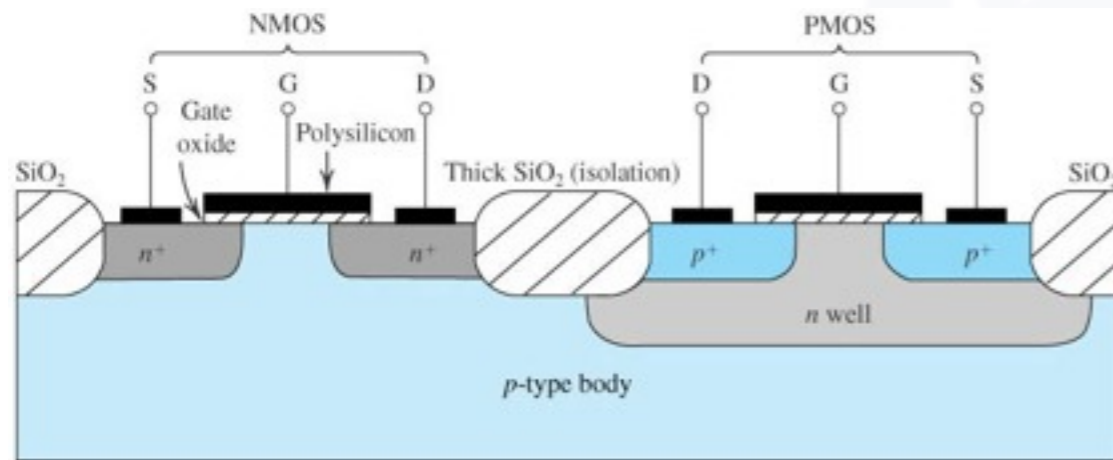

PMOS on

NMOS on

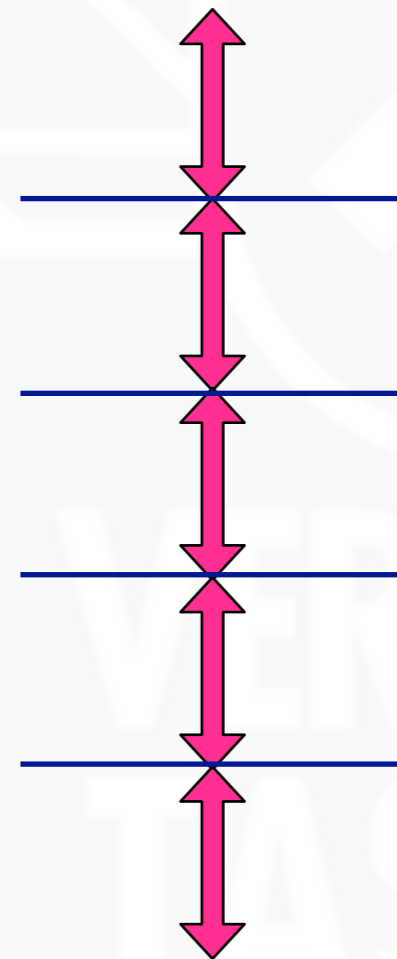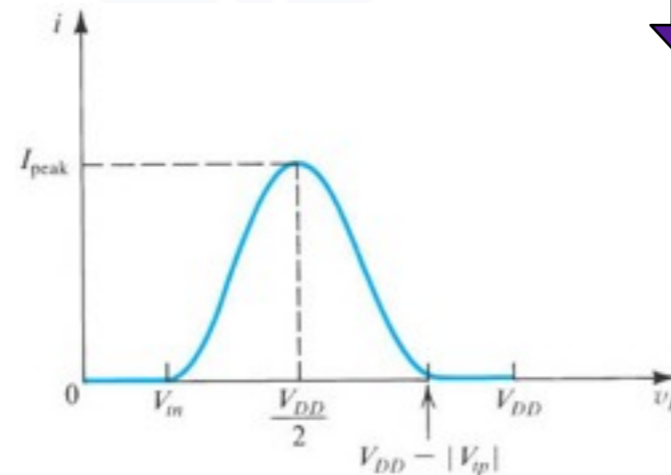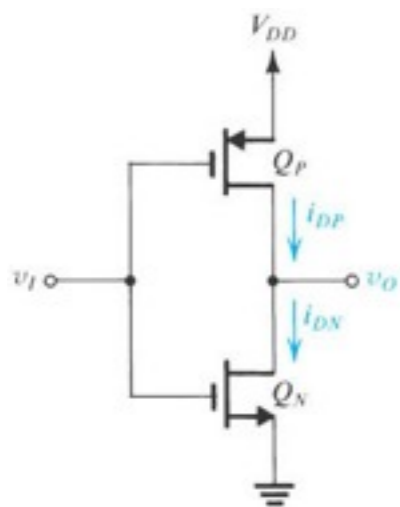

Gate is destroyed

VDD

Logic 1

VT of PMOS

Not allowed for steady state

VT of NMOS

Logic 0

GND


Gate is destroyed



Logic Tester


- Detect high

- Should have no loading effect

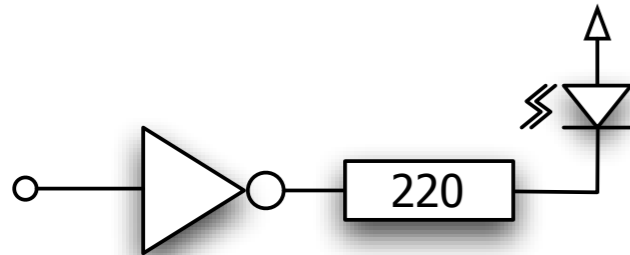

- Detect low

- Should have no loading effect

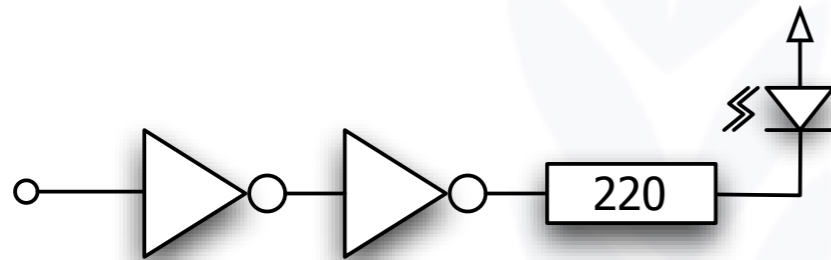

Symbol	Parameter		Min	Typ	Max	Unit
V _{CC}	Supply Voltage	54	4.5	5.0	5.5	V
		74	4.75	5.0	5.25	
T _A	Operating Ambient Temperature Range	54	-55	25	125	°C
		74	0	25	70	
I _{OH}	Output Current — High	54, 74			-0.4	mA
I _{OL}	Output Current — Low	54			4.0	mA
		74			8.0	

74LS04

- How current sink for the LED drive?

- Output impedance




SYMBOL	PARAMETER	CONDITIONS	MIN.	MAX.	UNIT
V _{CC}	supply voltage		-0.5	+7.0	V
I _{IK}	input diode current	$V_I < -0.5\text{ V}$ or $V_I > V_{CC} + 0.5\text{ V}$	-	±20	mA
I _{OK}	output diode current	$V_O < -0.5\text{ V}$ or $V_O > V_{CC} + 0.5\text{ V}$	-	±20	mA
I _O	output source or sink current	$-0.5\text{ V} < V_O < V_{CC} + 0.5\text{ V}$	-	±25	mA

74HCT04



Diode (1)



- P-N junction diode
 - 1N4148

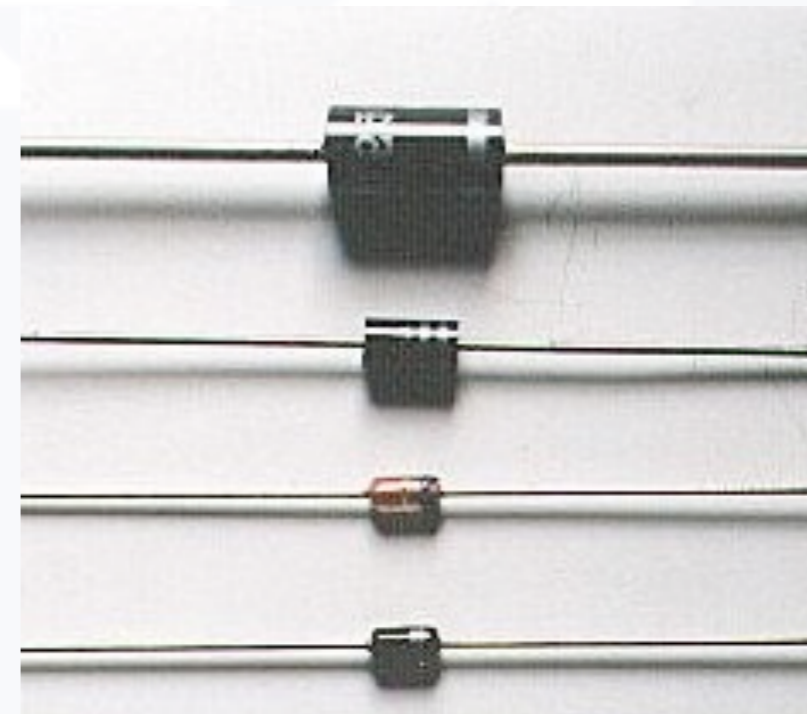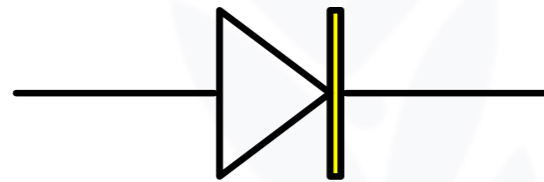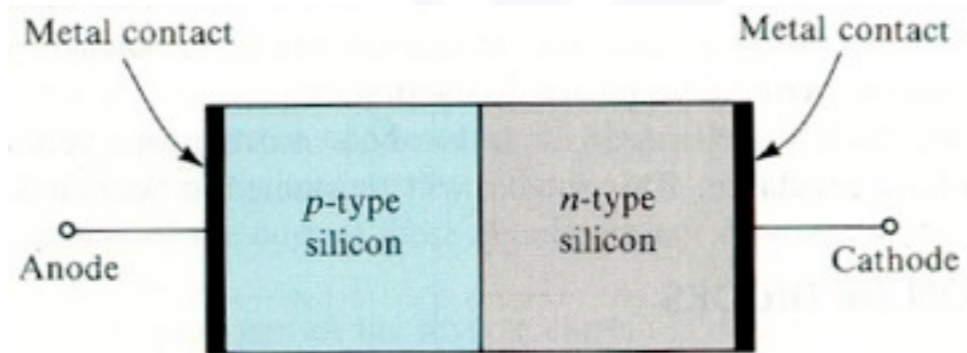

Diode (2)

- Ideal diode

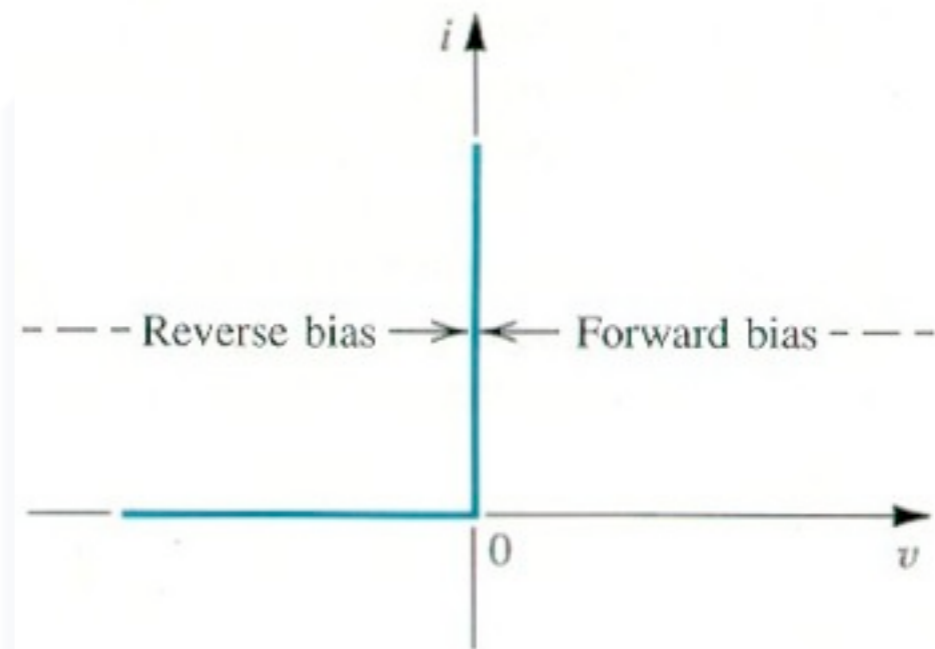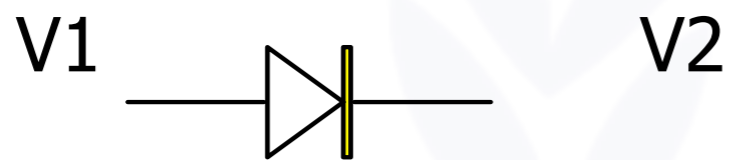- Forward bias: $V1 > V2$
- Reverse bias: $V1 < V2$



Diode (4)

- Real diode
 - Break down
- Silicon Diode
- Germanium Diode


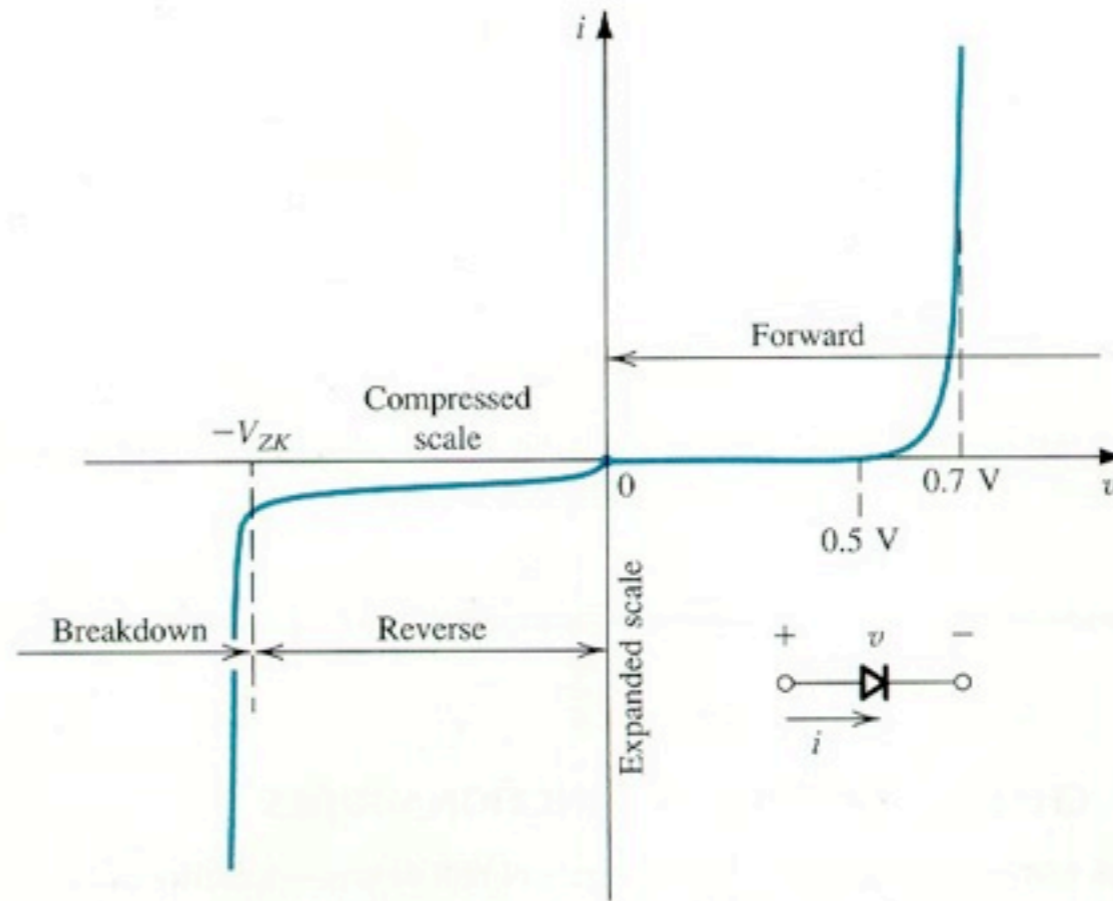


Fig. 3.8 The diode $i-v$ relationship with some scales expanded and others compressed in order to reveal details.




Logic Tester

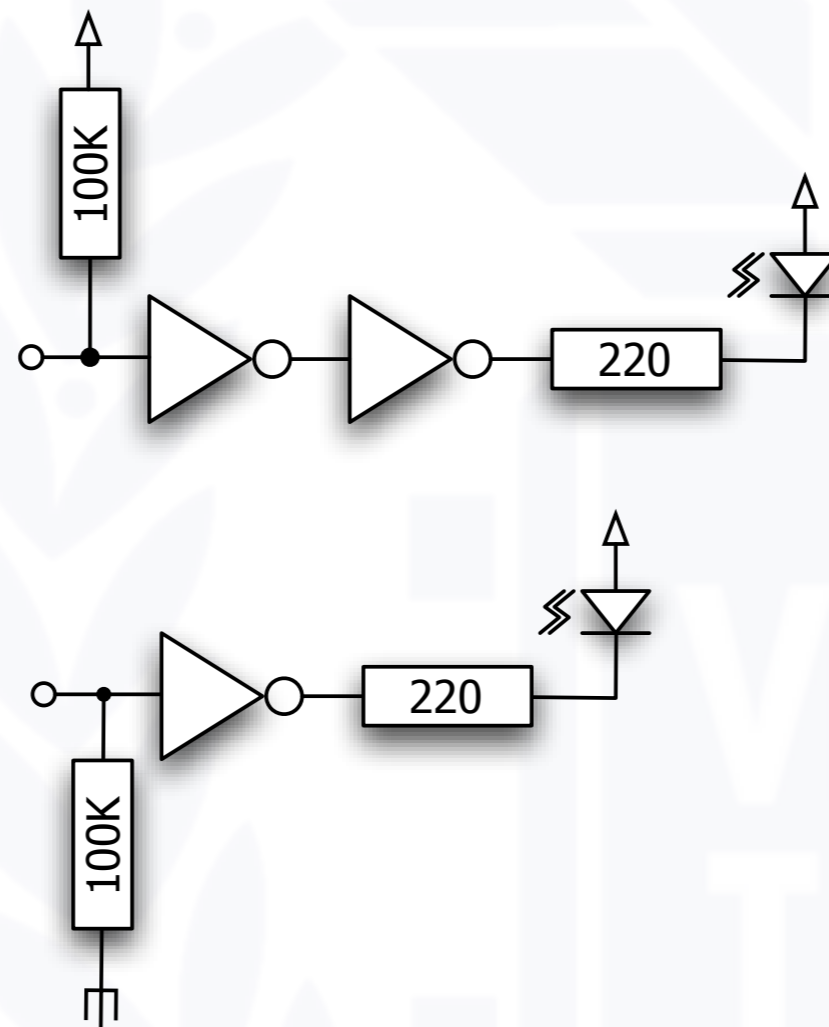- Prevent from floating
 - Can we combine these together?



Diode (6)

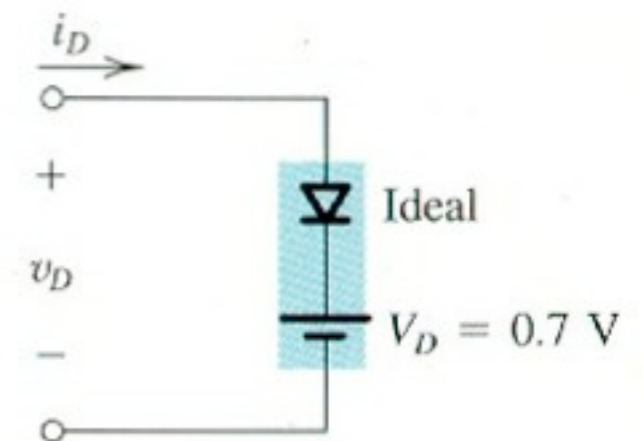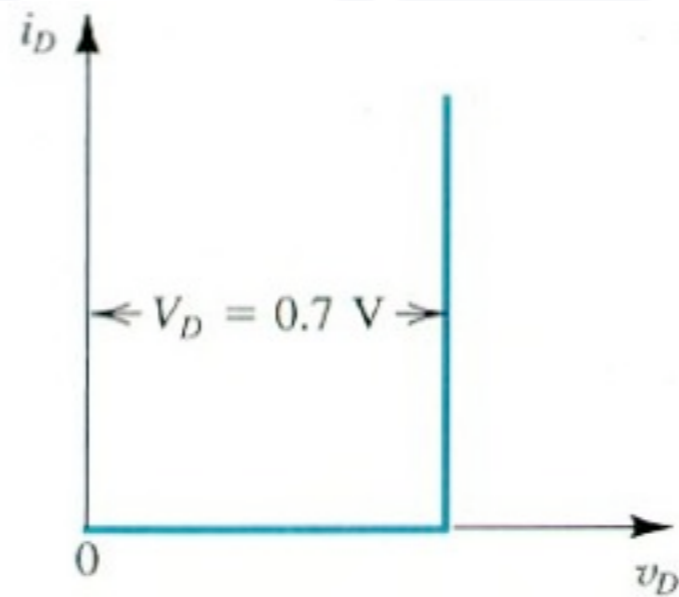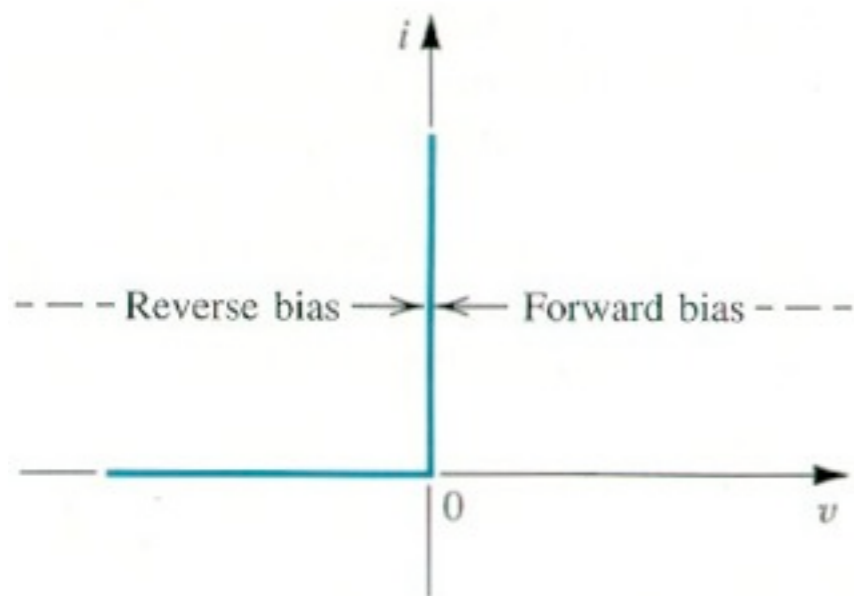- Diode in digital circuits
 - Silicon Diode: switching and rectification
 - Germanium Diode: detection



Logic Tester

- Final design

