

Quiz #6

1. Consider the following circuit below.

Assume that $V_{CC} = 15V$, $V_{EE} = -15V$, $V_T = 26mV$, $I_{S,Q1} = I_{S,Q2} = I_{S,Q3} = I_{S,Q4} = 10^{-14}A$, $V_A = \infty$, and $\beta_{Q1} = \beta_{Q2} = \beta_{Q3} = \beta_{Q4} = 100$. Also assume that the output is sinusoidal with maximum amplitude of 8V (i.e. $V_{OUT} = 8\sin\omega t$).

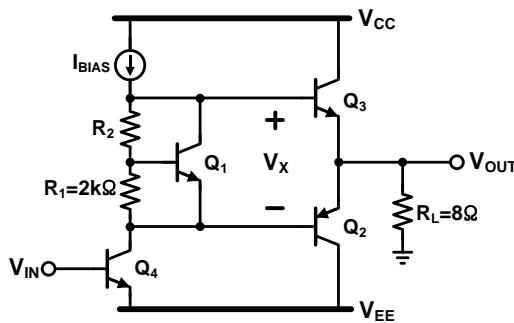


Fig. 1

- (a) Calculate the minimum value of a bias current, I_{BIAS} .


$V_{OUT} = 8V$ 일 때 I_{B3} 가 최대이므로, 이 때 $I_{B,Q3} \leq I_{BIAS}$ 조건을 만족시켜야 함.

$$\Rightarrow I_{C,Q3} = \frac{8V}{8\Omega} = (\beta + 1)I_{B,Q3}$$

$$\Rightarrow I_{B,Q3} \approx 10mA$$

$$\therefore I_{BIAS} \geq 10mA \Rightarrow I_{BIAS,min} = 10mA$$

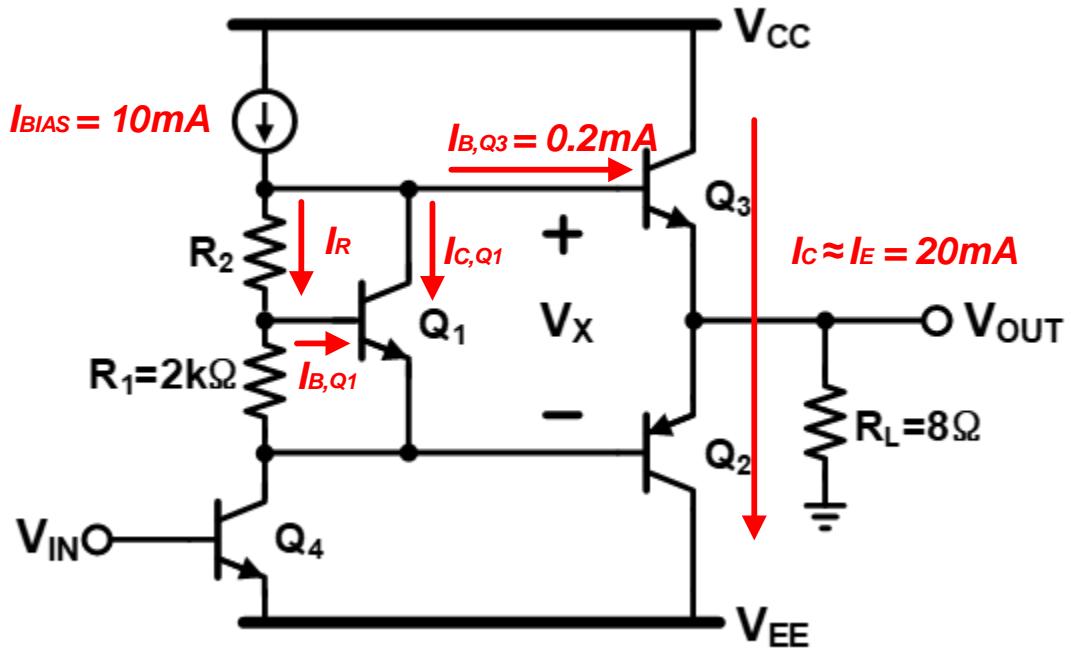- (b) Using the minimum value of (a), find the value of R_2 to set the quiescent current at the output to 20mA. (Quiescent current condition : $V_{OUT}=0$)



$$V_X = V_{BE3} + V_{EB2} = V_T \ln \frac{I_{C,Q3}}{I_{S,Q3}} + V_T \ln \frac{I_{C,Q2}}{I_{S,Q2}} = 2 \times 26mV \times \ln \frac{20mA}{10^{-14}A} = 1.473V \quad (1)$$

$$V_{BE1} = V_T \ln \frac{I_{C,Q1}}{I_{S,Q1}} = 2k\Omega \times \left(I_R - \frac{I_{C,Q1}}{\beta} \right), \quad I_{C,Q1} = 10mA - 200\mu A - I_R$$

$$\Rightarrow I_R \approx 452\mu A, \quad V_{BE1} = 0.717V \quad (2)$$

$$(1), (2) \text{에 의해 } V_X = V_{BE1} + R_2 \times I_R \Rightarrow 1.473V = 0.717 + R_2 \times 452\mu A$$

$$\therefore R_2 \approx 1.673k\Omega$$