

Chapter 1

Electric Circuit Variables

Seoul National University
Department of Electrical and Computer Engineering

Prof. SungJune Kim

Electric Circuits and Current

■ Electric circuit (or Electric network)

- An interconnection of electrical elements linked together in a closed path so that an electric current may flow continuously.

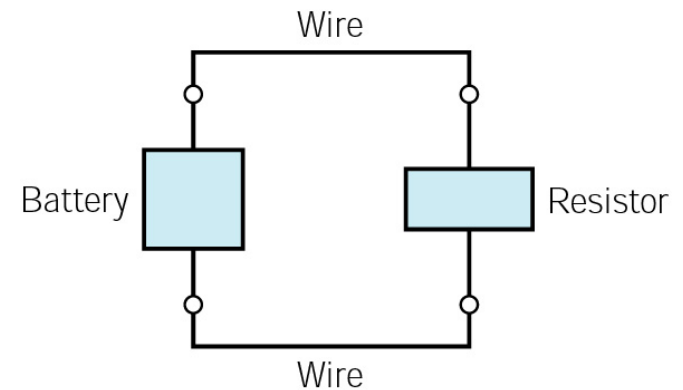


Figure 1.2-1 (p. 2)
A simple circuit

■ Charge

- Charge: The quantity of electricity responsible for electric phenomena.
- Quantity of charge; q
 - $q = -1.602 \times 10^{-19} \text{ C}$ (coulombs)
 - -1 C (Coulomb) is the charge on 6.24×10^{18} electrons.



Electric Circuits and Current (cont'd)

■ Current

- Current: The time rate of flow of electric charge past a given point.
- The unit of current: ampere (A)

$$i = \frac{dq}{dt} \quad \left\{ \begin{array}{l} i: \text{current} \\ q: \text{charge} \\ t: \text{time} \end{array} \right. \quad (\text{e.g. } 1\text{A is } 1\text{C per second.})$$

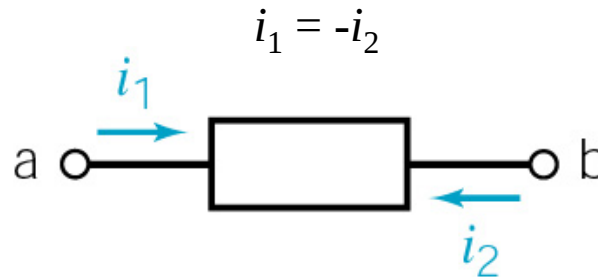


Figure 1.2-3 (p. 2)
Current in a circuit element.



Electric Circuits and Current (cont'd)

■ DC; Direct current

- A current of constant magnitude.

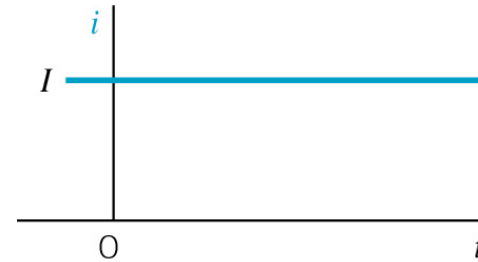


Figure 1.2-4 (p. 3)

A direct current of magnitude I .

■ AC; Alternating current

- Alternating current = sinusoidal current

$$i = I \sin \omega t, t \geq 0$$

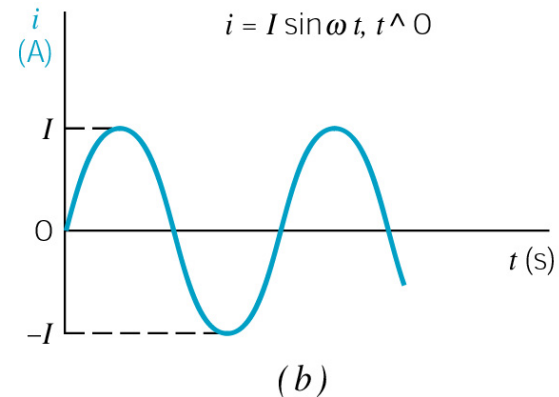


Figure 1.2-5 (p. 3)

(b) A sinusoid.



Example 1.2-2 *Charge from Current*

- Find the charge that has entered the terminal of an element from $t = 0$ s to $t = 3$ s when the current entering the element is as shown in Figure 1.2-6


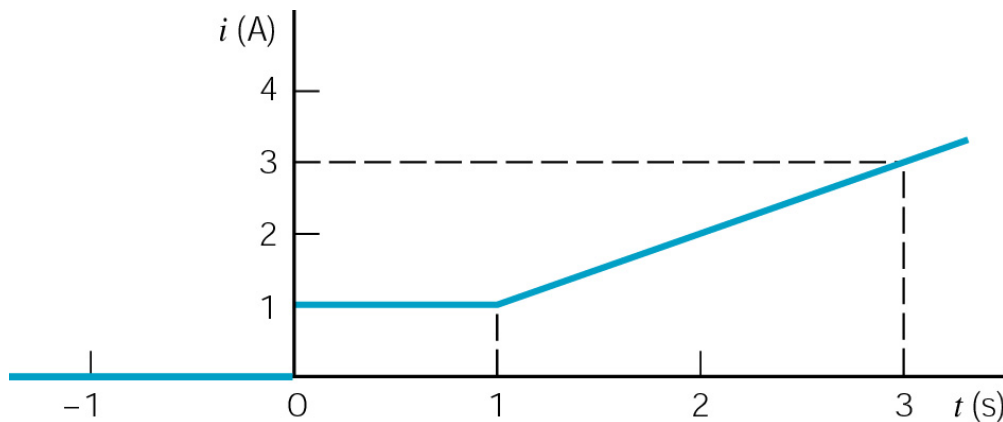


Figure 1.2-6 (p. 4)

Current waveform for Example 1.2-2

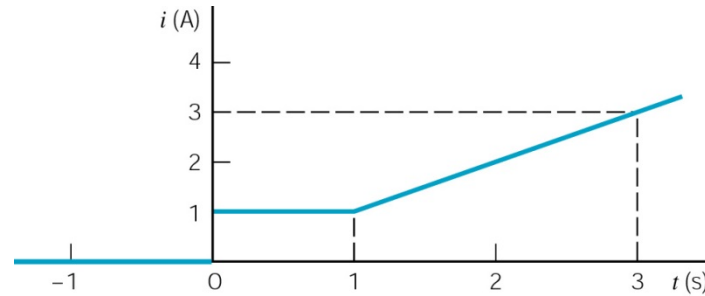

Solution



- From Figure 1.2-6 we can describe $i(t)$ as

$$i(t) = \begin{cases} 0 & t < 0 \\ 1 & 0 < t \leq 1 \\ t & t > 1 \end{cases}$$

- Using Eq. 1.3-2, we have

$$\begin{aligned} q &= \int_0^3 i(t) dt = \int_0^1 1 dt + \int_1^3 t dt \\ &= t \Big|_0^1 + \frac{t^2}{2} \Big|_1^3 \\ &= 1 + \frac{1}{2}(9-1) = 5 \text{ C} \end{aligned}$$


- Alternatively, we note that integration of $i(t)$ from $t=0$ to $t=3$ s simply requires the calculation of the area under the curve shown in Figure 1.3-6. Then, we have

$$q = 1 + 2 \times 2 = 5 \text{ C}$$



Voltage

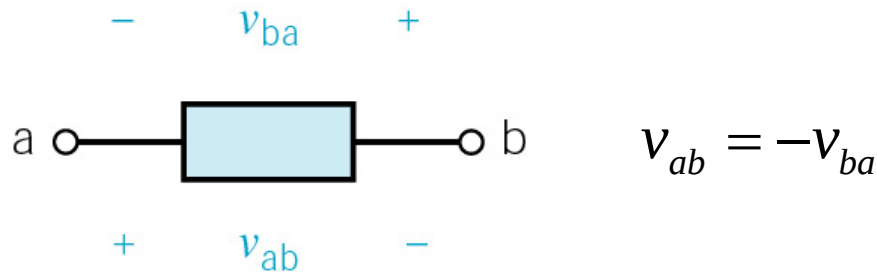- Voltage: Difference of electrical potential between two points of an electrical or electronic circuit.
- The **voltage** across an element is work (energy) required to move a unit positive charge from the – terminal to the + terminal.



Voltage across the element

$$v = \frac{dw}{dq}$$

Figure 1.4-1 (p. 7)
Voltage across a circuit element.

- The unit of voltage: volt (V)



Power and Energy

- **Energy:** The capacity to do work.
- **Power:** The time rate of expanding or absorbing energy.

$$p = \frac{dw}{dt} \quad \left\{ \begin{array}{l} p: \text{power (W)} \\ w: \text{energy (J)} \\ t: \text{time (s)} \end{array} \right.$$

$$p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = v \cdot i$$


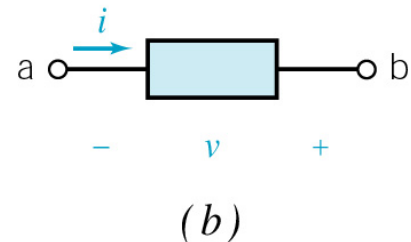


Figure 1.5-1 (p. 8)

(a) The passive convention is used for element voltage and current.


(b) The passive convention is not used.

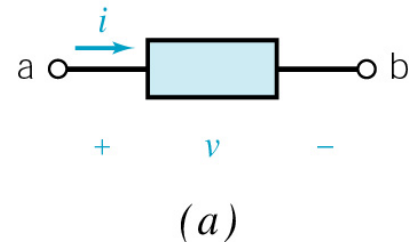

Power and Energy


Table 1.5-1 **Power Absorbed or Supplied by an Element**

POWER ABSORBED BY AN ELEMENT

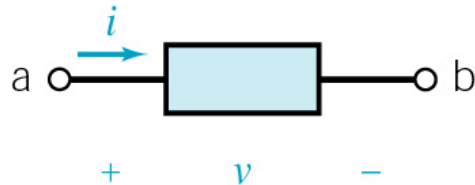

Since the reference directions of v and i adhere to the passive convention, the power $p=vi$ is the power absorbed by the element.

POWER SUPPLIED BY AN ELEMENT

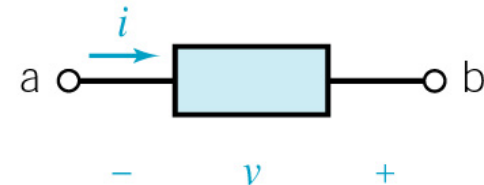

Since the reference directions of v and i do not adhere to the passive convention, the power $p=vi$ is the power supplied by the element.


power absorbed = - power supplied

$$w = \int_{-\infty}^t p d\tau \quad \left(w = \int_0^t p d\tau, t \geq 0 \right)$$



Active and Passive Circuit Elements

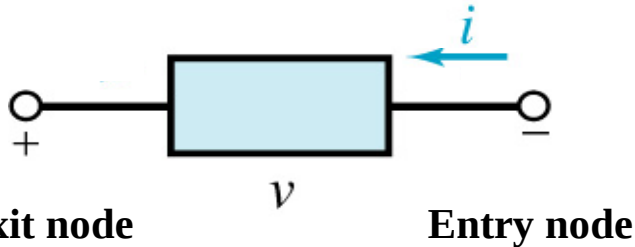
An **active element** is capable of supplying energy.



Active element는 아래 수식을 만족하는 시간 t 가 적어도 1개 있다.

$$w = \int_{-\infty}^t vi \, d\tau \geq 0$$

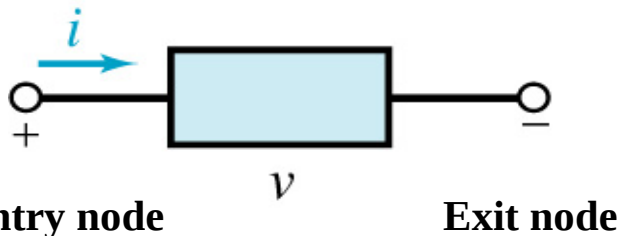A **passive element** is not capable of supplying energy. It simply absorbs energy.



Passive element는 모든 시간 t 에 대하여 아래 수식을 만족한다.

$$w = \int_{-\infty}^t vi \, d\tau \geq 0$$



Example 1.5-1 *Electrical Power and Energy*

- Let us consider the element shown in Figure 1.5-2 when $v = 8\text{ V}$ and $i = 25\text{ mA}$. Find the power absorbed by the element and the energy absorbed over a 10-ms interval.


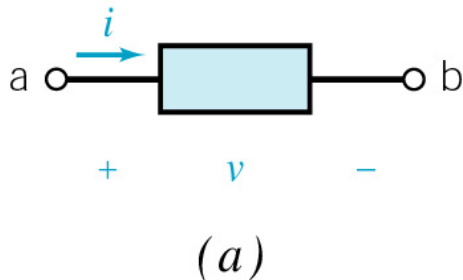


Figure 1.5-2 (p. 9)

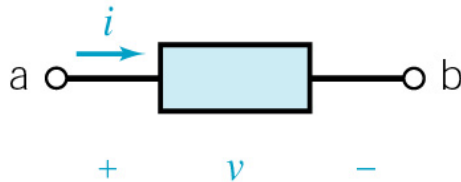

Solution



(a)

- The power absorbed by the element is

$$p = vi = 8 \cdot 0.025 = 0.2W = 200mW$$

- The energy absorbed by the element is

$$w = \int_0^t p dt = \int_0^{0.010} 0.2 dt = 0.2(0.010) = 0.002J = 2mJ$$



Example 1.5-2 *Electrical Power and the Passive Convention*

- Consider the element shown in Figure 1.5-3. The current i and voltage v_{ab} adhere to the passive convention, so the power *absorbed* by this element is

$$\text{Power absorbed} = i \cdot v_{ab} = 2 \cdot (-4) = -8\text{W}$$

The current i and voltage v_{ba} do not adhere to the passive convention, so the power *supplied* by this element is

$$\text{Power supplied} = i \cdot v_{ba} = 2 \cdot (4) = 8\text{W}$$

As expected

$$\text{Power absorbed} = -\text{Power supplied}$$

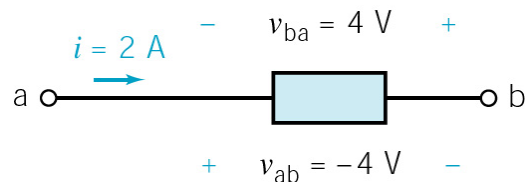


Figure 1.5-3 (p. 9)

The element considered in Example 1.5-2.



Example 1.5-3 *Electrical Power and the Passive Convention*

- Consider the circuit shown in Figure 1.5-4 with $v = 12e^{-8t}$ V and $i = 5e^{-8t}$ A for $t \geq 0$. Find the power supplied by this element and the energy supplied by the element over the first 100ms of operation. We assume that v and i are zero for $t < 0$.

Solution

- The power supplied is

$$p = vi = (12e^{-8t})(5e^{-8t}) = 60e^{-16t} \text{ W}$$

- This element is providing energy to the charge flowing through it.

The energy supplied during the first second is

$$\begin{aligned} w &= \int_0^{0.1} p dt = \int_0^{0.1} (60e^{-16t}) dt \\ &= 60 \frac{e^{-16t}}{-16} \bigg|_0^{0.1} = \frac{60}{-16} (e^{-1.6} - 1) = 3.75(1 - e^{-1.6}) = 2.99 \text{ J} \end{aligned}$$

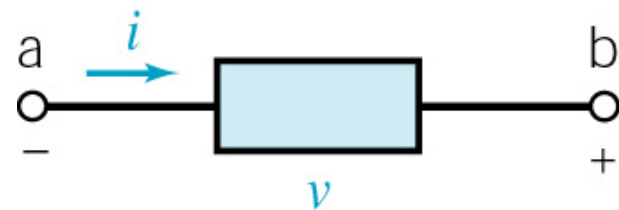


Figure 1.5-4 (p. 10)

An element with the current flowing into the terminal with a negative voltage sign.



Example 1.7-1 *How Can We Check Power and the Passive Convention*

- A laboratory report states that the measured values of v and i for the circuit element shown in Figure 1.7-1 are -5V and -2A, respectively. The report also states that the power absorbed by the element is 10W. **How can we check** the reported value of the power absorbed by this element?

Solution

- The power absorbed is

$$p = vi$$

- Substituting v and i , we have

$$p = (-5)(-2) = 10W$$

- Thus, we have verified that the circuit element is absorbing 10W.**

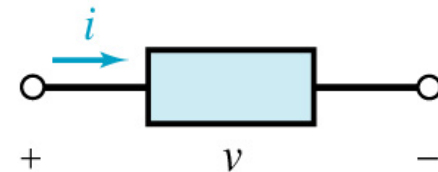


Figure 1.7-1 (p. 13)
A circuit element with a measured current and voltage.

