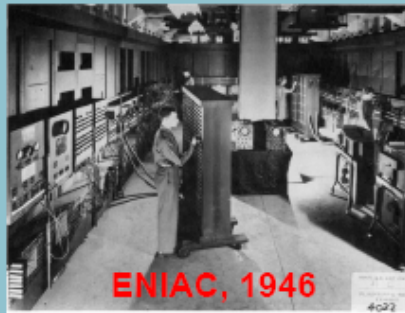

Ch 4. Combinational Logic Technologies

History

- From Switches to Integrated Circuits

- The underlying implementation technologies for digital systems

Vacuum Tubes




ENIAC, 1946



UNIVAC, 1951

1900 adds/sec

Transistors

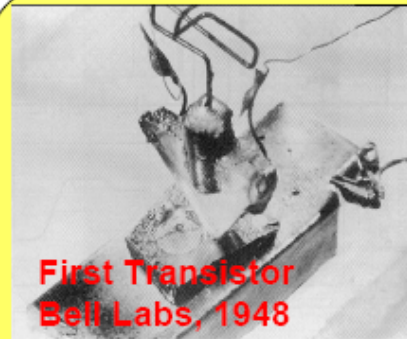

First Transistor
Bell Labs, 1948




IBM System/360, 1964

500,000 adds/sec

VLSI Circuits



4004, 1971

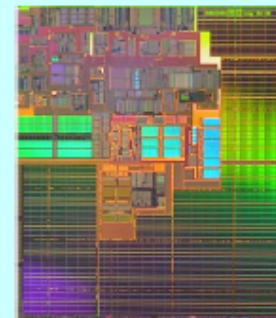

Intel Itanium, 2003

2,000,000,000
adds/sec

Packaged Logic, Configurability, and Programmable Logic

- Standard parts
 - Integrated circuits that contain small number of simple logic gates widely used
- ROM and PLA/PAL
 - ROM
 - A fixed array of ones and zeros
 - Programmable logic array (PLA), Programmable array logic (PAL)
 - An array of fixed logic gates, arranged in a standard two-level form such as AND/OR
- Application-Specific Integrated Circuit (ASIC)
 - Gate array / Standard cells
- Field-Programmable Gate Array (FPGA)

Packaged Logic, Configurability, and Programmable Logic (cont'd)

- Historical development of components

TABLE 4.2		<i>Historical Development of Components (Adapted from Oldfield and Dorf, <i>Field Programmable Gate Arrays</i>, John Wiley, New York, 1995)</i>			
	<i>1960s SSI/MSI</i>	<i>1970s LSI</i>	<i>1980s VLSI</i>	<i>1990s Programmable Logic</i>	
<i>Components</i>	Logic, Resistor/ Transistor elements	8-bit μ processor, Memory, ROM	32-bit μ processor, Gate arrays	64-bit μ processor, PALs, FPGAs	
<i>Complexity Level (# of gates)</i>	100s	10,000s	1 million	100,000s to millions	
<i>Pervasive Components</i>	TTL 7400 series	Intel 8008, ROM	Intel 8086, Motorola 68000, Gate arrays, PALs	Pentium I, II, III, FPGAs, Complex PLDs	
<i>Dominant Trend</i>	Standard catalog of components	Larger, General-purpose components, e.g., Micro- processors and Random- access memories	Application-spe- cific integrated circuits	Field- programmable components	

Technology Metrics

- Gate delay
 - The time delay from an input change to an output change
 - $t(50\% \text{ output final value}) - t(50\% \text{ of input final value})$
- Degree of integration
 - The chip area and number of chip packages required to implement a given function in a technology
- Power dissipation
 - Power consumed as gates perform their logic functions
- Noise margin
 - The maximum voltage that can be added to or subtracted from the logic voltages carried on wires and still have the circuit interpret the voltage as the correct logic value
- Component cost

Technology Metrics (cont'd)



- Fan-out
 - The number of gate inputs to which a given gate output can be connected without exceeding electrical limitations
- Driving capability
 - The speed of communications between packaged components
- Configurability

Basic Logic Components

- Fixed Logic

■ Cell-based design

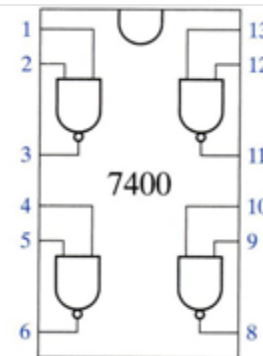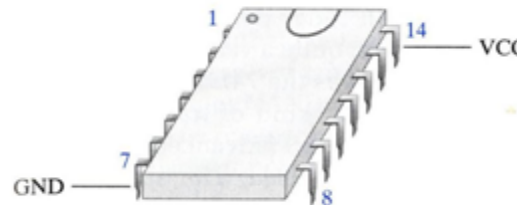- Designers pick and choose gates in a given standard cell library for logic functions they want to implement.
 - NAND, NOR, XOR, ADDER, MUX, ...
- SSI and MSI (Small and Medium Scale Integrated Circuit)
 - TTL: a family of packaged logic components
 - Example: TTL 7400





□ Standard cell library for modern ASIC

- provides the same kinds of logic functions as those TTL standard catalog contains.

Fixed Logic (cont'd)

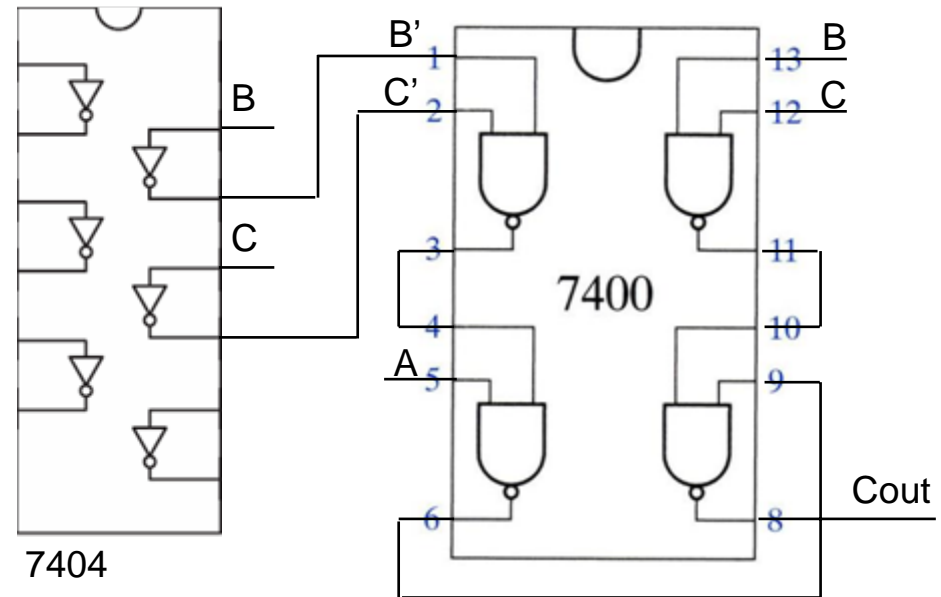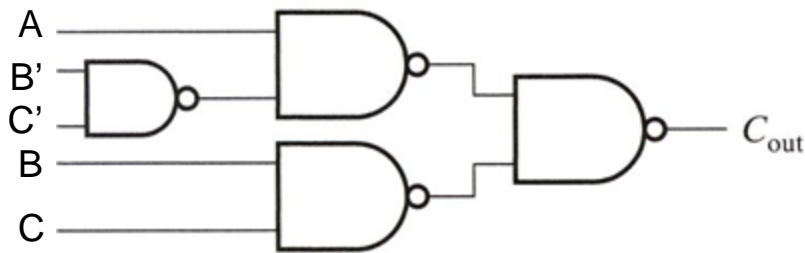- Combinational logic implementation
 - Pick logic packages and wire them
 - Make Package/Cell Counts minimal



Basic Logic Components (cont'd)

- Look-Up Tables

- Look-up table approach
 - Storing the output value of a function for each input combination in a table
 - Using the current input value as an index to look-up what the output should be
 - To change the function, simply change the values stored in the table, not change any wiring
 - Less sensitive to the complexity of the function

■ Example

- If the input $A=0$, $B=1$, and $C=0$, the corresponding index (address) of the table = 010 and the value of the entry = 0100.
- Thus, the output $F0=0$, $F1=1$, $F2=0$, $F3=0$


Index			Output			
A	B	C	F0	F1	F2	F3
0	0	0	0	0	1	0
0	0	1	1	1	1	0
0	1	0	0	1	0	0
0	1	1	0	0	0	1
1	0	0	1	0	1	1
1	0	1	1	0	0	0
1	1	0	0	0	0	1
1	1	1	0	1	0	0

**Storing the outputs
at each entry
in a table device**

Look-Up Tables (cont'd)

■ ROM (Read-Only Memory)


- an array of values intended to be read many times but only written once
- We can program the output of a truth table directly into a ROM
- Address: index of the array
 - Inputs are used to index a row of the array
- The value of the corresponding row are read out as the values of the outputs
- Each additional input bit doubles the size of the memory array
 - Good to implement a complicated function that is difficult to simplify using the standard methods or change often the function.
- Variants
 - Programmable ROM (PROM)
 - Erasable PROM (EPROM)
 - Electrically erasable PROM (EEPROM)

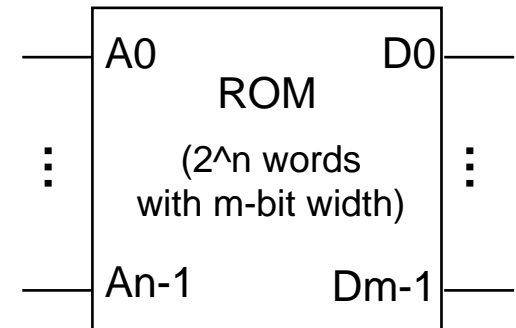

Look-Up Tables (cont'd)


■ Internal organization of a ROM

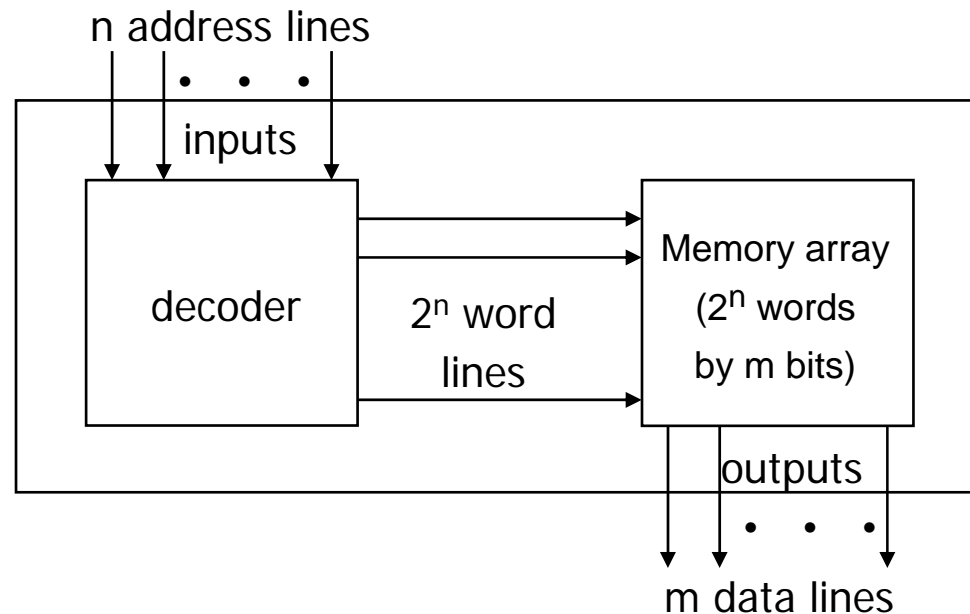- Each row of the array is called a word and is selected by the control inputs, which are called the address.
- The number of columns in the array is called the bit-width or word size.
- Similar to a PLA structure but with a fully decoded AND array
 - completely flexible OR array (unlike PAL)



Look-Up Tables (cont'd)

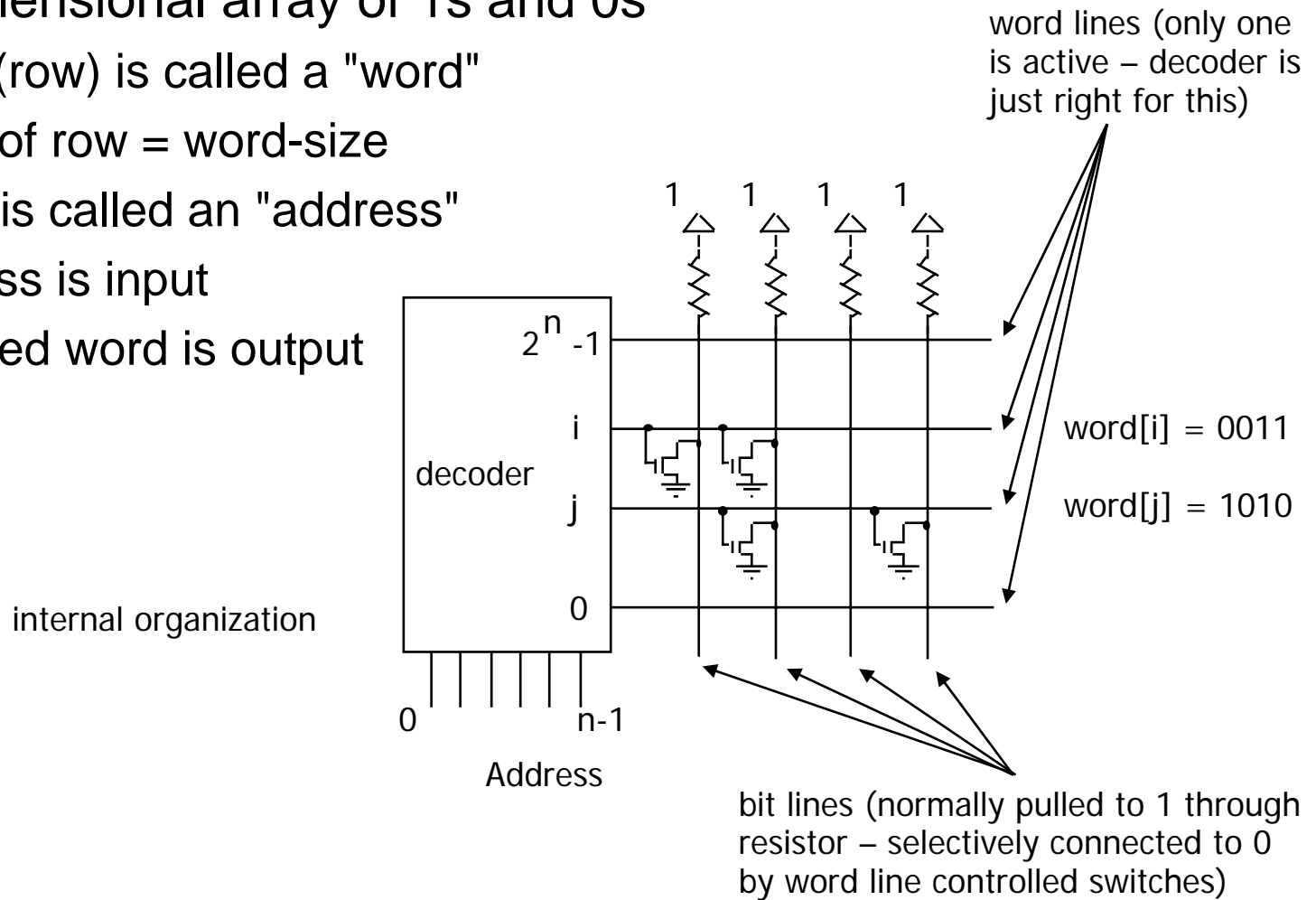- Two dimensional array of 1s and 0s
 - entry (row) is called a "word"
 - width of row = word-size
 - index is called an "address"
 - address is input
 - selected word is output



Look-Up Tables (cont'd)

- Combinational logic implementation (two-level canonical form) using a ROM

$$F0 = A' B' C + A B' C' + A B' C$$


$$F1 = A' B' C + A' B C' + A B C$$

$$F2 = A' B' C' + A' B' C + A B' C'$$

$$F3 = A' B C + A B' C' + A B C'$$

A	B	C	F0	F1	F2	F3
0	0	0	0	0	1	0
0	0	1	1	1	1	0
0	1	0	0	1	0	0
0	1	1	0	0	0	1
1	0	0	1	0	1	1
1	0	1	1	0	0	0
1	1	0	0	0	0	1
1	1	1	0	1	0	0

truth table

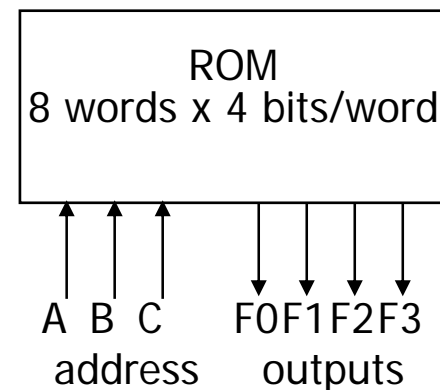

block diagram


Basic Logic Components (cont'd)

- Multiplexer/Selector

■ Multiplexer/Selector (MUX)

- Sets its single output to the same value as one of its inputs under the direction of its control inputs.
- 2^n data inputs, n control inputs (called "selects"), 1 output
- used to connect 2^n input points to a single output point
- control signal pattern forms binary index of input connected to output

■ Functional description

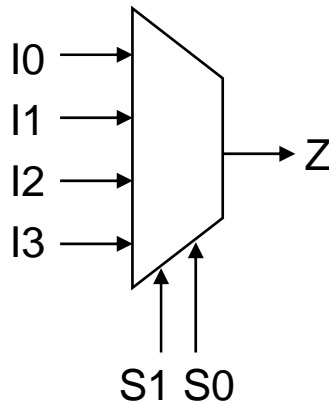

Input : $I_j = \{0,1\}$ where $j = 0, 1, \dots, 2^n - 1$

$S_i = \{0,1\}$ where $i = 0, 1, \dots, n-1$

Output : $Z = \{0,1\}$

Function : $Z = I_j$ where $j = S = \sum_{i=0}^{n-1} S_i 2^i$

Multiplexer/Selector (cont'd)

- Truth table of MUX
 - 2:1 MUX

$$Z = A' I_0 + A I_1$$

A	Z
0	I_0
1	I_1

functional form
logical form

I_1	I_0	A	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

two alternative forms
for a 2:1 Mux truth table

Multiplexer/Selector (cont'd)

- Boolean equation of MUX

- 2:1 mux: $Z = A'I_0 + AI_1$




- 4:1 mux: $Z = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3$

- 8:1 mux: $Z = A'B'C'I_0 + A'B'CI_1 + A'BC'I_2 + A'BCI_3 + AB'C'I_4 + AB'CI_5 + ABC'I_6 + ABCI_7$

- In general:

$$Z = \sum_{k=0}^{2^n-1} m_k I_k$$

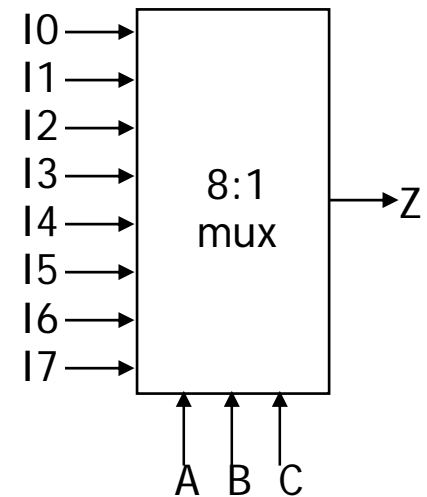 
 
- in minterm shorthand form for a $2^n:1$ Mux





Multiplexer/Selector (cont'd)

■ Gate Level Implementation of MUX

□ 2:1 mux

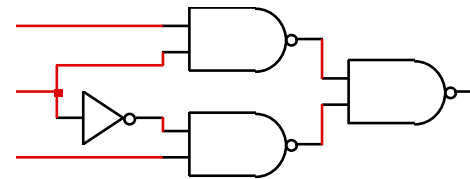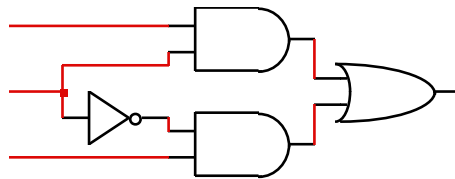



□ 4:1 mux

  

Multiplexer/Selector (cont'd)


- Mux and Demux

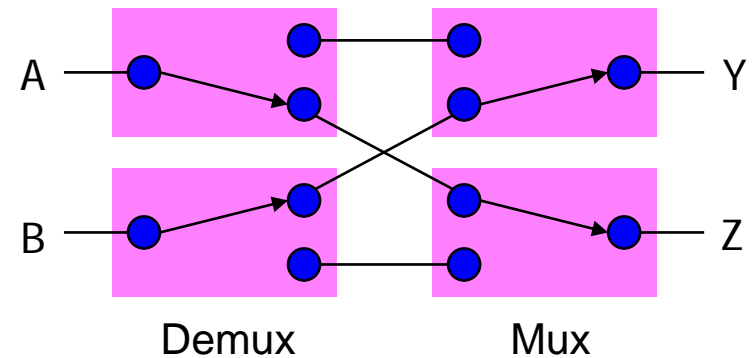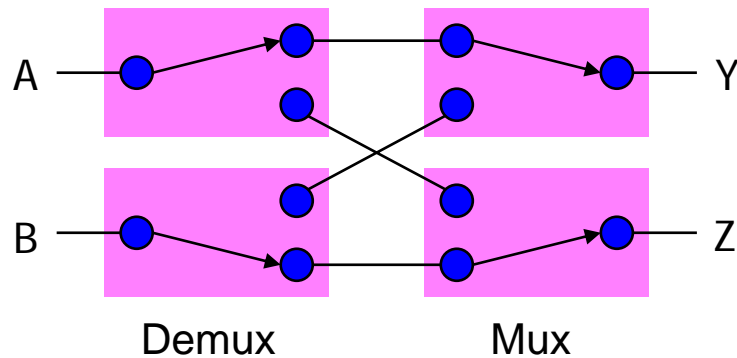- Switch implementation of multiplexers and demultiplexers
 - can be composed to make arbitrary size switching networks
 - used to implement multiple-source/multiple-destination interconnections



Mux and Demux (cont'd)

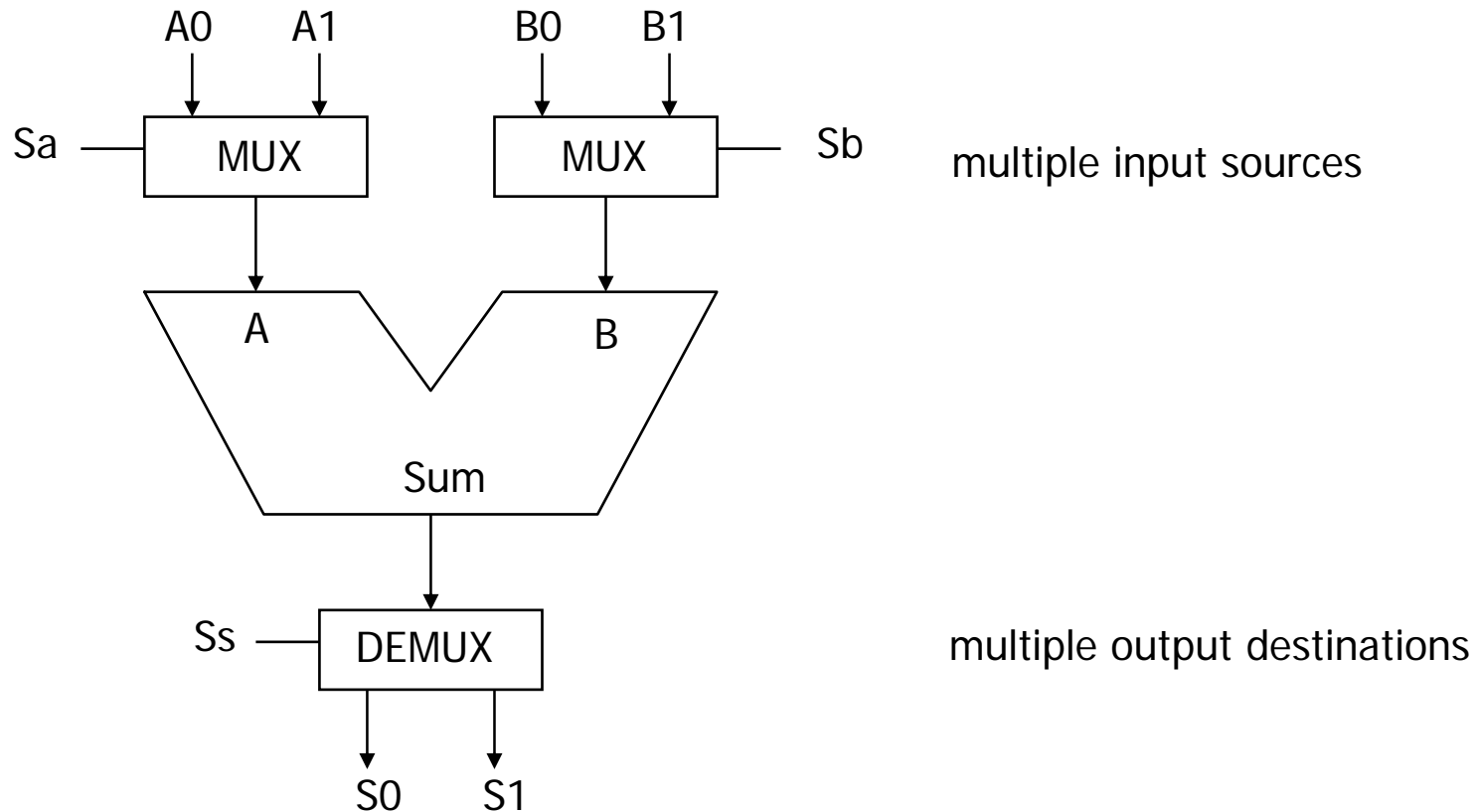
- Uses of multiplexers/demultiplexers in multi-point connections



Multiplexer/Selector (cont'd)


- Cascading Multiplexers

 - Large multiplexers can be made by cascading smaller ones



control signals B and C simultaneously choose one of I0, I1, I2, I3 and one of I4, I5, I6, I7

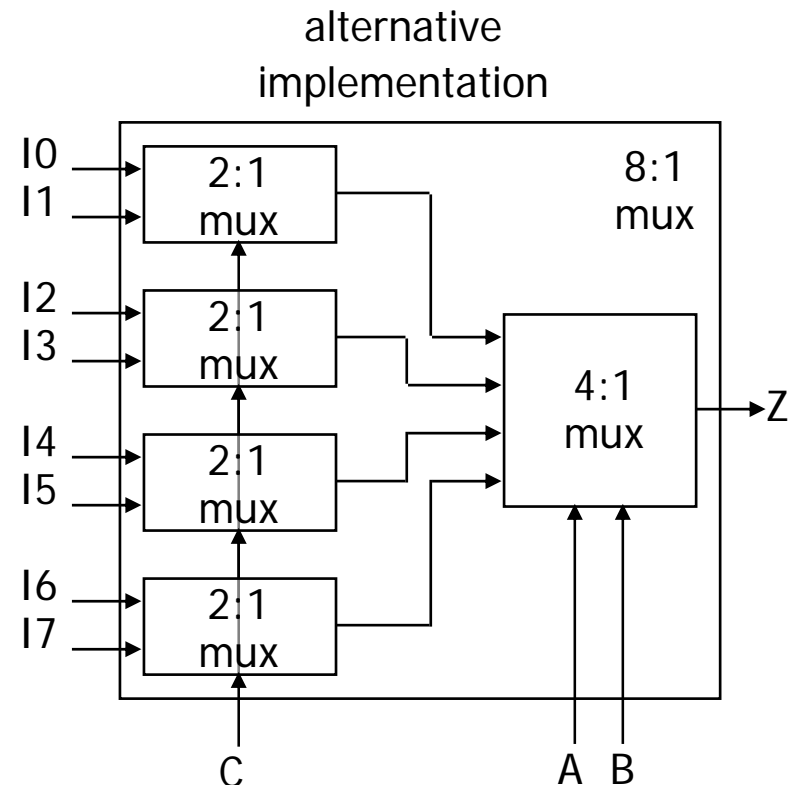control signal A chooses which of the upper or lower mux's output to gate to Z




Multiplexer/Selector (cont'd)

- Multiplexers as a Logic Building Block

- A $2^n:1$ multiplexer can implement any function of n variables
 - with the variables used as control inputs and
 - the data inputs tied to 0 or 1
 - in essence, a lookup table

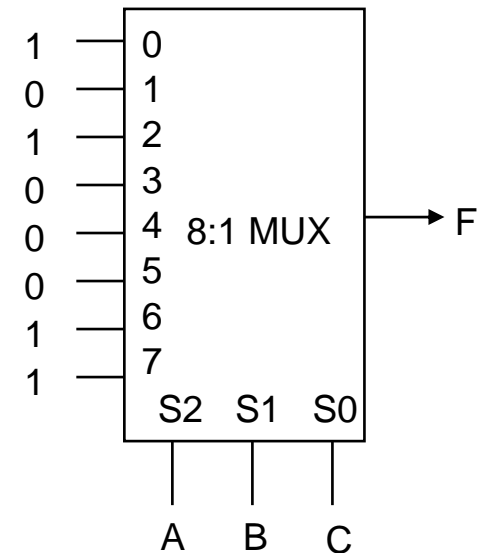- Example:


- $$\begin{aligned} F(A,B,C) &= m_0 + m_2 + m_6 + m_7 \\ &= A'B'C' + A'BC' + ABC' + ABC \\ &= A'B'C'(1) + A'B'C(0) \\ &\quad + A'BC'(1) + A'BC(0) \\ &\quad + AB'C'(0) + AB'C(0) \\ &\quad + ABC'(1) + ABC(1) \end{aligned}$$




$$F = A'B'C'I_0 + A'B'CI_1 + A'BC'I_2 + A'BCI_3 + AB'C'I_4 + AB'CI_5 + ABC'I_6 + ABCI_7$$

Multiplexers as a Logic Building Block (cont'd)

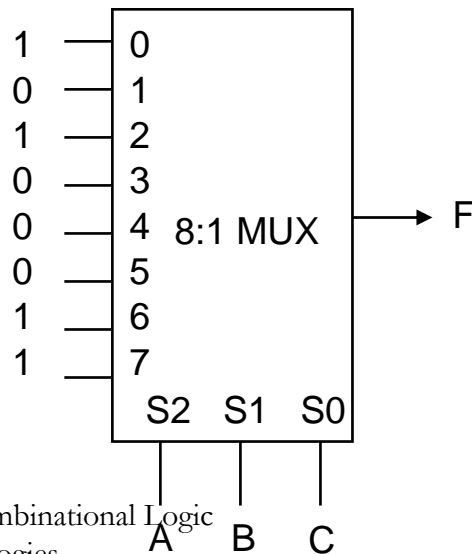- A $2^{n-1}:1$ multiplexer can implement any function of n variables
 - with $n-1$ variables used as control inputs and
 - the data inputs tied to the last variable or its complement
- Example:
 - $F(A,B,C) = m_0 + m_2 + m_6 + m_7$
 $= A'B'C' + A'BC' + ABC' + ABC$
 $= A'B'(C') + A'B(C') + AB'(0) + AB(1)$




A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

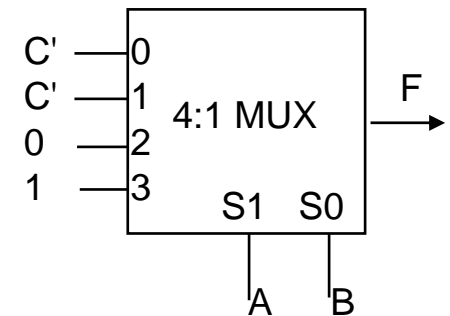

Multiplexers as a Logic Building Block (cont'd)


Generalization

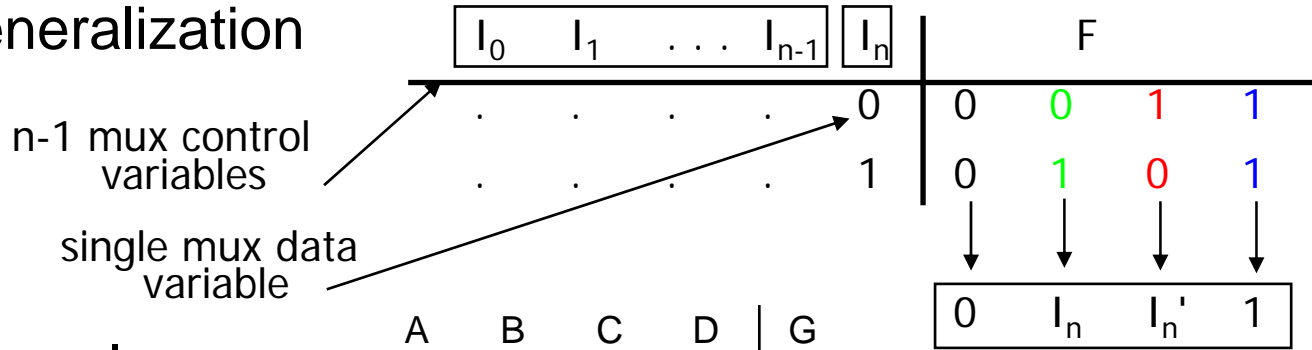

Example: $G(A,B,C,D)$ can be realized by an 8:1 MUX

A	B	C	D	G
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

choose A,B,C as control variables

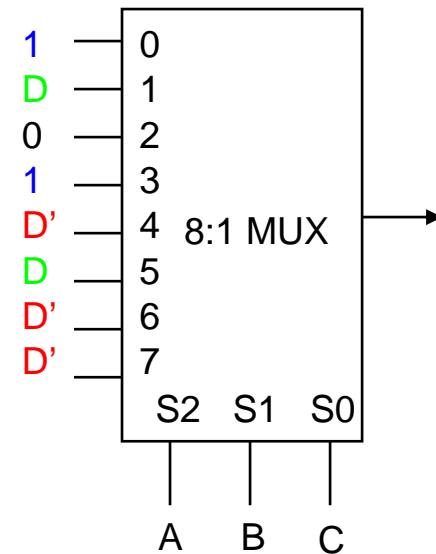


Basic Logic Components (cont'd)

- Demultiplexer/Decoder

- Decoders/demultiplexers

- single data input, n control inputs, 2^n outputs
- control inputs (called “selects” (S)) represent binary index of output to which the input is connected
- data input usually called “enable” (G)

- Functional description

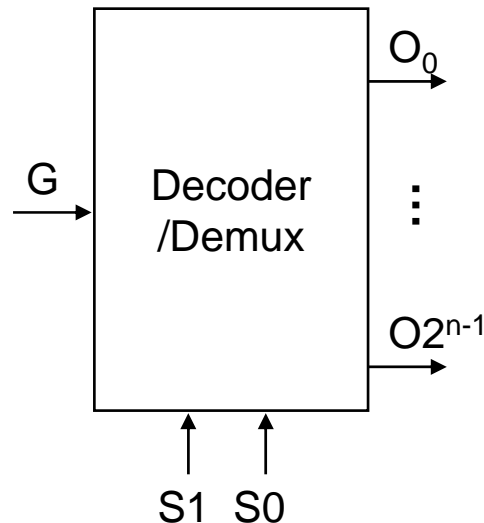

Input: $G = \{0,1\}$

$S_i = \{0,1\}$ where $i = 0, 1, \dots, n-1$

Output: $O_j = \{0,1\}$ where $j = 0, 1, \dots, 2^n - 1$

Function: $O_j = \begin{cases} 1 & \text{where } j = S = \sum_{i=0}^{n-1} S_i 2^i \\ 0 & \text{otherwise} \end{cases}$

Demultiplexer/Decoder (cont'd)

- Boolean equation of Decoder/Demux

- General form for n-selects:

- m_j refers to minterm

$$O_j = G \cdot m_j = \begin{cases} G & \text{where } j = S = \sum_{i=0}^{i=n-1} S_i 2^i \\ 0 & \text{otherwise} \end{cases}$$

- $n = 1$

1:2 Decoder:

$$O0 = G \cdot S'$$

$$O1 = G \cdot S$$

- $n = 2$

2:4 Decoder:

$$O0 = G \cdot S1' \cdot S0'$$

$$O1 = G \cdot S1' \cdot S0$$

$$O2 = G \cdot S1 \cdot S0'$$

$$O3 = G \cdot S1 \cdot S0$$

- $n = 3$

3:8 Decoder:

$$O0 = G \cdot S2' \cdot S1' \cdot S0'$$

$$O1 = G \cdot S2' \cdot S1' \cdot S0$$

$$O2 = G \cdot S2' \cdot S1 \cdot S0'$$

$$O3 = G \cdot S2' \cdot S1 \cdot S0$$

$$O4 = G \cdot S2 \cdot S1' \cdot S0'$$

$$O5 = G \cdot S2 \cdot S1' \cdot S0$$

$$O6 = G \cdot S2 \cdot S1 \cdot S0'$$


$$O7 = G \cdot S2 \cdot S1 \cdot S0$$

Demultiplexer/Decoder (cont'd)


- Gate level implementation of Demux

- 1:2 decoders



active-high enable

 

active-low enable

 


- 2:4 decoders

  

Demultiplexer/Decoder (cont'd)

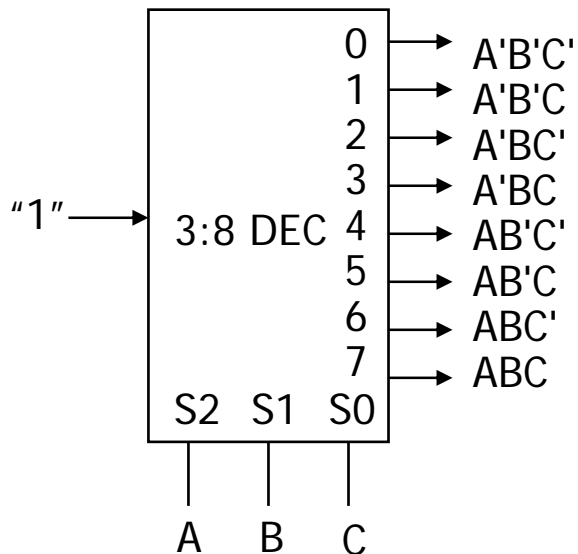- Demux as a general-purpose building block
 - A $n:2^n$ decoder can implement any function of n variables
 - with the variables used as control inputs
 - the enable inputs tied to 1 and
 - the appropriate minterms summed to form the function




demultiplexer generates appropriate minterm based on control signals (it "decodes" control signals)

Demultiplexer/Decoder (cont'd)

■ Demux as a general-purpose building block

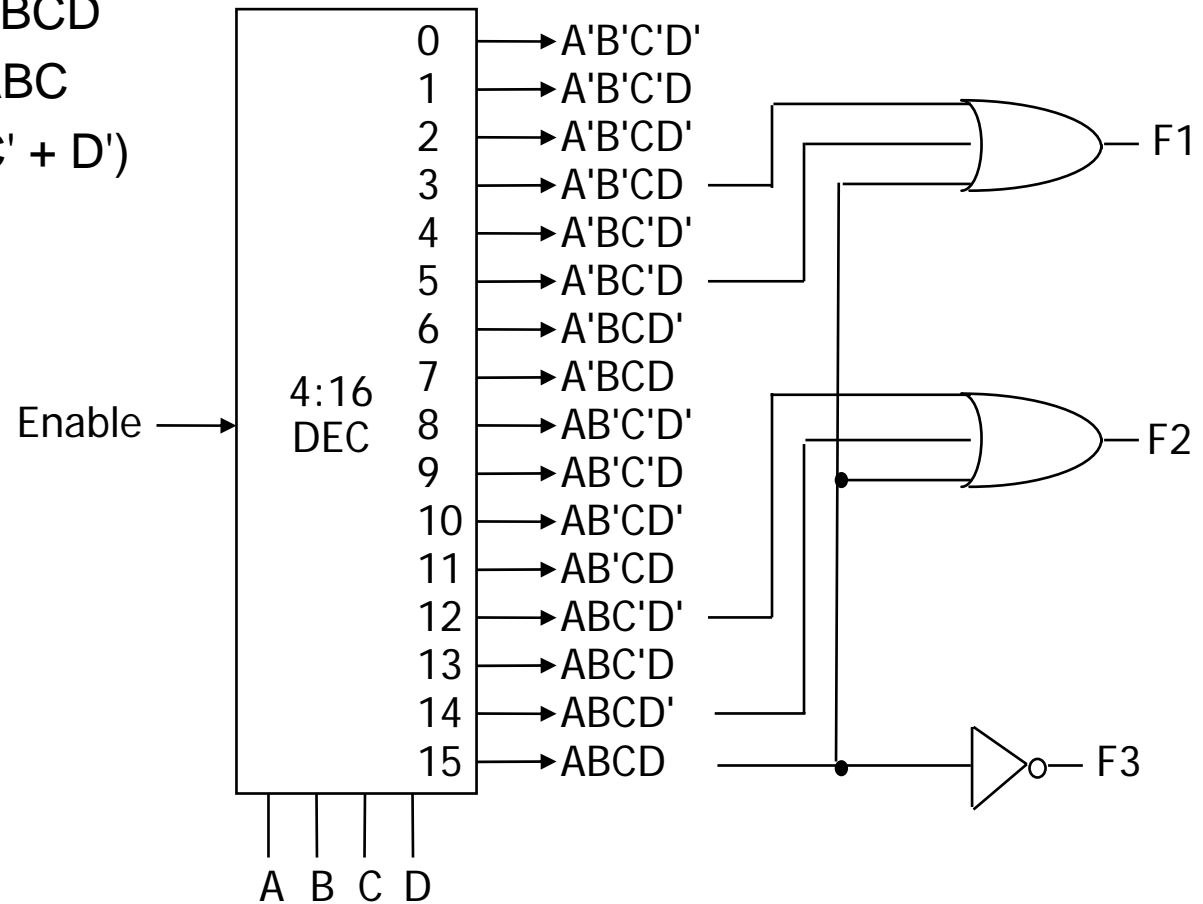- $F1 = A'BC'D + A'B'CD + ABCD$
- $F2 = ABC'D' + ABC$
- $F3 = (A' + B' + C' + D')$




Demultiplexer/Decoder (cont'd)

■ Cascading decoders

□ 5:32 decoder


- 1x2:4 decoder
- 4x3:8 decoders

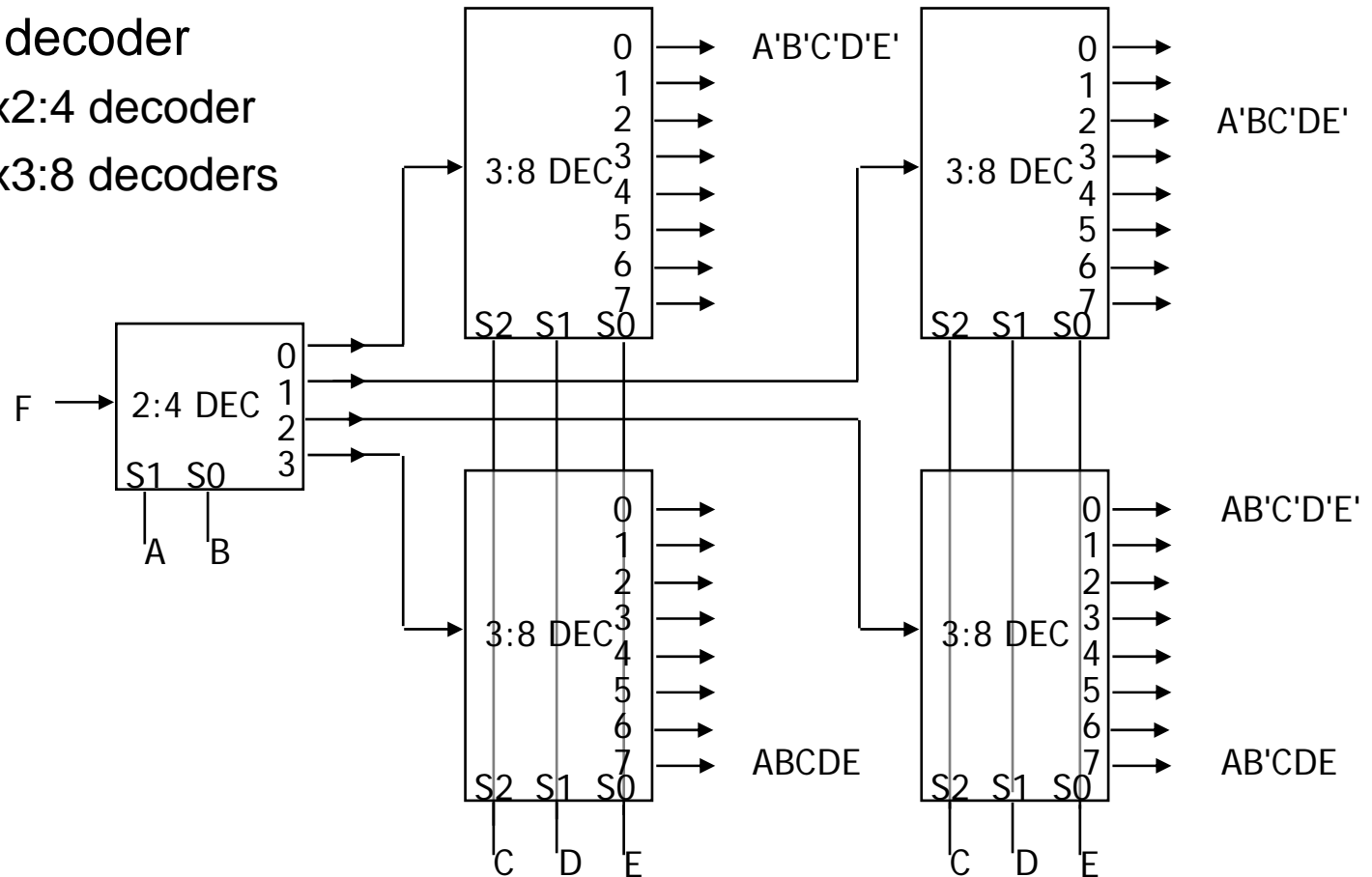

Basic Logic Components (cont'd)

- Programmable Logic Array

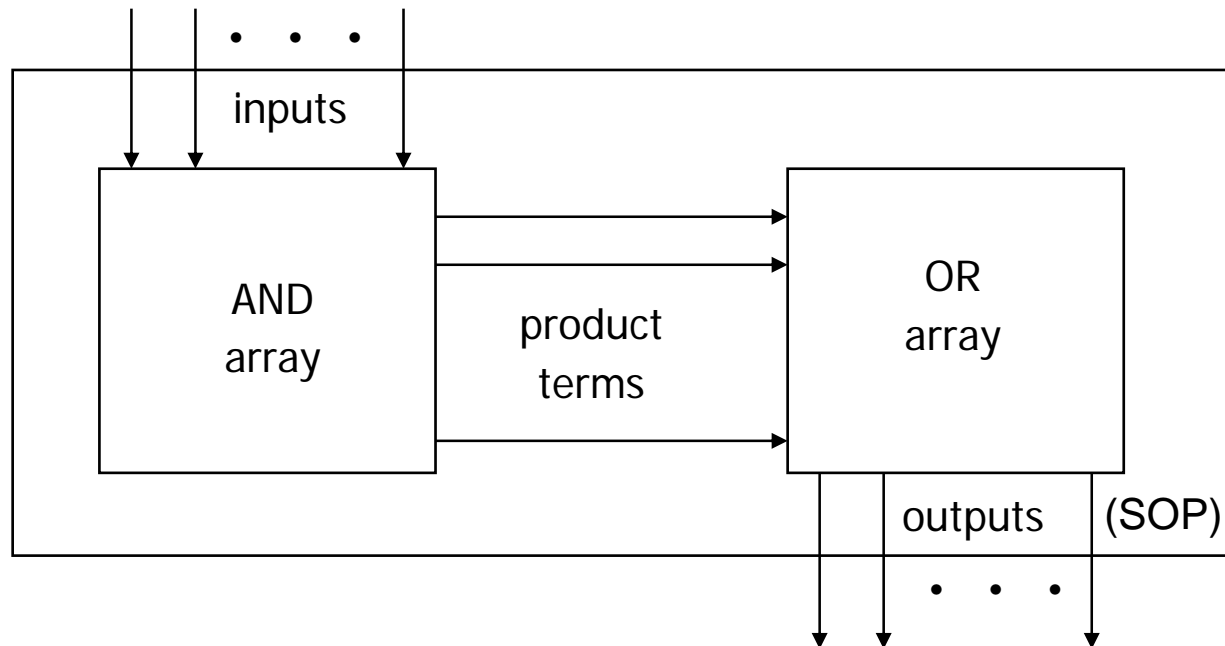- Pre-fabricated building block of many AND/OR gates
 - actually NOR or NAND
 - "personalized" by making/breaking connections among the gates
 - programmable array block diagram for sum of products form



Programmable Logic Array (cont'd)

- Enabling Concept

- Shared product terms among outputs

example:

$$F0 = A + B' C'$$

$$F1 = A C' + A B$$

$$F2 = B' C' + A B$$

$$F3 = B' C + A$$

personality matrix

product term	inputs			outputs			
	A	B	C	F0	F1	F2	F3
AB	1	1	-	0	1	1	0
B'C	-	0	1	0	0	0	1
AC'	1	-	0	0	1	0	0
B'C'	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

input side:

1 = uncomplemented in term
 0 = complemented in term
 - = does not participate

output side:


1 = term connected to output
 0 = no connection to output

reuse of terms

Programmable Logic Array (cont'd)

- Before Programming

 
- All possible connections are available before "programming"
 - in reality, all AND and OR gates are NANDs



Programmable Logic Array (cont'd)

- After Programming

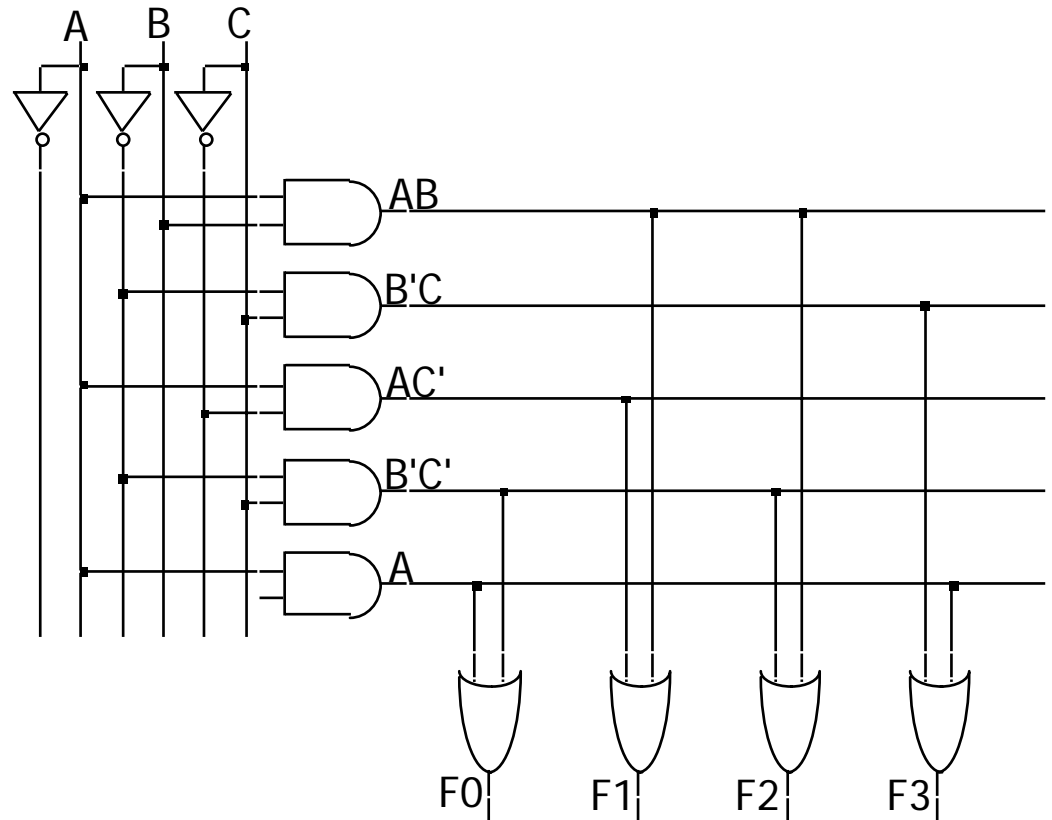
- Unwanted connections are "blown"
 - fuse (normally connected, break unwanted ones)
 - anti-fuse (normally disconnected, make wanted connections)
 - memory cell
 - 0 or 1 can be stored indicating whether there is to be a connection or not.



Programmable Logic Array (cont'd)

- Alternate Representation for High Fan-in Structures

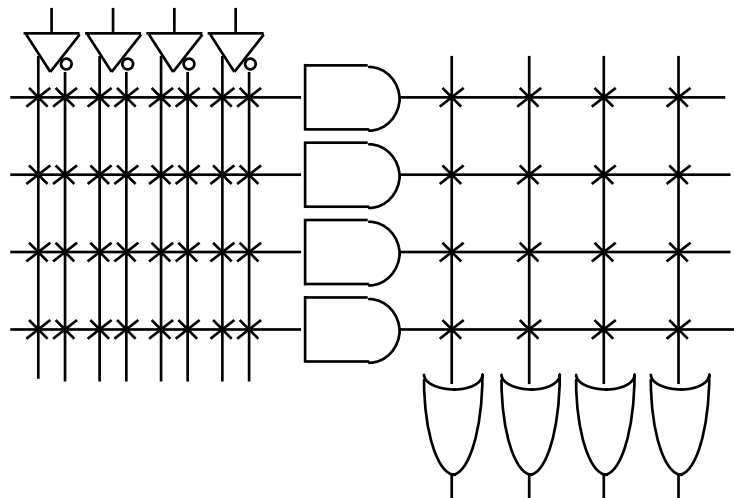
- Short-hand notation so we don't have to draw all the wires
 - × signifies a connection is present and perpendicular signal is an input to gate



notation for implementing

$$F0 = A B + A' B'$$

$$F1 = C D' + C' D$$

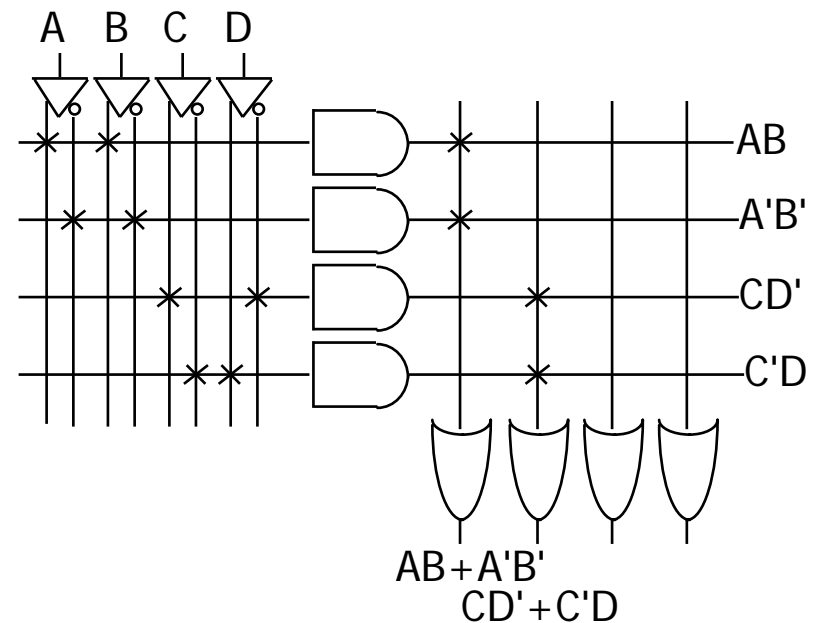


Programmable Logic Array (cont'd)

- Example

■ Multiple functions of A, B, C

- $F1 = A B C$
- $F2 = A + B + C$
- $F3 = A' B' C'$
- $F4 = A' + B' + C'$
- $F5 = A \text{ xor } B \text{ xor } C$
- $F6 = A \text{ xnor } B \text{ xnor } C$

A	B	C	F1	F2	F3	F4	F5	F6
0	0	0	0	0	1	1	0	0
0	0	1	0	1	0	1	1	1
0	1	0	0	1	0	1	1	1
0	1	1	0	1	0	1	0	0
1	0	0	0	1	0	1	1	1
1	0	1	0	1	0	1	0	0
1	1	0	0	1	0	1	0	0
1	1	1	1	1	0	0	1	1

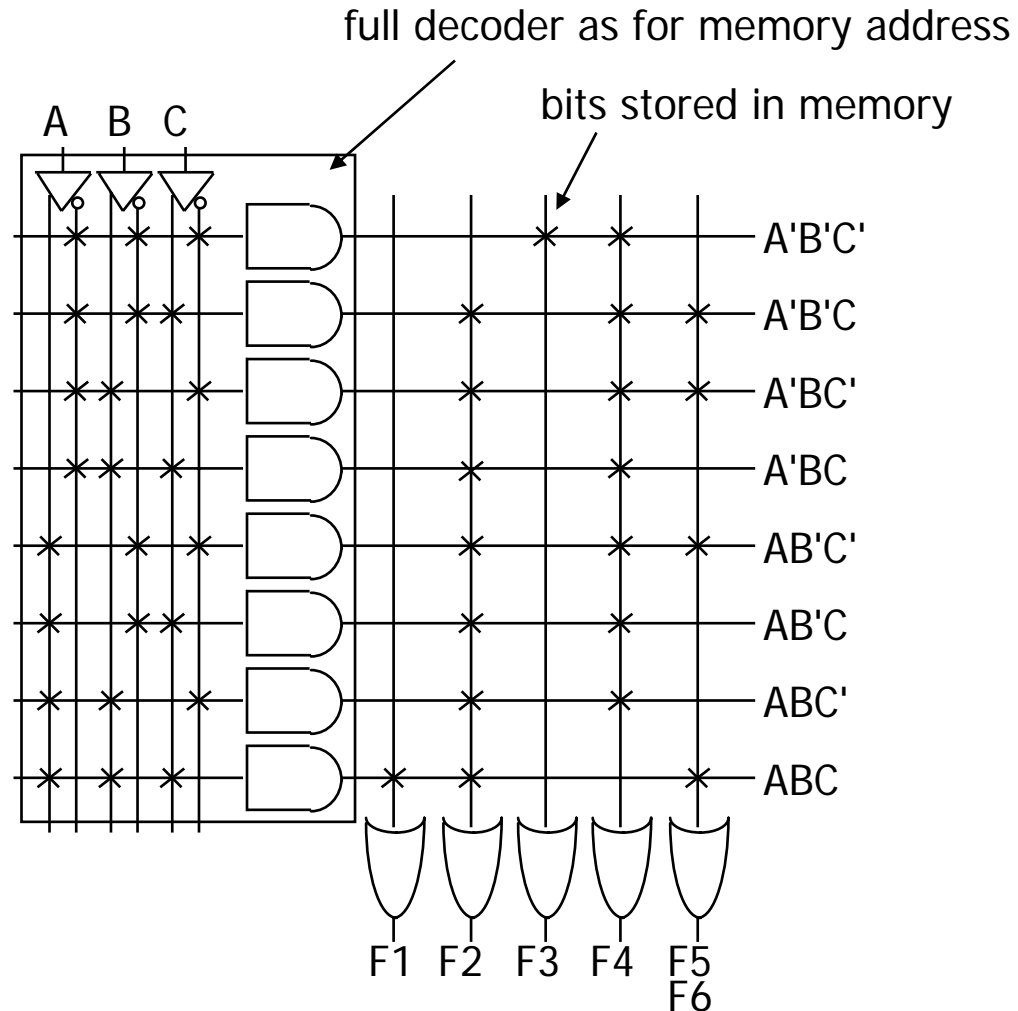


Basic Logic Components (cont'd)

- PALs and PLAs

- Programmable logic array (PLA)
 - what we've seen so far
 - unconstrained fully-general AND and OR arrays
- Programmable array logic (PAL)
 - constrained topology of the OR array
 - innovation by Monolithic Memories
 - faster and smaller OR plane

 a given column of the OR array
has access to only a subset of
the possible product terms



PALs and PLAs (cont'd)

- PALs and PLAs: Design Example

■ BCD to Gray code converter

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	-	-	-	-	-
1	1	-	-	-	-	-	-





minimized functions:

$$W = A + BD + BC$$

$$X = BC'$$


$$Y = B + C$$

$$Z = A'B'C'D + BCD + AD' + B'CD'$$

    

PALs and PLAs: Design Example (cont'd)

Code converter: programmed PLA

 

minimized functions:

$$W = A + BD + BC$$

$$X = B C'$$

$$Y = B + C$$

$$Z = A'B'C'D + BCD + AD' + B'CD'$$


not a particularly good
candidate for PLA
implementation since no terms
are shared among outputs

however, much more compact
and regular implementation
when compared with discrete
AND and OR gates

PALs and PLAs: Design Example (cont'd)



- Code converter: programmed PAL

4 product terms
per each OR gate

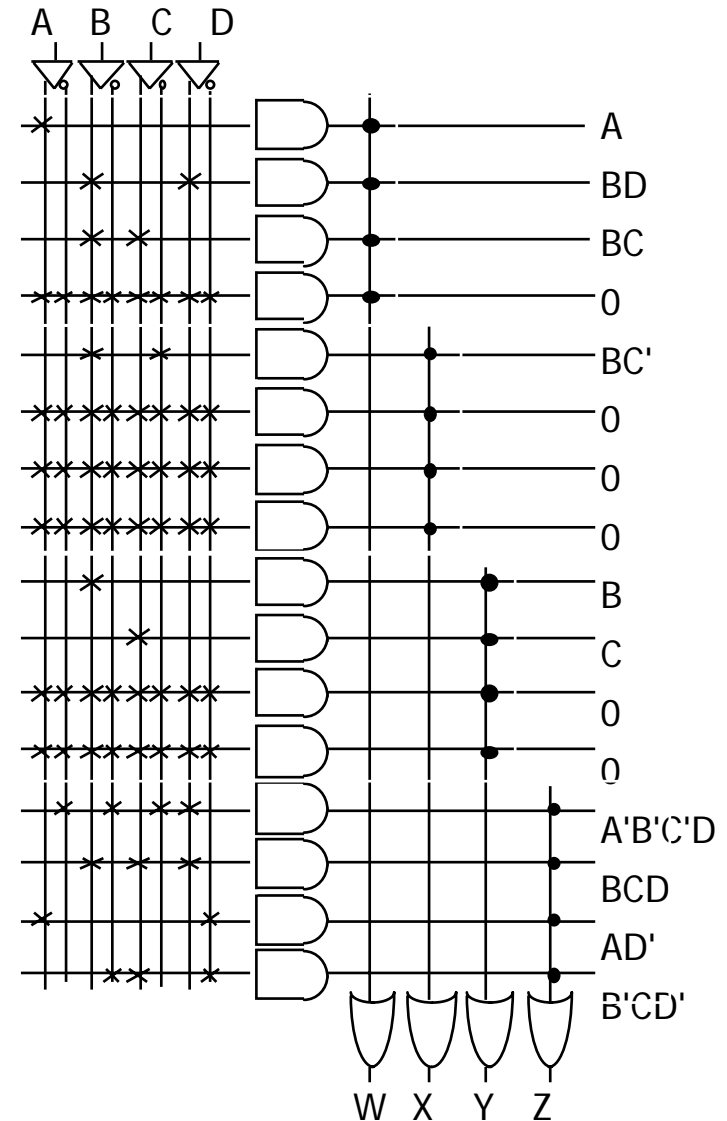

PALs and PLAs: Design Example (cont'd)

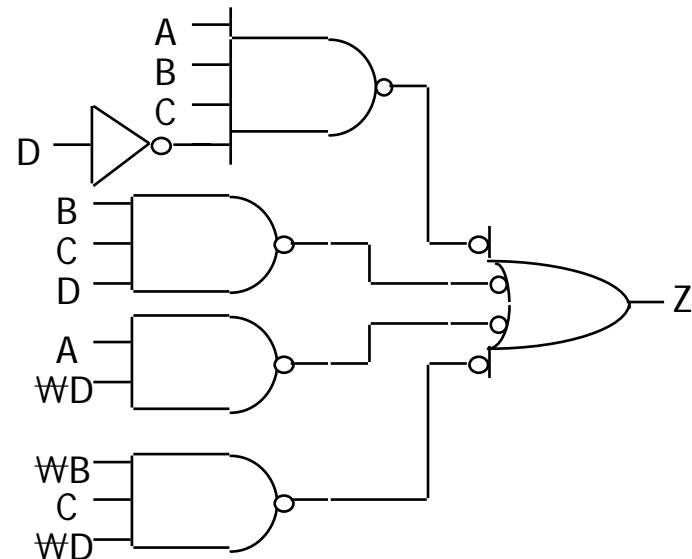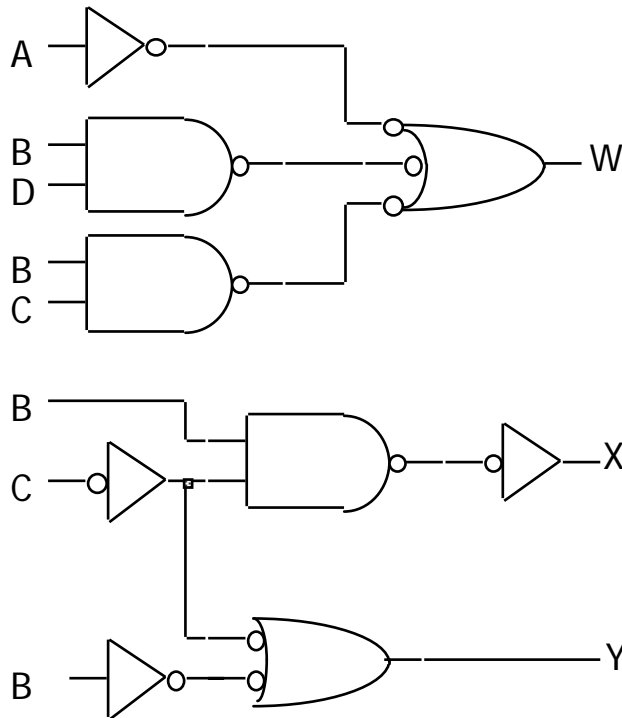- Code converter: NAND gate implementation
 - loss of regularity, harder to understand
 - harder to make changes



PALs and PLAs (cont'd)

- PALs and PLAs: Another Design Example

■ Magnitude comparator

Input: AB, CD where $A, B, C, D = \{0,1\}$

Output: $EQ, NE, LT, GT = \{0,1\}$

Function: $EQ = \begin{cases} 1 & \text{when } AB = CD \\ 0 & \text{otherwise} \end{cases}$



$NE = \begin{cases} 1 & \text{when } AB \neq CD \\ 0 & \text{otherwise} \end{cases}$

$LT = \begin{cases} 1 & \text{when } AB < CD \\ 0 & \text{otherwise} \end{cases}$

$GT = \begin{cases} 1 & \text{when } AB > CD \\ 0 & \text{otherwise} \end{cases}$

A	B	C	D	EQ	NE	LT	GT
0	0	0	0	1	0	0	0
0	0	0	1	0	1	1	0
0	0	1	0	0	1	1	0
0	0	1	1	0	1	1	0
0	1	0	0	0	1	0	1
0	1	0	1	1	0	0	0
0	1	1	0	0	1	1	0
0	1	1	1	0	1	1	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	0	1
1	0	1	0	1	0	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	1	0	1
1	1	0	1	0	1	0	1
1	1	1	0	0	1	0	1
1	1	1	1	1	0	0	0

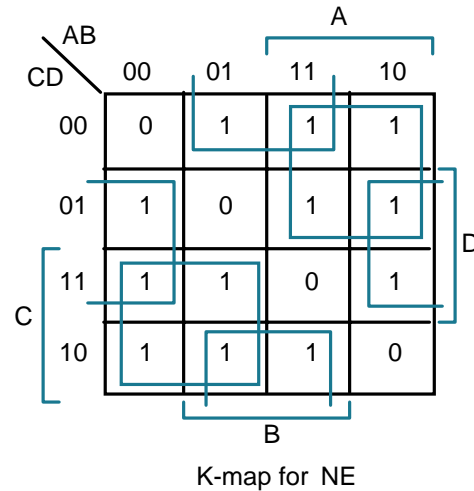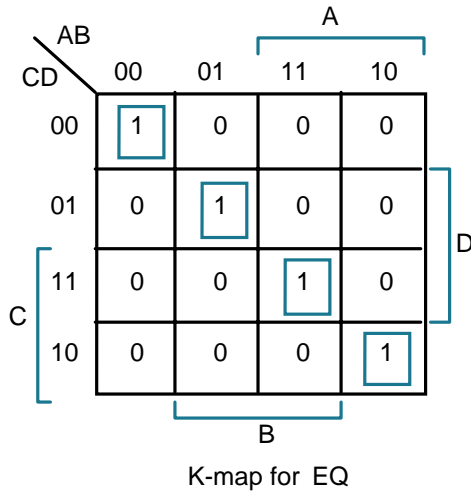PALs and PLAs: Another Design Example (cont'd)





minimized functions:

$$EQ = A'B'C'D' + A'BC'D + ABCD + AB'CD'$$


$$NE = AC' + A'C + B'D + BD'$$

$$LT = A'C + A'B'D + B'CD$$

$$GT = AC' + ABC + BC'D'$$

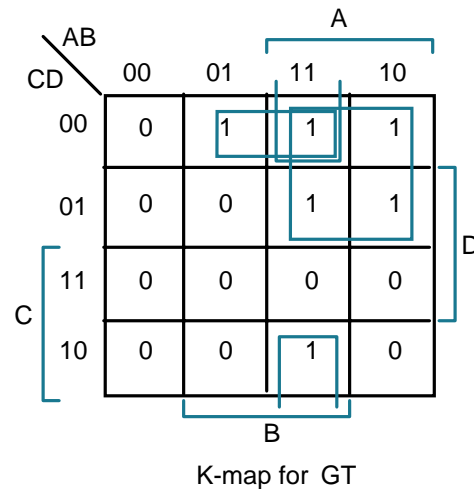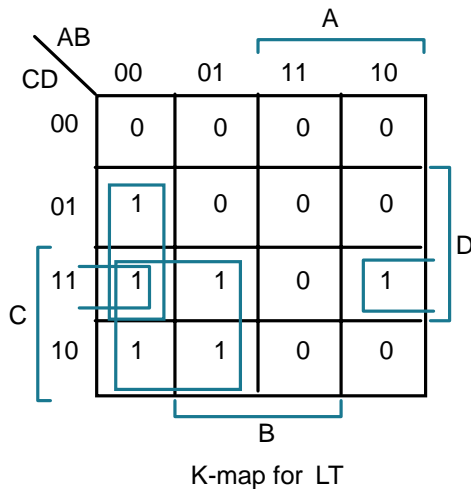

 PALs and PLAs: Another Design Example (cont'd)



Basic Logic Components (cont'd)

- Multiplexer-Based FPGA

- Actel logic module



- Example using a logic module

 - AND

- $Y = (S_0 + S_1)'(S'_{OA}D_0 + S_{OA}D_1) + (S_0 + S_1)(S'_{OB}D_2 + S_{OB}D_3)$

- $Y = (0 + 0)'(B'0 + BA) + (0 + 0)(S'_{OB}D_2 + S_{OB}D_3)$



- $Y = AB$

 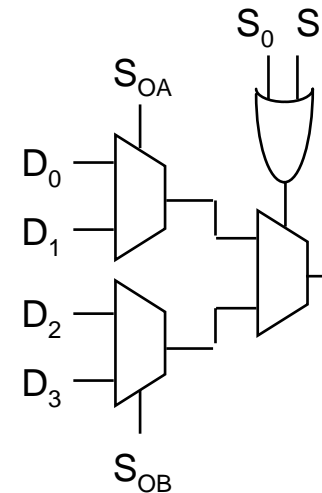

Basic Logic Components (cont'd)

- Look-Up Table Based FPGA

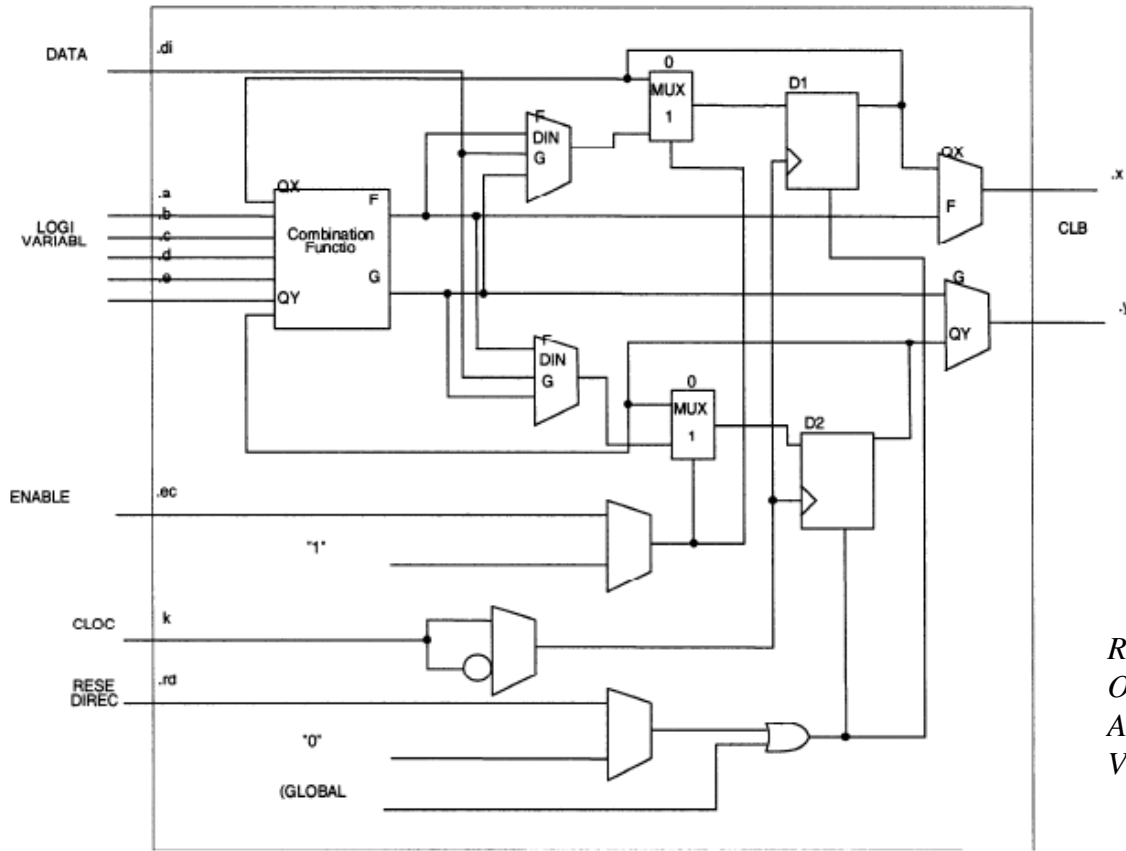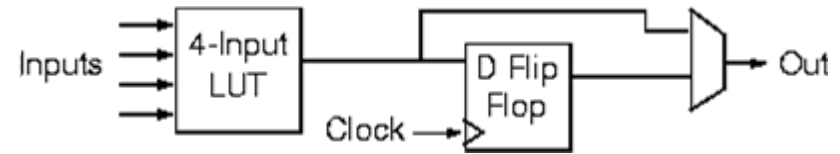- Simplified basic building block of FPGA
- Xilinx Configurable Logic Block (CLB)



*Ref.: IEEE TRANSACTIONS
ON INSTRUMENTATION
AND MEASUREMENT,
VOL. 52, NO. 5, OCTOBER 2003*

Two-Level and Multilevel Logic

- Regular Logic Structures for Two-Level Logic

- ROM – full AND plane, general OR plane
 - cheap (high-volume component)
 - can implement any function of n inputs
 - medium speed
- PAL – programmable AND plane, fixed OR plane
 - intermediate cost
 - can implement functions limited by number of terms
 - high speed (only one programmable plane that is much smaller than ROM's decoder)
- PLA – programmable AND and OR planes
 - most expensive (most complex in design, need more sophisticated tools)
 - can implement any function up to a product term limit
 - slow (two programmable planes)

Regular Logic Structures for Two-Level Logic (cont'd)

- ROM vs. PLA

- ROM approach advantageous when
 - design time is short (no need to minimize output functions)
 - most input combinations are needed (e.g., code converters)
 - little sharing of product terms among output functions
- ROM problems
 - size doubles for each additional input
 - can't exploit don't cares
- PLA approach advantageous when
 - design tools are available for multi-output minimization
 - there are relatively few unique minterm combinations
 - many minterms are shared among the output functions
- PAL problems
 - constrained fan-ins on OR plane

Two-Level and Multilevel Logic (cont'd)

- Regular Logic Structures for Multilevel Logic

- Difficult to devise a regular structure for arbitrary connections between a large set of different types of gates
 - efficiency/speed concerns for such a structure
 - FPGA: just such programmable multi-level structures
 - programmable multiplexers for wiring
 - lookup tables for logic functions (programming fills in the table)
 - multi-purpose cells (utilization is the big issue)

Regular Logic Structures for Multilevel Logic (cont'd)

■ Using multiple levels of PALs/PLAs/ROMs


- output intermediate result
- make it an input to be used in further logic
- Example: Full Adder

■ Boolean equations

- $\text{Sum} = A'B'C_{in} + A'BC_{in}' + AB'C_{in}' + ABC_{in}$
- $C_{out} = AB + BC_{in} + AC_{in}$

■ Boolean equations for feedback PAL implementation

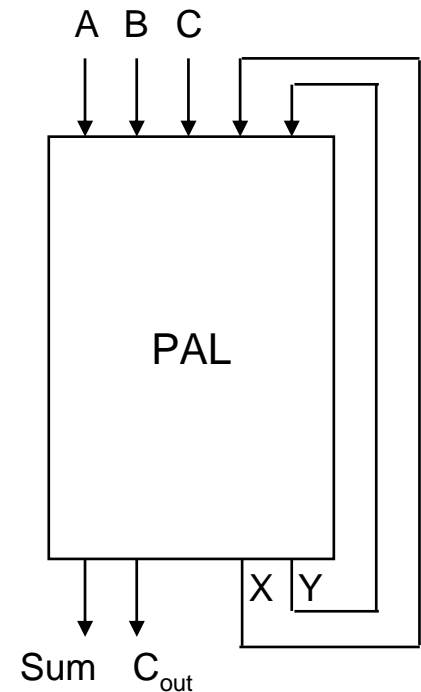
- $X = AB' + A'B$, $Y = AB$
- $\text{Sum} = XC_{in}' + X'C_{in}$
- $C_{out} = XC_{in} + Y$





Two-level and Multilevel Logic (cont'd)

- 7-Segment Display Decoder

 - Understanding the problem:
 - input is a 4 bit BCD digit
 - output is the control signals for the display
 - 4 inputs A, B, C, D
 - 7 outputs C0 ~ C6



7-segment display

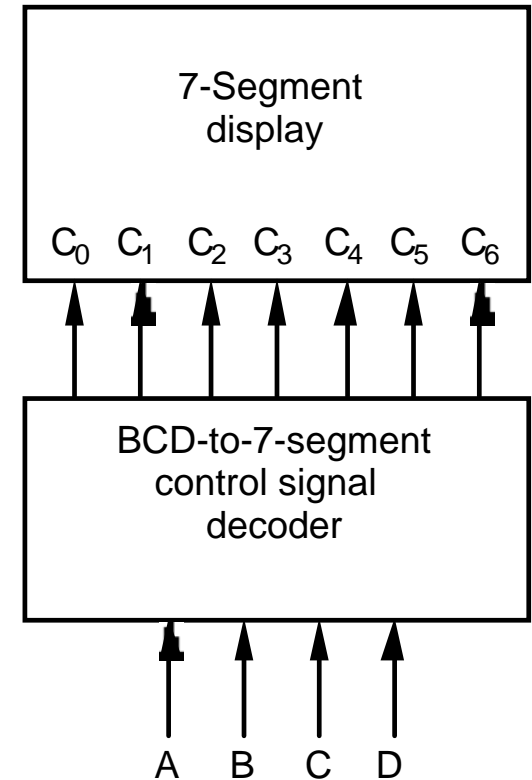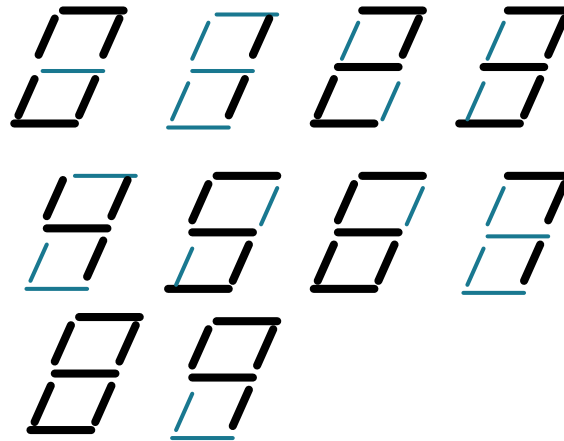

Block Diagram


7-Segment Display Decoder (cont'd)

- Truth table


ABCD	C0	C1	C2	C3	C4	C5	C6
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	0	0	1	1
101x	x	x	x	x	x	x	x
11xx	x	x	x	x	x	x	x

- Formulate the problem in terms of a truth table
- Choose implementation target:
 - if ROM, we are done
 - don't cares imply PAL/PLA may be attractive
- Follow implementation procedure:
 - hand reduced K-maps
 - espresso


7-Segment Display Decoder (cont'd)

 


K-map for C₀

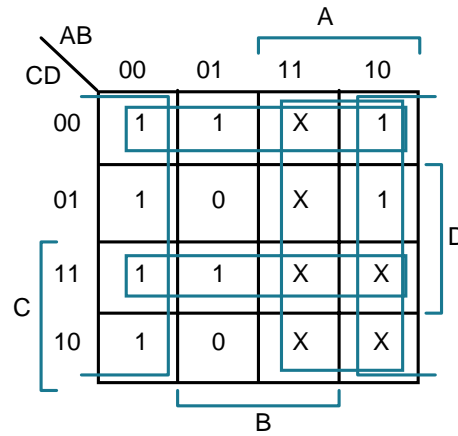


K-map for C₁

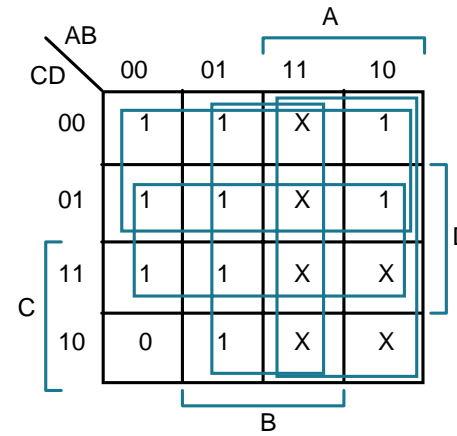


K-map for C₂

 


K-map for C₃

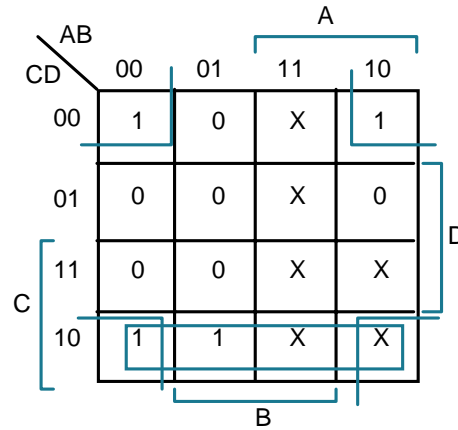

K-map for C₄

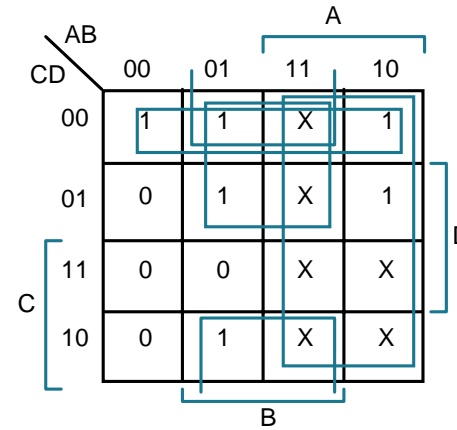

K-map for C₅

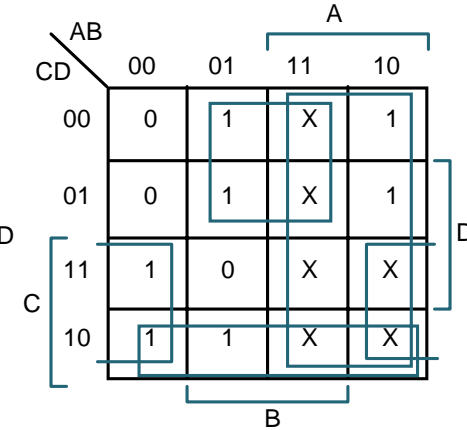

K-map for C₆

$$C_0 = A + B D + C + B' D'$$

$$C_1 = C' D' + C D + B'$$

$$C_2 = B + C' + D$$

$$C_3 = B' D' + C D' + B C' D + B' C$$

$$C_4 = B' D' + C D'$$

$$C_5 = A + C' D' + B D' + B C'$$


$$C_6 = A + C D' + B C' + B' C$$

14 Unique Product Terms

7-Segment Display Decoder (cont'd)

16H8PAL
*(10 external inputs,
 6 feedback inputs
 8 outputs)*

**Can Implement
 the function**

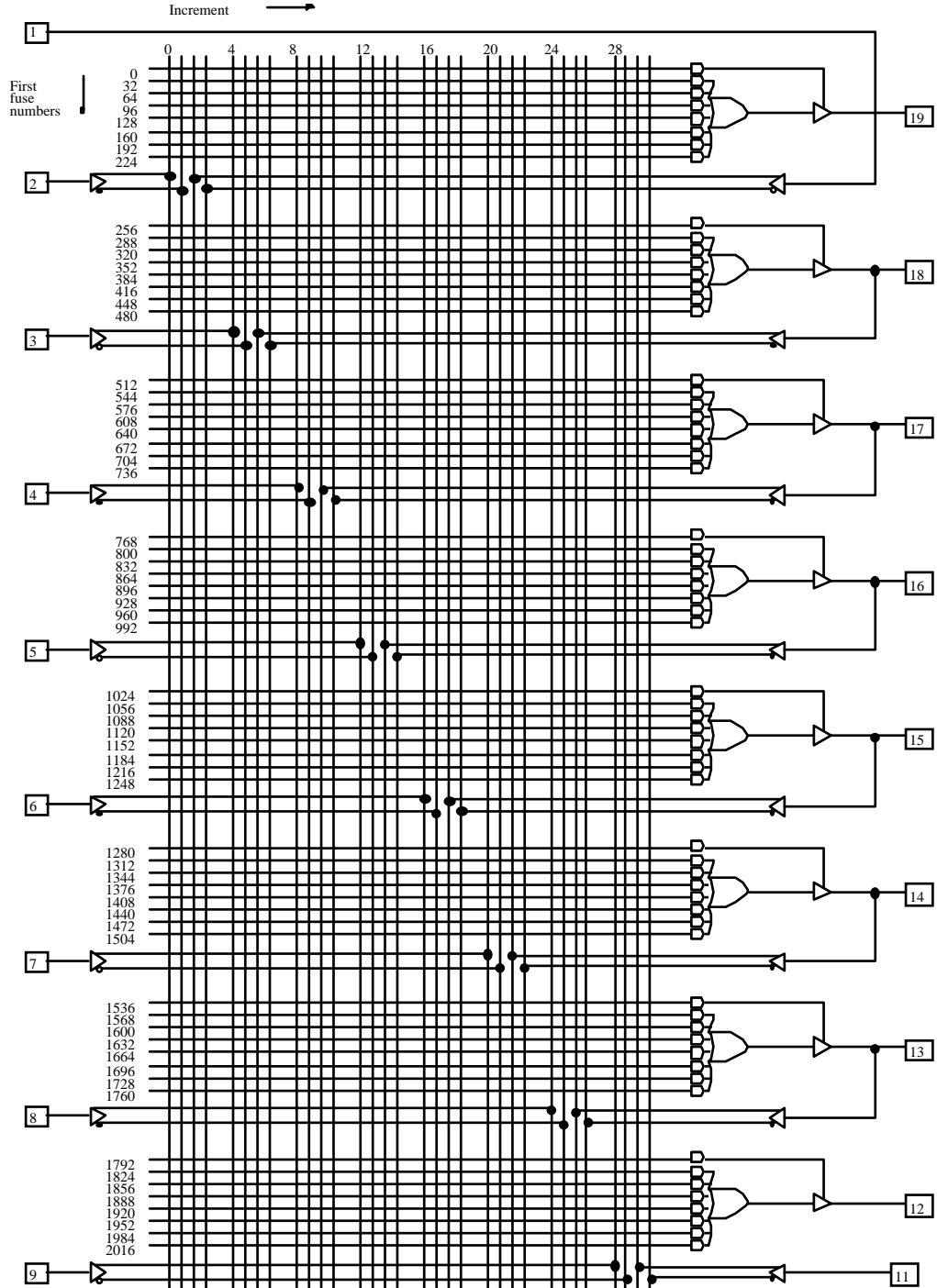


Note: Fuse number = first fuse number + increment

7-Segment Display Decoder (cont'd)

14H8PAL
(14 inputs, 8 outputs, but only two 4-input product terms can be computed.)

Cannot Implement the function

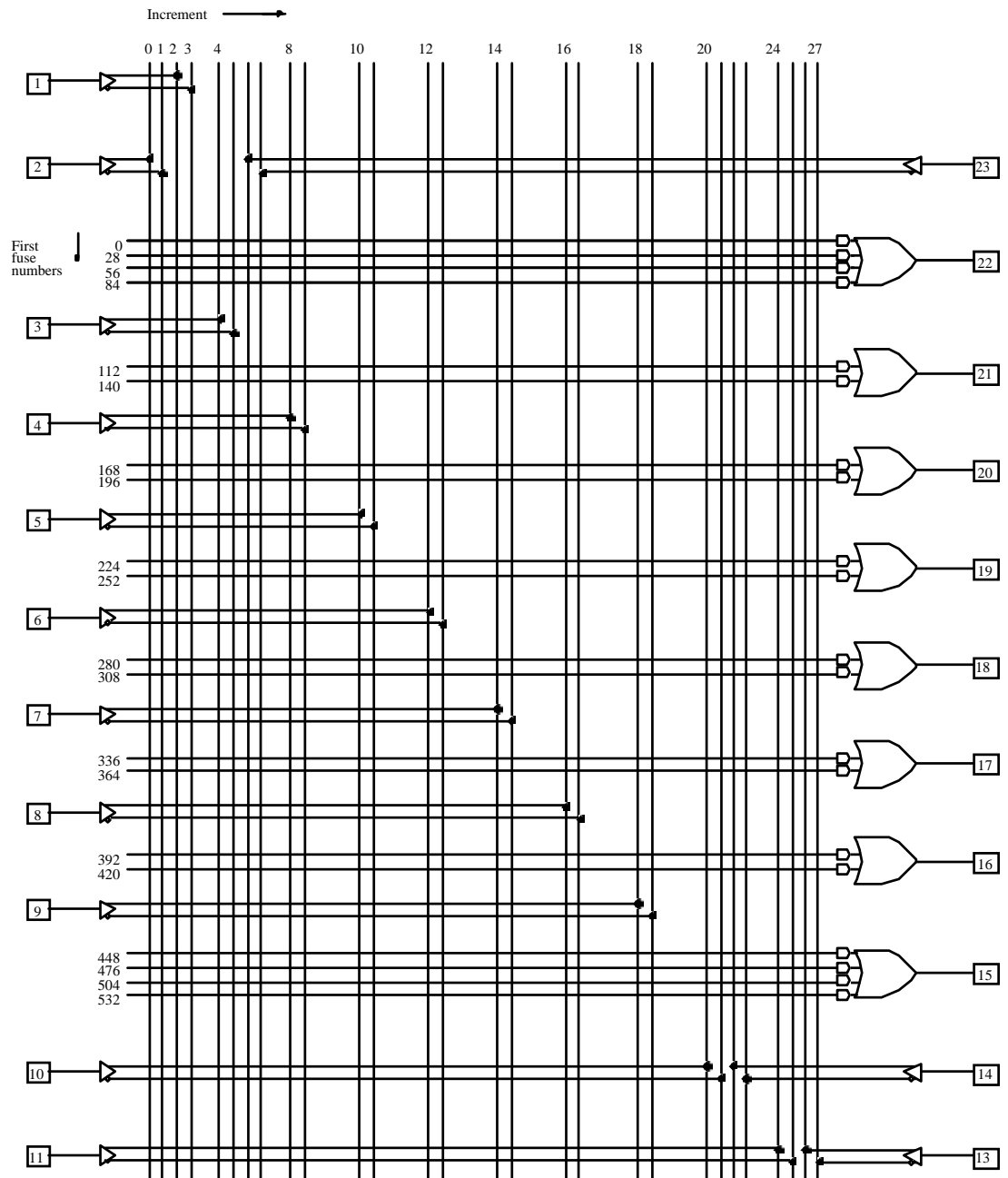

7-Segment Display Decoder (cont'd)

**CAD (espresso)
input**

```
.i 4
.o 7
.ilb a b c d
.ob c0 c1 c2 c3 c4 c5 c6
.p 16
0000 1111110
0001 0110000
0010 1101101
0011 1111001
0100 0110011
0101 1011011
0110 1011111
0111 1110000
1000 1111111
1001 1110011
1010 -----
1011 -----
1100 -----
1101 -----
1110 -----
1111 -----
.e
```

**CAD (espresso)
output**

```
.i 4
.o 7
.ilb a b c d
.ob c0 c1 c2 c3 c4 c5 c6
.p 9
-10- 0000001
-01- 0001001
-0-1 0110000
-101 1011010
--00 0110010
--11 1110000
-0-0 1101100
1--- 1000011
-110 1011111
.e
```


$$\begin{aligned}
 C0 &= B C' D + C D + B' D' + B C D' + A \\
 C1 &= B' D + C' D' + C D + B' D' \\
 C2 &= B' D + B C' D + C' D' + C D + B C D' \\
 C3 &= B C' D + B' D + B' D' + B C D' \\
 C4 &= B' D' + B C D' \\
 C5 &= B C' D + C' D' + A + B C D' \\
 C6 &= B' C + B C' + B C D' + A
 \end{aligned}$$

**63 Literals, 20 Gates
9 Unique Product Terms!**

***The results are more complex
than those of manual method.
However, #unique product terms
has been reduced 15->9***

7-Segment Display Decoder (cont'd)

- PLA Implementation

 

7-Segment Display Decoder (cont'd)

- Multilevel Implementation

$$X = C' + D'$$

$$Y = B' C'$$

$$C0 = C3 + A' B X' + A D Y$$

$$C1 = Y + A' C5' + C' D' C6$$

$$C2 = C5 + A' B' D + A' C D$$

$$C3 = C4 + B D C5 + A' B' X'$$

$$C4 = D' Y + A' C D'$$

$$C5 = C' C4 + A Y + A' B X$$

$$C6 = A C4 + C C5 + C4' C5 + A' B' C$$

52 literals


33 gates

Ineffective use of don't cares

Non-Gate Logic

- Tri-State Outputs

- The Third State
 - Logic States: "0", "1"
 - Don't Care/Don't Know State: "X" (must be some value in real circuit!)
 - Third State: "Z": high impedance: infinite resistance, no connection
- Tri-state gates:
 - output values are "0", "1", and "Z"
 - additional input: output enable (OE)
 - When OE is high, this gate is a non-inverting "buffer"
 - When OE is low, it is as though the gate was disconnected from the output!
 - This allows more than one gate to be connected to the same output wire, as long as only one has its output enabled at the same time

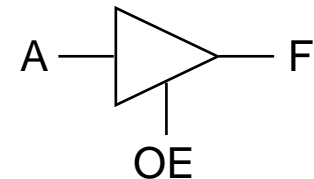


Tri-State Outputs (cont'd)


- Tri-state gates (cont'd)

- Truth table

A	OE	F
X	0	Z
0	1	0
1	1	1

 


- Non-inverting buffer's timing waveform

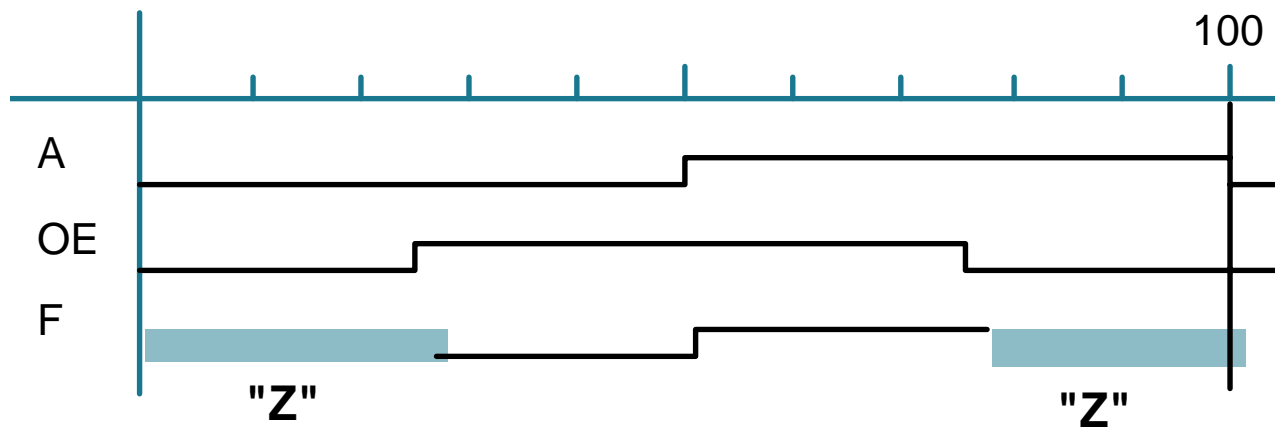


Tri-State Outputs (cont'd)

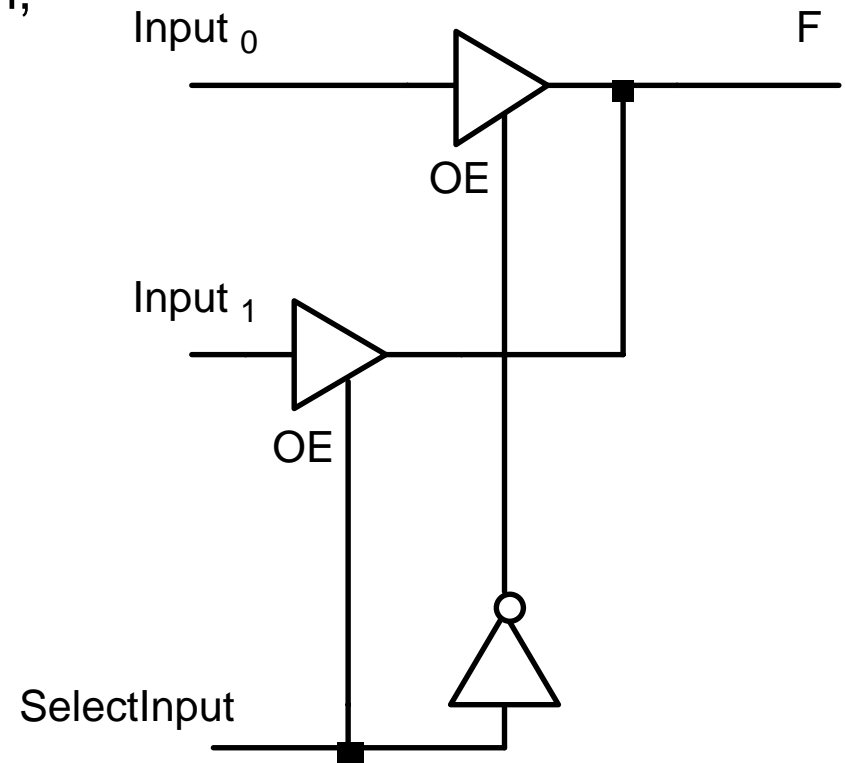- Using tri-state gates to implement an economical multiplexer:
 - When SelectInput is asserted high, Input1 is connected to F
 - When SelectInput is driven low, Input0 is connected to F
 - This is essentially a 2:1 Mux




Tri-State Outputs (cont'd)

- Alternative Tri-state Fragment

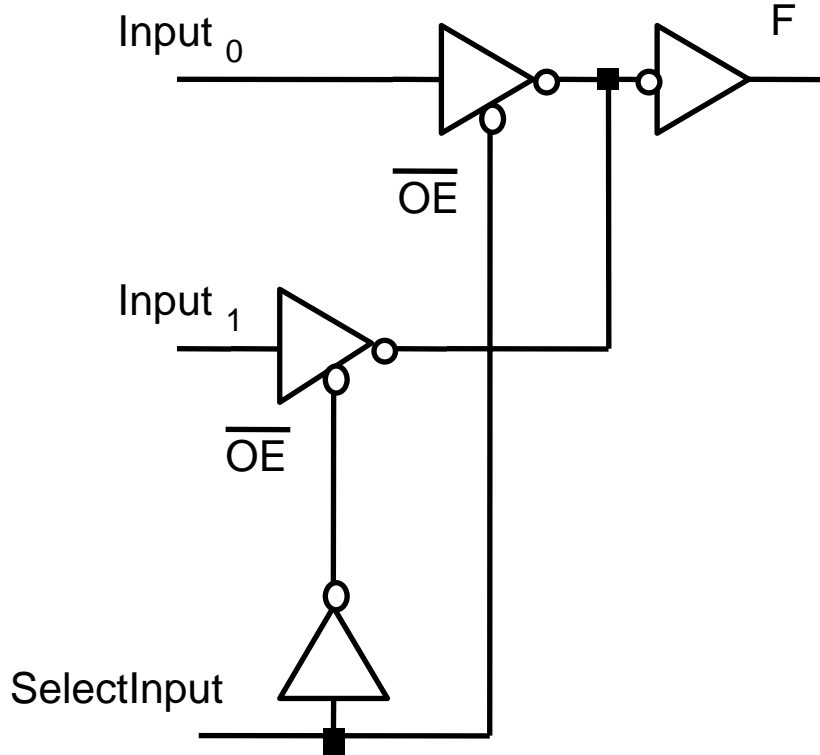


Active low tri-state enables plus inverting tri-state buffers

 - Switch Level Implementation of tri-state gate



Tri-State Outputs (cont'd)


- 4:1 Multiplexer, Revisited

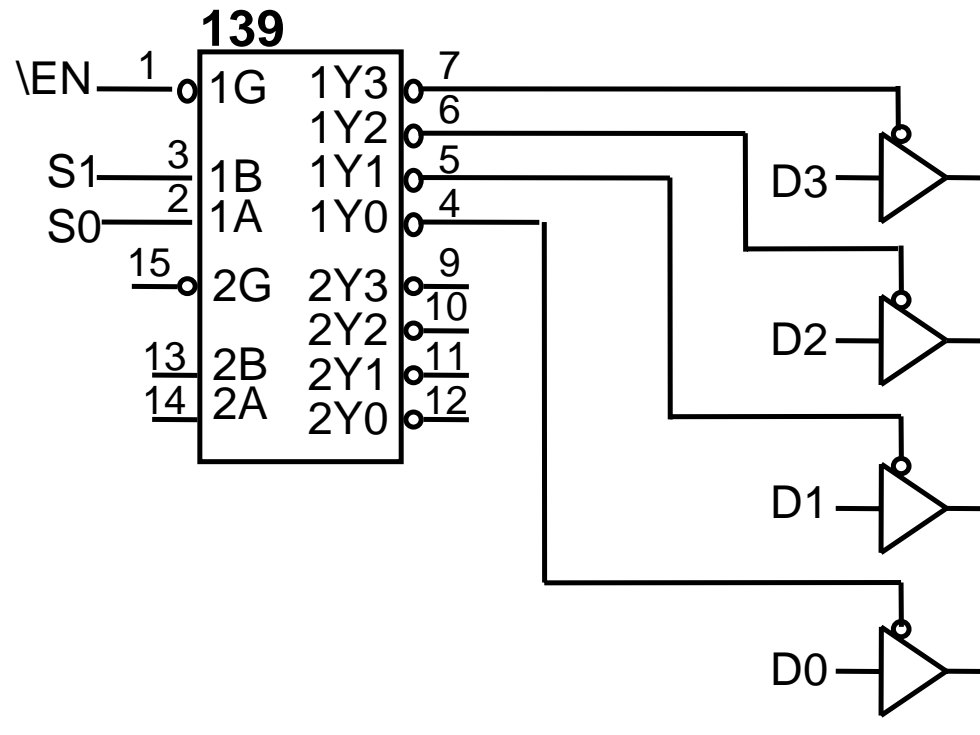

Decoder + 4 tri-state Gates

Tri-State Outputs (cont'd)

- Output Enable Signal of ROM

 


Non-Gate Logic (cont'd)

- Open-Collector Logic

■ Open Collector

- another way to connect multiple gates to the same output wire
- The gate only has the ability to pull its output low; it cannot actively drive the wire high
- this is done by pulling the wire up to a logic 1 voltage through a resistor

■ Switch representation of an OC NAND

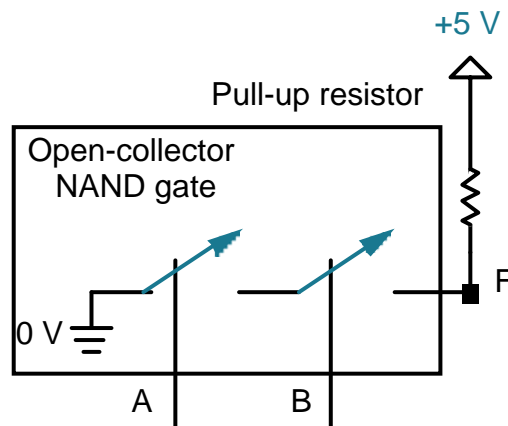


- When A=1 and B=1, equivalent circuit of OC-NAND:

$$(R_A + R_B) \cdot 0.5V$$

Open-Collector Logic (cont'd)

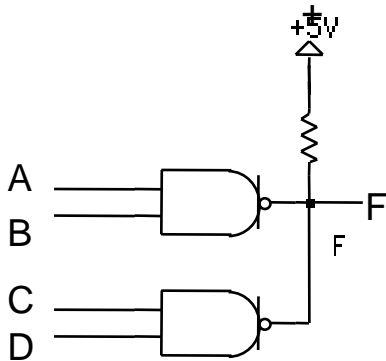
- Example: OC-NANDs in wired-AND configuration



- If A and B are "1", output is actively pulled low
- If C and D are "1", output is actively pulled low
- If one gate is low, the other high, then low wins
- If both gates are "1", the output floats, pulled high by resistor
- Hence, the two NAND functions are AND'd together!

Open-Collector Logic (cont'd)

- 4:1 Multiplexer

 

Decoder + 4 Open Collector Gates

Summary

- Theme:
 - How to construct digital systems with more complex logic building blocks than discrete gates
- Overview of the different classes of basic components:
 - Fixed logic
 - Look-up table based logic (ROM)
 - Steering logic (Mux, Demux)
 - PLA, PAL
 - FPGA
- Non-gate logic
 - Enables efficient multiplexing of large numbers of signals
 - Tristate
 - Open-collector